

# Gates and Logic

Hakim Weatherspoon


CS 3410, Spring 2012

Computer Science

Cornell University

See: P&H Appendix C.2 and C.3 (Also, see C.0 and C.1)

# A switch

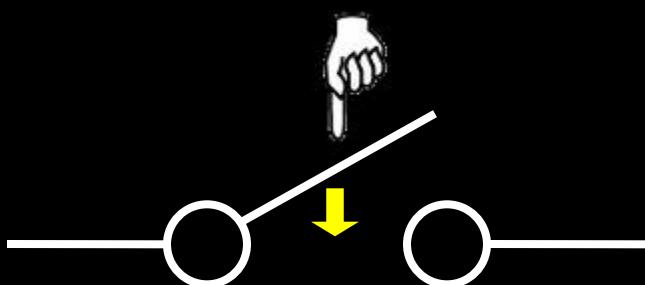

- Acts as a *conductor* or *insulator*
- Can be used to build amazing things...



# Goals for today


---

To understand how to program,  
we will build a processor (i.e. a logic circuit)

## Logic circuits

- Use P- and N-transistors to implement NAND or NOR gates
- Use NAND or NOR gates to implement the logic circuits
- Build efficient logic circuits


# Better Switch

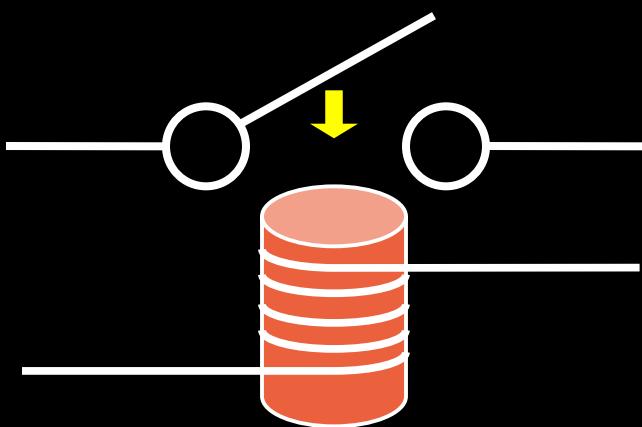

- One current controls another (larger) current
- Static Power:
  - Keeps consuming power when in the *ON* state
- Dynamic Power:
  - Jump in power consumption when switching


# Atoms

---

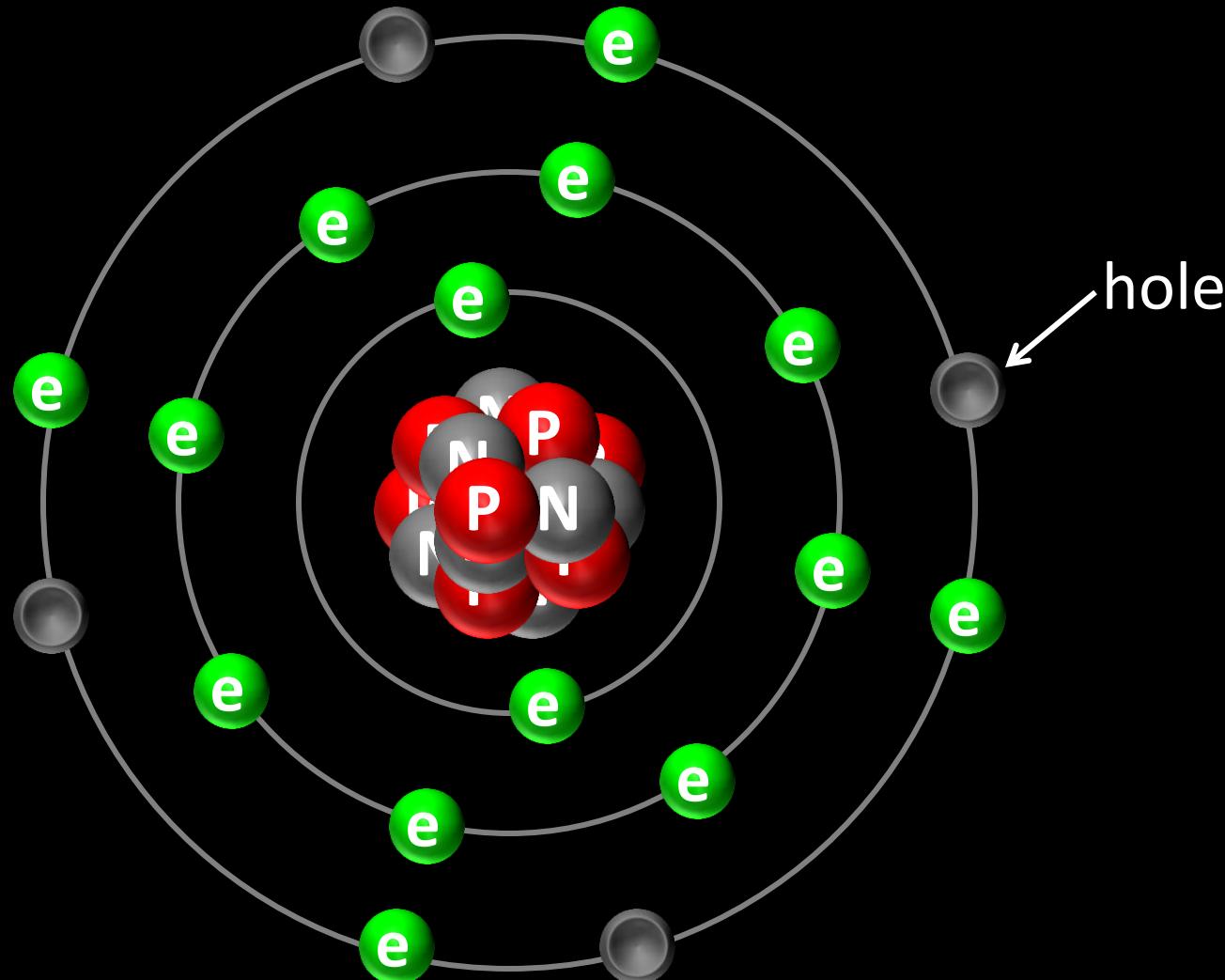

# Elements


---

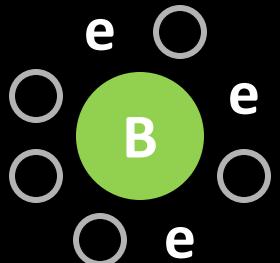

Boron




Silicon

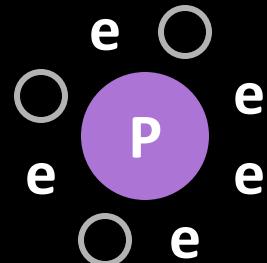

Phosphorus


# Silicon Crystal

## Silicon

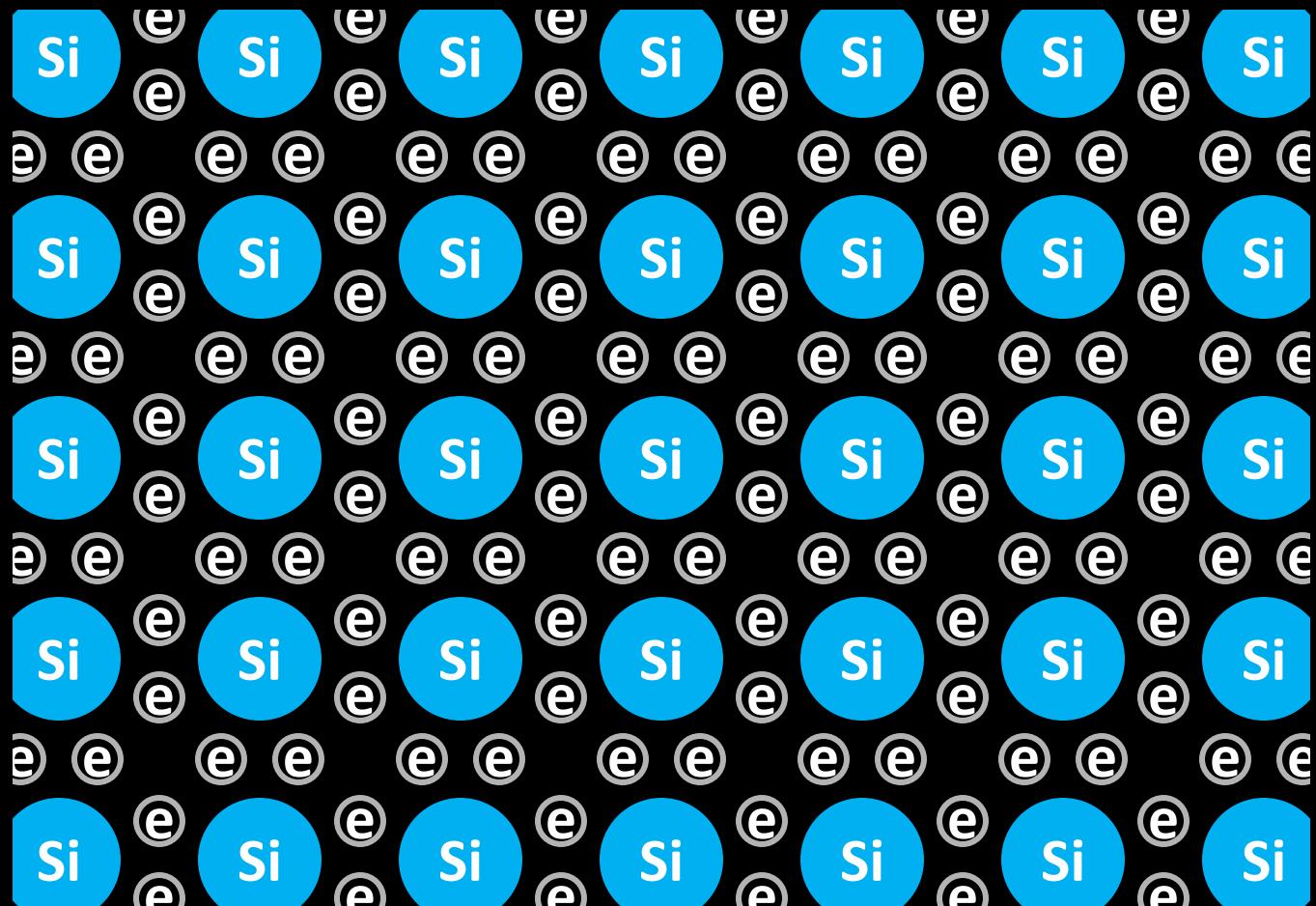


# Phosphorus Doping

## N-Type: Silicon + Phosphorus

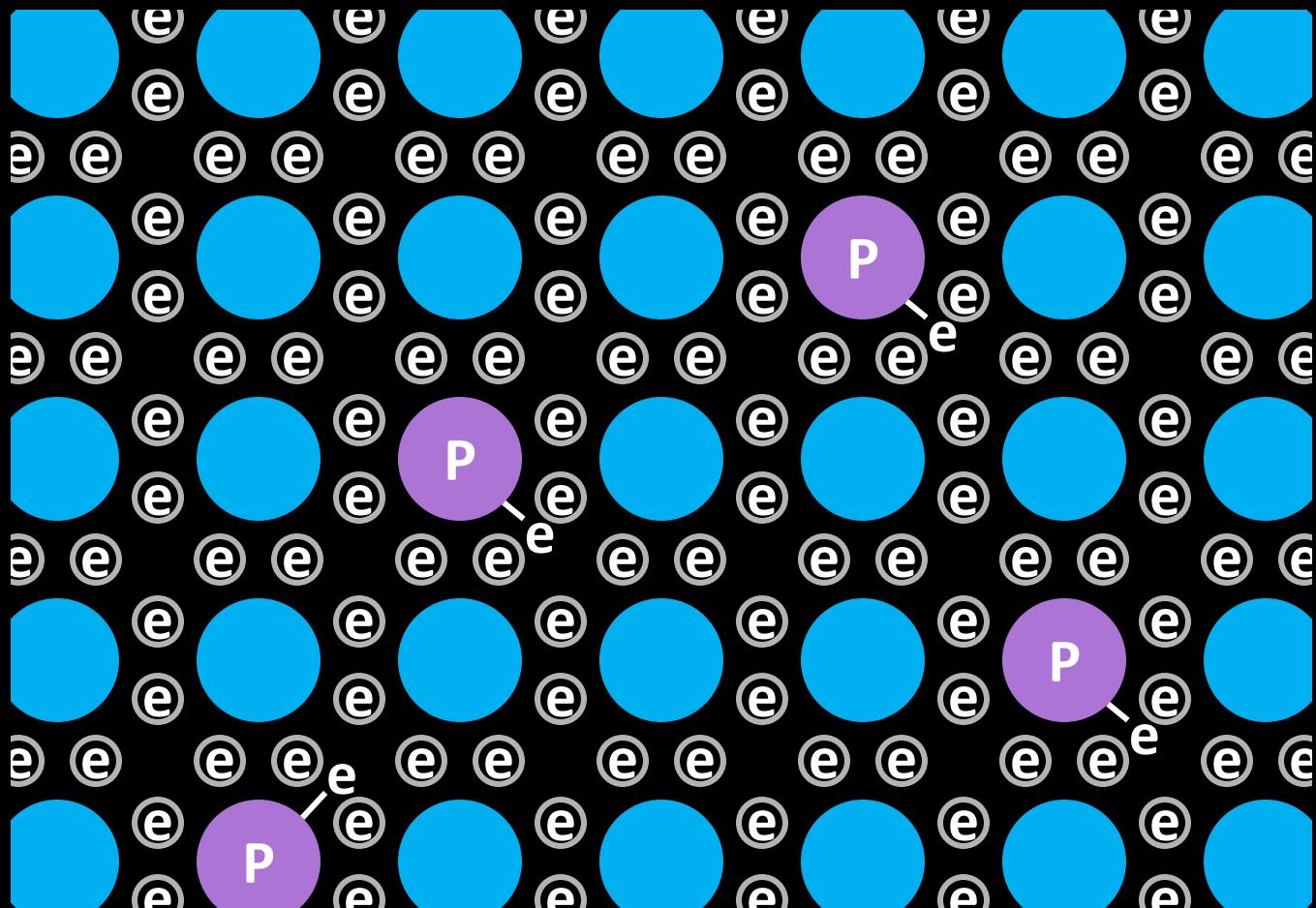


# Boron Doping

## P-Type: Silicon + Boron

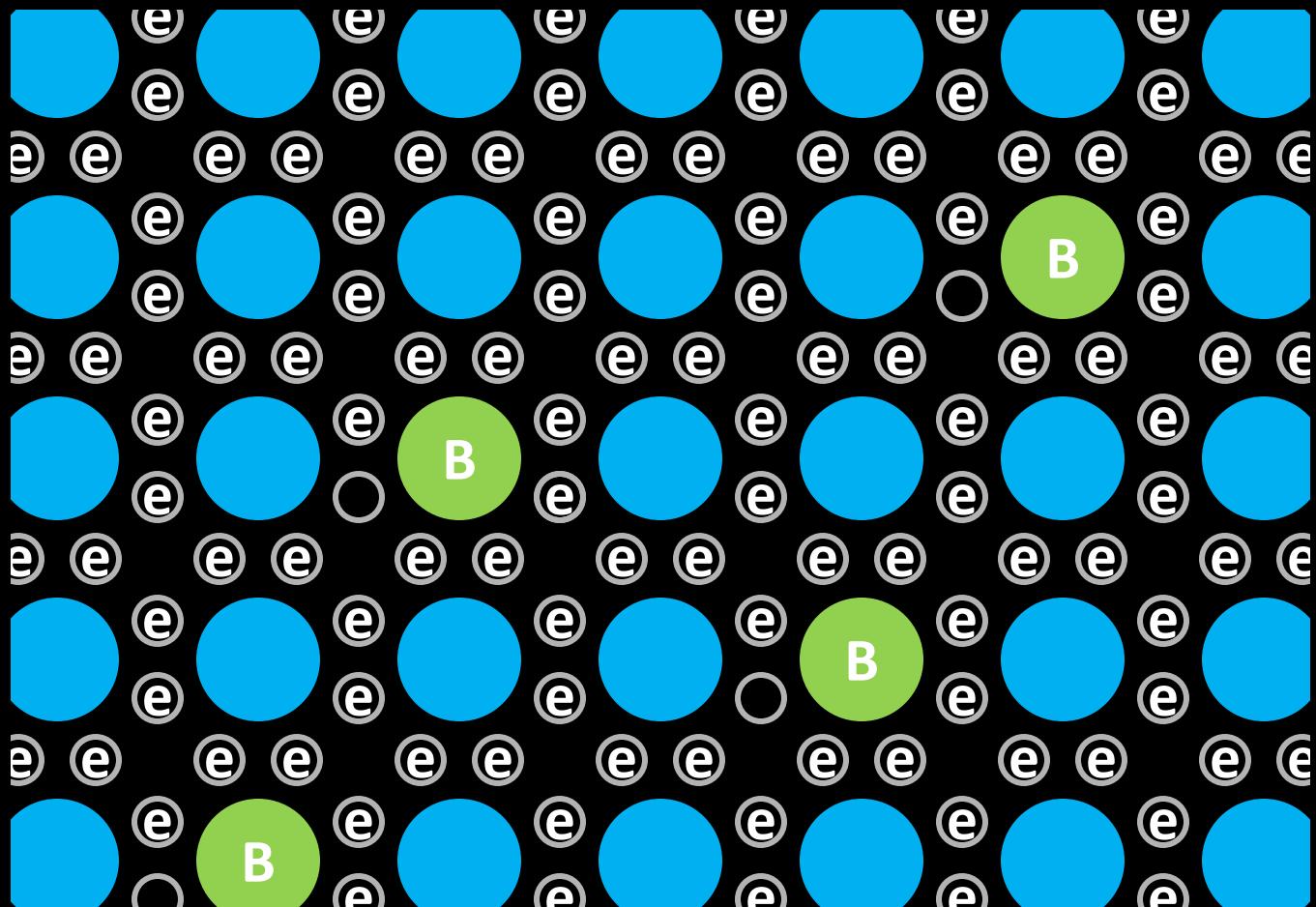

# Semiconductors

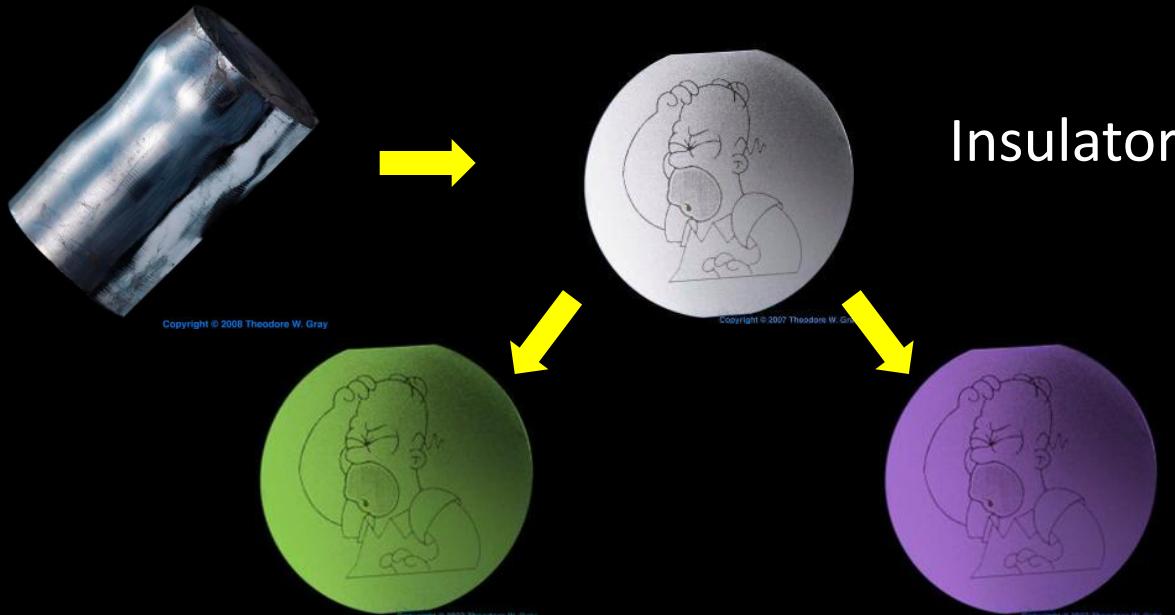

**p-type (Si+Boron)**  
has mobile holes:

low voltage (depleted)  
→ insulator


high voltage (mobile holes)  
→ conductor

**n-type (Si+Phosphorus)**  
has mobile electrons:

low voltage (mobile electrons)  
→ conductor

high voltage (depleted)  
→ insulator

# Bipolar Junction

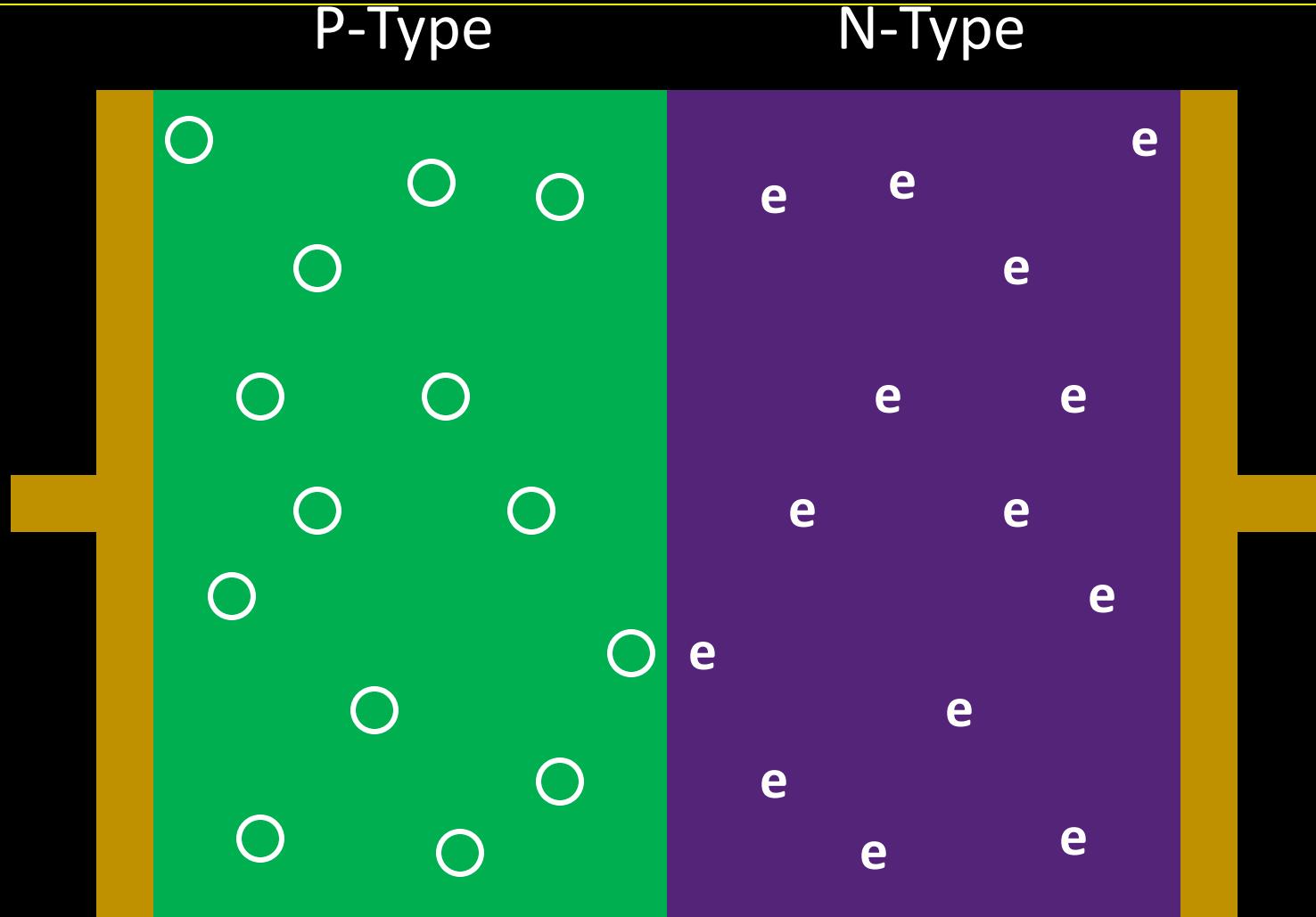


low  $v \rightarrow$  insulator

high  $v \rightarrow$  conductor


low  $v \rightarrow$  conductor

high  $v \rightarrow$  insulator

# Reverse Bias


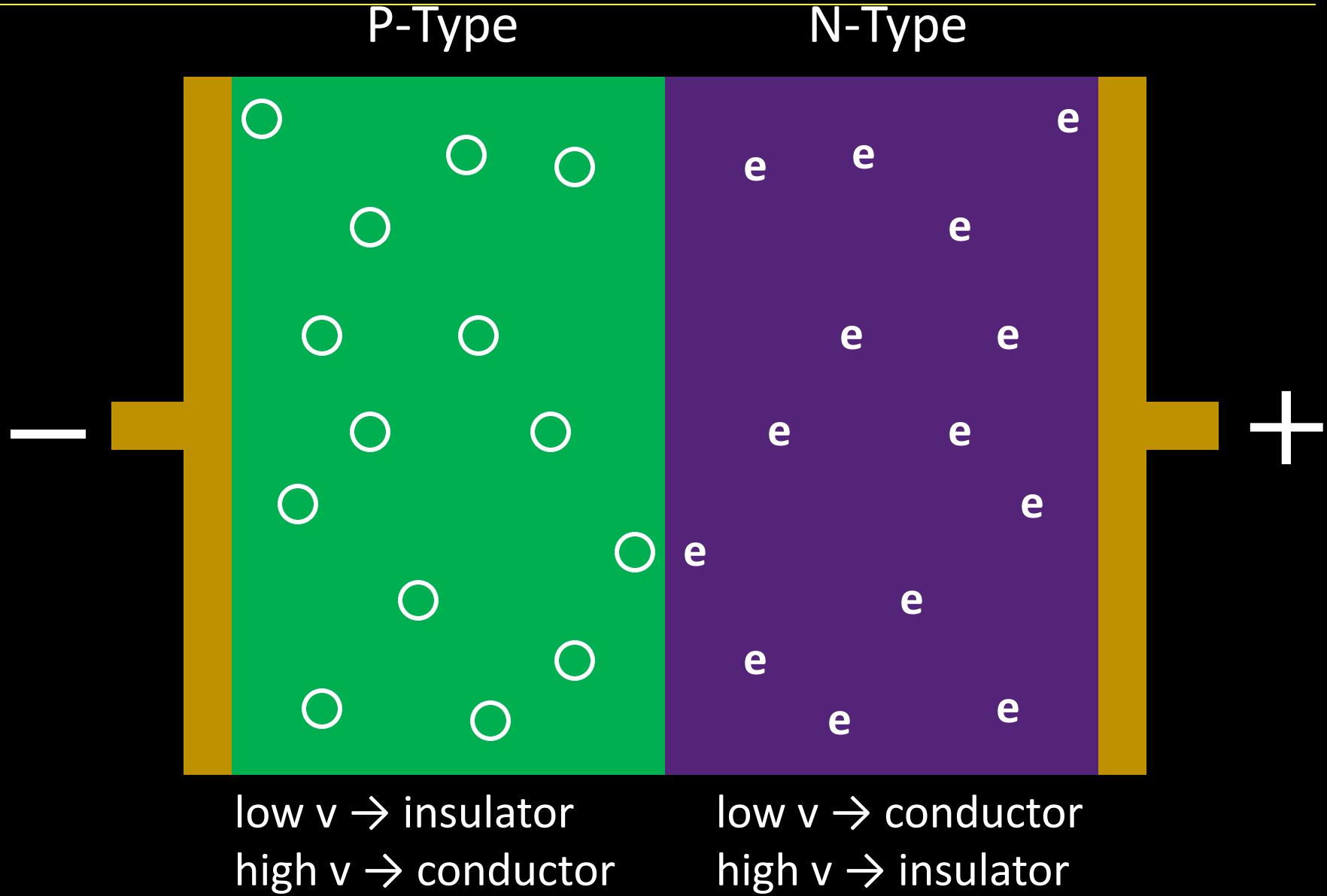


# Forward Bias

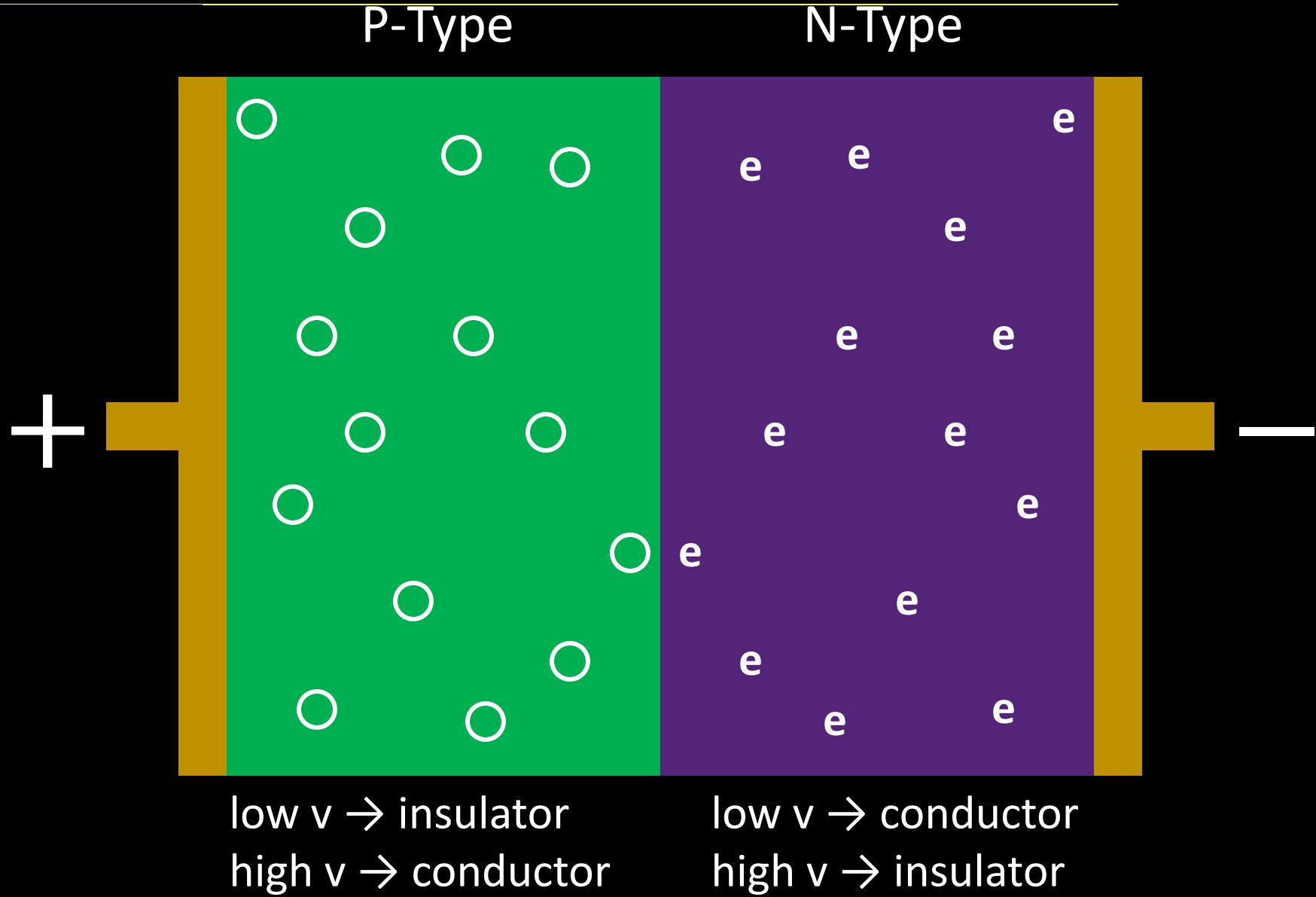

# Diodes

PN Junction “Diode”

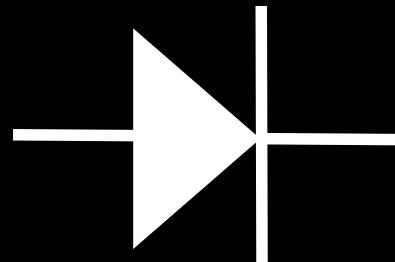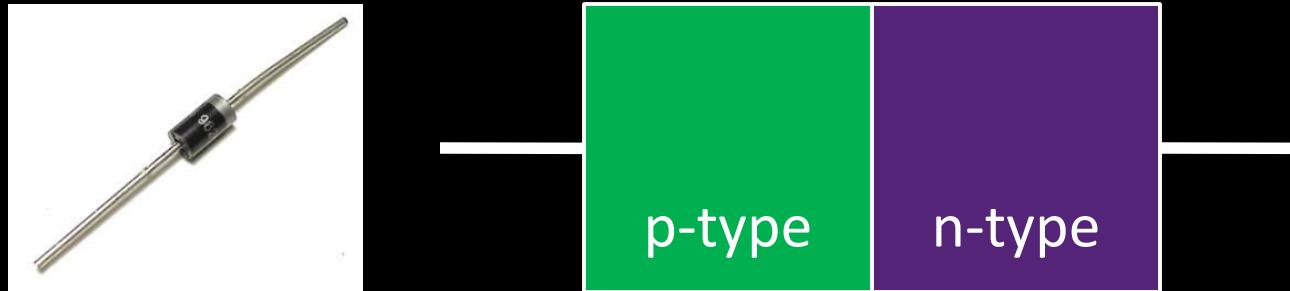


Conventions:

$v_{dd} = v_{cc} = +1.2v = +5v = hi$


$v_{ss} = v_{ee} = 0v = gnd$

# PNP Junction

---


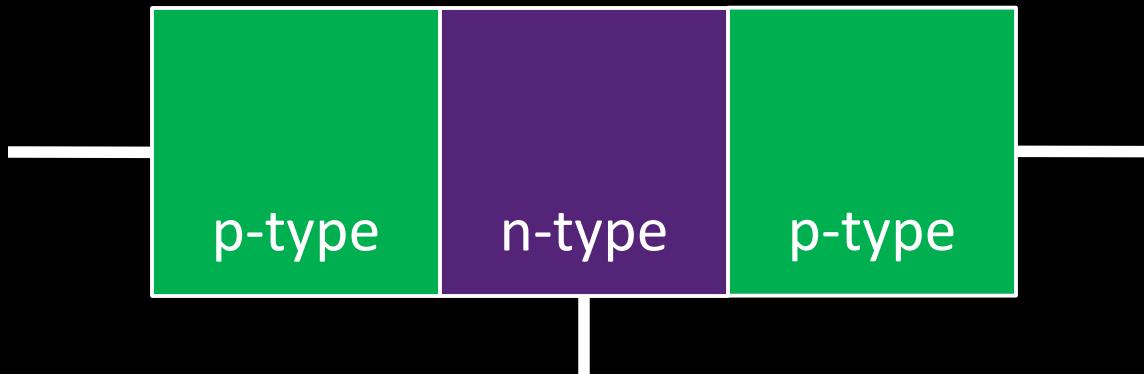


# Bipolar Junction Transistors


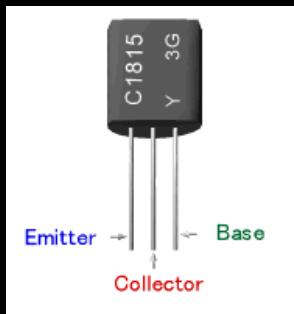


- Solid-state switch: The most amazing invention of the 1900s  
Emitter = “input”, Base = “switch”, Collector = “output”

PNP Transistor

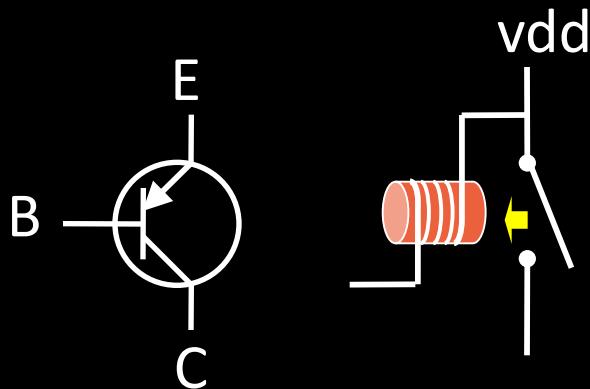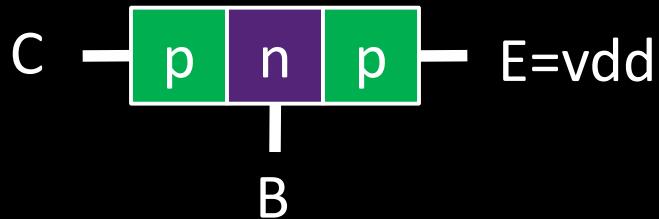


NPN Transistor

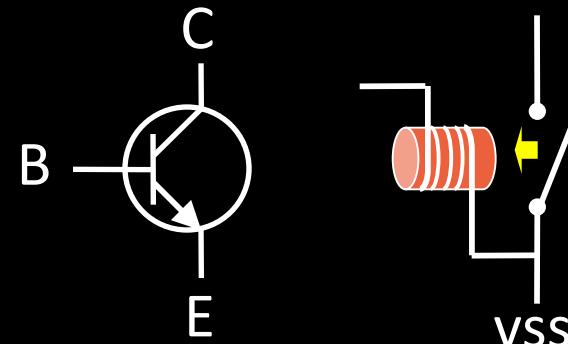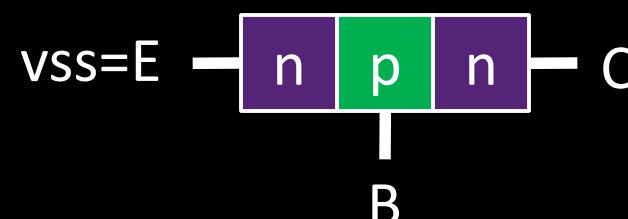


# Field Effect Transistors

## P-type FET

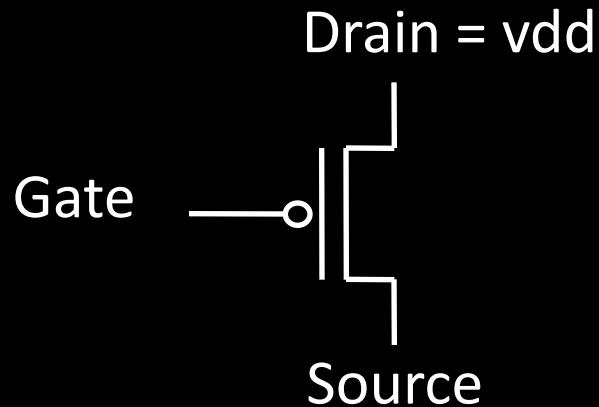



## N-type FET

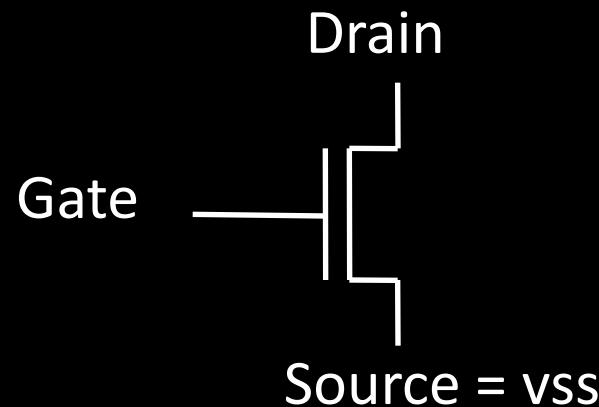

- Connect Source to Drain when Gate = lo
- Drain must be vdd, or connected to source of another P-type transistor

- Connect Source to Drain when Gate = hi
- Source must be vss, or connected to drain of another N-type transistor

# Multiple Transistors

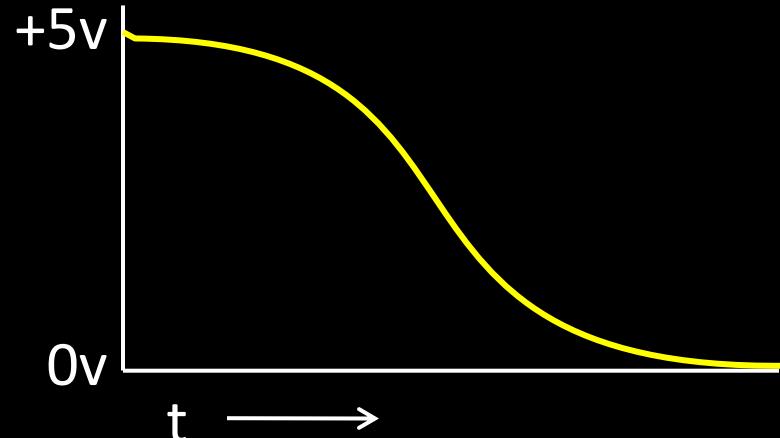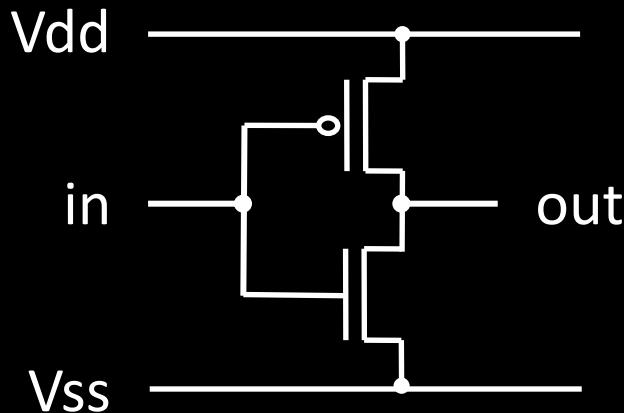

In	Out

voltage

## Gate delay



- transistor switching time
- voltage, propagation, fanout, temperature, ...

## CMOS design

(complementary-symmetry metal–oxide–semiconductor)

- Power consumption = dynamic + leakage

# Digital Logic

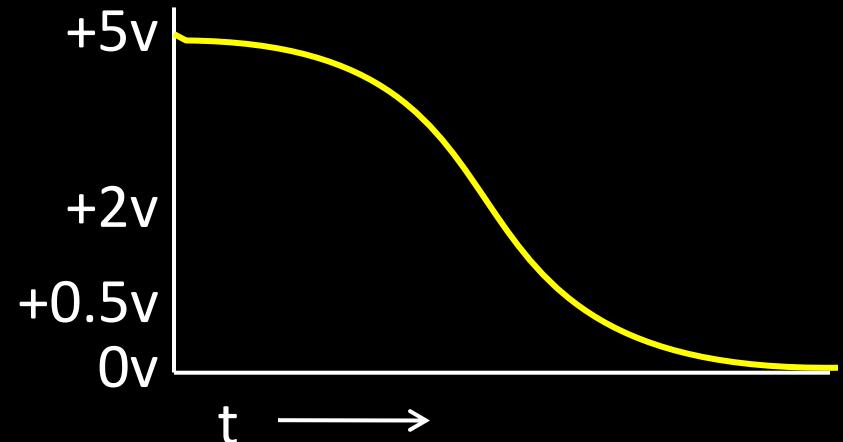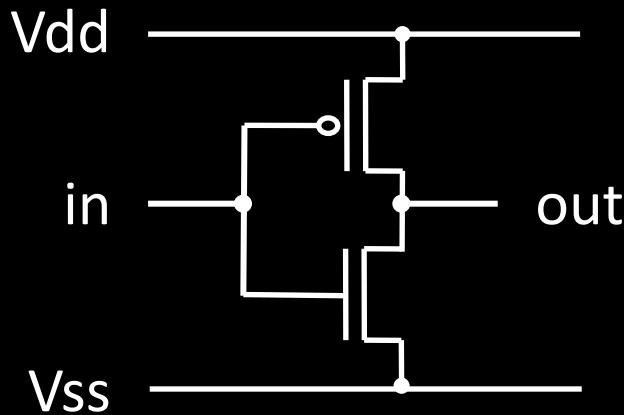

In	Out
+5v	0v
0v	+5v

voltage

In	Out


truth table

Conventions:

**vdd = vcc = +1.2v = +5v = hi = true = 1**


**vss = vee = 0v = gnd = false = 0**

# NOT Gate (Inverter)

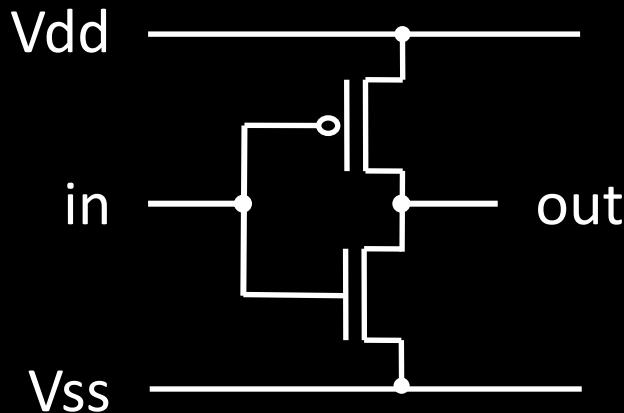

Function: NOT


- Symbol:

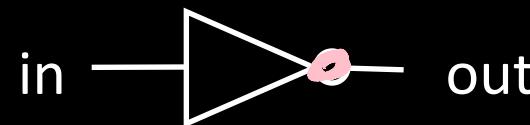

In	Out
0	1
1	0


Truth table

# NAND Gate

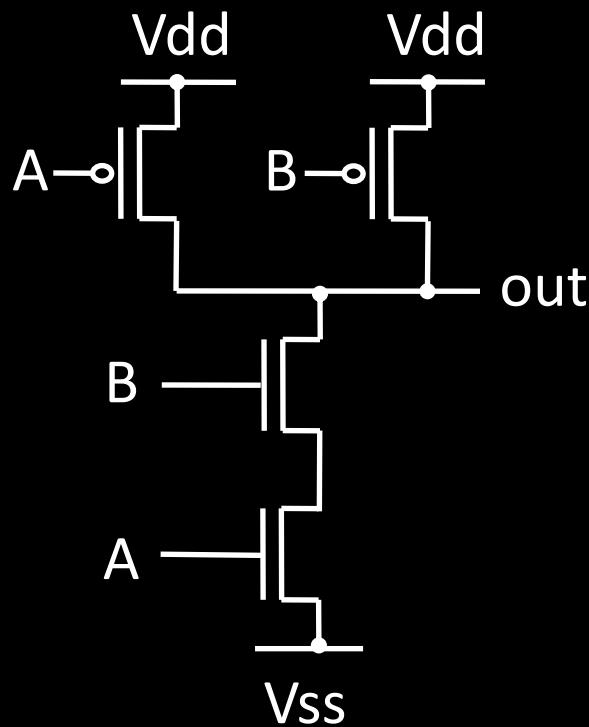


Function: NAND

- Symbol:

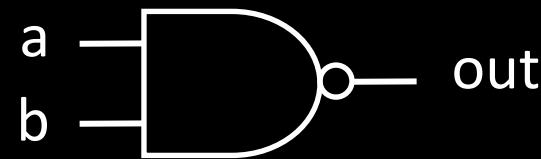


A	B	out
0	0	1
0	1	1
1	0	1
1	1	0

# NOR Gate

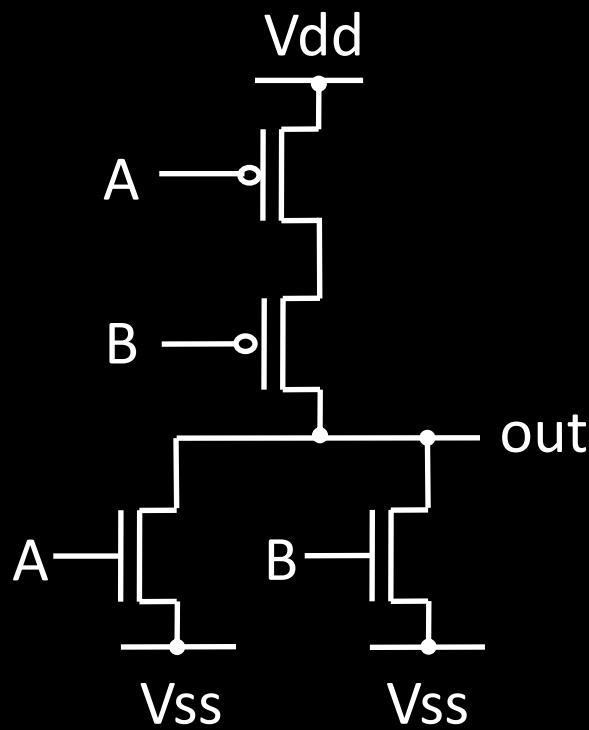

Function: NOR

- Symbol:

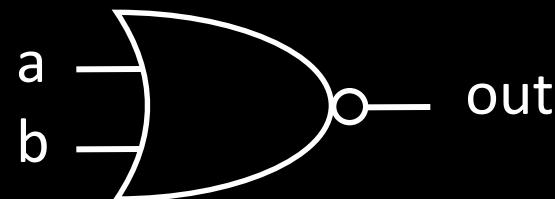


A	B	out
0	0	1
0	1	0
1	0	0
1	1	0


# Building Functions

---


- AND:

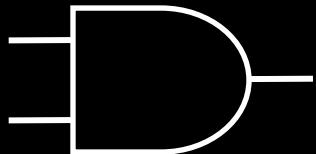

- OR:

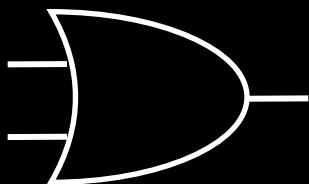

- NOT:

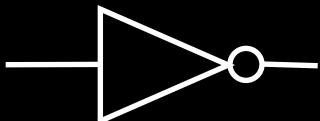


# Universal Gates

---

NAND is universal (so is NOR)

- Can implement any function with just NAND gates
  - De Morgan's laws are helpful (pushing bubbles)
- useful for manufacturing

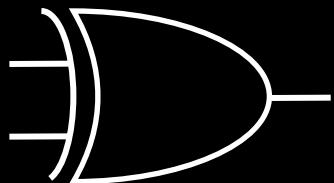E.g.: XOR ( $A, B$ ) =  $A$  or  $B$  but not both ("exclusive or")



Proof: ?

# Administrivia

---

Make sure you have access to CMS and Piazza.com

## Lab Sections started ***this*** week

- Lab0 turned in during Section
- Bring laptop to section, if possible (not required)
- Lab1 available Monday next week (due following Monday)
- Group projects start in week 4 (partner in same section)

## Homework1 available Monday

- Due following Monday

## Office hours start next week

- More information available on website by this weekend

## Clickers not required, bring to every lecture

- Participation, not attendance

# Logic Equations

---

Some notation:

- constants: true = 1, false = 0
- variables: a, b, out, ...
- operators:
  - $\text{AND}(a, b) = a \cdot b = a \& b = a \wedge b$
  - $\text{OR}(a, b) = a + b = a | b = a \vee b$
  - $\text{NOT}(a) = \bar{a} = !a = \neg a$

# Identities

---

Identities useful for manipulating logic equations

- For optimization & ease of implementation

$$a + 0 = a$$

$$a + 1 = 1$$

$$a + \bar{a} = 1$$

$$a \cdot 0 = 0$$

$$a \cdot 1 = a$$

$$a \cdot \bar{a} = 0$$

$$\overline{(a + b)} = \bar{a} \bar{b}$$

$$\overline{(a \cdot b)} = \bar{a} + \bar{b}$$

$$a + a \cdot b = a$$

$$a(b+c) = ab + ac$$

$$\overline{a(b+c)} = \bar{a} + \bar{b}\bar{c}$$

# Logic Manipulation

---

- functions: gates  $\leftrightarrow$  truth tables  $\leftrightarrow$  equations
- Example:

a	b	c					
0	0	0					
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					



# Logic Minimization

---

- A common problem is how to implement a desired function most efficiently
- One can derive the equation from the truth table

a	b	c	minterm
0	0	0	$\overline{abc}$
0	0	1	$\overline{ab}\overline{c}$
0	1	0	$\overline{a}\overline{b}\overline{c}$
0	1	1	$\overline{a}\overline{b}c$
1	0	0	$a\overline{b}\overline{c}$
1	0	1	$a\overline{b}c$
1	1	0	$a\overline{b}\overline{c}$
1	1	1	$abc$

for all outputs  
that are 1,  
take the corresponding  
minterm  
Obtain the result in  
“sum of products” form

- How does one find the most efficient equation?
  - Manipulate algebraically until satisfied
  - Use Karnaugh maps (or K maps)


# Karnaugh maps

---

- Encoding of the truth table where adjacent cells differ in only one bit

a	b	out
0	0	0
0	1	0
1	0	0
1	1	1





truth table  
for AND

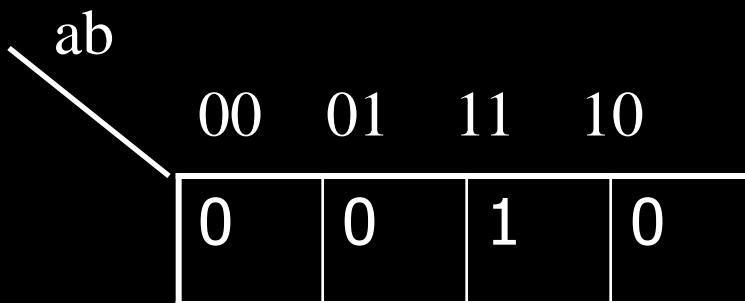

Corresponding  
Karnaugh map

# Bigger Karnaugh Maps

---

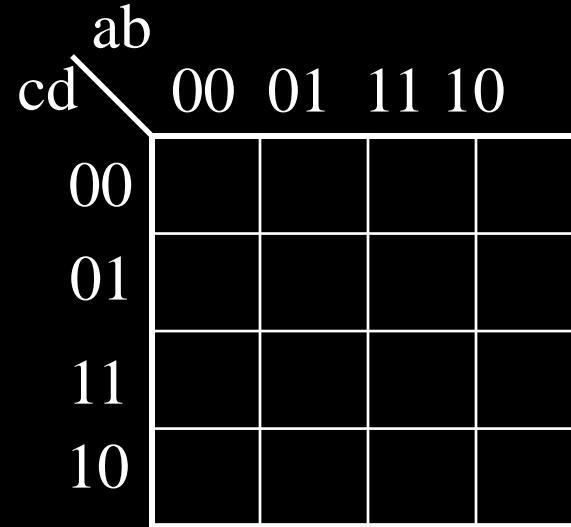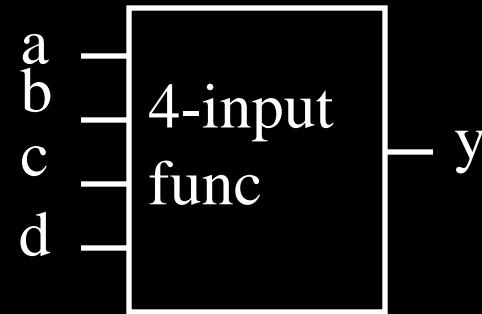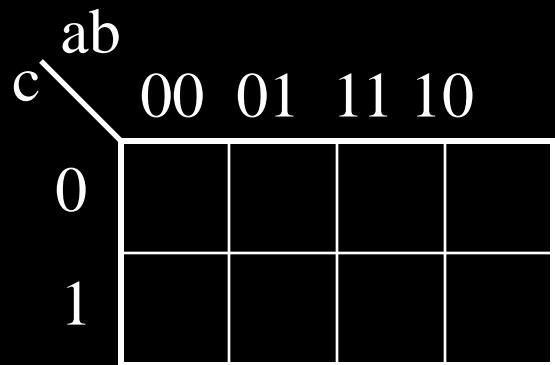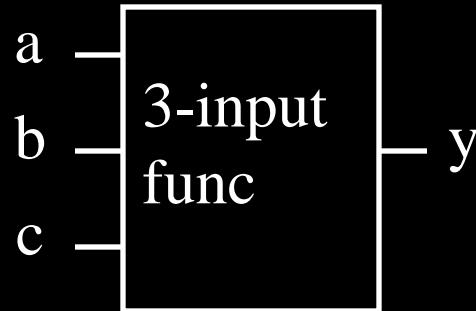

# Minimization with Karnaugh maps (1)

---

a	b	c	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

- ◆ Sum of minterms yields
  - $\bar{a}\bar{b}c + \bar{a}bc + a\bar{b}\bar{c} + ab\bar{c}$

# Minimization with Karnaugh maps (2)

a	b	c	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0


ab  
00 01 11 10

0	0	0	1
1	1	1	0

- ◆ Sum of minterms yields
  - $\bar{a}\bar{b}c + \bar{a}bc + a\bar{b}c + abc$
  
- ◆ Karnaugh maps identify which inputs are (ir)relevant to the output

# Minimization with Karnaugh maps (2)

a	b	c	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

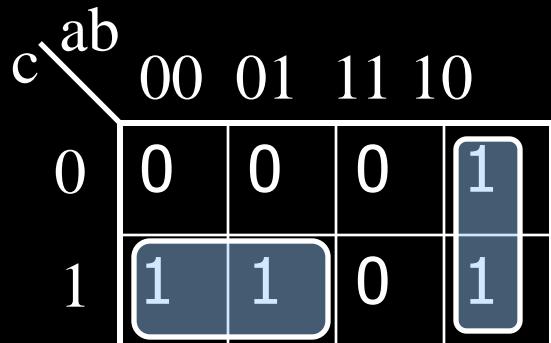

- ◆ Sum of minterms yields
  - $\bar{a}\bar{b}c + \bar{a}bc + a\bar{b}c + abc$
  
- ◆ Karnaugh map minimization
  - Cover all 1's
  - Group adjacent blocks of  $2^n$  1's that yield a rectangular shape
  - Encode the common features of the rectangle
    - ◆  $out = a\bar{b} + \bar{a}c$

# Karnaugh Minimization Tricks (1)

c \ ab	00	01	11	10
0	0	1	1	1
1	0	0	1	0

◆ Minterms can overlap

- $\text{out} = b\bar{c} + a\bar{c} + ab$

c \ ab	00	01	11	10
0	1	1	1	1
1	0	0	1	0

◆ Minterms can span 2, 4, 8 or more cells

- $\text{out} = \bar{c} + ab$

# Karnaugh Minimization Tricks (2)

cd \ ab	00	01	11	10
00	0	0	0	0
01	1	0	0	1
11	1	0	0	1
10	0	0	0	0

- The map wraps around
  - $\text{out} = \overline{bd}$

cd \ ab	00	01	11	10
00	1	0	0	1
01	0	0	0	0
11	0	0	0	0
10	1	0	0	1

- $\text{out} = \overline{bd}$

# Karnaugh Minimization Tricks (3)

cd \ ab	00	01	11	10
00	0	0	0	0
01	1	x	x	x
11	1	x	x	1
10	0	0	0	0


- “Don’t care” values can be interpreted individually in whatever way is convenient
  - assume all x’s = 1
  - out = d

cd \ ab	00	01	11	10
00	1	0	0	x
01	0	x	x	0
11	0	x	x	0
10	1	0	0	1

- assume middle x’s = 0
- assume 4<sup>th</sup> column x = 1
- out = bd

# Multiplexer


---

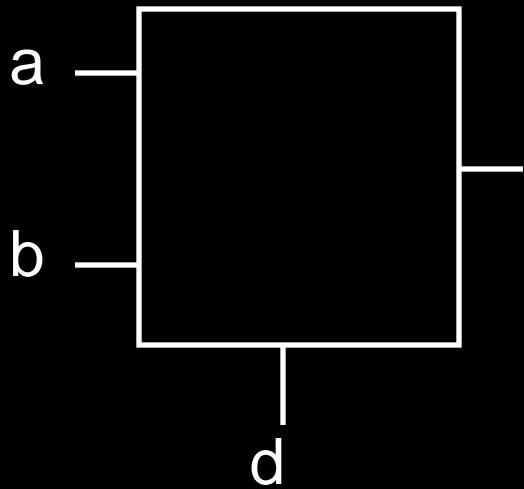

- A multiplexer selects between multiple inputs
  - $\text{out} = a$ , if  $d = 0$
  - $\text{out} = b$ , if  $d = 1$
- Build truth table
- Minimize diagram
- Derive logic diagram

# Multiplexer Implementation

---

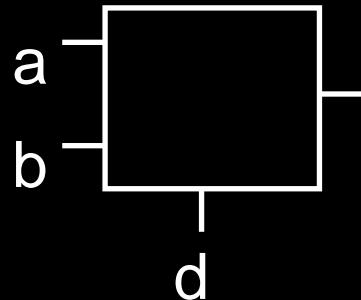


- Build a truth table  
 $= abd + ab\bar{d} + \bar{a} bd + a \bar{b} \bar{d}$

a	b	d	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1


# Multiplexer Implementation

---

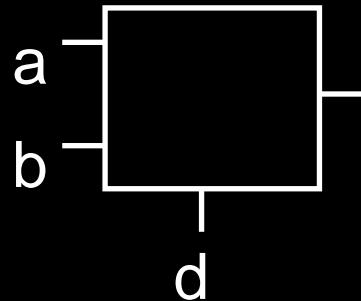


a	b	d	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

- Build the Karnaugh map

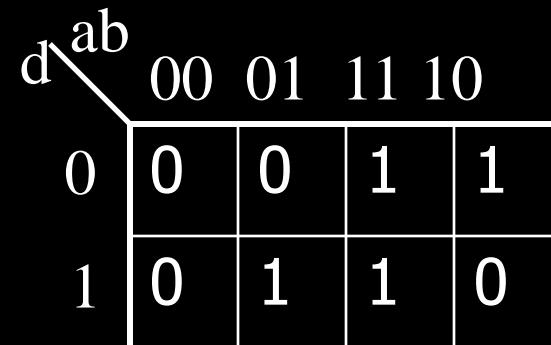


# Multiplexer Implementation

---

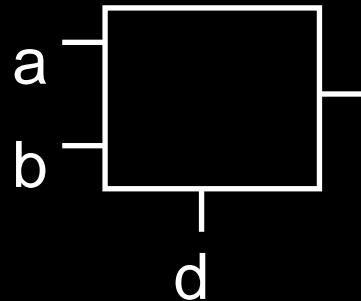

a	b	d	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1


- Derive Minimal Logic Equation

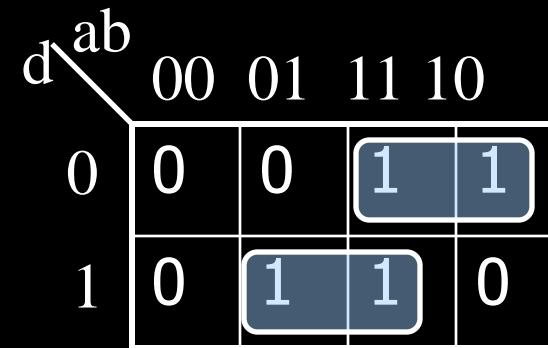

- $out = ad + bd$


# Multiplexer Implementation

---

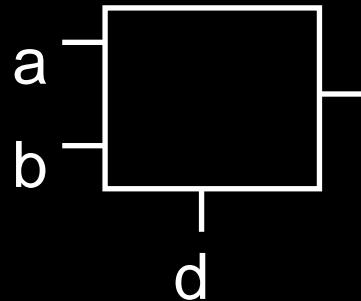

a	b	d	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

- Derive Minimal Logic Equation

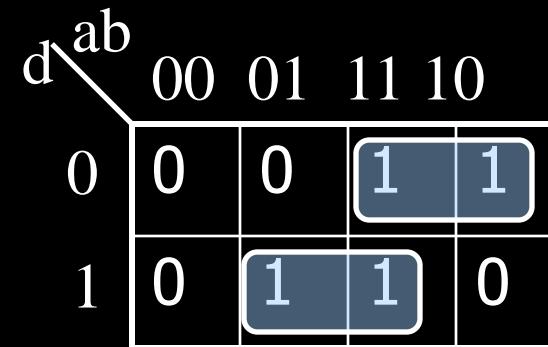

- $out = ad + bd$

# Summary

---

- We can now implement any logic circuit
  - Can do it efficiently, using Karnaugh maps to find the minimal terms required
  - Can use either NAND or NOR gates to implement the logic circuit
  - Can use P- and N-transistors to implement NAND or NOR gates