


---

# Memory

Hakim Weatherspoon  
CS 3410, Spring 2012  
Computer Science  
Cornell University

See: P&H Appendix C.8, C.9

# Big Picture: Building a Processor

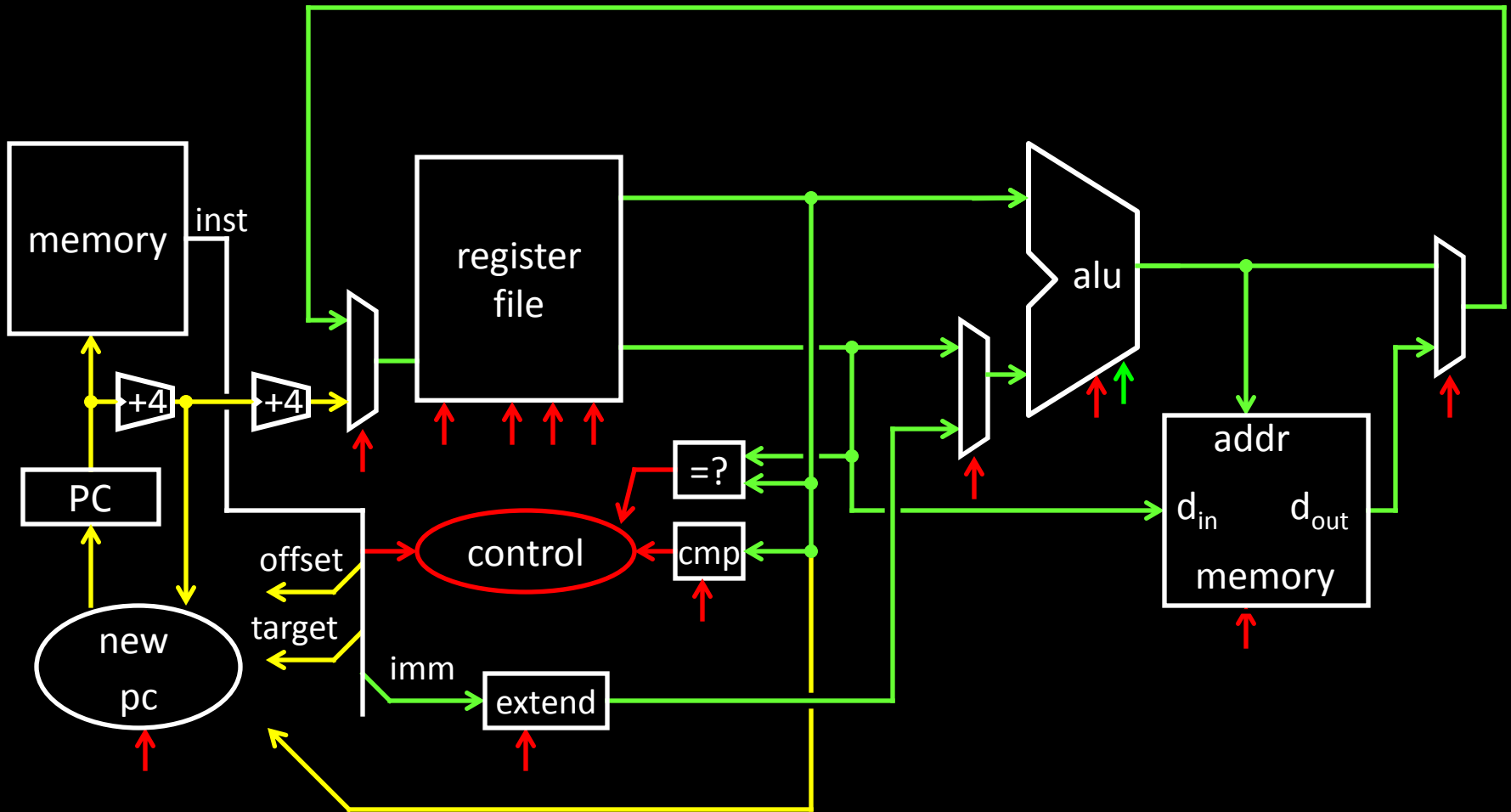

A Single cycle processor

# Goals for today

---

## Review

- Finite State Machines

## Memory

- Register Files
- Tri-state devices
- SRAM (Static RAM—random access memory)
- DRAM (Dynamic RAM)


# Which statement(s) is true

---

- (A) In a Moore Machine output depends on both current state and input
- (B) In a Mealy Machine output depends on current state and input
- (C) In a Mealy Machine output depends on next state and input
- (D) All the above are true
- (E) None are true

# Mealy Machine


## General Case: Mealy Machine

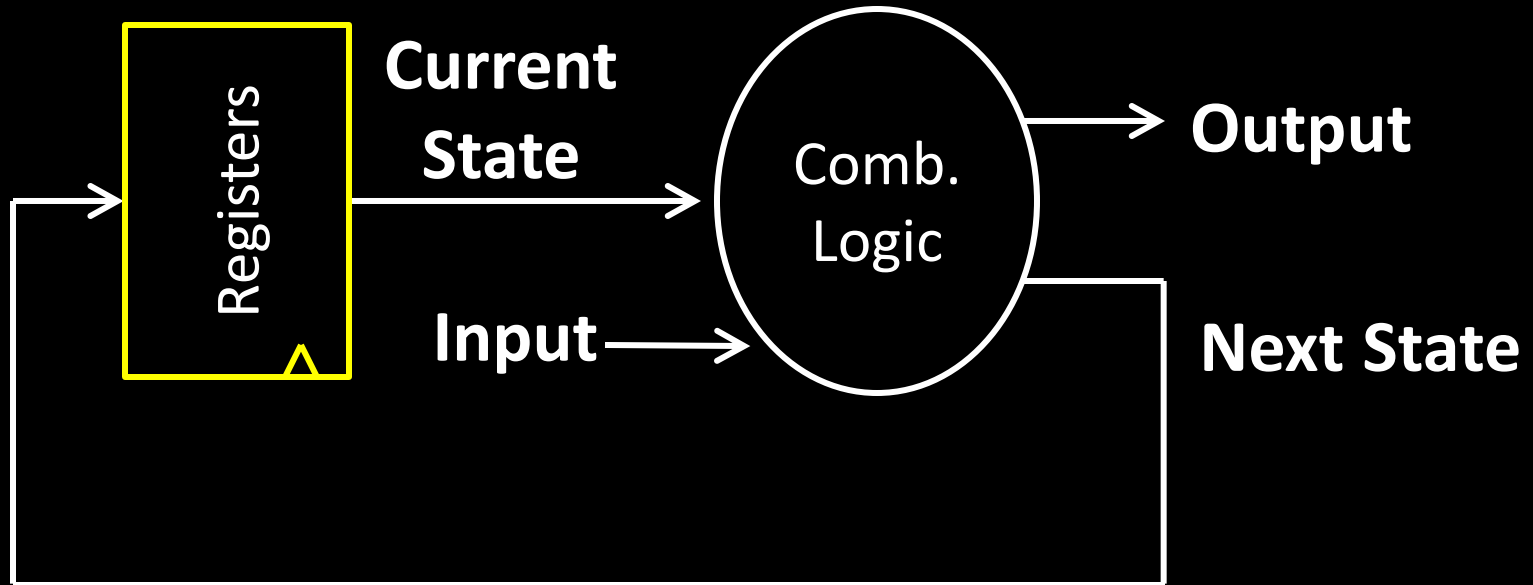

Outputs and next state depend on both current state and input

# Moore Machine

## Special Case: Moore Machine

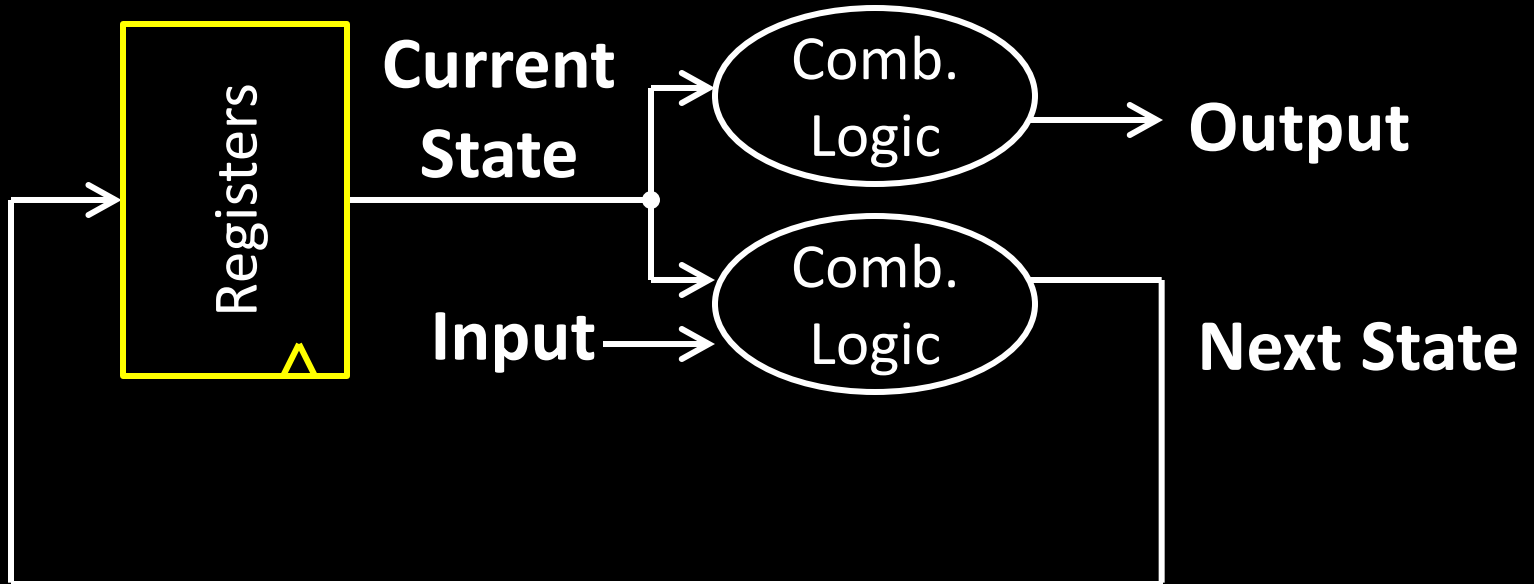

Outputs depend only on current state

# Goals for today

---

## Review

- Finite State Machines

## Memory

- Register Files
- Tri-state devices
- SRAM (Static RAM—random access memory)
- DRAM (Dynamic RAM)

# Example: Digital Door Lock

---



## Digital Door Lock

Inputs:

- keycodes from keypad
- clock

Outputs:

- “unlock” signal
- display how many keys pressed so far



# Door Lock: Inputs

Assumptions:

- signals are synchronized to clock
- Password is B-A-B




K  
A  
B

K	A	B	Meaning
0	0	0	$\emptyset$ (no key)
1	1	0	'A' pressed
1	0	1	'B' pressed


# Door Lock: Outputs

Assumptions:


- High pulse on U unlocks door

 


# Door Lock: Simplified State Diagram

 


# Door Lock: Simplified State Diagram

 

# Door Lock: Simplified State Diagram

 

# Door Lock: Simplified State Diagram

 

Cur. State	Input	Next State
Idle	$\emptyset$	Idle
Idle	"B"	G1
Idle	"A"	B1
G1	$\emptyset$	G1
G1	"A"	G2
G1	"B"	B2
G2	$\emptyset$	B2
G2	"B"	G3
G2	"A"	Idle
G3	any	Idle
B1	$\emptyset$	B1
B1	K	B2
B2	$\emptyset$	B2
B2	K	Idle

# State Table Encoding


$S_2$	$S_1$	$S_0$	$D_3$	$D_2$	$D_1$	$D_0$	$U$
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	0	0	1	1	1
1	0	0	0	0	0	1	0
1	0	1	0	0	1	0	0

$D_3$  [

State	$S_2$	$S_1$	$S_0$
Idle	0	0	0
G1	0	0	1
G2	0	1	0
G3	0	1	1
B1	1	0	0
B2	1	0	1

$S_2$	$S_1$	$S_0$	$K$	$A$	$B$	$S'_2$	$S'_1$	$S'_0$
0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0	1
0	0	0	1	1	0	1	0	0
0	0	1	0	0	0	0	0	1
0	0	1	1	1	0	0	1	0
0	0	1	1	0	1	1	0	1
0	1	0	0	0	0	0	1	0
0	1	0	1	0	1	0	1	1
0	1	0	1	1	0	0	0	0
0	1	1	x	x	x	0	0	0
1	0	0	0	0	0	1	0	0
1	0	0	1	x	x	1	0	1
1	0	1	0	0	0	1	0	1
1	0	1	1	x	x	0	0	0

# Door Lock: Implementation

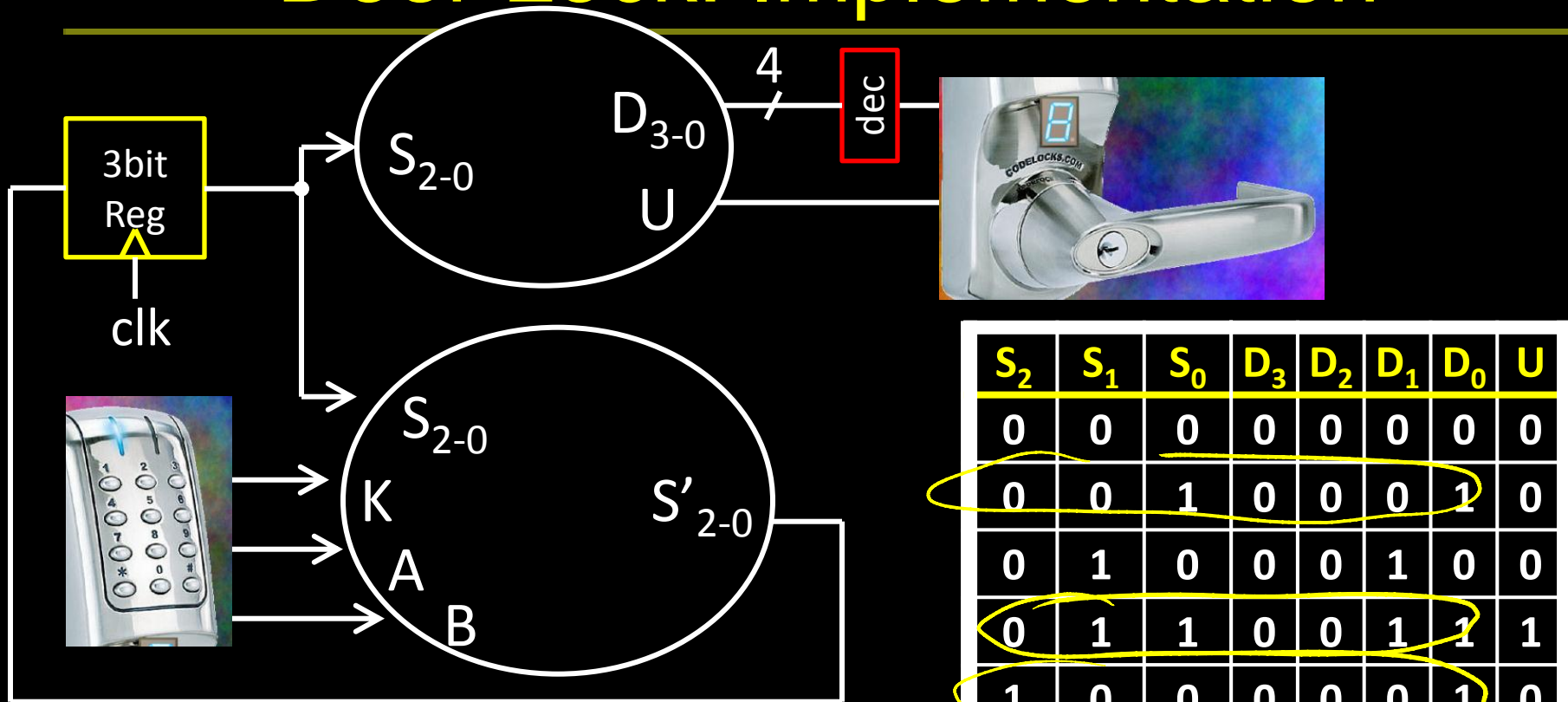

$S_2$	$S_1$	$S_0$	$D_3$	$D_2$	$D_1$	$D_0$	$U$
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	0	0	1	1	1
1	0	0	0	0	0	1	0
1	0	1	0	0	1	0	0

## Strategy:


- (1) Draw a state diagram (e.g. Moore Machine)
- (2) Write output and next-state tables
- (3) Encode states, inputs, and outputs as bits
- (4) Determine logic equations for next state and outputs

$$U = \bar{S}_2 S_1 S_0$$

$$D_0 = \bar{S}_2 \bar{S}_1 S_0 + \bar{S}_2 S_1 S_0 + S_2 \bar{S}_1 \bar{S}_0$$



# Door Lock: Implementation

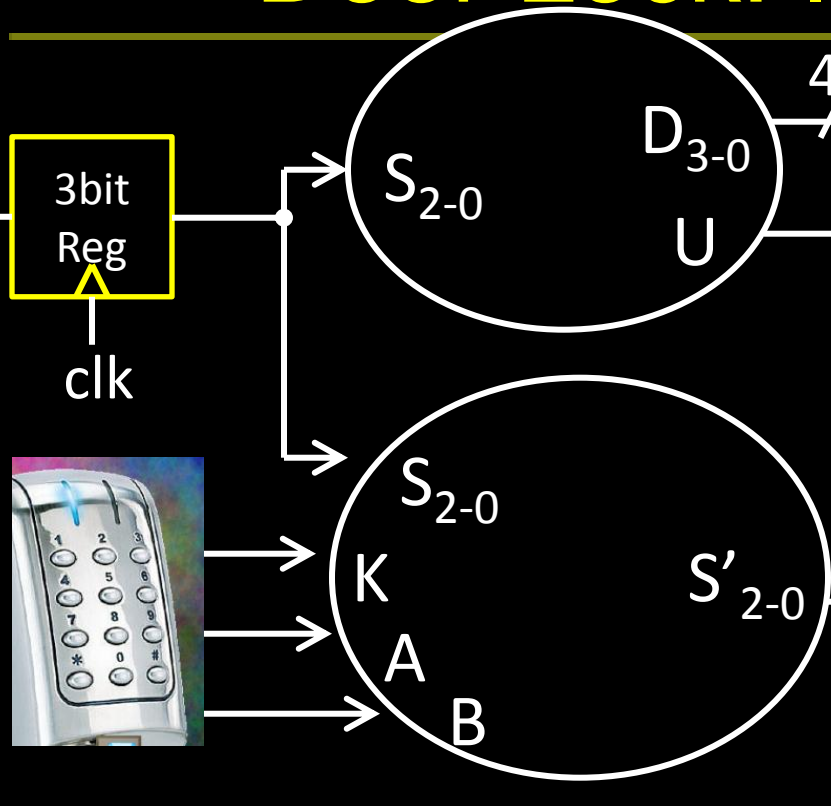

$S_2$	$S_1$	$S_0$	K	A	B	$S'_2$	$S'_1$	$S'_0$
0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0	1
0	0	0	1	1	0	1	0	0
0	0	1	0	0	0	0	0	1
0	0	1	1	1	0	0	1	0
0	0	1	1	0	1	1	0	1
0	1	0	0	0	0	0	1	0
0	1	0	1	0	1	0	1	1
0	1	0	1	1	0	0	0	0
0	1	1	x	x	x	0	0	0
1	0	0	0	0	0	1	0	0
1	0	0	1	x	x	1	0	1
1	0	1	0	0	0	1	0	1
1	0	1	1	x	x	0	0	0

## Strategy:

- (1) Draw a state diagram (e.g. Moore Machine)
- (2) Write output and next-state tables
- (3) Encode states, inputs, and outputs as bits
- (4) Determine logic equations for next state

# Administrivia

---

Make sure partner in same Lab Section ***this week***

Lab2 is out

Due in one week, next Monday, start early

Work **alone**

**Save your work!**

- **Save often.** Verify file is non-zero. Periodically save to Dropbox, email.
- **Beware of MacOSX 10.5 (leopard) and 10.6 (snow-leopard)**

Use your resources

- Lab Section, Piazza.com, Office Hours, Homework Help Session,
- Class notes, book, Sections, CSUGLab

No Homework this week

# Administrivia

---

Check online syllabus/schedule

- <http://www.cs.cornell.edu/Courses/CS3410/2012sp/schedule.html>

Slides and Reading for lectures

Office Hours

Homework and Programming Assignments

Prelims (in evenings):

- Tuesday, February 28<sup>th</sup>
- Thursday, March 29<sup>th</sup>
- Thursday, April 26<sup>th</sup>

Schedule is subject to change

# Collaboration, Late, Re-grading Policies

---

## “Black Board” Collaboration Policy

- Can discuss approach together on a “black board”
- **Leave and write up solution independently**
- Do not copy solutions

## Late Policy

- Each person has a **total of *four* “slip days”**
- **Max of *two* slip days** for any individual assignment
- **Slip days deducted first** for *any* late assignment, cannot selectively apply slip days
- For projects, slip days are deducted from all partners
- 20% deducted per day late after slip days are exhausted

## Regrade policy

- Submit written request to lead TA,  
and lead TA will pick a different grader
- Submit another written request,  
lead TA will regrade directly
- Submit yet another written request for professor to regrade.

# Goals for today

---

## Review

- Finite State Machines

## Memory

- Register Files
- Tri-state devices
- SRAM (Static RAM—random access memory)
- DRAM (Dynamic RAM)


# Register File

## Register File

- N read/write registers
- Indexed by register number
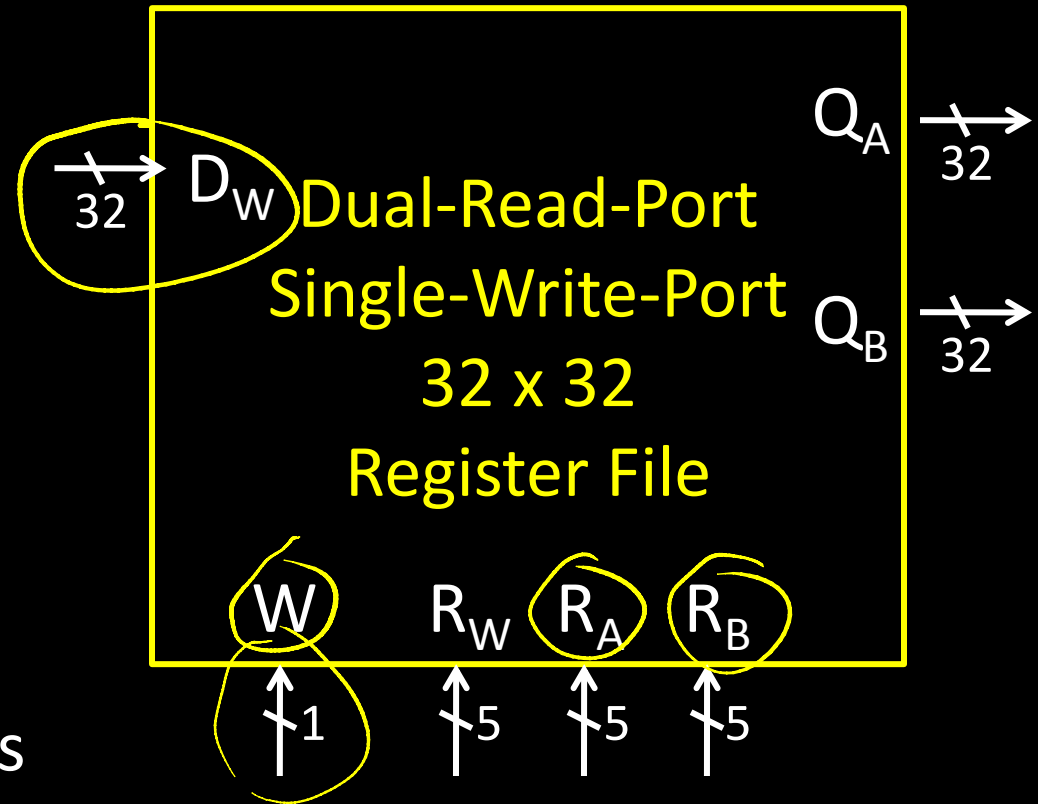
## Implementation:

- D flip flops to store bits
- Decoder for each **write port**
- Mux for each **read port**



$$2^5 = 32 \text{ Registers}$$


# Register File

## Register File

- N read/write registers
- Indexed by register number
 
## Implementation:

- D flip flops to store bits
- Decoder for each write port
- Mux for each read port




# Register File

## Register File

- N read/write registers
- Indexed by register number
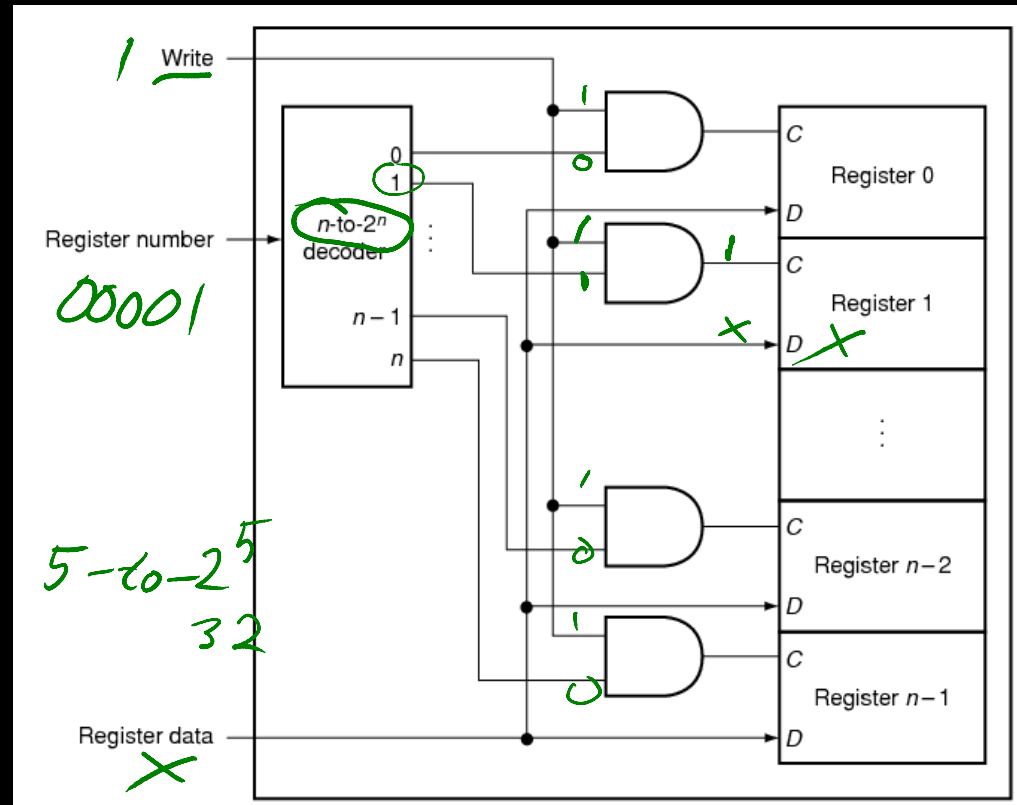
## Implementation:

- D flip flops to store bits
- Decoder for each write port
- Mux for each read port





# Register File

---

## Register File

- N read/write registers
- Indexed by register number

## Implementation:

- D flip flops to store bits
- Decoder for each **write port**
- Mux for each **read port**

What happens if same register read and writtend during same clock cycle?

# Tradeoffs

## Register File tradeoffs

- + Very fast (a few gate delays for both read and write)
- + Adding extra ports is straightforward

- Doesn't scale

$$\begin{aligned}2^{10} &= 1024 \approx 1K \\2^{20} &= 1M \\2^{30} &= 1G \\2^{40} &= 1T\end{aligned}$$

8 MB

1M x 8 bits


1M - to - 1  
20 bits

# Building Large Memories

---


Need a shared **bus** (or shared **bit line**)

 - Many FFs/outputs/etc. connected to single wire
- Only one output *drives* the bus at a time




# Tri-State Devices

## Tri-State Buffers

 


E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

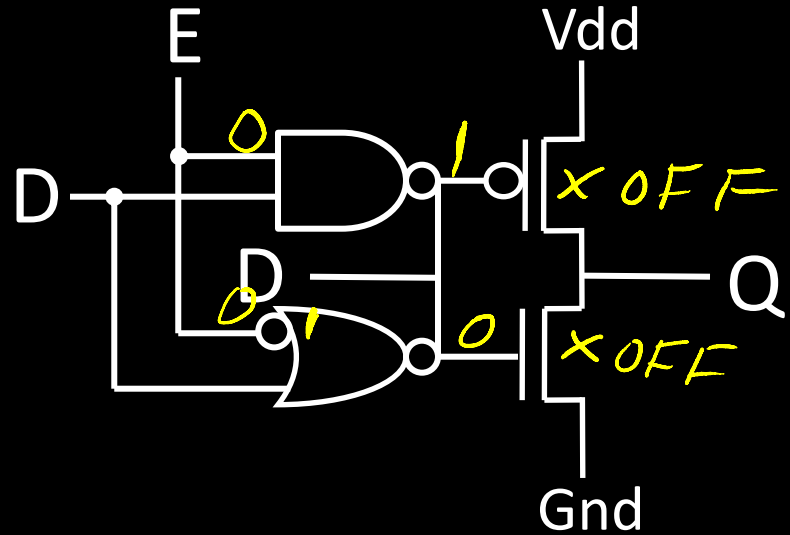


high impedance  
not connected

# Tri-State Devices

## Tri-State Buffers

 


E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

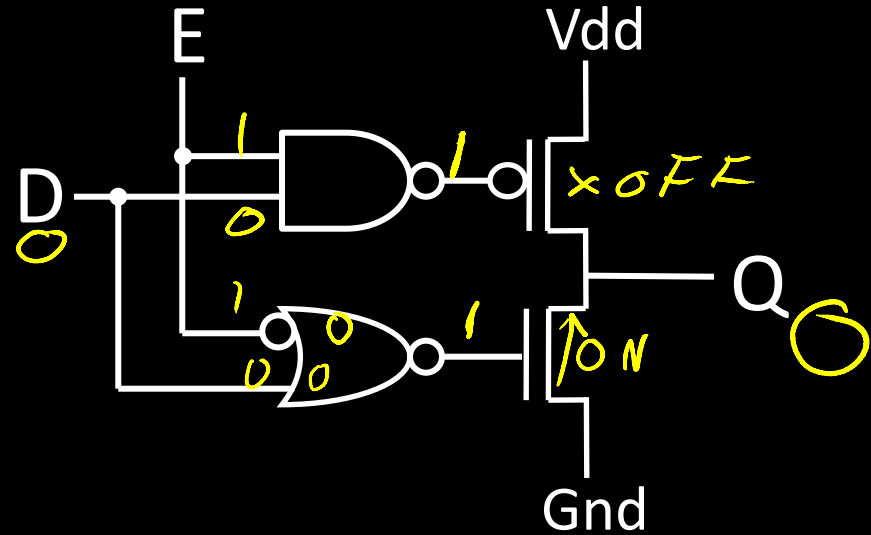

if  $E=1$ ,  $Q=D$


# Shared Bus

 

# SRAM
 
## Static RAM (SRAM)


- Essentially just SR Latches + tri-states buffers



# SRAM
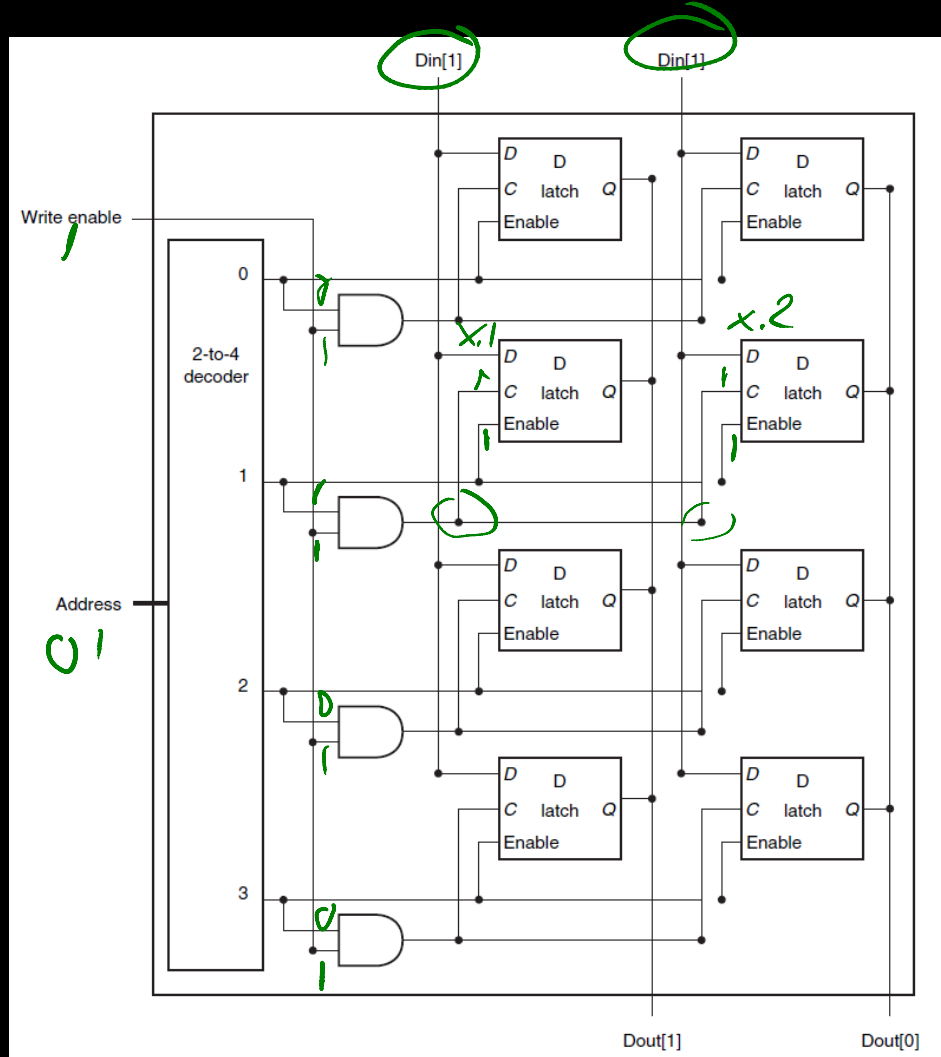
## Static RAM (SRAM)


- Essentially just SR Latches + tri-states buffers



4 x 2 SRAM




# SRAM Chip

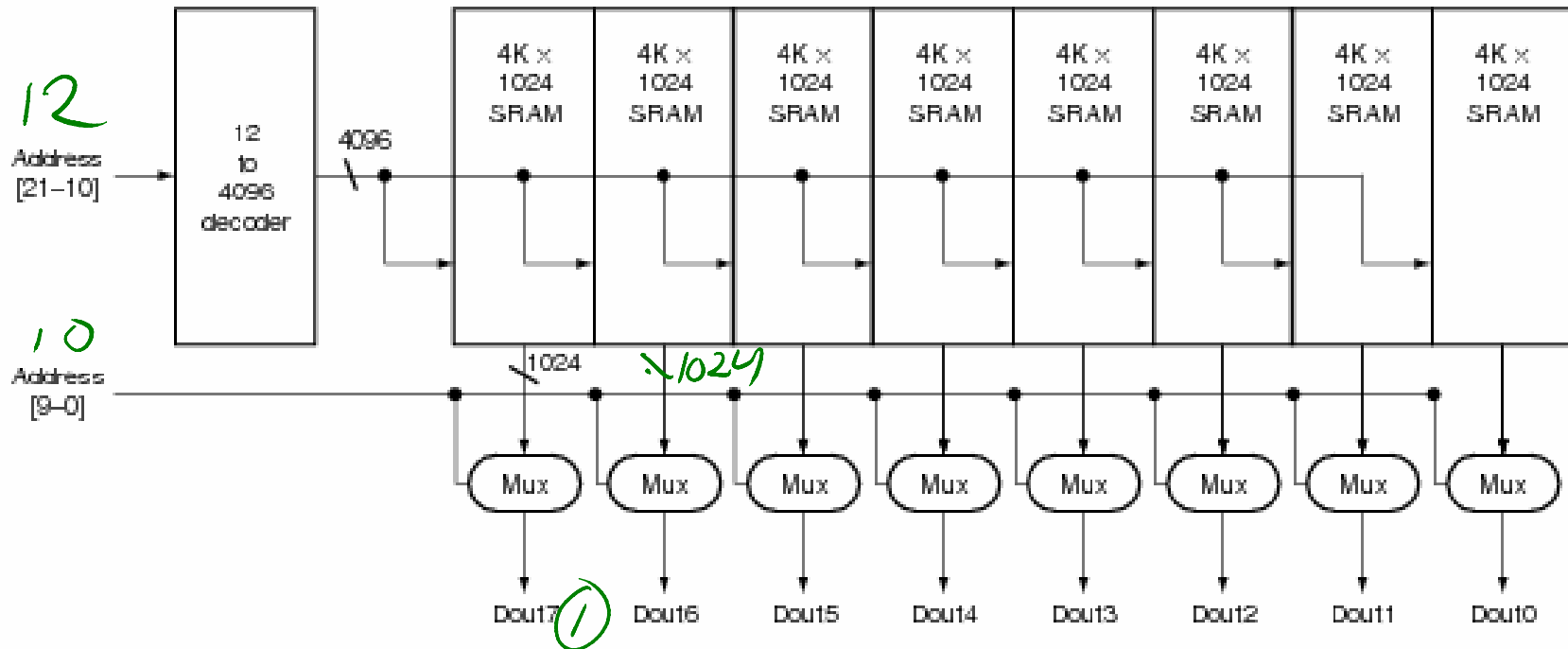


**FIGURE B.9.4 Typical organization of a 4M x 8 SRAM as an array of 4K x 1024 arrays.** The first decoder generates the addresses for eight 4K x 1024 arrays; then a set of multiplexers is used to select 1 bit from each 1024-bit-wide array. This is a much easier design than a single-level decode that would need either an enormous decoder or a gigantic multiplexer. In practice, a modern SRAM of this size would probably use an even larger number of blocks, each somewhat smaller.

# SRAM Chip

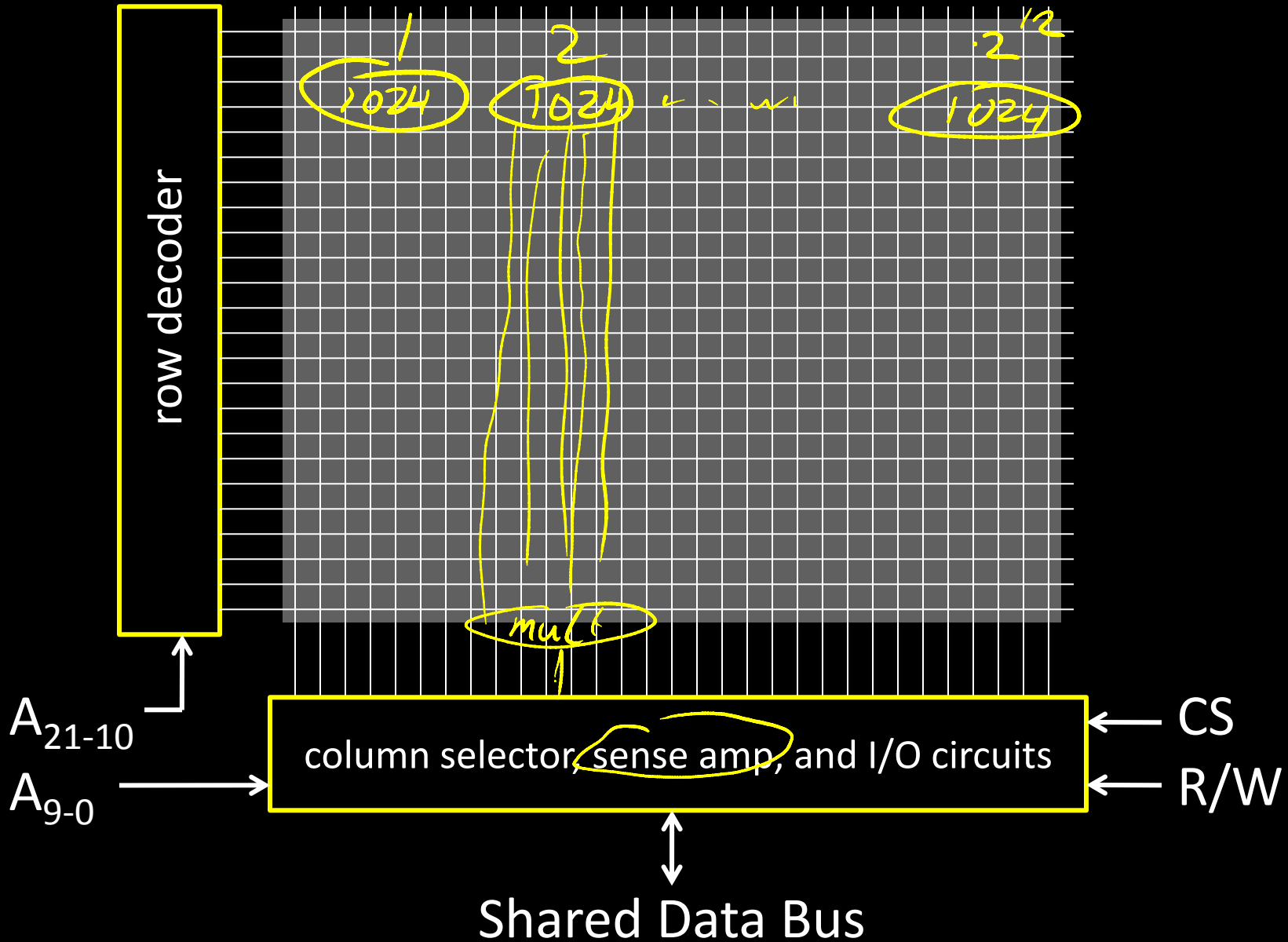

# SRAM Cell

## Typical SRAM Cell

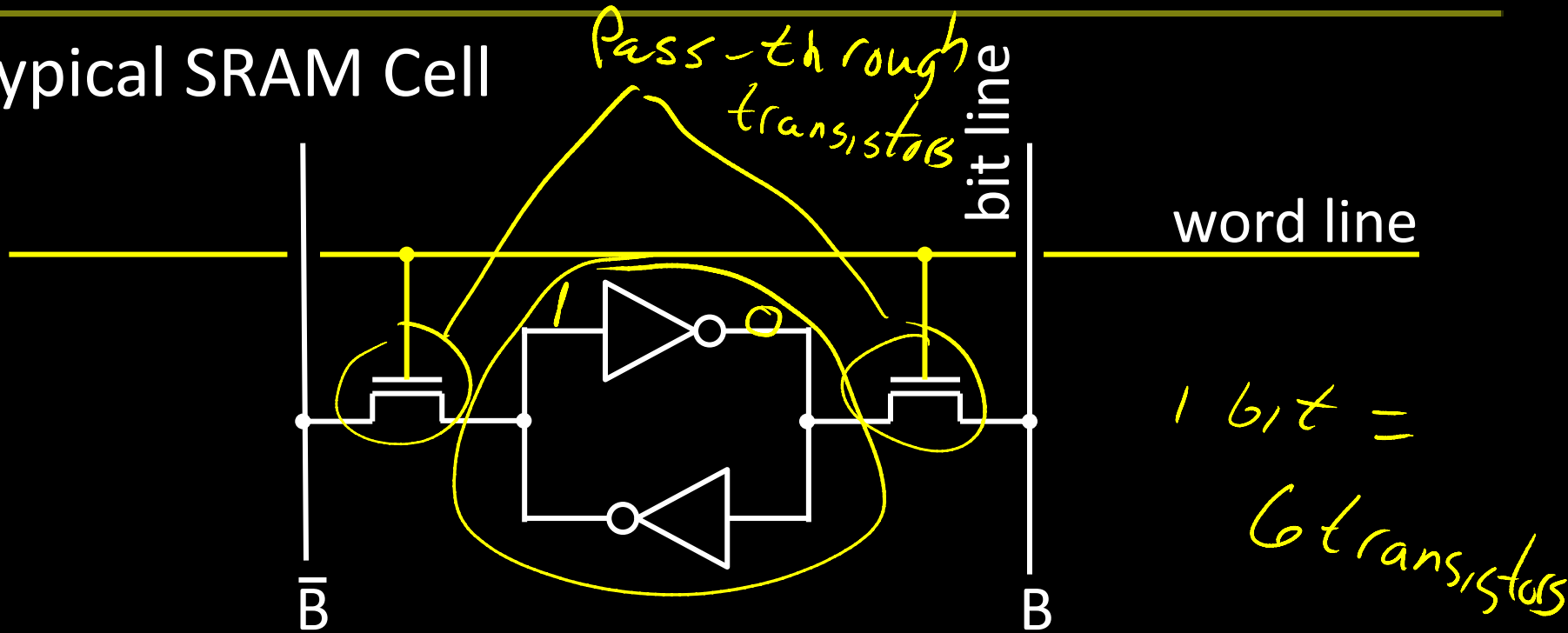

Each cell stores one bit, and requires 4 – 8 transistors (6 is typical)


### Read:

- pre-charge  $B$  and  $\bar{B}$  to  $V_{dd}/2$
- pull word line high
- cell pulls  $B$  or  $\bar{B}$  low, sense amp detects voltage difference

### Write:

- pull word line high
- drive  $B$  and  $\bar{B}$  to flip cell

# SRAM Modules and Arrays

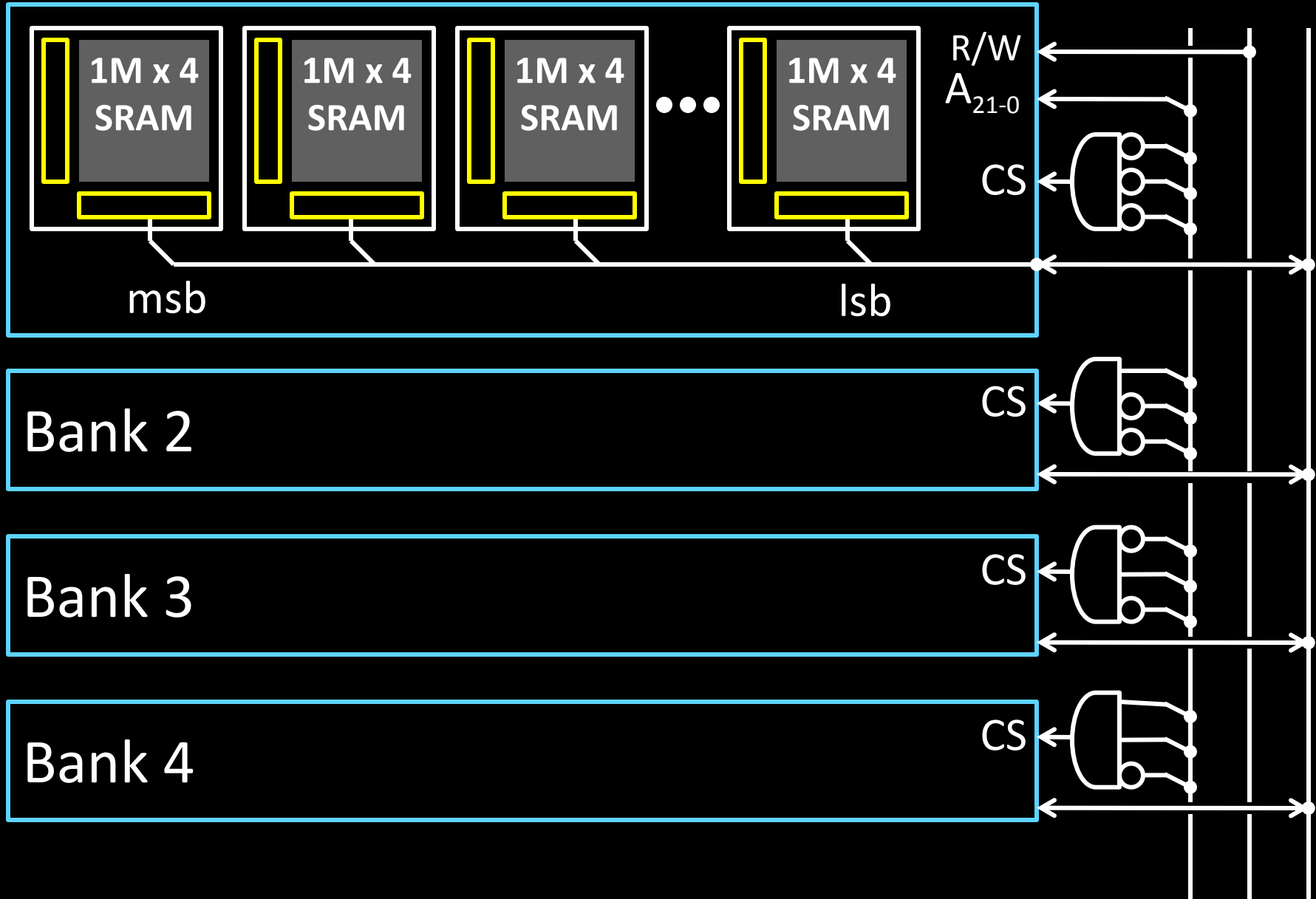

# SRAM Summary

---


## SRAM

- A few transistors (~6) per cell
- Used for working memory (caches)
- But for even higher density...

# Dynamic RAM: DRAM

## Dynamic-RAM (DRAM)

- Data values require constant refresh

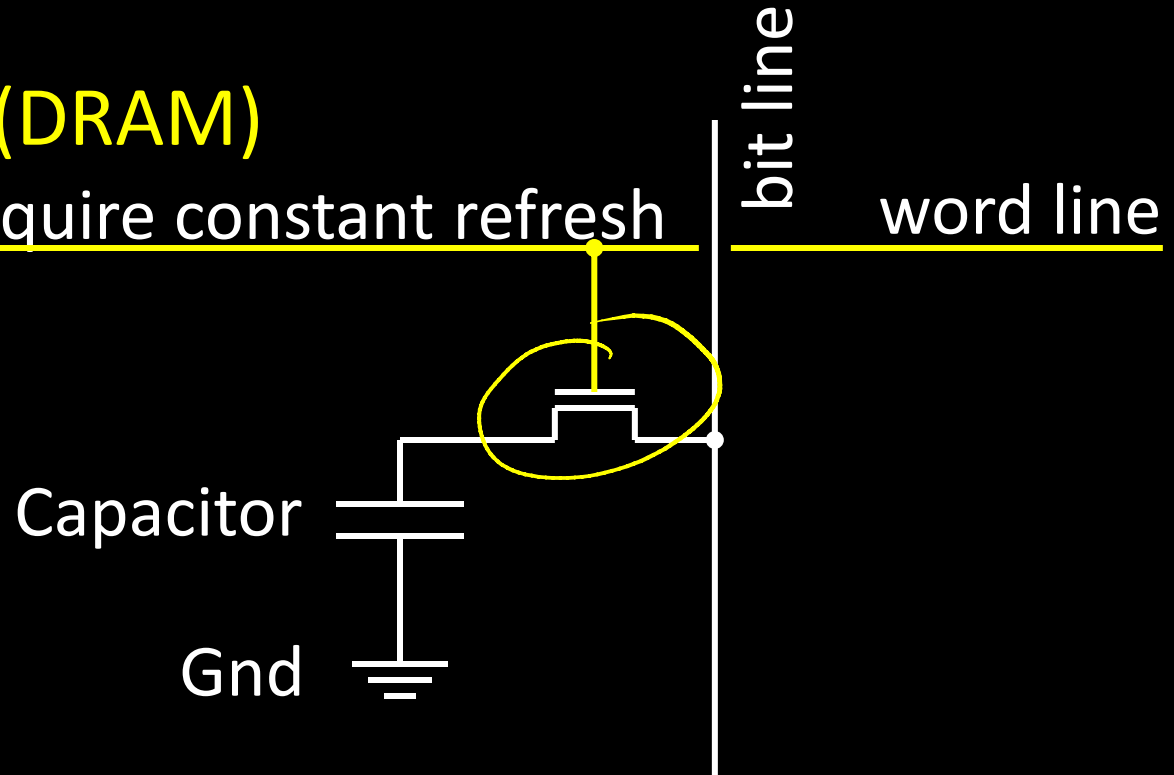

# DRAM vs. SRAM

---

Single transistor vs. many gates

- Denser, cheaper (\$30/1GB vs. \$30/2MB)
- But more complicated, and has analog sensing

Also needs refresh

- Read and write back...
- ...every few milliseconds
- Organized in 2D grid, so can do rows at a time
- Chip can do refresh internally

Hence... slower and energy inefficient

# Memory

---

## Register File tradeoffs

- + Very fast (a few gate delays for both read and write)
- + Adding extra ports is straightforward
- Expensive, doesn't scale
- Volatile

## Volatile Memory alternatives: SRAM, DRAM, ...

- Slower
- + Cheaper, and scales well
- Volatile

## Non-Volatile Memory (NV-RAM): Flash, EEPROM, ...

- + Scales well
- Limited lifetime; degrades after 100000 to 1M writes



# Summary

---

We now have enough building blocks to build machines that can perform non-trivial computational tasks

Register File: Tens of words of working memory

SRAM: Millions of words of working memory

DRAM: Billions of words of working memory

NVRAM: long term storage

(usb fob, solid state disks, BIOS, ...)

**Next time we will build a simple processor!**