

Numbers & Arithmetic

Hakim Weatherspoon
CS 3410, Spring 2012
Computer Science
Cornell University

See: P&H Chapter 2.4 - 2.6, 3.2, C.5 – C.6

Example: Big Picture

- Computer System Organization and Programming platform from 10 years ago

Goals for today

Today

- Review Logic Minimization
- Build a circuit (e.g. voting machine)
- Number representations
- Building blocks (encoders, decoders, multiplexors)

Binary Operations

- One-bit and four-bit adders
- Negative numbers and two's compliment
- Addition (two's compliment)
- Subtraction (two's compliment)
- Performance


Logic Minimization

- How to implement a desired function?

a	b	c	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

$\bar{a}\bar{b}\bar{c}$
 
$$\text{out} = \bar{a}\bar{b}c + \bar{a}b\bar{c} + a\bar{b}c$$



Logic Minimization

- How to implement a desired function?

a	b	c	out	minterm
0	0	0	0	$\bar{a} \bar{b} \bar{c}$
0	0	1	1	$\bar{a} \bar{b} c$
0	1	0	0	$\bar{a} b \bar{c}$
0	1	1	1	$\bar{a} b c$
1	0	0	0	$a \bar{b} \bar{c}$
1	0	1	1	$a \bar{b} c$
1	1	0	0	$a b \bar{c}$
1	1	1	0	$a b c$

sum of products:

- OR of all minterms where out=1

corollary: *any* combinational circuit *can be* implemented in two levels of logic (ignoring inverters)

Karnaugh Maps

How does one find the most efficient equation?

- Manipulate algebraically until...?
- Use Karnaugh maps (optimize visually)
- Use a software optimizer


For large circuits

- Decomposition & reuse of building blocks

Minimization with Karnaugh maps (1)

a	b	c	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0
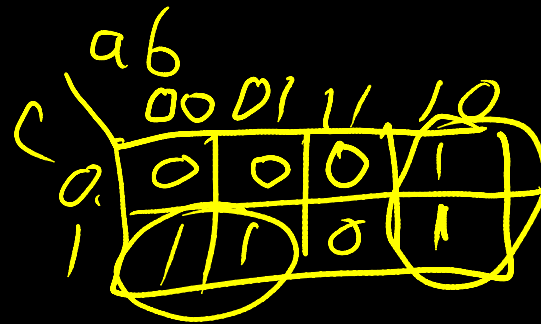
$$\text{out} = \bar{a}bc + \bar{a}b\bar{c} + a\bar{b}c + abc$$



$$abc = 100$$

$$\text{out} = a\bar{b} + \bar{a}c$$

Minimization with Karnaugh maps (1)

a	b	c	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

- ◆ Sum of minterms yields
 - $\bar{a}bc + a\bar{b}c + a\bar{b}\bar{c} + a\bar{b}c$

Minimization with Karnaugh maps (2)

a	b	c	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

◆ Sum of minterms yields

- $\bar{a}\bar{b}c + \bar{a}bc + a\bar{b}\bar{c} + ab\bar{c}$

◆ Karnaugh maps identify which inputs are (ir)relevant to the output

		ab			
		00	01	11	10
c	0	0	0	0	1
	1	1	1	0	1

Minimization with Karnaugh maps (2)

a	b	c	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

		ab			
		00	01	11	10
c	0	0	0	0	1
	1	1	1	0	1

◆ Sum of minterms yields

- $\bar{a}bc + \bar{a}bc + a\bar{b}c + a\bar{b}c$

◆ Karnaugh map minimization

- Cover all 1's
- Group adjacent blocks of 2^n 1's that yield a rectangular shape
- Encode the common features of the rectangle
 - ◆ $out = a\bar{b} + \bar{a}c$

Karnaugh Minimization Tricks (1)

c \ ab	00	01	11	10
0	0	1	1	1
1	0	0	1	0

$$out = a\bar{c} + b\bar{c} + ab$$

c \ ab	00	01	11	10
0	1	1	1	1
1	0	0	1	0

$$out = \bar{c} + ab$$

Karnaugh Minimization Tricks (1)

c \ ab	00	01	11	10
0	0	1	1	1
1	0	0	1	0

◆ Minterms can overlap

- $out = b\bar{c} + a\bar{c} + ab$

c \ ab	00	01	11	10
0	1	1	1	1
1	0	0	1	0

◆ Minterms can span 2, 4, 8 or more cells

- $out = \bar{c} + ab$

Karnaugh Minimization Tricks (2)

cd \ ab	00	01	11	10
00	0	0	0	0
01	1	0	0	1
11	1	0	0	1
10	0	0	0	0

$$\text{out} = \overline{bd}$$

cd \ ab	00	01	11	10
00	1	0	0	1
01	0	0	0	0
11	0	0	0	0
10	1	0	0	1

$$\text{out} = \overline{bd}$$

Karnaugh Minimization Tricks (2)

cd \ ab	00	01	11	10
00	0	0	0	0
01	1	0	0	1
11	1	0	0	1
10	0	0	0	0

- The map wraps around
 - $\text{out} = \overline{b}d$

cd \ ab	00	01	11	10
00	1	0	0	1
01	0	0	0	0
11	0	0	0	0
10	1	0	0	1

- $\text{out} = \overline{b}d$

Karnaugh Minimization Tricks (3)

		ab			
		00	01	11	10
cd	00	0	0	0	0
	01	1	x	x	x
	11	1	x	x	1
	10	0	0	0	0

$$\text{out} = d$$

		ab			
		00	01	11	10
cd	00	1	0	0	x
	01	0	x	x	0
	11	0	x	x	0
	10	1	0	0	1

$$\text{out} = \overline{d}$$

Karnaugh Minimization Tricks (3)


cd \ ab		ab			
		00	01	11	10
cd	00	0	0	0	0
	01	1	x	x	x
	11	1	x	x	1
	10	0	0	0	0

- “Don’t care” values can be interpreted individually in whatever way is convenient
 - assume all x’s = 1
 - out = d

cd \ ab		ab			
		00	01	11	10
cd	00	1	0	0	x
	01	0	x	x	0
	11	0	x	x	0
	10	1	0	0	1

- assume middle x’s = 0
- assume 4th column x = 1
- out = \overline{bd}

Multiplexer

 


- A multiplexer selects between multiple inputs
 - out = a, if d = 0
 - out = b, if d = 1

a	b	d	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

- Build truth table
- Minimize diagram
- Derive logic diagram


$$\text{out} = \bar{a}bc + a\bar{b}\bar{c} + a\bar{b}c + abc$$

Multiplexer Implementation

 


- Build a truth table
 $= abd + ab\bar{d} + \bar{a}bd + a\bar{b}\bar{d}$

a	b	d	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

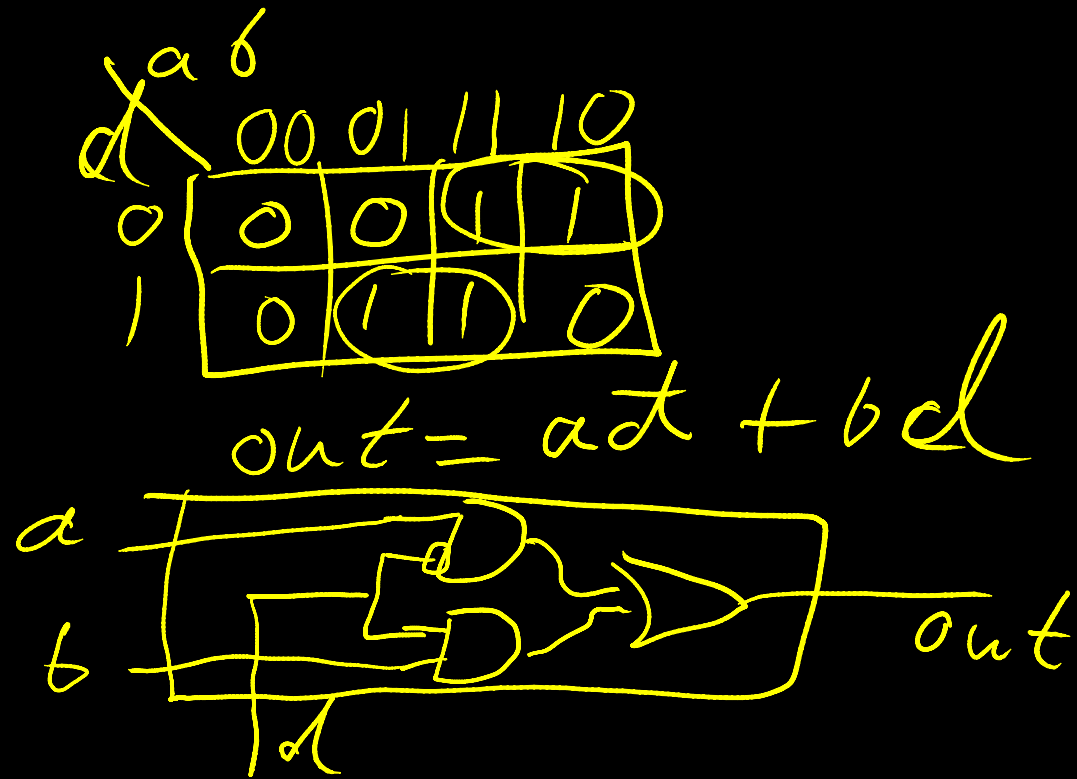

Multiplexer Implementation

 


- Build the Karnaugh map

a	b	d	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

d \ ab	00	01	11	10
0	0	0	1	1
1	0	1	1	0

Multiplexer Implementation

 


a	b	d	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

- Derive Minimal Logic Equation

d \ ab	00	01	11	10
0	0	0	1	1
1	0	1	1	0

- $out = a\bar{d} + bd$

Multiplexer Implementation

 


a	b	d	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

- Derive Minimal Logic Equation

d \ ab	00	01	11	10
0	0	0	1	1
1	0	1	1	0

- $out = a\bar{d} + bd$

 


Question

- How many logic gates and transistors did we **save** with minimized circuit?

– (do not count inverters)

– $out = abd + ab\bar{d} + \bar{a}bd + a\bar{b}\bar{d}$


– $out = a\bar{d} + bd$

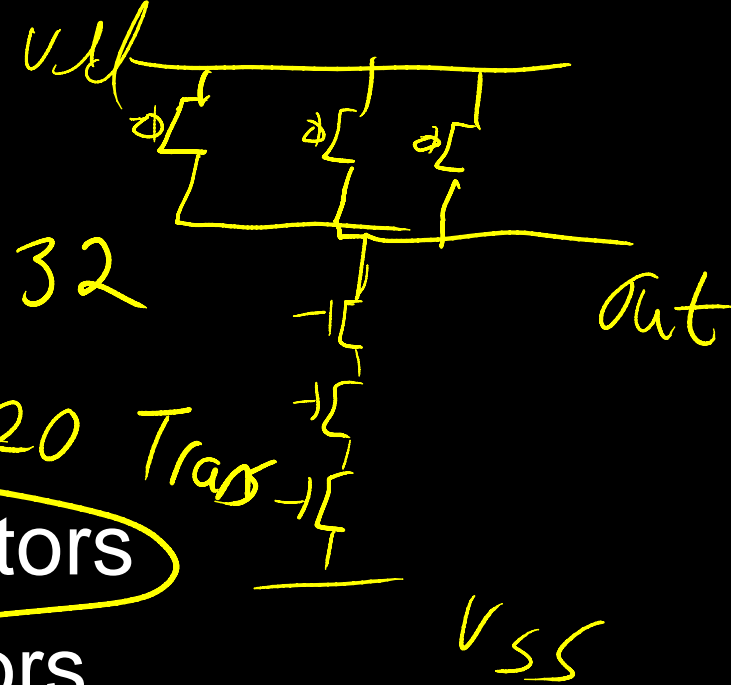


12

2 gate + 20 Trans

 - ~~(a) 2 gates and 16 transistors~~
- ~~(b) 2 gates and 8 transistors~~
- (c) 4 gates and 8 transistors
- (d) 8 gates and 8 transistors
- (e) none of the above




Logic Gates

 

- One can buy gates separately
 - ex. 74xxx series of integrated circuits
 - cost ~\$1 per chip, mostly for packaging and testing
- Cumbersome, but possible to build devices using gates put together manually

Integrated Circuits

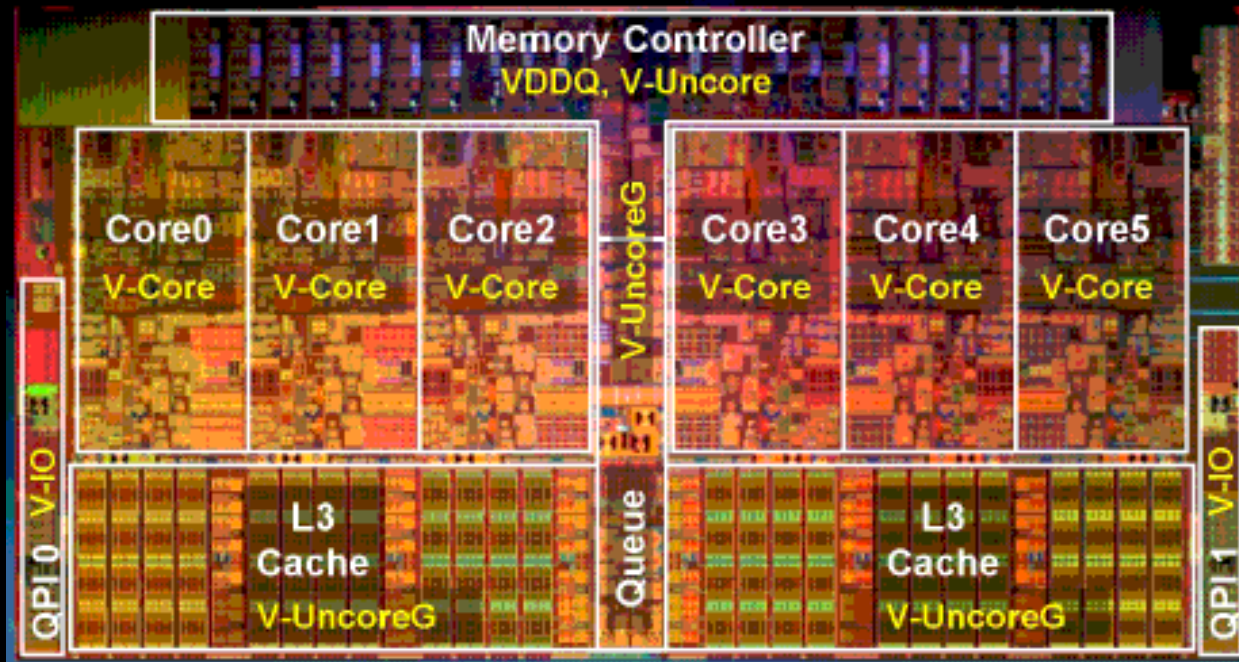

- Or one can manufacture a complete design using a custom mask
- Intel Westmere has approximately 1.17 **billion** transistors

Recap

- We can now implement any logic circuit
 - Can do it efficiently, using Karnaugh maps to find the minimal terms required
 - Can use either NAND or NOR gates to implement the logic circuit
 - Can use P- and N-transistors to implement NAND or NOR gates

Voting machine

- Lets build something interesting
- A voting machine
- Assume:
 - A vote is recorded on a piece of paper,
 - by punching out a hole,
 - there are at most 7 choices
 - we will not worry about “hanging chads” or “invalids”


Voting machine

- For now, let's just display the numerical identifier to the ballot supervisor
 - we won't do counting yet, just decoding
 - we can use four photo-sensitive transistors to find out which hole is punched out



- A photo-sensitive transistor detects the presence of light
- Photo-sensitive material triggers the gate

Ballot Reading

 

- **Input:** paper with a hole in it
- **Output:** number the ballot supervisor can record


Ballots

The 3410 optical scan
vote counter reader
machine

Input



 
- **Photo-sensitive transistor**
 - photons replenish gate depletion region
 - can distinguish dark and light spots on paper



- Use array of N sensors for voting machine input


Output

 - 7-Segment LED
- photons emitted when electrons fall into holes




$5 = 01101011$

Block Diagram

 

Encoders

 

- N might be large
- Routing wires is expensive
- More efficient encoding?

$$\log_2(N)$$

Number Representations

- Base 10 - **Decimal**

$$\begin{array}{ccc} \underline{6} & \underline{3} & \underline{7} \\ 10^2 & 10^1 & 10^0 \end{array}$$

- Just as easily use other bases
 - Base 2 - **Binary**
 - Base 8 - **Octal**
 - Base 16 - **Hexadecimal**

Counting

- Counting

<u>doc</u>	<u>oct</u>
0	0
1	1
2	2
3	3
4	4
5	5
6	6
7	7
8	10
9	11
10	12
11	:
⋮	77
99	100
100	

Base Conversion

- Base conversion via repetitive division
 - Divide by base, write remainder, move left with quotient

$$637 \div 10 = 63 \text{ rem } 7$$

$$\div 10 = 6 \text{ rem } 3$$

$$\div 10 = 0$$

rem 6
msb

lsb

Base Conversion

- Base conversion via repetitive division
 - Divide by base, write remainder, move left with quotient

$$637 \div 2 = 318 \text{ rem } 1$$

$$\div 2 = 159 \text{ rem } 0$$

$$\div 2 = 79 \text{ rem } 1$$

$$\div 2 = 39 \text{ rem } 1$$

$$2 = 19$$

$$2 = 9$$

$$2 = 4$$

$$2 = 2$$

$$2 = 1$$

$$2 = 0$$



10 = a

11 = b

12 = c

13 = d

14 = e

15 = f

lsb

1011 111001₂

msb₂ 7 d
 10 0111 1101

0x27d

1 msb

Base Conversion


- Base conversion via repetitive division
 - Divide by base, write remainder, move left with quotient

$$\begin{array}{l} 637 \div 16 = 39 \text{ rem } 13 \\ 39 \div 16 = 2 \text{ rem } 7 \\ 2 \div 16 = 0 \end{array}$$

~~0x~~ 27d

Hexadecimal, Binary, Octal Conversions

Encoder Truth Table

 


A 3-bit
encoder
with 4 inputs
for simplicity

binary encoder

<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>o₀</i>	<i>o₁</i>	<i>o₂</i>
0	0	0	0	0	0	0
1	0	0	1	1	0	0
0	1	0	0	0	1	0
0	0	1	0	0	0	1
1	1	0	0	1	1	0
0	1	1	0	0	1	1
0	0	1	1	0	0	1
1	1	1	1	1	1	1

Encoder Truth Table

 


A 3-bit
encoder
with 4 inputs
for simplicity


a	b	c	d		o ₂	o ₁	o ₀
0	0	0	0		0	0	0
1	0	0	0		0	0	1
0	1	0	0		0	1	0
0	0	1	0		0	1	1
0	0	0	1		1	0	0

- $o_2 = \overline{abcd}$
- $o_1 = \overline{a}bcd + a\overline{b}cd$
- $o_0 = \overline{a}bcd + a\overline{b}cd$

Ballot Reading

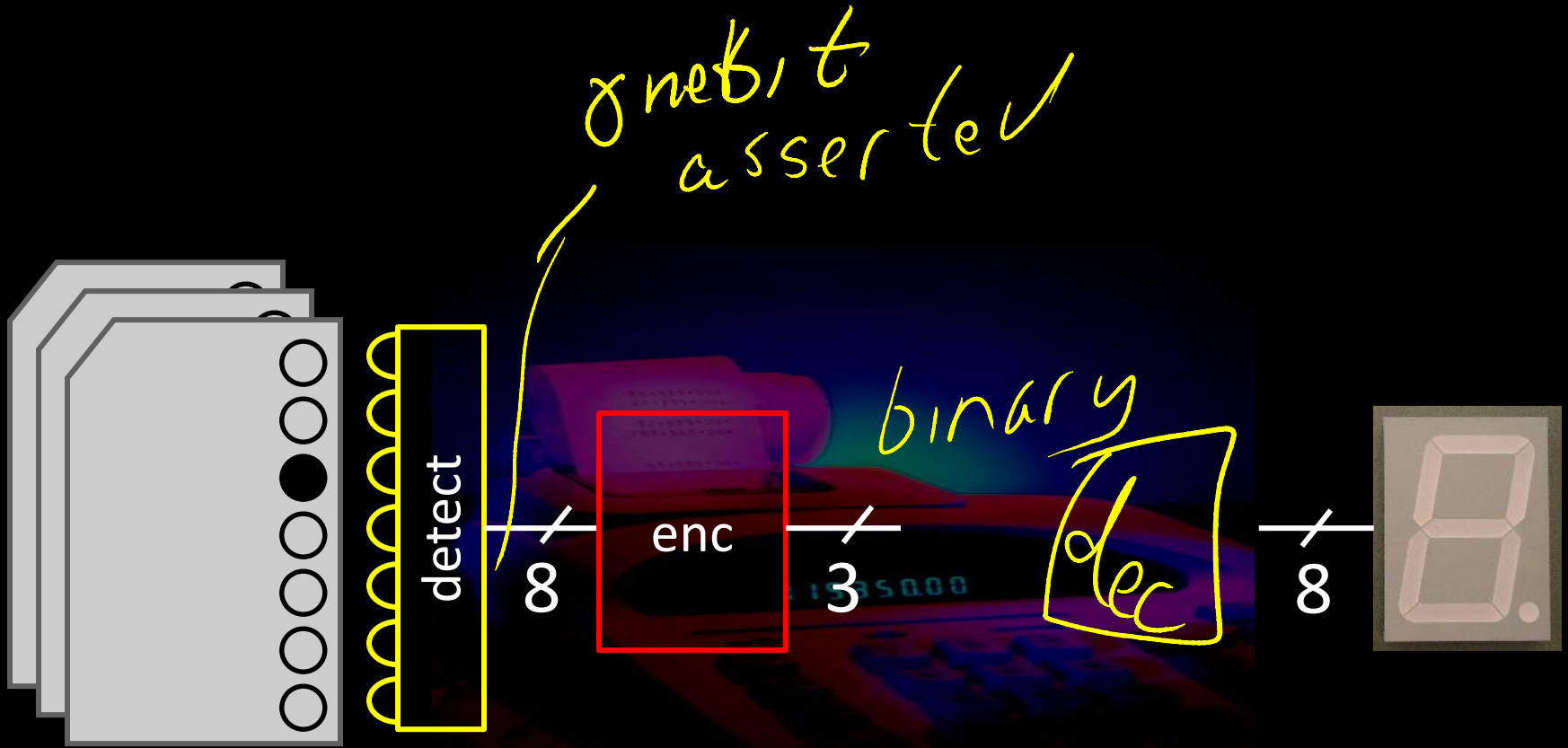

Ballot Reading

 


- Ok, we built first half of the machine
- Need to display the result

Ballots

The 3410 optical scan
vote counter reader machine


7-Segment LED Decoder

 

- 3 inputs
- encode 0 – 7 in binary
- 7 outputs
- one for each LED

7 Segment LED Decoder Implementation

b2	b1	b0	d6	d5	d4	d3	d2	d1	d0
0	0	0							
0	0	1							
0	1	0							
0	1	1							
1	0	0							
1	0	1							
1	1	0							
1	1	1	1	0	0	0	0	1	1

 


7 Segment LED Decoder Implementation

b2	b1	b0	d6	d5	d4	d3	d2	d1	d0
0	0	0	1	1	1	0	1	1	1
0	0	1	1	0	0	0	0	0	1
0	1	0	0	1	1	1	0	1	1
0	1	1	1	1	0	1	0	1	1
1	0	0	1	0	0	1	1	0	1
1	0	1	1	1	0	1	1	1	0
1	1	0	1	1	1	1	1	1	0
1	1	1	1	0	0	0	0	1	1




Ballot Reading and Display

 

Ballots

The 3410 optical scan
vote counter reader
machine

Building Blocks

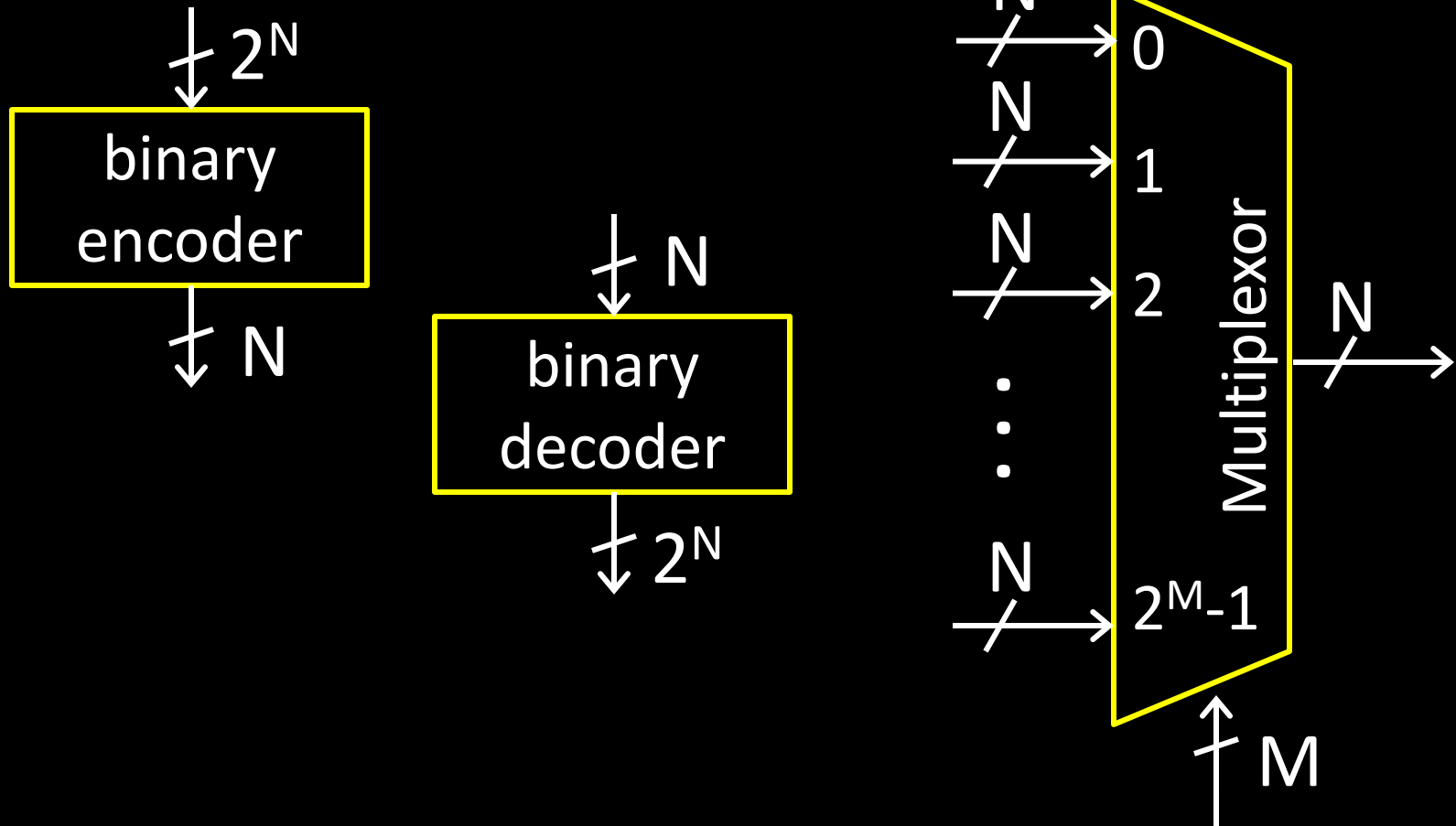

Administrivia

Make sure you are

- Registered for class, can access CMS
- Have a Section you can go to
- **Have project partner in same Lab Section**

Lab1 and HW1 are out

- Both due in one week, next Monday, start early
- Work **alone**
- **But**, use your resources
 - Lab Section, Piazza.com, Office Hours, Homework Help Session,
 - Class notes, book, Sections, CSUGLab

Homework Help Session

- Wednesday and Friday from 3:30-5:30pm
- Location: 203 Thurston

Administrivia

Check online syllabus/schedule

- <http://www.cs.cornell.edu/Courses/CS3410/2012sp/schedule.html>
- Slides and Reading for lectures
- Office Hours
- Homework and Programming Assignments
- Prelims (in evenings):
 - Tuesday, February 28th
 - Thursday, March 29th
 - April 26th

Schedule is subject to change

Binary Addition


$$\begin{array}{r} \uparrow \\ 183 \\ + 254 \\ \hline \end{array}$$

437

$$\begin{array}{r} 001110 \\ + 011100 \\ \hline 101010 \end{array}$$

- Addition works the same way regardless of base
- Add the digits in each position
- Propagate the carry

1-bit Adder

 


Half Adder

- Adds two 1-bit numbers
- Computes 1-bit result and 1-bit carry

A	B	C	R
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

1-bit Adder with Carry

 


Full Adder

- Adds three 1-bit numbers
- Computes 1-bit result and 1-bit carry
- Can be cascaded

a	b	C _{in}	C _{out}	R
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


4-bit Adder

 


4-Bit Full Adder

- Adds two 4-bit numbers and carry in
- Computes 4-bit result and carry out
- Can be cascaded

4-bit Adder

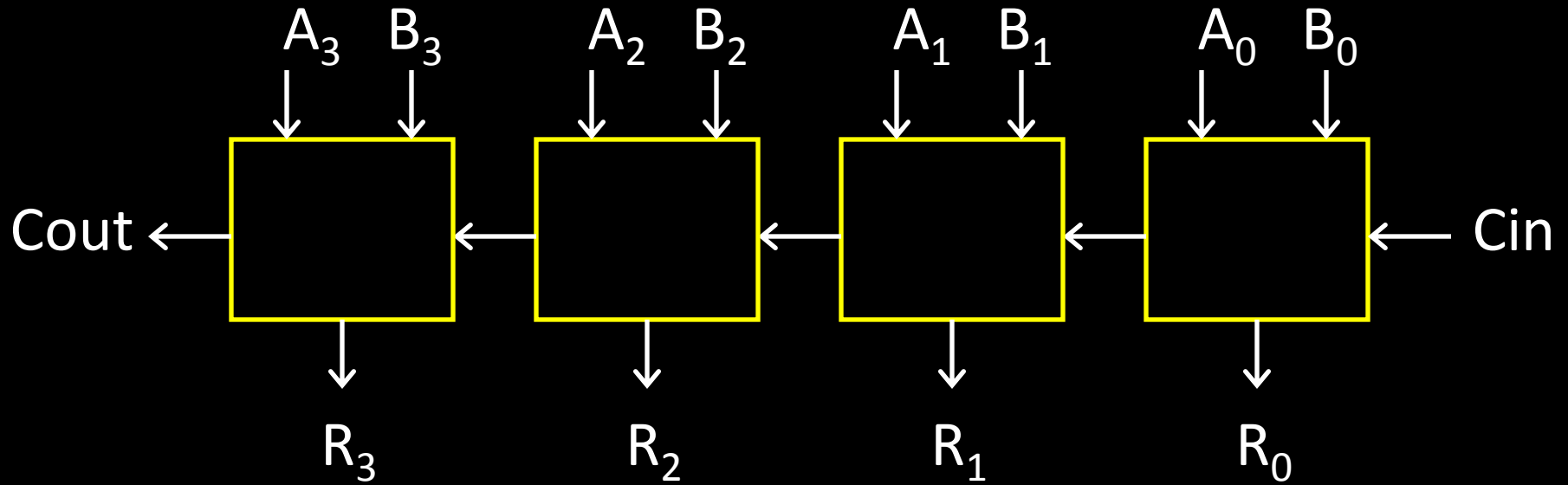

4-bit Adder

 

- Adds two 4-bit numbers, along with carry-in
- Computes 4-bit result and carry out

Arithmetic with Negative Numbers

- Addition with negatives:
 - $\text{pos} + \text{pos} \rightarrow$ add magnitudes, result positive
 - $\text{neg} + \text{neg} \rightarrow$ add magnitudes, result negative
 - $\text{pos} + \text{neg} \rightarrow$ subtract smaller magnitude,
keep sign of bigger magnitude

First Attempt: Sign/Magnitude Representation

- First Attempt: Sign/Magnitude Representation
- 1 bit for sign (0=positive, 1=negative)
- N-1 bits for magnitude

Two's Complement Representation

- Better: Two's Complement Representation
- Leading 1's for negative numbers
- To negate **any** number:
 - complement *all* the bits
 - then add 1

Two's Complement

- **Non-negatives** **Negatives**

- (as usual): (two's complement: flip then add 1):

- +0 = 0000 $\sim 0 = 1111$ -0 = 0000
- +1 = 0001 $\sim 1 = 1110$ -1 = 1111
- +2 = 0010 $\sim 2 = 1101$ -2 = 1110
- +3 = 0011 $\sim 3 = 1100$ -3 = 1101
- +4 = 0100 $\sim 4 = 1011$ -4 = 1100
- +5 = 0101 $\sim 5 = 1010$ -5 = 1011
- +6 = 0110 $\sim 6 = 1001$ -6 = 1010
- +7 = 0111 $\sim 7 = 1000$ -7 = 1001
- +8 = 1000 $\sim 8 = 0111$ -8 = 1000

Two's Complement Facts

- Signed two's complement
 - Negative numbers have leading 1's
 - zero is unique: $+0 = -0$
 - wraps from largest positive to largest negative
- N bits can be used to represent
 - unsigned:
 - eg: 8 bits \Rightarrow
 - signed (two's complement):
 - ex: 8 bits \Rightarrow


Sign Extension & Truncation

- Extending to larger size

- Truncate to smaller size

Two's Complement Addition

 - Addition with two's complement signed numbers
- Perform addition as usual, regardless of sign (it just works)



Diversion: 10's Complement

- How does that work?


$$\begin{array}{r} -154 \\ +283 \\ \hline \end{array}$$

Overflow

- **Overflow**
 - adding a negative and a positive?
 - adding two positives?
 - adding two negatives?
- **Rule of thumb:**
 - Overflow happened iff
carry into msb \neq carry out of msb


Two's Complement Adder

 - Two's Complement Adder with overflow detection



Binary Subtraction

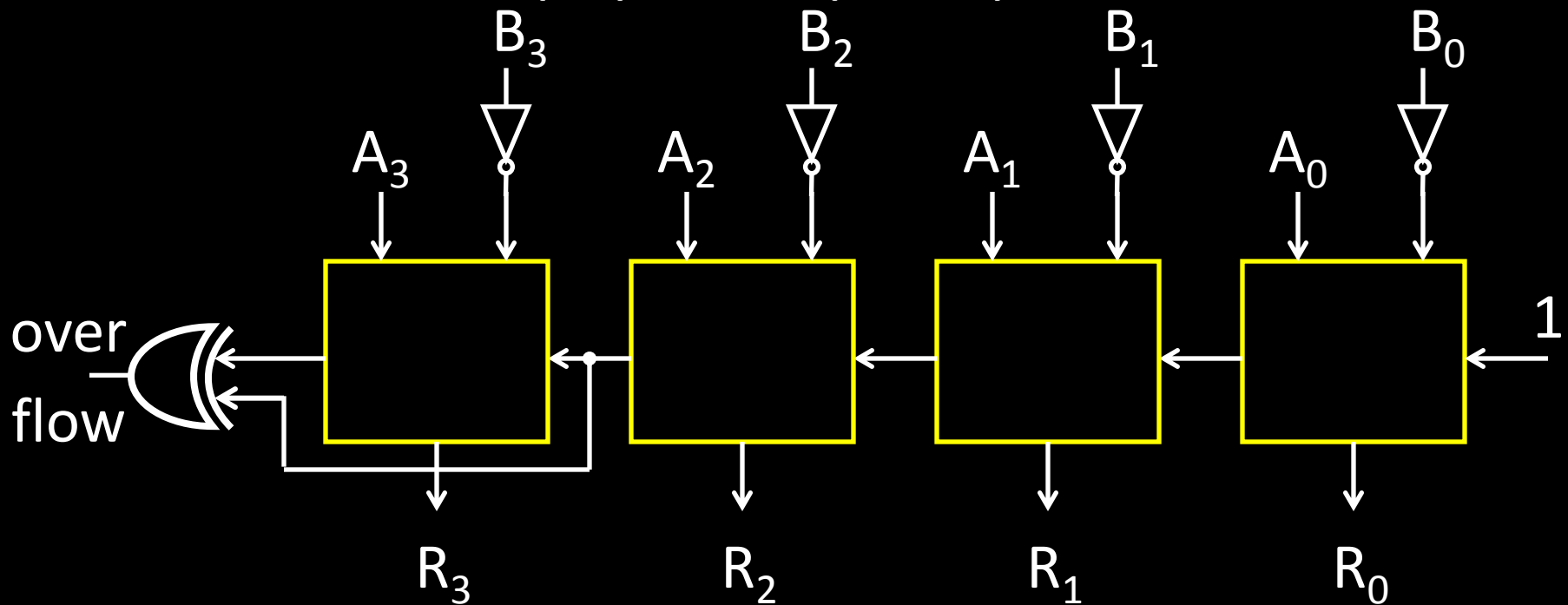- Two's Complement Subtraction
- Lazy approach —
- $A - B = A + (-B) = A + (B + 1)$



Q: What if $(-B)$ overflows?

A Calculator


A $\frac{8}{\text{---}}$

B $\frac{8}{\text{---}}$


S ---

0=add

1=sub

 

A Calculator

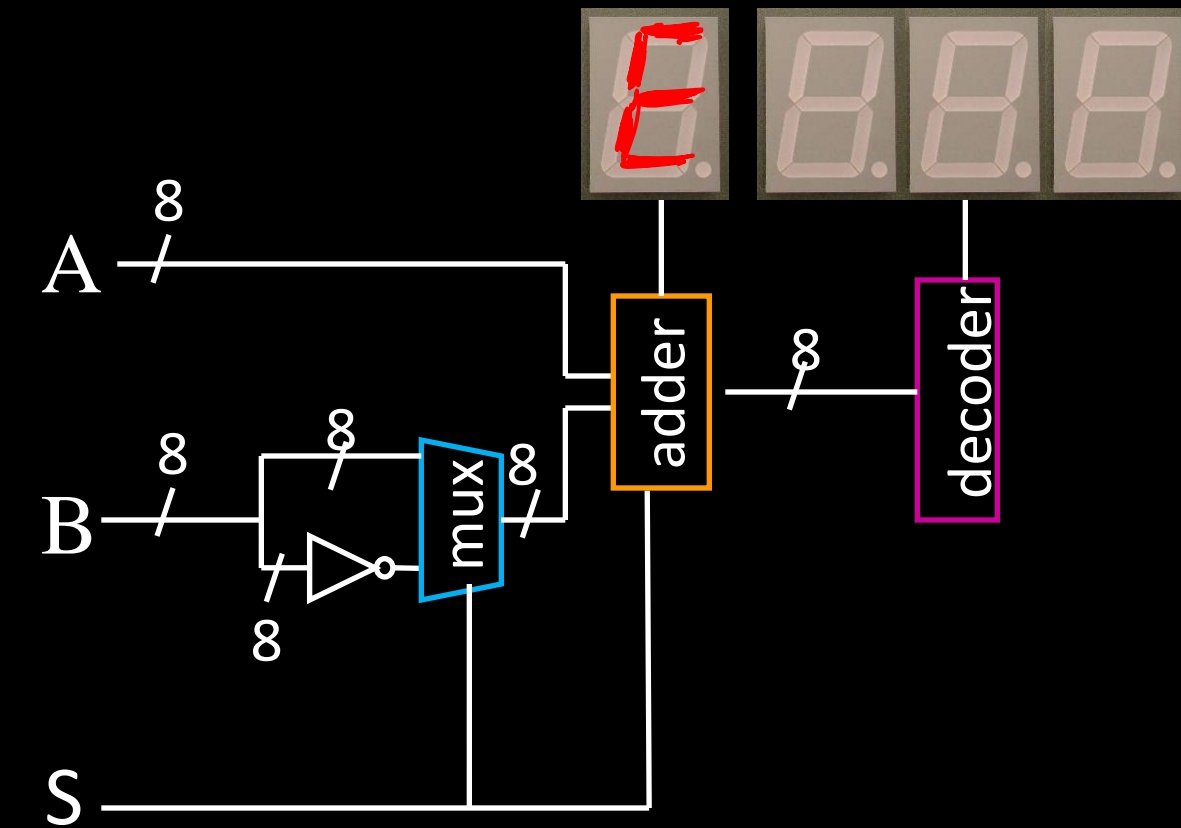


0=add

1=sub


Efficiency and Generality

 - Is this design fast enough?
- Can we generalize to 32 bits? 64? more?




Performance

 - Speed of a circuit is affected by the number of gates in series (on the *critical path* or the *deepest level of logic*)



4-bit Ripple Carry Adder

 

- First full adder, 2 gate delay
- Second full adder, 2 gate delay
- ...

Summary

- We can now implement any combinational (combinatorial) logic circuit
 - Decompose large circuit into manageable blocks
 - Encoders, Decoders, Multiplexors, Adders, ...
 - Design each block
 - Binary encoded numbers for compactness
 - Can implement circuits using NAND or NOR gates
 - Can implement gates using use P- and N-transistors
 - **And can add and subtract numbers (in two's compliment)!**
 - Next time, state and finite state machines...