

# Arithmetic

**Hakim Weatherspoon**

**CS 3410, Spring 2012**

Computer Science

Cornell University

See P&H 2.4 (signed), 2.5, 2.6, C.6, and Appendix C.6

# Goals for today

---

## Binary (Arithmetic) Operations

- One-bit and four-bit adders
- Negative numbers and two's compliment
- Addition (two's compliment)
- Subtraction (two's compliment)
- Performance

# Binary Addition

---

$$\begin{array}{r} 183 \\ + 254 \\ \hline 437 \\ \phantom{00}111 \\ 001110 \\ + 011100 \\ \hline 101010 \end{array}$$


Addition works the same way regardless of base

- Add the digits in each position
- Propagate the carry

Unsigned binary addition is pretty easy

- Combine two bits at a time
- Along with a carry

# 1-bit Adder

 

## Half Adder


- Adds two 1-bit numbers
- Computes 1-bit result and 1-bit carry

$$R = \bar{A}B + A\bar{B}$$

$$C = AB$$

A	B	C	R
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# 1-bit Adder with Carry

 


## Full Adder

- Adds three 1-bit numbers
- Computes 1-bit result and 1-bit carry
- Can be cascaded

A	B	C <sub>in</sub>	C <sub>out</sub>	R
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

# 4-bit Adder


---

 

## 4-Bit Full Adder

- Adds two 4-bit numbers and carry in
- Computes 4-bit result and carry out
- Can be cascaded

# 4-bit Adder

 

- Adds two 4-bit numbers, along with carry-in
- Computes 4-bit result and carry out
- Carry-out = overflow indicates result does not fit in 4 bits

# Arithmetic with Negative Numbers

---

Negative Numbers Complicate Arithmetic

Recall addition with negatives:

$$\underline{0}111 = 7$$

$$\underline{1}111 = -7$$

$$0000 = +0$$

$$1000 = -0$$



# Arithmetic with Negative Numbers

---

Negative Numbers Complicate Arithmetic

Recall addition with negatives:

- $\text{pos} + \text{pos} \rightarrow$  add magnitudes, result positive
- $\text{neg} + \text{neg} \rightarrow$  add magnitudes, result negative
- $\text{pos} + \text{neg} \rightarrow$  subtract smaller magnitude,  
keep sign of bigger magnitude

# First Attempt: Sign/Magnitude Representation

First Attempt: Sign/Magnitude Representation

- 1 bit for sign (0=positive, 1=negative)
- N-1 bits for magnitude

# Two's Complement Representation

## Better: Two's Complement Representation

- Leading 1's for negative numbers

- To negate **any** number:

- complement *all* the bits

- then add 1

$$20 = 0001\ 0100$$

$$\overline{20} = 1110\ 1011$$

$$\begin{array}{r} 6 = 0110 \\ \overline{6} = 1001 \\ \quad \quad \quad +1 \\ -6 = 1010 \end{array} \quad \begin{array}{r} 1110 \\ \hline 1100 \\ \quad \quad \quad +1 \\ = -26 \end{array}$$

# Two's Complement

Non-negatives

(as usual):

$$+0 = 0000$$

$$+1 = 0001$$

$$+2 = 0010$$

$$+3 = 0011$$

$$+4 = 0100$$

$$+5 = 0101$$

$$+6 = 0110$$

$$+7 = 0111$$

$$+8 = 1000$$

Negatives

(two's complement: flip then add 1):

$$1111$$

$$1110$$

$$1101$$

$$1100$$

$$1011$$

⋮

$$0111$$

$[-8, 7]$

$$0000 = 0$$

$$1111 = -1$$

$$1110 = -2$$

$$1101 = -3$$

$$1100 = -4$$

⋮

$$1000 = -8$$

# Two's Complement

---

## Non-negatives

(as usual):

$$+0 = 0000$$

$$+1 = 0001$$

$$+2 = 0010$$

$$+3 = 0011$$

$$+4 = 0100$$

$$+5 = 0101$$

$$+6 = 0110$$

$$+7 = 0111$$

$$+8 = 1000$$

## Negatives

(two's complement: flip then add 1):

$$\sim 0 = 1111$$

$$\sim 1 = 1110$$

$$\sim 2 = 1101$$

$$\sim 3 = 1100$$

$$\sim 4 = 1011$$

$$\sim 5 = 1010$$

$$\sim 6 = 1001$$

$$\sim 7 = 1000$$

$$\sim 8 = 0111$$

$$-0 = 0000$$

$$-1 = 1111$$

$$-2 = 1110$$

$$-3 = 1101$$

$$-4 = 1100$$

$$-5 = 1011$$

$$-6 = 1010$$

$$-7 = 1001$$

$$-8 = 1000$$

# Two's Complement Facts

## Signed two's complement

- Negative numbers have leading 1's
- zero is unique:  $+0 = -0$
- wraps from largest positive to largest negative

## N bits can be used to represent

- unsigned:

– eg: 8 bits  $\Rightarrow$

$$0 - 2^N - 1$$
$$0 - (2^8 - 1) = (256 - 1) = 255$$

- signed (two's complement):

– ex: 8 bits  $\Rightarrow$

$$-\frac{2^N}{2} \dots 0 \dots \left(\frac{2^N}{2}\right) - 1$$
$$-128 \dots \dots \dots 127$$

# Sign Extension & Truncation

---

Extending to larger size

$$1111 = -1$$

$$1111 \ 1111 = -1$$

$$0111 = 7$$

$$0000 \ 0111 = 7$$

Truncate to smaller size

$$~~0000~~ \ 1111 = 15$$

$$1111 = -1$$

# Two's Complement Addition

---

## Addition with two's complement signed numbers

- Perform addition as usual, regardless of sign (it just works)

$$\begin{array}{r} 4 = 0100 \\ 4 = 0100 \\ \hline 1000 \\ \hline \end{array}$$


$$\begin{array}{r} 3 = 0011 \\ 4 = 0100 \\ \hline 7 = 0111 \end{array}$$



# Two's Complement Addition
 
## Addition with two's complement signed numbers

- Perform addition as usual, regardless of sign (it just works)



# Overflow


## Overflow

$$\begin{array}{r}
 0111 - 7 \\
 0011 - 2 \\
 \hline
 1110
 \end{array}$$

- adding a negative and a positive?
- adding two positives?
- adding two negatives?

A	B	C <sub>in</sub>	C <sub>out</sub>	R
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	0	
1	0	0	0	
1	0	1	1	
1	1	0	1	
1	1	1	1	
 
$$\begin{array}{r}
 1000 - 8 \\
 1000 - 8 \\
 \hline
 0000
 \end{array}$$



# Overflow

---

## Overflow


- adding a negative and a positive?
- adding two positives?
- adding two negatives?

## Rule of thumb:

Overflow happened iff  
carry into msb  $\neq$  carry out of msb

# Two's Complement Adder

 
## Two's Complement Adder with overflow detection



# Binary Subtraction

## Two's Complement Subtraction

$$A - B = A + (-B) = A + (\bar{B} + 1)$$

 


# Binary Subtraction

## Two's Complement Subtraction

$A = 3 = 0011$   
 $B = 6 = 0110$   
 $3 - 6 = -3$


$$A - B = A + (-B) = A + (\bar{B} + 1)$$

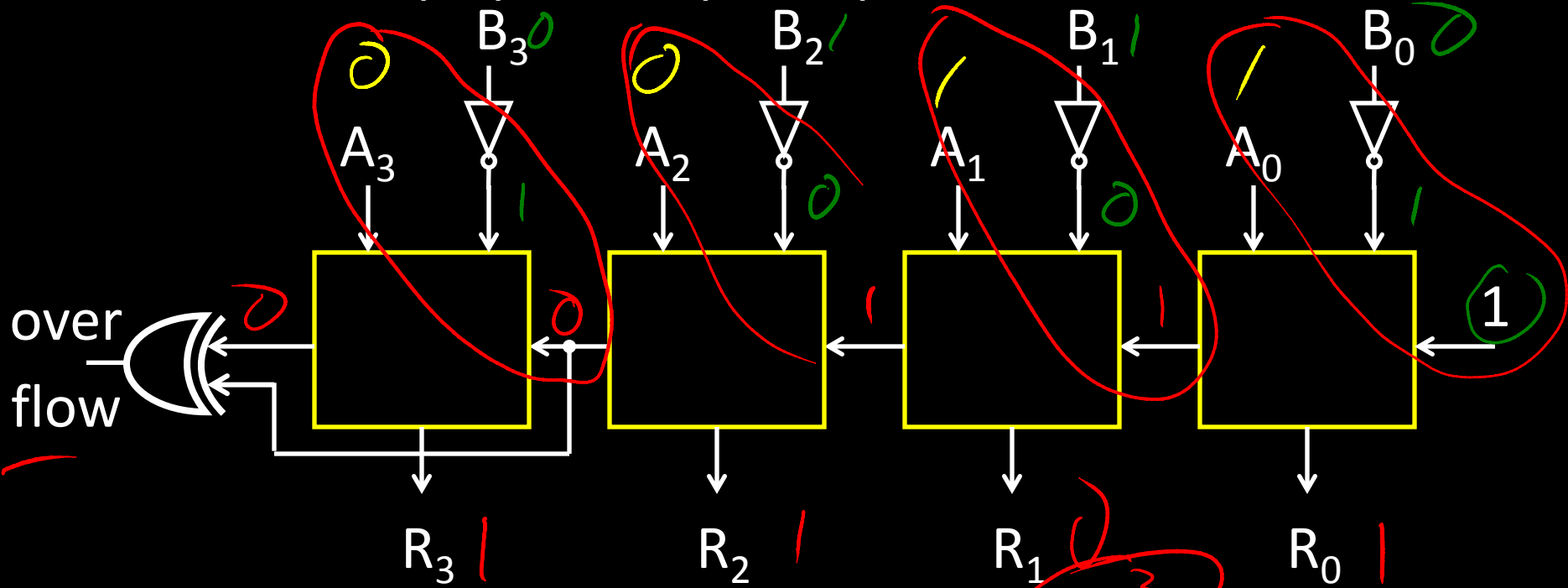


$1101 = -3$   
 $0010$   
 $1101$

Q: What if (-B) overflows?

# A Calculator

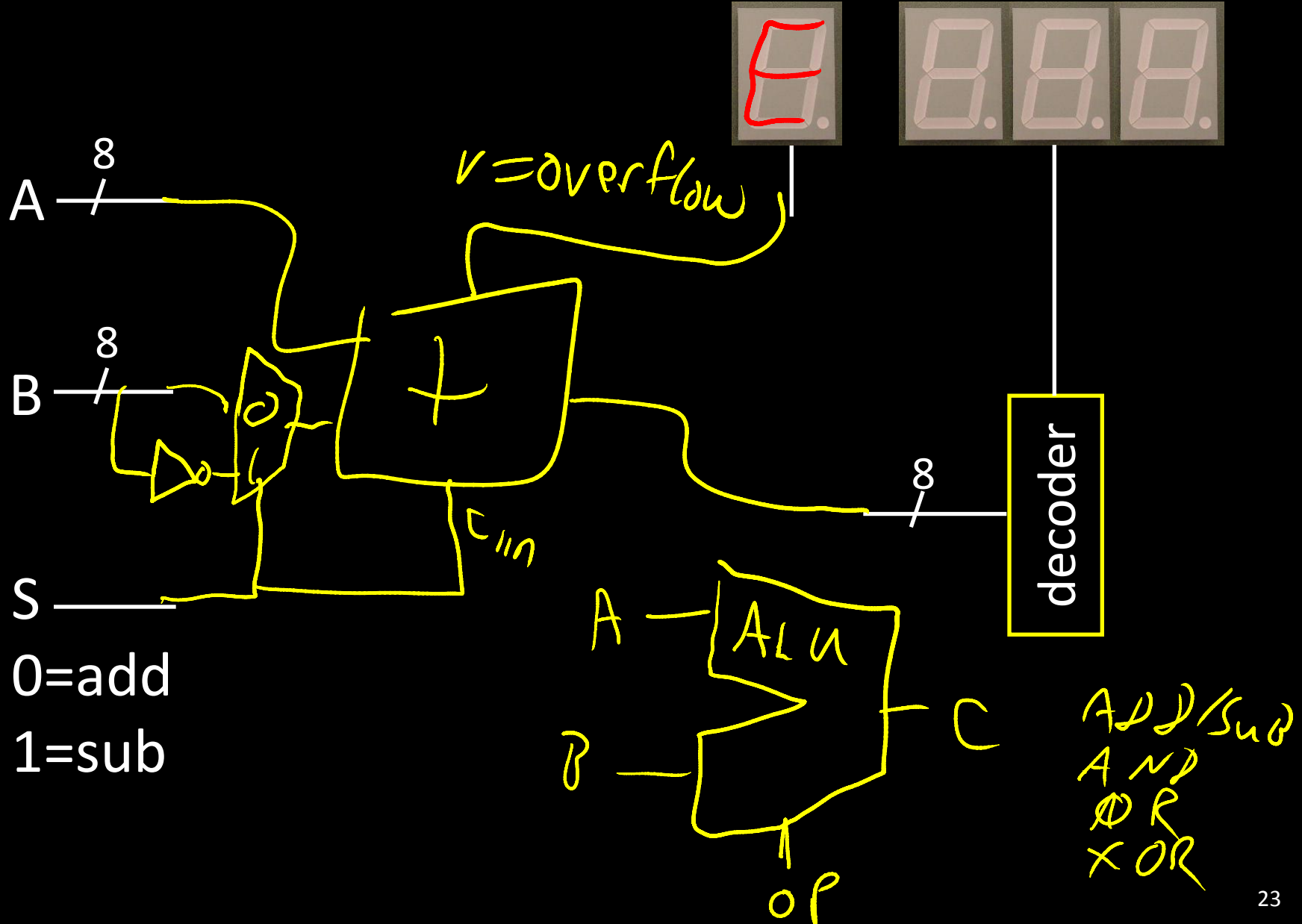

# A Calculator

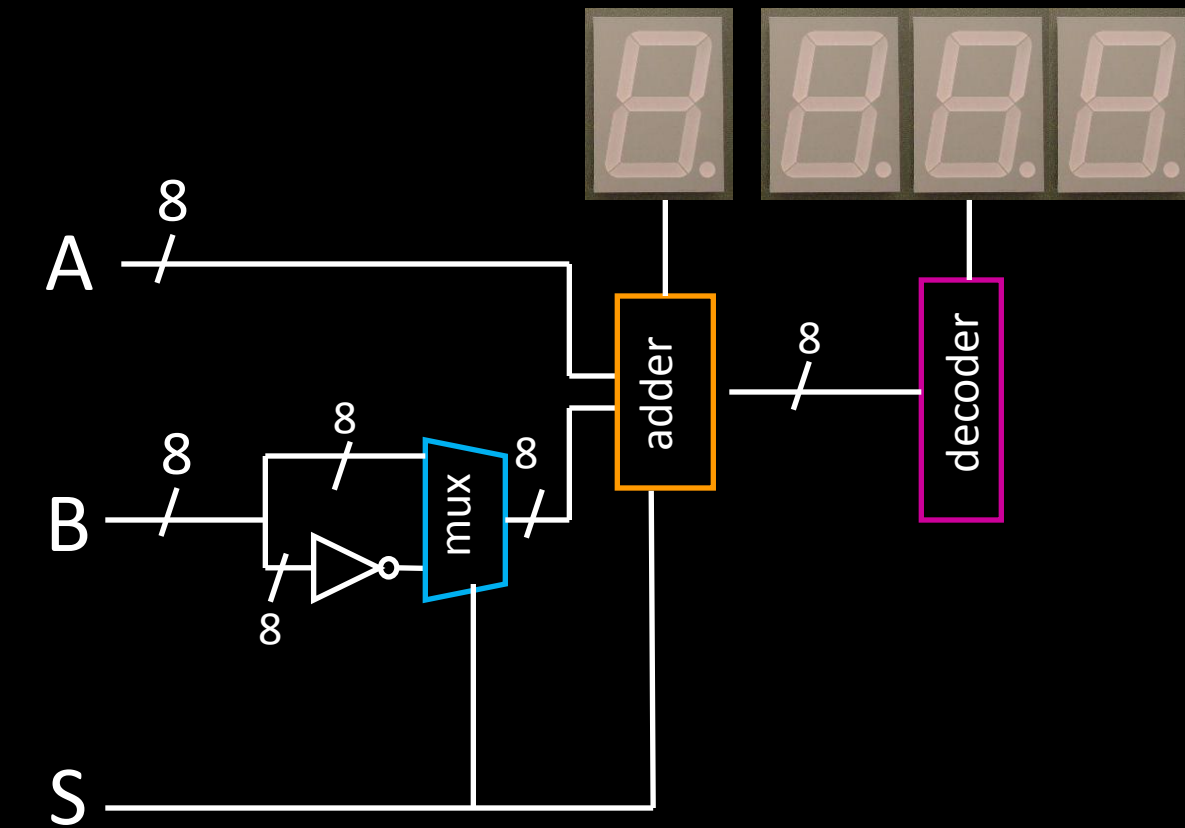


0=add

1=sub



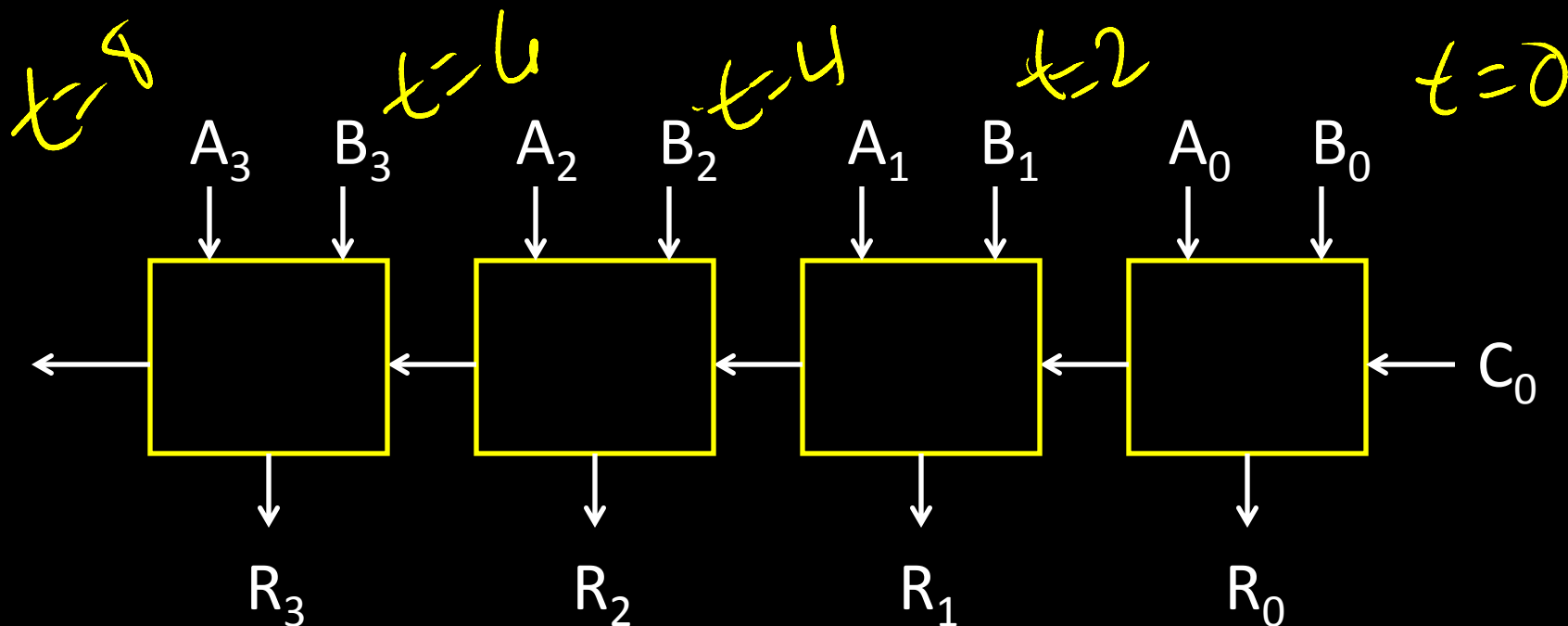
# Efficiency and Generality

- Is this design fast enough?
- Can we generalize to 32 bits? 64? more?



 
# Performance

Speed of a circuit is affected by the number of gates in series (on the *critical path* or the *deepest level of logic*)



# 4-bit Ripple Carry Adder

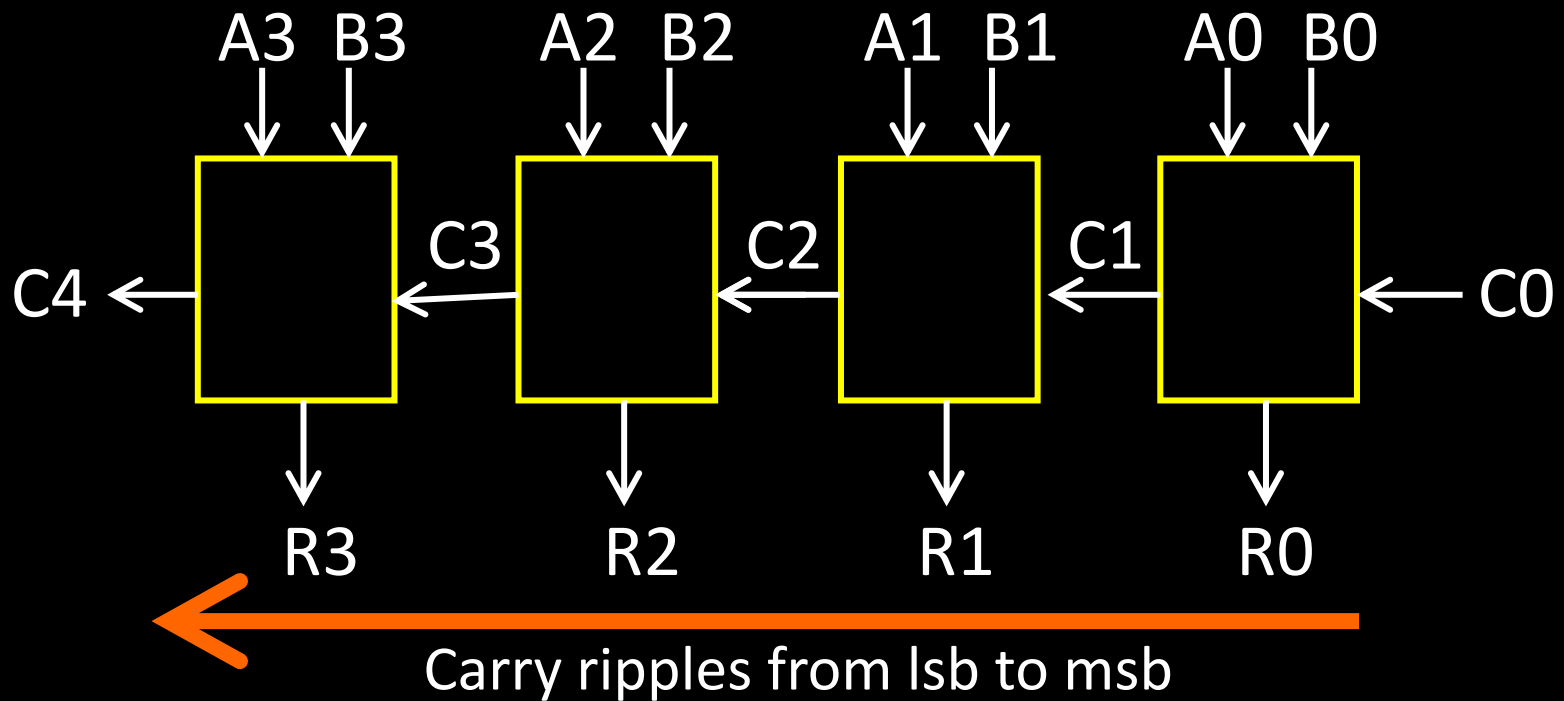


- First full adder, 2 gate delay
- Second full adder, 2 gate delay
- ...



# Critical Path

What is the length of the critical path (in gates)?  
(counting inverters)


- A) 3
- B) 5
- C) 9
- D) 11

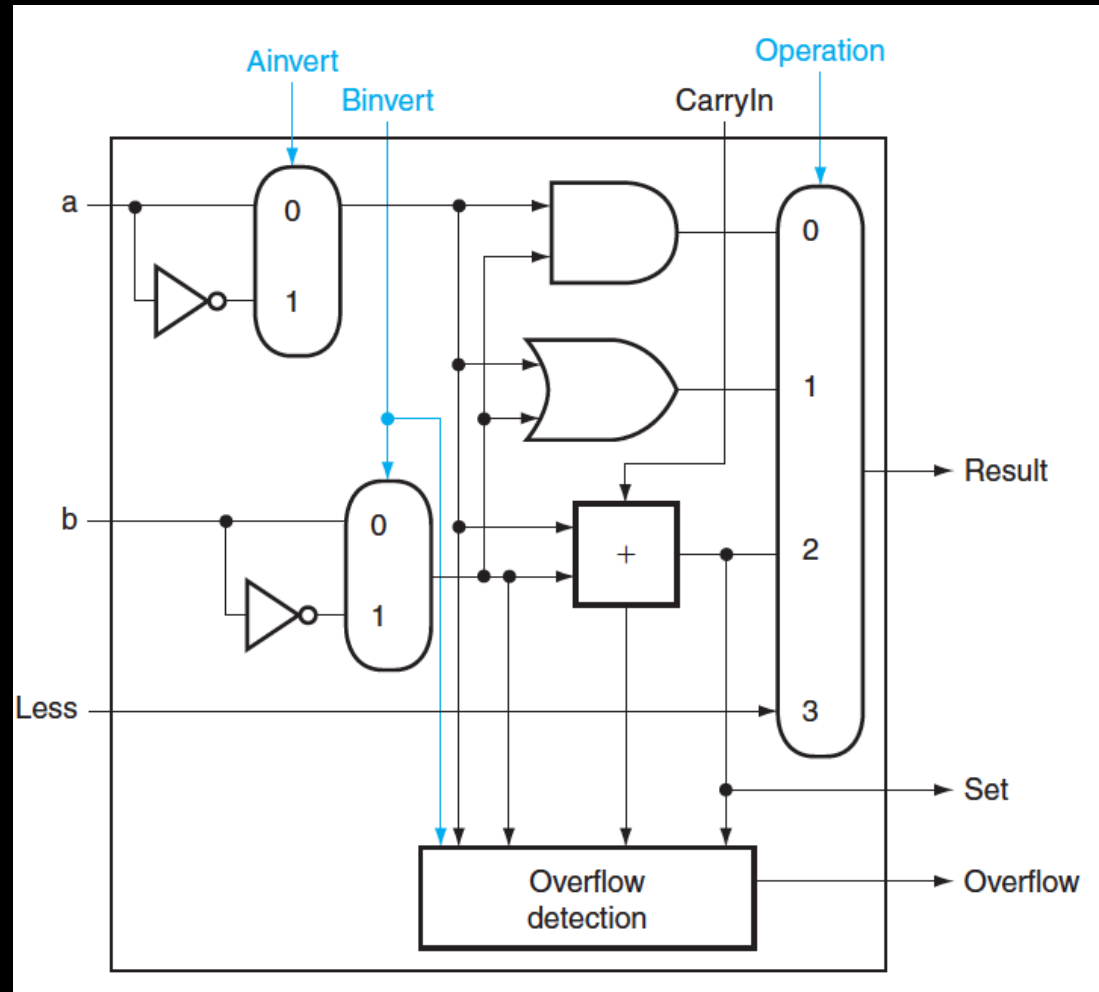

# Critical Path

What is the length of the critical path for a 32-bit ALU (in gates)? (counting inverters)

- A) 11
- B) 32
- C) 64
- D) 71

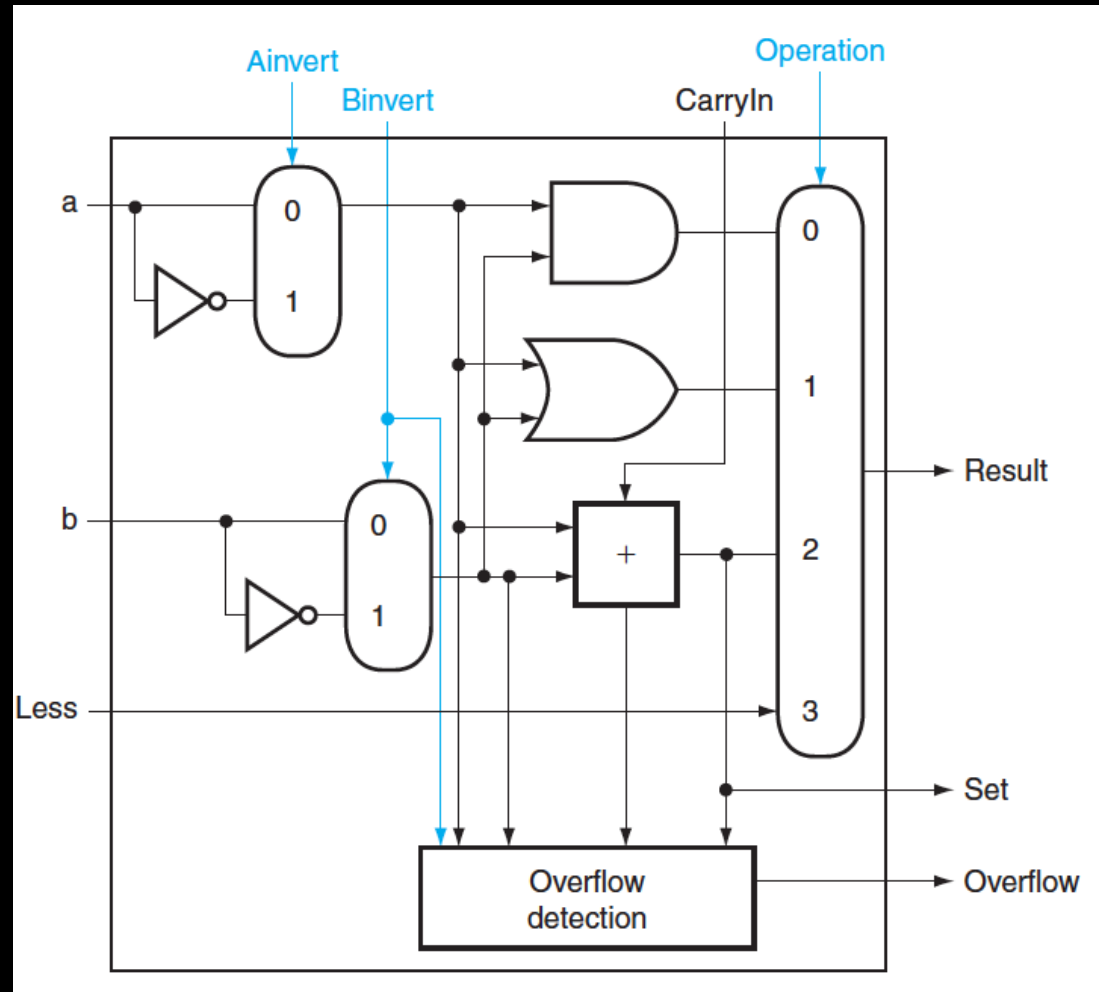

# Recap

---

We can now implement any combinational (combinatorial) logic circuit

- Decompose large circuit into manageable blocks
  - Encoders, Decoders, Multiplexors, Adders, ...
- Design each block
  - Binary encoded numbers for compactness
- Can implement circuits using NAND or NOR gates
- Can implement gates using use P- and N-transistors
- **And can add and subtract numbers (in two's compliment)!**
- Next, state and finite state machines...

# Administrivia

---

Make sure you are

Registered for class, can access CMS

Have a Section you can go to

**Have project partner in same Lab Section**

**Lab1 and HW1 are out**

Both due in one week, next Monday, start early

Work **alone**

**But**, use your resources

- Lab Section, Piazza.com, Office Hours, Homework Help Session,
- Class notes, book, Sections, CSUGLab

**Homework Help Session**

Wednesday and Friday from 3:30-5:30pm

Location: 203 Thurston



# Administrivia

---

Check online syllabus/schedule

- <http://www.cs.cornell.edu/Courses/CS3410/2012sp/schedule.html>

Slides and Reading for lectures

Office Hours

Homework and Programming Assignments

Prelims (in evenings):

- Tuesday, February 28<sup>th</sup>
- Thursday, March 29<sup>th</sup>
- Thursday, April 26<sup>th</sup>


Schedule is subject to change

# Stateful Components

---

Until now is combinatorial logic

 - Output is computed when inputs are present
- System has no internal state
- Nothing computed in the present can depend on what happened in the past!





Need a way to record data

Need a way to build **stateful** circuits

Need a state-holding device


**Finite State Machines**

# How can we store *and* change values?

  


Ballots

 How do we create  
vote counter  
machine




(d) All the above

 

(e) None


# Unstable Devices

---

 



# Bistable Devices

- Stable and unstable equilibria?

 

A Simple Device

- In stable state,  $\bar{A} = B$

  

- How do we change the state?



# SR Latch

## Set-Reset (SR) Latch

Stores a value  $Q$  and its complement  $\bar{Q}$

S	R	Q	$\bar{Q}$
0	0	$Q$	$\bar{Q}$
0	1	0	1
1	0	1	0
1	1		

*hold*

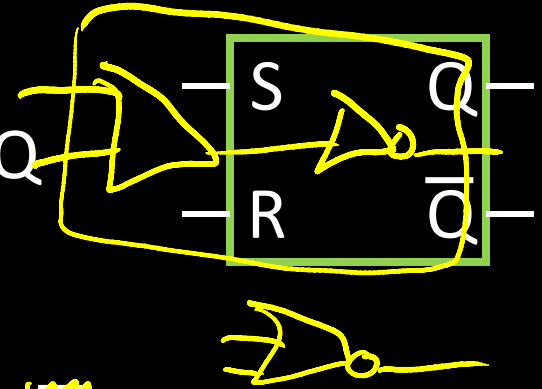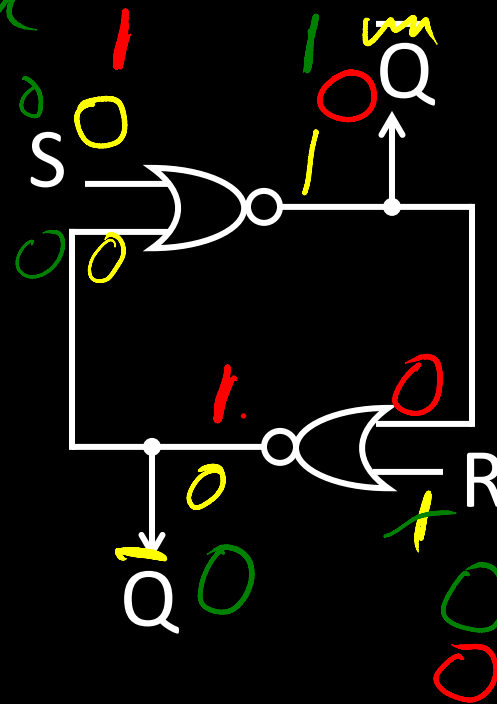


# SR Latch

## Set-Reset (SR) Latch


Stores a value  $Q$  and its complement  $\bar{Q}$

S	R	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	0	1
1	0	1	0
1	1	forbidden	

hold

 


$S, R = 0, 0$

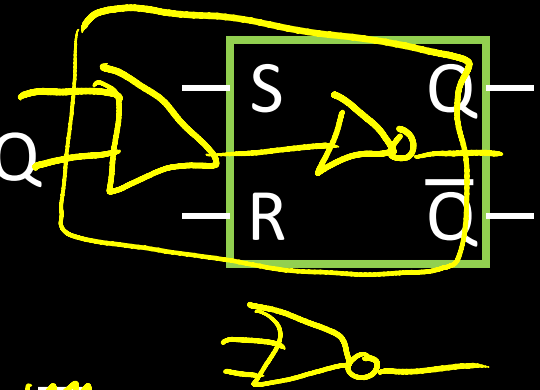

# Unclocked D Latch

## Data (D) Latch

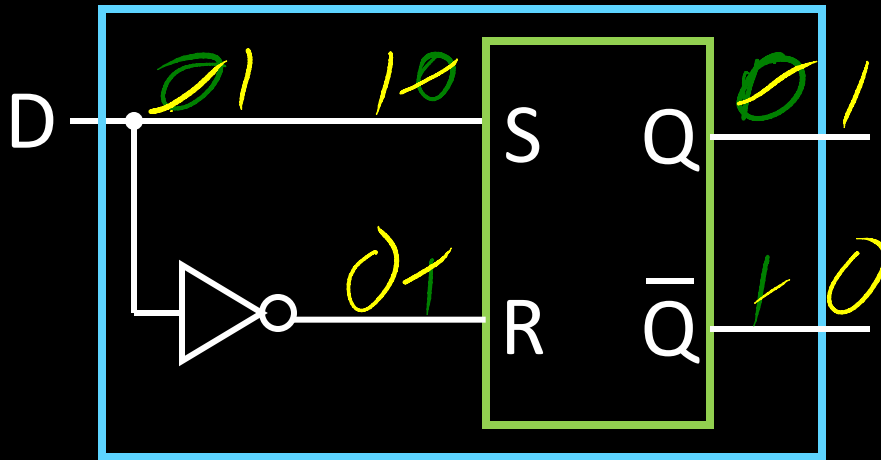


D	Q	$\bar{Q}$
0	0	1
1	1	0



# Unclocked D Latch

## Data (D) Latch

 

D	Q	$\bar{Q}$
0	0	1
1	1	0

## Data Latch

- Easier to use than an SR latch
- No possibility of entering an undefined state

When D changes, Q changes

– ... immediately (after a delay of 2 Ors and 2 NOTs)

Need to control when the output changes

# D Latch with Clock



## Level Sensitive D Latch

Clock high:


set/reset (according to D)

Clock low:

keep state (ignore D)

 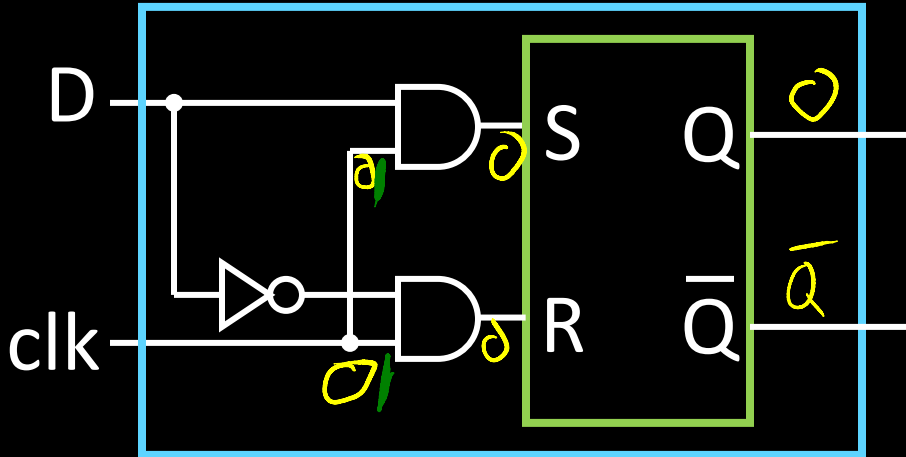

# D Latch with Clock

 


D	Q	$\bar{Q}$
0	0	1
1	1	0


S	R	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	0	1
1	0	1	0
1	1	forbidden	

clk	D	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	Q	$\bar{Q}$
1	0	0	1
1	1	1	0

# D Latch with Clock

 

D	Q	$\bar{Q}$
0	0	1
1	1	0

 


clk	D	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	Q	$\bar{Q}$
1	0	0	1
1	1	1	0

# Clocks

---



**Clock** helps coordinate state changes

 
- Usually generated by an oscillating crystal
- Fixed period; frequency =  $1/\text{period}$


 
# Edge-triggering

---


- Can design circuits to change on the rising or falling edge
- Trigger on rising edge = positive edge-triggered 
- Trigger on falling edge = negative edge-triggered 
- Inputs must be stable just before the triggering edge



# Clock Methodology

## Clock Methodology


- Negative edge, synchronous

 

– Signals must be stable near falling clock edge


- Positive edge synchronous
- Asynchronous, multiple clocks, . . .

# Edge-Triggered D Flip-Flop

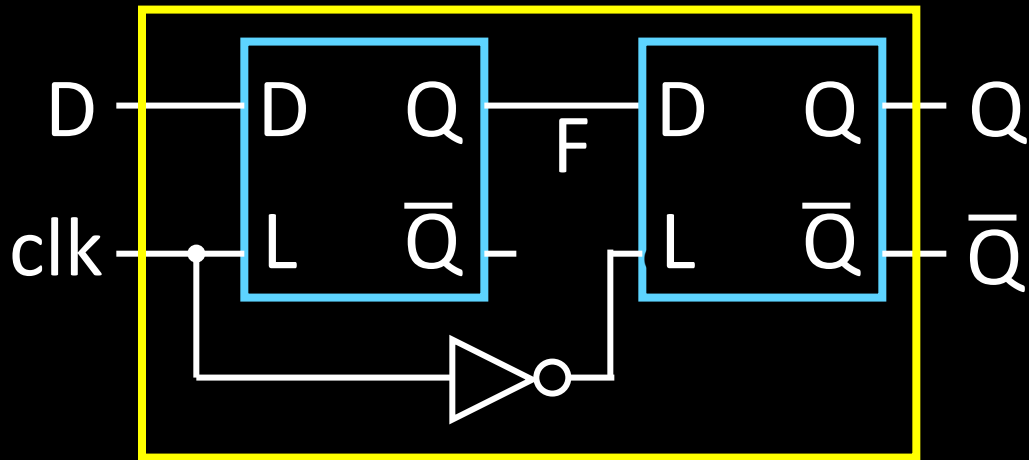
 
## D Flip-Flop

- Edge-Triggered
- Data is captured when clock is high
- Outputs change only on falling edges





# Clock Disciplines

---

## Level sensitive

- State changes when clock is high (or low)


## Edge triggered

- State changes at clock edge

positive edge-triggered





negative edge-triggered

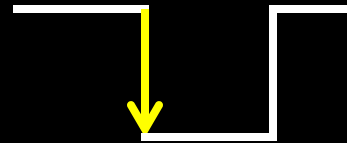

# Registers
 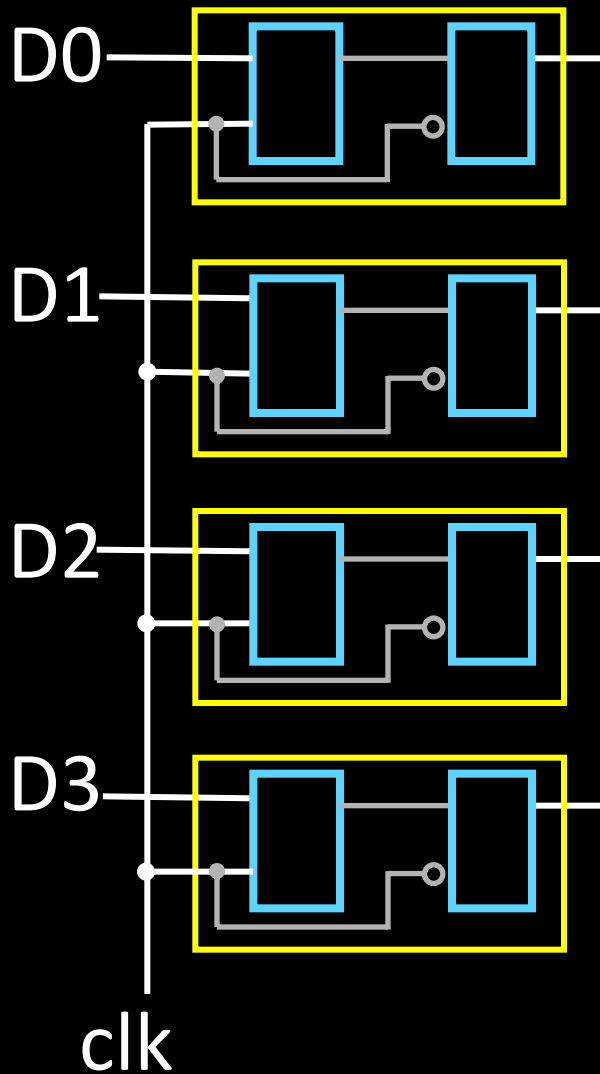
## Register

- D flip-flops in parallel
- shared clock
- extra clocked inputs: write\_enable, reset, ...



# An Example: What will this circuit do?

