



# Gates and Logic: From switches to Transistors, Logic Gates and Logic Circuits

**Prof. Kavita Bala and Prof. Hakim Weatherspoon**

**CS 3410, Spring 2014**

Computer Science

Cornell University


See: P&H Appendix B.2 and B.3 (Also, see B.1)

# Goals for Today

From Switches to Logic Gates to Logic Circuits

Understanding the foundations of

 Computer Systems Organization and Programming




# Goals for Today

From Switches to Logic Gates to Logic Circuits

Understanding the foundations of

Computer Systems Organization and Programming

e.g. Galaxy Note 3

 

# Goals for Today


From Switches to Logic Gates to Logic Circuits

Understanding the foundations of

Computer Systems Organization and Programming

e.g. Galaxy Note 3

with the big.LITTLE 8-core ARM processor

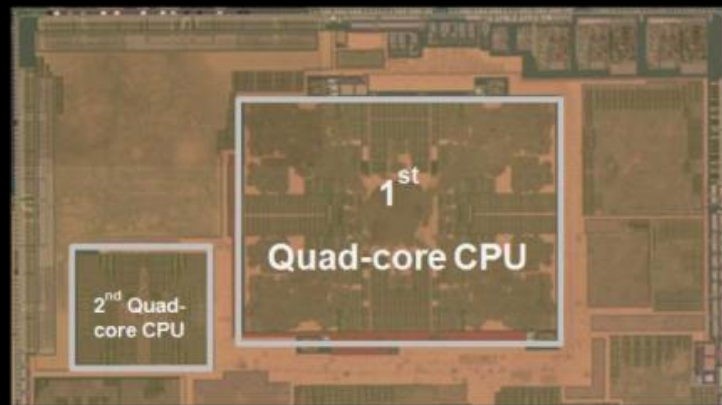

# Goals for Today

From Switches to Logic Gates to Logic Circuits

Understanding the foundations of

Computer Systems Organization and Programming

e.g. Galaxy Note 3

with the big.LITTLE 8-core ARM processor

	big Quad Core	LITTLE Quad Core
Architecture	ARM v7a	ARM v7a
Process	Samsung 28nm	Samsung 28nm
Frequency	200MHz~1.8GHz+	200MHz~1.2GHz
Area	19mm <sup>2</sup>	3.8mm <sup>2</sup>
Power-ratio	1	0.17
L1 Cache Size	32 KB I/D Cache	32 KB I/D Cache
L2 Cache Size	2 MB Data Cache	512 KB Data Cache

# Goals for Today

From Switches to Logic Gates to Logic Circuits

Logic Gates

- From switches
- Truth Tables

Logic Circuits

- Identity Laws
- From Truth Tables to Circuits (Sum of Products)

Logic Circuit Minimization



- Algebraic Manipulations
- Truth Tables (Karnaugh Maps)

Transistors (electronic switch)
  
# A switch




- Acts as a *conductor* or *insulator*
- Can be used to build amazing things...



The Bombe used to break the German Enigma machine during World War II
 
# Basic Building Blocks: Switches to Logic Gates




Truth Table

A	B	Light
OFF	OFF	
OFF	ON	
ON	OFF	
ON	ON	


 
# Basic Building Blocks: Switches to Logic Gates




Truth Table

A	B	Light
OFF	OFF	OFF
OFF	ON	ON
ON	OFF	ON
ON	ON	ON

A	B	Light
OFF	OFF	
OFF	ON	
ON	OFF	
ON	ON	

 
# Basic Building Blocks: Switches to Logic Gates



Either (OR)

Truth Table

A	B	Light
OFF	OFF	OFF
OFF	ON	ON
ON	OFF	ON
ON	ON	ON

 

Both (AND)

A	B	Light
OFF	OFF	OFF
OFF	ON	OFF
ON	OFF	OFF
ON	ON	ON

# Basic Building Blocks: Switches to Logic Gates



Either (OR)

Truth Table


A	B	Light
OFF	OFF	OFF
OFF	ON	ON
ON	OFF	ON
ON	ON	ON

Both (AND)

A	B	Light
OFF	OFF	OFF
OFF	ON	OFF
ON	OFF	OFF
ON	ON	ON

  
 
# Basic Building Blocks: Switches to Logic Gates




Either (OR)

Truth Table

A	B	Light
0	0	0
0	1	1
1	0	1
1	1	1



0 = OFF  
1 = ON

 


Both (AND)

A	B	Light
0	0	0
0	1	0
1	0	0
1	1	1
  
# Basic Building Blocks: Switches to Logic Gates



**George Boole, (1815-1864)**

 

**Did you know?**


**George Boole** Inventor of the idea of logic gates. He was born in Lincoln, England and he was the son of a shoemaker in a low class family.

# Takeaway

Binary (two symbols: true and false) is the basis of Logic Design


# Building Functions: Logic Gates

NOT:

 


A	Out

AND:

 

A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1

OR:

 

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1

## Logic Gates


- digital circuit that either allows a signal to pass through it or not.
- Used to build logic functions
- There are seven basic logic gates:

**AND**, **OR**, **NOT**,

**NAND** (not AND), **NOR** (not OR), **XOR**, and **XNOR** (not XOR) [later]


# Building Functions: Logic Gates

NOT:

 


A	Out
0	1
1	0

AND:

 

A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1

OR:

 

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1

## Logic Gates

- digital circuit that either allows a signal to pass through it or not.
- Used to build logic functions
- There are seven basic logic gates:


**AND**, **OR**, **NOT**,

**NAND** (not AND), **NOR** (not OR), **XOR**, and **XNOR** (not XOR) [later]




# Building Functions: Logic Gates

NOT:

 


A	Out
0	1
1	0

AND:

 


A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1

NAND:

 


A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

OR:

 

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1

NOR:

 

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

## Logic Gates

- digital circuit that either allows a signal to pass through it or not.
- Used to build logic functions
- There are seven basic logic gates:

AND, OR, NOT,


NAND (not AND), NOR (not OR), XOR, and XNOR (not XOR) [later]

# Activity#1: Logic Gates

Fill in the truth table, given the following Logic Circuit made from Logic AND, OR, and NOT gates.

What does the logic circuit do?

a	b	Out

 


# Activity#1: Logic Gates

XOR: out = 1 if a or b is 1, but not both;  
out = 0 otherwise.

out = 1, only if a = 1 AND b = 0

OR a = 0 AND b = 1

a	b	Out
0	0	0
0	1	1
1	0	1
1	1	0

 


# Activity#1: Logic Gates

XOR: out = 1 if a or b is 1, but not both;  
out = 0 otherwise.

out = 1, only if a = 1 AND b = 0

OR a = 0 AND b = 1

a	b	Out
0	0	0
0	1	1
1	0	1
1	1	0

 


## Activity#2: Logic Gates

Fill in the truth table, given the following Logic Circuit made from Logic AND, OR, and NOT gates.

What does the logic circuit do?

a	b	d	Out
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

 


# Activity#2: Logic Gates

**Multiplexor:** select (**d**) between two inputs (**a** and **b**) and set one as the output (**out**)?

**out** = **a**, if **d** = 0

**out** = **b**, if **d** = 1

a	b	d	Out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

 

# Goals for Today

From Switches to Logic Gates to Logic Circuits

Logic Gates

- From switches
- Truth Tables

Logic Circuits

- Identity Laws
- From Truth Tables to Circuits (Sum of Products)

Logic Circuit Minimization

- Algebraic Manipulations
- Truth Tables (Karnaugh Maps)

Transistors (electronic switch)

## Next Goal

Given a Logic function, create a Logic Circuit that implements the Logic Function...


...and, *with the minimum number of logic gates*

Fewer gates: A cheaper (\$\$\$) circuit!




# Logic Gates

NOT:

 


A	Out
0	1
1	0

AND:

 


A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1

OR:

 

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1


XOR:

 

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0


# Logic Gates

NOT:

 


A	Out
0	1
1	0

AND:

 


A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1

NAND:

 


A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

OR:

 

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1

NOR:

 


A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

XOR:



A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0

XNOR:

 

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	1

# Logic Equations

NOT:

- $\text{out} = \bar{a} = !a = \neg a$

AND:

- $\text{out} = a \cdot b = a \& b = a \wedge b$

OR:

- $\text{out} = a + b = a \mid b = a \vee b$

XOR:

- $\text{out} = a \oplus b = a\bar{b} + \bar{a}b$

## Logic Equations

- Constants: true = 1, false = 0
- Variables: a, b, out, ...
- Operators (above): AND, OR, NOT, etc.

# Logic Equations

NOT:

- $\text{out} = \bar{a} = !a = \neg a$

AND:

- $\text{out} = a \cdot b = a \& b = a \wedge b$

NAND:

- $\text{out} = \overline{a \cdot b} = !(a \& b) = \neg (a \wedge b)$

OR:

- $\text{out} = a + b = a | b = a \vee b$

NOR:

- $\text{out} = \overline{a + b} = !(a | b) = \neg (a \vee b)$

XOR:

- $\text{out} = a \oplus b = a\bar{b} + \bar{a}b$

XNOR:

- $\text{out} = \overline{a \oplus b} = ab + \bar{a}\bar{b}$

## Logic Equations

- Constants: true = 1, false = 0
- Variables: a, b, out, ...
- Operators (above): AND, OR, NOT, etc.

# Identities

Identities useful for manipulating logic equations

— For optimization & ease of implementation

$$a + 0 =$$

$$a + 1 =$$

$$a + \bar{a} =$$

$$a \cdot 0 =$$

$$a \cdot 1 =$$

$$a \cdot \bar{a} =$$

# Identities

Identities useful for manipulating logic equations

– For optimization & ease of implementation

$$a + 0 = a$$



$$a + 1 = 1$$

$$a + \bar{a} = 1$$

$$a \cdot 0 = 0$$

$$a \cdot 1 = a$$

$$a \cdot \bar{a} = 0$$

  

# Identities

Identities useful for manipulating logic equations

- For optimization & ease of implementation

$$\overline{(a + b)} =$$

$$\overline{(a \cdot b)} =$$

$$a + a b =$$

$$a(b+c) =$$

$$\overline{a(b + c)} =$$

# Identities


Identities useful for manipulating logic equations

- For optimization & ease of implementation

$$\overline{(a + b)} = \bar{a} \cdot \bar{b}$$


 
$$\overline{(a \cdot b)} = \bar{a} + \bar{b}$$



$$a + a \cdot b = a$$

$$a(b+c) = ab + ac$$

$$\overline{a(b + c)} = \bar{a} + \bar{b} \cdot \bar{c}$$



## Activity #2: Identities

$$a + 0 = a$$

$$a + 1 = 1$$

$$a + \bar{a} = 1$$

$$a 0 = 0$$

$$a 1 = a$$

$$a \bar{a} = 0$$

$$\overline{(a + b)} = \bar{a} \bar{b}$$

$$\overline{(a b)} = \bar{a} + \bar{b}$$

$$a + a b = a$$

$$a(b+c) = ab + ac$$

$$\overline{a(b + c)} = \bar{a} + \bar{b} \cdot \bar{c}$$

Show that the Logic equations below are equivalent.

$$(a+b)(a+c) = a + bc$$

$$(a+b)(a+c) =$$

## Activity #2: Identities

$$a + 0 = a$$

$$a + 1 = 1$$

$$a + \bar{a} = 1$$

$$a 0 = 0$$

$$a 1 = a$$

$$a \bar{a} = 0$$

$$\overline{(a + b)} = \bar{a} \bar{b}$$

$$\overline{(a b)} = \bar{a} + \bar{b}$$

$$a + a b = a$$

$$a(b+c) = ab + ac$$

$$\overline{a(b + c)} = \bar{a} + \overline{bc}$$

Show that the Logic equations below are equivalent.

$$(a+b)(a+c) = a + bc$$

$$\begin{aligned}(a+b)(a+c) &= aa + ab + ac + bc \\ &= a + a(b+c) + bc \\ &= a(1 + (b+c)) + bc \\ &= a + bc\end{aligned}$$

# Logic Manipulation


- functions: gates  $\leftrightarrow$  truth tables  $\leftrightarrow$  equations
- Example:  $(a+b)(a+c) = a + bc$

a	b	c					
0	0	0					
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

# Logic Manipulation

- functions: gates  $\leftrightarrow$  truth tables  $\leftrightarrow$  equations
- Example:  $(a+b)(a+c) = a + bc$

a	b	c	a+b	a+c	LHS	bc	RHS
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

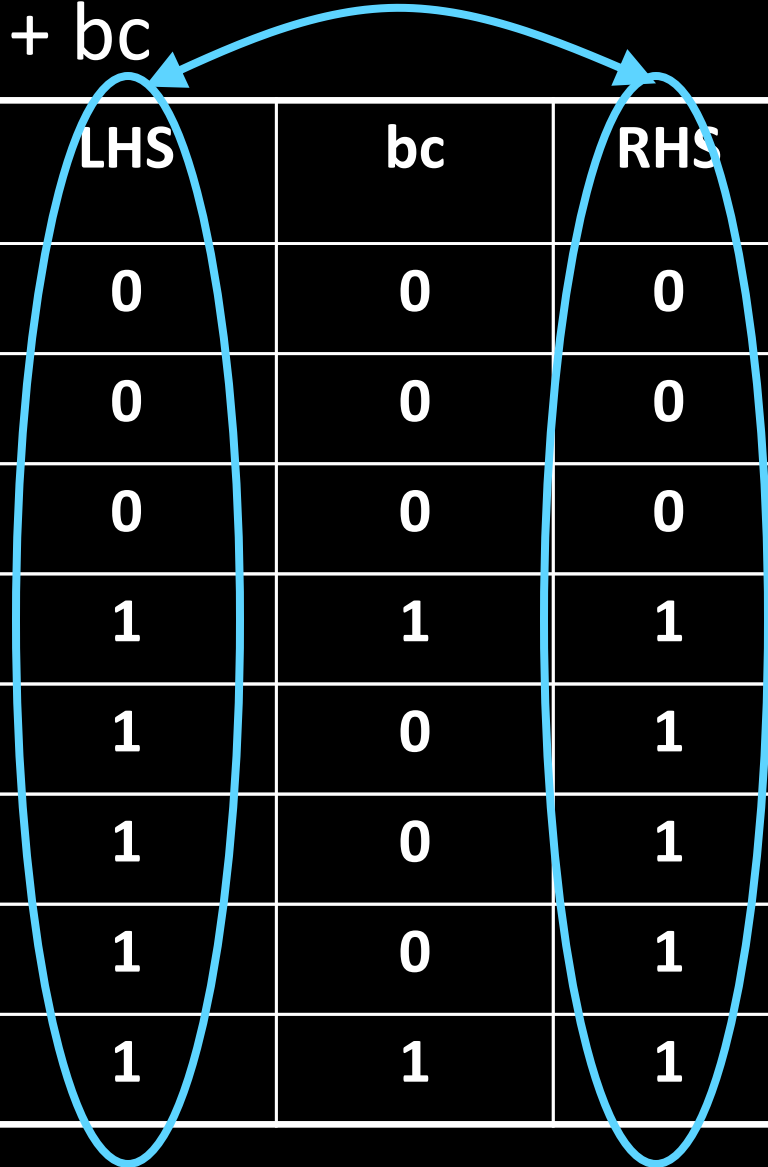

# Takeaway

Binary (two symbols: true and false) is the basis of Logic Design

More than one Logic Circuit can implement same Logic function. Use Algebra (Identities) or Truth Tables to show equivalence.



# Goals for Today

From Switches to Logic Gates to Logic Circuits

Logic Gates

- From switches
- Truth Tables

Logic Circuits

- Identity Laws
- From Truth Tables to Circuits (Sum of Products)

Logic Circuit Minimization

- Algebraic Manipulations
- Truth Tables (Karnaugh Maps)

Transistors (electronic switch)

# Next Goal

How to standardize minimizing logic circuits?



# Logic Minimization

How to implement a desired logic function?

a	b	c	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

# Logic Minimization

How to implement a desired logic function?

a	b	c	out	minterm
0	0	0	0	$\bar{a} \bar{b} \bar{c}$
0	0	1	1	$\bar{a} \bar{b} c$
0	1	0	0	$\bar{a} b \bar{c}$
0	1	1	1	$\bar{a} b c$
1	0	0	0	$a \bar{b} \bar{c}$
1	0	1	1	$a \bar{b} c$
1	1	0	0	$a b \bar{c}$
1	1	1	0	$a b c$

1) Write minterms

2) sum of products:

- OR of all minterms where out=1

# Logic Minimization

How to implement a desired logic function?


a	b	c	out	minterm
0	0	0	0	$\bar{a} \bar{b} \bar{c}$
0	0	1	1	$\bar{a} \bar{b} c$
0	1	0	0	$\bar{a} b \bar{c}$
0	1	1	1	$\bar{a} b c$
1	0	0	0	$a \bar{b} \bar{c}$
1	0	1	1	$a \bar{b} c$
1	1	0	0	$a b \bar{c}$
1	1	1	0	$a b c$

1) Write minterms

 2) sum of products:

- OR of all minterms where out=1

- E.g.  $out = \bar{a} \bar{b} c + \bar{a} b c + a \bar{b} c$



corollary: *any* combinational circuit *can be* implemented in two levels of logic (ignoring inverters)

# Karnaugh Maps

How does one find the most efficient equation?

- Manipulate algebraically until...?
- Use Karnaugh maps (optimize visually)
- Use a software optimizer

For large circuits

- Decomposition & reuse of building blocks

# Minimization with Karnaugh maps (1)

◆ Sum of minterms yields

■ out =

a	b	c	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

# Minimization with Karnaugh maps (2)

◆ Sum of minterms yields

■  $out = \overline{a}bc + a\overline{b}c + a\overline{b}\overline{c} + a\overline{b}c$

a	b	c	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

◆ Karnaugh maps identify which inputs are (ir)relevant to the output

		ab			
		00	01	11	10
c	0				
	1				

# Minimization with Karnaugh maps (2)

◆ Sum of minterms yields

■  $out = \overline{a}bc + a\overline{b}c + a\overline{b}\overline{c} + a\overline{b}c$

◆ Karnaugh maps identify which inputs are (ir)relevant to the output

a	b	c	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

		ab			
		00	01	11	10
c	0	0	0	0	1
	1	1	1	0	1

# Minimization with Karnaugh maps (2)

a	b	c	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

		ab			
		00	01	11	10
c	0	0	0	0	1
	1	1	1	0	1

◆ Sum of minterms yields

- $out = \overline{a}bc + \overline{a}bc + \overline{a}bc + \overline{a}bc$

◆ Karnaugh map minimization

- Cover all 1's
- Group adjacent blocks of  $2^n$  1's that yield a rectangular shape
- Encode the common features of the rectangle

◆  $out =$



# Karnaugh Minimization Tricks (1)

		ab			
c		00	01	11	10
	0	0	1	1	1
	1	0	0	1	0

◆ Minterms can overlap

■ out =

		ab			
c		00	01	11	10
	0	1	1	1	1
	1	0	0	1	0

◆ Minterms can span 2, 4, 8 or more cells

■ out =

# Karnaugh Minimization Tricks (1)

		ab			
c		00	01	11	10
	0	0	1	1	1
	1	0	0	1	0

◆ Minterms can overlap

■  $out = b\bar{c} + a\bar{c} + ab$

		ab			
c		00	01	11	10
	0	1	1	1	1
	1	0	0	1	0

◆ Minterms can span 2, 4, 8 or more cells

■  $out = \bar{c} + ab$

# Karnaugh Minimization Tricks (2)

		ab			
cd	00	00	01	11	10
	00	0	0	0	0
	01	1	0	0	1
	11	1	0	0	1
	10	0	0	0	0

The map wraps around

- out =

		ab			
cd	00	00	01	11	10
	00	1	0	0	1
	01	0	0	0	0
	11	0	0	0	0
	10	1	0	0	1

# Karnaugh Minimization Tricks (2)

		ab			
cd		00	01	11	10
	00	0	0	0	0
01	1	0	0	1	
11	1	0	0	1	
10	0	0	0	0	

The map wraps around

- $out = \bar{b}d$

		ab			
cd		00	01	11	10
	00	1	0	0	1
01	0	0	0	0	0
11	0	0	0	0	0
10	1	0	0	1	

- $out = \bar{b} \bar{d}$

# Karnaugh Minimization Tricks (3)

		ab			
cd		00	01	11	10
		0	0	0	0
00		0	0	0	0
01		1	x	x	x
11		1	x	x	1
10		0	0	0	0

“Don’t care” values can be interpreted individually in whatever way is convenient

- assume all x’s = 1

• out =

		ab			
cd		00	01	11	10
		1	0	0	x
00		1	0	0	x
01		0	x	x	0
11		0	x	x	0
10		1	0	0	1

- assume middle x’s = 0

- assume 4<sup>th</sup> column x = 1

• out =

# Karnaugh Minimization Tricks (3)

		ab			
cd		00	01	11	10
		0	0	0	0
00		0	0	0	0
01		1	x	x	x
11		1	x	x	1
10		0	0	0	0


“Don’t care” values can be interpreted individually in whatever way is convenient

- assume all x’s = 1
- $out = d$

		ab			
cd		00	01	11	10
		1	0	0	x
00		1	0	0	x
01		0	x	x	0
11		0	x	x	0
10		1	0	0	1

- assume middle x’s = 0
- assume 4<sup>th</sup> column x = 1
- $out = \bar{b} \bar{d}$

# Multiplexer

 

A multiplexer selects between multiple inputs

- $\text{out} = a$ , if  $d = 0$
- $\text{out} = b$ , if  $d = 1$


a	b	d	out
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Build truth table

Minimize diagram

Derive logic diagram

# Multiplexer Implementation

 


- Build a truth table

$$\text{out} = \bar{a}bd + a\bar{b}\bar{d} + ab\bar{d} + abd$$

a	b	d	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1



# Multiplexer Implementation

 


- Build the Karnaugh map

a	b	d	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

d \ ab	00	01	11	10
0				
1				

# Multiplexer Implementation

 


- Build the Karnaugh map

a	b	d	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

d \ ab	00	01	11	10
	0	1	1	0
0	0	0	1	1
1	0	1	1	0

# Multiplexer Implementation

 


a	b	d	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

- Derive Minimal Logic Equation

	ab			
d	00	01	11	10
0	0	0	1	1
1	0	1	1	0

- $out = a\bar{d} + bd$

 

# Takeaway

Binary (two symbols: true and false) is the basis of Logic Design

More than one Logic Circuit can implement same Logic function. Use Algebra (Identities) or Truth Tables to show equivalence.

Any logic function can be implemented as “sum of products”. Karnaugh Maps minimize number of gates.

# Administrivia

## Dates to keep in Mind

- Prelims: Tue Mar 4<sup>th</sup> and Thur May 1<sup>st</sup>
- Lab 1: Due Fri Feb 14<sup>th</sup> before Winter break
- Proj2: Due Fri Mar 28<sup>th</sup> before Spring break
- Final Project: Due when final would be (not known until Feb 14<sup>th</sup>)

## Lab Sections (start *this week; today*)

T	2:55 – 4:10pm	Carpenter Hall 104 (Blue Room)
W	8:40—9:55am	Carpenter Hall 104 (Blue Room)
W	11:40am – 12:55pm	Carpenter Hall 104 (BlueRoom)
W	3:35 – 4:50pm	Carpenter Hall 104 (Blue Room)
W	7:30—8:45pm	Carpenter Hall 235 (Red Room)
R	8:40 – 9:55pm	Carpenter Hall 104 (Blue Room)
R	11:40 – 12:55pm	Carpenter Hall 104 (Blue Room)
R	2:55 – 4:10pm	Carpenter Hall 104 (Blue Room)
F	8:40 – 9:55am	Carpenter Hall 104 (Blue Room)
F	11:40am – 12:55pm	Upton B7
F	2:55 – 4:10pm	Carpenter Hall 104 (Blue Room)

- Labs are separate than lecture and homework
- Bring laptop to Labs
- *This* week: intro to logisim and building an adder

# iClicker

Attempt to balance the iClicker graph

Register iClicker

- <http://atcsupport.cit.cornell.edu/pollsrvcl/>
- iClicker GO  
<http://pollinghelp.cit.cornell.edu/iclicker-go/#students>

# Goals for Today

## From Transistors to Gates to Logic Circuits

### Logic Gates

- From transistors
- Truth Tables

### Logic Circuits

- Identity Laws
- From Truth Tables to Circuits (Sum of Products)

### Logic Circuit Minimization

- Algebraic Manipulations
- Truth Tables (Karnaugh Maps)

### Transistors (electronic switch)

# Activity#1 How do we build *electronic* switches?


Transistors:

- 6:10 minutes (watch from from 41s to 7:00)
- <http://www.youtube.com/watch?v=QO5FgM7MLGg>
- Fill our Transistor Worksheet with info from Video




# NMOS and PMOS Transistors

- NMOS Transistor

 

- PMOS Transistor

 


- Connect source to drain when gate = 1
- N-channel


Connect source to drain when gate = 0  
P-channel

# NMOS and PMOS Transistors

- NMOS Transistor

 


- PMOS Transistor

 

- Connect source to drain when gate = 1
- N-channel

- Connect source to drain when gate = 0
- P-channel


# Inverter

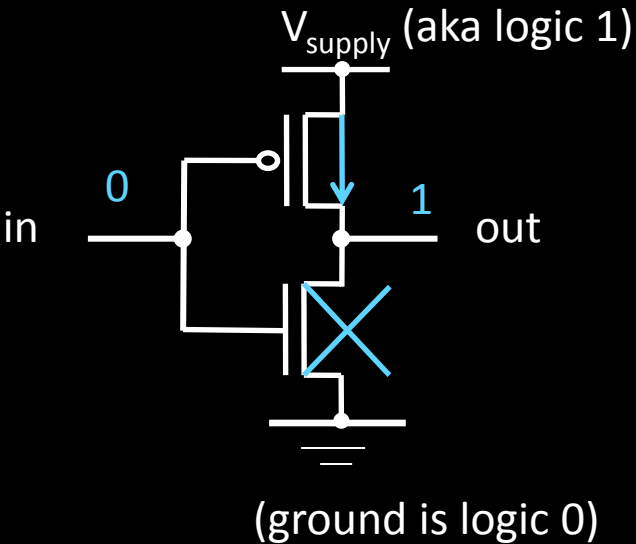

In	Out
0	1
1	0


Truth table

 - Function: NOT
- Called an inverter
- Symbol:



- Useful for taking the inverse of an input
- CMOS: complementary-symmetry metal-oxide-semiconductor


# Inverter

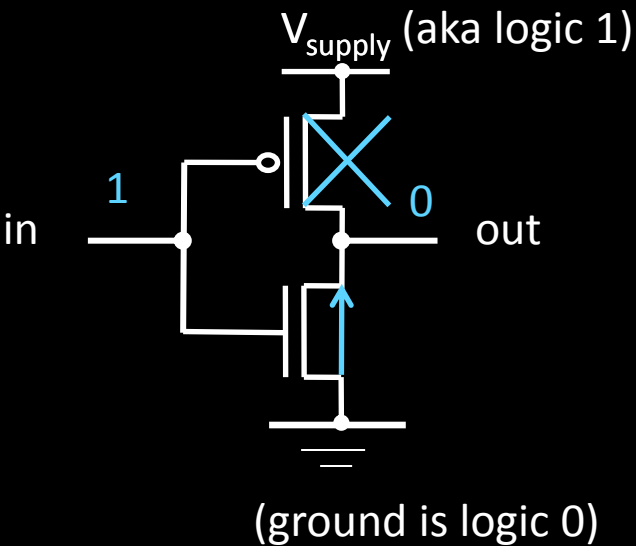

In	Out
0	1
1	0


Truth table

 - Function: NOT
- Called an inverter
- Symbol:




- Useful for taking the inverse of an input
- CMOS: complementary-symmetry metal-oxide-semiconductor

# Inverter

 

 - Function: NOT
- Called an inverter
- Symbol:




A	Out
0	1
1	0

Truth table


- Useful for taking the inverse of an input
- CMOS: complementary-symmetry metal-oxide-semiconductor

# NAND Gate

 


A	B	out
0	0	1
1	0	1
0	1	1
1	1	0


- Function: NAND
- Symbol:

 

# NOR Gate

 


- Function: NOR
- Symbol:

 


A	B	out
0	0	1
1	0	0
0	1	0
1	1	0

# Building Functions (Revisited)


NOT:

 

AND:

 

OR:

 



NAND and NOR are universal

- Can implement **any** function with NAND or just NOR gates
- useful for manufacturing





# Building Functions (Revisited)



NOT:

  

AND:

  


OR:

  

NAND and NOR are universal

- Can implement **any** function with NAND or just NOR gates
- useful for manufacturing

# Logic Gates

 


One can buy gates separately


- ex. 74xxx series of integrated circuits
- cost ~\$1 per chip, mostly for packaging and testing

Cumbersome, but possible to build devices using gates put together manually

# Then and Now

 
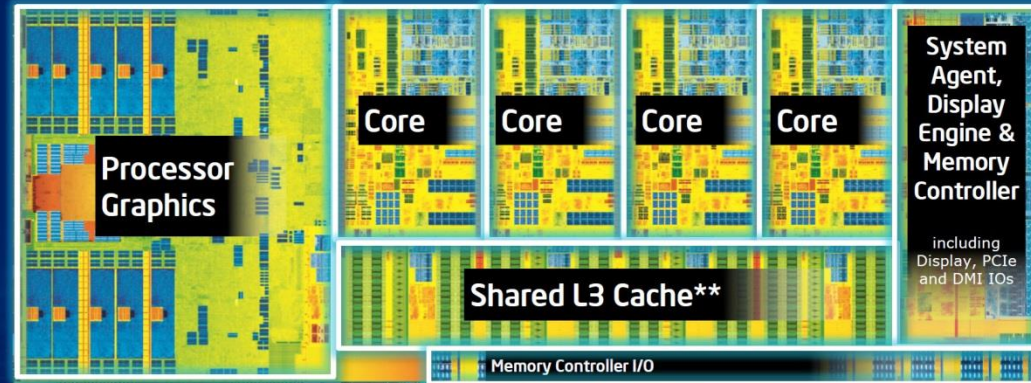
## 4th Generation Intel® Core™ Processor Die Map 22nm Tri-Gate 3-D Transistors



Quad core die shown above | Transistor count: 1.4 Billion | Die size: 177mm<sup>2</sup>

\*\* Cache is shared across all 4 cores and processor graphics

<http://techguru3d.com/4th-gen-intel-haswell-processors-architecture-and-lineup/>

## The first transistor



- on a workbench at AT&T Bell Labs in 1947
- Bardeen, Brattain, and Shockley

- An Intel Haswell
  - 1.4 billion transistors
  - 177 square millimeters
  - Four processing cores
  
# Big Picture: Abstraction

Hide complexity through simple abstractions

- Simplicity
  - Box diagram represents inputs and outputs
- Complexity
  - Hides underlying NMOS- and PMOS-transistors and atomic interactions



# Summary

Most modern devices are made from billions of on /off switches called transistors

- We will build a processor in this course!
- Transistors made from semiconductor materials:
  - MOSFET – Metal Oxide Semiconductor Field Effect Transistor
  - NMOS, PMOS – Negative MOS and Positive MOS
  - CMOS – complementary MOS made from PMOS and NMOS transistors
- Transistors used to make logic gates and logic circuits

We can now implement any logic circuit

- Can do it efficiently, using Karnaugh maps to find the minimal terms required
- Can use either NAND or NOR gates to implement the logic circuit
- Can use P- and N-transistors to implement NAND or NOR gates