

Processor


CS 3410, Spring 2014

Computer Science

Cornell University

See P&H Chapter: [4.1-4.4](#), [1.4](#), [Appendix A](#)

Full Datapath

 


Iclicker

How many stages of a datapath are there in our single cycle MIPS design?


- A) 1
- B) 2
- C) 3
- D) 4
- E) 5

Stages of datapath (1/5)

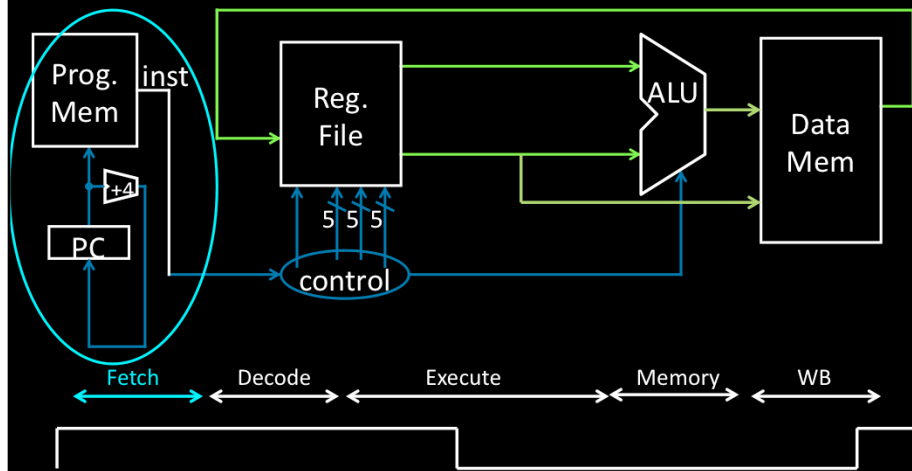


A Single cycle processor

Stages of datapath (2/5)

 


A Single cycle processor

Stages of datapath (3/5)

 


A Single cycle processor

Stages of datapath (4/5)

 

A Single cycle processor

Stages of datapath (5/5)

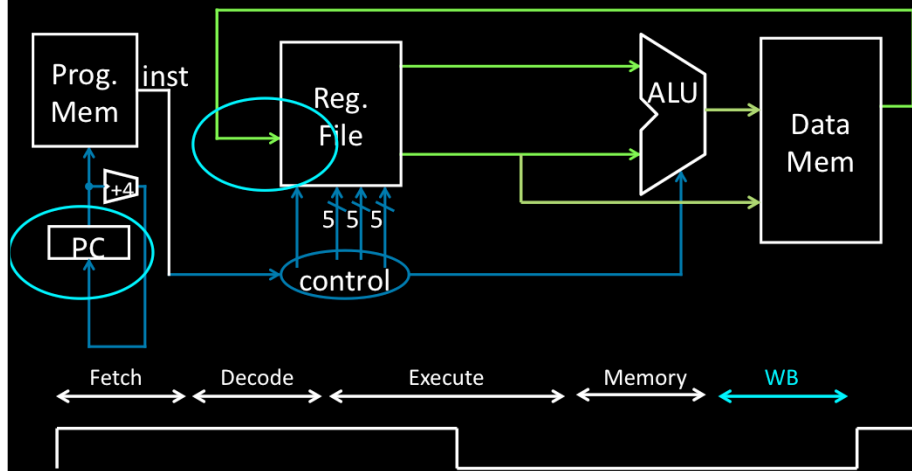

Takeaway

The datapath for a MIPS processor has five stages:

1. Instruction Fetch
2. Instruction Decode
3. Execution (ALU)
4. Memory Access
5. Register Writeback

This five stage datapath is used to execute all MIPS instructions


Iclicker

There are how many types of instructions in the MIPS ISA?

 - A) 1
- B) 3
- C) 5
- D) 200
- E) 1000s

MIPS instructions

All MIPS instructions are 32 bits long, has 3 formats



MIPS Instruction Functions

Arithmetic/Logical

- R-type: result and two source registers, shift amount
- I-type: 16-bit immediate with sign/zero extension

Memory Access

- load/store between registers and memory
- word, half-word and byte operations

Control flow

- conditional branches: pc-relative addresses
- jumps: fixed offsets, register absolute

Arithmetic Instructions: Shift

0000000000000001000100000110000000


op - rt rd shamt func
6 bits 5 bits 5 bits 5 bits 5 bits 6 bits

R-Type

op	func	mnemonic	description
0x0	0x0	SLL rd, rt, shamt	R[rd] = R[rt] << shamt
0x0	0x2	SRL rd, rt, shamt	R[rd] = R[rt] >>> shamt (zero ext.)
0x0	0x3	SRA rd, rt, shamt	R[rd] = R[rt] >> shamt (sign ext.)

ex: r8 = r4 * 64 # SLL r8, r4, 6
 r8 = r4 << 6

Shift

 

Arithmetic Instructions: Immediates

0010000010100101000000000000101

op

rs

rd

immediate

I-Type

6 bits

5 bits

5 bits

16 bits

op	mnemonic	description
0x8	ADDI rd, rs, imm	$R[rd] = R[rs] + imm$
0xc	ANDI rd, rs, imm	$R[rd] = R[rs] \& imm$
0xd	ORI rd, rs, imm	$R[rd] = R[rs] imm$

ex: $r5 = r5 + 5$ # ADDI r5, r5, 5
 $r5 += 5$


What if immediate is negative?

ex: $r5 += -1$


For addi, sign extension and can do positive and negative. Will signal overflow.
For addiu, still use sign extension, but no overflow

Add vs. addu: no overflow for addu

Immediates

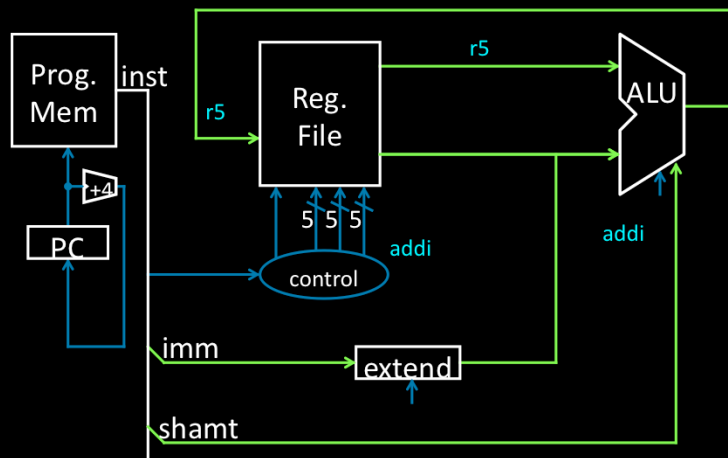

Immediates

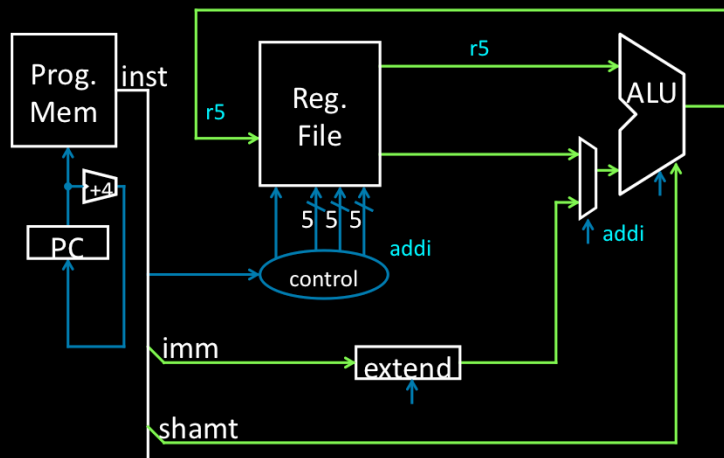

Arithmetic Instructions: Immediates

0011110000000101000000000000101

op

-

rd

immediate

I-Type

6 bits

5 bits

5 bits

16 bits

op	mnemonic	description
0xF	LUI rd, imm	R[rd] = imm << 16


ex: r5 = 0x50000 # LUI r5, 5

ex: LUI r5, 0xdead

ORI r5, r5 0xbeef

What does r5 = ?

r5 = 0xdeadbeef

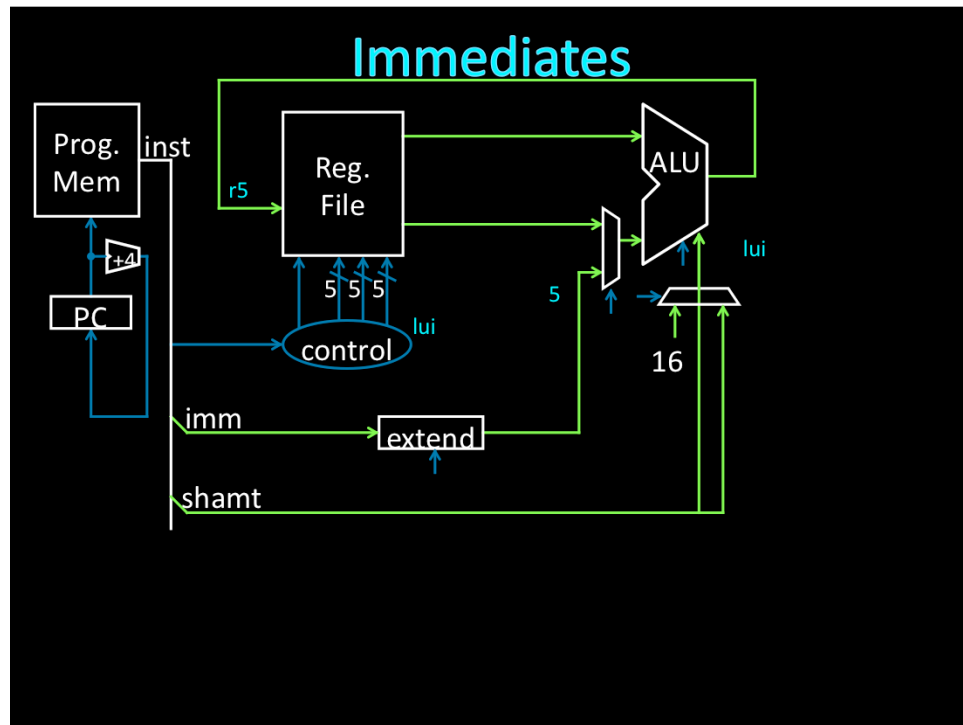

or, extra input to alu B mux from before/after extend
(or, extra mux after alu)

Goals for today

MIPS Datapath

- Memory layout
- Control Instructions

Performance

- How fast can we make it?
- CPI (Cycles Per Instruction)
- MIPS (Instructions Per Cycle)
- Clock Frequency

MIPS Instruction Types

Arithmetic/Logical

- R-type: result and two source registers, shift amount
- I-type: 16-bit immediate with sign/zero extension

Memory Access

- load/store between registers and memory
- word, half-word and byte operations

Control flow

- conditional branches: pc-relative addresses
- jumps: fixed offsets, register absolute

Memory Instructions

1010110010100001000000000000100

I-Type


op	rs	rd	offset
6 bits	5 bits	5 bits	16 bits
op	mnemonic	description	
0x23	LW rd, offset(rs)	R[rd] = Mem[offset+R[rs]]	
0x2b	SW rd, offset(rs)	Mem[offset+R[rs]] = R[rd]	

base + offset
addressing

signed
offsets

ex: = Mem[4+r5] = r1 # SW r1, 4(r5)

Memory Operations

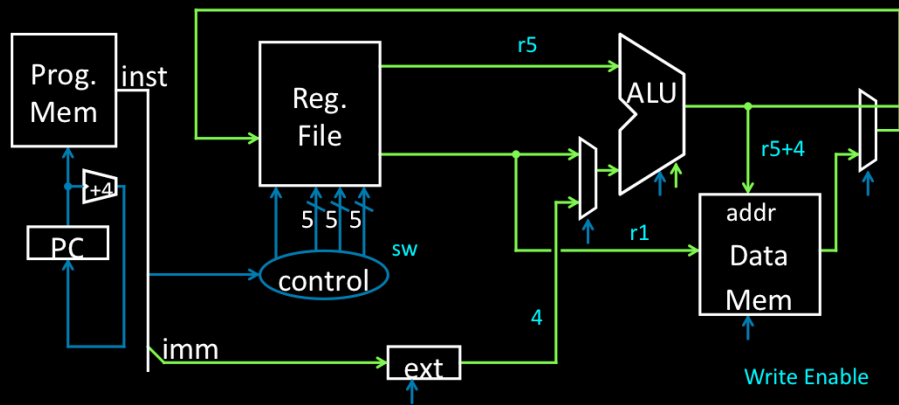

ex: = Mem[4+r5] = r1 # SW r1, 4(r5)

Memory Instructions

1010110010100001000000000000100

	op	rs	rd	offset
	6 bits	5 bits	5 bits	16 bits
op	mnemonic		description	
0x20	LB rd, offset(rs)		R[rd] = sign_ext(Mem[offset+R[rs]])	
0x24	LBU rd, offset(rs)		R[rd] = zero_ext(Mem[offset+R[rs]])	
0x21	LH rd, offset(rs)		R[rd] = sign_ext(Mem[offset+R[rs]])	
0x25	LHU rd, offset(rs)		R[rd] = zero_ext(Mem[offset+R[rs]])	
0x23	LW rd, offset(rs)		R[rd] = Mem[offset+R[rs]]	
0x28	SB rd, offset(rs)		Mem[offset+R[rs]] = R[rd]	
0x29	SH rd, offset(rs)		Mem[offset+R[rs]] = R[rd]	
0x2b	SW rd, offset(rs)		Mem[offset+R[rs]] = R[rd]	

sw r1 4(r5)

sb r1, 3(r5)

If you don't make sure half word accesses are half word aligned, or word accesses are word aligned, there will be an error signaled. We will talk about traps and exceptions later.

Endianness

Endianness: Ordering of bytes within a memory word

Little Endian = least significant part first (MIPS, x86)

	1000	1001	1002	1003
as 4 bytes	0x78	0x56	0x34	0x12
as 2 halfwords	0x5678		0x1234	
as 1 word	0x12345678			

Big Endian = most significant part first (MIPS, networks)

	1000	1001	1002	1003
as 4 bytes	0x12	0x34	0x56	0x78
as 2 halfwords	0x1234		0x5678	
as 1 word	0x12345678			

Comes from Gulliver travels

Memory Layout

Examples (big/little endian):

r5 contains 5 (0x00000005)

SB r5, 2(r0)

LB r6, 2(r0)

R[r6] = 0x05

SW r5, 8(r0)

LB r7, 8(r0)

LB r8, 11(r0)

R[r7] = 0x00

R[r8] = 0x05

	0x00000000
	0x00000001
0x05	0x00000002
	0x00000003
	0x00000004
	0x00000005
	0x00000006
	0x00000007
0x00	0x00000008
0x00	0x00000009
0x00	0x0000000a
0x05	0x0000000b
	...

Big Endian means store MSB (most significant byte) first

MIPS Instruction Types

Arithmetic/Logical

- R-type: result and two source registers, shift amount
- I-type: 16-bit immediate with sign/zero extension

Memory Access

- load/store between registers and memory
- word, half-word and byte operations

Control flow

- conditional branches: pc-relative addresses
- jumps: fixed offsets, register absolute

Control Flow: Absolute Jump

00001010100001001000011000000011



op	Mnemonic	Description
0x2	J target	$PC = (PC+4)_{31..28} \bullet \text{target} \bullet 00$
		<div> <div>(PC+4)_{31..28}</div> <div>target</div> <div>00</div> </div> <div> <div>4 bits</div> <div>26 bits</div> <div>2 bits</div> </div>

(PC+4)_{31..28} 010000000000000000000000000000 00

ex: j 0x1000000

$PC = ((PC+4) \& 0xf0000000) | 0x04000000$

Where • is used to concatenate

Why should the offset be left shifted by 2. To keep the jump address word aligned.

AND to not waste two bits that we *know* are going to be 0.

Control Flow: Absolute Jump

00001010100001001000011000000011

op

6 bits

immediate

26 bits

J-Type

op	Mnemonic	Description
0x2	J target	$PC = (PC+4)_{31..28} \bullet \text{target} \bullet 00$

Absolute addressing for jumps

$(PC+4)_{31..28}$ will be the same


- Jump from 0x30000000 to 0x20000000?
 - But: Jumps from 0x2FFFFFFF to 0x3xxxxxxx are possible, but not reverse
- Trade-off: out-of-region jumps vs. 32-bit instruction encoding

MIPS Quirk:

- jump targets computed using *already incremented* PC

Where • is used to concatenate

Absolute Jump

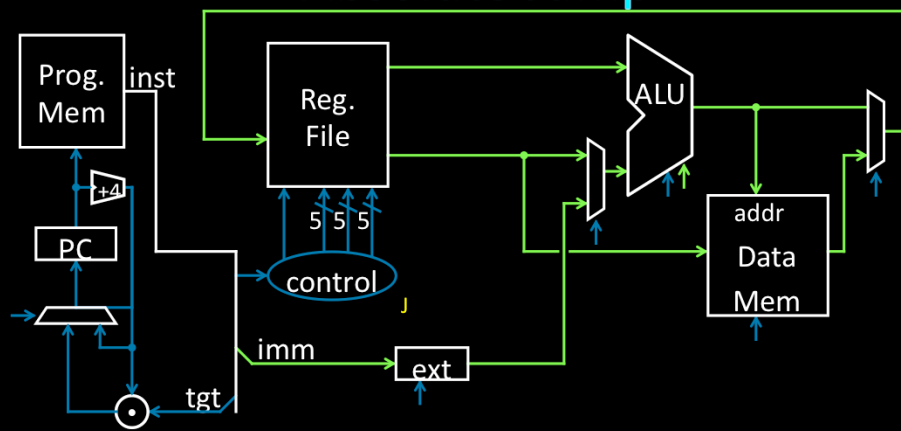

op	Mnemonic	Description
0x2	J target	$PC = (PC+4)_{31..28} \bullet \text{target} \bullet 00$

Control Flow: Jump Register

000000 00011 000000 000000 000000 001000


op rs - - - func
6 bits 5 bits 5 bits 5 bits 5 bits 6 bits

R-Type

op	func	mnemonic	description
0x0	0x08	JR rs	PC = R[rs]

ex: JR r3

Jump Register

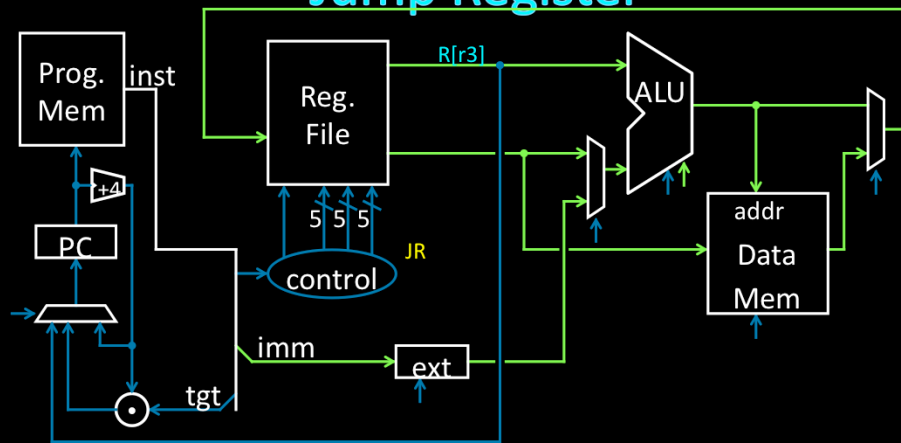

op	func	mnemonic	description
0x0	0x08	JR rs	PC = R[rs]

Examples

E.g. Use Jump or Jump Register instruction to
jump to 0xabcd1234

But, what about a jump based on a condition?

assume $0 \leq r3 \leq 1$

if ($r3 == 0$) jump to 0xdecafe00

else jump to 0xabcd1234

Control Flow: Branches

00010000101000010000000000000011

op	rs	rd	offset
6 bits	5 bits	5 bits	16 bits

I-Type

signed
offsets

op	mnemonic	description
0x4	BEQ rs, rd, offset	if R[rs] == R[rd] then PC = PC+4 + (offset<<2)
0x5	BNE rs, rd, offset	if R[rs] != R[rd] then PC = PC+4 + (offset<<2)


ex: BEQ r5, r1, 3

If(R[r5]==R[r1]) then PC = PC+4 + 12

Why should the offset be left shifted by 2. To keep the jump address word aligned.

AND to not waste two bits that we *know* are going to be 0.

Control Flow: Branches

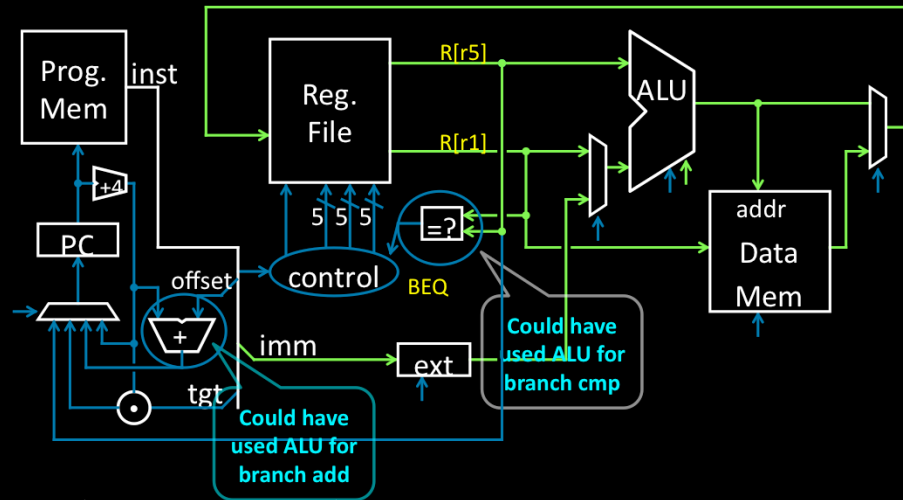

op	mnemonic	description
0x4	BEQ rs, rd, offset	if $R[rs] == R[rd]$ then $PC = PC + 4 + (offset \ll 2)$
0x5	BNE rs, rd, offset	if $R[rs] != R[rd]$ then $PC = PC + 4 + (offset \ll 2)$

In the book, the ALU is used to determine the branch comparison. We are choosing to do it separately.

Anyway, can't use ALU for both branch comparison and PC determination. At most, we can use it once. The book uses it for branch

Control Flow: More Branches

Conditional Jumps (cont.)

00000100101000010000000000000010

op rs subop offset
6 bits 5 bits 5 bits 16 bits

almost I-Type


signed
offsets

op	subop	mnemonic	description
0x1	0x0	BLTZ rs, offset	if $R[rs] < 0$ then $PC = PC + 4 + (\text{offset} \ll 2)$
0x1	0x1	BGEZ rs, offset	if $R[rs] \geq 0$ then $PC = PC + 4 + (\text{offset} \ll 2)$
0x6	0x0	BLEZ rs, offset	if $R[rs] \leq 0$ then $PC = PC + 4 + (\text{offset} \ll 2)$
0x7	0x0	BGTZ rs, offset	if $R[rs] > 0$ then $PC = PC + 4 + (\text{offset} \ll 2)$

ex: BGEZ r5, 2

If($R[r5] \geq 0$) then $PC = PC + 4 + 8$

Control Flow: More Branches

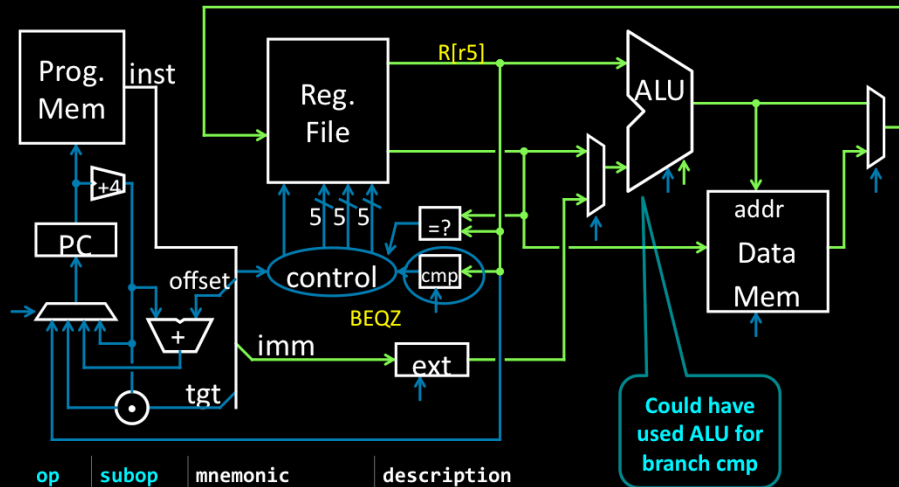

op	subop	mnemonic	description
0x1	0x0	BLTZ rs, offset	if $R[rs] < 0$ then $PC = PC + 4 + (\text{offset} \ll 2)$
0x1	0x1	BGEZ rs, offset	if $R[rs] \geq 0$ then $PC = PC + 4 + (\text{offset} \ll 2)$
0x6	0x0	BLEZ rs, offset	if $R[rs] \leq 0$ then $PC = PC + 4 + (\text{offset} \ll 2)$
0x7	0x0	BGTZ rs, offset	if $R[rs] > 0$ then $PC = PC + 4 + (\text{offset} \ll 2)$

Control Flow: Jump and Link

Why? Function/procedure calls

000011000000001001000011000000010

op immediate
6 bits 26 bits

J-Type

Discuss later

op	mnemonic	description
0x3	JAL target	r31 = PC+8 (+8 due to branch delay slot) PC = (PC+4) _{31..28} • target • 00

ex: JAL 0x1000000


r31 = PC+8

PC = (PC+4)_{31..28} • 0x4000000

op	mnemonic	description
0x2	J target	PC = (PC+4) _{31..28} • target • 00

0x0121808 == 1185800

Jump and Link

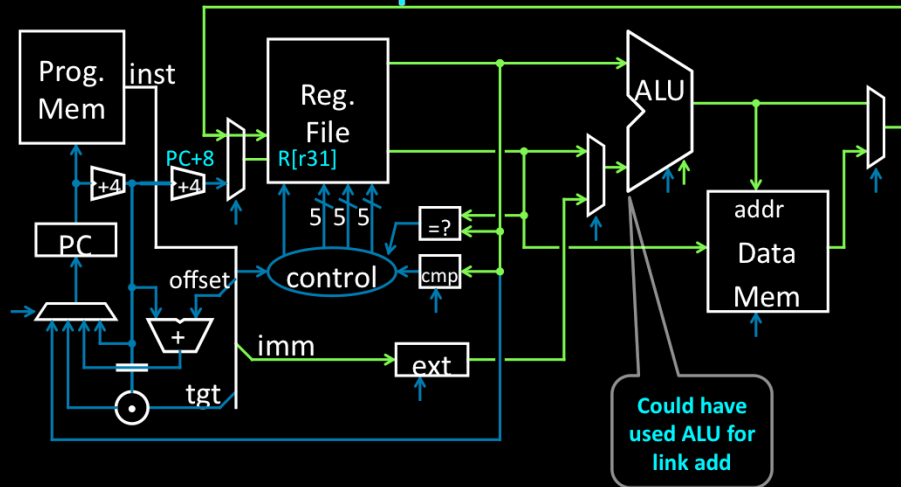

op	mnemonic	description
0x3	JAL target	$r31 = PC+8$ (+8 due to branch delay slot) $PC = (PC+4)_{31..28} (target \ll 2)$

Goals for today

MIPS Datapath

- Memory layout
- Control Instructions

Performance

- How to get it?
- CPI (Cycles Per Instruction)
- MIPS (Instructions Per Cycle)
- Clock Frequency

Pipelining

- Latency vs throughput

Questions

How do we measure performance?

What is the performance of a single cycle CPU?


How do I get performance?

See: P&H 1.4

What instruction has the longest path

- A) LW
- B) SW
- C) ADD/SUB/AND/OR/etc
- D) BEQ
- E) J

Memory Operations

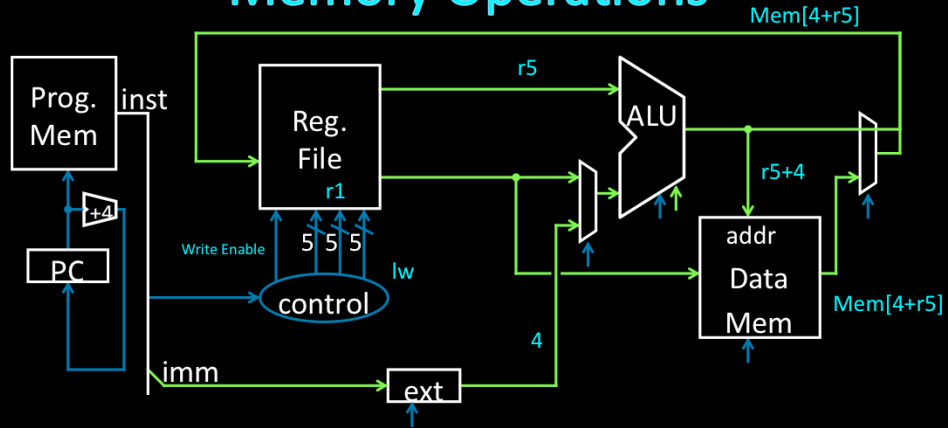

ex: = r1 = Mem[4+r5] # LW r1, 4(r5)

Performance

How do I get it?


Parallelism

Pipelining


Both!

Performance: Aside

 Speed of a circuit is affected by the number of gates in series (on the *critical path* or the *deepest level of logic*)



4-bit Ripple Carry Adder

 

- First full adder, 2 gate delay
- Second full adder, 2 gate delay
- ...

Adding

Main ALU, slows us down

Does it need to be this slow?

Observations

- Have to wait for C_{in}
- Can we compute in parallel in some way?
- CLA carry look-ahead adder

Carry Look Ahead Logic


Can we reason independent of C_{in} ?

- Just based on (A,B) only

When is $C_{out} == 1$, irrespective of C_{in}

If $C_{in} == 1$, when is C_{out} also $== 1$

1-bit Adder with Carry

 


Full Adder

- Adds three 1-bit numbers
- Computes 1-bit result and 1-bit carry
- Can be cascaded

A	B	C _{in}	C _{out}	S
0	0	0	0	0
0	1	0	0	1
1	0	0	0	1
1	1	0	1	0
0	0	1	0	1
0	1	1	1	0
1	0	1	1	0
1	1	1	1	1

1-bit CLA adder

 

Create two terms: propagator, generator

$g = 1$, generates Cout: $g = AB$


- Irrespective of Cin

$p = 1$, propagates Cin to Cout: $p = A + B$

p and g generated in 1 cycle delay

R is 2 cycle delay after we get Cin

1-bit Adder with Carry

 


Full Adder

- Adds three 1-bit numbers
- Computes 1-bit result and 1-bit carry
- Can be cascaded

A	B	C _{in}	C _{out}	S
0	0	0	0	0
0	1	0	0	1
1	0	0	0	1
1	1	0	1	0
0	0	1	0	1
0	1	1	1	0
1	0	1	1	0
1	1	1	1	1

4-bit CLA

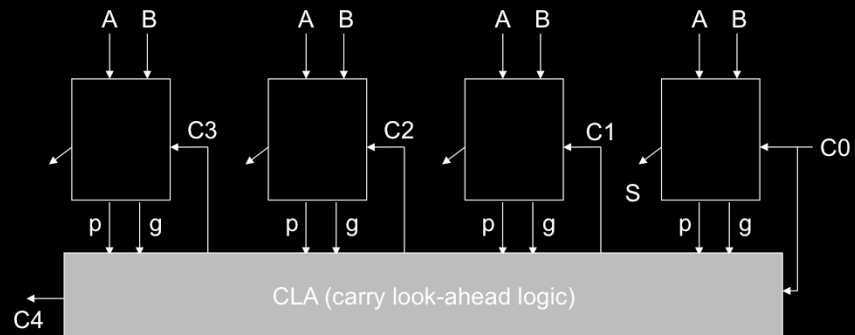

- CLA takes p,g from all 4 bits, C0 and generates all Cs: 2 gate delay

$$C_1 = g_0 + p_0 C_0$$


$$C_2 = g_1 + p_1 C_1 = g_1 + p_1 (g_0 + p_0 C_0) = g_1 + p_1 g_0 + p_1 p_0 C_0$$

$$C_3 = g_2 + p_2 C_2 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 C_0$$

$$C_4 = g_3 + p_3 C_3 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 C_0$$

$C_i = \text{Function } (C_0, p \text{ and } g \text{ values})$

4-bit CLA

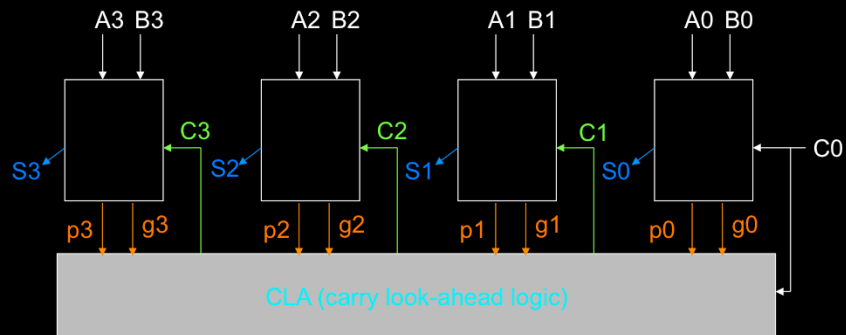

- Given A,B's, all p,g's are generated in 1 gate delay in parallel
- Given all p,g's, all C's are generated in 2 gate delay in parallel
- Given all C's, all S's are generated in 2 gate delay in parallel

Sequential operation is made into parallel operation!!

Performance

Ripple carry adder vs carry lookahead adder for 8 bits

- 2 x 8 vs. 5

Performance

How do I get it?

Parallelism

Pipelining

Both!