

State and Finite State Machines

Prof. Hakim Weatherspoon

CS 3410, Spring 2015

Computer Science

Cornell University

See P&H Appendix B.7, B.8, B.10, B.11

Announcements

Make sure you are

- Registered for class, can access CMS
- Have a Section you can go to.
- *Lab Sections are required.*
 - “Make up” lab sections **only 8:40am Wed, Thur, or Fri**
 - Bring laptop to Labs
- Project partners are required for projects.
 - Have project partner in same Lab Section, if possible

HW1 and Lab1 available today, after lecture

- *Do HW1 problems with lecture, i.e. finish part1 and 2 this week*
- Work alone on both
- But, use your resources
 - Lab Section, Piazza.com, Office Hours, Homework Help Session,
 - Class notes, book, Sections, CSUGLab

Announcements

Make sure to go to **your** Lab Section this week

Completed Lab1 due ***before*** winter break, Friday, Feb 13th

Note, a Design Document is due when you submit Lab1 final circuit

Work **alone**

Homework1 is out

Due a week before prelim1, Monday, February 23rd

Work on problems incrementally, as we cover them in lecture

Office Hours for help

Work **alone**

Work alone, **BUT** use your resources

- Lab Section, Piazza.com, Office Hours
- Class notes, book, Sections, CSUGLab

Announcements

Check online syllabus/schedule

- <http://www.cs.cornell.edu/Courses/CS3410/2015sp/schedule.html>
- Slides and Reading for lectures
- Office Hours
- ***Pictures of all TAs***
- Homework and Programming Assignments
- Dates to keep in Mind
 - Prelims: Tue Mar 3rd and Thur April 30th
 - *Lab 1: Due next Friday, Feb 13th before Winter break*
 - Proj2: Due Thur Mar 26th before Spring break
 - Final Project: Due when final would be (not known until Feb 14t

Schedule is subject to change

Collaboration, Late, Re-grading Policies

“Black Board” Collaboration Policy

- Can discuss approach together on a “black board”
- Leave and write up solution independently
- Do not copy solutions

Late Policy

- Each person has a total of **four** “slip days”
- Max of **two** slip days for any individual assignment
- Slip days deducted first for *any* late assignment, cannot selectively apply slip days
- For projects, slip days are deducted from all partners
- 25% deducted per day late after slip days are exhausted


Regrade policy

- Submit written request to lead TA,
and lead TA will pick a different grader
- Submit another written request,
lead TA will regrade directly
- Submit yet another written request for professor to regrade.

Stateful Components

Until now is combinational logic

 - Output is computed when inputs are present
- System has no internal state
- Nothing computed in the present can depend on what happened in the past!



Need a way to record data

Need a way to build stateful circuits

Need a state-holding device

Finite State Machines

Goals for Today

State

- How do we store *one* bit?
- Attempts at storing (and changing) one bit
 - Set-Reset Latch
 - D Latch
 - D Flip-Flops
 - Master-Slave Flip-Flops
- Register: storing more than one bit, N-bits

Basic Building Blocks

- Decoders and Encoders


Finite State Machines (FSM)

- How do we design logic circuits with state?
- Types of FSMs: Mealy and Moore Machines
- Examples: Serial Adder and a Digital Door Lock

Goal


How do we store store *one* bit?

First Attempt: Unstable Devices

 


Second Attempt: Bistable Devices

- Stable and unstable equilibria?

 


A Simple Device

Third Attempt: Set-Reset Latch

 

Third Attempt: Set-Reset Latch

 



A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

S	R	Q	Q̄
0	0		
0	1		
1	0		
1	1		

Set-Reset (S-R) Latch

Stores a value Q and its complement

Third Attempt: Set-Reset Latch

  

S	R	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		

Set-Reset (S-R) Latch

Stores a value Q and its complement



Takeaway

Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But, SR Latch has a forbidden state.

Next Goal

How do we avoid the forbidden state of S-R Latch?

Fourth Attempt: (Unclocked) D Latch

  

Fill in the truth table?

D	Q	\bar{Q}
0		
1		

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

Takeaway

Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But, SR Latch has a forbidden state.

(Unclocked) D Latch can store and change a bit like an SR Latch while avoiding the forbidden state.


Next Goal

How do we coordinate state changes to a D Latch?

Clocks

Clock helps coordinate state changes

 
- Usually generated by an oscillating crystal
- Fixed period; frequency = $1/\text{period}$



Clock Disciplines

Level sensitive

 
- State changes when clock is high (or low)




Edge triggered

- State changes at clock edge

positive edge-triggered

 


negative edge-triggered

 

Clock Methodology

Clock Methodology


- Negative edge, synchronous

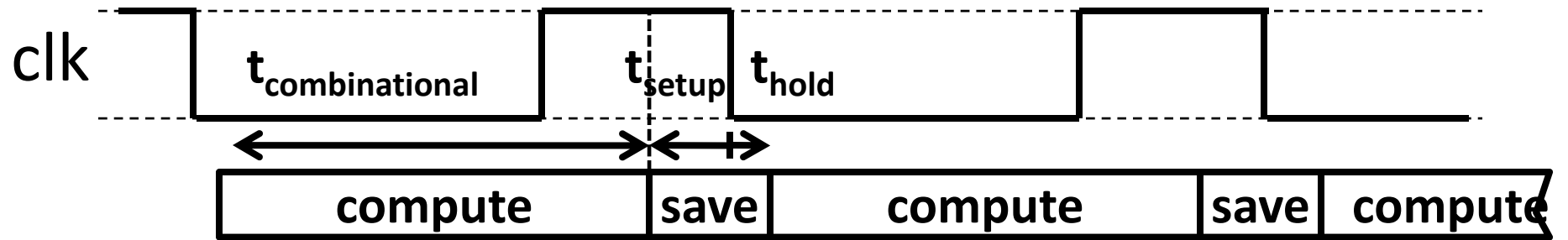


– Edge-Triggered: Signals must be stable near falling clock edge

- Positive edge synchronous

Fifth Attempt: D Latch with Clock

 


Fifth Attempt: D Latch with Clock

 

Fill in the truth table

clk	D	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		

Fifth Attempt: D Latch with Clock

 

Fill in the truth table

S	R	Q	\bar{Q}	
0	0	Q	\bar{Q}	hold
0	1	0	1	reset
1	0	1	0	set
1	1	forbidden		

clk	D	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		

Fifth Attempt: D Latch with Clock

Level Sensitive D Latch



Clock high:

set/reset (according to D)

Clock low:


keep state (ignore D)

Fill output signal for Q

  

clk	D	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		

 
Sixth Attempt: Edge-Triggered D Flip-Flop



D Flip-Flop

- Edge-Triggered
- Data captured when clock is high
- Output changes only on falling edges

 Activity#1: Fill in timing graph and values for X and Q



Takeaway

Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But, SR Latch has a forbidden state.

(Unclocked) D Latch can store and change a bit like an SR Latch while avoiding a forbidden state.

An Edge-Triggered D Flip-Flop (aka Master-Slave D Flip-Flop) stores one bit. The bit can be changed in a synchronized fashion on the edge of a clock signal.



Next Goal

How do we store more than one bit, N bits?

Registers

Register

  - D flip-flops in parallel
- shared clock
- extra clocked inputs: write_enable, reset, ...



Takeaway


Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But, SR Latch has a forbidden state.

(Unclocked) D Latch can store and change a bit like an SR Latch while avoiding a forbidden state.

An Edge-Triggered D Flip-Flop (aka Master-Slave D Flip-Flop) stores one bit. The bit can be changed in a synchronized fashion on the edge of a clock signal.

An N -bit **register** stores N -bits. It is created with N D-Flip-Flops in parallel along with a shared clock.

An Example: What will this circuit do?

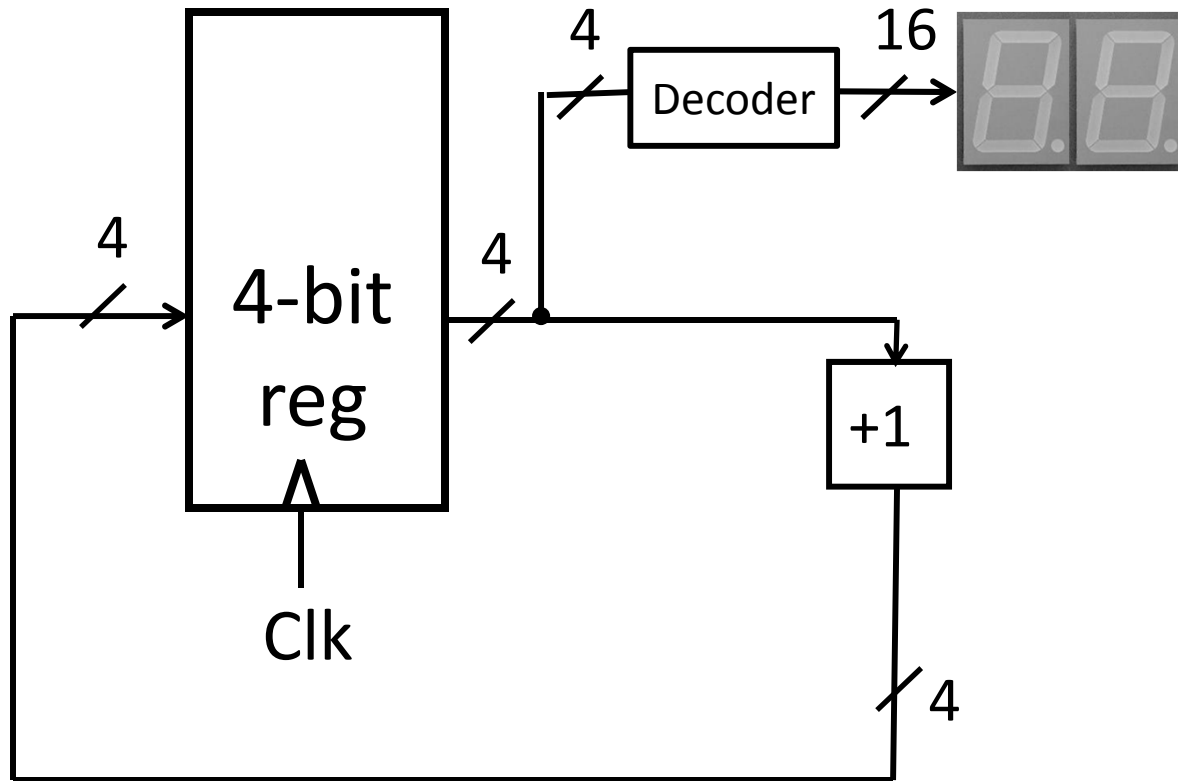


Decoder Example: 7-Segment LED

7-Segment LED

- photons emitted when electrons fall into holes



Decoder Example: 7-Segment LED Decoder

 

3 inputs


- encode 0 – 7 in binary

7 outputs

- one for each LED


7 Segment LED Decoder Implementation

b2	b1	b0	d6	d5	d4	d3	d2	d1	d0
0	0	0							
0	0	1							
0	1	0							
0	1	1							
1	0	0							
1	0	1							
1	1	0							
1	1	1							



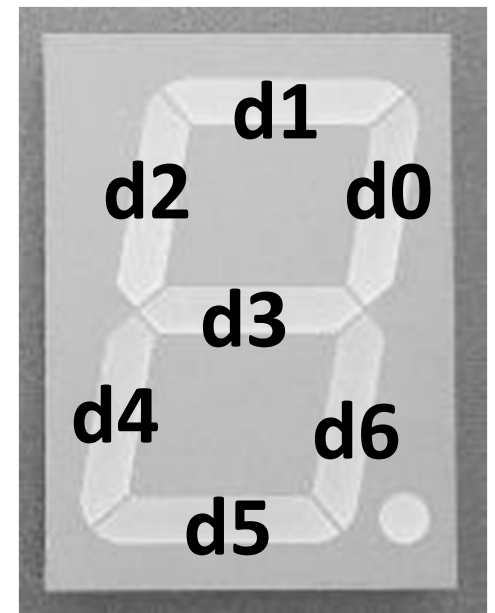


7 Segment LED Decoder Implementation


b2	b1	b0	d6	d5	d4	d3	d2	d1	d0
0	0	0	1	1	1	0	1	1	1
0	0	1	1	0	0	0	0	0	1
0	1	0	0	1	1	1	0	1	1
0	1	1	1	1	0	1	0	1	1
1	0	0	1	0	0	1	1	0	1
1	0	1	1	1	0	1	1	1	0
1	1	0	1	1	1	1	1	1	0
1	1	1	1	0	0	0	0	1	1

 

Basic Building Blocks We have Seen

   


Encoders

 

But can encode vote efficiently with binary encoding.

Example Encoder Truth Table

 

A 3-bit
encoder
with 4 inputs
for simplicity

a	b	c	d				
0	0	0	0				
1	0	0	0				
0	1	0	0				
0	0	1	0				
0	0	0	1				

Basic Building Blocks Example: Voting



Ballots

The 3410 optical scan
vote reader
machine

Recap

We can now build interesting devices with sensors

- Using combinational logic

We can also store data values (aka Sequential Logic)

- In state-holding elements
- Coupled with clocks

Goals for Today

State

- How do we store *one* bit?
- Attempts at storing (and changing) one bit
 - Set-Reset Latch
 - D Latch
 - D Flip-Flops
 - Master-Slave Flip-Flops
- Register: storing more than one bit, N-bits

Basic Building Blocks

- Decoders and Encoders

Finite State Machines (FSM)

- How do we design logic circuits with state?
- Types of FSMs: Mealy and Moore Machines
- Examples: Serial Adder and a Digital Door Lock

Finite State Machines

Next Goal

How do we design logic circuits with state?

Finite State Machines

An electronic machine which has

- external inputs
- externally visible outputs
- internal state

Output and next state depend on

- inputs
- current state

Abstract Model of FSM

Machine is

$$M = (S, I, O, \delta)$$

S : Finite set of states

I : Finite set of inputs


O : Finite set of outputs

δ : State transition function

Next state depends on present input *and* present state



Automata Model

Finite State Machine

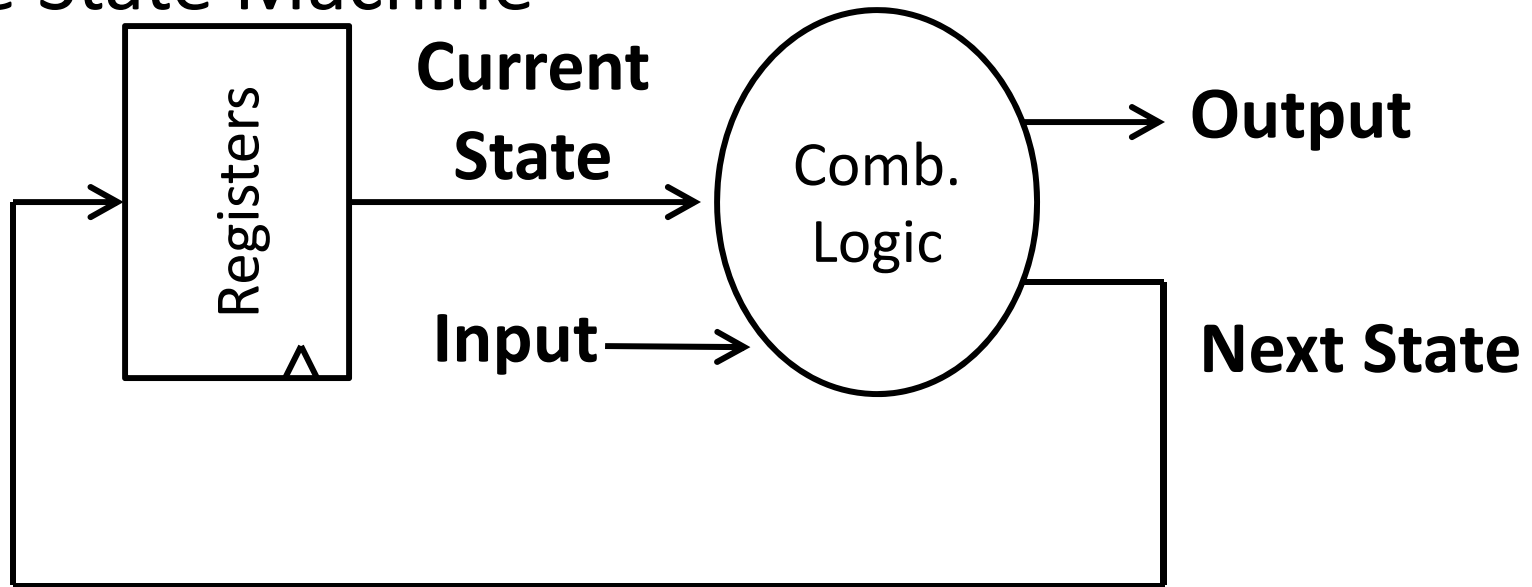

- inputs from external world
- outputs to external world
- internal state
- combinational logic

FSM Example

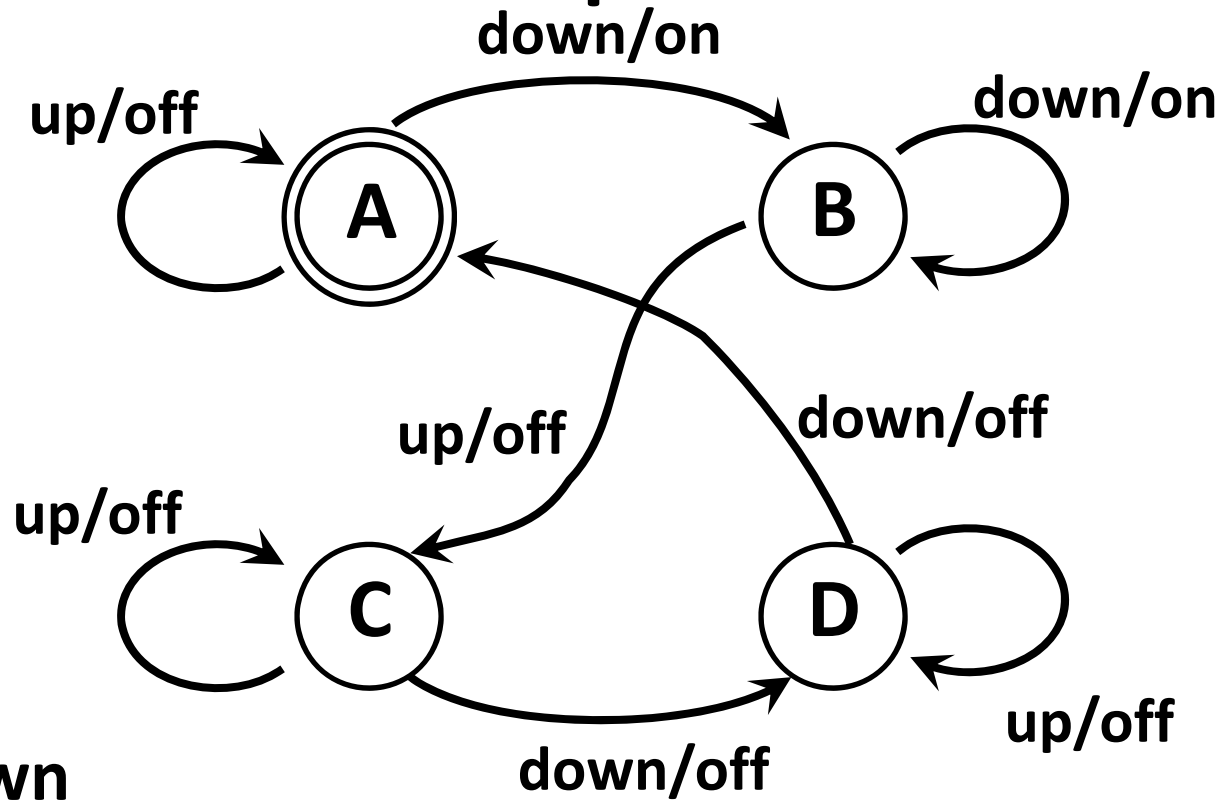
 


Input: **up** or **down**

Output: **on** or **off**

States: **A**, **B**, **C**, or **D**

FSM Example

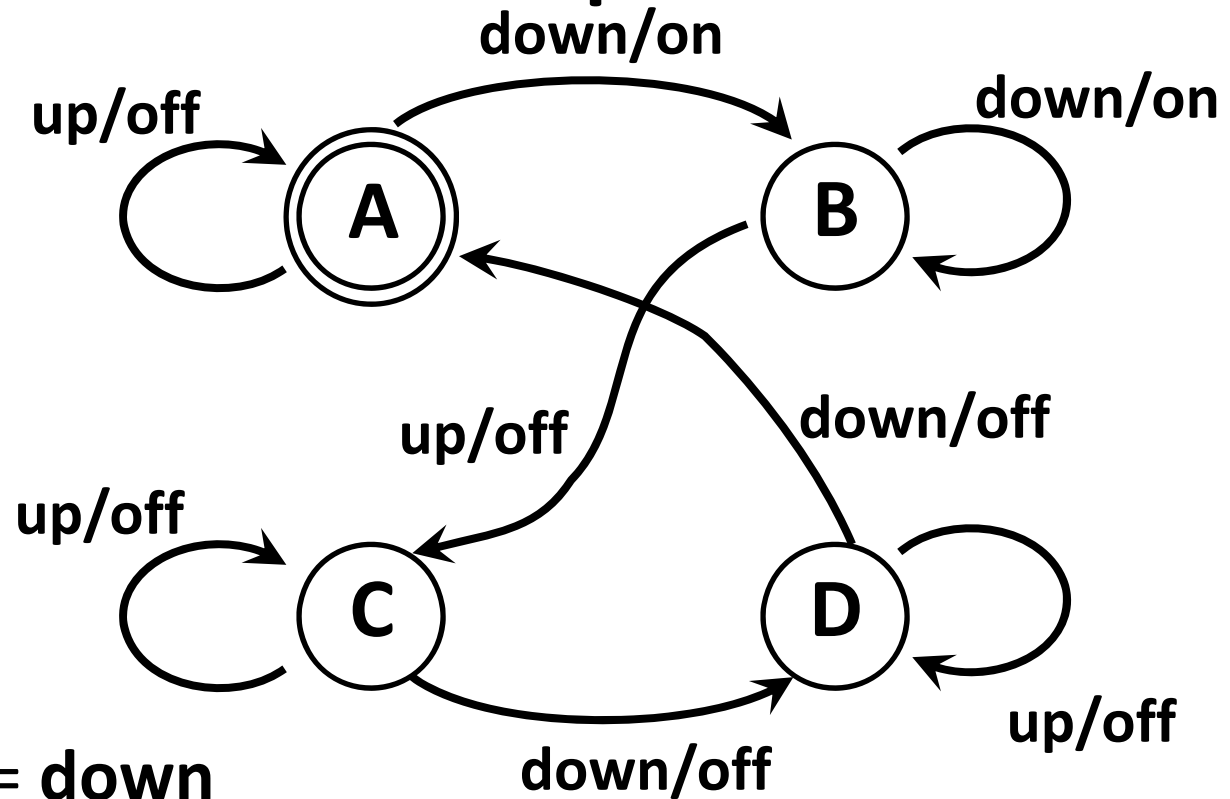
 


Input: = **up** or = **down**

Output: = **on** or = **off**

States: = **A**, = **B**, = **C**, or = **D**

FSM Example

  


Input: **0**=up or **1**=down

Output: **1**=on or **0**=off

States: **00**=A, **01**=B, **10**=C, or **11**=D

Mealy Machine


General Case: Mealy Machine

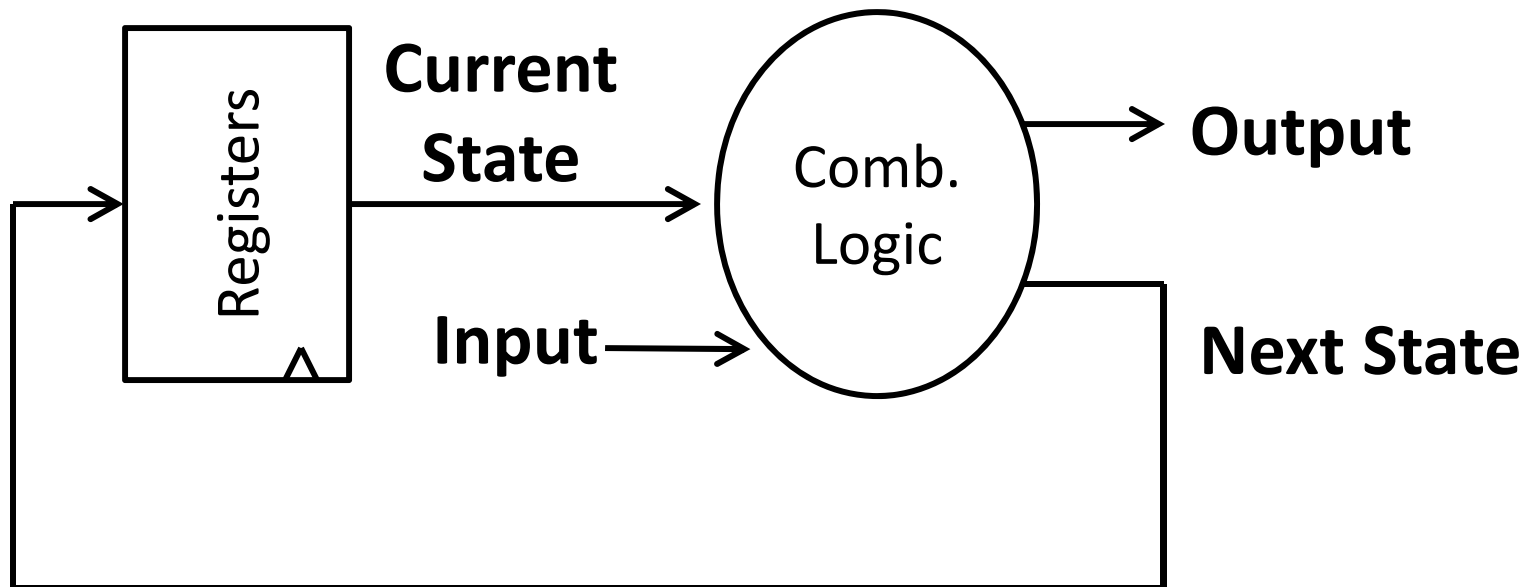

Outputs and next state depend on both current state and input



Moore Machine

Special Case: Moore Machine

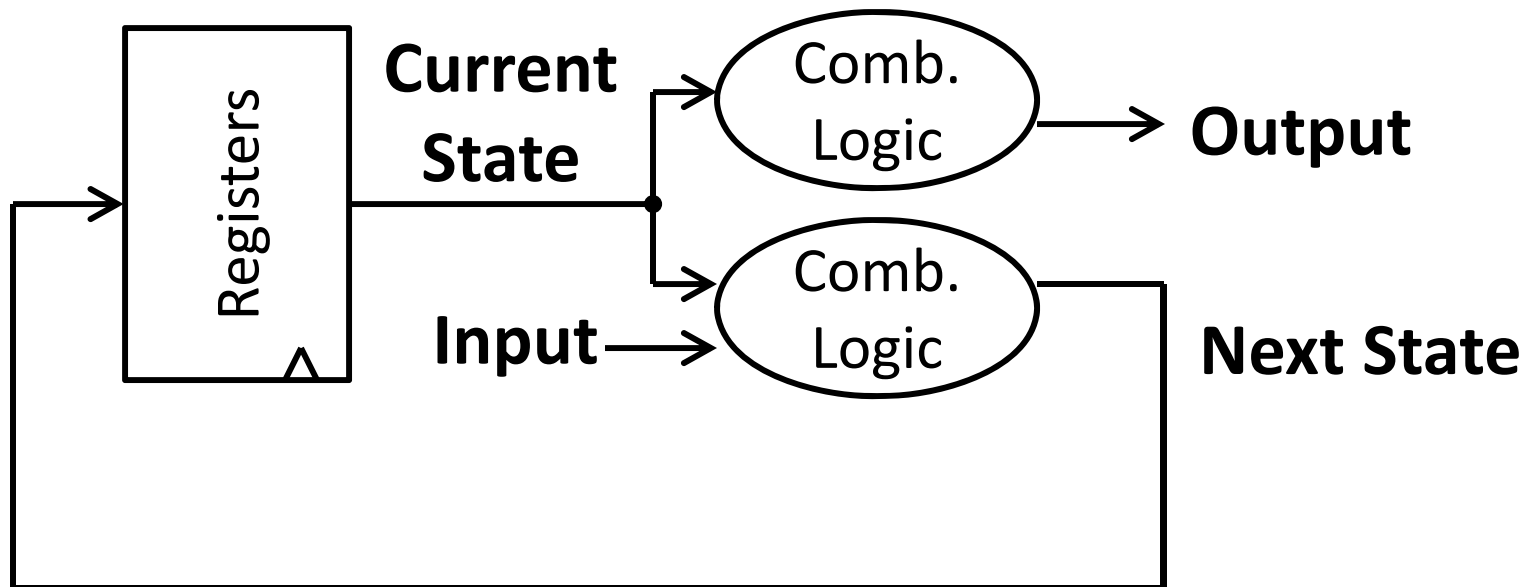

Outputs depend only on current state

Moore Machine FSM Example

 
 


Input: **up** or **down**

Output: **on** or **off**

States: **A**, **B**, **C**, or **D**

Mealy Machine FSM Example

  

Input: **up** or **down**


Output: **on** or **off**

States: **A**, **B**, **C**, or **D**

Activity#2: Create a Logic Circuit for a Serial Adder

Add two infinite input bit streams

 
- streams are sent with least-significant-bit (lsb) first
- How many states are needed to represent FSM?
- Draw and Fill in FSM diagram



Strategy:

- (1) Draw a state diagram (e.g. Mealy Machine)
- (2) Write output and next-state tables
- (3) Encode states, inputs, and outputs as bits
- (4) Determine logic equations for next state and outputs

FSM: State Diagram

 



___ states:

Inputs: ??? and ???

Output: ???

• .

FSM: State Diagram

 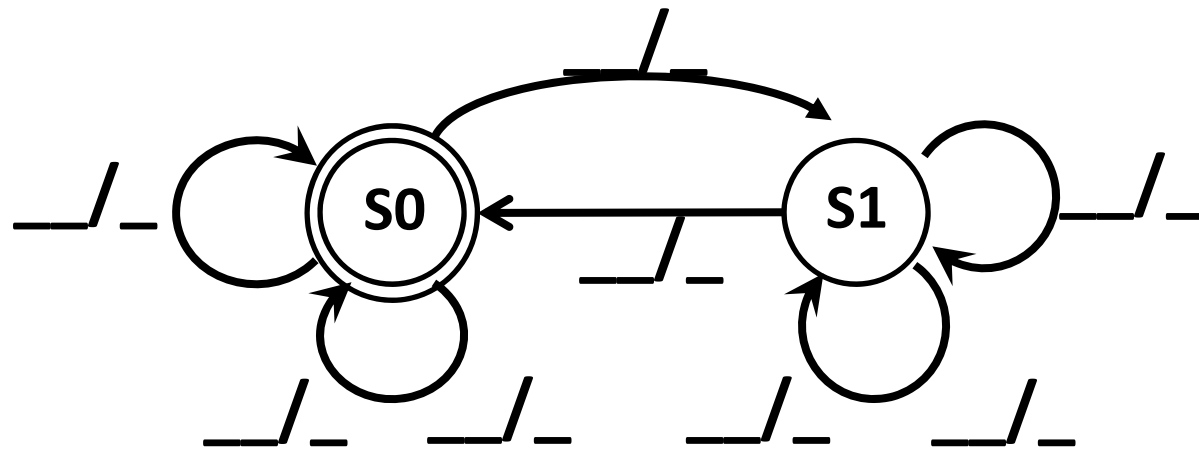


___ states:

Inputs: ??? and ???

Output: ???

• .


FSM: State Diagram

 

??	??	Current state	?	Next state

(2) Write down all input and state combinations

FSM: State Diagram

 

??	??	Current state	?	Next state

(3) Encode states, inputs, and outputs as bits

FSM: State Diagram

??	??	Current state	?	Next state

(4) Determine logic equations for next state and outputs

Summary

We can now build interesting devices with sensors

- Using combinational logic

We can also store data values

- Stateful circuit elements (D Flip Flops, Registers, ...)
- Clock to synchronize state changes
- State Machines or Ad-Hoc Circuits