
 



Datapath: addu

 


Datapath: addiu




Datapath: lw

 


Datapath: sw

 


Datapath: beq

 

Datapath: j

 


Performance

 

How fast can we run the clock?




Multi-Cycle Datapath

 

Observation: we can run the clock faster by partitioning the execution into multiple stages.



Multi-Cycle Datapath

 


Stages: instruction fetch, register fetch/decode, execute, memory, writeback.

Idea: break down single instruction execution into smaller parts, some instructions skip parts of execution.



Multi-Cycle Datapath

 

✓	✓	✓	✓	✓	lw \$1,-4(\$3)
✓	✓	✓		✓	add \$1,\$2,\$3
✓	✓	✓			beq \$1,\$2,L

- PC needs a write-enable signal
- Design FSM for control

(textbook has details: sections 5.4, 5.5)



Performance

Suppose we had:

- IF: 5ns, RD: 3ns, ALU: 6ns, MEM: 5ns, WB: 4ns

Single-cycle datapath cycle time: 23ns

Multi-cycle datapath:


- l_w: 30ns
- add: 24ns
- beq: 18ns

Is this better? Depends on the instruction mix!
(should have balanced pipeline stages)



Pipelining

 Why not start executing the next instruction as soon as the first one has been fetched?




Hardware resource conflict...



Pipelining

 
Simple fix: make all instructions take the same number of cycles.



Each instruction takes 30ns, but we complete an instruction every 6ns (caveat: flop/latch overhead).




Pipelined Datapath

 

Introduce positive-edge triggered flip-flops between pipeline stages to hold intermediate values.



Pipelined Datapath: Control

 

Basic idea: copy the instruction, and generate local control in each pipeline stage.




Pipelined Datapath: Timing

	IF	RD	EX	MEM	WB	
cycle i	ins1					ins1
	ins2	ins1				ins2
	ins3	ins2	ins1			ins3
	ins4	ins3	ins2	ins1		ins4
	ins5	ins4	ins3	ins2	ins1	ins5
						program

Instructions flow through the datapath, advancing every cycle.




Pipelined Datapath: Timing

 

- Flops between stages: positive-edge triggered
- PC, register file: negative-edge triggered




Single Instruction Execution

 


CLK




Single Instruction Execution

 


CLK

 


Single Instruction Execution

 

CLK

 

Single Instruction Execution

 

Register file output can change!

