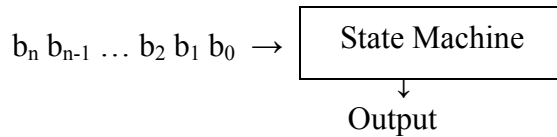



State Machines

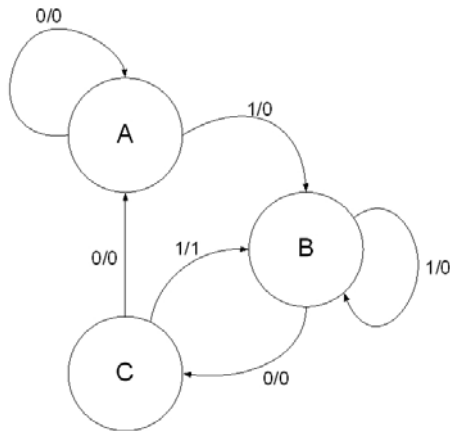Problem:

Implement a 3-bit sequence recognizer that produces a high on its output bit when the bit sequence 101 is recognized. Assume that the input is a bit sequence entering from the left one bit at a time:



Mealy Machine: outputs depend on both state and inputs (asynchronous output)



	S1	S0
A	0	0
B	0	1
C	1	0

On each arc, the label x/y means the input is x and the output is y.

Current State		Input	Next State		Output
S1	S0		S1'	S0'	Out
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	0	1	1
1	1	0	X	X	X
1	1	1	X	X	X


Using Espresso, the following reduced equations can be obtained:

$$S1' = S0 \cdot I$$

$$S0' = I$$

$$Out = S1 \cdot I$$

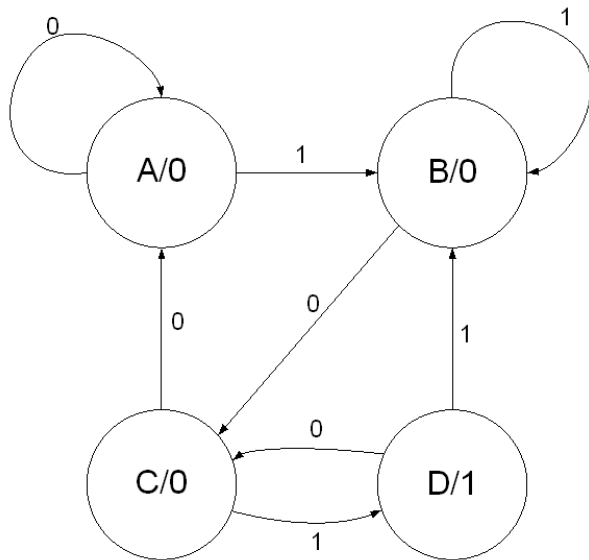Moore Machine: outputs depend only on states



	S1	S0
A	0	0
B	0	1
C	1	0
D	1	1

Note that in a Moore machine, the outputs are attached to the states, rather than the arcs.

Current State		Input	Next State		Output
S1	S0		S1'	S0'	Out
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	0	0	0
1	0	1	1	1	0
1	1	0	1	0	1
1	1	1	0	1	1

Using Espresso, the following reduced equations can be obtained:

$$S1' = S1 \cdot \underline{S0} \cdot I + S0 \cdot \underline{I}$$

$$S0' = I$$

$$\text{Out} = S1 \cdot S0$$