

CS 316: Logic

Kavita Bala

Fall 2007

Computer Science

Cornell University

Karnaugh maps

- Encoding of the truth table where adjacent cells differ in only one bit

a	b	out
0	0	0
0	1	0
1	0	0
1	1	1





truth table
for AND

ab

	00	01	11	10
0	0	0	1	0

Corresponding
Karnaugh map

Bigger Karnaugh Maps

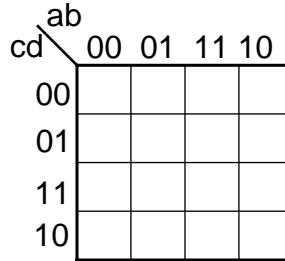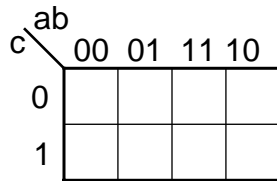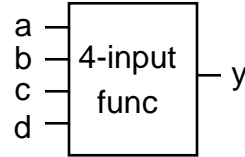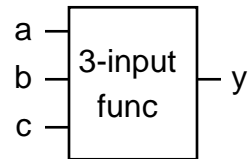


Kavita Bala, Computer Science, Cornell University

Minimization with Karnaugh maps (2)

a	b	c	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

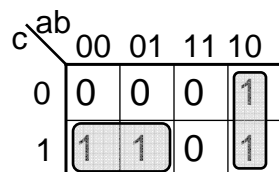- Karnaugh map minimization
 - Cover all 1's
 - Group adjacent blocks of 2^n 1's that yield a rectangular shape
 - Encode the common features of the rectangle
 - $out = \bar{a}\bar{b} + \bar{a}c$



Kavita Bala, Computer Science, Cornell University

Karnaugh Minimization Tricks (1)

c \ ab	00	01	11	10
0	0	1	1	1
1	0	0	1	0

- Minterms can overlap
– out = $b\bar{c} + a\bar{c} + ab$

c \ ab	00	01	11	10
0	1	1	1	1
1	0	0	1	0

- Minterms can span 2, 4, 8 or more cells
– out = $\bar{c} + ab$

Kavita Bala, Computer Science, Cornell University

Karnaugh Minimization Tricks (2)

cd \ ab	00	01	11	10
00	0	0	0	0
01	1	0	0	1
11	1	0	0	1
10	0	0	0	0

- The map wraps around
– out = $\bar{b}d$

cd \ ab	00	01	11	10
00	1	0	0	1
01	0	0	0	0
11	0	0	0	0
10	1	0	0	1

- out = $\bar{b}\bar{d}$

Kavita Bala, Computer Science, Cornell University

Karnaugh Minimization Tricks (3)

	ab			
cd	00	01	11	10
00	0	0	0	0
01	1	x	x	x
11	1	x	x	1
10	0	0	0	0

- “Don’t care” values can be interpreted individually in whatever way is convenient


- assume all x’s = 1
- out = d

	ab			
cd	00	01	11	10
00	1	0	0	x
01	0	x	x	0
11	0	x	x	0
10	1	0	0	1

- assume middle x’s = 0
- assume 4th column x = 1
- out = $\bar{b}\bar{d}$

Kavita Bala, Computer Science, Cornell University

Multiplexer

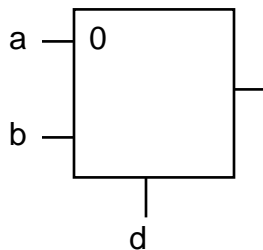


- A multiplexer selects between multiple inputs

- out = a, if d = 0
- out = b, if d = 1

- Build truth table
- Build Karnaugh map
- Derive logic diagram

Kavita Bala, Computer Science, Cornell University

Multiplexer Implementation

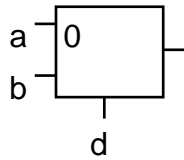


- Build a truth table

a	b	d	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Kavita Bala, Computer Science, Cornell University

Multiplexer Implementation

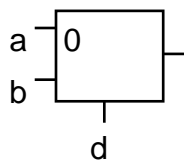


- Build the Karnaugh map

a	b	d	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

d \ ab	00	01	11	10
0	0	0	1	1
1	0	1	1	0

Kavita Bala, Computer Science, Cornell University

Multiplexer Implementation

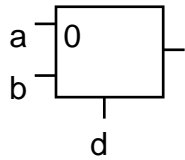

- Derive minimal logic equation


a	b	d	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

d \ ab	00	01	11	10
0	0	0	1	1
1	0	1	1	0

$$\text{out} = a\bar{d} + bd$$

Kavita Bala, Computer Science, Cornell University

Multiplexer Implementation

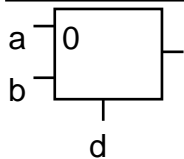


- Draw the circuit

a	b	d	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

d \ ab	00	01	11	10
0	0	0	1	1
1	0	1	1	0

$$\text{out} = a\bar{d} + bd$$

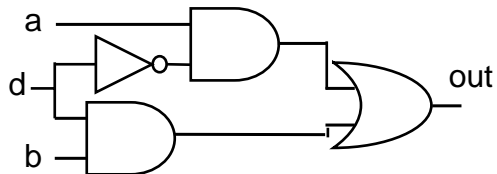



Kavita Bala, Computer Science, Cornell University

Summary

- We can now implement any logic circuit
 - Use P- and N-transistors to implement NAND or NOR gates
 - Use NAND or NOR gates to implement the logic circuit
 - Efficiency: use Karnaugh maps to find the minimal terms required

Kavita Bala, Computer Science, Cornell University


Logic Gates

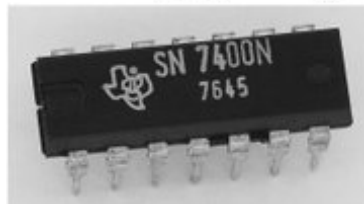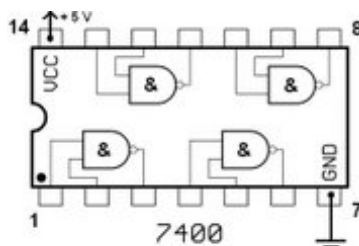

- One can buy gates separately
 - ex. 74xxx series of integrated circuits
 - cost ~\$1 per chip, mostly for packaging and testing
- Cumbersome, but possible to build devices using gates put together manually

Kavita Bala, Computer Science, Cornell University

Integrated Circuits

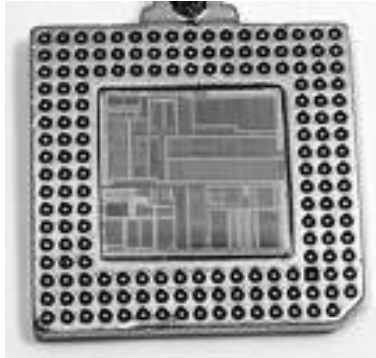

- Or one can manufacture a complete design using a custom mask
- Intel Pentium has approximately 125 million transistors

Kavita Bala, Computer Science, Cornell University

Voting machine

- Build something interesting
- A voting machine
 - Elections are coming up!
- Assume:
 - A vote is recorded on a piece of paper,
 - by punching out a hole
 - there are at most 7 choices
 - we will not worry about “hanging chads” or “invalids”

Kavita Bala, Computer Science, Cornell University

Voting machine


- For now, let's just display the numerical identifier to the ballot supervisor
 - we won't do counting yet, just decoding
 - we can use four photo-sensitive transistors to find out which hole is punched out



- A photo-sensitive transistor detects the presence of light
- Photo-sensitive material triggers the gate

Kavita Bala, Computer Science, Cornell University

Ballot Reading

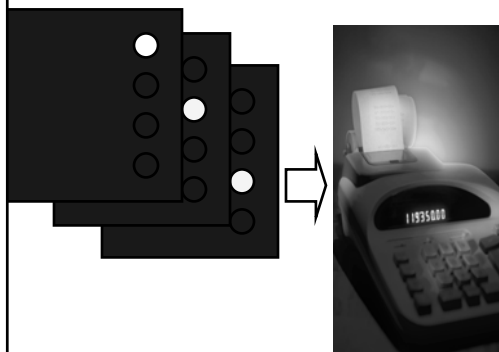


- Input: paper with a hole in it
- Out: number the ballot supervisor can record

Ballots

The 316 vote recording
machine

Kavita Bala, Computer Science, Cornell University

Encoders

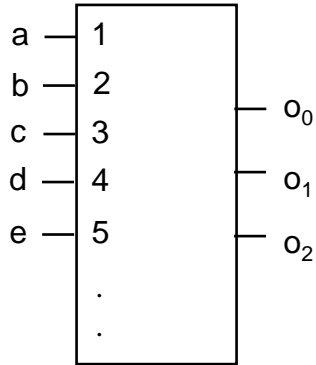

A 3-bit encoder
(7-to-3)
(5 inputs shown)

- N sensors in a row
- Want to distinguish which of the N sensors has fired
- Want to represent the firing sensor number in compact form
 - N might be large
 - Only one wire is on at any time
 - Silly to route N wires everywhere, better to encode in $\log N$ wires

Kavita Bala, Computer Science, Cornell University

Number Representations

$$\begin{array}{r} 37 \\ \hline 10^1 \quad 10^0 \end{array}$$

- Decimal numbers are written in base 10
 - $3 \times 10^1 + 7 \times 10^0 = 37$
- Just as easily use other bases
 - Base 2 - “Binary”
 - Base 8 - “Octal”
 - Base 16 - “Hexadecimal”

Kavita Bala, Computer Science, Cornell University

Number Representations

37

 $10^1 \ 10^0$

- Base conversion via repetitive division
 - Divide by base, write remainder, move left with quotient
 - Sanity check with 37 and 10

Kavita Bala, Computer Science, Cornell University

Binary Representation

- $37 = 32 + 4 + 1$

0100101

 $2^6 \ 2^5 \ 2^4 \ 2^3 \ 2^2 \ 2^1 \ 2^0$
64 32 16 8 4 2 1

Kavita Bala, Computer Science, Cornell University


Hexadecimal Representation

25
 $16^1 \ 16^0$

- 37 decimal = $(25)_{16}$
- Convention
 - Base 16 is written with a leading 0x
 - $37 = 0x25$
- Need extra digits!
 - 0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, C, D, E, F
- Binary to hexadecimal is easy
 - Divide into groups of 4, translate groupwise into hex digits

Kavita Bala, Computer Science, Cornell University

Encoder Truth Table

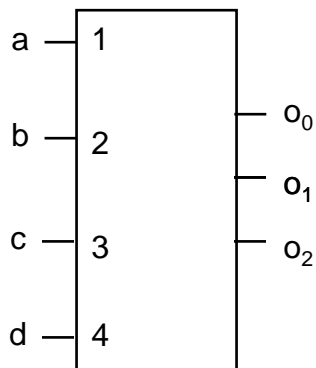


A 3-bit
encoder
with 4 inputs
for simplicity.

a	b	c	d		o2	o1	o0
0	0	0	0		0	0	0
1	0	0	0		0	0	1
0	1	0	0		0	1	0
0	0	1	0		0	1	1
0	0	0	1		1	0	0

- $o2 = \bar{a}\bar{b}\bar{c}d$
- $o1 = \bar{a}b\bar{c}d + a\bar{b}c\bar{d}$
- $o0 = \bar{a}b\bar{c}\bar{d} + a\bar{b}c\bar{d}$

Kavita Bala, Computer Science, Cornell University

Ballot Reading

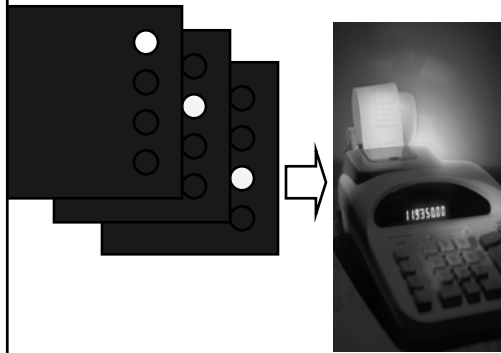


Ballots

The 316 voting machine

- Ok, we built first half of the machine
- Need to display the result

Kavita Bala, Computer Science, Cornell University


7-Segment LED Decoder

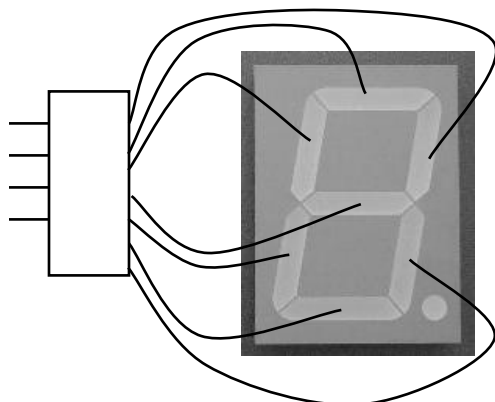

- 4 inputs encoded in binary
- 7 outputs, each driving an independent, rectangular LED
- Can display numbers
- Just a simple logic circuit
- Write the truth table

Kavita Bala, Computer Science, Cornell University


7-Segment LED Decoder

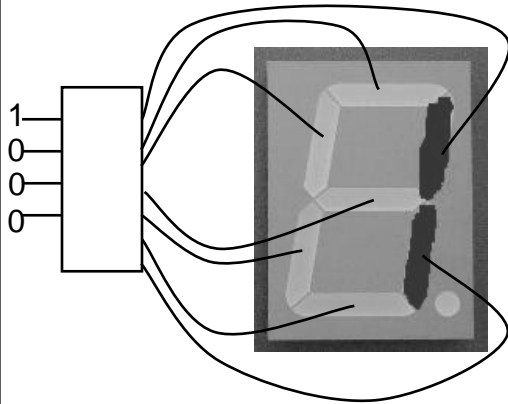

- 4 inputs encoded in binary
- 8 outputs, each driving an independent, rectangular LED
- Can display numbers

Kavita Bala, Computer Science, Cornell University

7-Segment LED Decoder

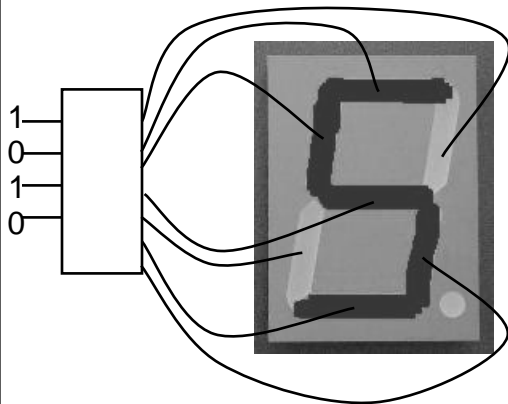


- 4 inputs encoded in binary
- 8 outputs, each driving an independent, rectangular LED
- Can display numbers

Kavita Bala, Computer Science, Cornell University

7-Segment Decoder Truth Table

i_3	i_2	i_1	i_0		o_0	o_1	o_2	o_3	o_4	o_5	o_6
0	0	0	0		1	1	1	0	1	1	1
0	0	0	1		1	0	0	0	0	0	1
0	0	1	0		1	1	0	1	1	1	0
0	0	1	1		1	1	0	1	0	1	1
0	1	0	0		1	0	1	1	0	0	1
0	1	0	1		0	1	1	1	0	1	1
0	1	1	0		0	1	1	1	1	1	1
0	1	1	1		1	1	0	0	0	0	0
1	0	0	0		1	1	1	1	1	1	1
1	0	0	1		1	1	1	1	0	1	1
1	0	1	0	A	1	1	1	1	1	0	1
1	0	1	1	B	0	0	1	1	1	1	1
				C							

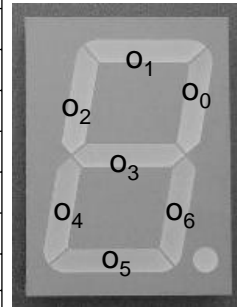


Exercise: find the error(s) in this truth table

Kavita Bala, Computer Science, Cornell University

7-Segment Decoder Truth Table


i_3	i_2	i_1	i_0		o_0	o_1	o_2	o_3	o_4	o_5	o_6
0	0	0	0		1	1	1	0	1	1	1
0	0	0	1		1	0	0	0	0	0	1
0	0	1	0		1	1	0	1	1	1	0
0	0	1	1		1	1	0	1	0	1	1
0	1	0	0		1	0	1	1	0	0	1
0	1	0	1		0	1	1	1	0	1	1
0	1	1	0		0	1	1	1	1	1	1
0	1	1	1		1	1	0	0	0	0	1
1	0	0	0		1	1	1	1	1	1	1
1	0	0	1		1	1	1	1	0	1	1
1	0	1	0	a	1	1	1	1	1	0	1
1	0	1	1	b	0	0	1	1	1	1	1
1	1	0	0	c	0	1	1	0	1	1	0
1	1	0	1	d	1	0	0	1	1	1	1
1	1	1	0	e	0	1	1	1	1	1	0
1	1	1	1	f							

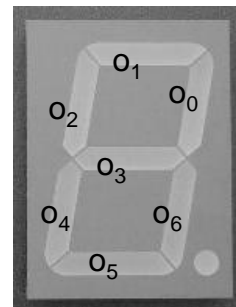

Kavita Bala, Computer Science, Cornell University

Ballot Reading

- Done!

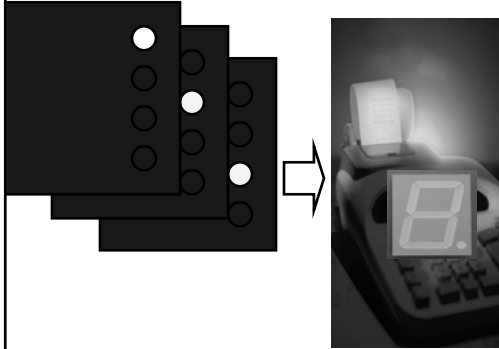

Ballots

The 316 voting machine

Kavita Bala, Computer Science, Cornell University