


# CS 316: Binary Arithmetic

**Kavita Bala**

**Fall 2007**

Computer Science

Cornell University

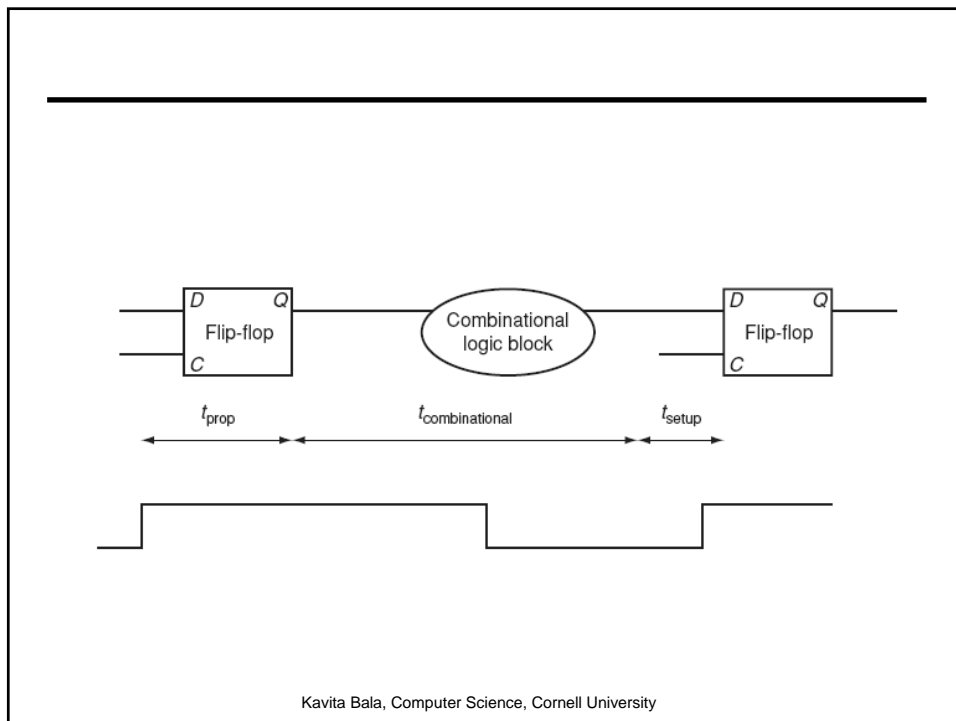

## References

---

- Look at Appendix B in textbook
- Look in Chapter 3 in textbook for today

Kavita Bala, Computer Science, Cornell University

## Recap

---

- We can build combinatorial circuits
  - Gates, Karnaugh maps, minimization
- We can build stateful circuits
  - Record 1-bit values in latches and flip-flops
- Powerful combination
  - We can build real, useful devices
  - But we will often need to perform arithmetic

Kavita Bala, Computer Science, Cornell University

## Binary Arithmetic

$$\begin{array}{r} 12 \\ + 25 \\ \hline 37 \end{array}$$


- Arithmetic works the same way regardless of base
  - Add the digits in each position
  - Propagate the carry

$$\begin{array}{r} 001100 \\ + 011010 \\ \hline 100110 \end{array}$$

- Unsigned binary addition is pretty easy
  - Combine two bits at a time
  - Along with a carry

Kavita Bala, Computer Science, Cornell University

## 1-bit Adder

 


A <sub>0</sub>	B <sub>0</sub>	C <sub>out</sub>	R <sub>0</sub>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

- Adds two 1-bit numbers, computes 1-bit result and carry out
- Useful for the rightmost binary digit, not much else

Kavita Bala, Computer Science, Cornell University

## 1-bit Adder with Carry

 


$C_i$	$A_i$	$B_i$	$C_{out}$	$R_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

- Adds two 1-bit numbers, along with carry-in, computes 1-bit result and carry out
- Can be cascaded to add N-bit numbers

Kavita Bala, Computer Science, Cornell University


## 4-bit Adder

 

- Adds two 4-bit numbers, along with carry-in, computes 4-bit result and overflow
- Overflow indicates that the result does not fit in 4 bits

Kavita Bala, Computer Science, Cornell University

## 4-bit Ripple Carry Adder

 

- First adder, 2 gate delay
- Second adder, 2 gate delay

Kavita Bala, Computer Science, Cornell University

## Observations

- Have to wait for C<sub>in</sub>
- Can we compute in parallel in some way?
- CLA carry look-ahead adder

Kavita Bala, Computer Science, Cornell University

## Carry Look Ahead Logic


---

- Can we reason independent of  $C_{in}$ ?
  - Just based on (A,B) only
- When is  $C_{out} == 1$ , irrespective of  $C_{in}$
- If  $C_{in} == 1$ , when is  $C_{out}$  also  $== 1$

Kavita Bala, Computer Science, Cornell University

## 1-bit CLA adder


---

 

- Create two terms: propagator, generator
- $g = 1$ , generates  $C_{out}$ :  $g = AB$ 
  - Irrespective of  $C_{in}$
- $p = 1$ , propagates  $C_{in}$  to  $C_{out}$ :  $p = A + B$
- $p$  and  $g$  generated in 1 cycle delay
- $R$  is 2 cycle delay after we get  $C_{in}$

Kavita Bala, Computer Science, Cornell University


## 4-bit CLA

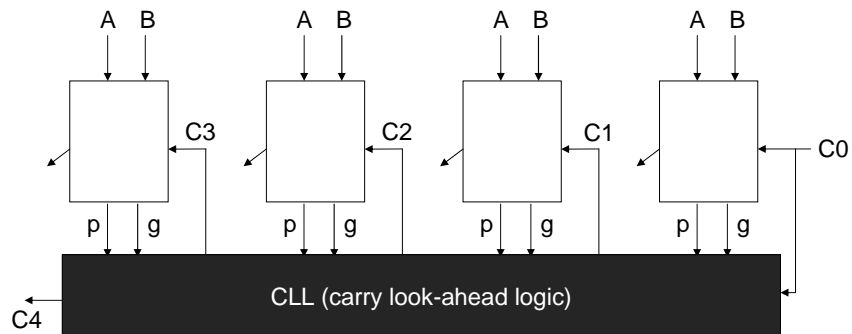

- CLL takes  $p, g$  from all 4 bits,  $C_0$  and generates all  $C_s$ 
  - 2 gate delay
- $C_1 = g_0 + p_0 C_0$ ,
- $C_2 = g_1 + p_1(g_0 + p_0 C_0) = g_1 + p_1 g_0 + p_1 p_0 C_0$
- $C_3 = g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 C_0$ ,
- $C_4 = g_3 + p_3 g_2 + p_3 p_2 g_1 + p_3 p_2 p_1 g_0 + p_3 p_2 p_1 p_0 C_0$

Kavita Bala, Computer Science, Cornell University

## 4-bit CLA

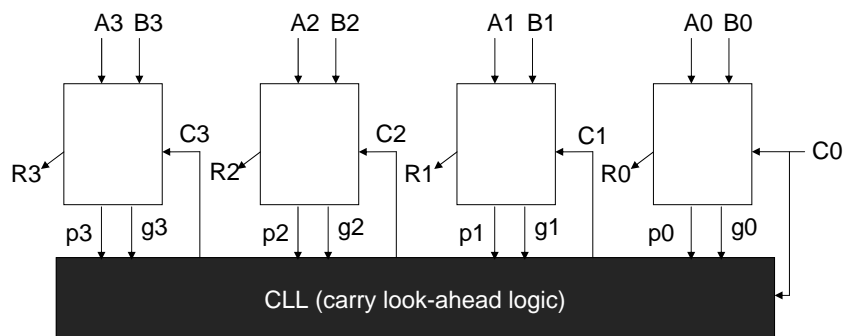

- Given  $A, B$ 's, all  $p, g$ 's are generated in 1 gate delay in parallel.
- Given all  $p, g$ 's, all  $C$ 's are generated in 2 gate delay in parallel.
- Given all  $C$ 's, all  $R$ 's are generated in 2 gate delay in parallel.
- Sequential operation in RCA is made into parallel operation!!

Kavita Bala, Computer Science, Cornell University

## Bigger CLAs?

---

- Can't do it for all 32 bits though
- So use hierarchical construction

Kavita Bala, Computer Science, Cornell University

## Arithmetic with Negative Numbers

---

- Negative numbers complicate arithmetic
- Recall that for addition and subtraction, the rules are:
  - Both positive => add, result positive
  - One +, one - => subtract small number from larger one
  - Both negative => add, result negative

Kavita Bala, Computer Science, Cornell University



## Arithmetic with Negative Numbers

---

- We could represent sign with an explicit bit
  - the “sign-magnitude form”
  - But arithmetic would be much easier to perform in hardware if we did not have to examine the operands’ signs
- Two’s complement representation enables arithmetic to be performed without examining the operands

Kavita Bala, Computer Science, Cornell University

## Two’s Complement

---

- Nonnegative numbers are represented as usual
  - 0 = 0000
  - 1 = 0001
  - 3 = 0011
  - 7 = 0111
- To negate a number, flip all bits, add one
  - -1: 1  $\Rightarrow$  0001  $\Rightarrow$  1110  $\Rightarrow$  1111
  - -3: 3  $\Rightarrow$  0011  $\Rightarrow$  1100  $\Rightarrow$  1101
  - -7: 7  $\Rightarrow$  0111  $\Rightarrow$  1000  $\Rightarrow$  1001
  - -8: 8  $\Rightarrow$  1000  $\Rightarrow$  0111  $\Rightarrow$  1000
  - -0: 0  $\Rightarrow$  0000  $\Rightarrow$  1111  $\Rightarrow$  0000 (this is good, -0 = +0)

Kavita Bala, Computer Science, Cornell University

## Two's Complement Facts

---

- Negative numbers have a leading 1
  - Similar to signed magnitude form
  - Largest negative=1000...0
  - Largest positive=0111...1
  - Top most bit: sign bit
- N bits can be used to represent
  - unsigned: the range  $0..2^N-1$
  - ex: 8 bits  $\Rightarrow 0..255$
  - two's complement: the range  $-(2^{N-1})..(2^{N-1})-1$
  - ex: 8 bits  $\Rightarrow (10000000)..(01111111) \Rightarrow -128..127$

Kavita Bala, Computer Science, Cornell University

## Want to change bit size of number?

---

- 4 bit to 8 bit
  - For positive number, just 0's in new 4 bits
  - For negative number, 1's in new 4 bits
- What about shifting
  - sll (shift left logical)
  - sra (shift right arithmetic), srl (shift right logical)

Kavita Bala, Computer Science, Cornell University

## Two's Complement Addition

---

- Perform addition as usual, regardless of sign
  - $1 = 0001$ ,  $3 = 0011$ ,  $7 = 0111$ ,  $0 = 0000$
  - $-1 = 1111$ ,  $-3 = 1101$ ,  $-7 = 1001$
- Examples
  - $1 + -1 = 1111 + 0001 = 0000$  (0)
  - $-3 + -1 = 1111 + 1101 = 1100$  (-4)
  - $-7 + 3 = 1001 + 0011 = 1100$  (-4)

Kavita Bala, Computer Science, Cornell University

## Overflow


---

- When can it occur?
  - If you add a negative and positive number
    - Cannot occur (Why?)
  - If you add two negatives or two positives
    - Can occur (Why?)
  - Add two positives, and get a negative number
  - Or, add two negatives, get a positive number
    - Overflow!
  - Overflow when
    - Carry into most significant bit (msb)  $\neq$  carry out of msb

Kavita Bala, Computer Science, Cornell University

## Two's Complement Adder

- Let's build a two's complement adder

 


- Already built, just needed to modify overflow checking

Kavita Bala, Computer Science, Cornell University

 
## Two's Complement Subtraction

- Subtraction is simply addition, where one of the operands has been negated
  - Negation is done by inverting all bits and adding one



Kavita Bala, Computer Science, Cornell University

## A Calculator

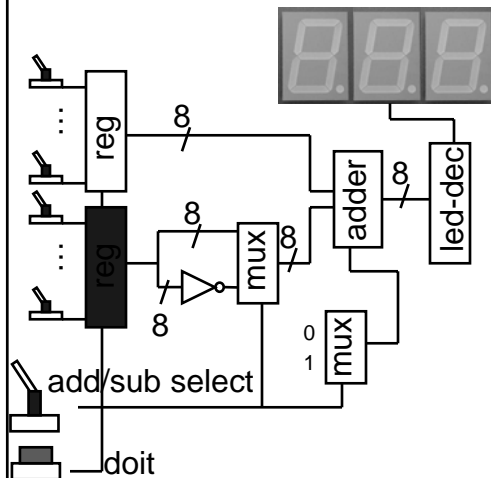

- Enter numbers to be added or subtracted using toggle switches
- Select: ADD or SUBTRACT
- Muxes feed A and B, or A and  $-B$ , to the 8-bit adder
- The 8-bit decoder for the hex display is straightforward

Kavita Bala, Computer Science, Cornell University

## Summary

- We can now perform arithmetic
  - And build basic circuits that operate on numbers

Kavita Bala, Computer Science, Cornell University