

CS 316:
Arithmetic (contd.)

Kavita Bala
Fall 2007
Computer Science
Cornell University

Announcements

- Office Hours
 - No recitation this week; instead TAs will hold office hours and discuss

Two's Complement Addition

- Perform addition as usual, regardless of sign
 - $1 = 0001$, $3 = 0011$, $7 = 0111$, $0 = 0000$
 - $-1 = 1111$, $-3 = 1101$, $-7 = 1001$
- Examples
 - $1 + -1 = 1111 + 0001 = 0000$ (0)
 - $-3 + -1 = 1111 + 1101 = 1100$ (-4)
 - $-7 + 3 = 1001 + 0011 = 1100$ (-4)

Kavita Bala, Computer Science, Cornell University


Overflow

- When can it occur?
 - If you add a negative and positive number
 - Cannot occur (Why?)
 - If you add two negatives or two positives
 - Can occur (Why?)
 - Add two positives, and get a negative number
 - Or, add two negatives, get a positive number
 - Overflow!
 - Overflow when
 - Carry into most significant bit (msb) \neq carry out of msb

Kavita Bala, Computer Science, Cornell University

Two's Complement Adder

- Let's build a two's complement adder

 


- Already built, just needed to modify overflow checking

Kavita Bala, Computer Science, Cornell University


Two's Complement Subtraction

 - Subtraction is simply addition, where one of the operands has been negated
 - Negation is done by inverting all bits and adding one



Kavita Bala, Computer Science, Cornell University

A Calculator

 

- Enter numbers to be added or subtracted using toggle switches
- Select: ADD or SUBTRACT
- Muxes feed A and B, or A and $-B$, to the 8-bit adder
- The 8-bit decoder for the hex display is straightforward


Kavita Bala, Computer Science, Cornell University

Summary

- We can now perform arithmetic
 - And build basic circuits that operate on numbers

Kavita Bala, Computer Science, Cornell University

A Vote Counter

 

- Data values flow from set of parallel registers (a register file)
- to the addition unit
- back into the register file

Kavita Bala, Computer Science, Cornell University

CS 316: Memory

Kavita Bala

Fall 2007

Computer Science
Cornell University

Register File

- Set of registers
 - Read or written
 - Use register number to access it
- Read or write ports
 - Decoder for each port
- D flip flops to store bits

Kavita Bala, Computer Science, Cornell University


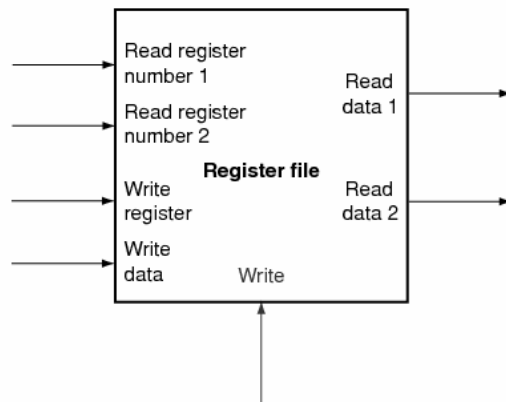
 


FIGURE B.8.7 A register file with two read ports and one write port has five inputs and two outputs. The control input Write is shown in color.

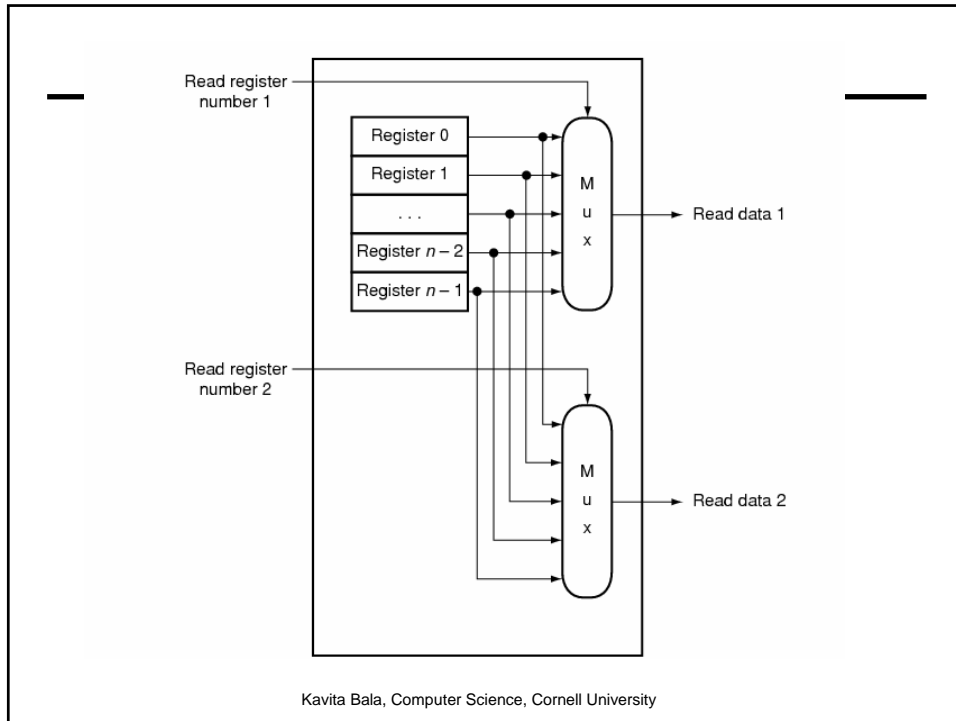Kavita Bala, Computer Science, Cornell University




Memory

- Various technologies
 - S-RAM, D-RAM, NV-RAM
- Non-Volatile RAM
 - Data remains valid even through power outages
 - More expensive
 - Limited lifetime; after 100000 to 1M writes, NV-RAM degrades
- Flash cards

Kavita Bala, Computer Science, Cornell University

Static RAM: SRAM

 - Static-RAM
 - So called because once stored, data values are stable as long as electricity is supplied
 - Based on regular flip-flops with gates



How to build large memories?

- Cannot use a 4M->1 multiplexer!
- Use a shared line (called bit line)
- Multiple memory cells can assert line
 - Need 3 state buffer
 - 3 states: asserted (1), deasserted (0), or high impedance

Kavita Bala, Computer Science, Cornell University


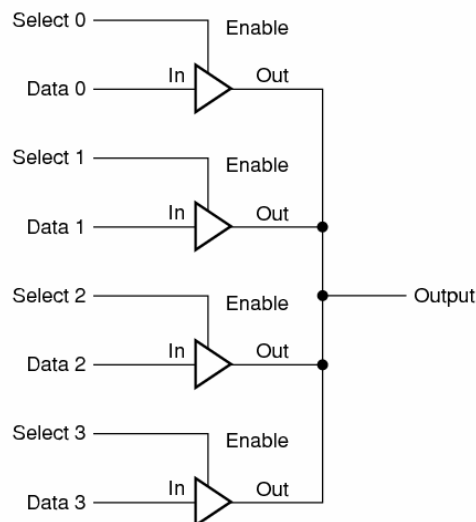


FIGURE B.9.2 Four three-state buffers are used to form a multiplexor. Only one of the four Select inputs can be asserted. A three-state buffer with a deasserted Output enable has a high-impedance output that allows a three-state buffer whose Output enable is asserted to drive the shared output line.

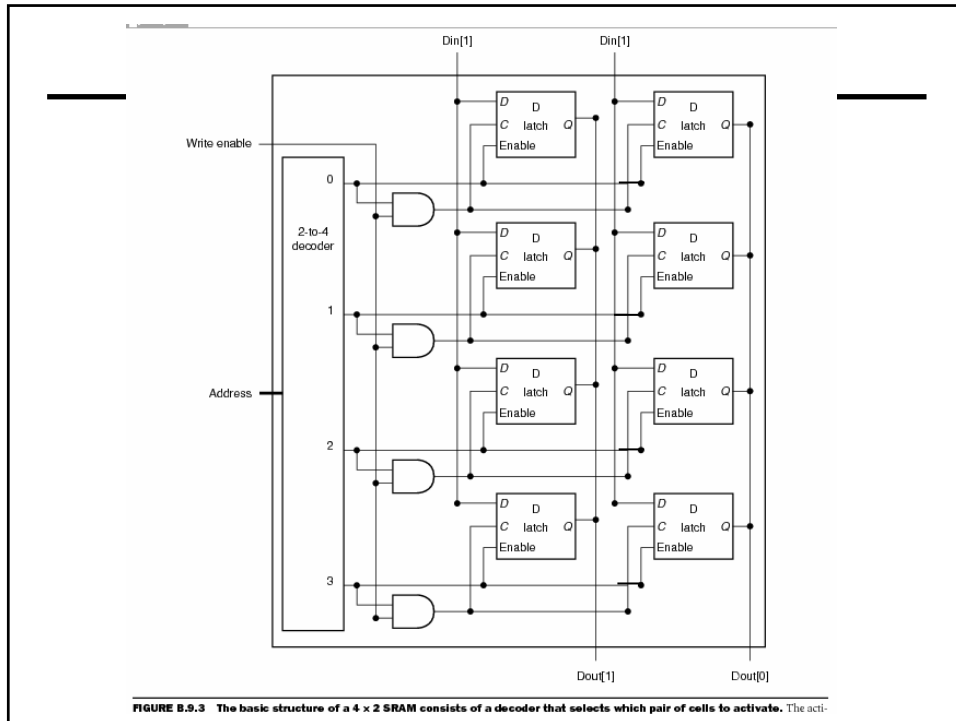Kavita Bala, Computer Science, Cornell University



Big Memories

- Tri state buffer got rid of big mux
- But still need a big decoder to pick the right entry
 - $4M \times 8$ SRAM requires
 - 22 to 4M decoder
 - And 4M lines!
- Instead
 - Rectangular arrays
 - 2-step decode

Parallel Memory Banks

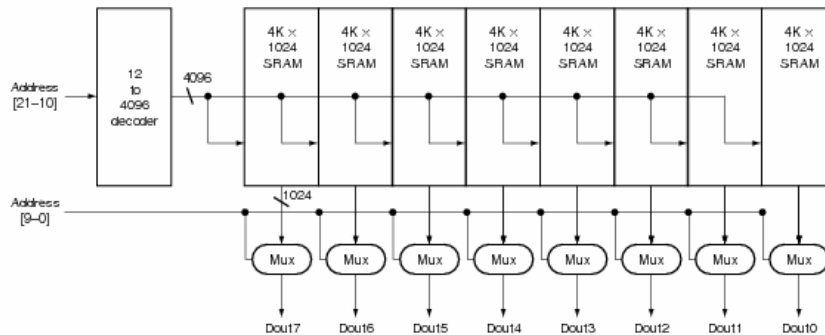


FIGURE B.9.4 Typical organization of a $4\text{M} \times 8$ SRAM as an array of $4\text{K} \times 1024$ arrays. The first decoder generates the addresses for eight $4\text{K} \times 1024$ arrays; then a set of multiplexers is used to select 1 bit from each 1024-bit-wide array. This is a much easier design than a single-level decode that would need either an enormous decoder or a gigantic multiplexer. In practice, a modern SRAM of this size would probably use an even larger number of blocks, each somewhat smaller.

Kavita Bala, Computer Science, Cornell University

SRAM

- Needs a few gates per cell
- Used for caches (we talk about this later)
- For higher density, use DRAM

Kavita Bala, Computer Science, Cornell University