

Lec 3: State and Finite State Machines

Kavita Bala
CS 3410, Fall 2008
Computer Science
Cornell University

Announcements


- Class newsgroup created
- Use it for partner finding
- First assignment is to find partners
 - Due this Friday
- Sections are on this week
- HW 1 out tomorrow
 - Work alone

Stateful Components



- Until now is combinatorial logic
 - Output is computed when inputs are present
 - System has no internal state
 - Nothing computed in the present can depend on what happened in the past!
- Need a way to record data
- Need a way to build stateful circuits
- Need a state-holding device

© Kavita Bala, Computer Science, Cornell University

Bistable Devices

 


- In stable state, $\bar{A} = B$

  

- How do we change the state?

© Kavita Bala, Computer Science, Cornell University

SR Latch

 


S	R	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	0	1
1	0	1	0
1	1	?	?

- Set-Reset (S-R) Latch
- Q: Stored value and its complement
- S=1 and R=1 ?

© Kavita Bala, Computer Science, Cornell University

D Latch

D	\bar{D}	Q	\bar{Q}
0	1	0	1
1	0	1	0

 


- Data Latch
 - Easier to use than an SR latch
 - No possibility of entering an undefined state
- When D changes, Q changes
 - ... immediately (after a delay of 2 Ors and 2 NOTs)
- Need to control when the output changes

© Kavita Bala, Computer Science, Cornell University

Clocks

 - Clocks help with modifying the contents of state-holding elements
- A free running signal
 - Generated by an oscillating crystal
- Clock signal has a fixed cycle time : cycle period
- Clock frequency = $1/\text{cycle time}$



Edge-triggering


- Can design circuits to change on the rising or falling edge
- Trigger on rising edge = positive edge-triggered
- Trigger on falling edge = negative edge-triggered
- Inputs must be stable just before the triggering edge



© Kavita Bala, Computer Science, Cornell University

First Attempt



- How does the output behave?

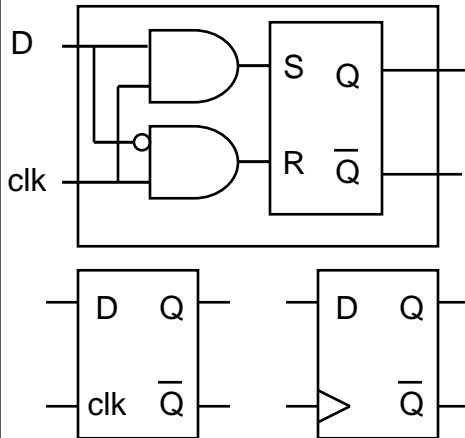

© Kavita Bala, Computer Science, Cornell University


First Attempt

- How does the output behave?

  

© Kavita Bala, Computer Science, Cornell University


First Attempt

 

- How does the output behave?
- Changes in D that occur when the clock is low are deferred until clock high
- Changes when clock is high are registered immediately

© Kavita Bala, Computer Science, Cornell University


Master-Slave Flip-Flop

 


- Outputs change only on falling edges
- Data is captured on rising edges
- 1 cycle delay – but works out perfectly – data for the next stage is ready 1 cycle ahead of time

© Kavita Bala, Computer Science, Cornell University

Registers

 


 - A register is simply a set of master-slave flip-flops in parallel with a shared clock



© Kavita Bala, Computer Science, Cornell University


Example: Keyboard

 

- When a key is pressed
 - Compute a 7-bit key identifier
- Store this keycode
 - The computer may not be ready to read it right away

© Kavita Bala, Computer Science, Cornell University

Keyboard with Last Key Display

 

© Kavita Bala, Computer Science, Cornell University

Summary

- We can now build interesting devices with sensors
 - Using combinatorial logic
- We can also store data values
 - In state-holding elements
 - Coupled with clocks

© Kavita Bala, Computer Science, Cornell University

Finite State Machines

Finite State Machines

- An electronic machine which has
 - external inputs
 - externally visible outputs
 - internal state
- Output and next state depend on
 - inputs
 - current state

Abstract Model of FSM

Machine is

$$M = (S, I, O, \delta)$$

S : Finite set of states

I : Finite set of inputs


O : Finite set of outputs

δ : State transition function

- Next state depends on present input and present state


© Kavita Bala, Computer Science, Cornell University

Primitive State Diagram

 


© Kavita Bala, Computer Science, Cornell University

Machine State Diagram

 

© Kavita Bala, Computer Science, Cornell University

Automata Model

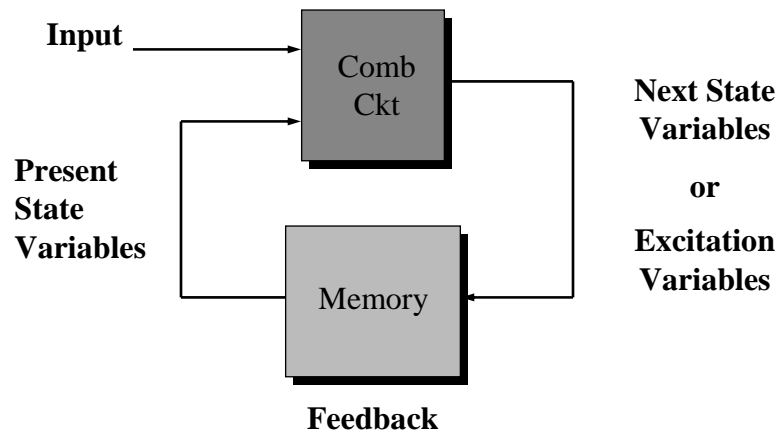


© Kavita Bala, Computer Science, Cornell University

Designing a FSM

- Draw a state diagram
- Write down state transition table
- Assign numbers to states
- Determine logic equations for all flip-flops and outputs

© Kavita Bala, Computer Science, Cornell University


A Simple Example

 

- Goal: flash hello on LEDs
- Inputs: clock
- Outputs: Just one 7-segment LED
- Flash “h” then “e” then “l” then “l” then “o”
 - h = <0011101>
 - e = <0111110>
 - l = <0010110>
 - o = <1110111>

© Kavita Bala, Computer Science, Cornell University

HELLObox: State Diagram

 

- Determine the transitions
 - label all edges (transitions) with the inputs that cause them, unlabeled edges are unconditional transitions
 - show start state

© Kavita Bala, Computer Science, Cornell University

HELLObox: State Table

- Build state table
 - rote encoding of the state diagram

Current State	Next State	Output
S0	S1	0011101
S1	S2	0111110
S2	S3	0010110
S3	S4	0010110
S4	S0	1110111

© Kavita Bala, Computer Science, Cornell University

HELLObox: State Assignment 1

- Assign bit patterns to states


- Try to make resulting device simple
- One option is shown

Current State	Next State	Output
000	001	0011101
001	010	0111110
010	011	0010110
011	100	0010110
100	000	1110111

- Determine logic equations for
 - every bit of output
 - next state
 - for every flip-flop and output

© Kavita Bala, Computer Science, Cornell University

HELLObox #1

 

- 10 bits of information (7 outputs + 3 bits of next state) are computed by the combinational circuit
- All 10 bits have non-trivial logic equations

© Kavita Bala, Computer Science, Cornell University


HELLObox: State Assignment 2

- Assign bit patterns to states to make the resulting device simple
- Here, we use far more bits than necessary
 - to simplify the combinatorial circuit

Current State	Next State	Output
00111010	01111100	0011101
01111100	00101100	0111110
00101100	00101101	0010110
00101101	11101110	0010110
11101110	00111010	1110111

© Kavita Bala, Computer Science, Cornell University

HELLObox #2

 

- 15 bits of information (7 outputs + 8 bits of next state) are computed by the combinatorial circuit
- 8 bits have non-trivial logic equations
 - all 7 outputs are simple pass-throughs

© Kavita Bala, Computer Science, Cornell University