

# Lec 4: Finite State Machines and Arithmetic

**Kavita Bala**  
**CS 3410, Fall 2008**  
Computer Science  
Cornell University

## References


---

- Look at Appendix B in textbook
- Look in Chapter 3 in textbook for today
 
## FSM: Serial Adder

---


- Add two input bit streams
  - streams are sent with least-significant-bit (lsb) first



© Kavita Bala, Computer Science, Cornell University

## FSM: State Diagram

---

 

- Two states: S0 (no carry), S1 (carry in)
- Inputs: a and b
- Output: z
  - Arcs labelled w/ input bits a and b, and output z

© Kavita Bala, Computer Science, Cornell University

## Serial Adder: State Table

a	b	state	z	next state
0	0	S0	0	S0
0	1	S0	1	S0
1	0	S0	1	S0
1	1	S0	0	S1
0	0	S1	1	S0
0	1	S1	0	S1
1	0	S1	0	S1
1	1	S1	1	S1

- Write down all input and state combinations

© Kavita Bala, Computer Science, Cornell University


## Serial Adder: State Assignment

a	b	s	z	s'
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

- Two states, so 1-bit is sufficient
  - A single flip-flop will encode the state

© Kavita Bala, Computer Science, Cornell University

## Serial Adder: Circuit

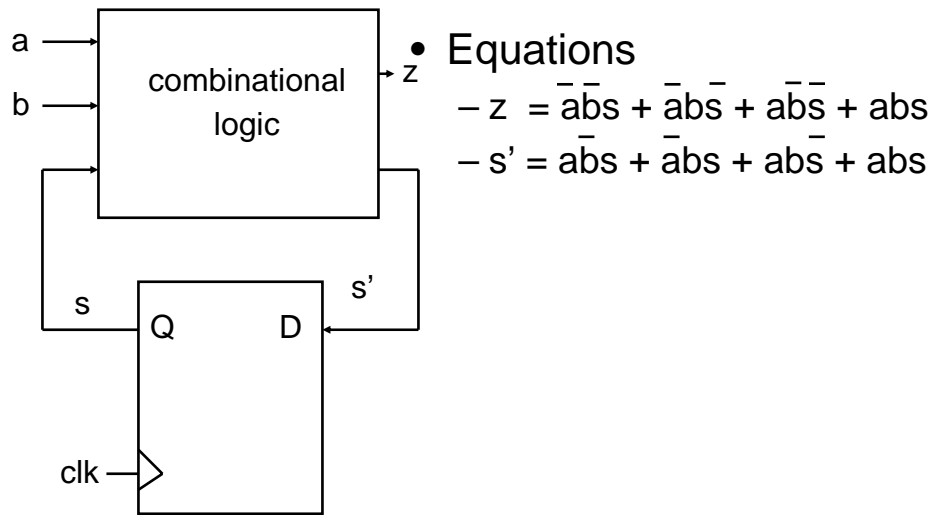

© Kavita Bala, Computer Science, Cornell University

## Recap

- We can build combinatorial circuits
  - Gates, minimization
- We can build stateful circuits
  - Record 1-bit values in latches and flip-flops
- Powerful combination
  - We can build real, useful devices
  - But we will often need to perform arithmetic

© Kavita Bala, Computer Science, Cornell University

## Binary Arithmetic

$$\begin{array}{r} 12 \\ + 25 \\ \hline 37 \end{array}$$


- Arithmetic works the same way regardless of base
  - Add the digits in each position
  - Propagate the carry

$$\begin{array}{r} 001100 \\ + 011010 \\ \hline 100110 \end{array}$$

- Unsigned binary addition is pretty easy
  - Combine two bits at a time
  - Along with a carry

© Kavita Bala, Computer Science, Cornell University

## 1-bit Adder

 


A <sub>0</sub>	B <sub>0</sub>	C <sub>out</sub>	R <sub>0</sub>
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

- Adds two 1-bit numbers, computes 1-bit result and carry out
- Useful for the rightmost binary digit, not much else

© Kavita Bala, Computer Science, Cornell University

## 1-bit Adder with Carry

 


$C_i$	$A_i$	$B_i$	$C_{out}$	$R_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

- Adds two 1-bit numbers, along with carry-in, computes 1-bit result and carry out
- Can be cascaded to add N-bit numbers

© Kavita Bala, Computer Science, Cornell University

## 4-bit Adder

 

- Adds two 4-bit numbers, along with carry-in, computes 4-bit result and overflow
- Overflow indicates that the result does not fit in 4 bits

© Kavita Bala, Computer Science, Cornell University

## Two Questions

---

- Addition is very important
  - Is this design fast enough?
  - Also, is this design general enough?

© Kavita Bala, Computer Science, Cornell University

## Arithmetic with Negative Numbers

---

- Negative numbers complicate arithmetic
- Recall that for addition and subtraction, the rules are:
  - Both positive => add, result positive
  - One +, one - => subtract small number from larger one
  - Both negative => add, result negative

© Kavita Bala, Computer Science, Cornell University

## Arithmetic with Negative Numbers

---

- We could represent sign with an explicit bit
  - the “sign-magnitude form”
  - But arithmetic would be much easier to perform in hardware if we did not have to examine the operands’ signs
- Two’s complement representation enables arithmetic to be performed without examining the operands

© Kavita Bala, Computer Science, Cornell University

## Two’s Complement

---

- Nonnegative numbers are represented as usual
  - 0 = 0000
  - 1 = 0001
  - 3 = 0011
  - 7 = 0111
- To negate a number, flip all bits, add one
  - -1: 1  $\Rightarrow$  0001  $\Rightarrow$  1110  $\Rightarrow$  1111
  - -3: 3  $\Rightarrow$  0011  $\Rightarrow$  1100  $\Rightarrow$  1101
  - -7: 7  $\Rightarrow$  0111  $\Rightarrow$  1000  $\Rightarrow$  1001
  - -8: 8  $\Rightarrow$  1000  $\Rightarrow$  0111  $\Rightarrow$  1000
  - -0: 0  $\Rightarrow$  0000  $\Rightarrow$  1111  $\Rightarrow$  0000 (this is good, -0 = +0)

© Kavita Bala, Computer Science, Cornell University



## Two's Complement Facts

---

- Negative numbers have a leading 1
  - Similar to signed magnitude form
  - Largest negative=1000...0
  - Largest positive=0111...1
  - Top most bit: sign bit
- N bits can be used to represent
  - unsigned: the range  $0..2^N-1$
  - ex: 8 bits  $\Rightarrow 0..255$
  - two's complement: the range  $-(2^{N-1})..(2^{N-1})-1$
  - ex: 8 bits  $\Rightarrow (10000000)..(01111111)$
  - $\Rightarrow -128..127$

© Kavita Bala, Computer Science, Cornell University

## Want to change bit size of number?

---

- 4 bit to 8 bit
  - For positive number, just 0's in new 4 bits
  - For negative number, 1's in new 4 bits
- What about shifting
  - sll (shift left logical)
  - sra (shift right arithmetic)
  - srl (shift right logical)

© Kavita Bala, Computer Science, Cornell University

## Two's Complement Addition

---

- Perform addition as usual, regardless of sign
  - $1 = 0001$ ,  $3 = 0011$ ,  $7 = 0111$ ,  $0 = 0000$
  - $-1 = 1111$ ,  $-3 = 1101$ ,  $-7 = 1001$
- Examples
  - $1 + -1 = 1111 + 0001 = 0000$  (0)
  - $-3 + -1 = 1111 + 1101 = 1100$  (-4)
  - $-7 + 3 = 1001 + 0011 = 1100$  (-4)
  - $7 + (-3) = 0111 + 1101 = 0100$  (4)
  - $-7 + 1$ ,  $-7 + -3$ ,  $-7 + -1$

© Kavita Bala, Computer Science, Cornell University

## Overflow

---


- When can it occur?
  - If you add a negative and positive number
    - Cannot occur (Why?)
  - If you add two negatives or two positives
    - Can occur (Why?)
  - Add two positives, and get a negative number
  - Or, add two negatives, get a positive number
    - Overflow!
  - Overflow when
    - Carry into most significant bit (msb)  $\neq$  carry out of msb

© Kavita Bala, Computer Science, Cornell University

## Two's Complement Adder

---

- Let's build a two's complement adder

 

- Already built, just needed to modify overflow checking

© Kavita Bala, Computer Science, Cornell University

## Subtraction


---

- Why create a new circuit?
- Just use addition
  - How?

© Kavita Bala, Computer Science, Cornell University

 
## Two's Complement Subtraction

- Subtraction is simply addition, where one of the operands has been negated
  - Negation is done by inverting all bits and adding one



© Kavita Bala, Computer Science, Cornell University

## A Calculator

 

- Enter numbers to be added or subtracted using toggle switches
- Select: ADD or SUBTRACT
- Muxes feed A and B, or A and  $-B$ , to the 8-bit adder
- The 8-bit decoder for the hex display is straightforward

© Kavita Bala, Computer Science, Cornell University