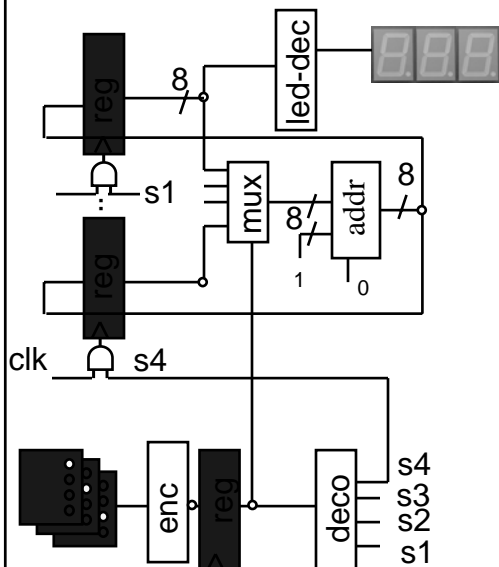


# Lec 5: Memory and a Simple Processor

**Kavita Bala**  
**CS 3410, Fall 2008**  
Computer Science  
Cornell University

## A Vote Counter



- Encode
- Decode
- Register file of counts
- Data values flow from register file
- To addition unit
- Back to register file

© Kavita Bala, Computer Science, Cornell University

## Two Questions

---


- Addition is very important
  - Is this design fast enough?
  - Also, is this design general enough?

© Kavita Bala, Computer Science, Cornell University
 
## Performance

---


- Speed of a circuit is affected by the number of gates in series (on the *critical path* or the *deepest level of logic*)



- The speed of a gate is affected by the number of inputs

© Kavita Bala, Computer Science, Cornell University

## 4-bit Ripple Carry Adder

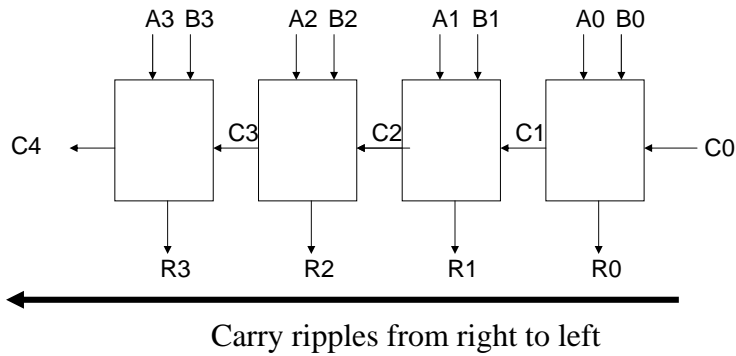

- First adder, 2 gate delay
- Second adder, 2 gate delay

© Kavita Bala, Computer Science, Cornell University

## Observations

- Have to wait for C<sub>in</sub>
- Can we compute in parallel in some way?
- CLA carry look-ahead adder

© Kavita Bala, Computer Science, Cornell University

## Carry Look Ahead Logic


---

- Can we reason independent of  $C_{in}$ ?
  - Just based on (A,B) only
- When is  $C_{out} == 1$ , irrespective of  $C_{in}$
- If  $C_{in} == 1$ , when is  $C_{out}$  also == 1

© Kavita Bala, Computer Science, Cornell University

## 1-bit CLA adder


---

 

- Create two terms: propagator, generator
- $g = 1$ , generates  $C_{out}$ :  $g = AB$ 
  - Irrespective of  $C_{in}$
- $p = 1$ , propagates  $C_{in}$  to  $C_{out}$ :  $p = A \text{ xor } B$
- $p$  and  $g$  generated in 1 cycle delay
- $R$  is 2 cycle delay after we get  $C_{in}$

© Kavita Bala, Computer Science, Cornell University

## 4-bit CLA

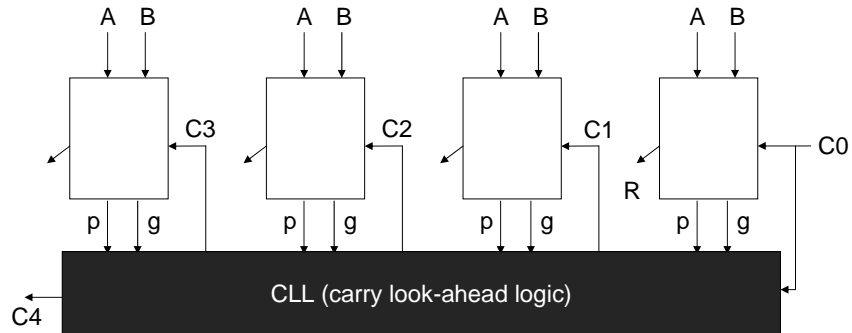

- CLL takes p,g from all 4 bits, C0 and generates all Cs

- 2 gate delay

$$C1 = g0 + p0C0$$

$$C2 = g1 + p1C1$$


$$= g1 + p1(g0 + p0C0) = g1 + p1g0 + p1p0C0$$

$$C3 = g2 + p2g1 + p2p1g0 + p2p1p0C0$$

$$C4 = g3 + p3g2 + p3p2g1 + p3p2p1g0 + p3p2p1p0C0$$

© Kavita Bala, Computer Science, Cornell University

## 4-bit CLA

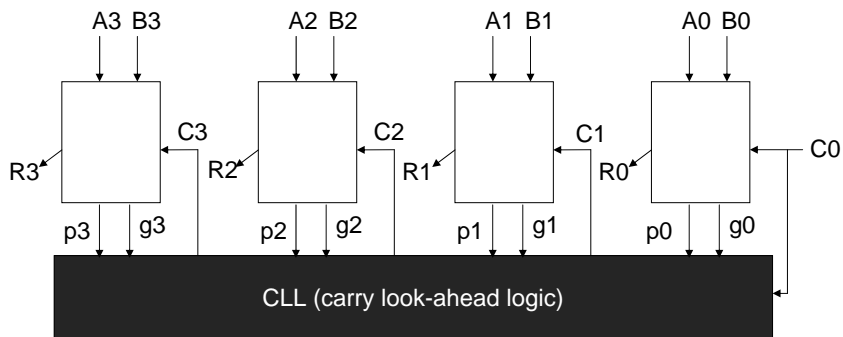

- Given A,B's, all p,g's are generated in 1 gate delay in parallel.
- Given all p,g's, all C's are generated in 2 gate delay in parallel.
- Given all C's, all R's are generated in 2 gate delay in parallel.

- Sequential operation in RCA is made into parallel operation!!

© Kavita Bala, Computer Science, Cornell University

## Ripple Carry vs Carry Lookahead

---

- Ripple carry adder vs Carry lookahead adder for 8 or 16 bits
  - 2 x 8 vs. 5
  - 2 x 16 vs. 5
- Can't do it for all 32 bits though
- So use hierarchical construction

© Kavita Bala, Computer Science, Cornell University


Memory

## Register File

---



- Set of registers
  - Read or written
  - Use register number to access it
- Read or write ports
  - Decoder for each port
- D or SR flip flops to store bits

© Kavita Bala, Computer Science, Cornell University

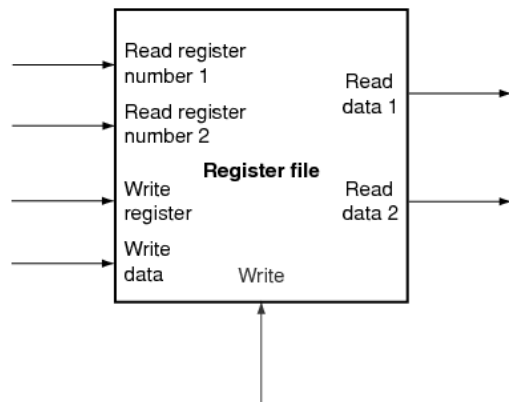

**FIGURE B.8.7** A register file with two read ports and one write port has five inputs and two outputs. The control input Write is shown in color.

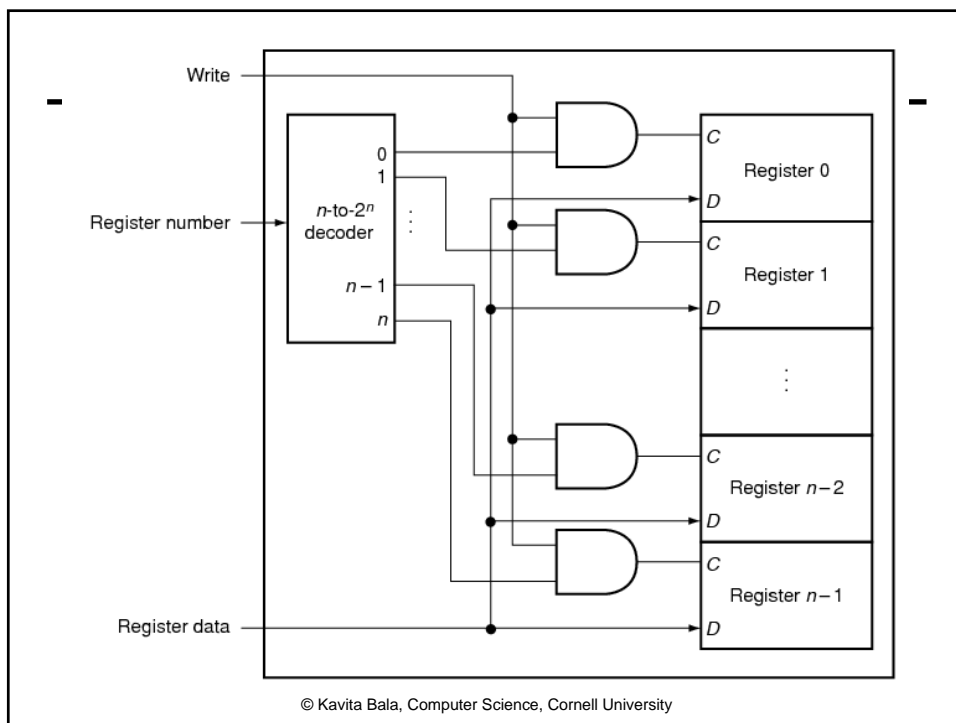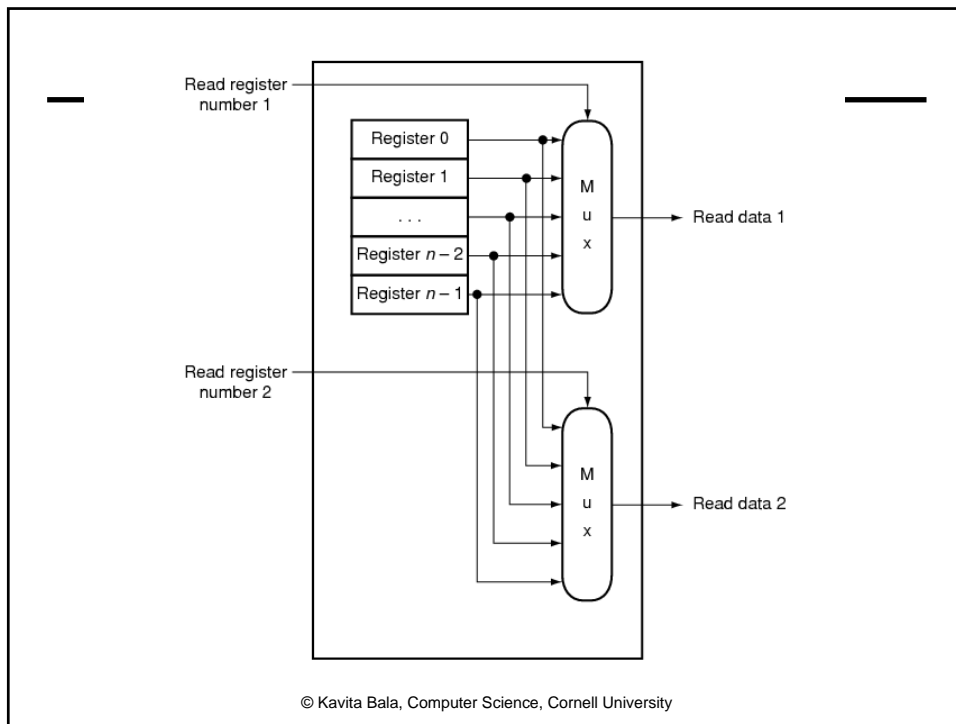© Kavita Bala, Computer Science, Cornell University





# Memory

---


- Various technologies
  - S-RAM, D-RAM, NV-RAM
- Non-Volatile RAM
  - Data remains valid even through power outages
  - More expensive
  - Limited lifetime; after 100000 to 1M writes, NV-RAM degrades
- Flash cards

© Kavita Bala, Computer Science, Cornell University

 
# Static RAM: SRAM

---

- Static-RAM
  - So called because once stored, data values are stable as long as electricity is supplied
  - Based on regular flip-flops with gates



## Tristate Buffers

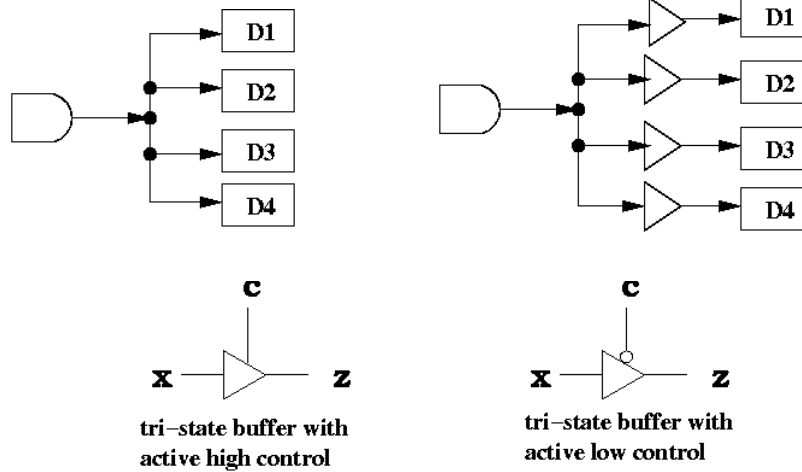



## Tristate Buffers

- 3 states
  - asserted (1)
  - deasserted (0)
  - high impedance (Z)

<b>c</b>	<b>x</b>	<b>z</b>
<b>0</b>	<b>0</b>	<b>Z</b>
<b>0</b>	<b>1</b>	<b>Z</b>
<b>1</b>	<b>0</b>	<b>0</b>
<b>1</b>	<b>1</b>	<b>1</b>


## How to build large memories?

- Cannot use a  $2^M \rightarrow 1$  multiplexer!
- Use a shared line (called bit line)
- Can create a bus out of multiple bit lines
- Only one of the inputs can drive the output

 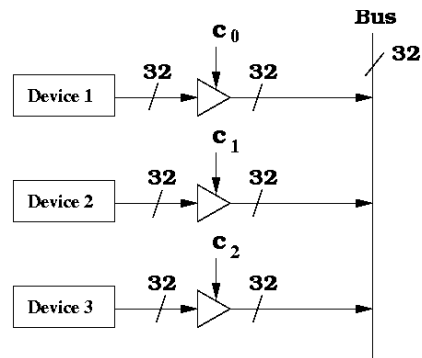

**FIGURE B.9.2** Four three-state buffers are used to form a multiplexor. Only one of the four Select inputs can be asserted. A three-state buffer with a deasserted Output enable has a high-impedance output that allows a three-state buffer whose Output enable is asserted to drive the shared output line.

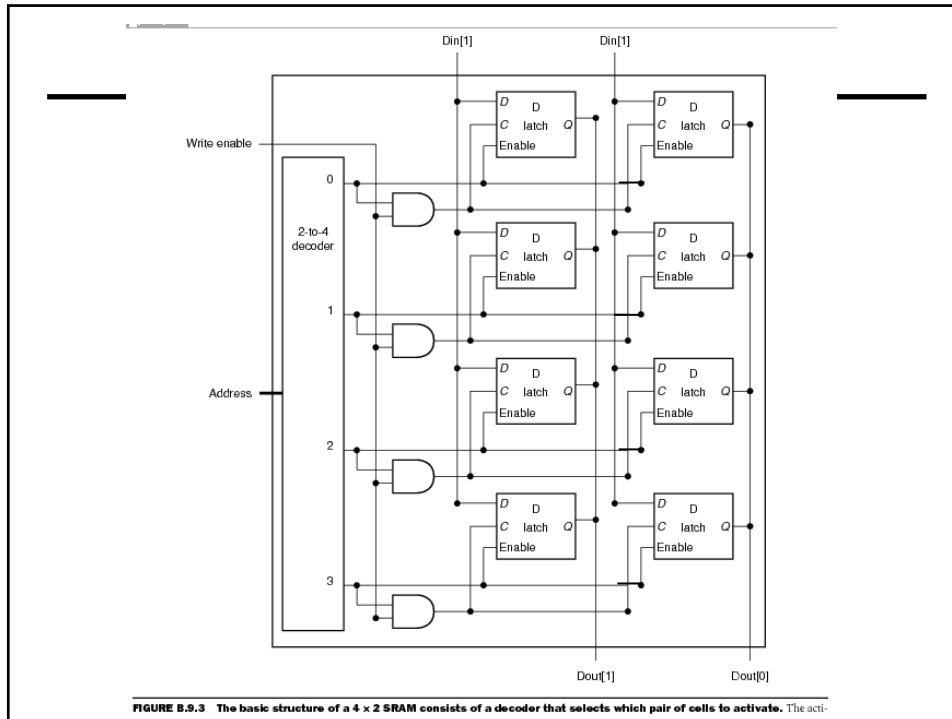
© Kavita Bala, Computer Science, Cornell University



## Big Memories

- Tri state buffer got rid of big mux
- But still need a big decoder to pick the right entry
  - $2M \times 16$  SRAM requires
    - 21 to  $2M$  decoder
    - And  $2M$  lines!
- Instead
  - Rectangular arrays
  - 2-step decode

## Parallel Memory Banks

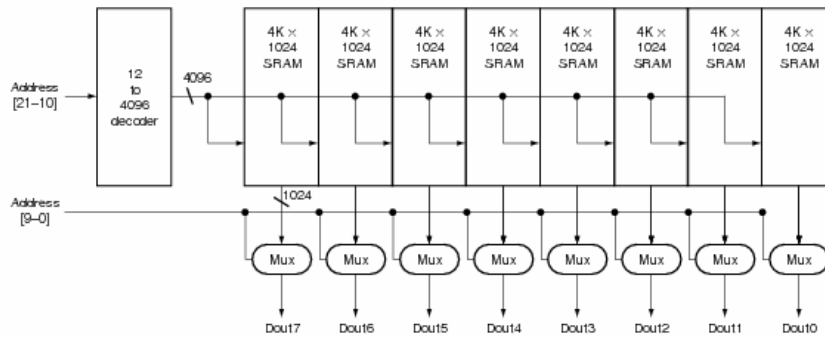

**FIGURE B.9.4** Typical organization of a  $4\text{M} \times 8$  SRAM as an array of  $4\text{K} \times 1024$  arrays. The first decoder generates the addresses for eight  $4\text{K} \times 1024$  arrays; then a set of multiplexers is used to select 1 bit from each 1024-bit-wide array. This is a much easier design than a single-level decoder that would need either an enormous decoder or a gigantic multiplexer. In practice, a modern SRAM of this size would probably use an even larger number of blocks, each somewhat smaller.

© Kavita Bala, Computer Science, Cornell University

## SRAM


- Needs a few gates per cell
- Used for caches (we talk about this later)
- For higher density, use DRAM

© Kavita Bala, Computer Science, Cornell University

## Dynamic RAM: DRAM

---

- Dynamic-RAM
  - Data values require constant refresh
  - Internal circuitry keeps capacitor charges

 

**FIGURE B.9.5** A single-transistor DRAM cell contains a capacitor that stores the cell contents and a transistor used to access the cell.

© Kavita Bala, Computer Science, Cornell University

## DRAM

---

- Single transistor vs. many gates
  - Denser and cheaper
- But, need refresh
  - Read and write back
  - Every few milliseconds...
  - Also organized in 2D grid, so can do rows at a time
  - Done independently on chip
- Hence, slower

© Kavita Bala, Computer Science, Cornell University

## Summary

---

- We now have enough building blocks to build machines that can perform non-trivial computational tasks
- SRAM: caches
- DRAM: main memory