



Sec 01: Logisim

Why Logisim?

- Most real-world hardware design is done using a text-based hardware description language – VHDL, AHDL, etc.
 - Schematics can be "compiled" into a text description
 - Can use a simulator to test the circuit
 - Other back-end tools optimize, perform layout and wire routing, floorplan, etc.
 - Final spec is either downloaded onto a programmable device, or etched into silicon
- We will be using Logisim for all hardware design
 - interactive, graphical schematic editor
 - educational use mainly (makes it user-friendly)

VHDL Example: Signed Adder

```
1 library ieee;
2 use ieee.std_logic_1164.all;
3 use ieee.numeric_std.all;
4
5 entity signed_adder is
6   port
7   (
8     aclr : in    std_logic;
9     clk  : in    std_logic;
10    a     : in    std_logic_vector;
11    b     : in    std_logic_vector;
12    q     : out   std_logic_vector
13  );
14 end signed_adder;
15
16 architecture signed_adder_arch of signed_adder is
17   signal q_s : signed(a'high+1 downto 0); -- extra bit wide
18
19 begin -- architecture
20   assert (a'length >= b'length)
21     report "Port A must be the longer vector if different sizes!"
22     severity FAILURE;
23   q <= std_logic_vector(q_s);
24
25   adding_proc:
26   process (aclr, clk)
27   begin
28     if (aclr = '1') then
29       q_s <= (others => '0');
30     elsif rising_edge(clk) then
31       q_s <= ('0' & signed(a)) + ('0' & signed(b));
32     end if; -- clk'd
33   end process;
34
35 end signed_adder_arch;
```

Why Logisim?

- Most real-world hardware design is done using a text-based hardware description language – VHDL, AHDL, etc.
 - Schematics can be "compiled" into a text description
 - Can use a simulator to test the circuit
 - Other back-end tools optimize, perform layout and wire routing, floorplan, etc.
 - Final spec is either downloaded onto a programmable device, or etched into silicon
- We will be using Logisim for all hardware design
 - interactive, graphical schematic editor
 - educational use mainly (makes it user-friendly)


What are we going to talk about?

- Using Logisim:
 - pins and subcircuits
 - probes for debugging
 - bundles/splitters (with labels!)
 - logging
 - test vectors
- Example Circuits: 1-bit & 32-bit 2:1 Mux
- Using Subcircuits: 2:1 Mux and Controller
- Logging & Test Vectors
- Logisim Don'ts


Example Circuit: 1-bit 2:1 Mux

$S = P$ if $R == 0$

$S = Q$ if $R == 1$

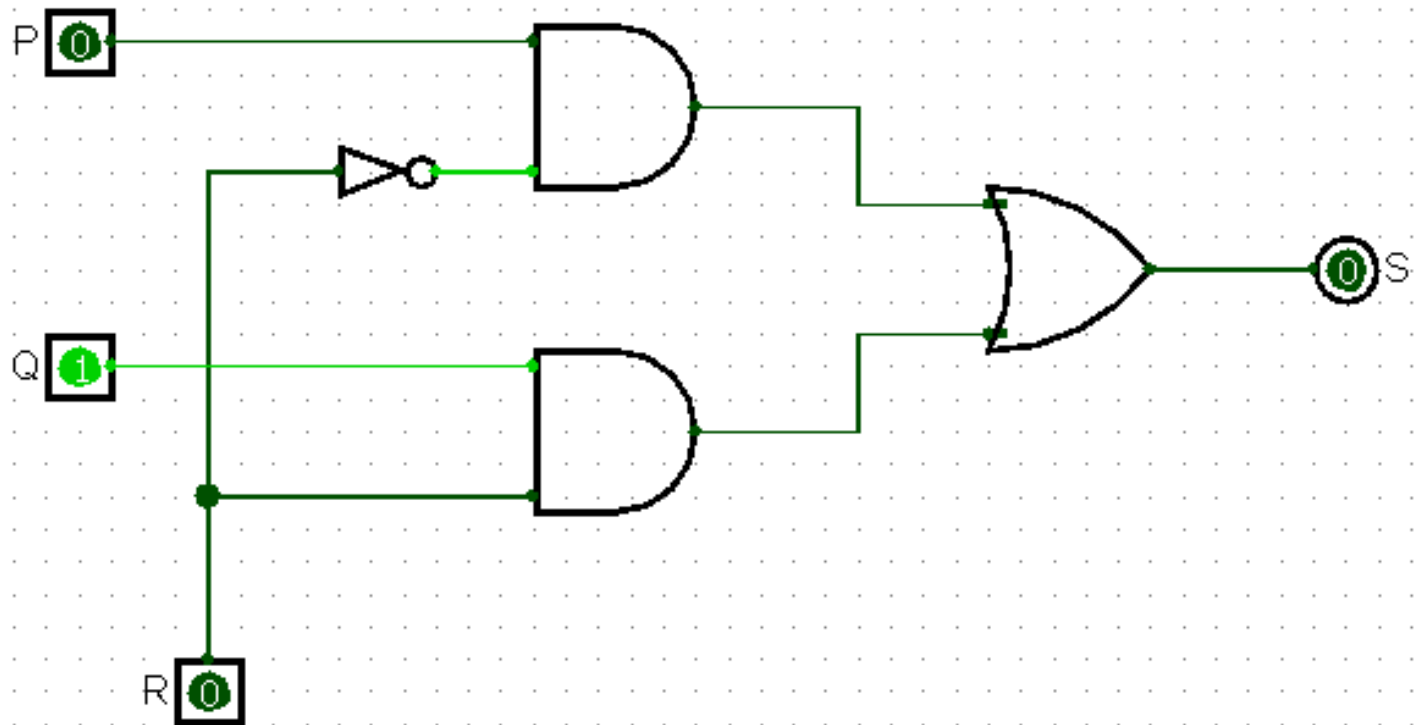


Example Circuit: 32-bit 2:1 Mux

 

Using Subcircuits: 2:1 Mux and Controller

$S = Q$ if $R == 010$

$S = P$ otherwise

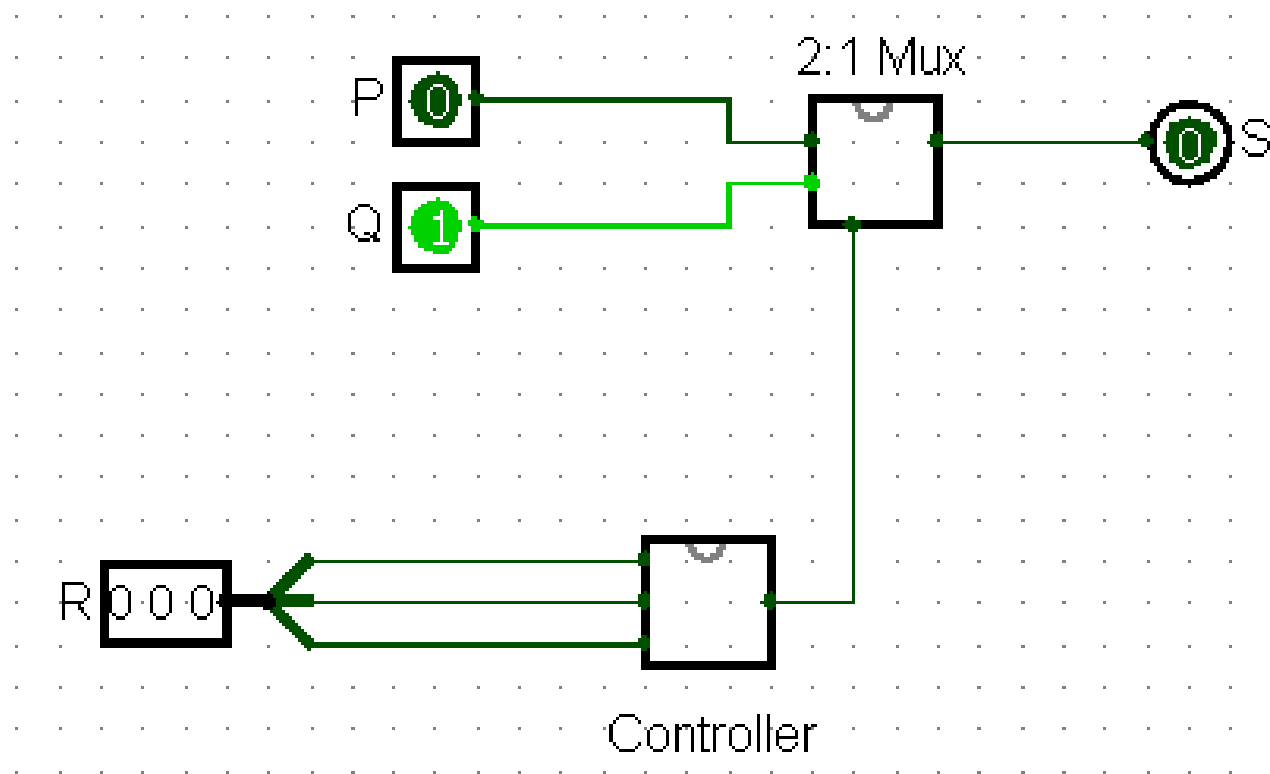

Logging & Test Vectors

Test Vector Truth Table

Log File

```
# Logisim: Log main of multiplexer1
# Mon Jan 25 11:18:42 EST 2010
P      Q      R      S
0      0      0      0
0      0      1      0
0      1      0      0
0      1      1      1
1      0      0      1
1      0      1      0
1      1      0      1
1      1      1      1
```


Passed: 8 Failed: 0

status	P	Q	R	S
pass	0	0	0	0
pass	0	0	1	0
pass	0	1	0	0
pass	0	1	1	1
pass	1	0	0	1
pass	1	0	1	0
pass	1	1	0	1
pass	1	1	1	1

Logisim Don'ts

No Controlled Buffers

 
- Leave wires floating
 - Works in Logisim
 - Breaks in real life
- Use a multiplexor instead



Logisim Don'ts

Don't Build Your Own

 - Building your own wastes time and is confusing to grade
- Almost every component customizable
 - Number of inputs
 - Bit depth




Building an 8-way
Mux the hard way

Logisim Don'ts

Don't Use Constants


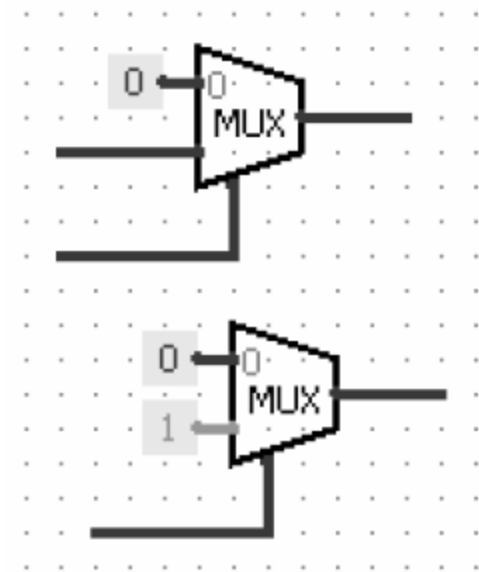
- Constants are almost never necessary
 - Exception is supplying value to extra input
- Try to optimize away before using
 - Think truth tables



Logisim Don'ts

Don't Make Trivial Sub-circuits

  - Try to build logical sub-circuits
- Problems
 - All sub-circuits look the same
 - Wastes time specifying inputs and outputs of small circuits
 - Big hierarchy harder to understand



Logisim Don'ts

Don't Use Invisible Splitters

- Please...
- Its really hard to see them when we grade





Bad



Good

Logisim Don'ts

Don't Work Right to Left

  

Some more information

- MIPS Assignments:
 - 32-bit ALU
 - 32-bit Processor
 - 32-bit Pipelined Processor
- Webpage:
<http://www.cs.cornell.edu/courses/cs3410/2010sp/>