Circuits & Numbers

Kevin Walsh CS 3410, Spring 2010 Computer Science Cornell University

See: P&H Chapter 2.4, 2.5, 3.2, C.5

Office Hours

HW1

CSUGLab

2

How to implement a desired function?

а	b	С	out	minterm
0	0	0	0	a b c
0	0	1	1	a b c
0	1	0	0	a b c
0	1	1	1	abc
1	0	0	0	a b c
1	0	1	1	a b c
1	1	0	0	a b c
1	1	1	0	a b c

sum of products:

OR of all minterms where out=1

corollary: *any* combinational circuit *can be* implemented in two levels of logic (ignoring inverters)

How does one find the most efficient equation?

- Manipulate algebraically until...?
- -Use Karnaugh maps (optimize visually)
- -Use a software optimizer

For large circuits

Decomposition & reuse of building blocks

Voting Machine!

 optical scan (thanks FL)

- Assume:
 - vote is recorded on paper by filling a circle
 - fixed number of choices
 - don't worry about "invalids"





5 Essential Components?

- Input: paper with at exactly one mark
- Datapath: process
 current ballot
- Output: a number the supervisor can record
- Memory & control: none for now

The 3410 optical scan vote counter reader machine



Photo-sensitive transistor

- photons replenish gate depletion region
- can distinguish dark and light spots on paper



 Use array of N sensors for voting machine input

7-Segment LED

 photons emitted when electrons fall into holes









N might be large

Routing wires is expensive

More efficient encoding?

Base 10 - Decimal

- Just as easily use other bases
 - Base 2 Binary
 - Base 8 Octal
 - Base 16 Hexadecimal

$10^2 \, 10^1 \, 10^0$

637

Counting

Base conversion via repetitive division

- Divide by base, write remainder, move left with quotient

Base conversion via repetitive division

- Divide by base, write remainder, move left with quotient

Base conversion via repetitive division

- Divide by base, write remainder, move left with quotient

Hexadecimal, Binary, Octal Conversions

Implementation . . .

- assume 8 choices, exactly one mark detected



3-bit encoder (8-to-3)





- 3 inputs
- encode 0 7 in binary

- 7 outputs
- one for each LED

b2	b1	b0	d6	d5	d4	d3	d2	d1	d0
0	0	0	1	1	1	0	1	1	1
0	0	1	1	0	0	0	0	0	1
0	1	0	0	1	1	1	0	1	1
0	1	1	1	1	0	1	0	1	1
1	0	0	1	0	0	1	1	0	1
1	0	1	1	1	0	1	1	1	0
1	1	0	1	1	1	1	1	1	0
1	1	1	1	0	0	0	0	1	1





Ballots

The 3410 optical scan vote counter reader machine



183 + 254 Addition works the same way regardless of base

- Add the digits in each position
- Propagate the carry

001110 + 011100



Half Adder

- Adds two 1-bit numbers
- Computes 1-bit result and 1-bit carry



Full Adder

- Adds three 1-bit numbers
- Computes 1-bit result and 1-bit carry
- Can be cascaded



4-Bit Full Adder

- Adds two 4-bit numbers and carry in
- Computes 4-bit result and carry out
- Can be cascaded



We can now implement any combinational (combinatorial) logic circuit

- Decompose large circuit into manageable blocks
 - Encoders, Decoders, Multiplexors, Adders, ...
- Design each block
 - Binary encoded numbers for compactness
- Can implement circuits using NAND or NOR gates
- Can implement gates using use P- and N-transistors