


State & Finite State Machines

Kevin Walsh
CS 3410, Spring 2010
Computer Science
Cornell University


See: P&H Appendix C.7, C.8, C.10, C.11

Prelim 1: 3/18/2010 (evening)

Prelim 2: 4/27/2010 (evening)

 


Stable and unstable equilibria?

 

So far:

 - Current output depends only on current input (no internal state)





Need a way to record data


- ... a way to build stateful circuits
- ... a state-holding device

Set-Reset (SR) Latch

Stores a value Q and its complement \bar{Q}

S	R	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		

  

 

Data (D) Latch

D	Q	\bar{Q}
0		
1		



Level Sensitive D Latch

Clock high:

set/reset (according to D)


Clock low:


keep state (ignore D)

  

Clock helps coordinate state changes

 
- Usually generated by an oscillating crystal
- Fixed period; frequency = $1/\text{period}$



 

D Flip-Flop

 - Edge-Triggered
- Data is captured when clock is high
- Outputs change only on falling edges




Level sensitive

- State changes when clock is high (or low)


Edge triggered


- State changes at clock edge

positive edge-triggered

 


negative edge-triggered

 


 

Register

 
- D flip-flops in parallel
- shared clock
- extra clocked inputs: write_enable, reset, ...




 

Q: What happens if input is changes near clock edge?

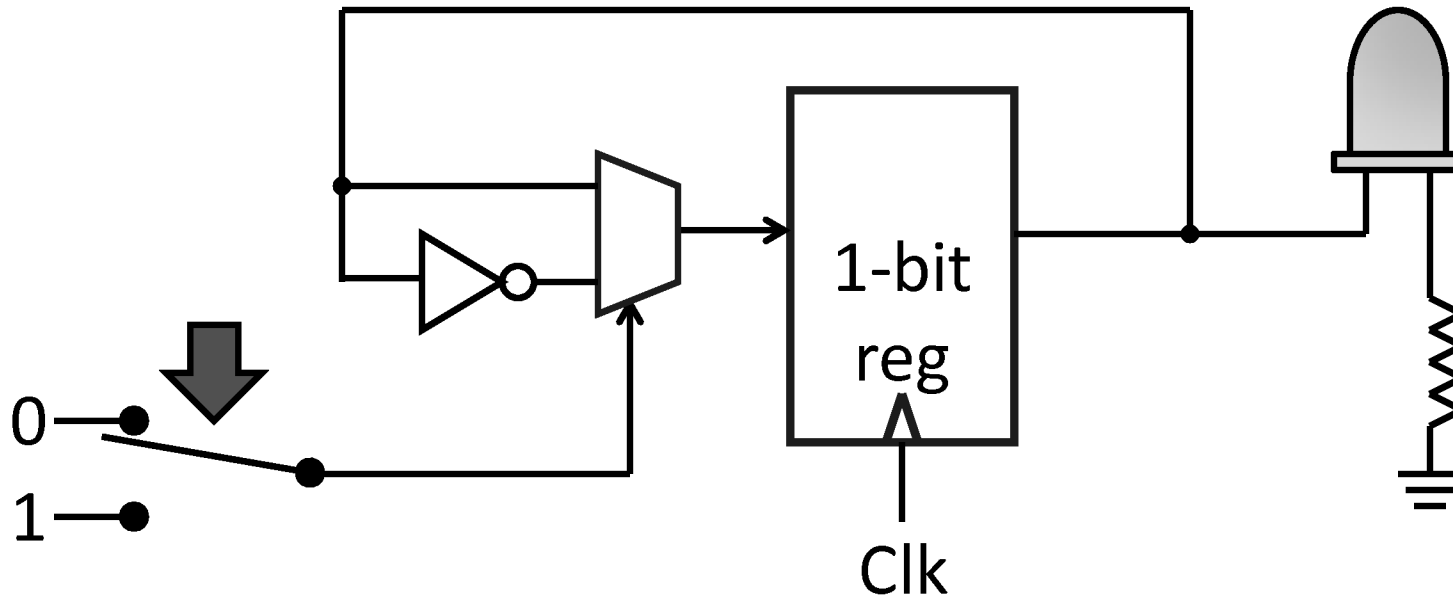
A: Google “Buridan’s Principle” by Leslie Lamport



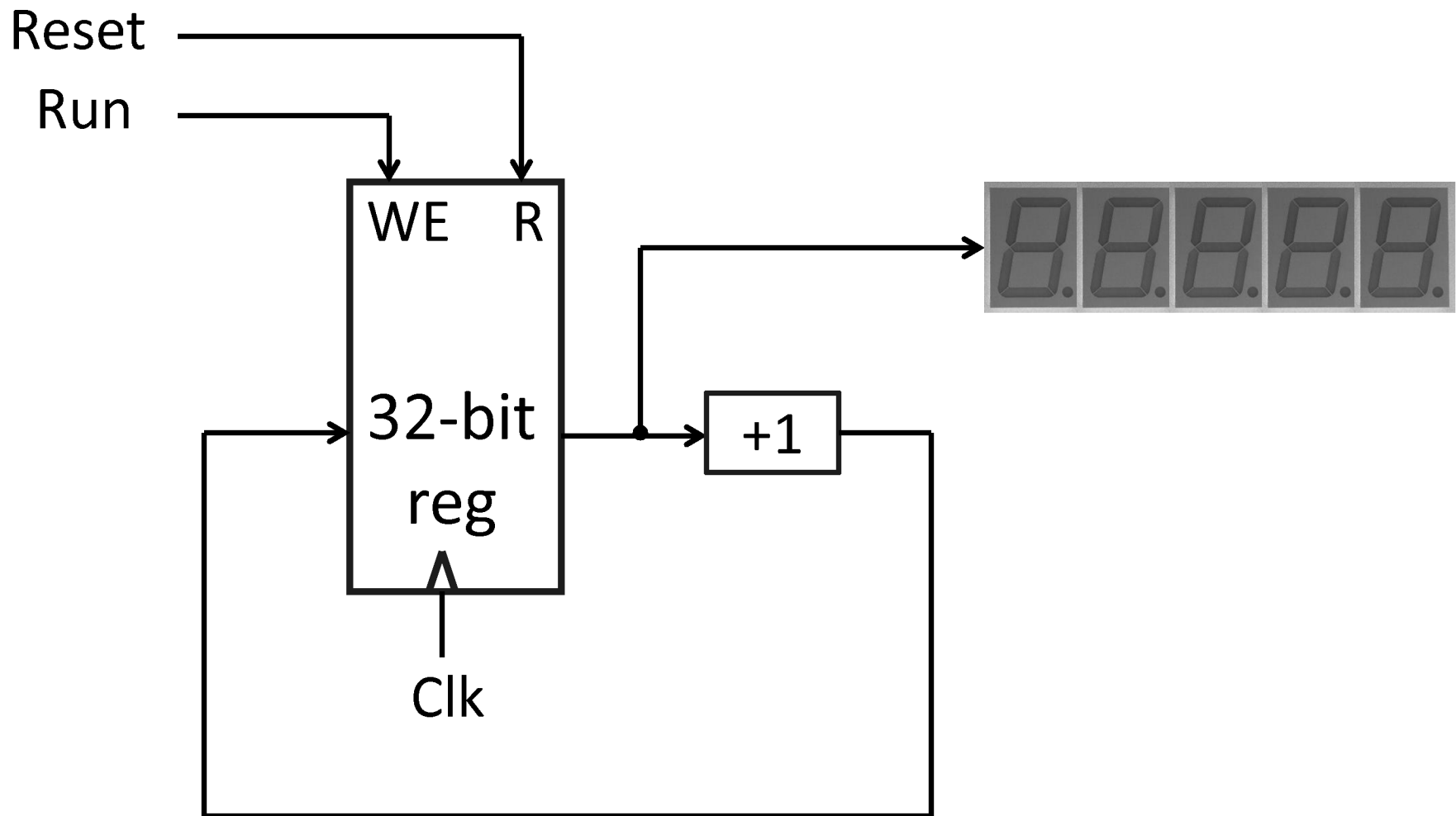


Clock Methodology

- Negative edge, synchronous

 


– Signals must be stable near falling clock edge


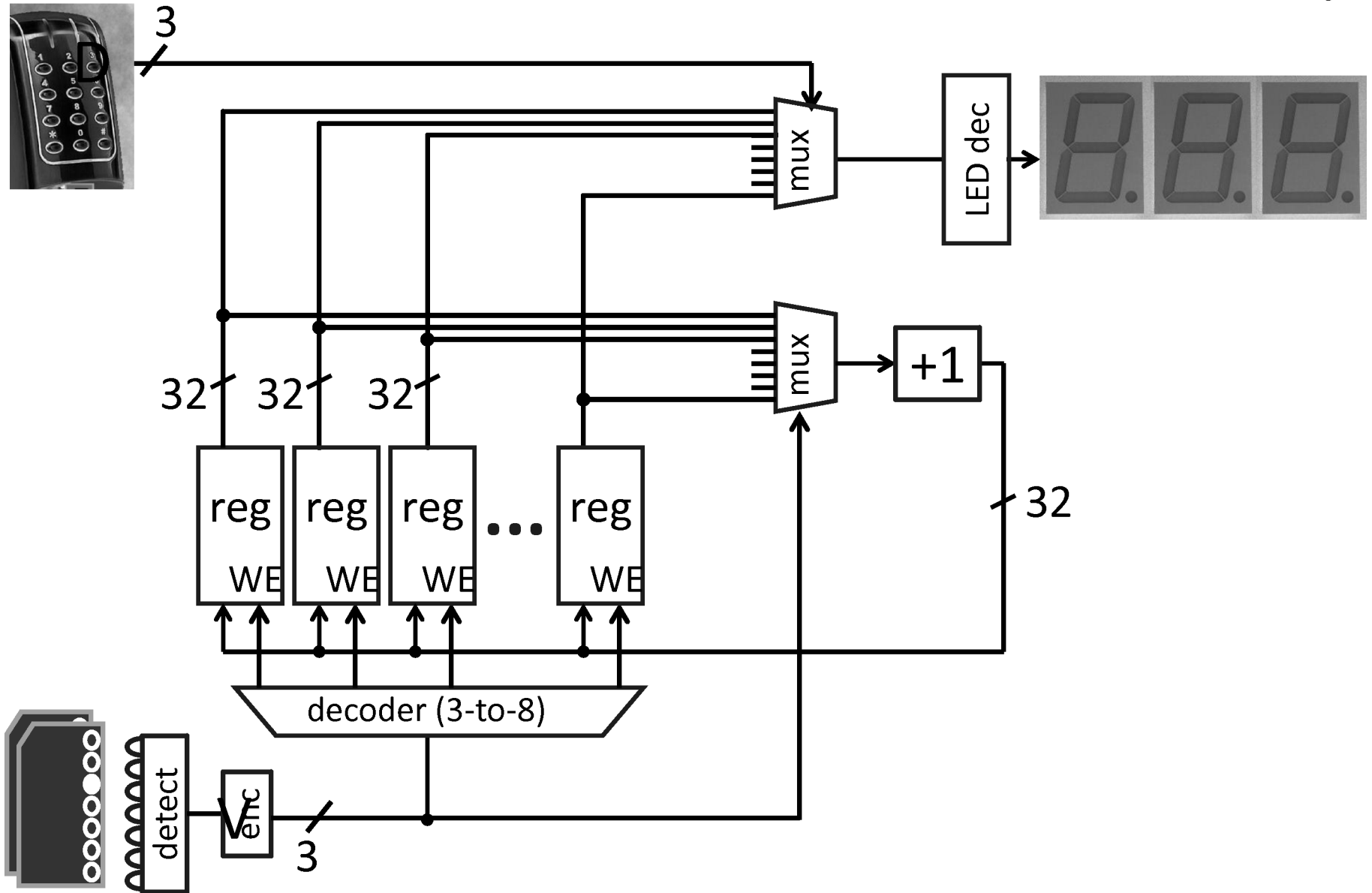
- Positive edge synchronous
- Asynchronous, multiple clocks, . . .



Finite State Machine

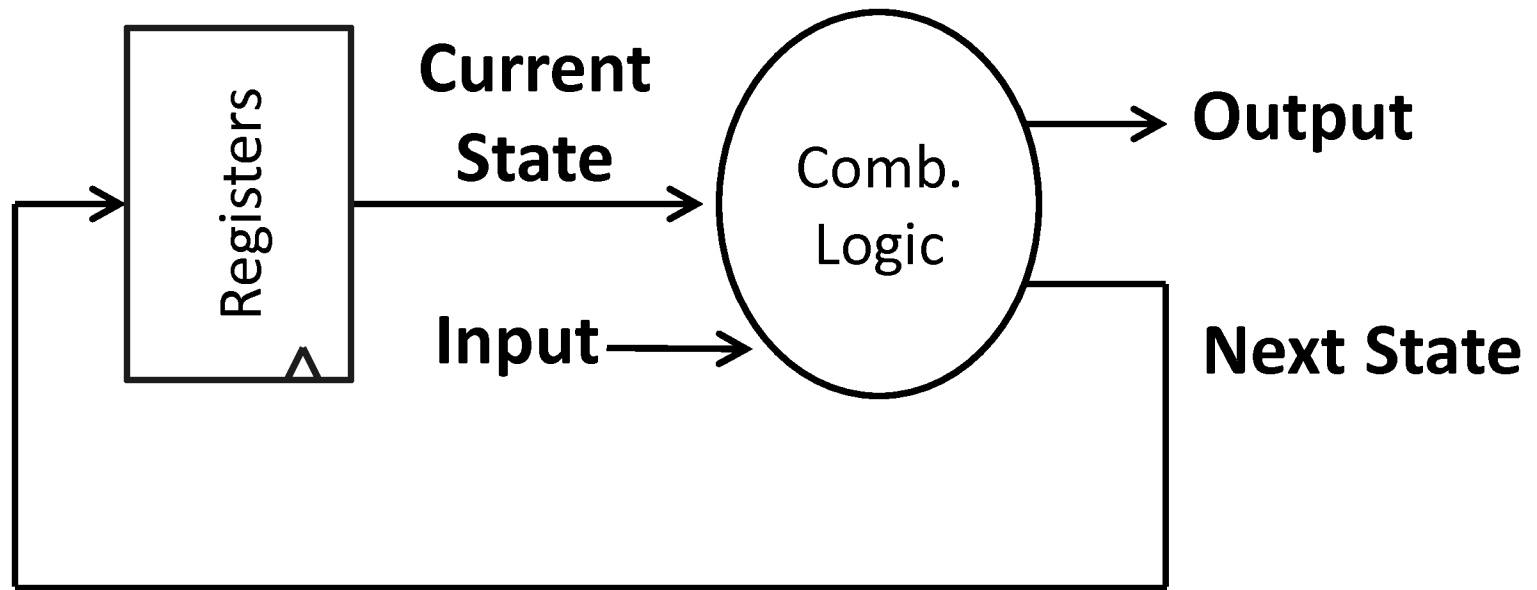

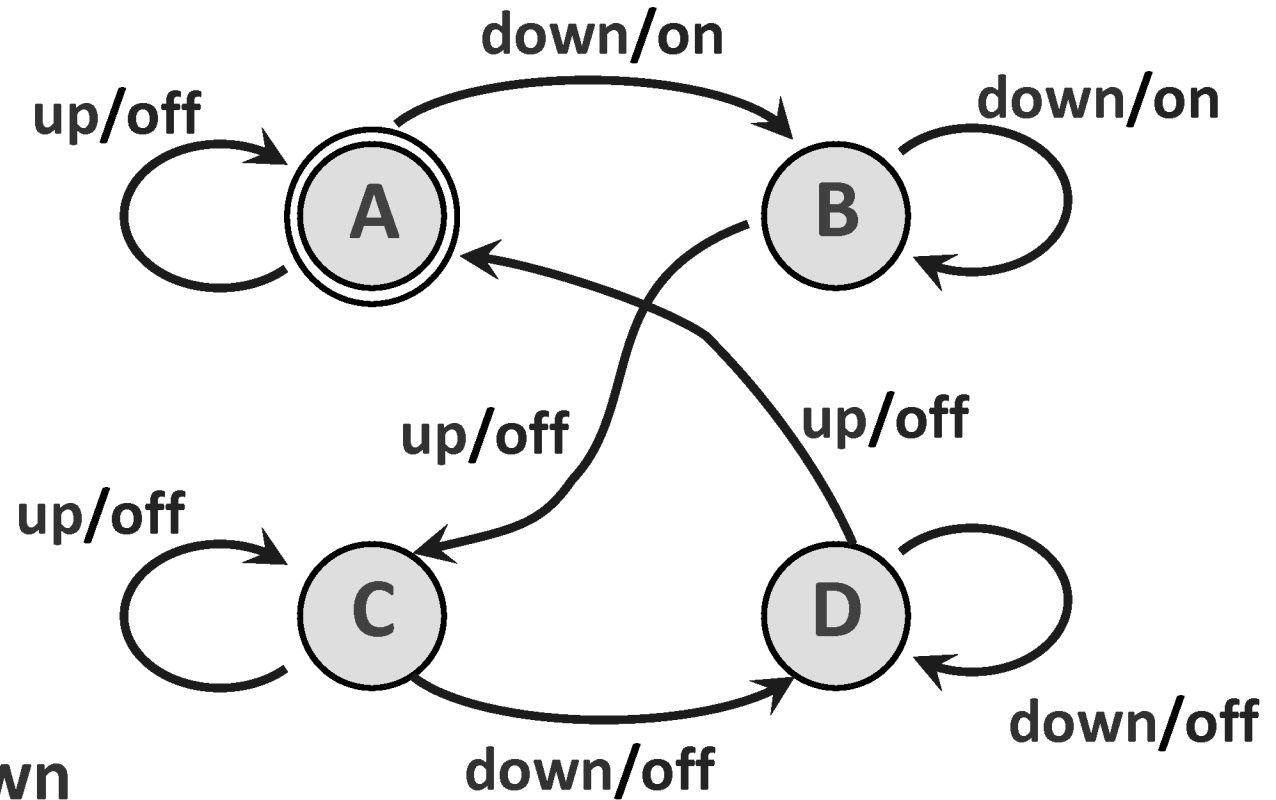
 
- inputs from external world
- outputs to external world
- internal state
- combinational logic



Input: **up** or **down**

Output: **on** or **off**

States: **A**, **B**, **C**, or **D**

  


Input: **0**=up or **1**=down

Output: **1**=on or **1**=off


States: **00**=A, **01**=B, **10**=C, or **11**=D

General Case: Mealy Machine


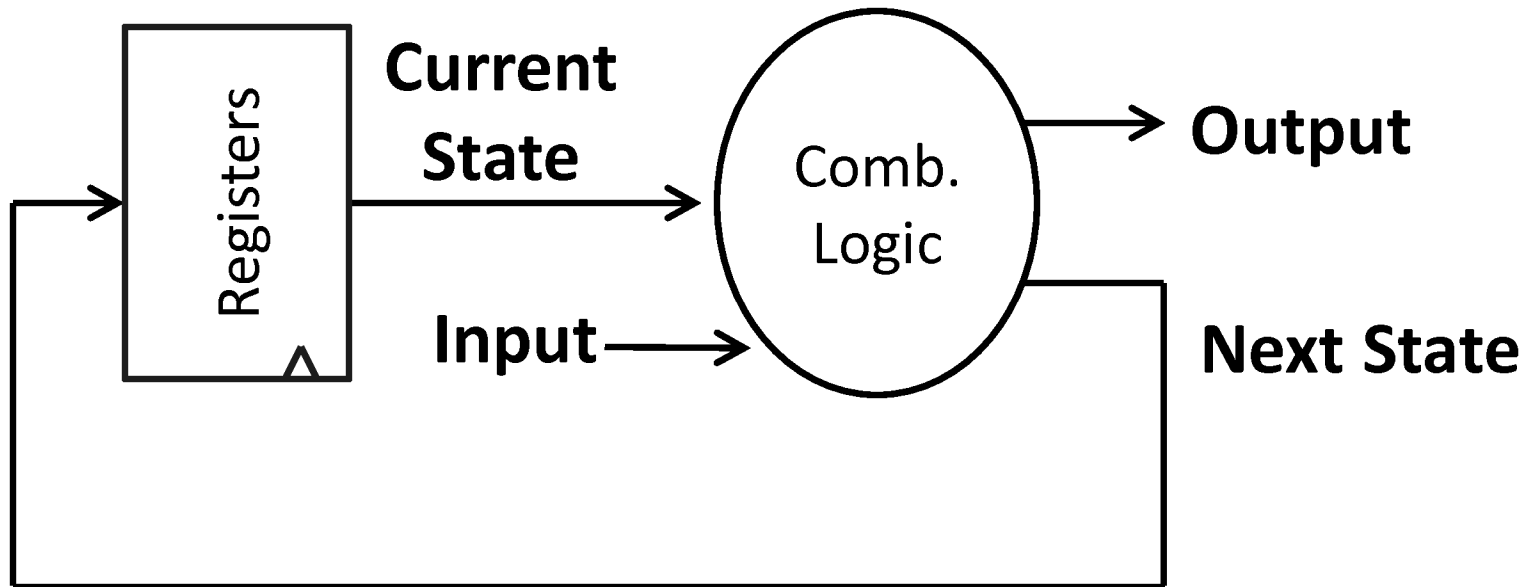


Outputs and next state depend on both current state and input

Special Case: Moore Machine

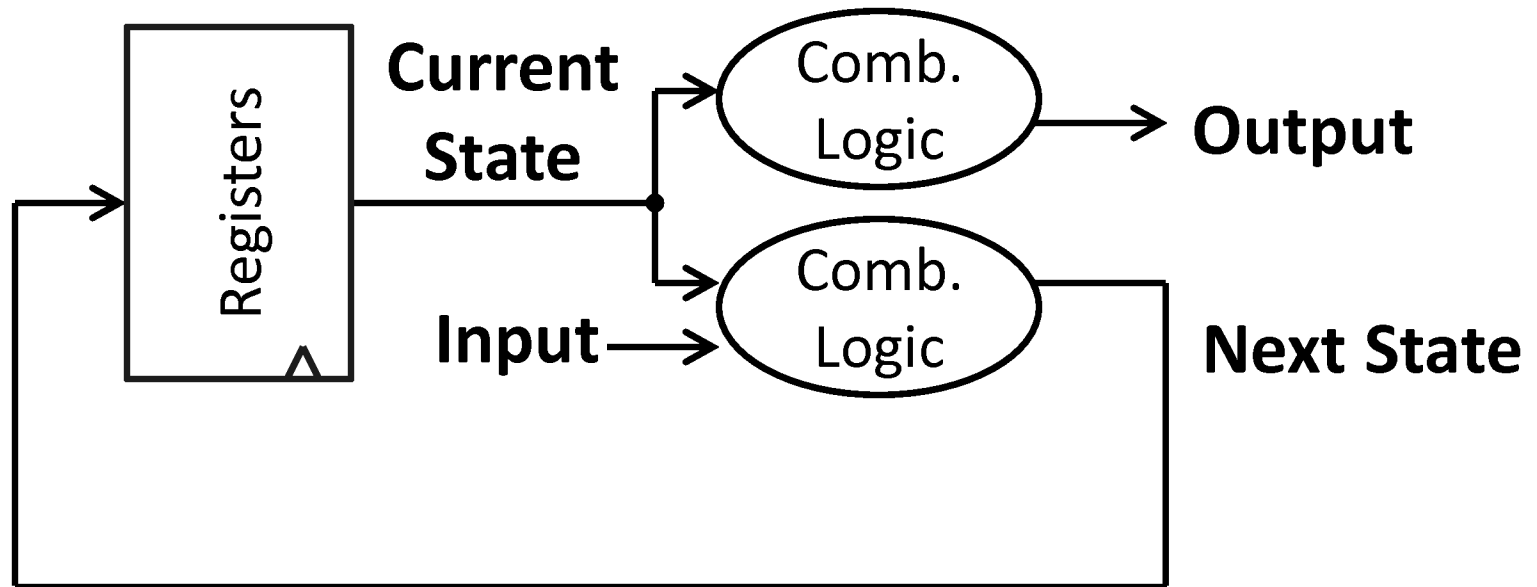

Outputs depend only on current state

  

Input: **up** or **down**

Output: **on** or **off**

States: **A**, **B**, **C**, or **D**



Digital Door Lock

Inputs:

- keycodes from keypad
- clock

Outputs:

- “unlock” signal
- display how many keys pressed so far

Assumptions:

- signals are synchronized to clock
- Password is B-A-B



K


A


B


K	A	B	Meaning
0	0	0	∅ (no key)
1	1	0	'A' pressed
1	0	1	'B' pressed


Assumptions:


- High pulse on U unlocks door

 

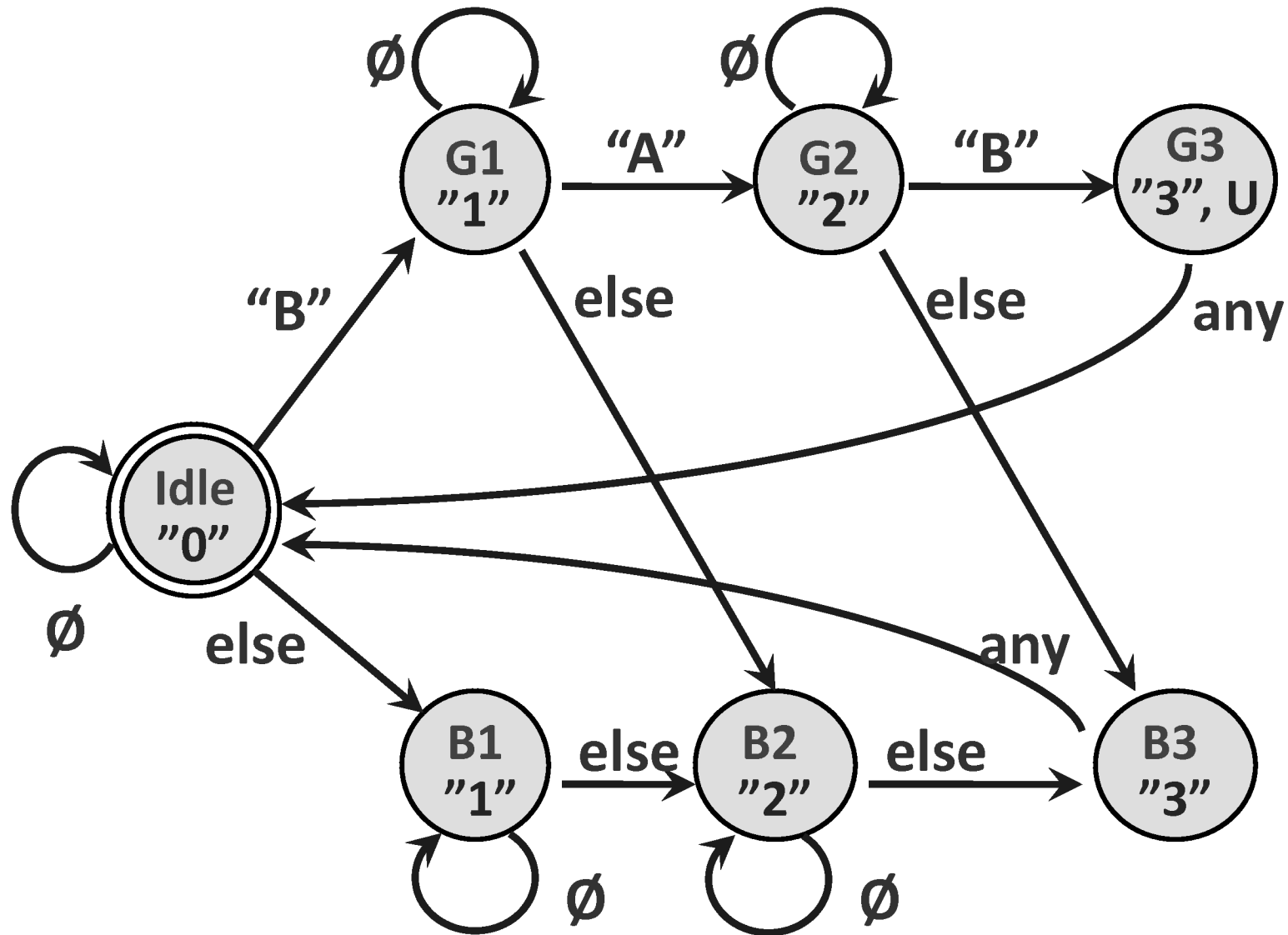

 

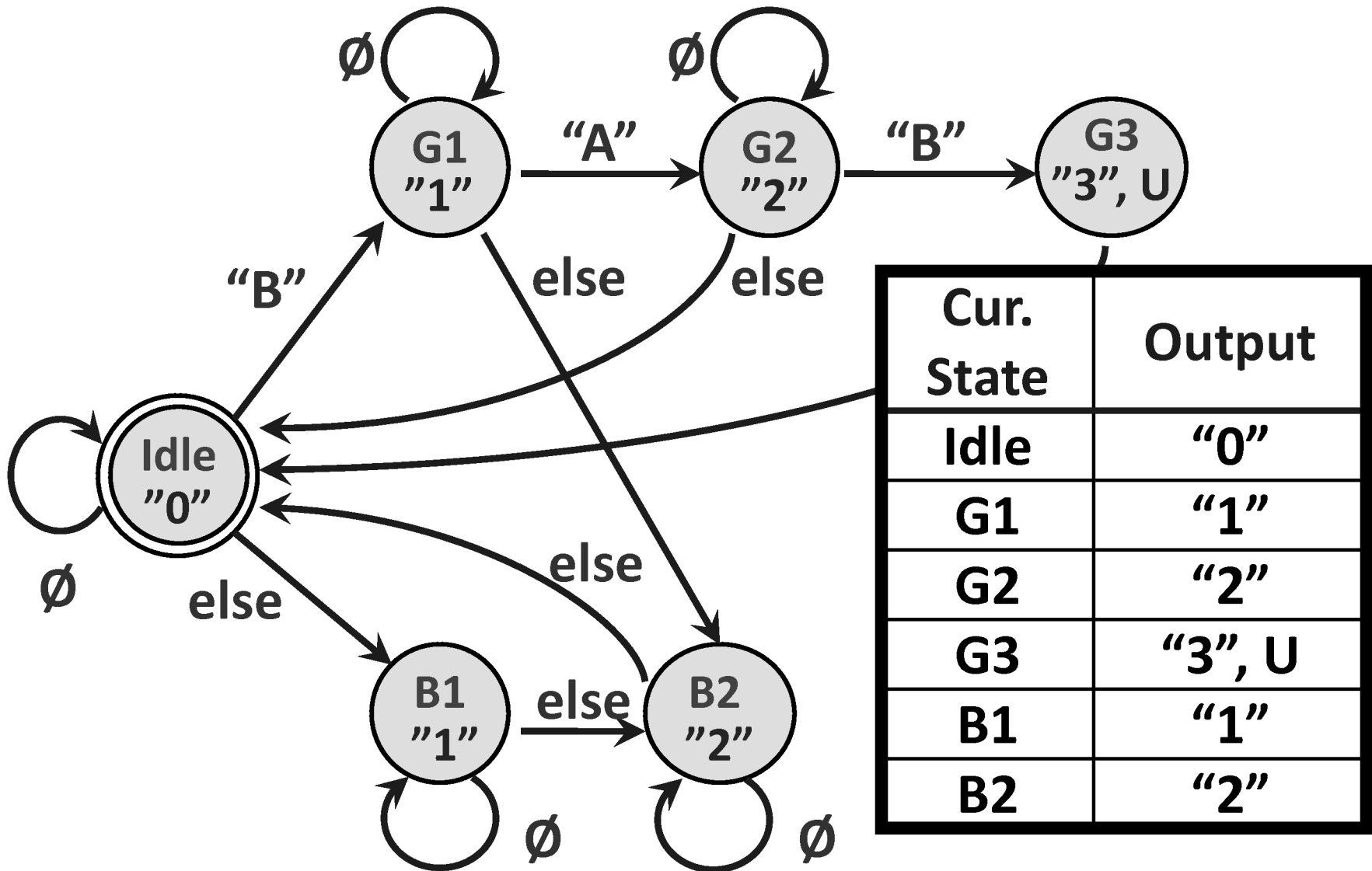

 


Cur. State	Input	Next State
Idle	∅	Idle
Idle	"B"	G1
Idle	"A"	B1
G1	∅	G1
G1	"A"	G2
G1	"B"	B2
G2	∅	B2
G2	"B"	G3
G2	"A"	Idle
G3	any	Idle
B1	∅	B1
B1	K	B2
B2	∅	B2
B2	K	Idle

S_2	S_1	S_0	D_3	D_2	D_1	D_0	U
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	0	0	1	1	1
1	0	0	0	0	0	1	0
1	0	1	0	0	1	0	0

 D_3

State	S_2	S_1	S_0
Idle	0	0	0
G1	0	0	1
G2	0	1	0
G3	0	1	1
B1	1	0	0
B2	1	0	1

S_2	S_1	S_0	K	A	B	S'_2	S'_1	S'_0
0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0	1
0	0	0	1	1	0	0	0	1
0	0	1	0	0	0	0	0	1
0	0	1	1	1	0	0	1	0
0	0	1	0	0	1	0	1	0
0	1	0	0	0	0	0	1	0
0	1	0	0	0	1	0	1	1
0	1	0	0	1	0	0	0	0
0	1	1	x	x	x	0	0	0
1	0	0	0	0	0	1	0	0
1	0	0	1	x	x	1	0	1
1	0	1	0	0	0	1	0	1
1	0	1	1	x	x	0	0	0

 

Strategy:

- (1) Draw a state diagram (e.g. Moore Machine)
- (2) Write output and next-state tables
- (3) Encode states, inputs, and outputs as bits
- (4) Determine logic equations for next state and outputs

We can now build interesting devices with sensors

- Using combinational logic

We can also store data values

- Stateful circuit elements (D Flip Flops, Registers, ...)
- Clock to synchronize state changes
- But be wary of asynchronous (un-clocked) inputs
- State Machines or Ad-Hoc Circuits