

# Arithmetic

**Hakim Weatherspoon**

**CS 3410, Spring 2012**

Computer Science

Cornell University

See P&H 2.4 (signed), 2.5, 2.6, C.6, and Appendix C.6

# Goals for today

---

## Binary (Arithmetic) Operations

- One-bit and four-bit adders
- Negative numbers and two's compliment
- Addition (two's compliment)
- Subtraction (two's compliment)
- Performance

# Binary Addition

---

$$\begin{array}{r} 183 \\ + 254 \\ \hline \end{array}$$

*437*

$$\begin{array}{r} 001110 \\ + 011100 \\ \hline \end{array}$$

*101010*


Addition works the same way regardless of base

- Add the digits in each position
- Propagate the carry

Unsigned binary addition is pretty easy

- Combine two bits at a time
- Along with a carry

# 1-bit Adder

 

## Half Adder


- Adds two 1-bit numbers
- Computes 1-bit result and 1-bit carry

$$R = \bar{A}B + A\bar{B}$$

$$C = AB$$

A	B	C	R
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# 1-bit Adder with Carry

 


## Full Adder

- Adds three 1-bit numbers
- Computes 1-bit result and 1-bit carry
- Can be cascaded

A	B	C <sub>in</sub>	C <sub>out</sub>	R
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

# 4-bit Adder

---

 


## 4-Bit Full Adder

- Adds two 4-bit numbers and carry in
- Computes 4-bit result and carry out
- Can be cascaded

# 4-bit Adder

---

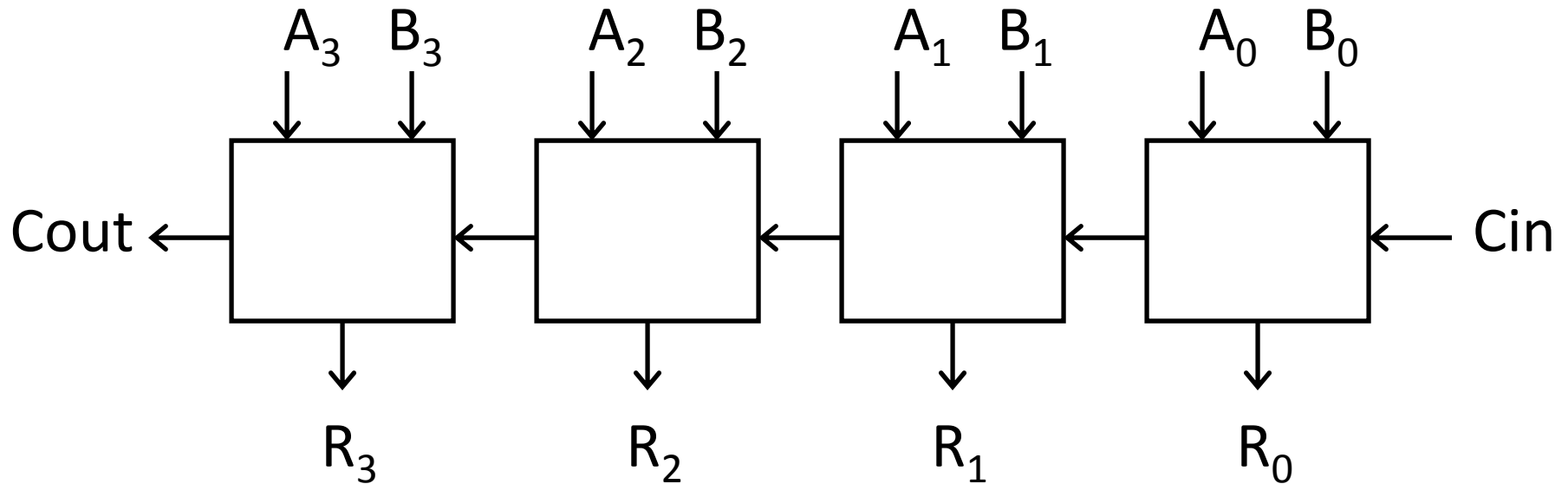

- Adds two 4-bit numbers, along with carry-in
- Computes 4-bit result and carry out
- Carry-out = overflow indicates result does not fit in 4 bits

# Arithmetic with Negative Numbers

---

Negative Numbers Complicate Arithmetic

Recall addition with negatives:

$$0111 = 7$$

$$\underline{1}111 = -7$$

$$0000 = +0$$

$$1000 = -0$$



# Arithmetic with Negative Numbers

---

Negative Numbers Complicate Arithmetic

Recall addition with negatives:

- $\text{pos} + \text{pos} \rightarrow$  add magnitudes, result positive
- $\text{neg} + \text{neg} \rightarrow$  add magnitudes, result negative
- $\text{pos} + \text{neg} \rightarrow$  subtract smaller magnitude,  
keep sign of bigger magnitude

# First Attempt: Sign/Magnitude Representation

---

## First Attempt: Sign/Magnitude Representation

- 1 bit for sign (0=positive, 1=negative)
- N-1 bits for magnitude

# Two's Complement Representation

---

Better: Two's Complement Representation

- Leading 1's for negative numbers
- To negate any number:

- complement *all* the bits

- then add 1

$$20 = 0001\ 0100$$

$$\overline{20} = 1110\ 1011$$

$$\begin{array}{r} 6 = 0110 \\ \overline{6} = 1001 \\ \hline -6 = 1001 + 1 \\ \phantom{-6} = 1010 \end{array}$$

# Two's Complement

---

Non-negatives  
(as usual):

$$+0 = 0000$$

$$+1 = 0001$$

$$+2 = 0010$$

$$+3 = 0011$$

$$+4 = 0100$$

$$+5 = 0101$$

$$+6 = 0110$$

$$+7 = 0111$$

$$+8 = 1000$$

Negatives

(two's complement: flip then add 1):

$$1111$$

$$1110$$

$$1101$$

$$1100$$

$$1011$$

$$\vdots$$

$$\vdots$$

$$\vdots$$

$$0111$$

$[-8, 7]$

$$0000 = 0$$

$$1111 = -1$$

$$1110 = -2$$

$$1101 = -3$$

$$1100 = -4$$

$$\vdots$$

$$\vdots$$

$$\vdots$$

$$1000 = -8$$

# Two's Complement

---

Non-negatives

(as usual):

$$+0 = 0000$$

$$+1 = 0001$$

$$+2 = 0010$$

$$+3 = 0011$$

$$+4 = 0100$$

$$+5 = 0101$$

$$+6 = 0110$$

$$+7 = 0111$$

$$+8 = 1000$$

Negatives

(two's complement: flip then add 1):

$$\sim 0 = 1111$$

$$\sim 1 = 1110$$

$$\sim 2 = 1101$$

$$\sim 3 = 1100$$

$$\sim 4 = 1011$$

$$\sim 5 = 1010$$

$$\sim 6 = 1001$$

$$\sim 7 = 1000$$

$$\sim 8 = 0111$$

$$-0 = 0000$$

$$-1 = 1111$$

$$-2 = 1110$$

$$-3 = 1101$$

$$-4 = 1100$$

$$-5 = 1011$$

$$-6 = 1010$$

$$-7 = 1001$$

$$-8 = 1000$$

# Two's Complement Facts

---

## Signed two's complement

- Negative numbers have leading 1's
- zero is unique:  $+0 = -0$
- wraps from largest positive to largest negative

## N bits can be used to represent

- unsigned:

– eg: 8 bits  $\Rightarrow$

$$0 - 2^N - 1$$
$$0 - (2^8 - 1) = (256 - 1) = 255$$

- signed (two's complement):

– ex: 8 bits  $\Rightarrow$

$$-\frac{2^N}{2} \dots 0 \dots \left(\frac{2^N}{2}\right) - 1$$
$$-128 \dots \dots 127$$

# Sign Extension & Truncation

---

Extending to larger size

$$\begin{array}{l} 1111 = -1 \\ 1111 \ 1111 = -1 \\ 0111 = 7 \\ 0000 \ 0111 = 7 \end{array}$$

Truncate to smaller size

$$\begin{array}{l} \cancel{0000} \ 1111 = 15 \\ 1111 = -1 \end{array}$$

# Two's Complement Addition

---

Addition with two's complement signed numbers

- Perform addition as usual, regardless of sign (it just works)

$$\begin{array}{r} 4 = 0100 \\ 7 = 0111 \\ \hline 1011 \end{array}$$

$$\begin{array}{r} 4 = 0100 \\ 7 = 0111 \\ \hline 1011 \end{array}$$




# Two's Complement Addition

---

Addition with two's complement signed numbers

 
- Perform addition as usual, regardless of sign (it just works)



# Overflow
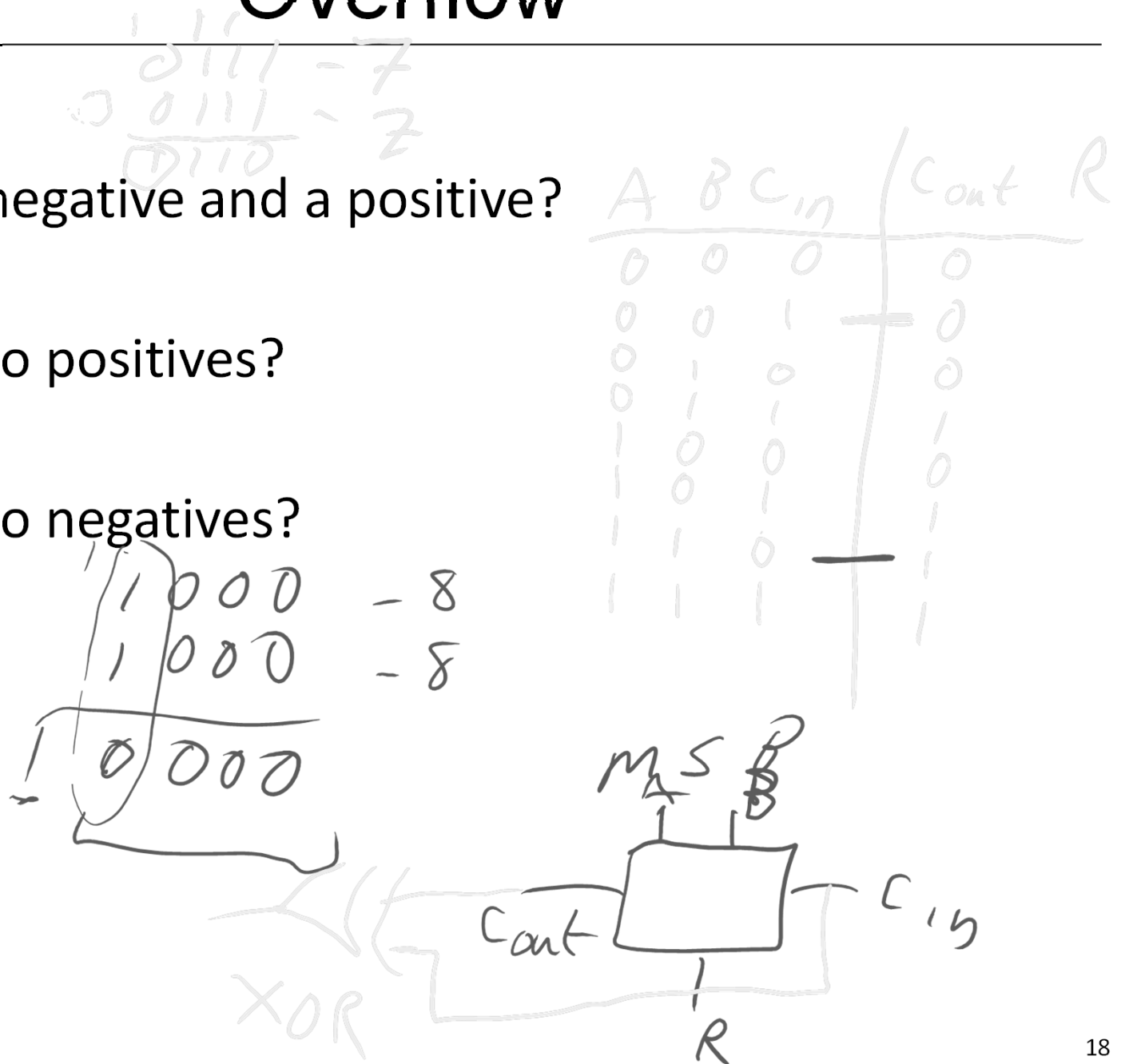
## Overflow

- adding a negative and a positive?
- adding two positives?
- adding two negatives?



# Overflow

---

## Overflow

- adding a negative and a positive?
- adding two positives?
- adding two negatives?


Rule of thumb:

Overflow happened iff  
carry into msb  $\neq$  carry out of msb
 
# Two's Complement Adder

---

Two's Complement Adder with overflow detection



# Binary Subtraction

## Two's Complement Subtraction

$A - B = A + (-B) = A + (\bar{B} + 1)$

$A = 7$   
 $B = -8$   
 $C_{in}$

$7 - (-8) = -15$


# Binary Subtraction

## Two's Complement Subtraction

*A = 3 = 0011*  
*B = 6 = 0110*

*3 - 6 = -3*

$$A - B = A + (-B) = A + (\bar{B} + 1)$$

 


*Handwritten binary subtraction:*  

$$\begin{array}{r} 1101 \\ - 0010 \\ \hline 1011 \end{array}$$
 The result  $1011$  is circled and labeled  $= 3$ .  
 Below it, another calculation shows  $1011$  with a slash and  $3$ .


Q: What if (-B) overflows?

# A Calculator

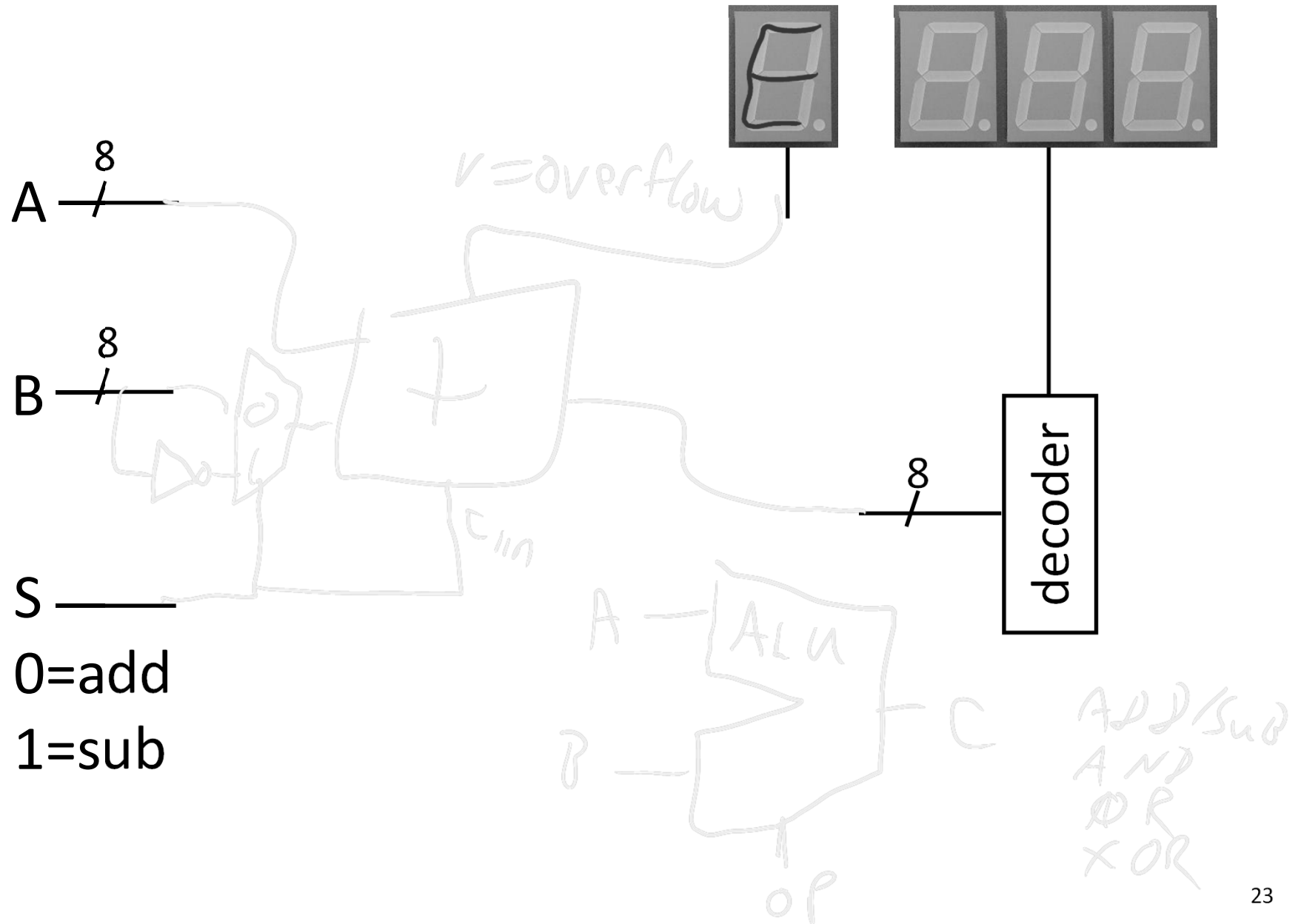

# A Calculator

---

 



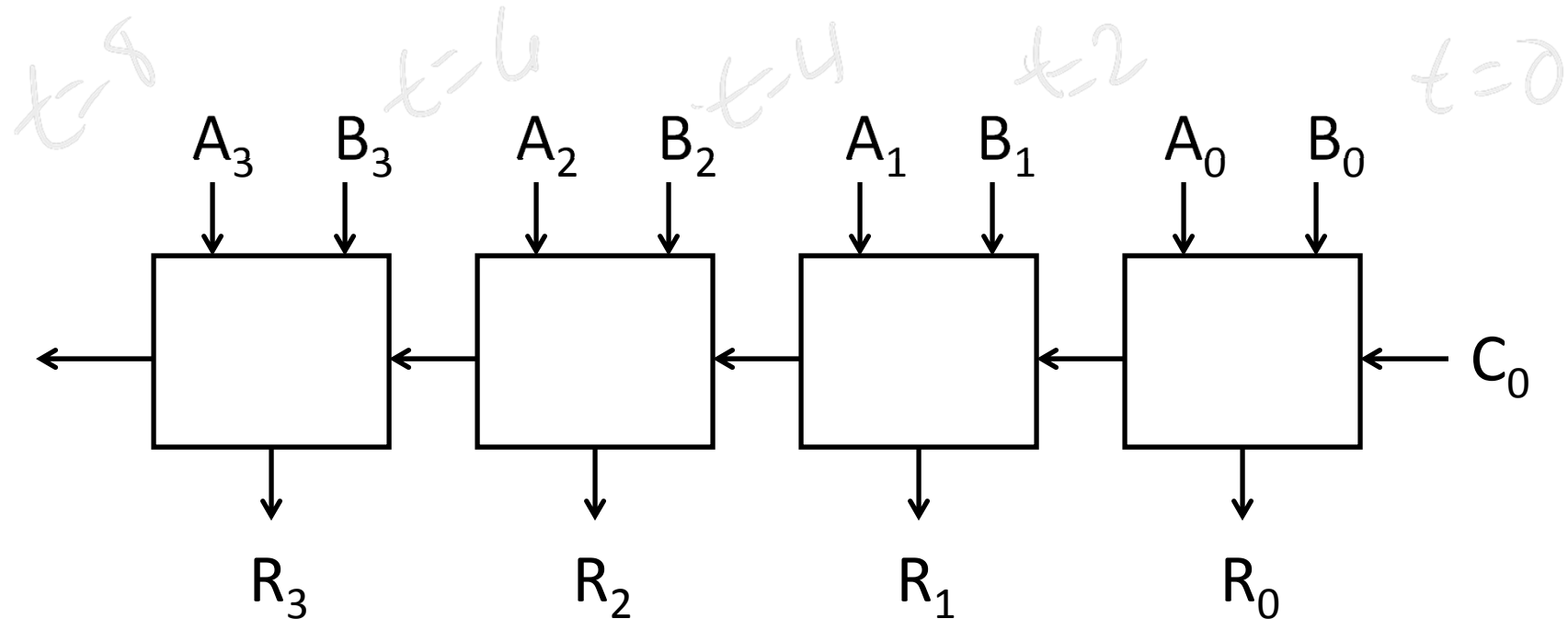
# Efficiency and Generality

---


- Is this design fast enough?
- Can we generalize to 32 bits? 64? more?


 
# Performance


---

Speed of a circuit is affected by the number of gates in series (on the *critical path* or the *deepest level of logic*)



# 4-bit Ripple Carry Adder

---

 


- First full adder, 2 gate delay
- Second full adder, 2 gate delay
- ...


# Critical Path

Which operation is the critical path?

- A) ADD/SUB
- B) AND
- C) OR
- D) LT

 

*C. 5.9*  
*select = 2*

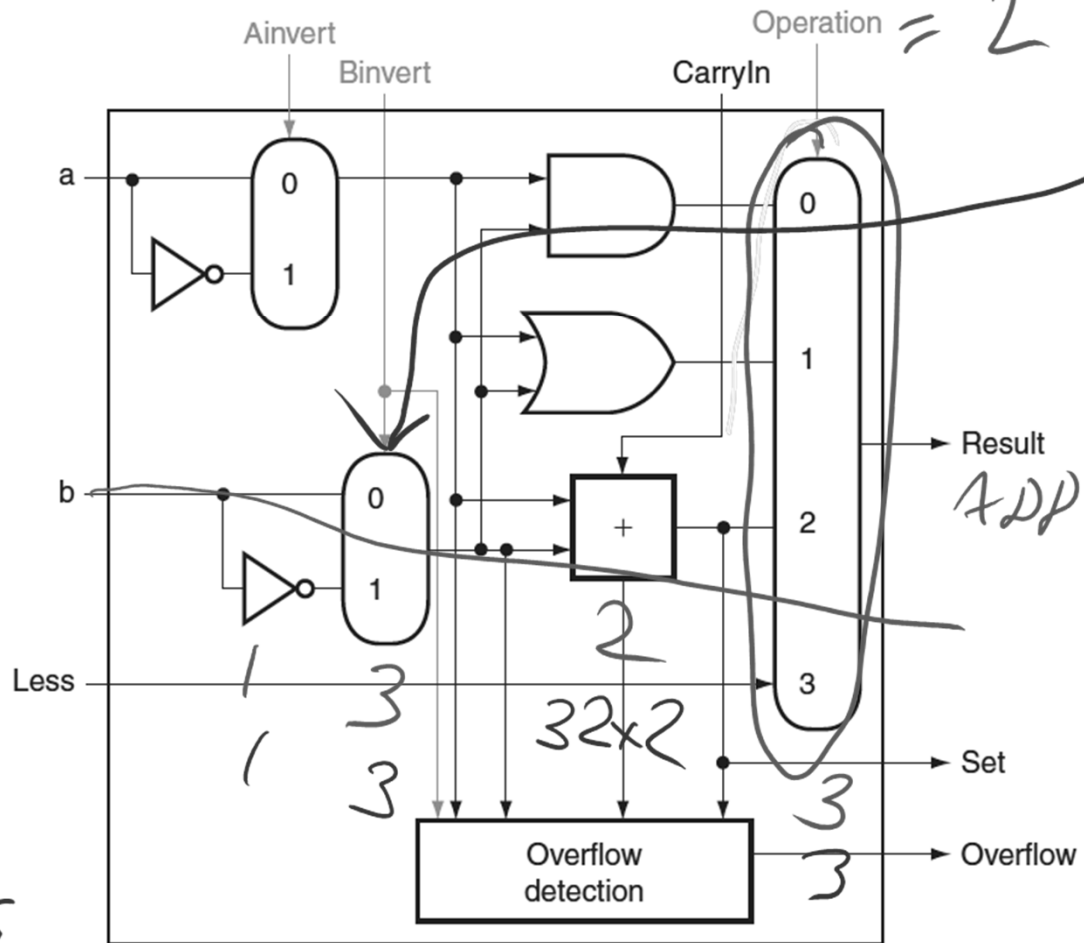

*1 - b, t*

*9 gatedelay*


*32 - bit*

*71 gate delays*

# Critical Path

What is the length of the critical path (in gates)?  
(counting inverters)


- A) 3
- B) 5
- C) 9
- D) 11

 

# Critical Path

What is the length of the critical path for a 32-bit ALU (in gates)? (counting inverters)

- A) 11
- B) 32
- C) 64
- D) 71

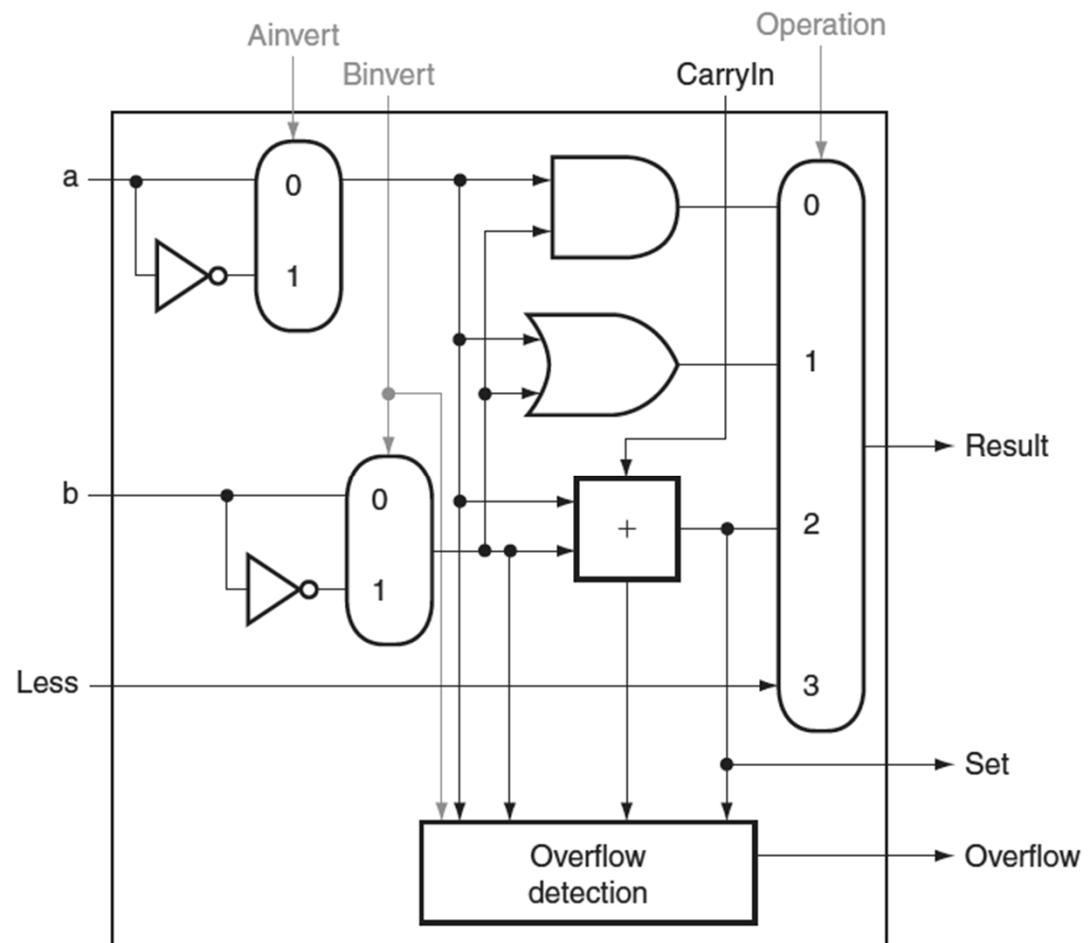

# Recap

---

We can now implement any combinational (combinatorial) logic circuit

- Decompose large circuit into manageable blocks
  - Encoders, Decoders, Multiplexors, Adders, ...
- Design each block
  - Binary encoded numbers for compactness
- Can implement circuits using NAND or NOR gates
- Can implement gates using use P- and N-transistors
- And can add and subtract numbers (in two's compliment)!
- Next, state and finite state machines...

# Administrivia

---

Make sure you are

Registered for class, can access CMS

Have a Section you can go to

Have project partner in same Lab Section

Lab1 and HW1 are out

Both due in one week, next Monday, start early

Work alone

But, use your resources

- Lab Section, Piazza.com, Office Hours, Homework Help Session,
- Class notes, book, Sections, CSUGLab

Homework Help Session

Wednesday and Friday from 3:30-5:30pm

Location: 203 Thurston



# Administrivia

---

Check online syllabus/schedule

- <http://www.cs.cornell.edu/Courses/CS3410/2012sp/schedule.html>

Slides and Reading for lectures

Office Hours

Homework and Programming Assignments

Prelims (in evenings):

- Tuesday, February 28<sup>th</sup>
- Thursday, March 29<sup>th</sup>
- Thursday, April 26<sup>th</sup>


Schedule is subject to change

# Stateful Components

---

Until now is combinatorial logic

 - Output is computed when inputs are present
- System has no internal state
- Nothing computed in the present can depend on what happened in the past!



Need a way to record data


Need a way to build stateful circuits

Need a state-holding device

Finite State Machines




# Unstable Devices

 

# Bistable Devices



---

- Stable and unstable equilibria?

 

A Simple Device

- In stable state,  $\bar{A} = B$

  

- How do we change the state?



# SR Latch

## Set-Reset (SR) Latch

Stores a value  $Q$  and its complement  $\bar{Q}$

S	R	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	0	1
1	0	1	0
1	1		

*hold*

  


# SR Latch

## Set-Reset (SR) Latch


Stores a value  $Q$  and its complement  $\bar{Q}$

S	R	Q	$\bar{Q}$
0	0	$Q$	$\bar{Q}$
0	1	0	1
1	0	1	0
1	1	forbidden	


hold

 

$S, R = 0, 0$

 

# Unclocked D Latch

 


Data (D) Latch

D	Q	$\bar{Q}$
0	0	1
1	1	0



# Unclocked D Latch

Data (D) Latch

 

D	Q	$\bar{Q}$
0	0	1
1	1	0

## Data Latch

- Easier to use than an SR latch
- No possibility of entering an undefined state

When D changes, Q changes

– ... immediately (after a delay of 2 Ors and 2 NOTs)

Need to control when the output changes

# D Latch with Clock



Level Sensitive D Latch

Clock high:


set/reset (according to D)

Clock low:

keep state (ignore D)

  

# D Latch with Clock

 


D	Q	$\bar{Q}$
0	0	1
1	1	0


S	R	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	0	1
1	0	1	0
1	1	forbidden	

clk	D	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	Q	$\bar{Q}$
1	0	0	1
1	1	1	0

# D Latch with Clock

 

D	Q	$\bar{Q}$
0	0	1
1	1	0

 


clk	D	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	Q	$\bar{Q}$
1	0	0	1
1	1	1	0

# Clocks

---



Clock helps coordinate state changes

 
- Usually generated by an oscillating crystal
- Fixed period; frequency =  $1/\text{period}$



# Edge-triggering

---

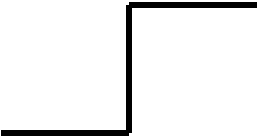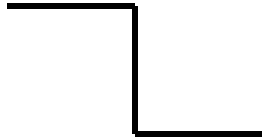 - Can design circuits to change on the rising or falling edge
- Trigger on rising edge = positive edge-triggered 
- Trigger on falling edge = negative edge-triggered 
- Inputs must be stable just before the triggering edge




# Clock Methodology

---

## Clock Methodology


- Negative edge, synchronous

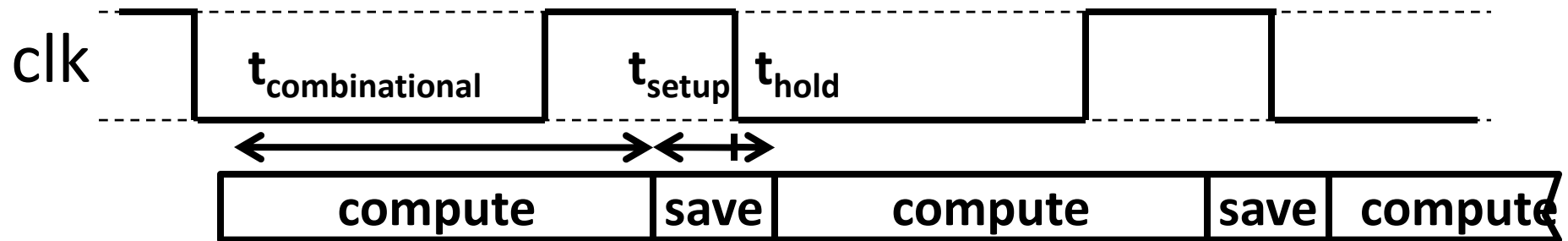

– Signals must be stable near falling clock edge


- Positive edge synchronous
- Asynchronous, multiple clocks, . . .

# Edge-Triggered D Flip-Flop

 
 
## D Flip-Flop

- Edge-Triggered
- Data is captured when clock is high
- Outputs change only on falling edges





# Clock Disciplines

---

## Level sensitive

- State changes when clock is high (or low)


## Edge triggered

- State changes at clock edge


positive edge-triggered



negative edge-triggered

 


# Registers

 
 
## Register

- D flip-flops in parallel
- shared clock
- extra clocked inputs: write\_enable, reset, ...



# An Example: What will this circuit do?

---

