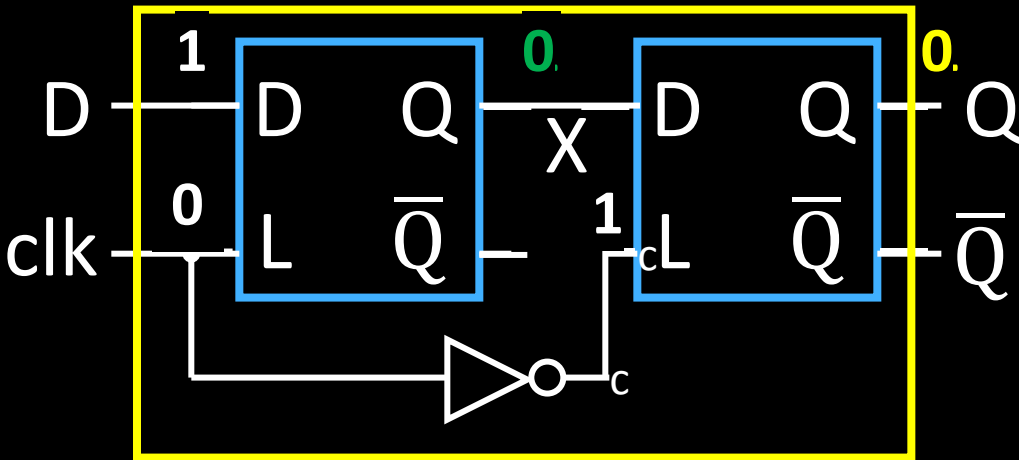


Sixth Attempt: Edge-Triggered D Flip-Flop



D Flip-Flop

- Edge-Triggered
- Data captured when clock is high
- Output changes only on falling edges

