
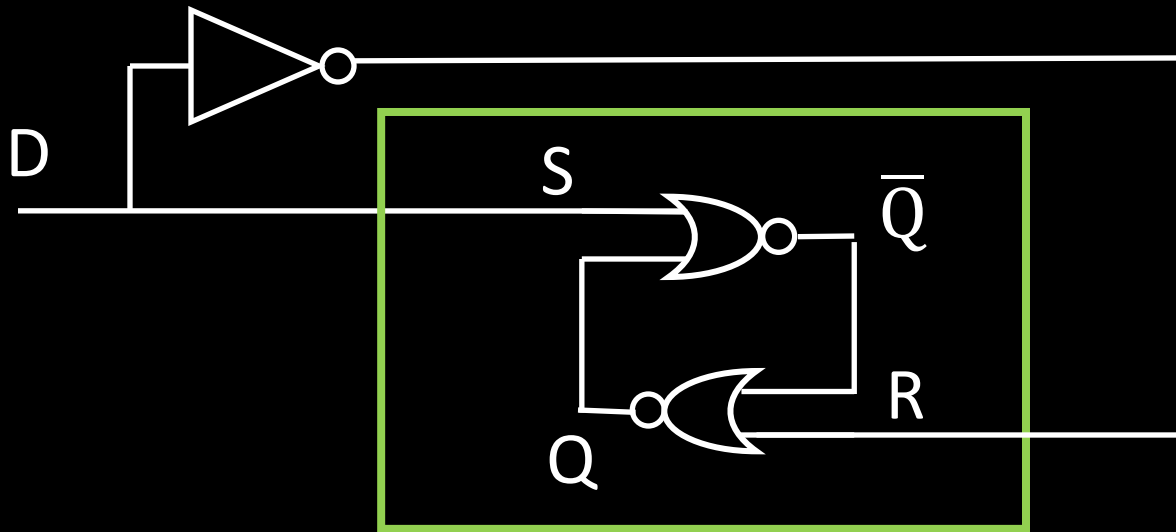


Fourth Attempt: (Unclocked) D Latch

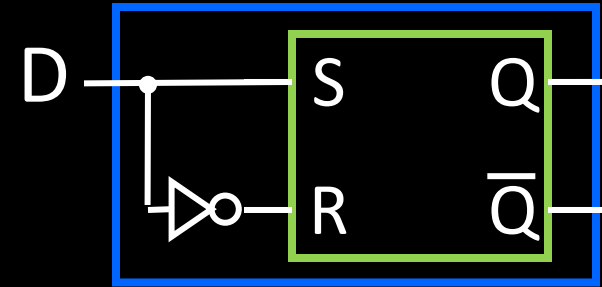

Fill in the truth table?



D	Q	\bar{Q}
0		
1		

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0