

# State and Finite State Machines

**Anne Bracy**

**CS 3410**

Computer Science

Cornell University


The slides are the product of many rounds of teaching CS 3410 by Professors Weatherspoon, Bala, Bracy, and Sirer.

See P&H Appendix B.7, B.8, B.10, B.11

# Stateful Components
 
## Combinational logic

- Output computed directly from inputs
- System has no internal state
- Nothing depends on the past!



Need:

- to record data
- to build stateful circuits
- a state-holding device

Enter: Sequential Logic & Finite State Machines

# Goals for Today

## State


- Storing 1 bit
  - Bistable Circuit
  - Set-Reset Latch
  - D Latch
  - D Flip-Flops
- Storing N bits:
  - Registers
  - Memory

## Finite State Machines (FSM)

- Mealy and Moore Machines
- Serial Adder Example



# Round 1: Bistable Circuit

- Stable and unstable equilibria?

 



A Simple Device

In stable state,  $\bar{A} = B$

  

How do we change the state?

# Round 2: Set-Reset (SR) Latch



 
 


Stores a value  $Q$  and its complement



S	R	Q	$\bar{Q}$
0	0		
0	1		
1	0		
1	1		

*For reference:*

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

    

# Round 2: Set-Reset (SR) Latch

  

Stores a value  $Q$  and its complement


S	R	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	0	1
1	0	1	0
1	1	0	0

For reference:


A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

If  $Q$  is 1, will stay 1  
if  $Q$  is 0, will stay 0

 
What happens when  $S, R$  changes from 1,1 to 0,0?  
 $Q, \bar{Q}$  become unstable, oscillate ( $0,0 \rightarrow 1,1 \rightarrow 0,0$ )




no change

 

Resets  $Q$

 

Sets  $Q$

 

Forbidden! <sup>6</sup>


# iClicker Question

Frequency should be set to **AA**

What's wrong with using the SR Latch to store 1 bit?

- A. Q is undefined when  $S=0$  and  $R=0$   
(That's why this is called the forbidden state.)
- B. Q oscillates between 0 and 1 when the inputs transition from  $S=1$  and  $R=1 \rightarrow S=0$  and  $R=0$
- C. The SR Latch is problematic b/c it has two outputs to store a single bit.
- D. There is nothing wrong with the SR Latch!

# Round 3: D Latch (1)

 


- Inverter prevents SR Latch from entering 1,1 state
- C = enables change

C	D	Q	$\bar{Q}$
0	0		
0	1		
1	0		
1	1		


C = 1, D Latch *transparent*:  
set/reset (according to D)

 C = 0, D Latch *opaque*:  
keep state (ignore D)





# Round 3: D Latch (1)

 


C	D	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	Q	$\bar{Q}$
1	0	0	1
1	1	1	0

- Inverter prevents SR Latch from entering 1,1 state
- C = enables change

C = 1, D Latch *transparent*:  
set/reset (according to D)

 
C = 0, D Latch *opaque*:  
keep state (ignore D)


 
# Aside: Clocks

Clock helps coordinate state changes


- Fixed period
- Frequency =  $1/\text{period}$



# Clock Disciplines
 
## Level sensitive

- State changes when clock is high (or low)




## Edge triggered

- State changes at clock edge

positive edge-triggered




negative edge-triggered

 

# Clock Methodology

## Clock Methodology

- Negative edge, synchronous

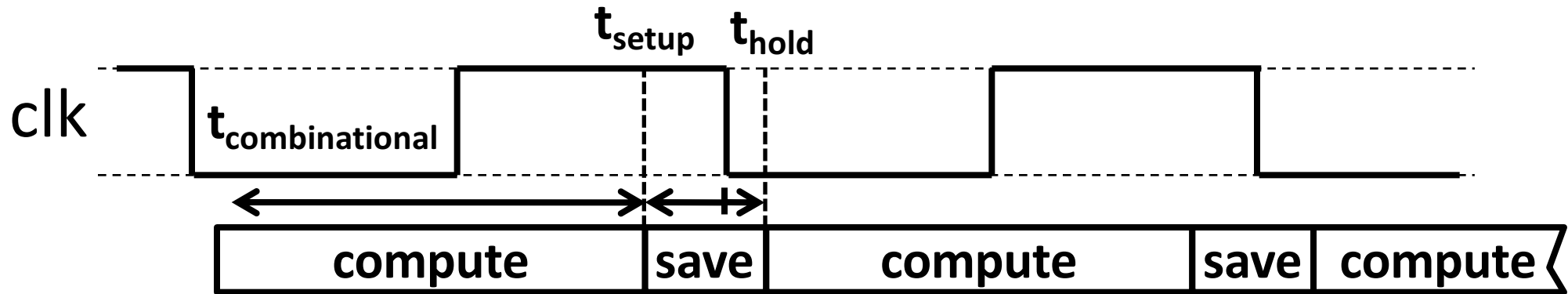


Edge-Triggered → signals must be stable near falling edge

“near” = before and after


$t_{\text{setup}}$   $t_{\text{hold}}$

# Round 3: D Latch (2)

 


- Level sensitive
- Inverter prevents SR Latch from entering 1,1 state
- clk = enables change

clk	D	Q	$\bar{Q}$
0	0		
0	1		
1	0		
1	1		

 


# Round 3: D Latch (2)

 


- Level sensitive
- Inverter prevents SR Latch from entering 1,1 state
- clk = enables change

clk	D	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	Q	$\bar{Q}$
1	0	0	1
1	1	1	0

 


# Round 4: D Flip-Flop

 


- Edge-Triggered
- Data captured when clock high
- Output changes only on falling edges
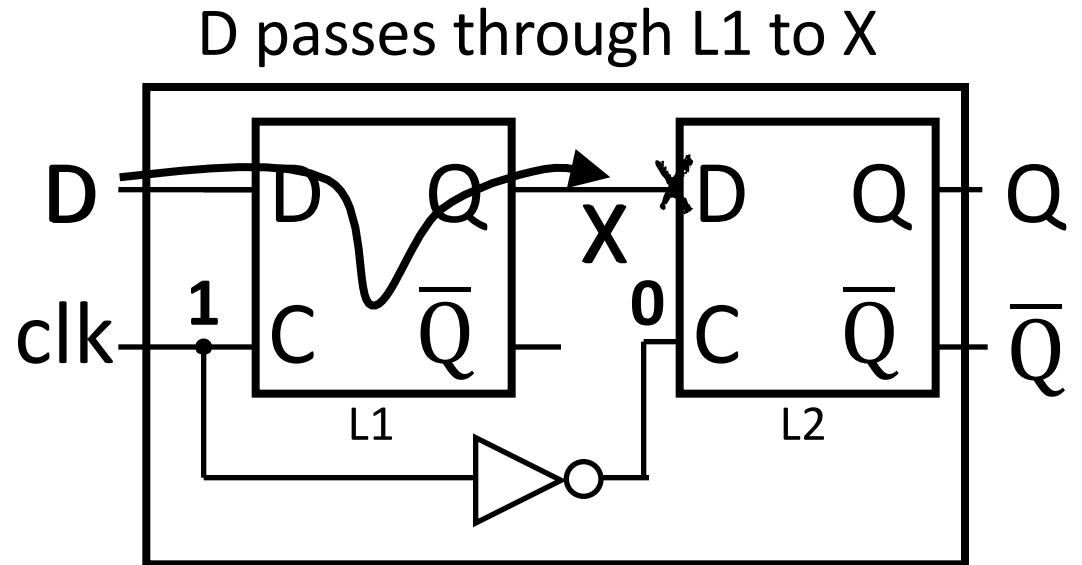
# Round 4: D Flip-Flop

Clock = 1: L1 *transparent*  
L2 *opaque*



 Clock = 0: L1 *opaque*  
L2 *transparent*




Thus, on edge of the clock  
(when **CLK falls from 1→0**)

(D passes through to Q)



# DFF Activity: Fill in the timing graph

 


Clock = 1


D passes through L1 to X

Clock = 0


X passes through L2 to Q

 

# Round 4: D Flip-Flop

 

 - Edge-Triggered
- Data captured when clock high
- Output changes only on falling edges



# Goals for Today

## State

- Storing 1 bit
  - Bistable Circuit
  - Set-Reset Latch
  - D Latch
  - D Flip-Flops
- Storing N bits:
  - Registers
  - Memory


~~A word about clocks~~

A word about terminology


## Finite State Machines (FSM)

- Mealy and Moore Machines
- Serial Adder Example

# Registers

 

 
- D flip-flops in parallel
- shared clock
- Additional (optional) inputs: writeEnable, reset, ...



# Register File
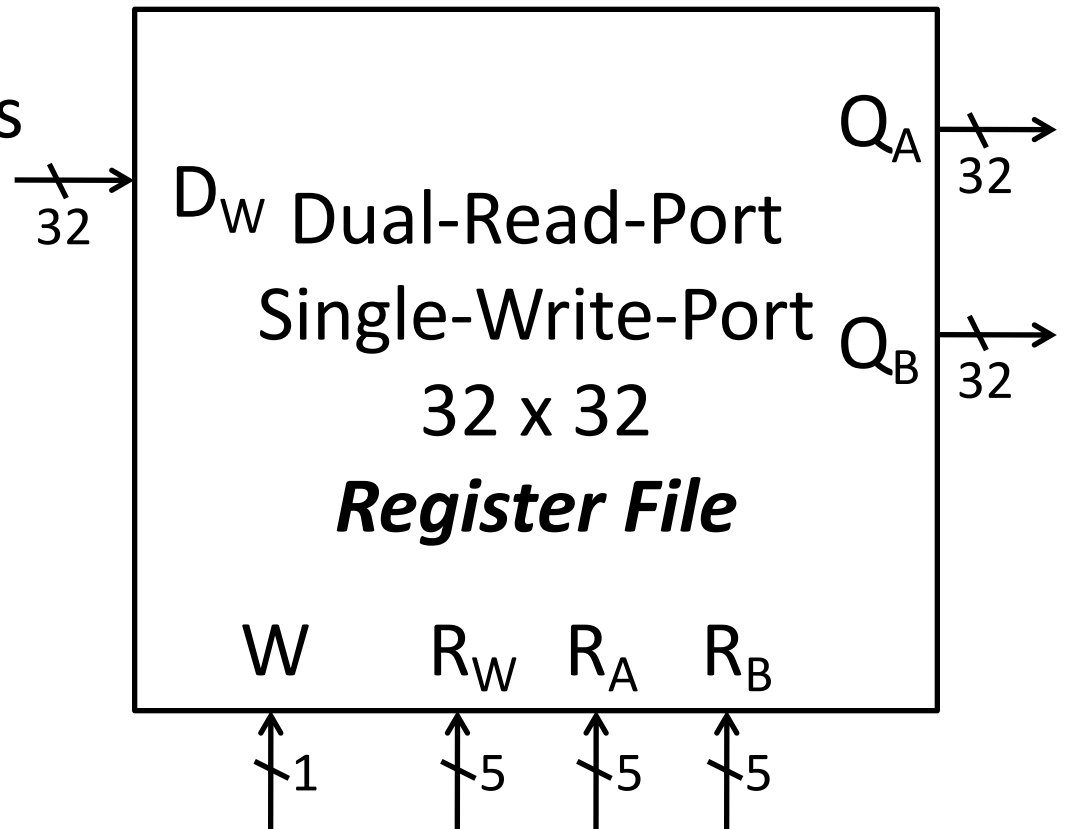
## Register File

- N read/write registers
- Indexed by register number




# Writing to the Register File (1)

## Register File

- N read/write registers
- Indexed by register number

`addi r5, r0, 10`

 


How to write to ***one*** register in the register file?

- Need a decoder




# Activity: 3-to-8 decoder truth table & circuit

i2	i1	i0	o0	o1	o2	o3	o4	o5	o6	o7
0	0	0								
0	0	1								
0	1	0								
0	1	1								
1	0	0								
1	0	1								
1	1	0								
1	1	1								

 

# Activity: 3-to-8 decoder truth table & circuit

i2	i1	i0	o0	o1	o2	o3	o4	o5	o6	o7
0	0	0	1							
0	0	1		1						
0	1	0			1					
0	1	1				1				
1	0	0					1			
1	0	1						1		
1	1	0							1	
1	1	1								1

   




# Writing to the Register File (2)

## Register File

- N read/write registers
- Indexed by register number

```
addi r5, r0, 10
```

 

How to write to **one** register in the register file?

- Need a decoder


# Reading from the Register File

## Register File

- N read/write registers
- Indexed by register number

## How to read from two registers?

- Need a multiplexor

 


# Register File

## Register File

- N read/write registers
- Indexed by register number
 
## Implementation:


- D flip flops to store bits
- Decoder for each write port
- Mux for each read port



# Register File
 
## Register File

- N read/write registers
- Indexed by register number



## Implementation:

- D flip flops to store bits
- Decoder for each write port
- Mux for each read port

# Tradeoffs


## Register File tradeoffs

- + Very fast (a few gate delays for both read and write)
- + Adding extra ports is straightforward
- Doesn't scale

e.g. 32Mb register file with  
32 bit registers

Need 32x 1M-to-1 multiplexor  
and 32x 20-to-1M decoder

How many logic gates/transistors?

 


# Takeaways

- Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But, SR Latch has a forbidden state.
- D Latch can store and change a bit like an SR Latch while avoiding a forbidden state.
- A D Flip-Flop stores one bit. The bit can be changed in a synchronized fashion on the edge of a clock signal.
- An  $N$ -bit **register** stores  $N$ -bits. It is created with  $N$  D-Flip-Flops in parallel plus a shared clock.
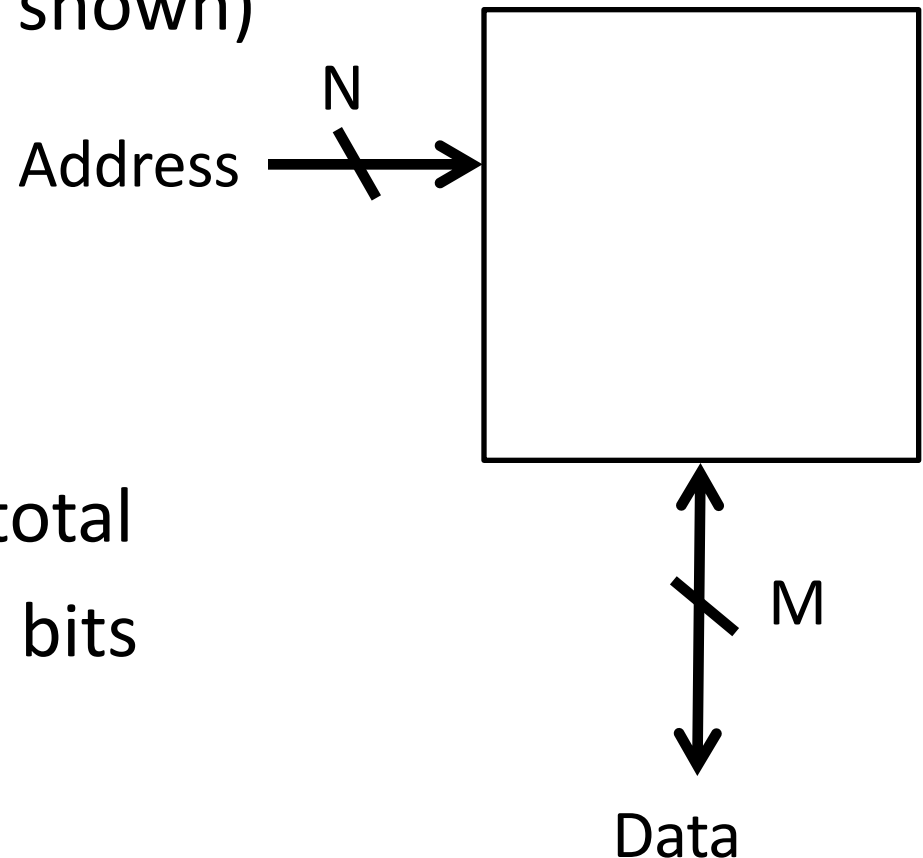
# Memory


- Storage Cells + bus
- Inputs: Address, Data (for writes)
- Outputs: Data (for reads)
- Also need R/W signal (not shown)



- $N$  address bits  $\rightarrow 2^N$  words total
- $M$  data bits  $\rightarrow$  each word  $M$  bits
 
# Memory

- Storage Cells + bus
- Decoder selects a word line
- R/W selector determines access type
- Word line is then coupled to the data lines





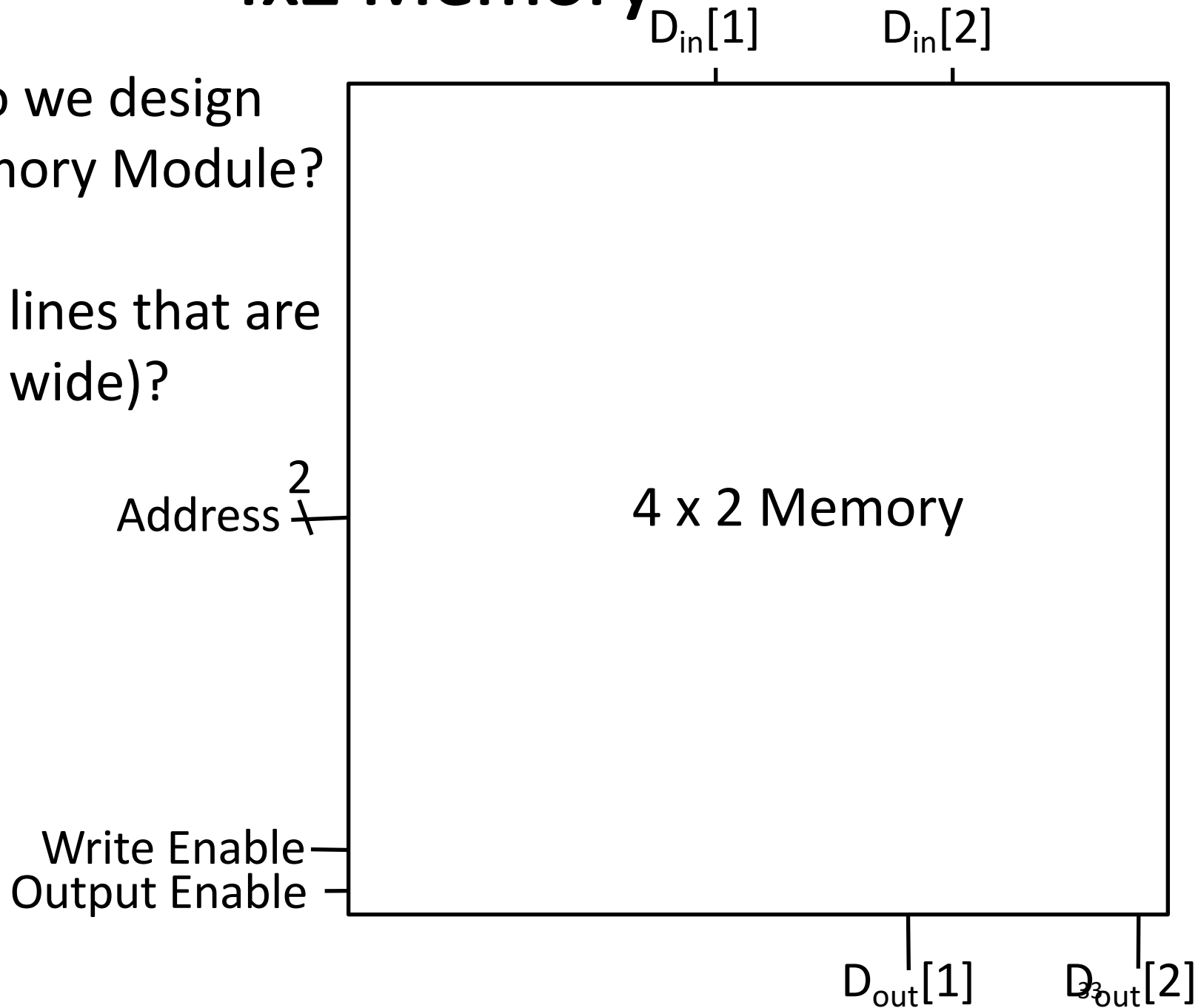
# 4x2 Memory

E.g. How do we design  
a 4 x 2 Memory Module?


(i.e. 4 word lines that are  
each 2 bits wide)?


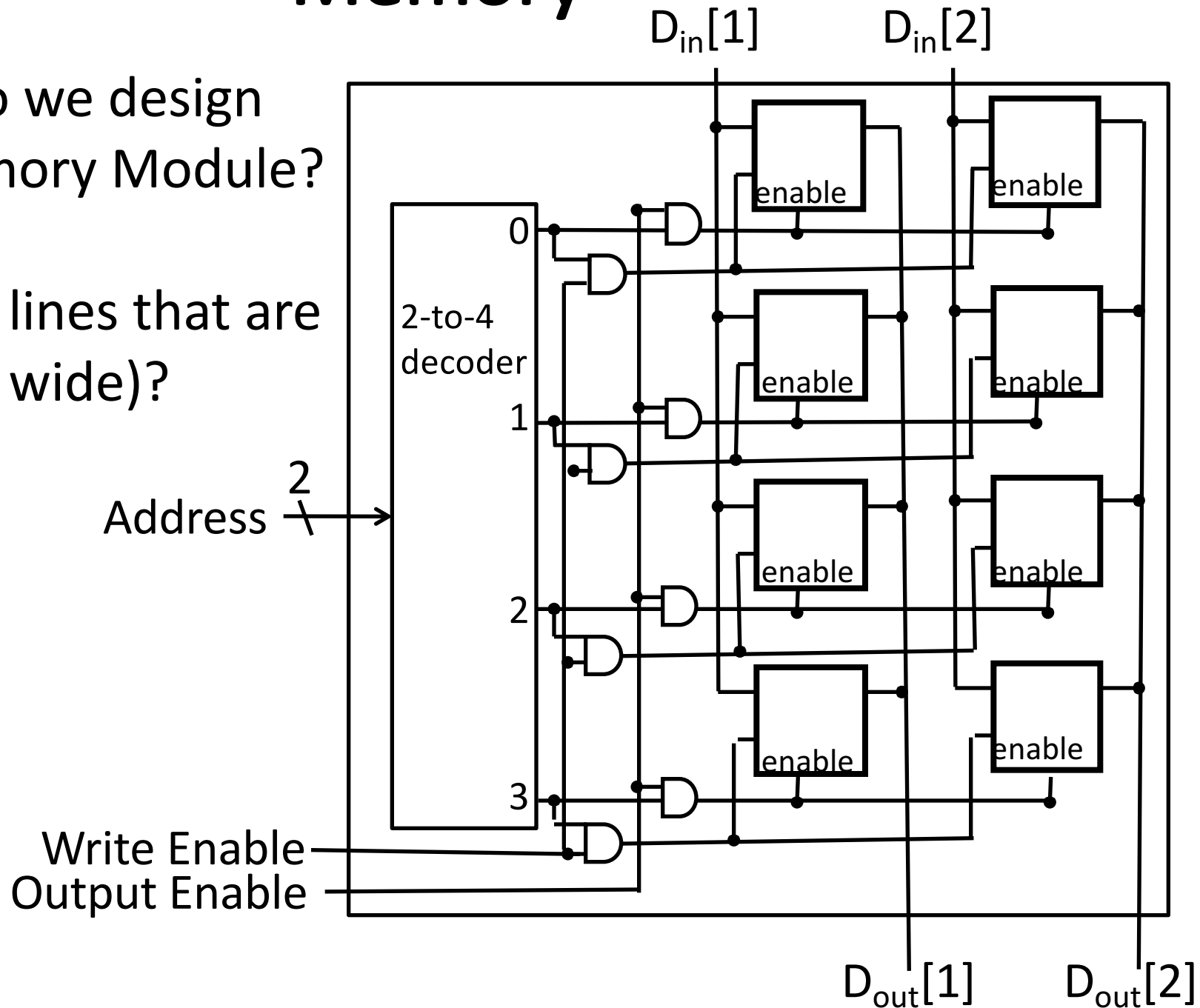
# Memory

E.g. How do we design  
a 4 x 2 Memory Module?


(i.e. 4 word lines that are  
each 2 bits wide)?


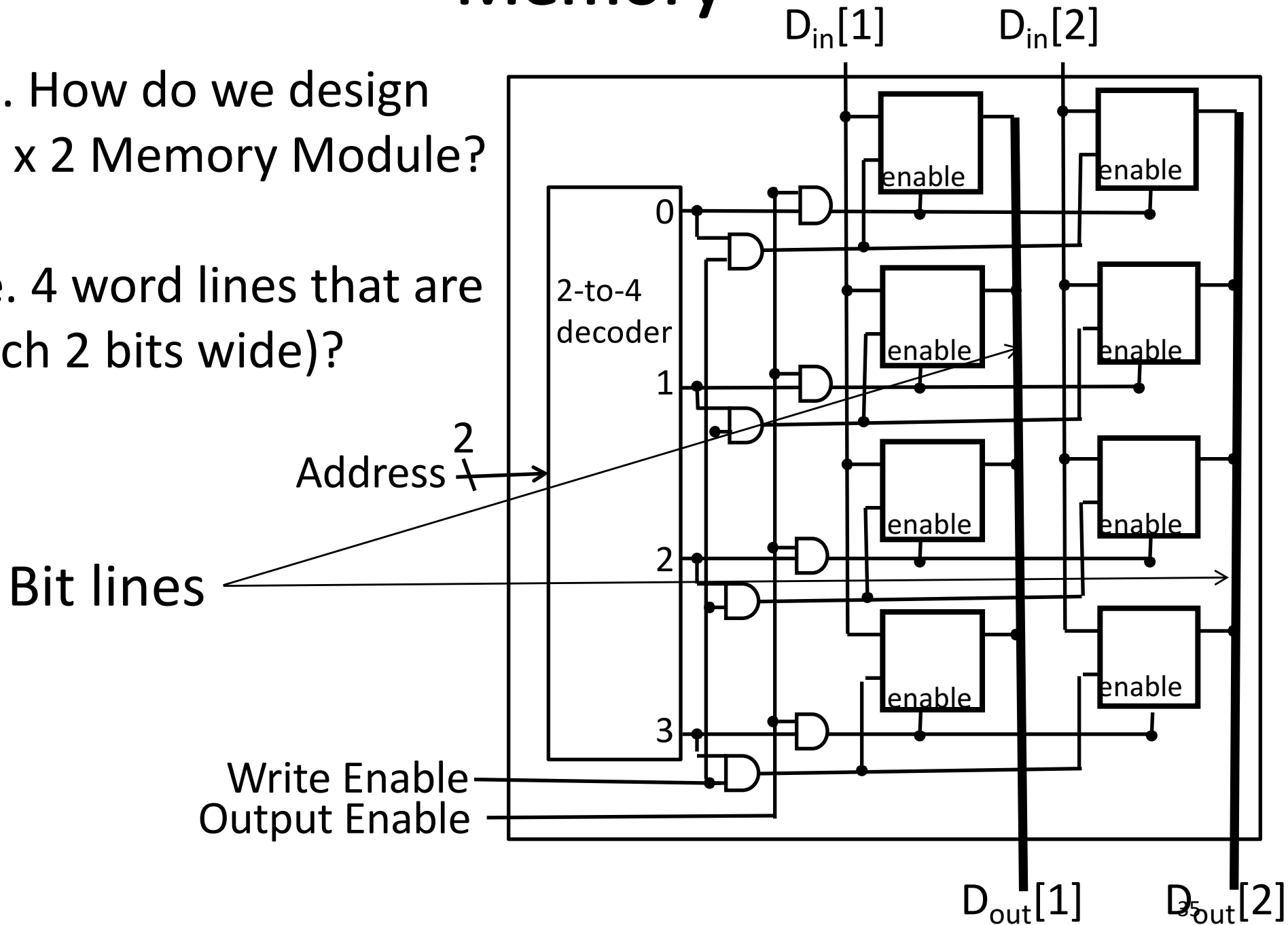
# Memory

E.g. How do we design  
a 4 x 2 Memory Module?

(i.e. 4 word lines that are  
each 2 bits wide)?




# Memory

E.g. How do we design  
a 4 x 2 Memory Module?

(i.e. 4 word lines that are  
each 2 bits wide)?

Word lines

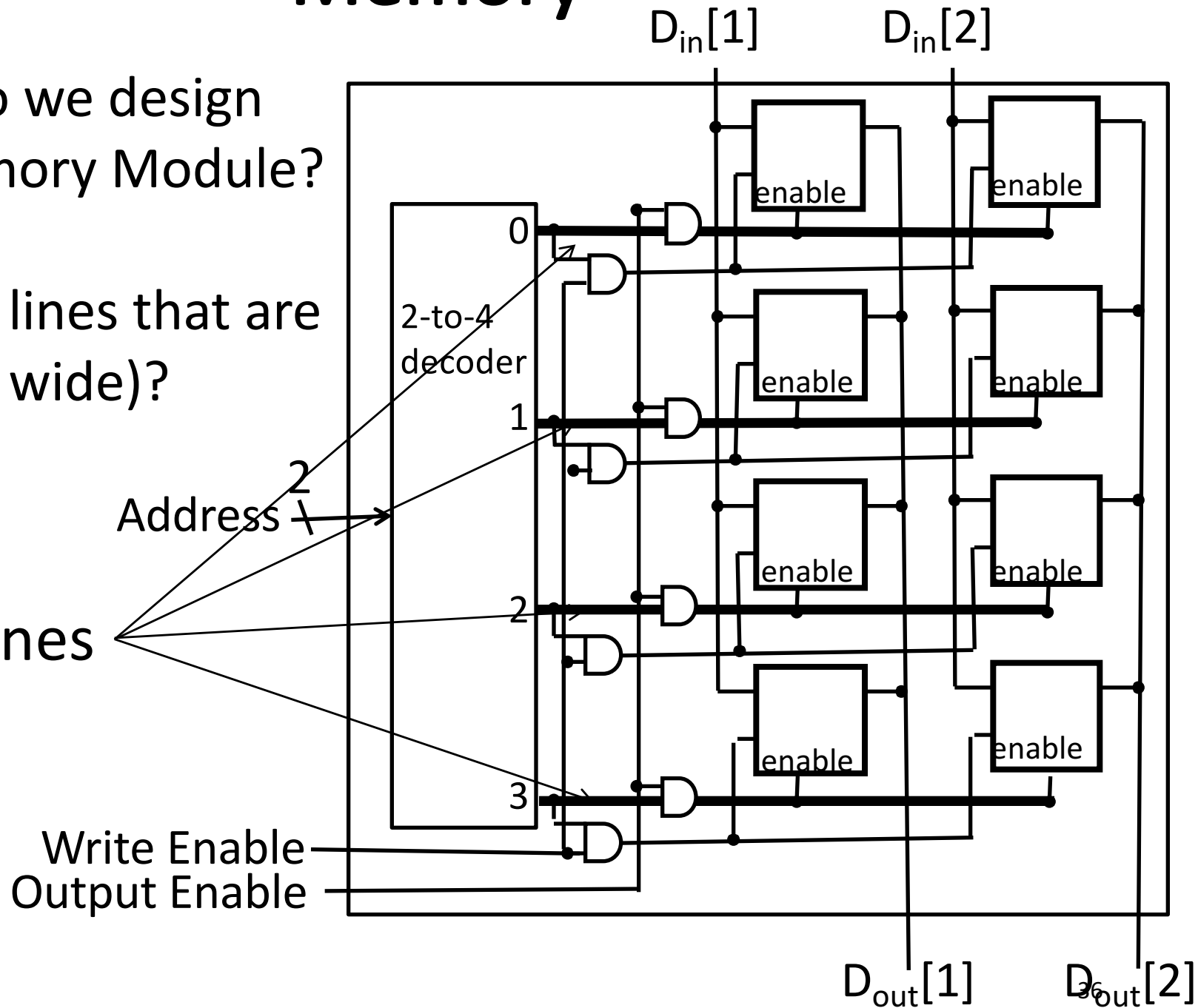


# iClicker Question

What's your familiarity with memory (SRAM, DRAM)?

- A. I've never heard of any of this.
- B. I've heard the words SRAM and DRAM, but I have no idea what they are.
- C. I know that DRAM means main memory.
- D. I know the difference between SRAM and DRAM and where they are used in a computer system.

# SRAM Cell

## Typical SRAM Cell

 

Each cell stores one bit, and requires 4 – 8 transistors (6 is typical)

Pass-Through  
Transistors

# SRAM Summary


## SRAM

- A few transistors ( $\sim 6$ ) per cell
- Used for working memory (caches)
- But for even higher density...

# Dynamic RAM: DRAM

## Dynamic-RAM (DRAM)

- Data values require constant refresh

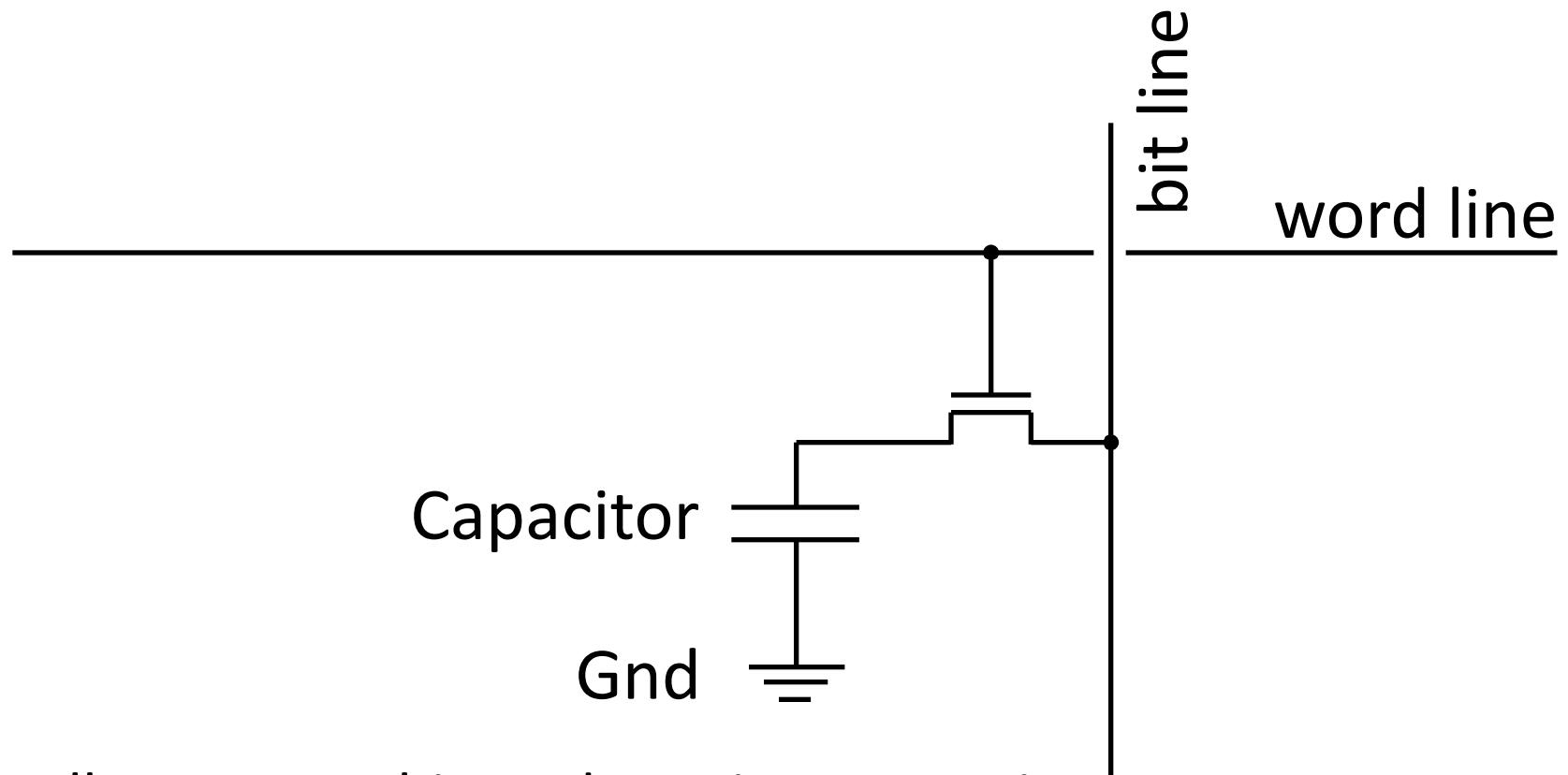


Each cell stores one bit, and requires 1 transistors



# Dynamic RAM: DRAM

## Dynamic-RAM (DRAM)

- Data values require constant refresh

 

Each cell stores one bit, and requires 1 transistors

# DRAM vs. SRAM

Single transistor vs. many gates

- Denser, cheaper (\$30/1GB vs. \$30/2MB)
- But more complicated, and has analog sensing

Also needs refresh

- Read and write back...
- ...every few milliseconds
- Organized in 2D grid, so can do rows at a time
- Chip can do refresh internally

Hence... slower and energy inefficient

# Memory

## Register File tradeoffs

- + Very fast (a few gate delays for both read and write)
- + Adding extra ports is straightforward
- Expensive, doesn't scale
- Volatile

## Volatile Memory alternatives: SRAM, DRAM, ...

- Slower
- + Cheaper, and scales well
- Volatile

## Non-Volatile Memory (NV-RAM): Flash, EEPROM, ...

- + Scales well
- Limited lifetime; degrades after 100000 to 1M writes

# Goals for Today

## State

- Storing 1 bit
  - Bistable Circuit
  - Set-Reset Latch
  - D Latch
  - D Flip-Flops
- Storing N bits:
  - Registers
  - Memory

## Finite State Machines (FSM)

- Mealy and Moore Machines
- Serial Adder Example

# Finite State Machines

An electronic machine which has


- external inputs
- externally visible outputs
- internal state

Output and next state depend on

- inputs
- current state



# Automata Model

## Finite State Machine

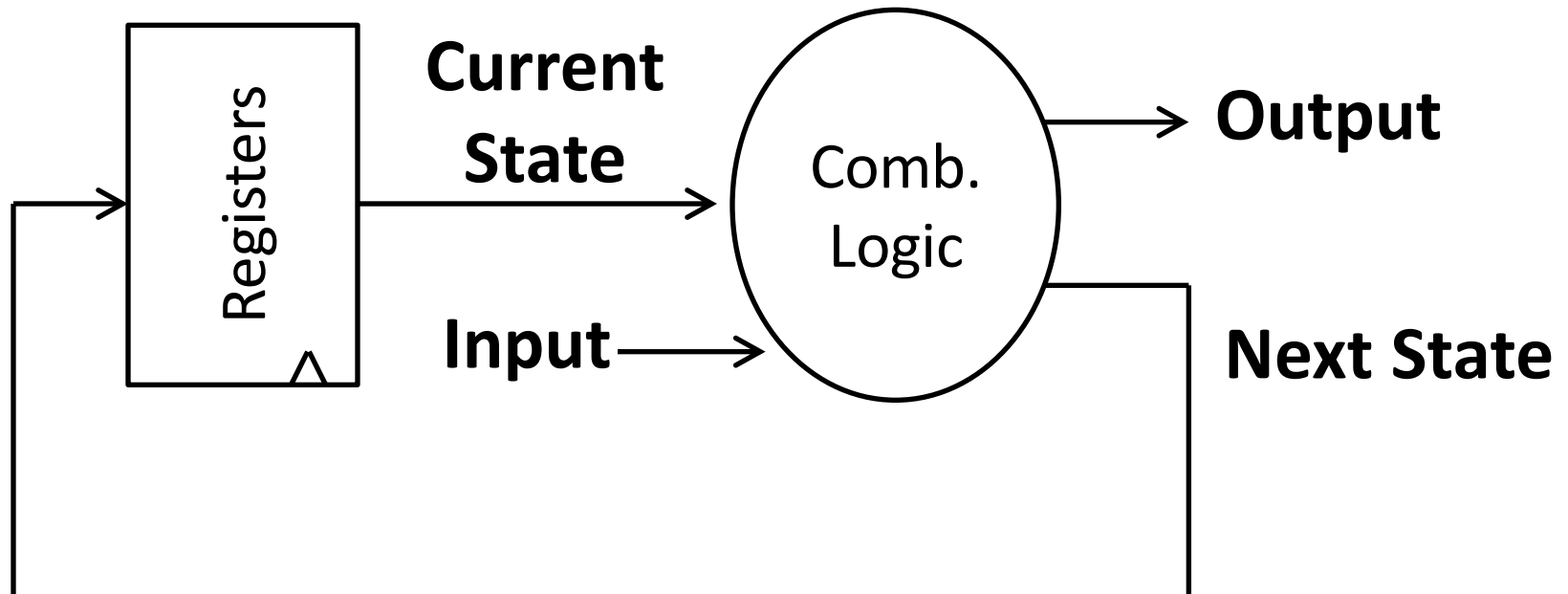

- inputs from external world
- outputs to external world
- internal state
- combinational logic

# FSM Example

  

Input: **1** or **0**

Output: **1** or **0**


States: **A** or **B**

*What input pattern is the FSM “looking for”?*

(Mealy Machine)

# Mealy Machine

## General Case: Mealy Machine



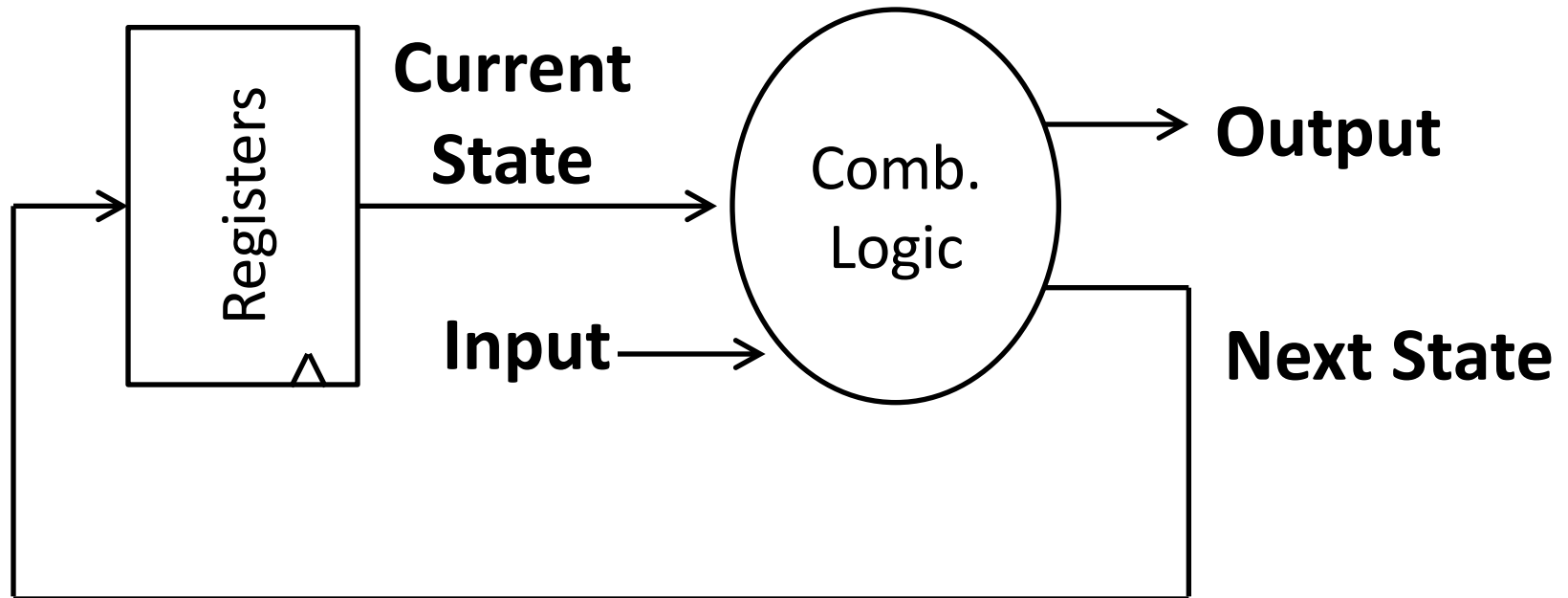


Outputs and next state depend on both current state and input



# Special Case: Moore Machine


Outputs depend only on current state

  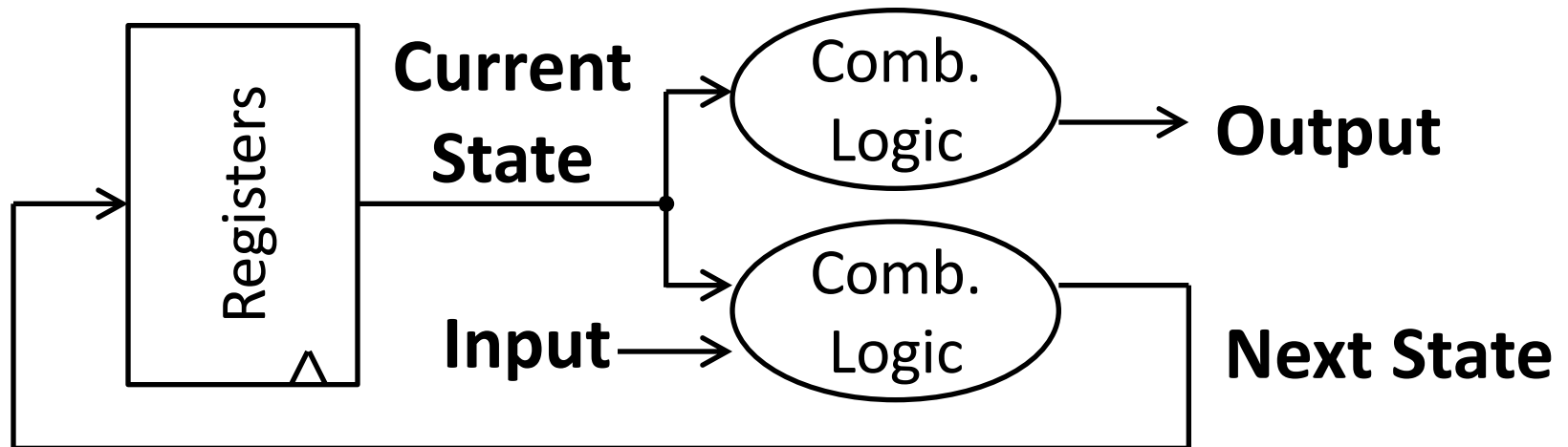
 
# Activity: Build a Logic Circuit for a Serial Adder

Add two infinite input bit streams


- streams are sent with least-significant-bit (lsb) first
- How many states are needed to represent FSM?
- Draw and Fill in FSM diagram



Strategy:

- (1) Draw a state diagram (e.g. Mealy Machine)
- (2) Write output and next-state tables
- (3) Encode states, inputs, and outputs as bits
- (4) Determine logic equations for next state and outputs



# FSM: State Diagram – start here

 

\_\_\_ states:  
Inputs: ??? and ???  
Output: ???





# FSM: State Diagram

  

\_\_\_ states:  
Inputs: ??? and ???  
Output: ???

# FSM: State Diagram

  

Two states: S0 (no carry in), S1 (carry in)


Inputs: a and b

Output: z

- z is the sum of inputs a, b, and carry-in (one bit at a time)
- A carry-out is the next carry-in state.
- .



# FSM: State Diagram

 


??	??	Current state	?	Next state

(2) Write down all input and state combinations




# Serial Adder: State Table

 

a	b	Current state	z	Next state

(2) Write down all input and state combinations

# Serial Adder: State Table

 


a	b	Current state	z	Next state
0	0	S0	0	S0
0	1	S0	1	S0
1	0	S0	1	S0
1	1	S0	0	S1
0	0	S1	1	S0
0	1	S1	0	S1
1	0	S1	0	S1
1	1	S1	1	S1

(2) Write down all input and state combinations






# FSM: State Diagram – start here

 

??	??	Current state	?	Next state

(3) Encode states, inputs, and outputs as bits

# Serial Adder: State Assignment

 

a	b	s	z	s'
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

(3) Encode states, inputs, and outputs as bits

Two states, so 1-bit is sufficient  
(single flip-flop will encode the state)




# FSM: State Diagram

??	??	Current state	?	Next state

(4) Determine logic equations for next state and outputs

# Serial Adder: Circuit

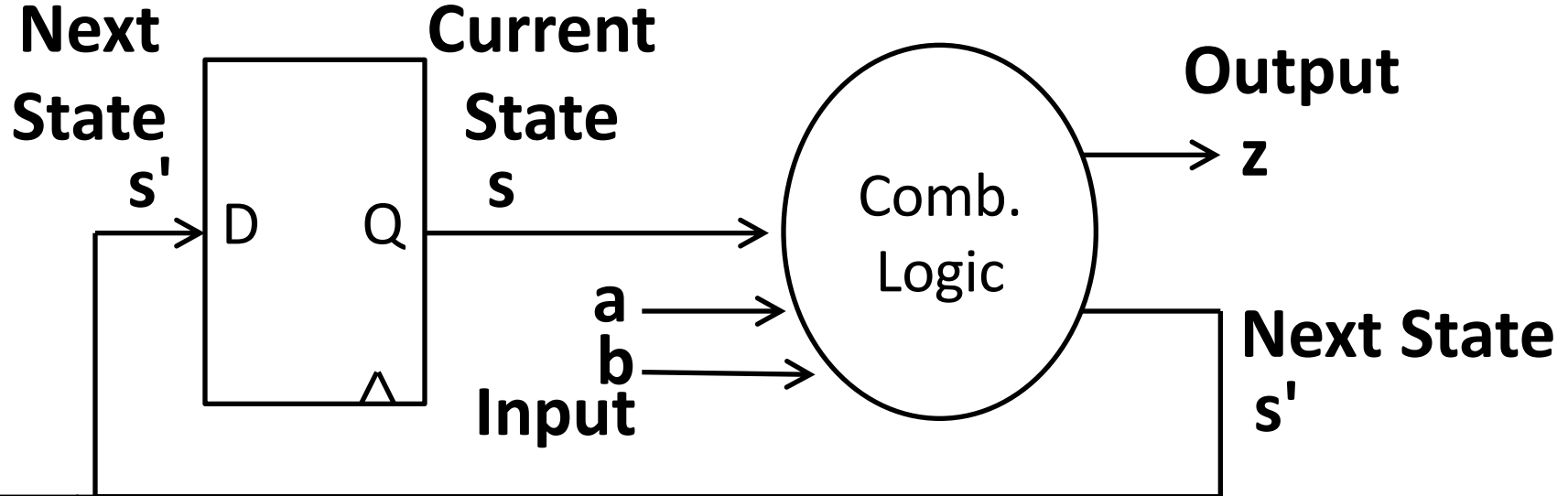

a	b	s	z	s'
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1


(4) Determine logic equations for next state and outputs

Combinational Logic Equations

$$z = \bar{a}b\bar{s} + a\bar{b}\bar{s} + \bar{a}bs + abs$$

$$s' = ab\bar{s} + \bar{a}bs + a\bar{b}s + abs$$

# Sequential Logic Circuits

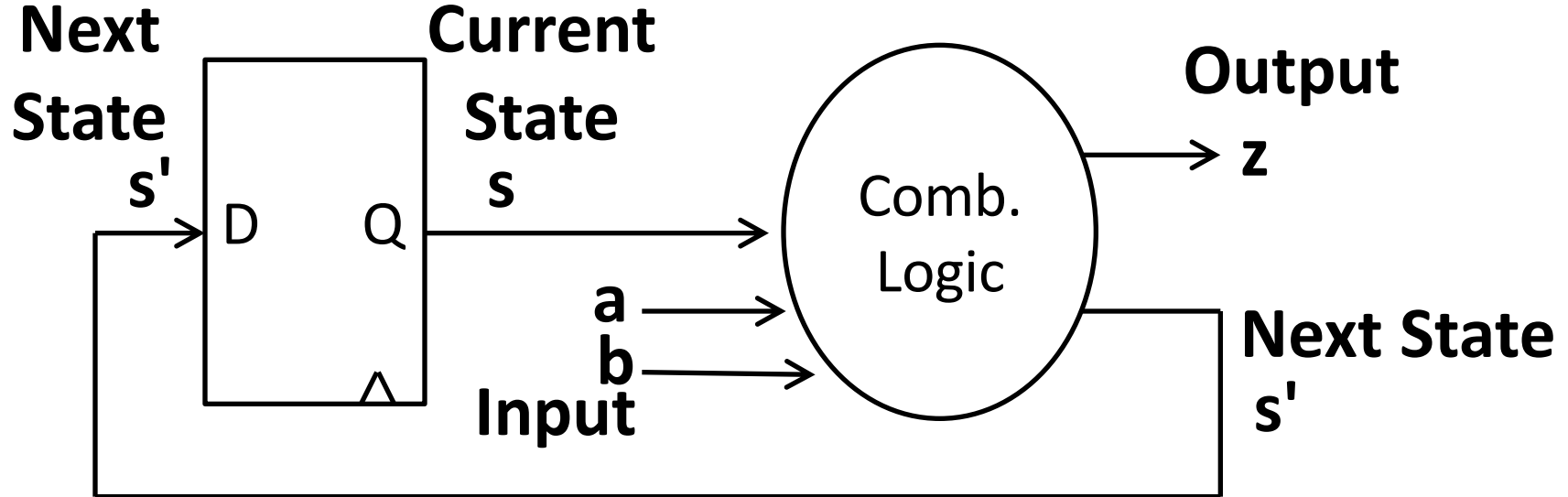

$$z = \bar{a}b\bar{s} + \bar{a}\bar{b}s + \bar{a}bs + abs$$

$$s' = ab\bar{s} + \bar{a}bs + \bar{a}\bar{b}s + abs$$

Strategy:

- (1) Draw a state diagram (e.g. Mealy Machine)
- (2) Write output and next-state tables
- (3) Encode states, inputs, and outputs as bits
- (4) Determine logic equations for next state and outputs

# Summary

We can now store data values

- Stateful circuit elements (D Flip Flops, Registers, ...)
- Clock synchronizes state changes
- State Machines or Ad-Hoc Circuits