

Finite State Machines

Hakim Weatherspoon

CS 3410

Computer Science


Cornell University

The slides are the product of many rounds of teaching CS 3410 by Professors Weatherspoon, Bala, Bracy, and Sirer.

Stateful Components

Combinational logic

 - Output computed directly from inputs
- System has no internal state
- Nothing depends on the past!



Need:

- To record data
- To build stateful circuits
- A state-holding device

Sequential Logic & Finite State Machines

Finite State Machines

An electronic machine which has

- external inputs
- externally visible outputs
- internal state

Output and next state depend on

- inputs
- current state

Abstract Model of FSM

Machine is

$$M = (S, I, O, \delta)$$

S : Finite set of states

I : Finite set of inputs


O : Finite set of outputs

δ : State transition function

Next state depends on present input *and* present state



Automata Model

Finite State Machine

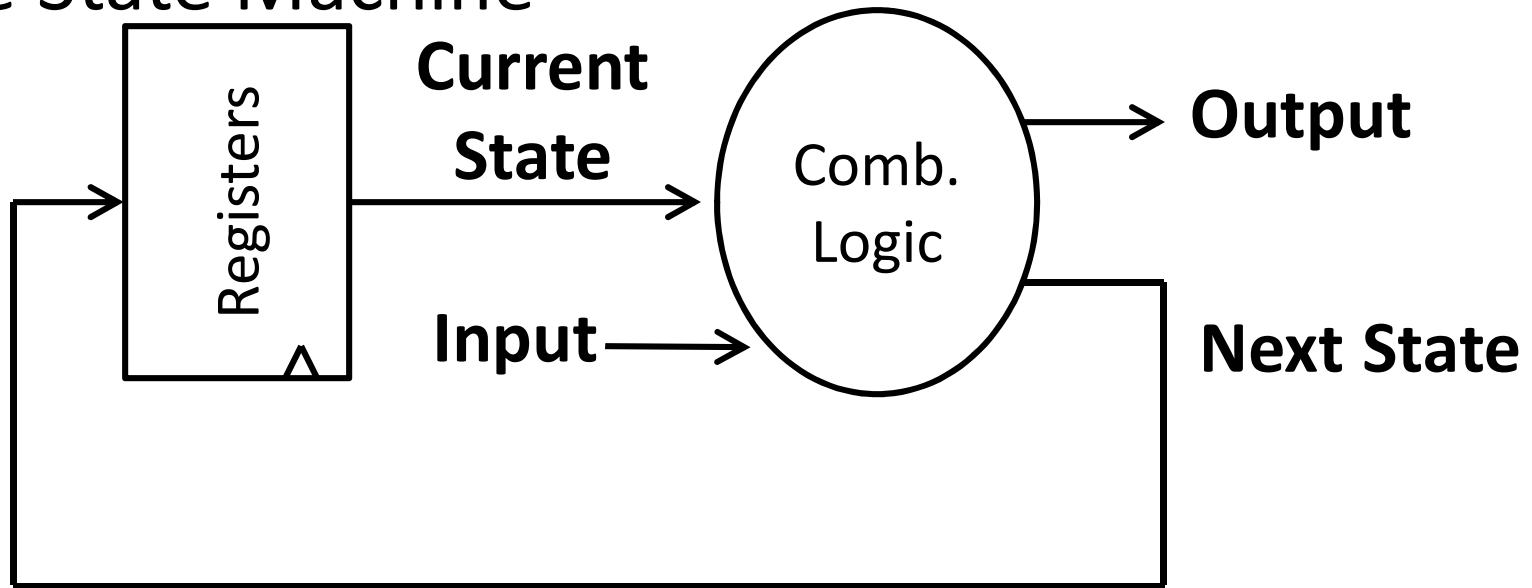

- inputs from external world
- outputs to external world
- internal state
- combinational logic

FSM Example

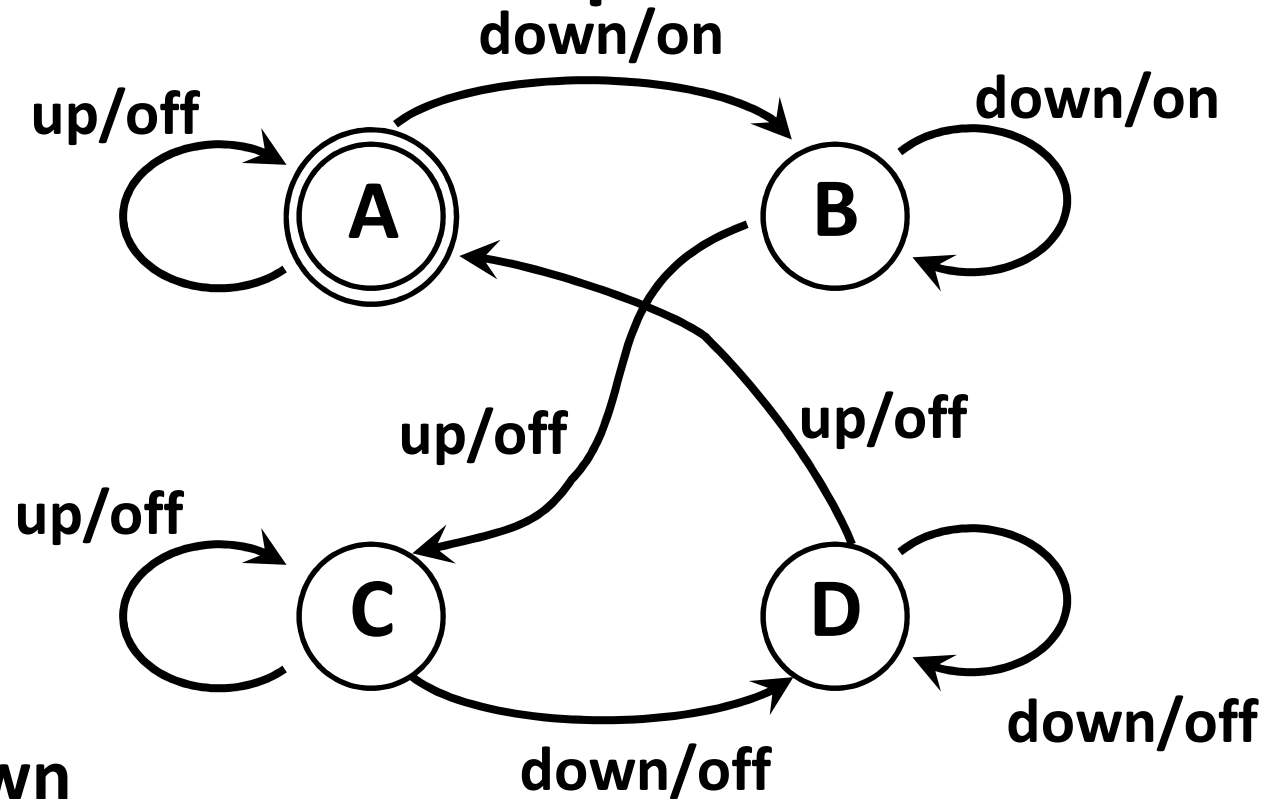
 


Input: **up** or **down**

Output: **on** or **off**

States: **A**, **B**, **C**, or **D**

FSM Example

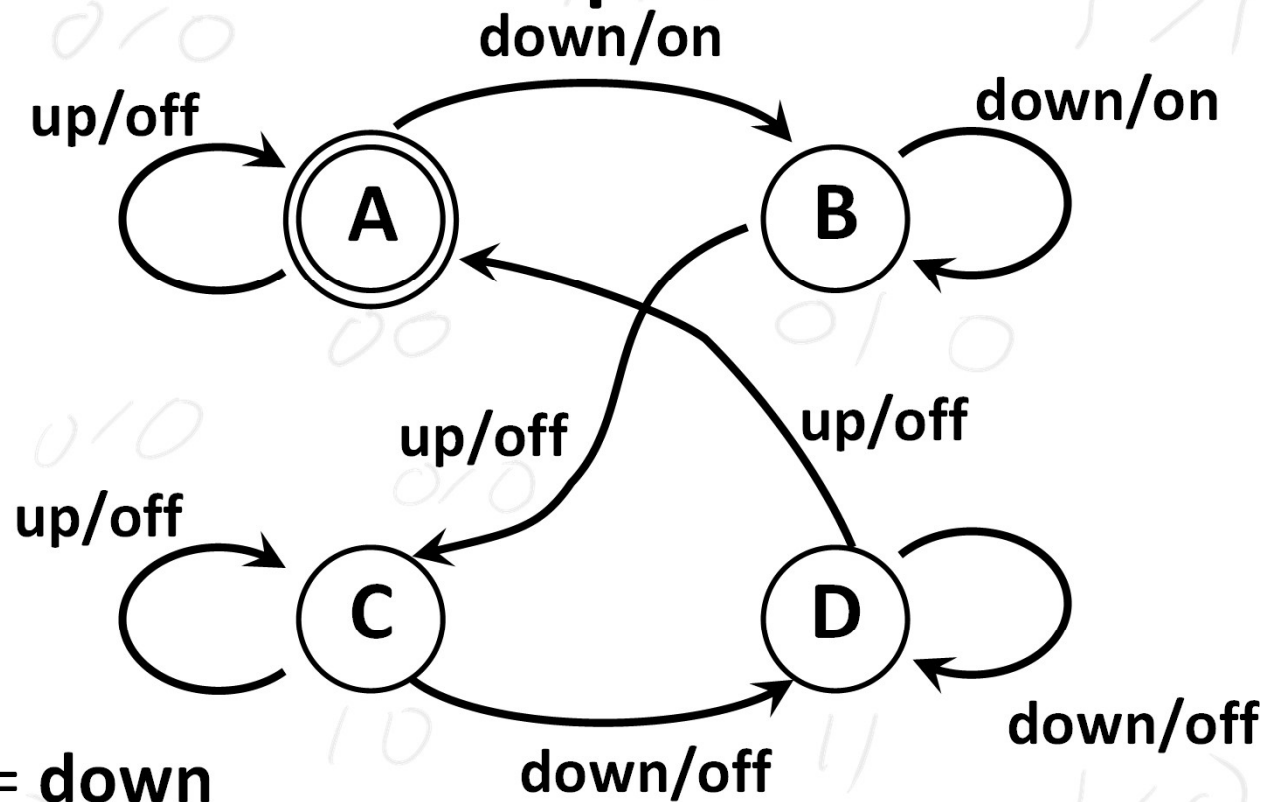
 


Input: = **up** or = **down**

Output: = **on** or = **off**

States: = **A**, = **B**, = **C**, or = **D**

FSM Example

  


Input: **0**=up or **1**=down

Output: **1**=on or **0**=off

States: **00**=A, **01**=B, **10**=C, or **11**=D

Mealy Machine


General Case: Mealy Machine

 

Outputs and next state depend on both current state and input



Moore Machine

Special Case: Moore Machine

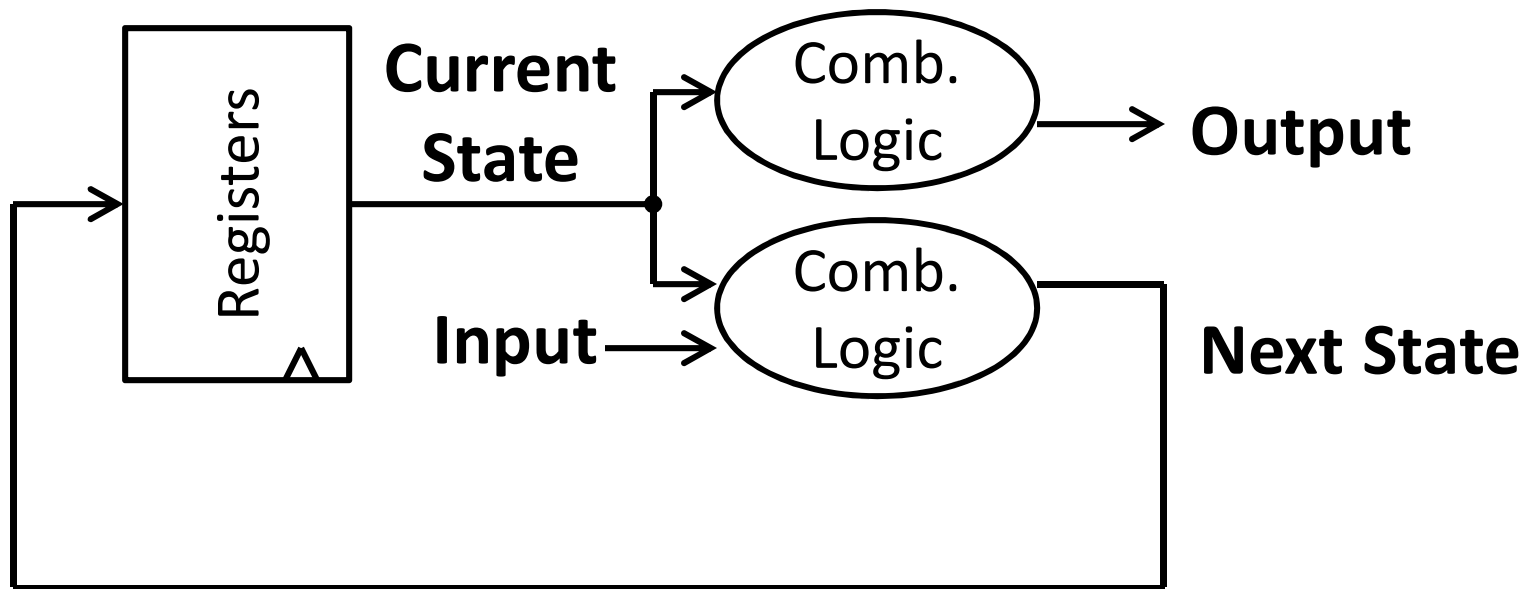

Outputs depend only on current state

Moore Machine FSM Example

 
 


Input: **up** or **down**

Output: **on** or **off**

States: **A**, **B**, **C**, or **D**

Mealy Machine FSM Example

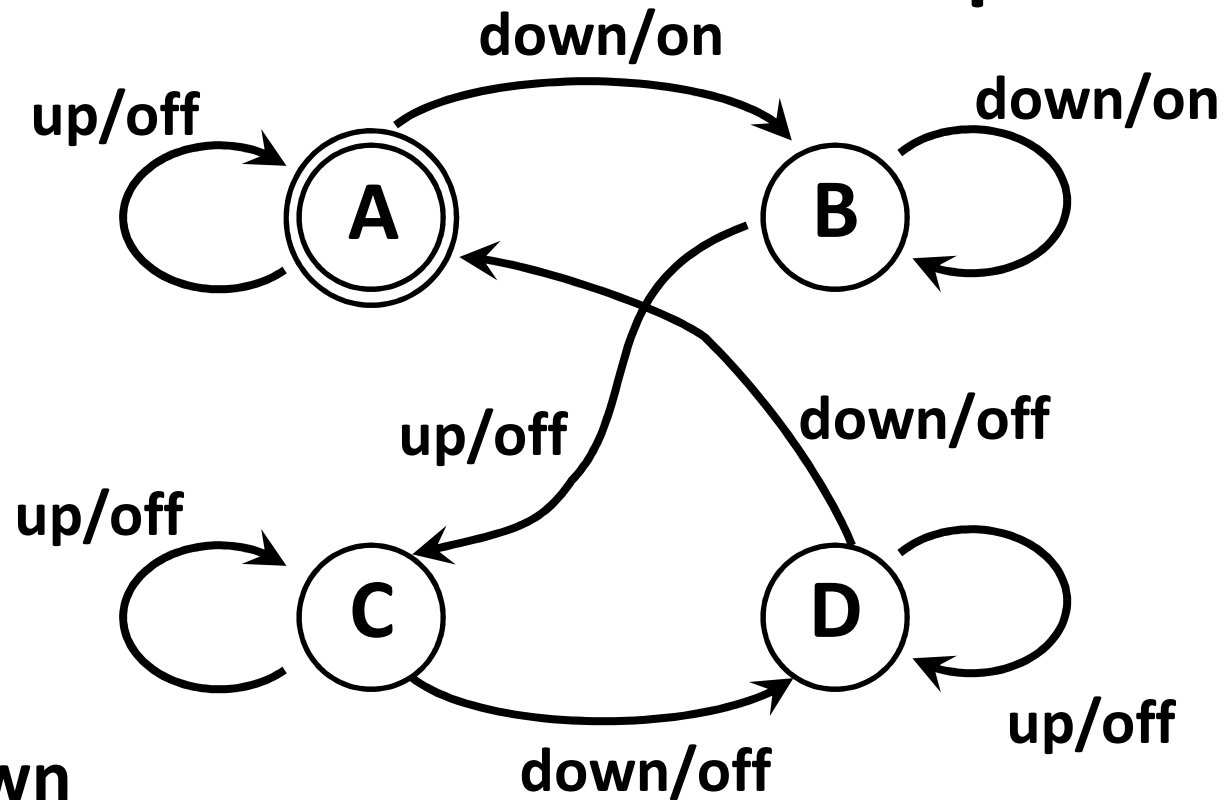 

Input: **up** or **down**


Output: **on** or **off**

States: **A**, **B**, **C**, or **D**

Activity#2: Create a Logic Circuit for a Serial Adder

Add two infinite input bit streams

 - streams are sent with least-significant-bit (lsb) first




Activity#2: Create a Logic Circuit for a Serial Adder

Add two infinite input bit streams

- streams are sent with least-significant-bit (lsb) first

Carry-out

 


Activity#2: Create a Logic Circuit for a Serial Adder

Add two infinite input bit streams

- streams are sent with least-significant-bit (lsb) first

Carry-*in*

 


Activity#2: Create a Logic Circuit for a Serial Adder

Add two infinite input bit streams

- streams are sent with least-significant-bit (lsb) first


Carry-**out**

 

iClicker Question

Add two infinite input bit streams

 - streams are sent with least-significant-bit (lsb) first




How many states are needed to represent FSM

- a) 0
- b) 1
- c) 2
- d) 3
- e) 4

Strategy for Building an FSM

- (1) Draw a state diagram (e.g. Mealy Machine)
- (2) Write output and next-state tables
- (3) Encode states, inputs, and outputs as bits
- (4) Determine logic equations for next state and outputs
- (5) Draw the Circuit

FSM: State Diagram

 


2 states ____ and ____

Inputs: ____ and ____

Output: ____

FSM: State Diagram

 



Two states: S0 (no carry in), S1 (carry in)

Inputs: a and b

Output: z

- z is the sum of inputs a, b, and carry-in (one bit at a time)
- A carry-out *is* the next carry-in state.
- .

FSM: State Diagram

  



Two states: S0 (no carry in), S1 (carry in)

Inputs: a and b

Output: z

- z is the sum of inputs a, b, and carry-in (one bit at a time)
- A carry-out *is* the next carry-in state.
- Arcs labeled with input bits a and b, and output z

FSM: State Diagram

  


Two states: S0 (no carry in), S1 (carry in)

Inputs: a and b

Output: z

- z is the sum of inputs a, b, and carry-in (one bit at a time)
- A carry-out *is* the next carry-in state.
- Arcs labeled with input bits a and b, and output z (Mealy Machine)


iClicker Question

 

Is this a Moore or Mealy Machine?

- a) Moore
- b) Mealy
- c) Cannot be determined

iClicker Question

 


Is this a Moore or Mealy Machine?

a) Moore

b) Mealy

c) Cannot be determined


Serial Adder: State Table

 

a	b	Current state	z	Next state

(2) Write down all input and state combinations


Serial Adder: State Table

 

a	b	Current state	z	Next state
0	0	S0	0	S0
0	1	S0	1	S0
1	0	S0	1	S0
1	1	S0	0	S1
0	0	S1	1	S0
0	1	S1	0	S1
1	0	S1	0	S1
1	1	S1	1	S1

(2) Write down all input and state combinations

Serial Adder: State Assignment

 


a	b	s	z	s'
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

(3) Encode states, inputs, and outputs as bits

Two states, so 1-bit is sufficient

- A single flip-flop will encode the state

Serial Adder: Circuit

 

a	b	s	z	s'
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1


(4) Determine logic equations for next state and outputs

Combinational Logic Equations

$$z = \bar{a}b\bar{s} + a\bar{b}\bar{s} + \bar{a}bs + abs$$

$$s' = ab\bar{s} + \bar{a}bs + a\bar{b}s + abs$$

Serial Adder: Circuit

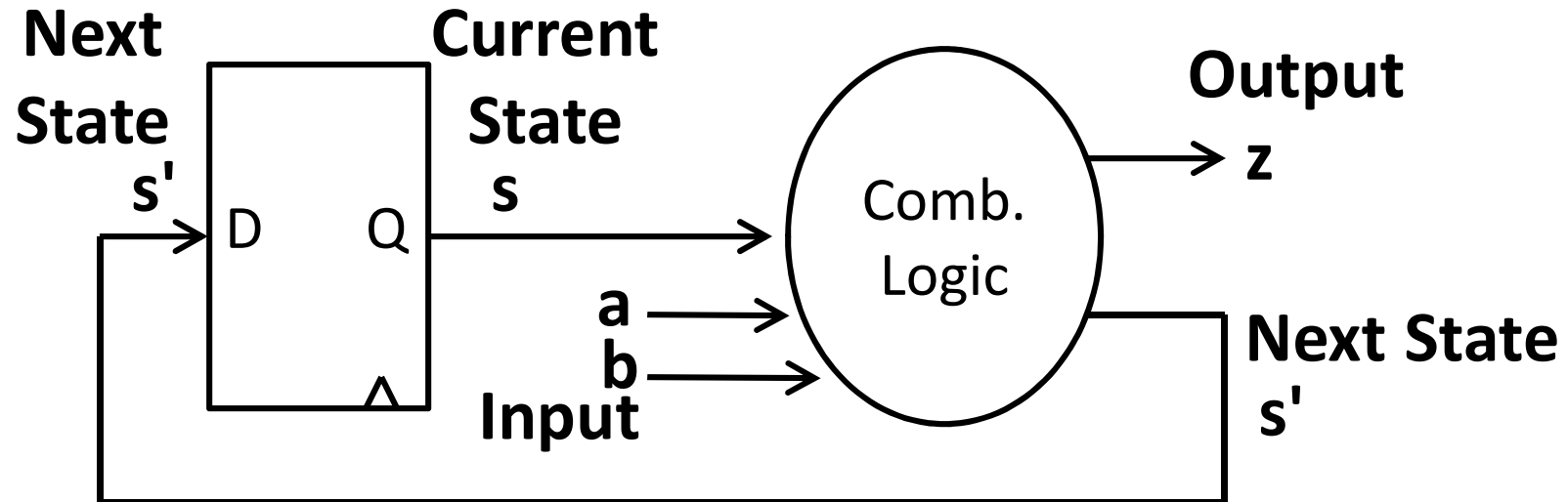

a	b	s	z	s'
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1


(4) Determine logic equations for next state and outputs

Combinational Logic Equations

$$z = \bar{a}b\bar{s} + a\bar{b}\bar{s} + \bar{a}bs + abs$$

$$s' = ab\bar{s} + \bar{a}bs + a\bar{b}s + abs$$

Sequential Logic Circuits

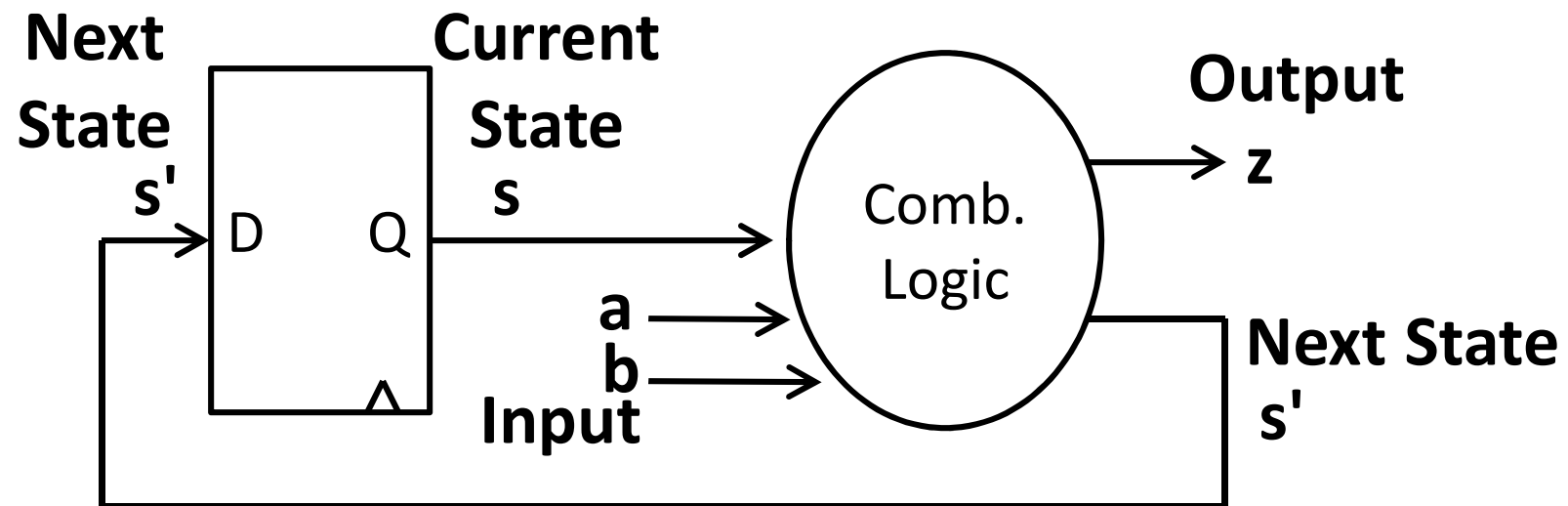

$$z = \bar{a}b\bar{s} + a\bar{b}\bar{s} + \bar{a}bs + abs$$

$$s' = ab\bar{s} + \bar{a}bs + a\bar{b}s + abs$$

Strategy:

- (1) Draw a state diagram (e.g. Mealy Machine)
- (2) Write output and next-state tables
- (3) Encode states, inputs, and outputs as bits
- (4) Determine logic equations for next state and outputs

Which statement(s) is true

- (A) In a Moore Machine output depends on both current state and input
- (B) In a Mealy Machine output depends on both current state and input
- (C) In a Mealy Machine output depends on next state and input
- (D) All the above are true
- (E) None are true

Which statement(s) is true

(A) In a Moore Machine output depends on both current state and input

(B) In a Mealy Machine output depends on both current state and input


(C) In a Mealy Machine output depends on next state and input

(D) All the above are true

(E) None are true

Mealy Machine


General Case: Mealy Machine

 

Outputs and next state depend on both current state and input

Moore Machine

Special Case: Moore Machine

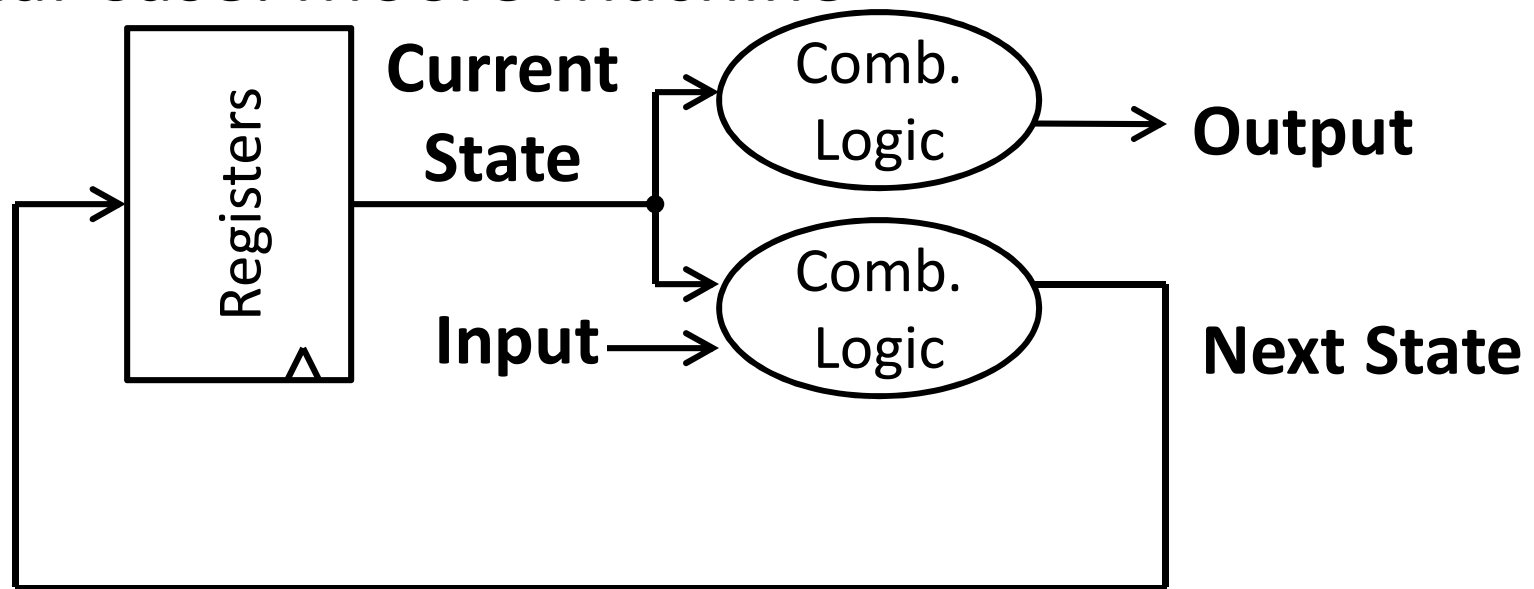

Outputs depend only on current state

Example: Digital Door Lock



Digital Door Lock

Inputs:

- keycodes from keypad
- clock


Outputs:

- “unlock” signal
- display how many keys pressed so far

Door Lock: Inputs

Assumptions:

 - signals are synchronized to clock
- Password is B-A-B




K	A	B	Meaning
0	0	0	∅ (no key)
1	1	0	'A' pressed
1	0	1	'B' pressed

Door Lock: Outputs

Assumptions:


- High pulse on U unlocks door

 

Strategy:


- (1) Draw a state diagram (e.g. Moore Machine)
- (2) Write output and next-state tables
- (3) Encode states, inputs, and outputs as bits
- (4) Determine logic equations for next state and outputs

Door Lock: Simplified State Diagram

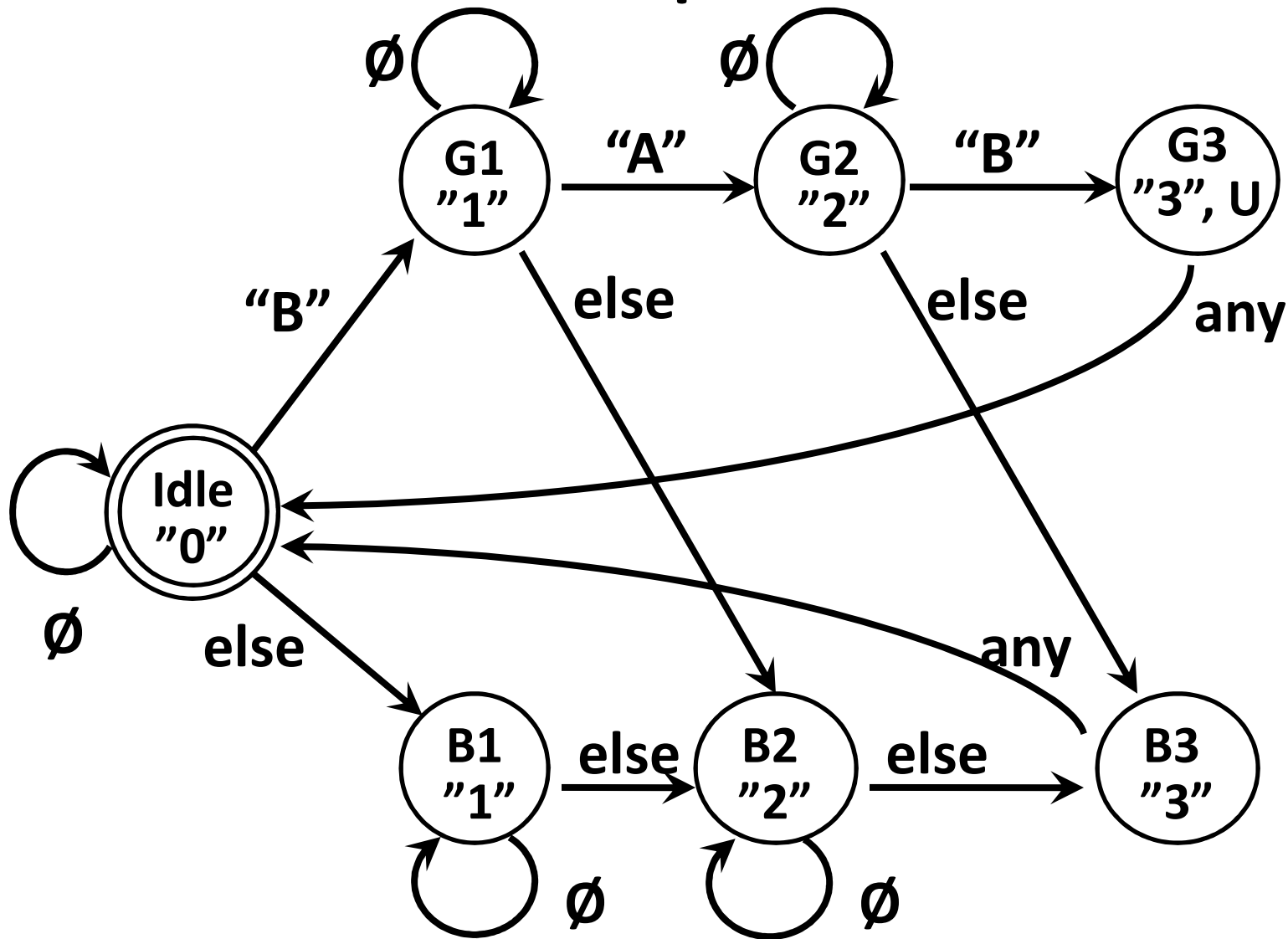


(1) Draw a state diagram (e.g. Moore Machine)

Door Lock: Simplified State Diagram

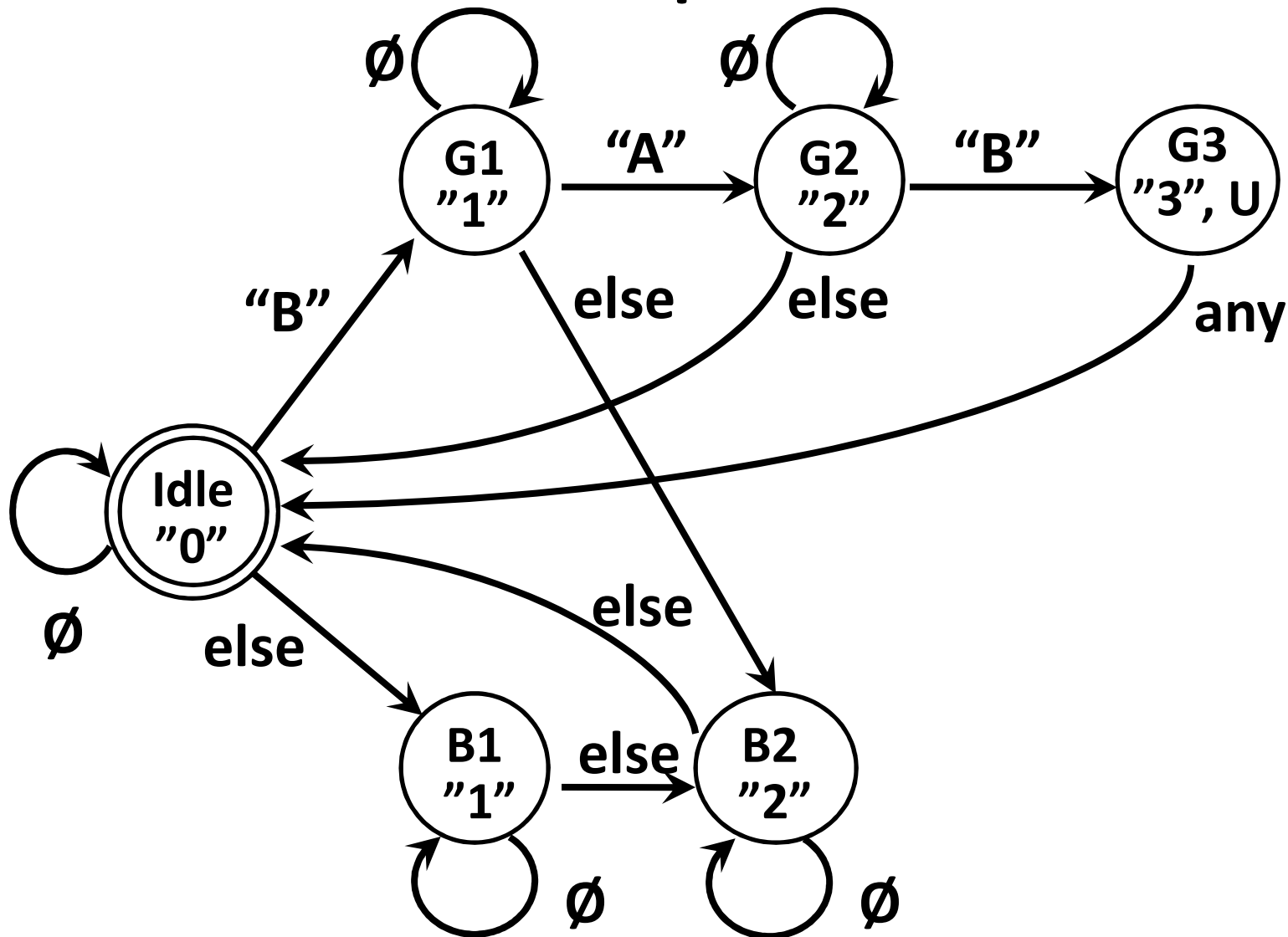


(1) Draw a state diagram (e.g. Moore Machine)

Door Lock: Simplified State Diagram

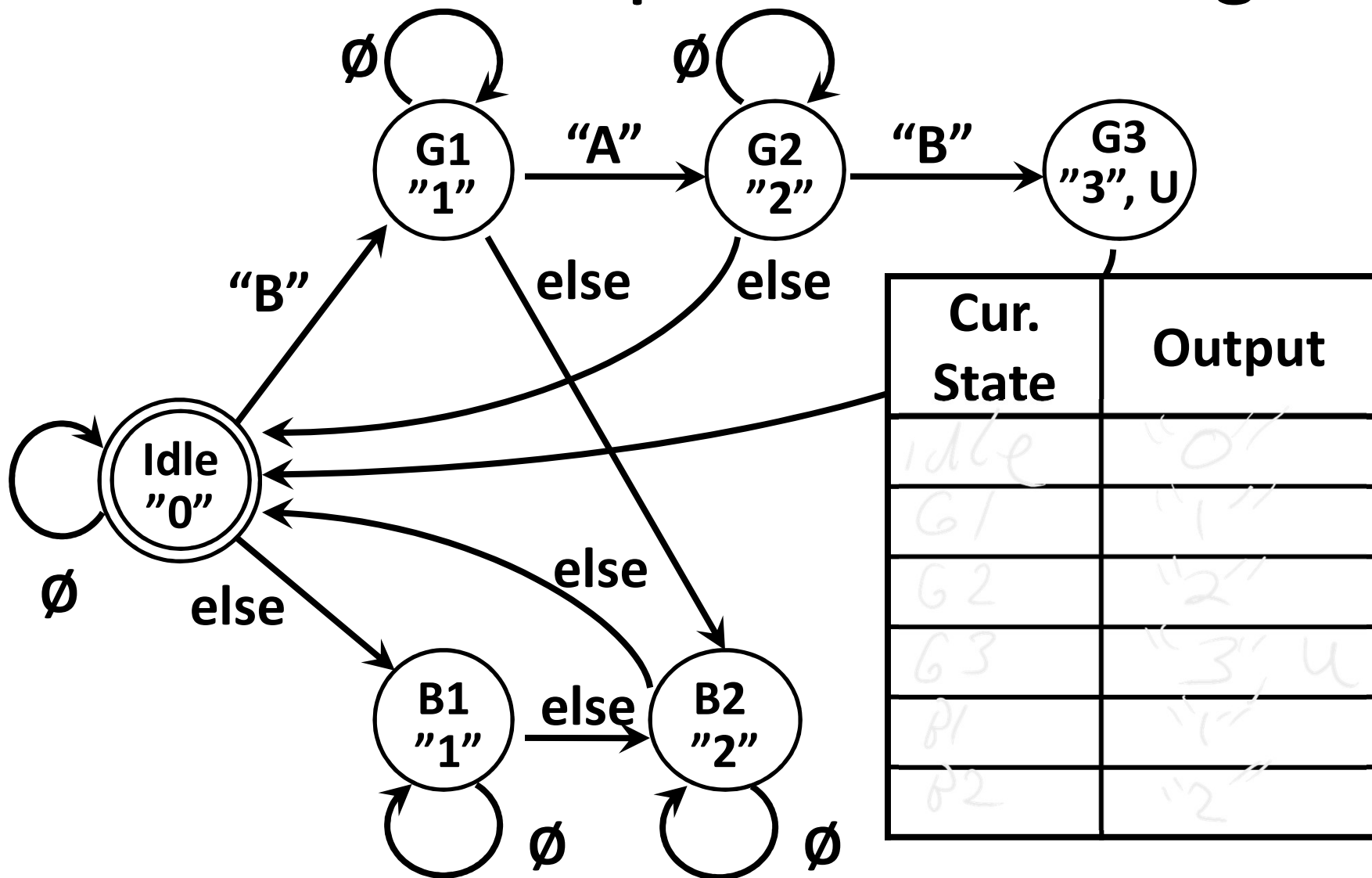


(2) Write output and next-state tables

Door Lock: Simplified State Diagram

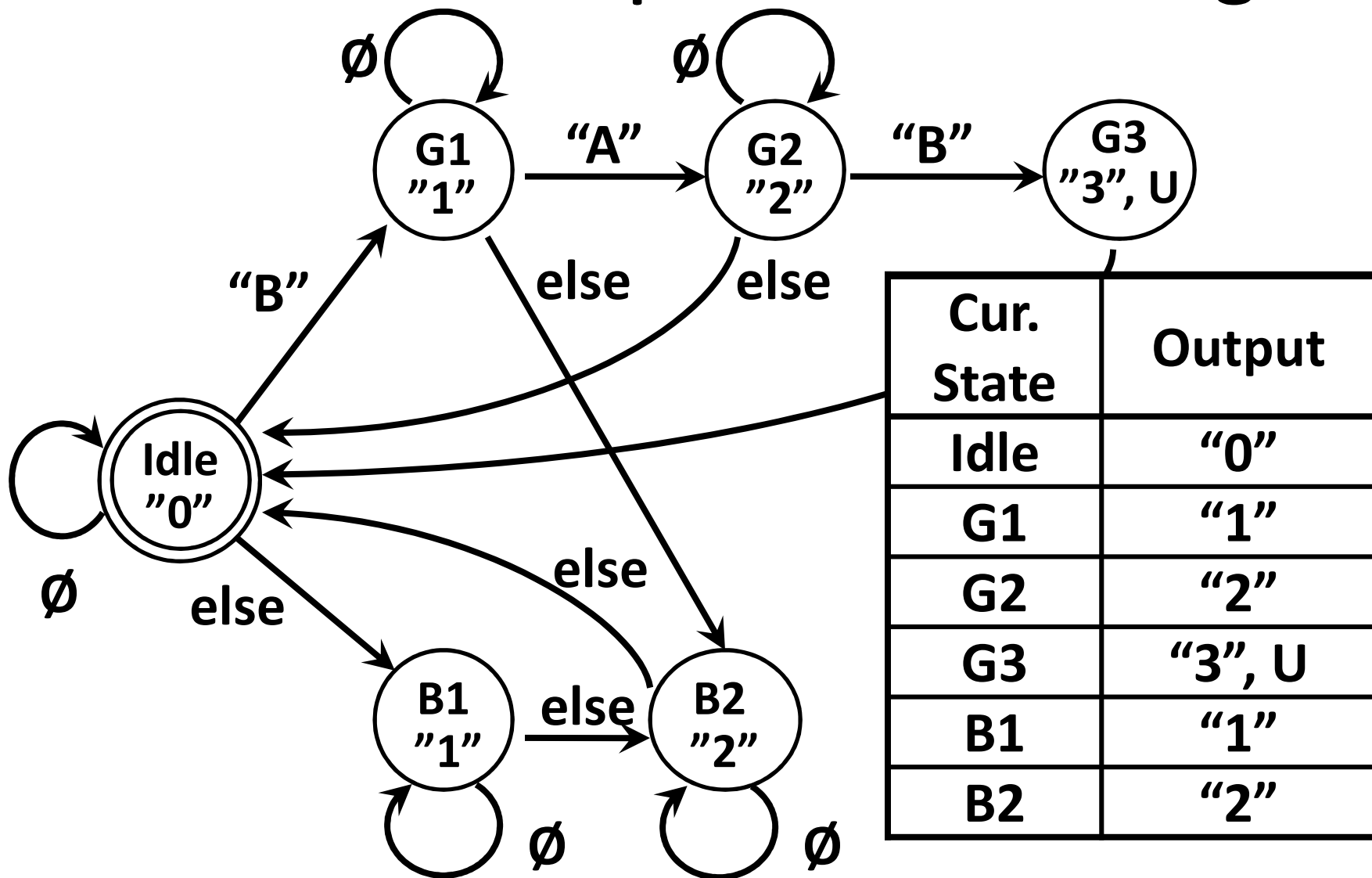


(2) Write output and next-state tables

Door Lock: Simplified State Diagram

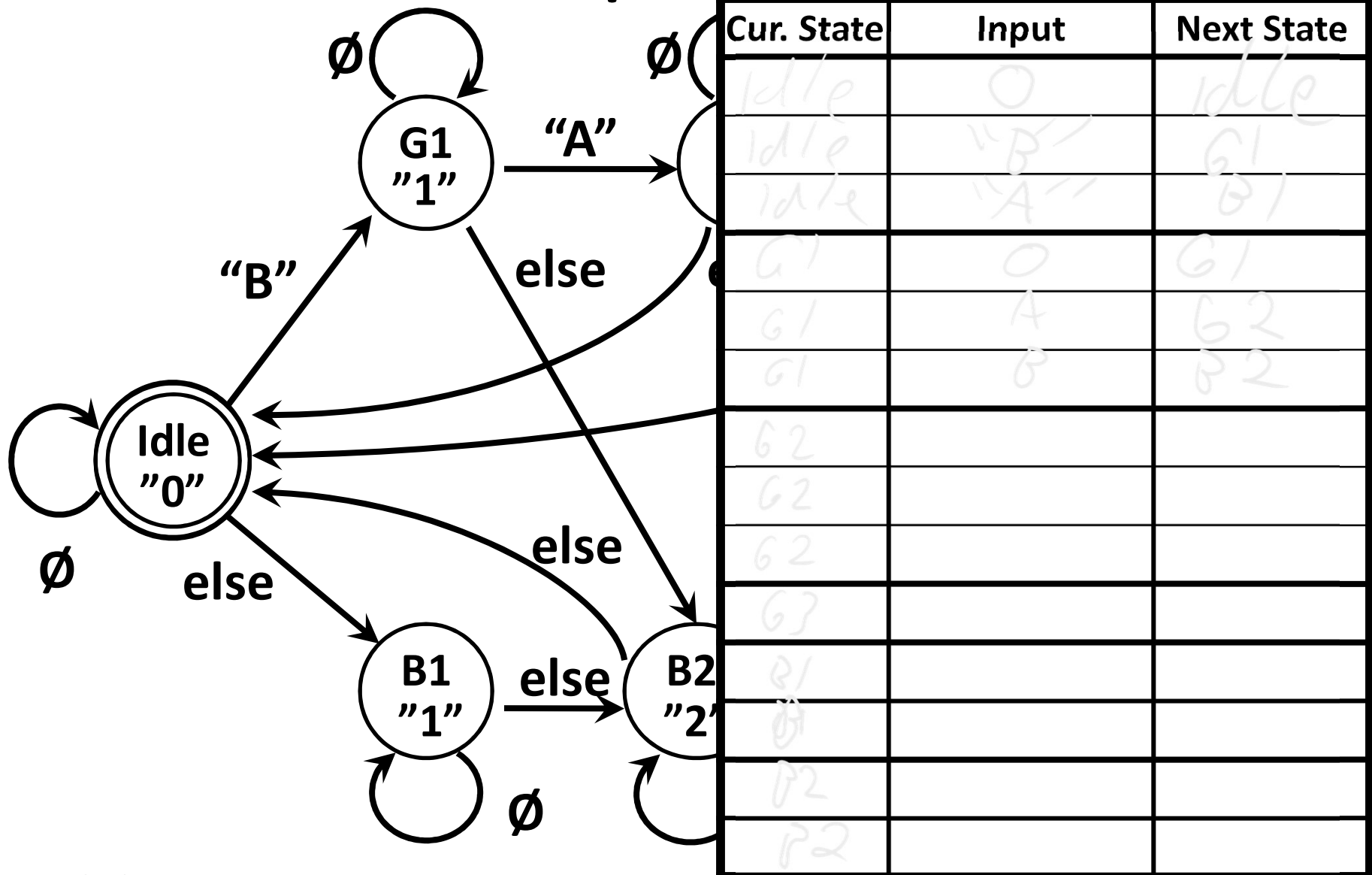

(2) Write output and next-state tables

Door Lock: Simplified State Diagram

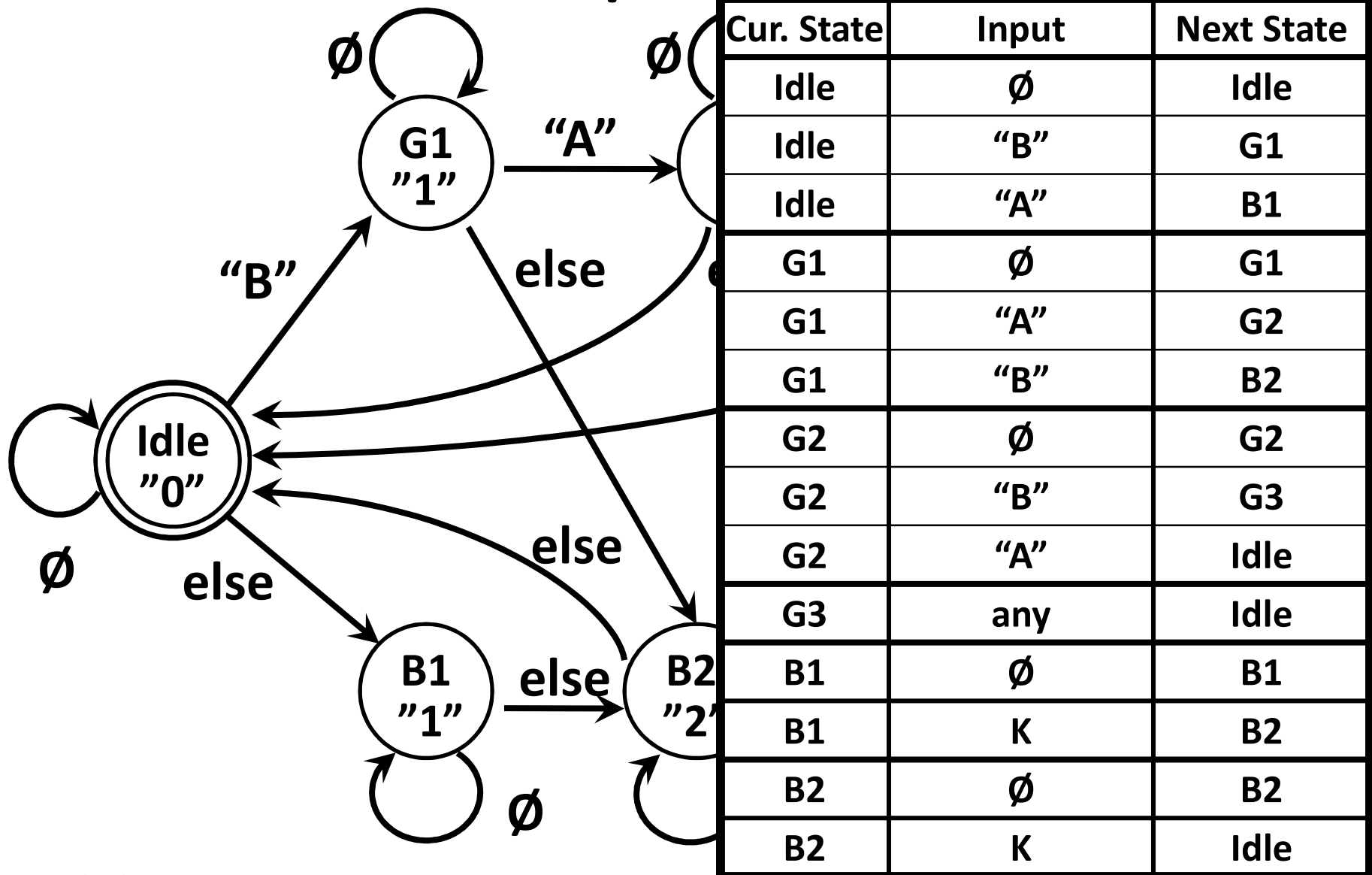

(2) Write output and next-state tables

State Table Encoding

S ₂	S ₁	S ₀	D ₃	D ₂	D ₁	D ₀	U
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	0	0	1	1	1
1	0	0	0	0	0	1	0
1	0	1	0	0	1	0	0


D₃ [

State	S ₂	S ₁	S ₀
Idle	0	0	0
G1	0	0	1
G2	0	1	0
G3	0	1	1
B1	1	0	0
B2	1	0	1

S ₂	S ₁	S ₀	K	A	B	S' ₂	S' ₁	S' ₀
0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0	1
0	0	0	1	1	0	1	0	0
0	0	1	0	0	0	0	0	1
0	0	1	1	1	0	0	1	0
0	0	1	1	0	1	1	0	1
0	1	0	0	0	0	0	1	0
0	1	0	1	0	1	0	1	1
0	1	0	1	1	0	0	0	0
0	1	1	x	x	x	0	0	0
1	0	0	0	0	0	1	0	0
1	0	0	1	x	x	1	0	1
1	0	1	0	0	0	1	0	1
1	0	1	1	x	x	0	0	0

(ts, and outputs as bits

Door Lock: Implementation

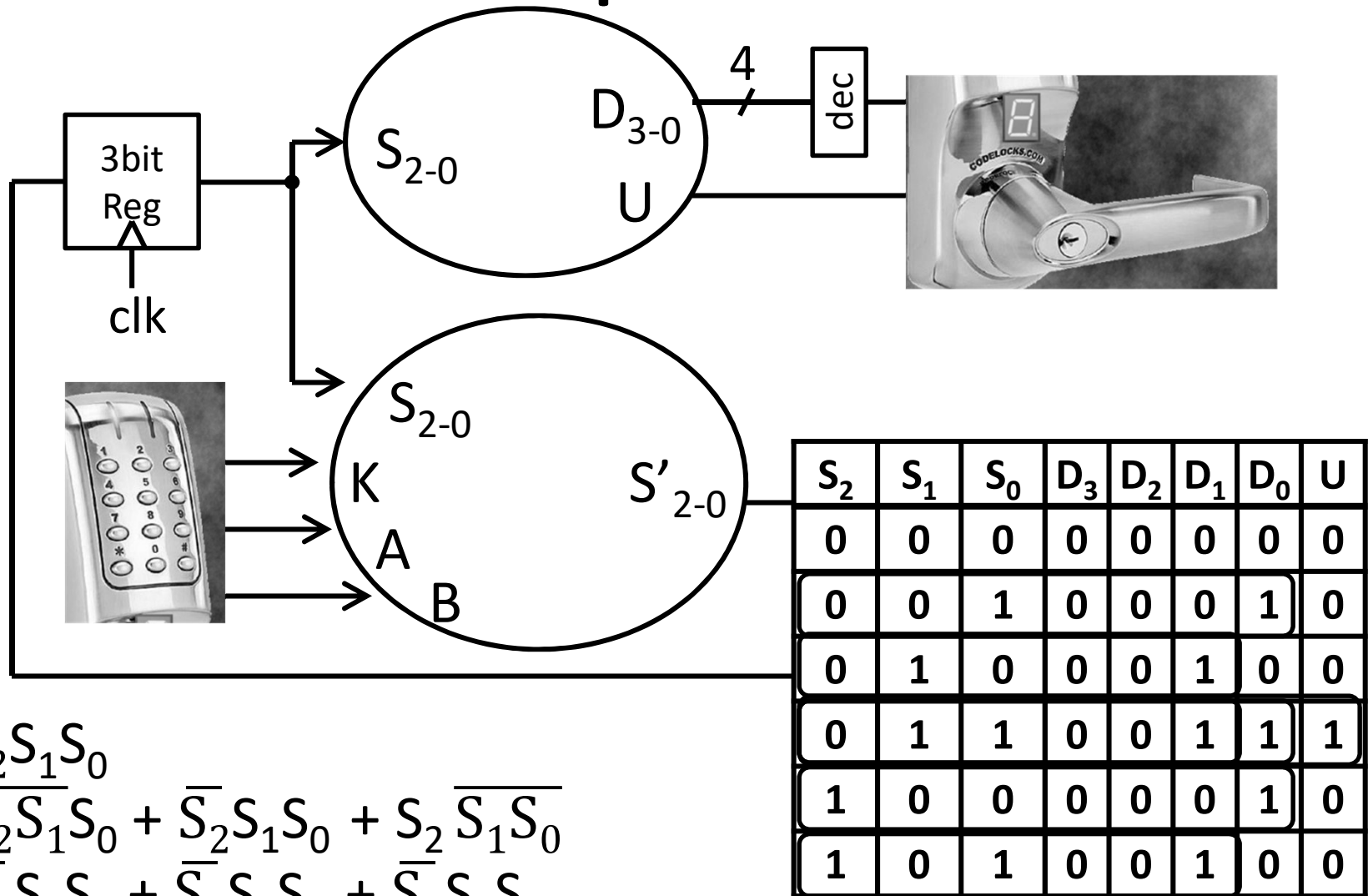


$$U = \bar{S}_2 S_1 S_0$$

$$D_0 = \bar{S}_2 \bar{S}_1 S_0 + \bar{S}_2 S_1 \bar{S}_0 + S_2 \bar{S}_1 \bar{S}_0$$

$$D_1 = \bar{S}_2 \bar{S}_1 S_0 + \bar{S}_2 S_1 S_0 + \bar{S}_2 S_1 \bar{S}_0$$

(4) Determine logic equations for next state and outputs

Door Lock: Implementation

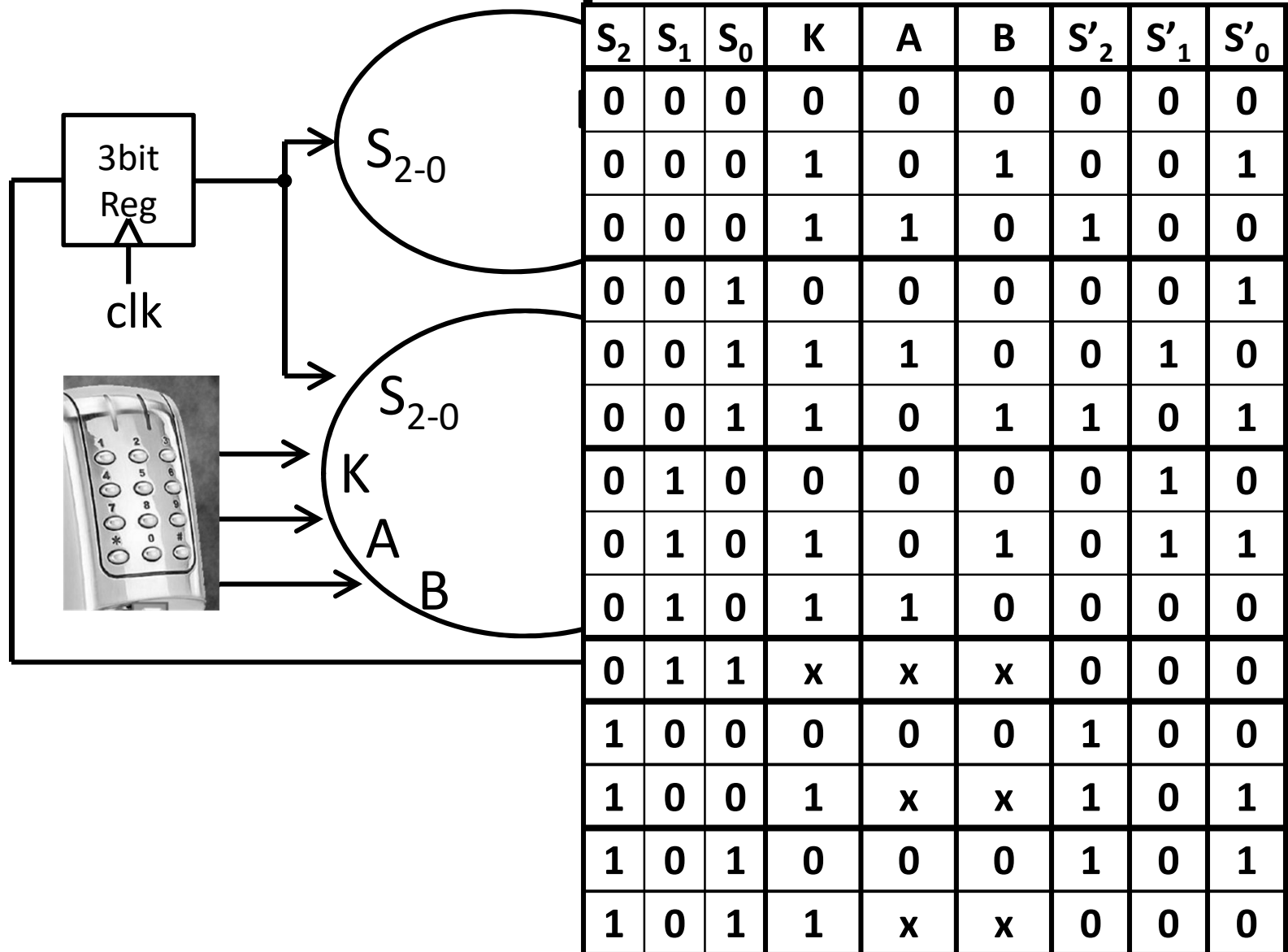


$$S'_0 = ?$$

$$S'_1 = ?$$

$$S'_2 = \overline{S_2} \overline{S_1} \overline{S_0} K A \overline{B} + \overline{S_2} \overline{S_1} \overline{S_0} K \overline{A} B + S_2 \overline{S_1} \overline{S_0} K A \overline{B} + \overline{S_2} S_1 \overline{S_0} K + S_2 \overline{S_1} \overline{S_0} \overline{K} A \overline{B}$$


Door Lock: Implementation

 

Strategy:

- (1) Draw a state diagram (e.g. Moore Machine)
- (2) Write output and next-state tables
- (3) Encode states, inputs, and outputs as bits
- (4) Determine logic equations for next state and outputs

Door Lock: Implementation

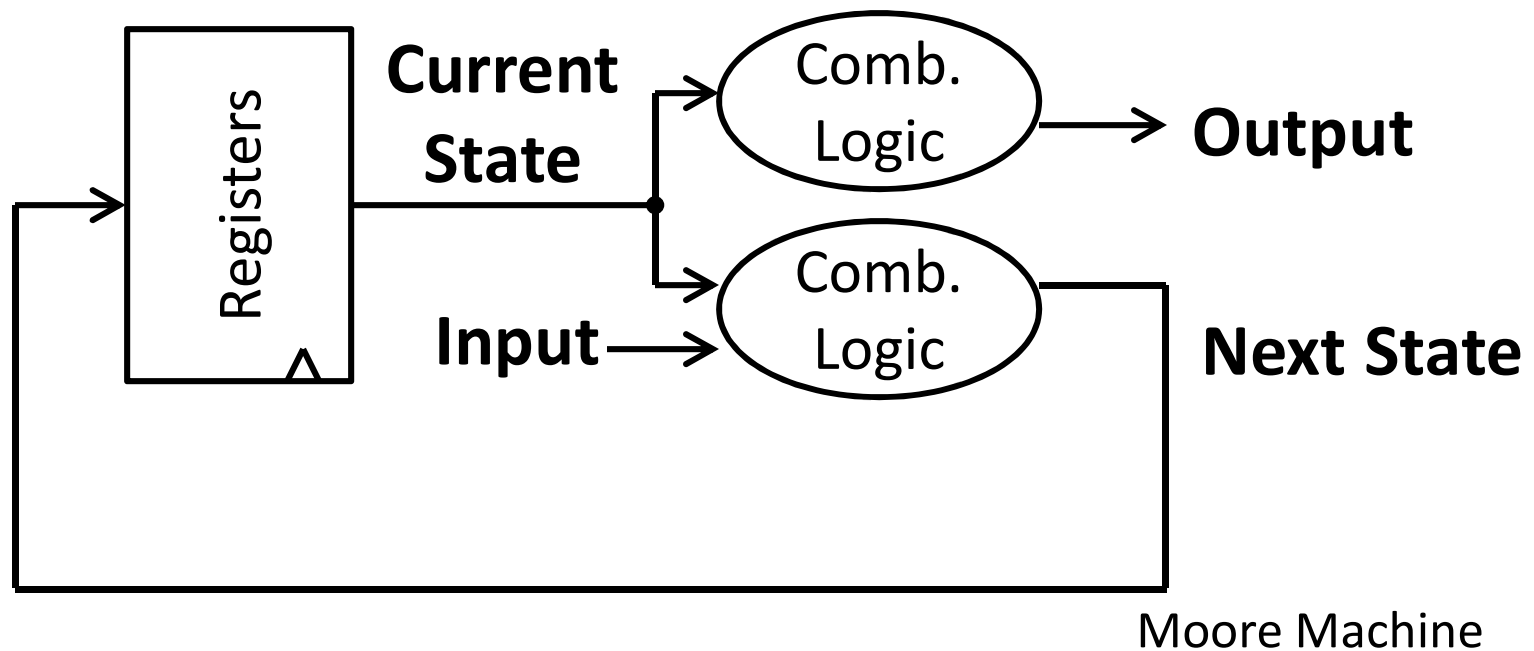

Strategy:

- (1) Draw a state diagram (e.g. Moore Machine)
- (2) Write output and next-state tables
- (3) Encode states, inputs, and outputs as bits
- (4) Determine logic equations for next state and outputs

Summary

We can now build interesting devices with sensors

- Using combinational logic

We can also store data values

- Stateful circuit elements (D Flip Flops, Registers, ...)
- State Machines or Ad-Hoc Circuits