


State

Prof. Hakim Weatherspoon

CS 3410

Computer Science

Cornell University

 

Cornell CIS
COMPUTING AND INFORMATION SCIENCE

[Weatherspoon, Bala, Bracy, and Sizer]


Goals for Today

State

- How do we store *one* bit?
- Attempts at storing (and changing) one bit
 - Set-Reset Latch
 - D Latch
 - D Flip-Flops
 - Master-Slave Flip-Flops
- Register: storing more than one bit, N-bits


Basic Building Blocks

- Decoders and Encoders

 


Goal

How do we store store ***one*** bit?

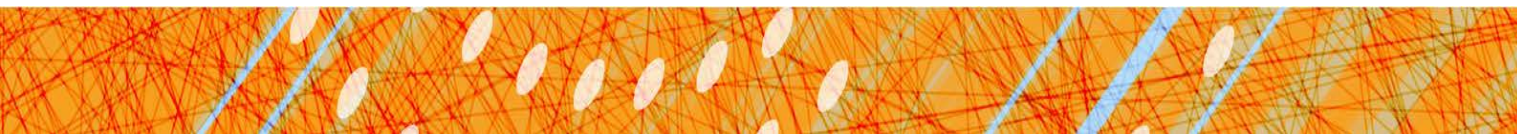


First Attempt: Unstable Devices

 


Second Attempt: Bistable Devices

- Stable and unstable equilibria?

 


A Simple Device

Third Attempt: Set-Reset Latch

 

Third Attempt: Set-Reset Latch

 



S	R	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		

Set-Reset (S-R) Latch

Stores a value Q and its complement

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

Third Attempt: Set-Reset Latch

  


S	R	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	0	1
1	0	1	0
1	1		

Set-Reset (S-R) Latch

Stores a value Q and its complement


Takeaway

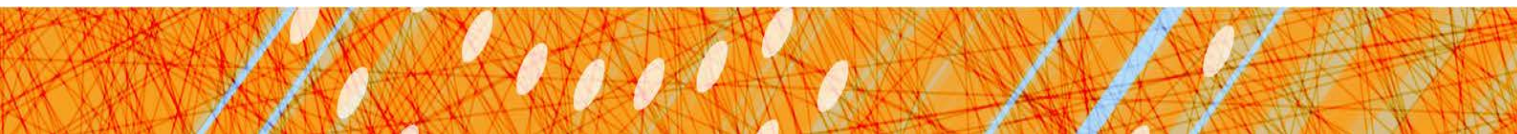Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But, SR Latch has a forbidden state.





Next Goal

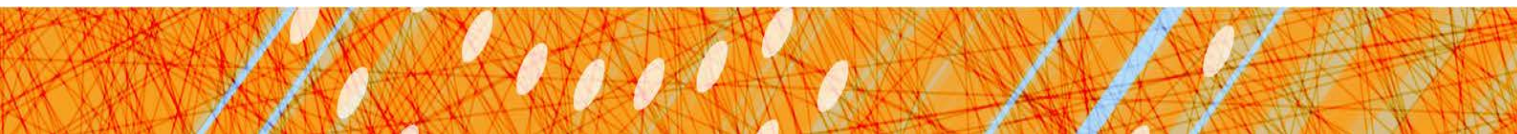How do we avoid the forbidden state of S-R Latch?



Fourth Attempt: (Unclocked) D Latch

  

Fill in the truth table?


D	Q	\bar{Q}
0		
1		

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

Takeaway


Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But, SR Latch has a forbidden state.

 (Unclocked) D Latch can store and change a bit like an SR Latch while avoiding the forbidden state.



Next Goal

 
How do we coordinate state changes to a D Latch?



Aside: Clocks

Clock helps coordinate state changes

 - Usually generated by an oscillating crystal
- Fixed period
- Frequency = $1/\text{period}$



Clock Disciplines

Level sensitive

- State changes when clock is high (or low)



Edge triggered

- State changes at clock edge

positive edge-triggered




negative edge-triggered



Clock Methodology

Clock Methodology

- Negative edge, synchronous

 


Edge-Triggered → signals must be stable near falling edge


“near” = before and after

t_{setup} t_{hold}

Round 2: D Latch (1)

 

 - Inverter prevents SR Latch from entering 1,1 state




	D	Q	\bar{Q}
0	0		
1	1		

Reset

Set

Round 2: D Latch (1)

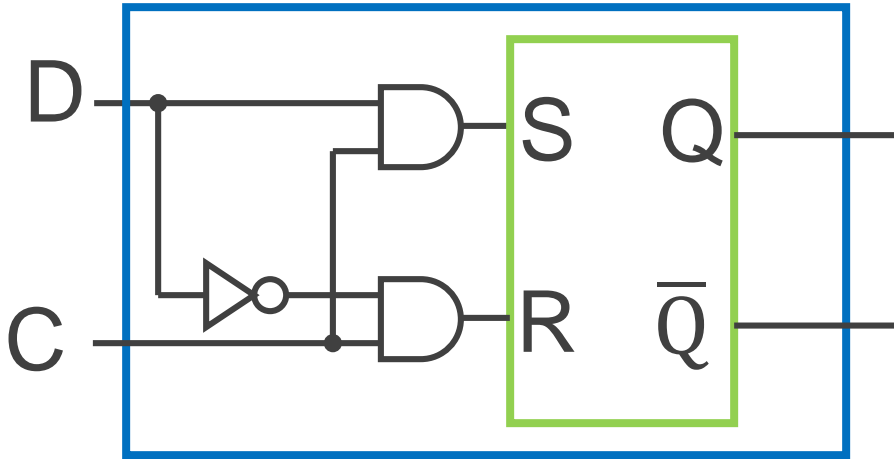

- Level sensitive
- Inverter prevents SR Latch from entering 1,1 state
- C enables changes

C = 1, D Latch *transparent*:
set/reset (according to D)


C = 0, D Latch *opaque*:
keep state (ignore D)

C	D	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		


No
Change

Reset

Set

 

Round 2: D Latch (1)

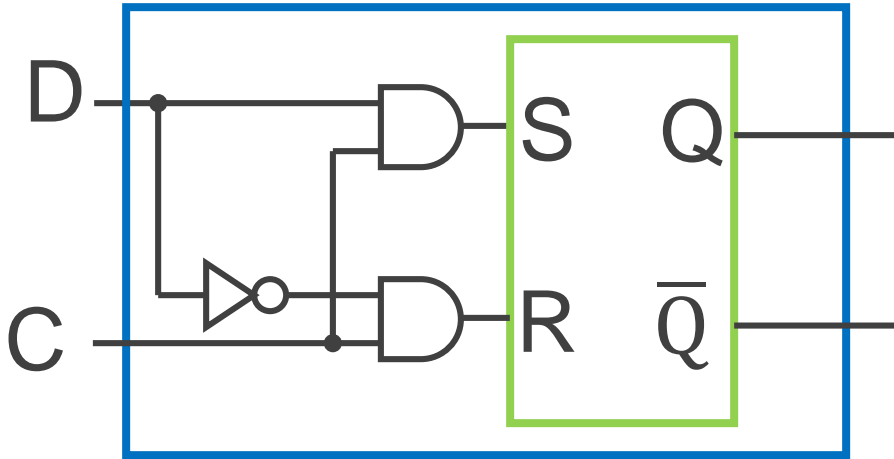


- Level sensitive
- Inverter prevents SR Latch from entering 1,1 state
- C enables changes

C = 1, D Latch *transparent*: set/reset (according to D)

C = 0, D Latch *opaque*: keep state (ignore D)

S	R	Q	\bar{Q}	
0	0	Q	\bar{Q}	hold
0	1	0	1	reset
1	0	1	0	set
1	1	forbidden		

 

C	D	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		


No
Change

Reset

Set

Round 2: D Latch(1)

Level Sensitive D Latch

 


Clock high:

set/reset (according to D)


Clock low:

keep state (ignore D)

 

clk	D	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		

Round 3: D Flip-Flop

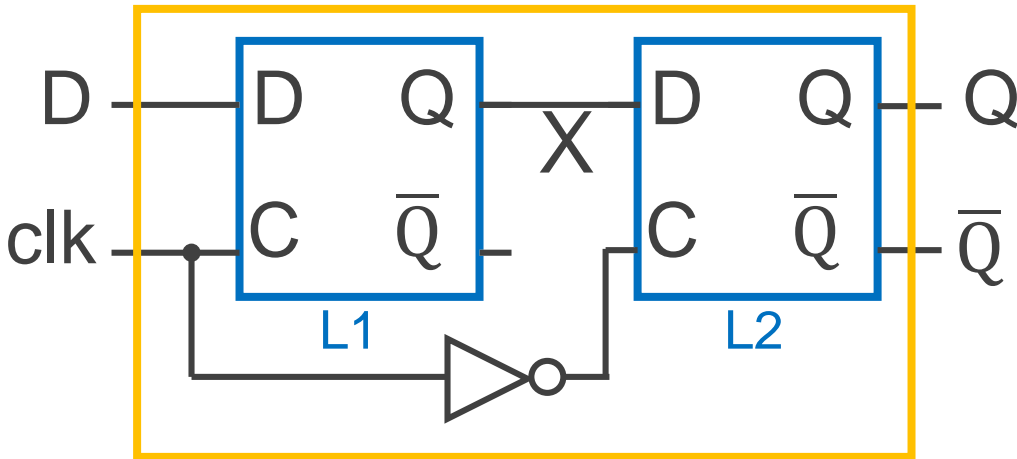


- Edge-Triggered
- Data captured when clock high
- Output changes only on falling edges

Round 3: D Flip-Flop


Clock = 1: L1 *transparent*
L2 *opaque*

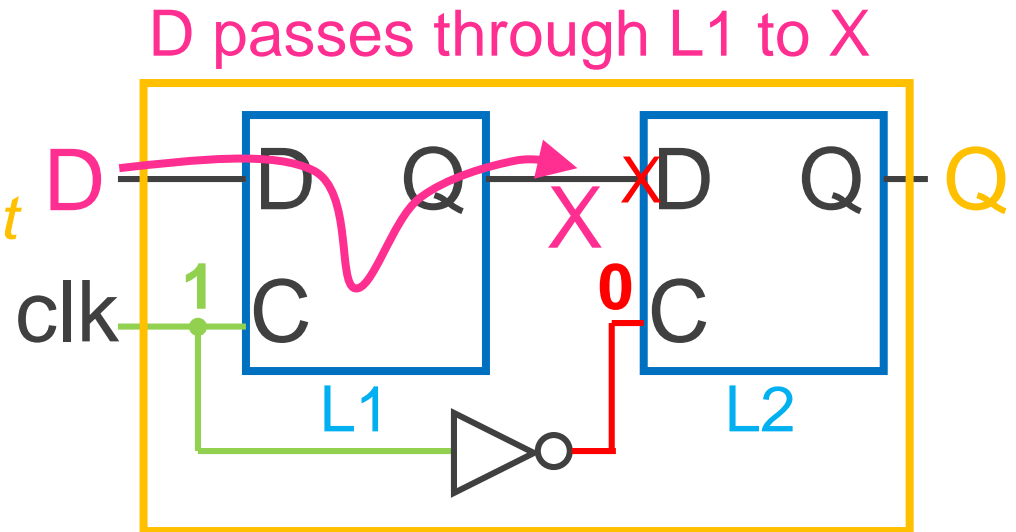When *CLK* rises ($0 \rightarrow 1$),
now *X* can change,
Q does not change



Clock = 0: L1 *opaque*
L2 *transparent*

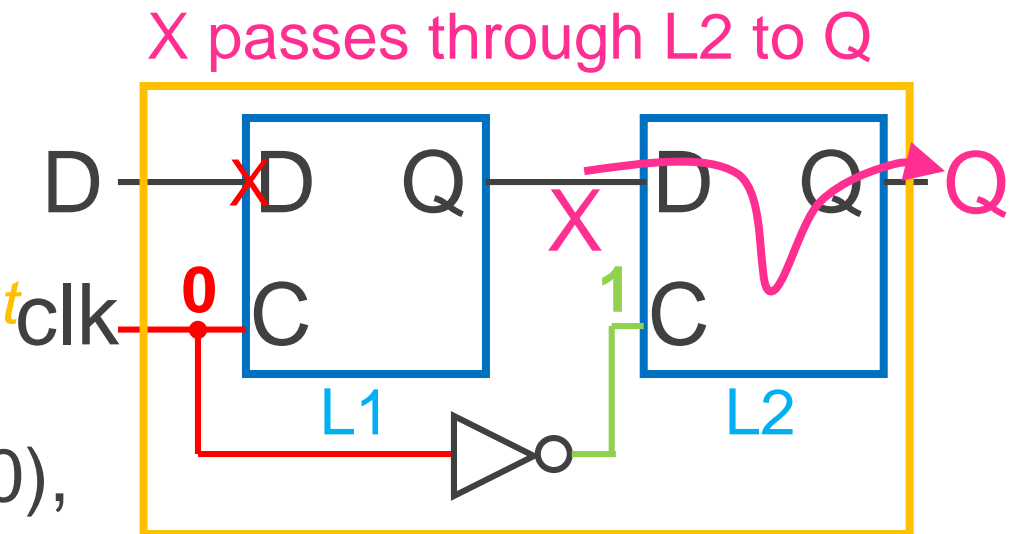When **CLK falls** ($1 \rightarrow 0$),
Q gets *X*, *X* cannot change



Takeaway


Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But, SR Latch has a forbidden state.

(Unclocked) D Latch can store and change a bit like an SR Latch while avoiding a forbidden state.


An Edge-Triggered D Flip-Flop (aka Master-Slave D Flip-Flop) stores one bit. The bit can be changed in a synchronized fashion on the edge of a clock signal.

Next Goal

 How do we store more than one bit, N bits?




Registers

 

Register

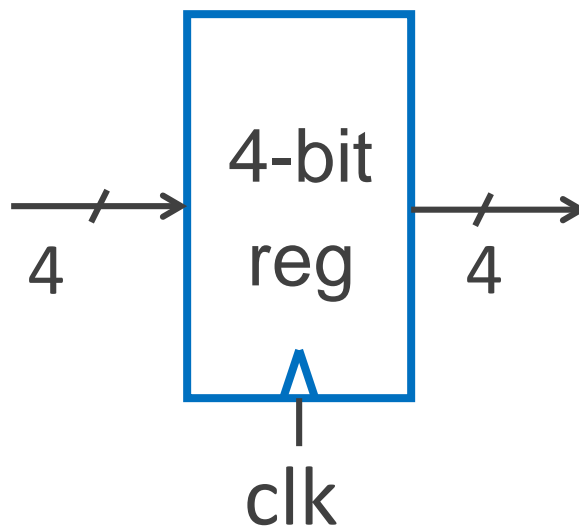- D flip-flops in parallel
- shared clock
- extra clocked inputs: write_enable, reset, ...




Takeaway

Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But, SR Latch has a forbidden state.


(Unclocked) D Latch can store and change a bit like an SR Latch while avoiding a forbidden state.

An Edge-Triggered D Flip-Flop (aka Master-Slave D Flip-Flop) stores one bit. The bit can be changed in a synchronized fashion on the edge of a clock signal.

 An N -bit **register** stores N -bits. It is created with N D-Flip-Flops in parallel along with a shared clock.



An Example: What will this circuit do?

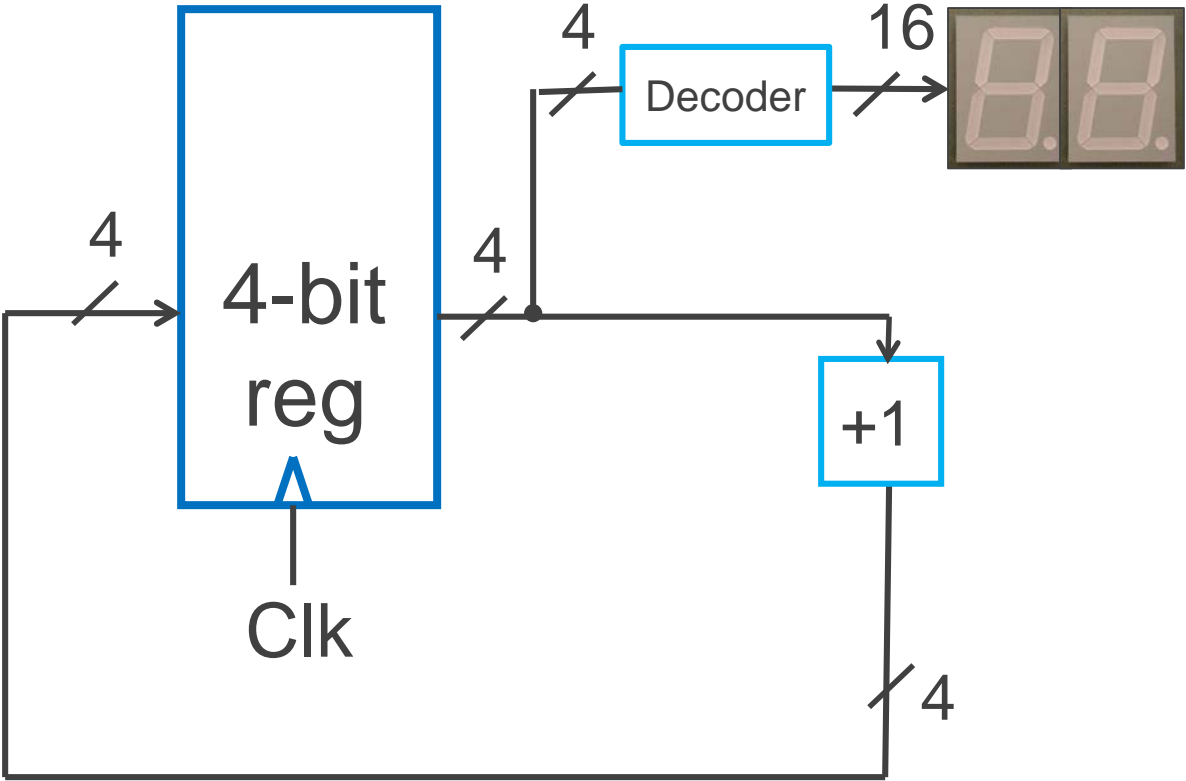


Decoder Example: 7-Segment LED

7-Segment LED

- photons emitted when electrons fall into holes



Decoder Example: 7-Segment LED Decoder

 

3 inputs


- encode 0 – 7 in binary

7 outputs




- one for each LED

7 Segment LED Decoder Implementation


b2	b1	b0	d6	d5	d4	d3	d2	d1	d0
0	0	0							
0	0	1							
0	1	0							
0	1	1							
1	0	0							
1	0	1							
1	1	0							
1	1	1							

 

Basic Building Blocks We have Seen

   

Encoders

 


e.g. Voting:

Can only vote for one out of N candidates, so N inputs.

But can encode vote efficiently with binary encoding.


Example Encoder Truth Table

 

A 3-bit
encoder
with 4 inputs
for simplicity

a	b	c	d				
0	0	0	0				
1	0	0	0				
0	1	0	0				
0	0	1	0				
0	0	0	1				




Basic Building Blocks Example: Voting

 

Ballots

The 3410 optical scan
vote reader
machine

Basic Building Blocks We have Seen

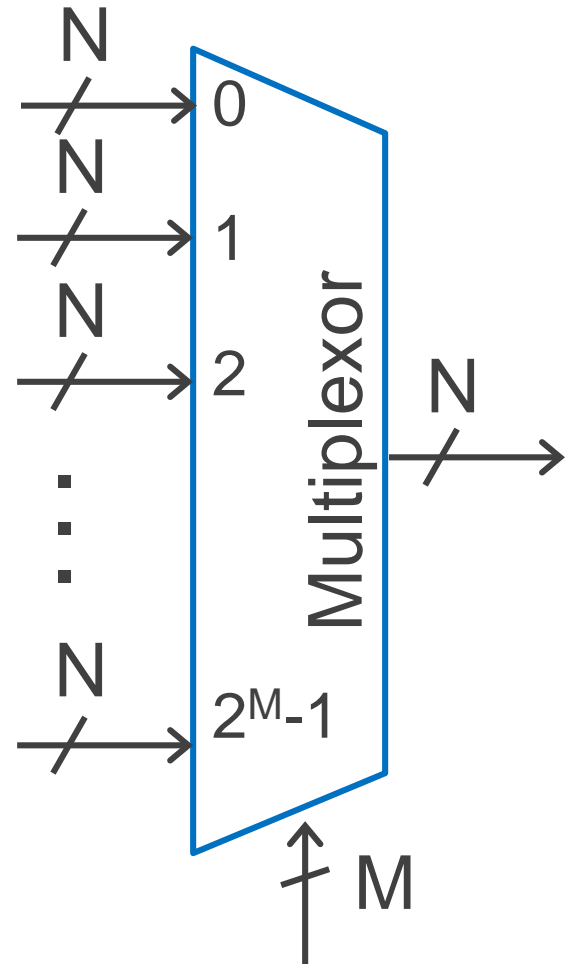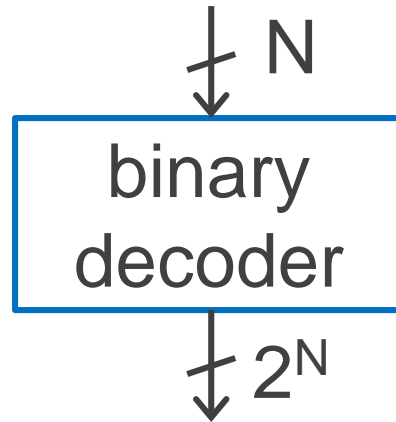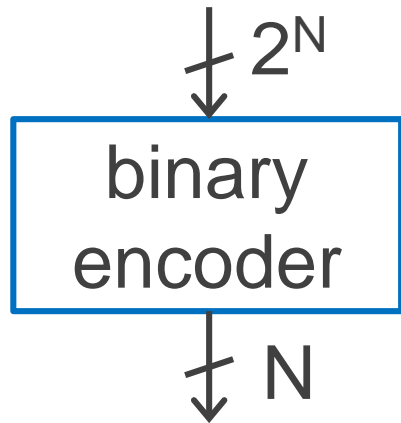


Recap

We can now build interesting devices with sensors

- Using combinational logic

We can also store data values (aka Sequential Logic)

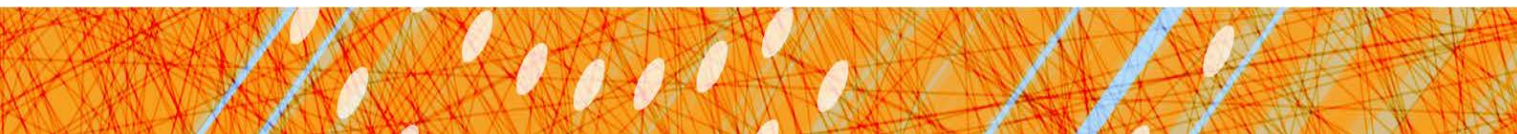- In state-holding elements
- Coupled with clocks



Summary

We can now build interesting devices with sensors

- Using combinational logic

We can also store data values

- Stateful circuit elements (D Flip Flops, Registers, ...)
- Clock to synchronize state changes

