


Finite State Machines

Hakim Weatherspoon

CS 3410

Computer Science

Cornell University

 


Cornell CIS
COMPUTING AND INFORMATION SCIENCE

[Weatherspoon, Bala, Bracy, McKee, and Sirer]

Stateful Components

Combinational logic

 - Output computed directly from inputs
- System has no internal state
- Nothing depends on the past!



Need:

- To record data
- To build **stateful** circuits
- A state-holding device

Sequential Logic & Finite State Machines

Goals for Today

- Finite State Machines (FSM)
 - How do we design logic circuits with state?
 - Types of FSMs: Mealy and Moore Machines
 - Examples: Serial Adder and a Digital Door Lock

Next Goal

- How do we design logic circuits with state?

Finite State Machines

Finite State Machines

An electronic machine which has

- external inputs
- externally visible outputs
- internal state

Output and next state depend on

- inputs
- current state

Abstract Model of FSM

Machine is

$$M = (S, I, O, \delta)$$

S : Finite set of states

I : Finite set of inputs


O : Finite set of outputs

δ : State transition function

Next state depends on present input *and* present state



Automata Model

Finite State Machine

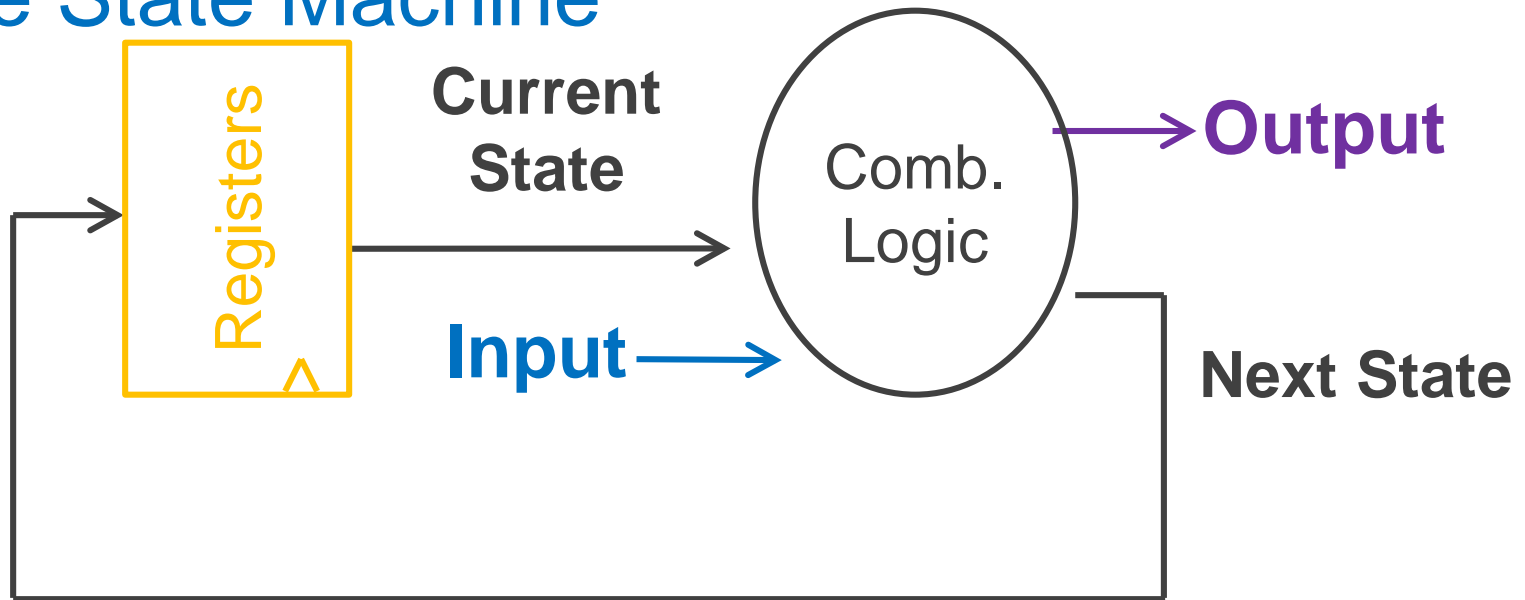

- inputs from external world
- outputs to external world
- internal state
- combinational logic

FSM Example

 
 


Input: **up** or **down**

Output: **on** or **off**

States: **A**, **B**, **C**, or **D**

FSM Example

  


Input: **0**=up or **1**=down

Output: **1**=on or **0**=off

States: **00**=A, **01**=B, **10**=C, or **11**=D

Mealy Machine


General Case: Mealy Machine

 

Outputs and next state depend on both current state and input



Moore Machine

Special Case: Moore Machine

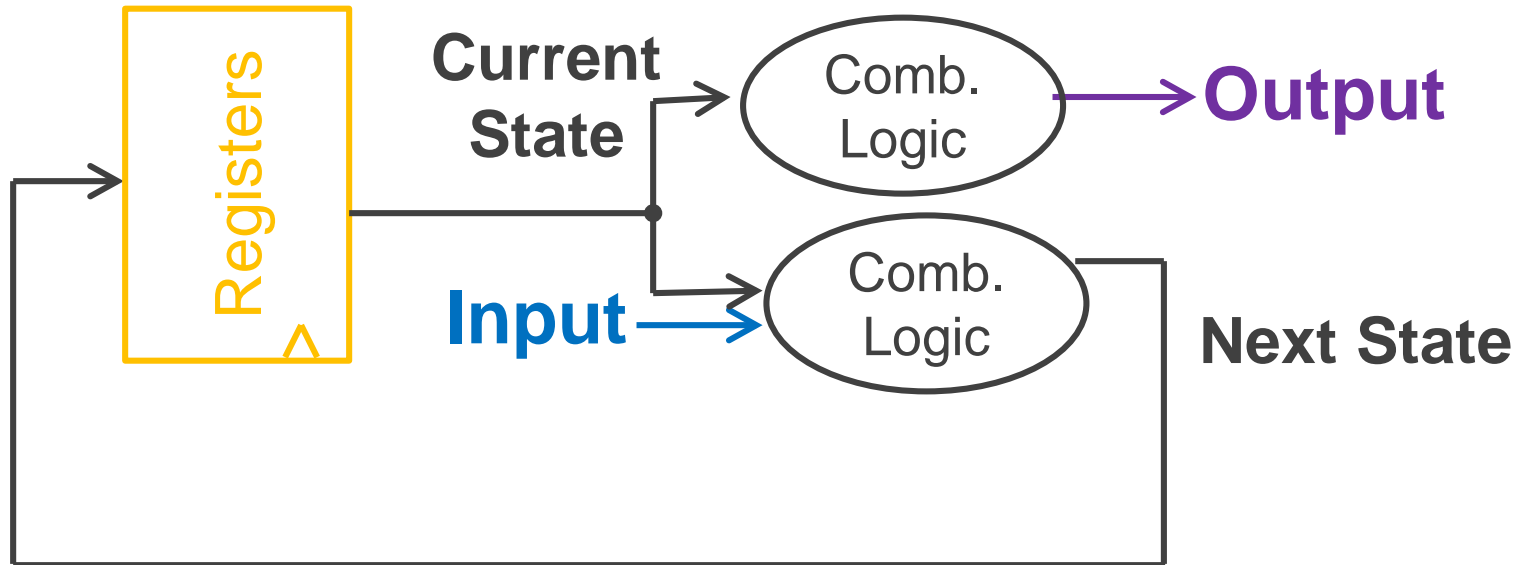

Outputs depend only on current state

Moore Machine FSM Example

 
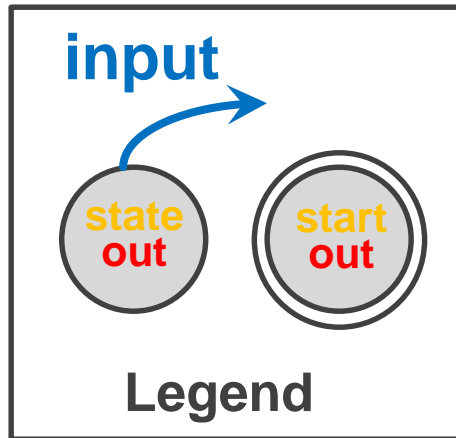


Input: **up** or **down**

Output: **on** or **off**

States: **A**, **B**, **C**, or **D**

Mealy Machine FSM Example

  

Input: **up** or **down**


Output: **on** or **off**

States: **A**, **B**, **C**, or **D**

Activity#2: Create a Logic Circuit for a Serial Adder

Add two infinite input bit streams

 - streams are sent with least-significant-bit (lsb) first
- How many states are needed to represent FSM?
- Draw and Fill in FSM diagram




Strategy:

- (1) Draw a state diagram (e.g. Mealy Machine)
- (2) Write output and next-state tables
- (3) Encode states, inputs, and outputs as bits
- (4) Determine logic equations for next state and outputs

Activity#2: Create a Logic Circuit for a Serial Adder

Add two infinite input bit streams

 
- streams are sent with least-significant-bit (lsb) first



Strategy for Building an FSM

- (1) Draw a state diagram (e.g. Mealy Machine)
- (2) Write output and next-state tables
- (3) Encode states, inputs, and outputs as bits
- (4) Determine logic equations for next state and outputs
- (5) Draw the Circuit

FSM: State Diagram

 


2 states and

Inputs: and

Output:

FSM: State Diagram

 

a...10110

b ...01111


...00101 z

2 states and

Inputs: and

Output:


Serial Adder: State Table

 

| a | b | Current state | z | Next state |
|---|---|---------------|---|------------|
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |

(2) Write down all input and state combinations


Serial Adder: State Table

 

| a | b | Current state | z | Next state |
|---|---|---------------|---|------------|
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |

(3) Encode states, inputs, and outputs as bits

Serial Adder: State Assignment

 

| a | b | s | z | s' |
|---|---|---|---|----|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

(4) Determine logic equations for next state and outputs

Serial Adder: State Assignment

| a | b | s | z | s' |
|---|---|---|---|----|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

(4) Determine logic equations for next state and outputs

Example: Digital Door Lock



Digital Door Lock

Inputs:

- keycodes from keypad
- clock


Outputs:

- “unlock” signal
- display how many keys pressed so far

Door Lock: Inputs

Assumptions:

 - signals are synchronized to clock
- Password is B-A-B




| K | A | B | Meaning |
|----------|----------|----------|----------------|
| 0 | 0 | 0 | ∅ (no key) |
| 1 | 1 | 0 | 'A' pressed |
| 1 | 0 | 1 | 'B' pressed |

Door Lock: Outputs

Assumptions:


- High pulse on U unlocks door

 

Strategy:


- (1) Draw a state diagram (e.g. Moore Machine)
- (2) Write output and next-state tables
- (3) Encode states, inputs, and outputs as bits
- (4) Determine logic equations for next state and outputs

Door Lock: Simplified State Diagram

 


(1) Draw a state diagram (e.g. Moore Machine)

Door Lock: Simplified State Diagram

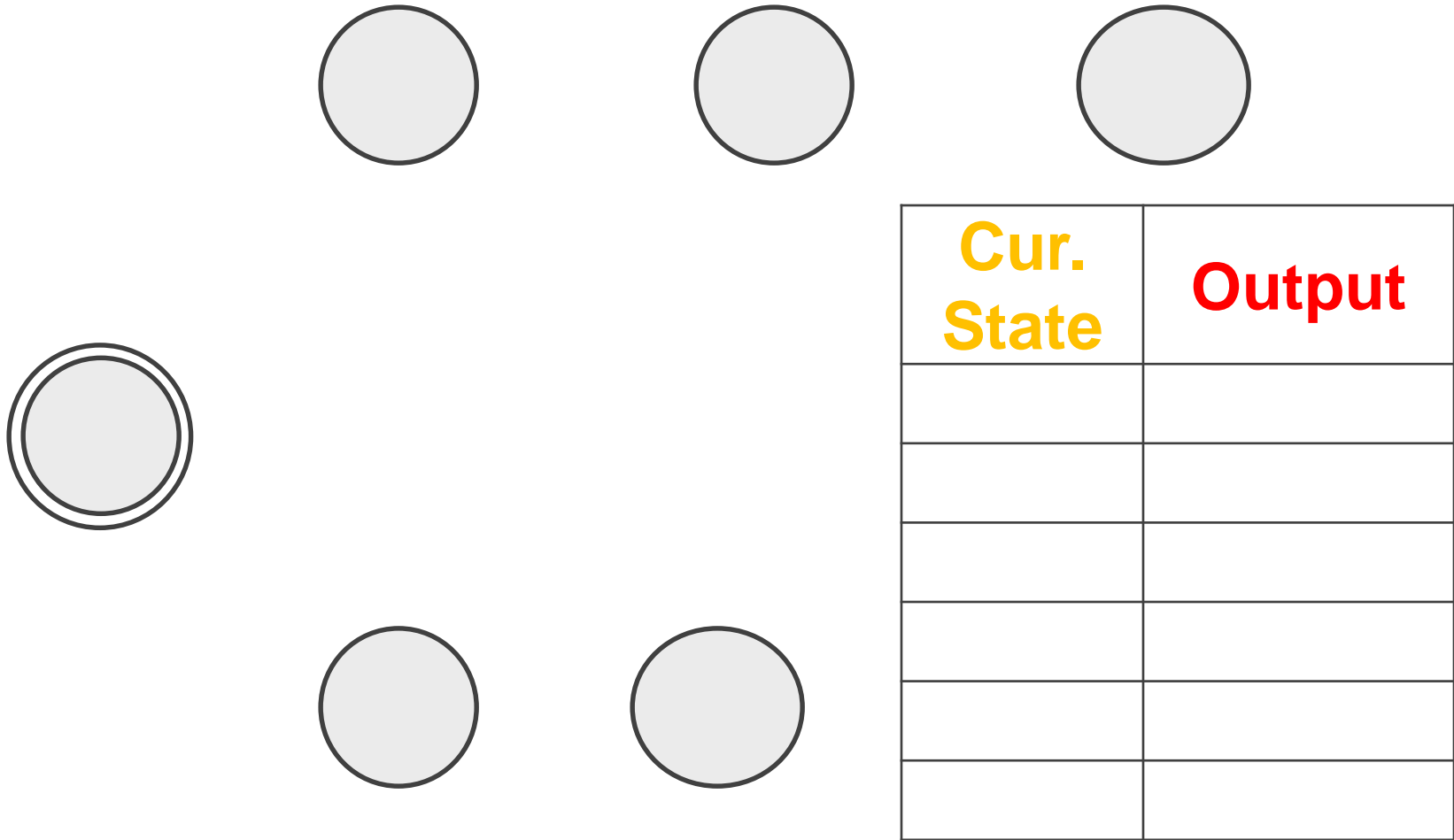

(2) Write output and next-state tables


Door Lock: Simplified State Diagram

 

| Cur. State | Input | Next State |
|------------|-------|------------|
| | | |
| | | |
| | | |
| | | |
| | | |
| | | |
| | | |
| | | |
| | | |
| | | |
| | | |
| | | |
| | | |
| | | |
| | | |
| | | |
| | | |
| | | |
| | | |
| | | |
| | | |
| | | |
| | | |
| | | |
| | | |
| | | |
| | | |
| | | |


(2) Write output and next-s

Door Lock: Implementation

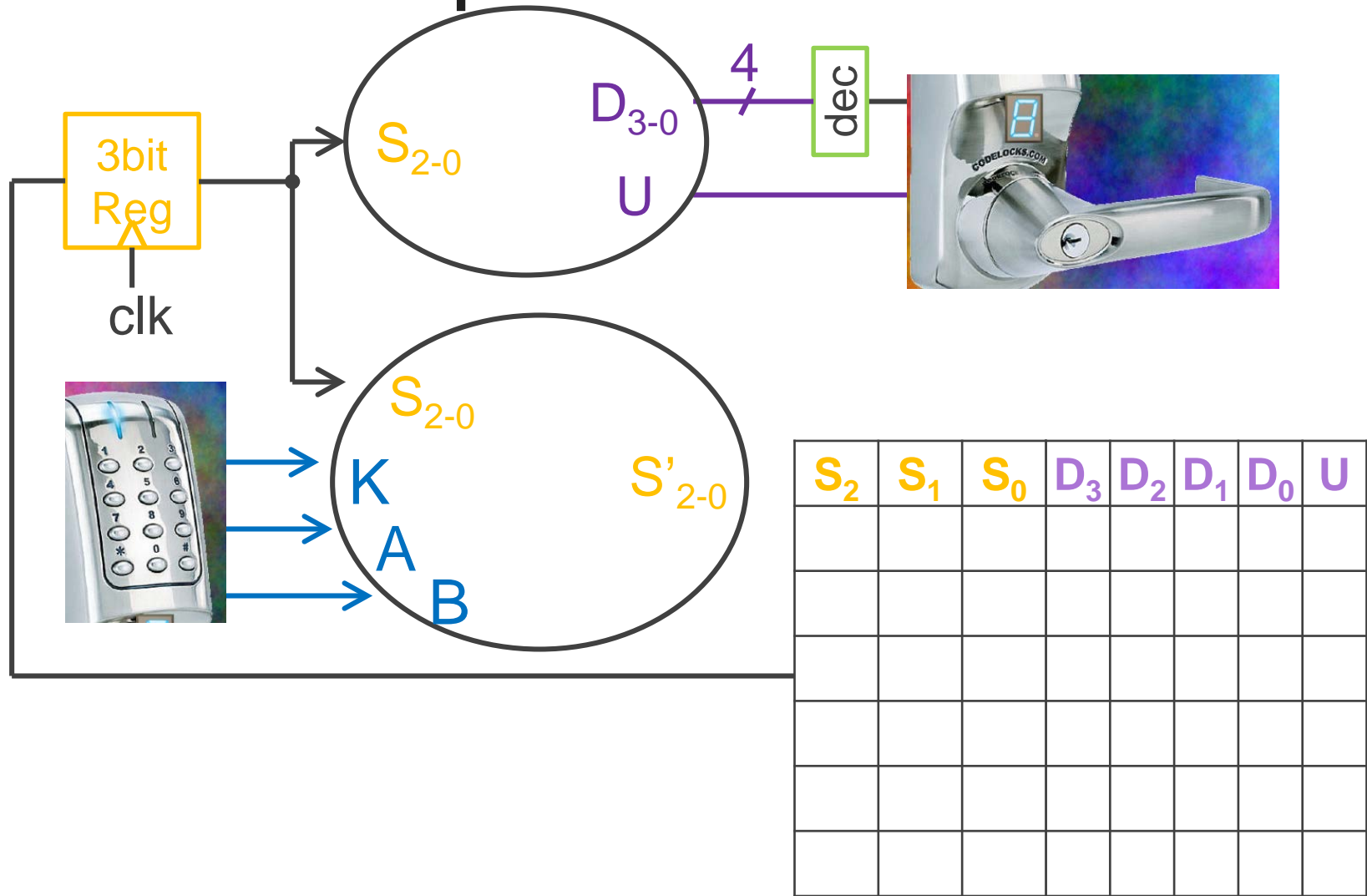


(4) Determine logic equations for next state and outputs

Door Lock: Implementation

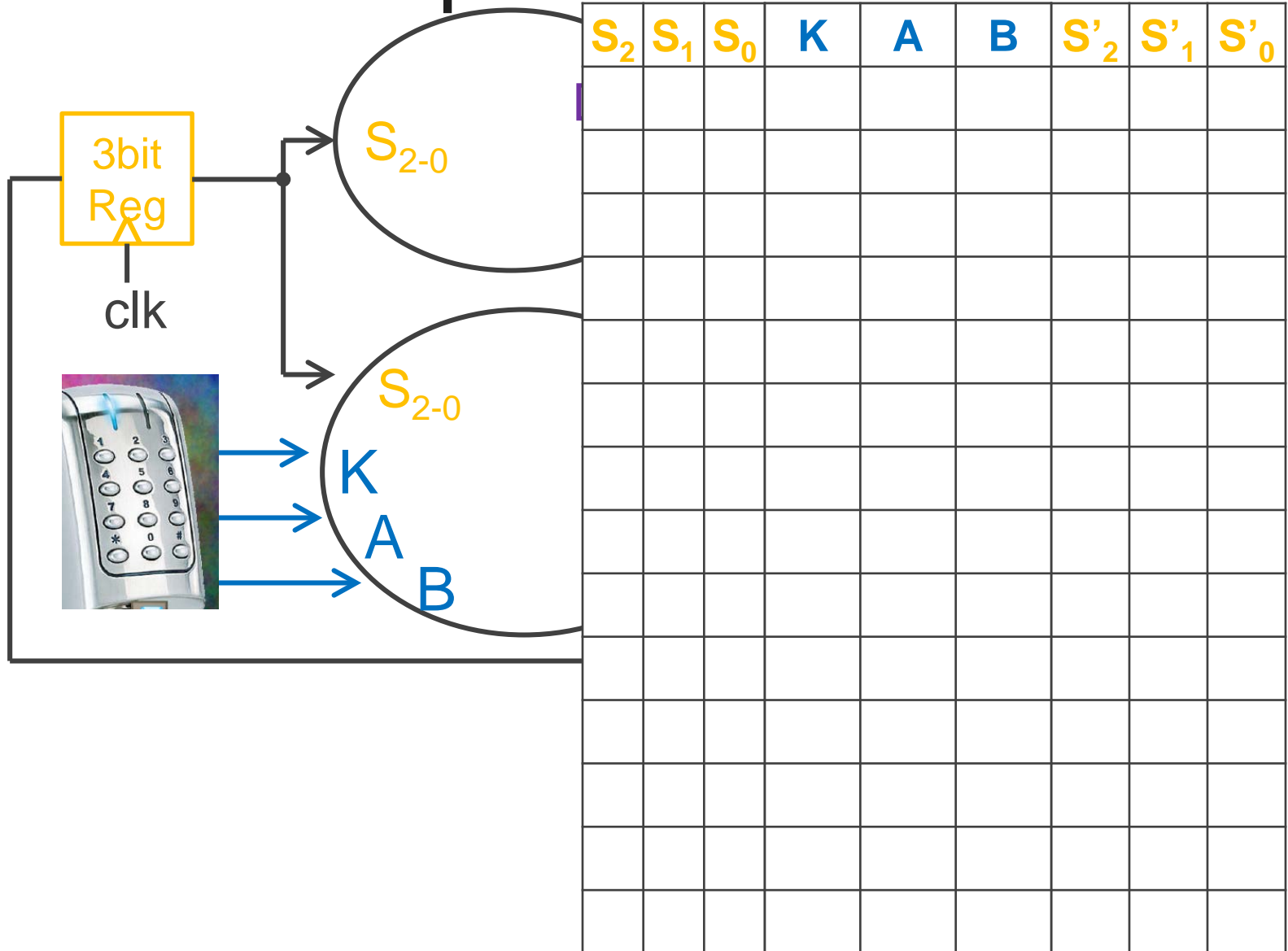

(4) Determine logic equations for next state and outputs


Door Lock: Implementation

 

Strategy:

- (1) Draw a state diagram (e.g. Moore Machine)
- (2) Write output and next-state tables
- (3) Encode states, inputs, and outputs as bits
- (4) Determine logic equations for next state and outputs

Door Lock: Implementation

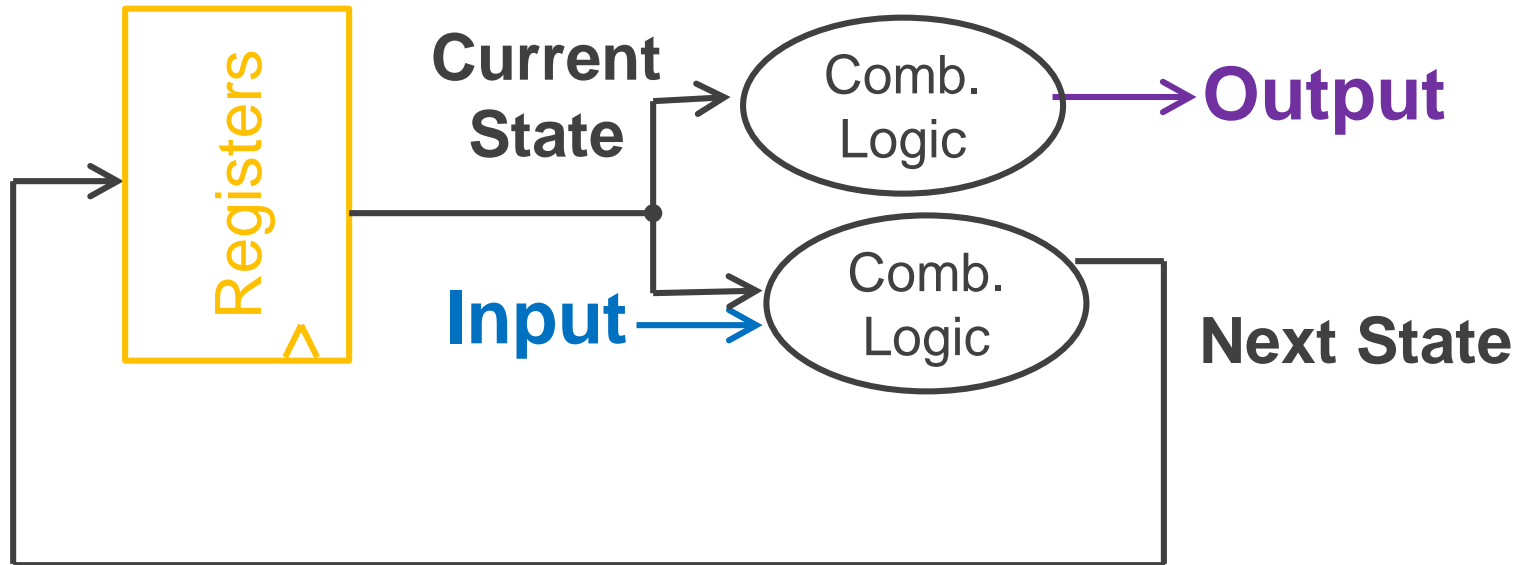

Strategy:

- (1) Draw a state diagram (e.g. Moore Machine)
- (2) Write output and next-state tables
- (3) Encode states, inputs, and outputs as bits
- (4) Determine logic equations for next state and outputs

Summary

We can now build interesting devices with sensors

- Using combinational logic

We can also store data values

- Stateful circuit elements (D Flip Flops, Registers, ...)
- State Machines or Ad-Hoc Circuits

