




Memory

Prof. Hakim Weatherspoon

CS 3410

Computer Science

Cornell University

 

Cornell CIS
COMPUTING AND INFORMATION SCIENCE

[Weatherspoon, Bala, Bracy, and Sirer]

Announcements

Make sure you are

- Registered for class, can access CMS
- Have a Section you can go to.
- *Lab Sections are required.*
 - “Make up” lab sections **only Friday 11:40am or 1:25pm**
 - Bring laptop to Labs
- Project partners are required for projects starting w/ project 2
 - Project partners will be assigned (from the same lab section, if possible)



Announcements

- Make sure to go to **your** Lab Section this week
- Completed **Proj1** due Friday, Feb 15th
- Note, a Design Document is due when you submit Proj1 final circuit
- Work **alone**

BUT use your resources

- Lab Section, Piazza.com, Office Hours
- Class notes, book, Sections, CSUGLab



Announcements

Check online syllabus/schedule

- <http://www.cs.cornell.edu/Courses/CS3410/2019sp/schedule>
- Slides and Reading for lectures
- Office Hours
- ***Pictures of all TAs***
- Project and Reading Assignments
- **Dates to keep in Mind**
 - Prelims: Tue Mar 5th and Thur May 2nd
 - ***Proj 1: Due next Friday, Feb 15th***
 - Proj3: Due before Spring break
 - Final Project: May 16th

Schedule is subject to change



Announcements

- Level Up (optional enrichment)
 - Teaches CS students tools and skills needed in their coursework as well as their career, such as Git, Bash Programming, study strategies, ethics in CS, and even applying to graduate school.
 - Thursdays at 7-8pm in 310 Gates Hall, starting this week
 - <http://www.cs.cornell.edu/courses/cs3110/2019sp/levelup/>




Goals for today

Memory

- CPU: Register Files (i.e. Memory w/in the CPU)
- Scaling Memory: Tri-state devices
- Cache: SRAM (Static RAM—random access memory)
- Memory: DRAM (Dynamic RAM)



Last time: How do we store one bit

 

D Flip Flop stores 1 bit




Goal for today

How do we store results from ALU computations?




Big Picture: Building a Processor

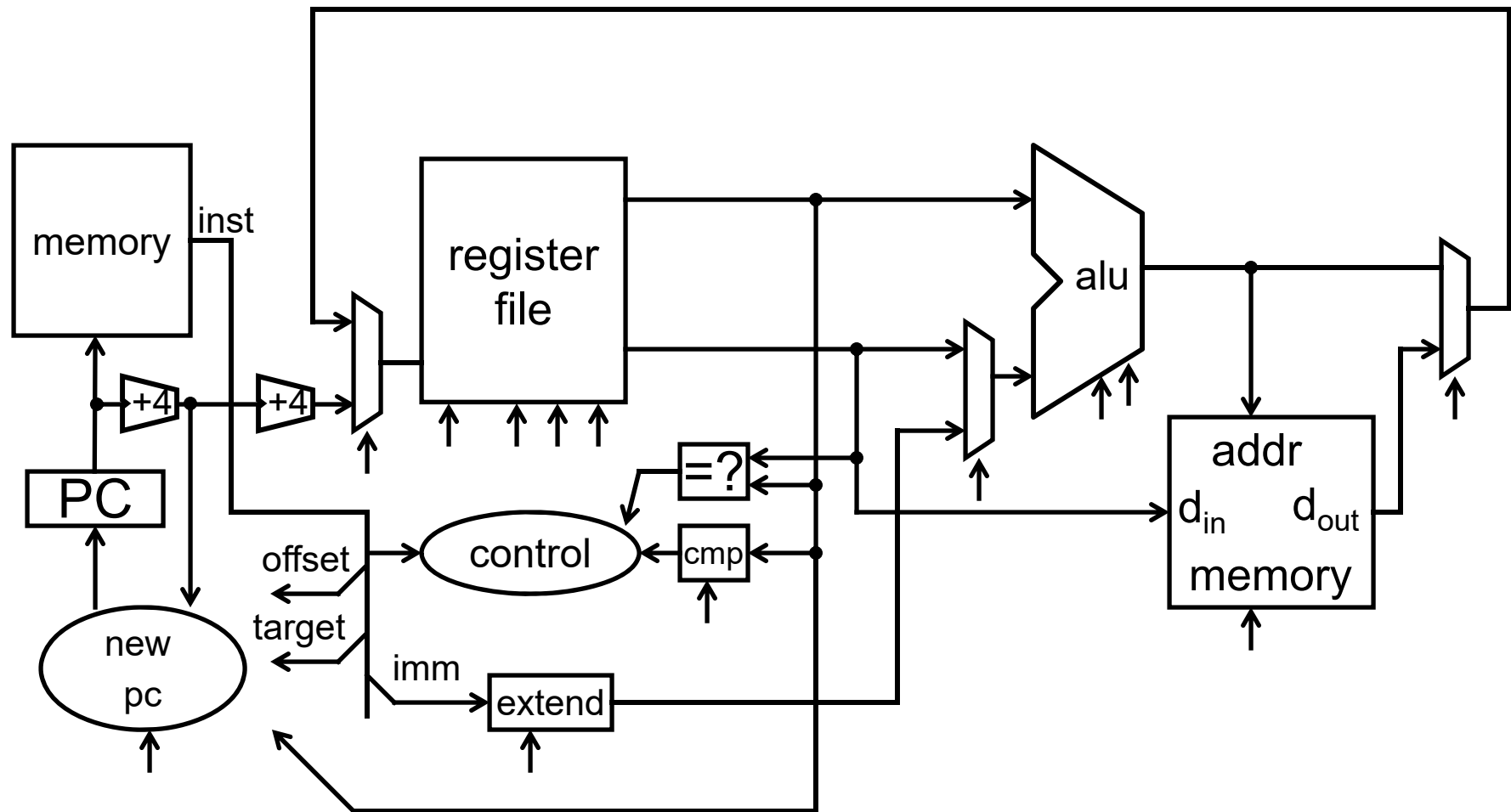

A Single cycle processor

Big Picture: Building a Processor

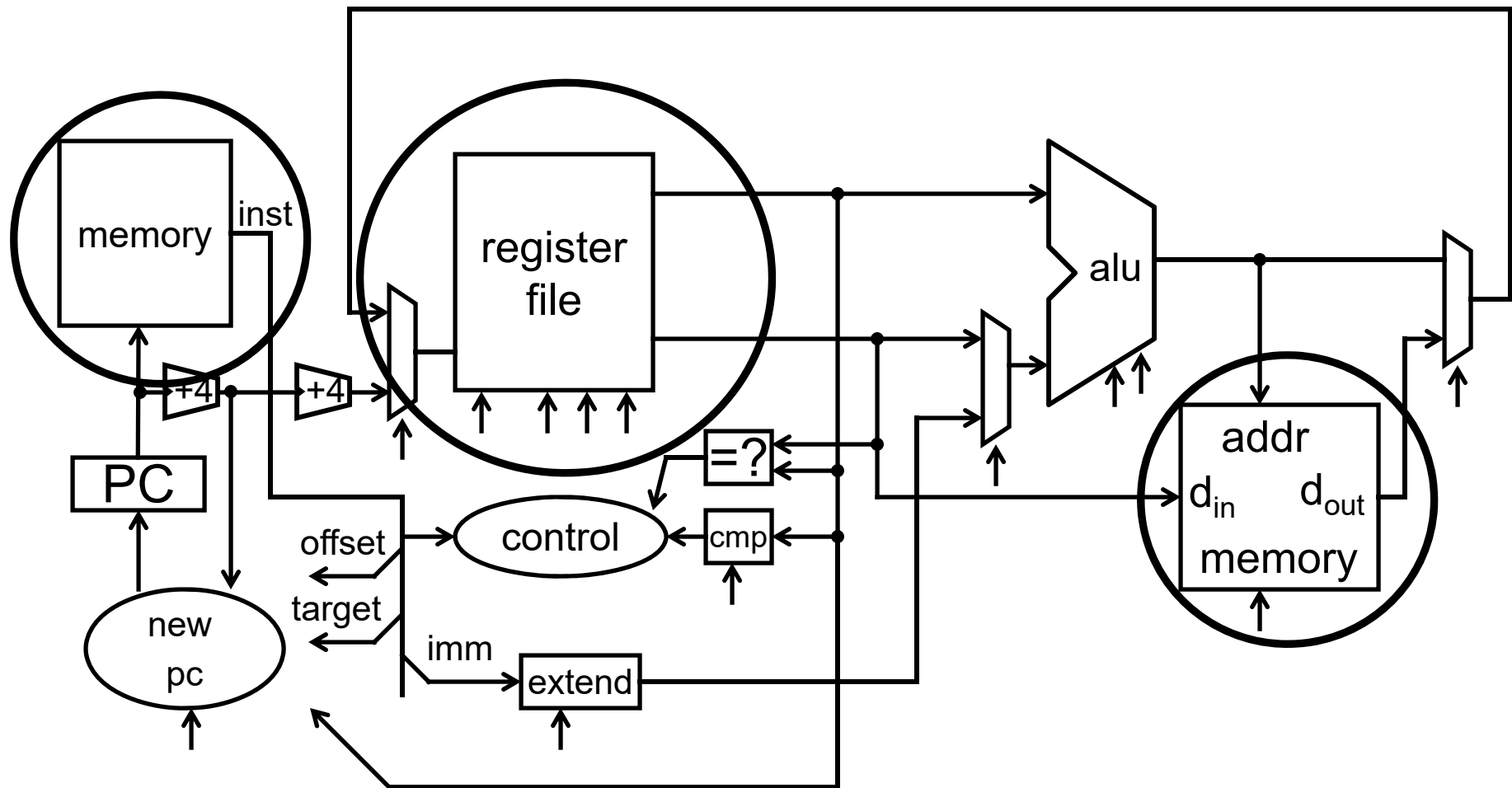

A Single cycle processor

Goal for today

How do we store results from ALU computations?

How do we use stored results in subsequent operations?

Register File


How does a Register File work? How do we design it?




Register File

Register File

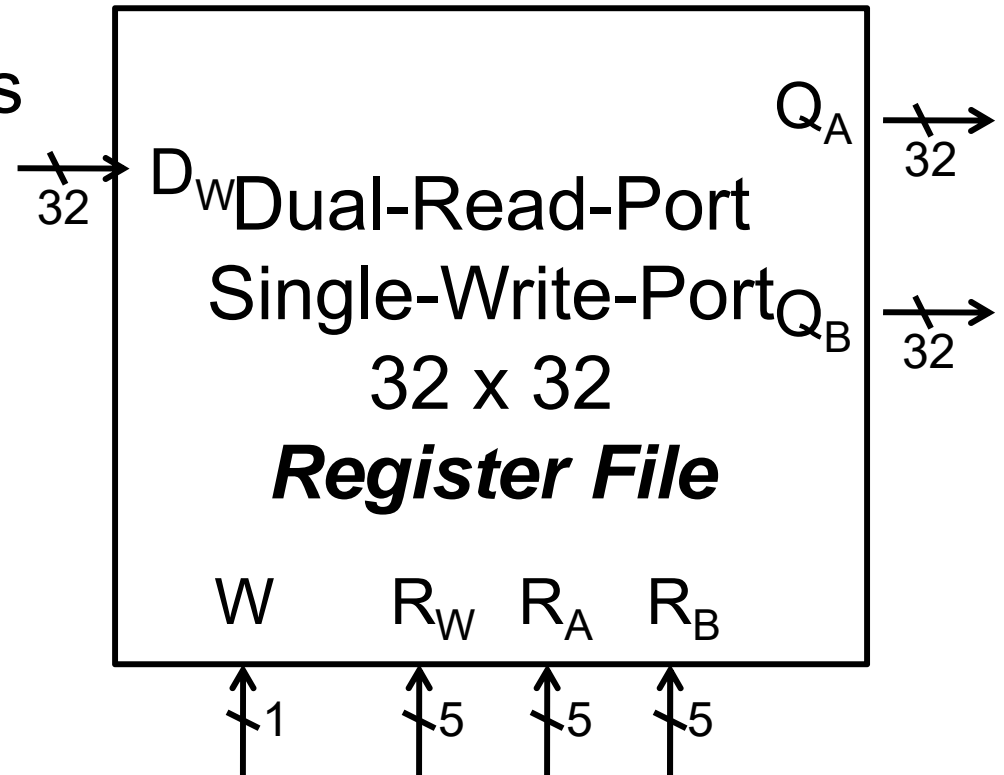- N read/write registers
- Indexed by register number




Register File

 


Recall: Register

 - D flip-flops in parallel
- shared clock
- extra clocked inputs: write_enable, reset, ...




Register File

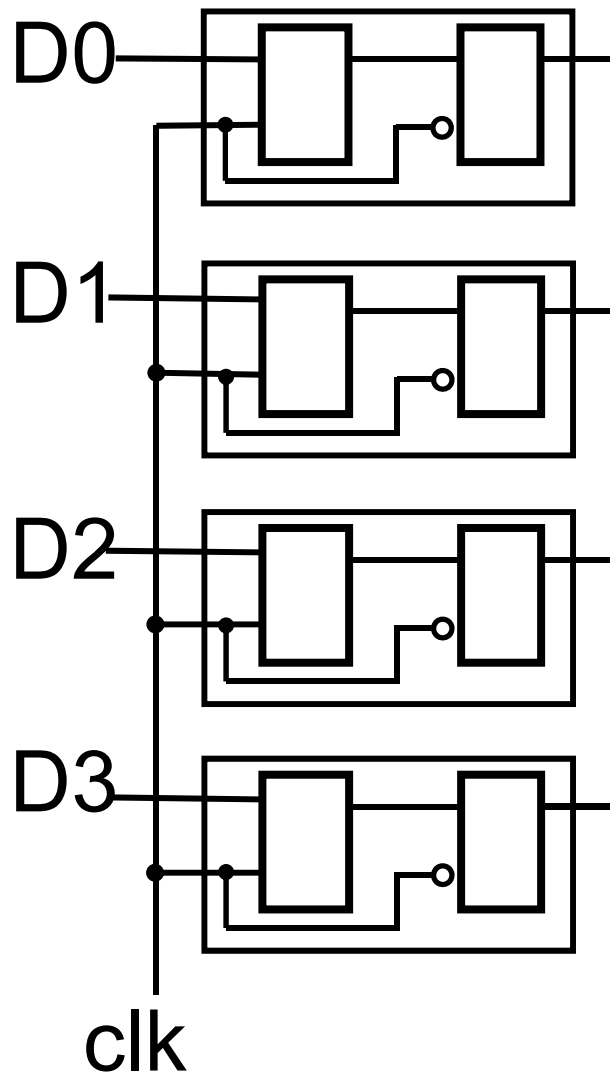

Recall: Register

 - D flip-flops in parallel
- shared clock
- extra clocked inputs: write_enable, reset, ...




Register File

Register File

- N read/write registers
- Indexed by register number

`addi x1, x0, 10`

 


How to write to **one** register in the register file?

- Need a decoder




🏠 Aside: 3-to-8 decoder truth table & circuit

i2	i1	i0	o0	o1	o2	o3	o4	o5	o6	o7
0	0	0								
0	0	1								
0	1	0								
0	1	1								
1	0	0								
1	0	1								
1	1	0								
1	1	1								

 

🏠 Aside: 3-to-8 decoder truth table & circuit

i2	i1	i0	o0	o1	o2	o3	o4	o5	o6	o7
0	0	0	1							
0	0	1		1						
0	1	0			1					
0	1	1				1				
1	0	0					1			
1	0	1						1		
1	1	0							1	
1	1	1								1

   

Register File


Register File

- N read/write registers
- Indexed by register number

add x1, x0, x5

How to read from two registers?

- Need a multiplexor

 


Register File

Register File

- N read/write registers
- Indexed by register number

Implementation:

 - D flip flops to store bits
- Decoder for each write port
- Mux for each read port




Register File

Register File

- N read/write registers
- Indexed by register number

Implementation:

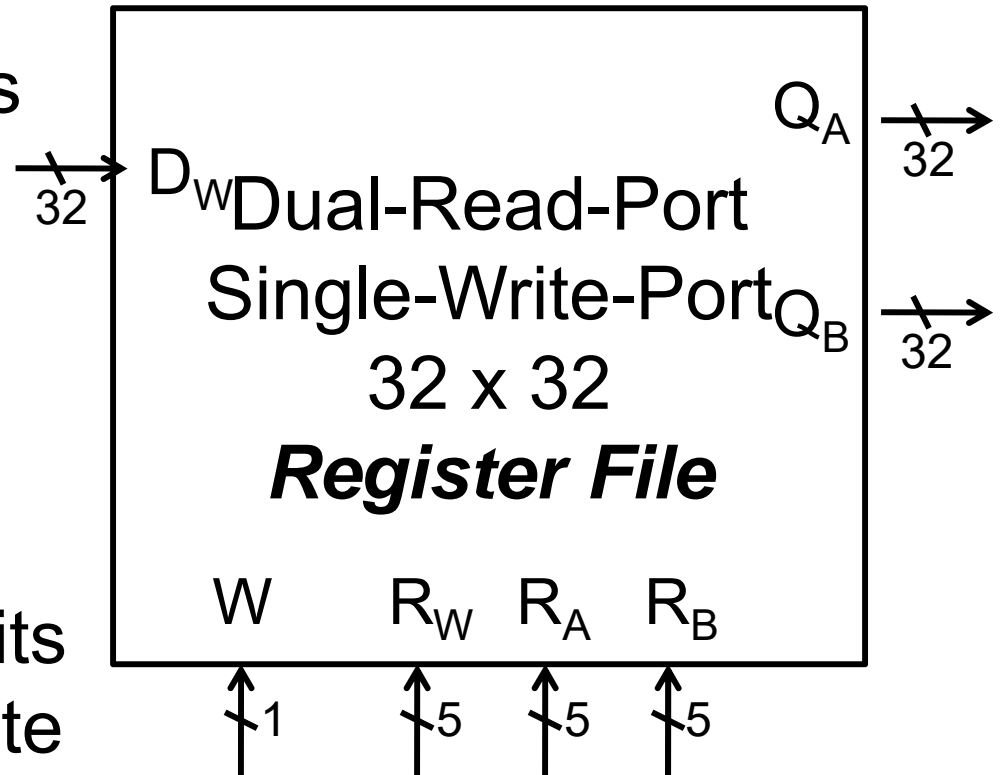- D flip flops to store bits
- Decoder for each write port
- Mux for each read port



Register File

Register File

- N read/write registers
- Indexed by register number

What happens if same register read and written during same clock cycle?

Implementation:

- D flip flops to store bits
- Decoder for each write port
- Mux for each read port

Tradeoffs


Register File tradeoffs

- + Very fast (a few gate delays for both read and write)
- + Adding extra ports is straightforward
- Doesn't scale

e.g. 32Mb register file with
32 bit registers

Need 32x 1M-to-1 multiplexor
and 32x 20-to-1M decoder

How many logic gates/transistors?

 

Takeway

Register files are very fast storage (only a few gate delays), but does not scale to large memory sizes.



Goals for today

Memory

- CPU: Register Files (i.e. Memory w/in the CPU)
- Scaling Memory: Tri-state devices
- Cache: SRAM (Static RAM—random access memory)
- Memory: DRAM (Dynamic RAM)



Next Goal


How do we scale/build larger memories?



Building Large Memories

Need a shared bus (or shared bit line)

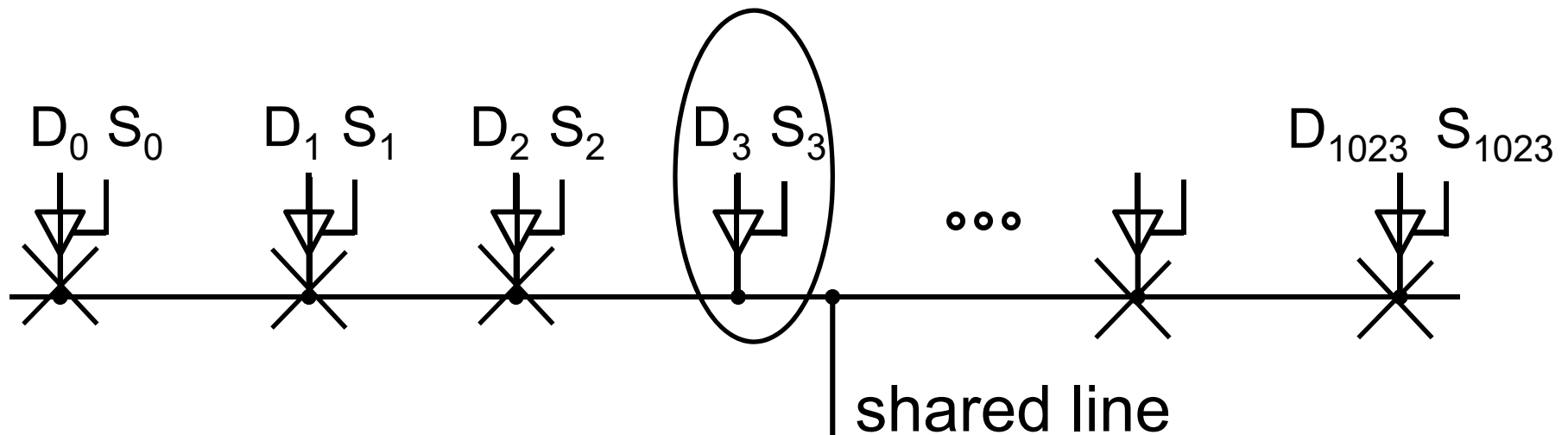- Many FlipFlops/outputs/etc. connected to single wire
- Only one output *drives* the bus at a time




- How do we build such a device?

Tri-State Devices

Tri-State Buffers

 - If enabled ($E=1$), then $Q = D$
- Otherwise, Q is not connected ($z = \text{high impedance}$)




E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1


Tri-State Devices

Tri-State Buffers

 - If enabled ($E=1$), then $Q = D$
- Otherwise, Q is not connected ($z = \text{high impedance}$)




E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

 


Tri-State Devices

Tri-State Buffers

 - If enabled ($E=1$), then $Q = D$
- Otherwise, Q is not connected ($z = \text{high impedance}$)




E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

 

Tri-State Devices

Tri-State Buffers

 
- If enabled ($E=1$), then $Q = D$
- Otherwise, Q is not connected (z = high impedance)



E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

A	B	AND	NAND
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0


A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

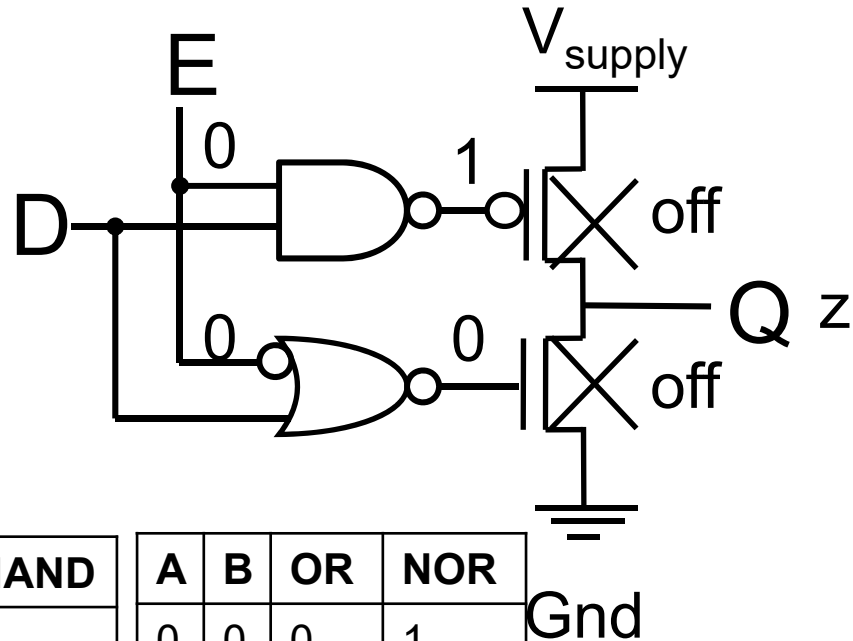

Tri-State Devices

Tri-State Buffers

 
- If enabled ($E=1$), then $Q = D$
- Otherwise, Q is not connected ($z = \text{high impedance}$)



E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

A	B	AND	NAND
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0


A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

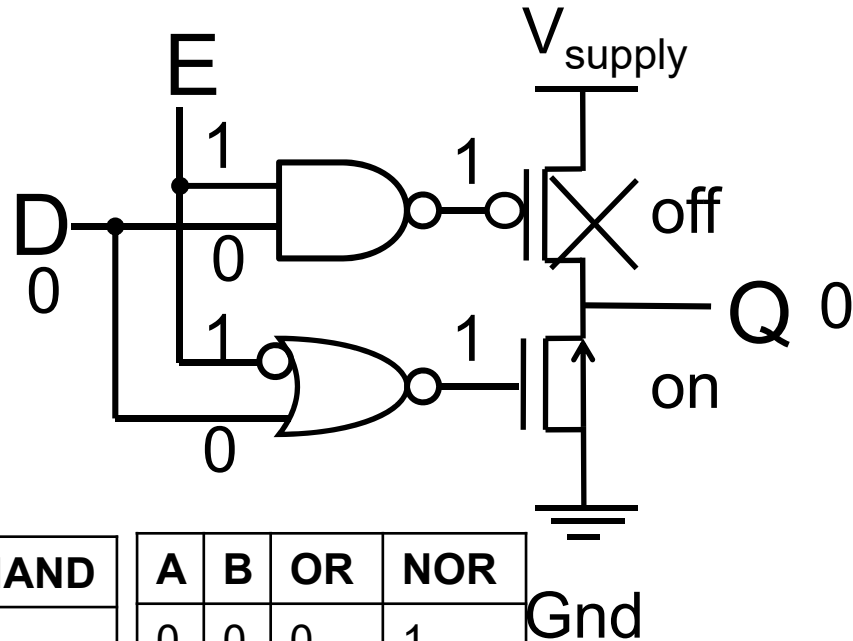

Tri-State Devices

Tri-State Buffers

 
- If enabled ($E=1$), then $Q = D$
- Otherwise, Q is not connected (z = high impedance)




E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

A	B	AND	NAND
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

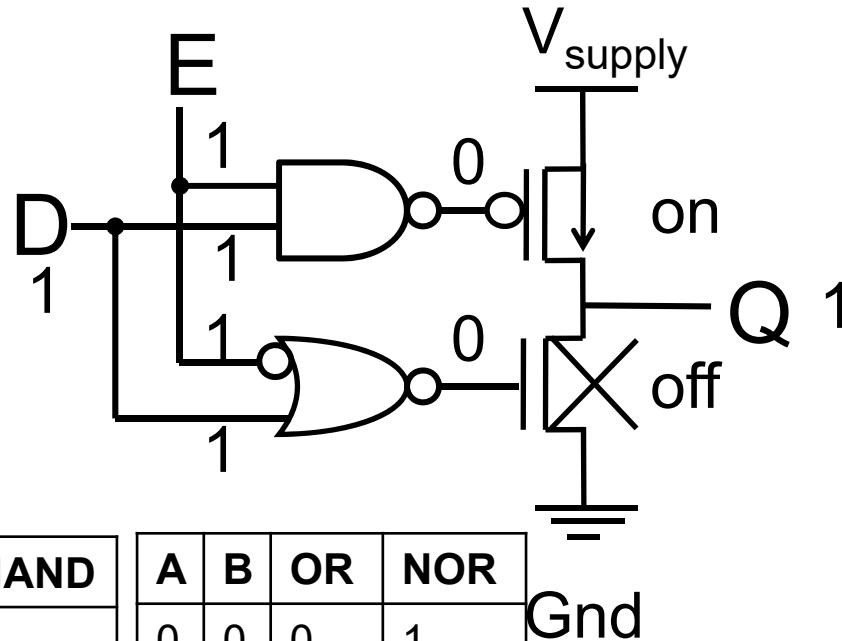

Shared Bus

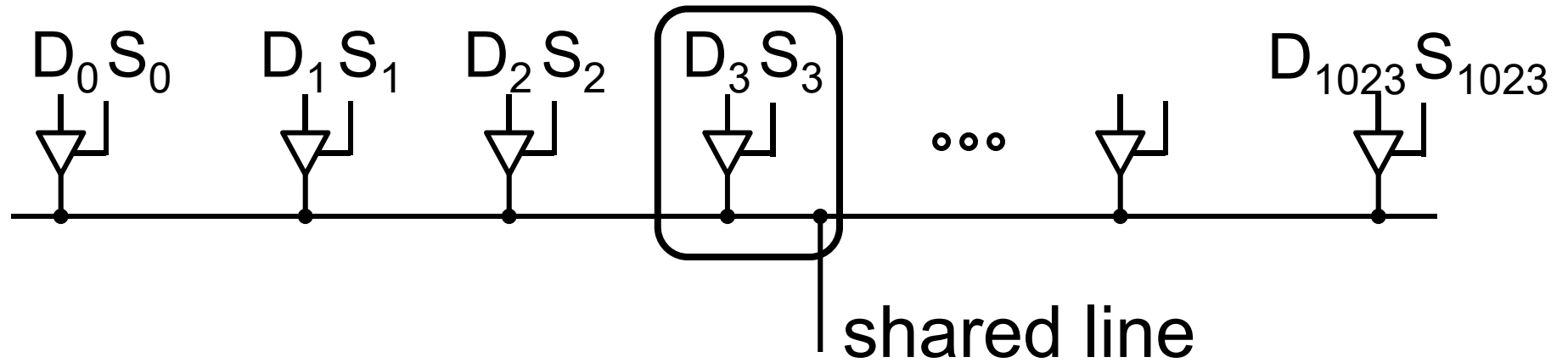

Takeway

Register files are very fast storage (only a few gate delays), but does not scale to large memory sizes.

Tri-state Buffers allow scaling since multiple registers can be connected to a single output, while only one register actually drives the output.



Goals for today

Memory

- CPU: Register Files (i.e. Memory w/in the CPU)
- Scaling Memory: Tri-state devices
- Cache: SRAM (Static RAM—random access memory)
- Memory: DRAM (Dynamic RAM)



Next Goal


How do we build large memories?

Use similar designs as Tri-state Buffers to connect multiple registers to output line. Only one register will drive output line.



Memory

 
- Storage Cells + bus
- Inputs: Address, Data (for writes)
- Outputs: Data (for reads)
- Also need R/W signal (not shown)



- N address bits $\rightarrow 2^N$ words total
- M data bits \rightarrow each word M bits


Memory

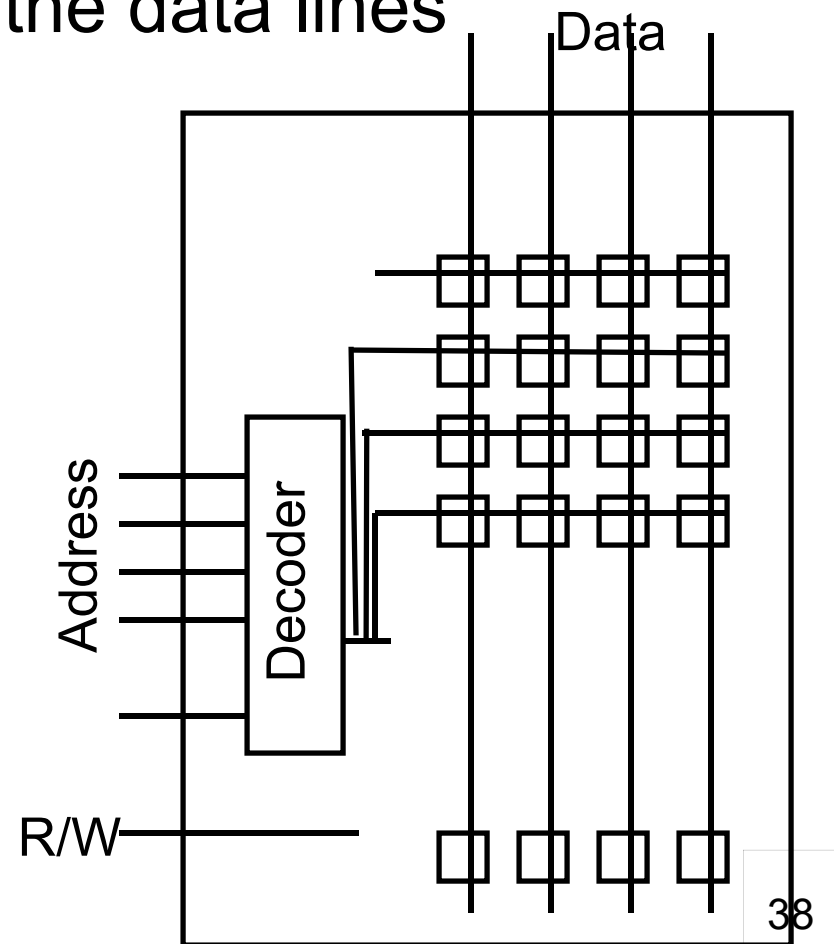- Storage Cells + bus
- Decoder selects a word line
- R/W selector determines access type
- Word line is then coupled to the data lines



Memory

 
- Storage Cells + bus
- Decoder selects a word line
- R/W selector determines access type
- Word line is then coupled to the data lines



Memory

E.g. How do we design
a 4 x 2 Memory Module

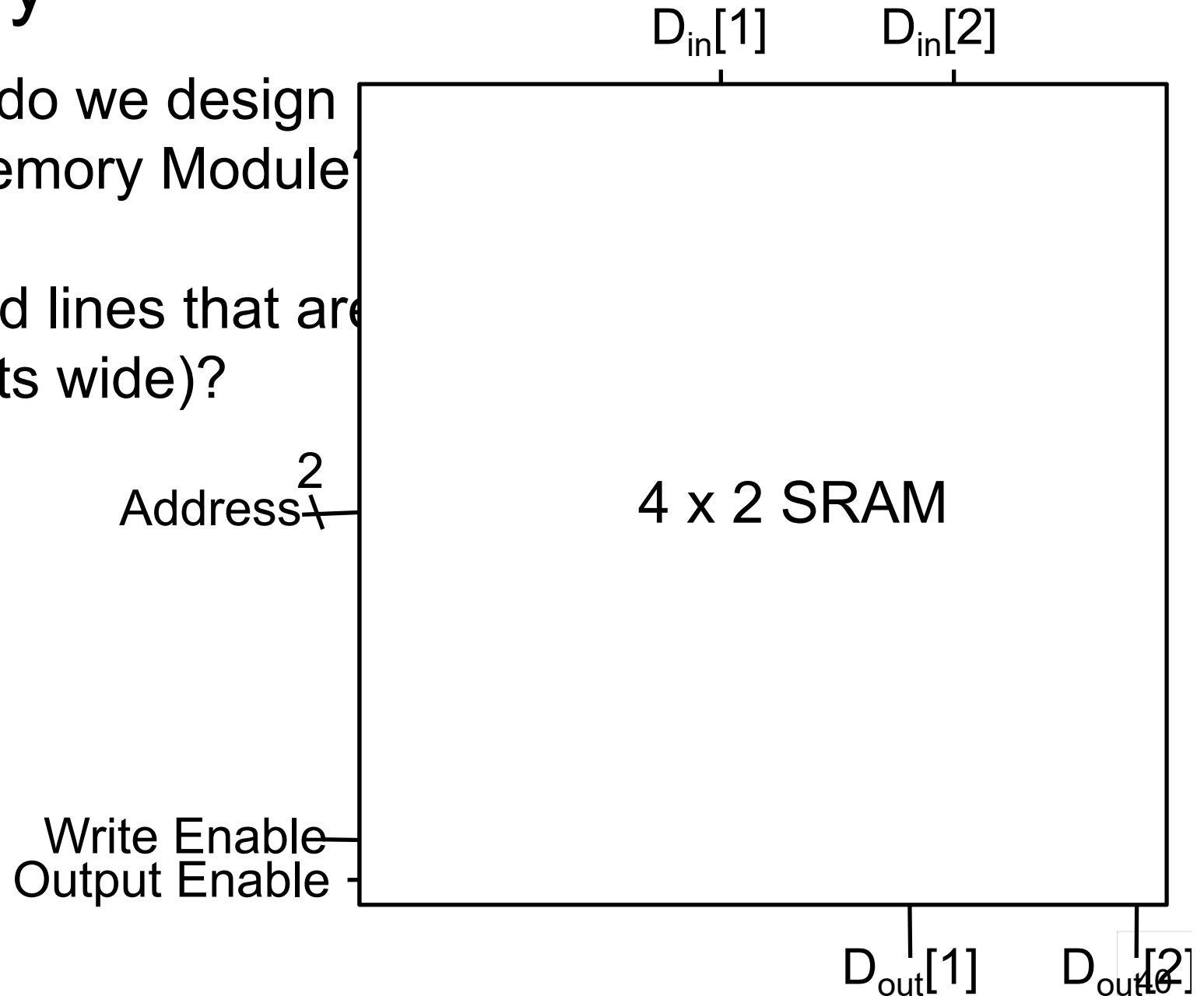
(i.e. 4 word lines that are
each 2 bits wide)?



Memory

E.g. How do we design
a 4 x 2 Memory Module?

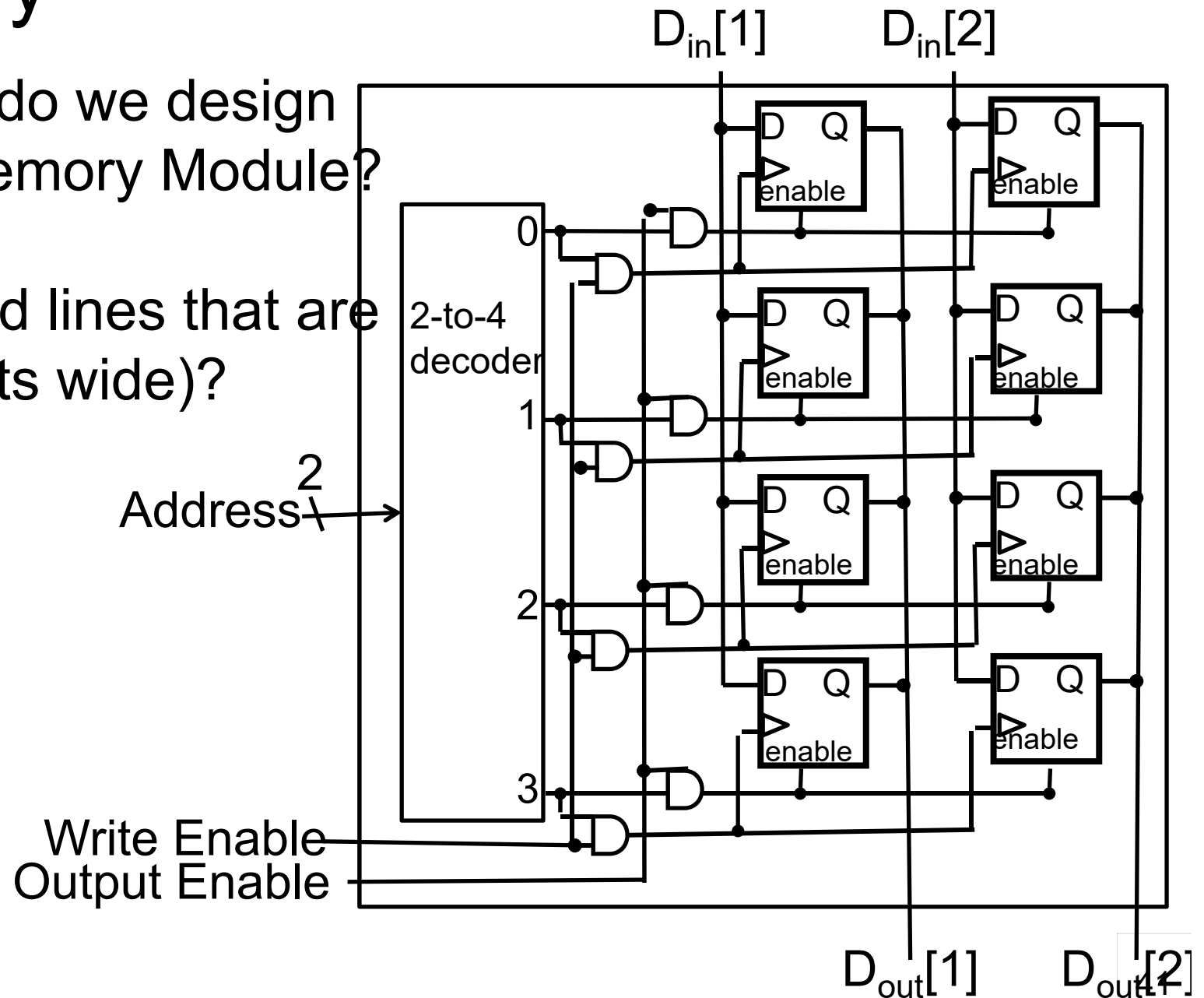(i.e. 4 word lines that are
each 2 bits wide)?




Register File

Register File

- N read/write registers
- Indexed by register number

`addi x1, x0, 10`

 

00001


How to write to **one** register in the register file?

- Need a decoder

Memory

E.g. How do we design
a 4 x 2 Memory Module?

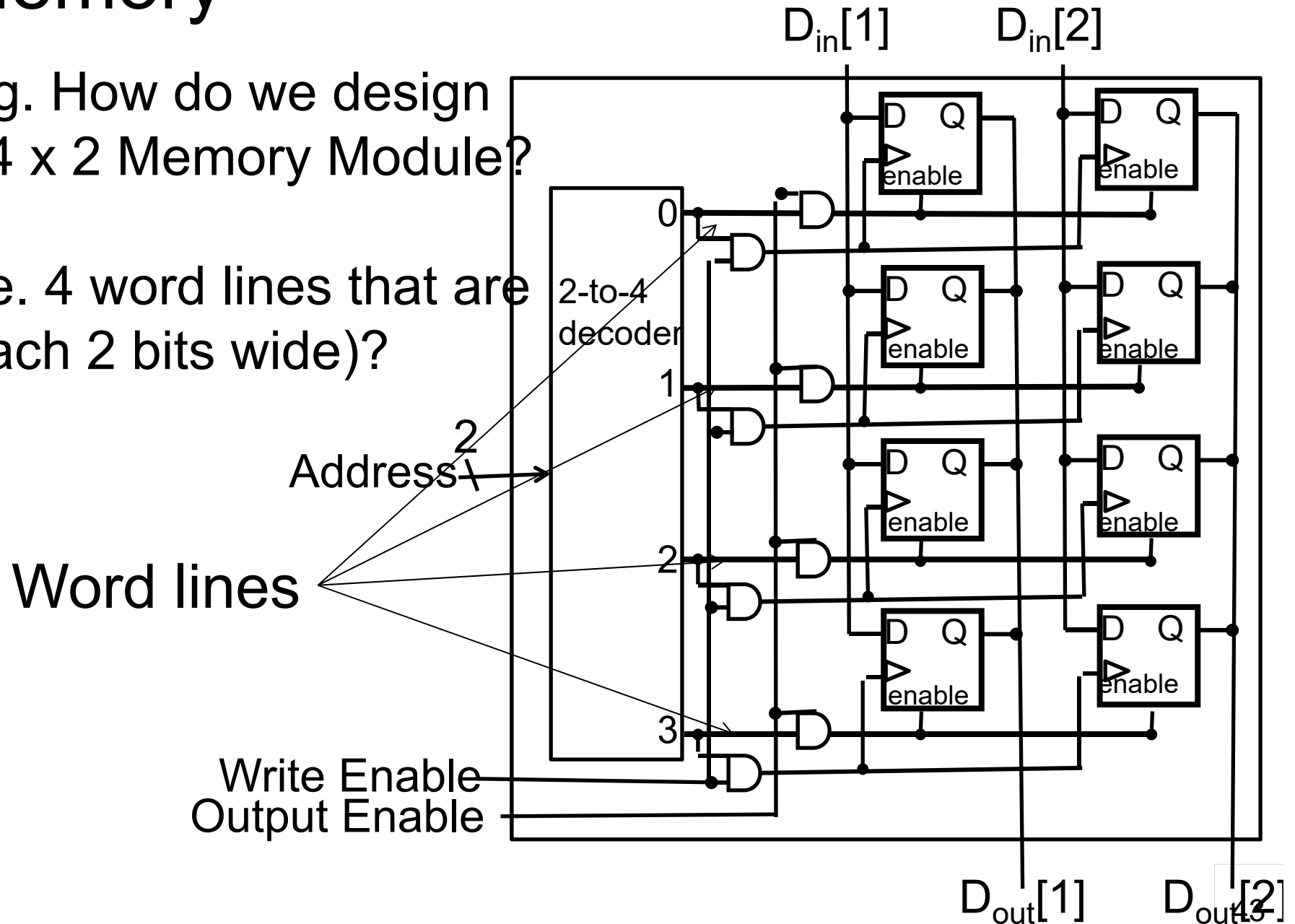
(i.e. 4 word lines that are
each 2 bits wide)?



Memory

E.g. How do we design
a 4 x 2 Memory Module?

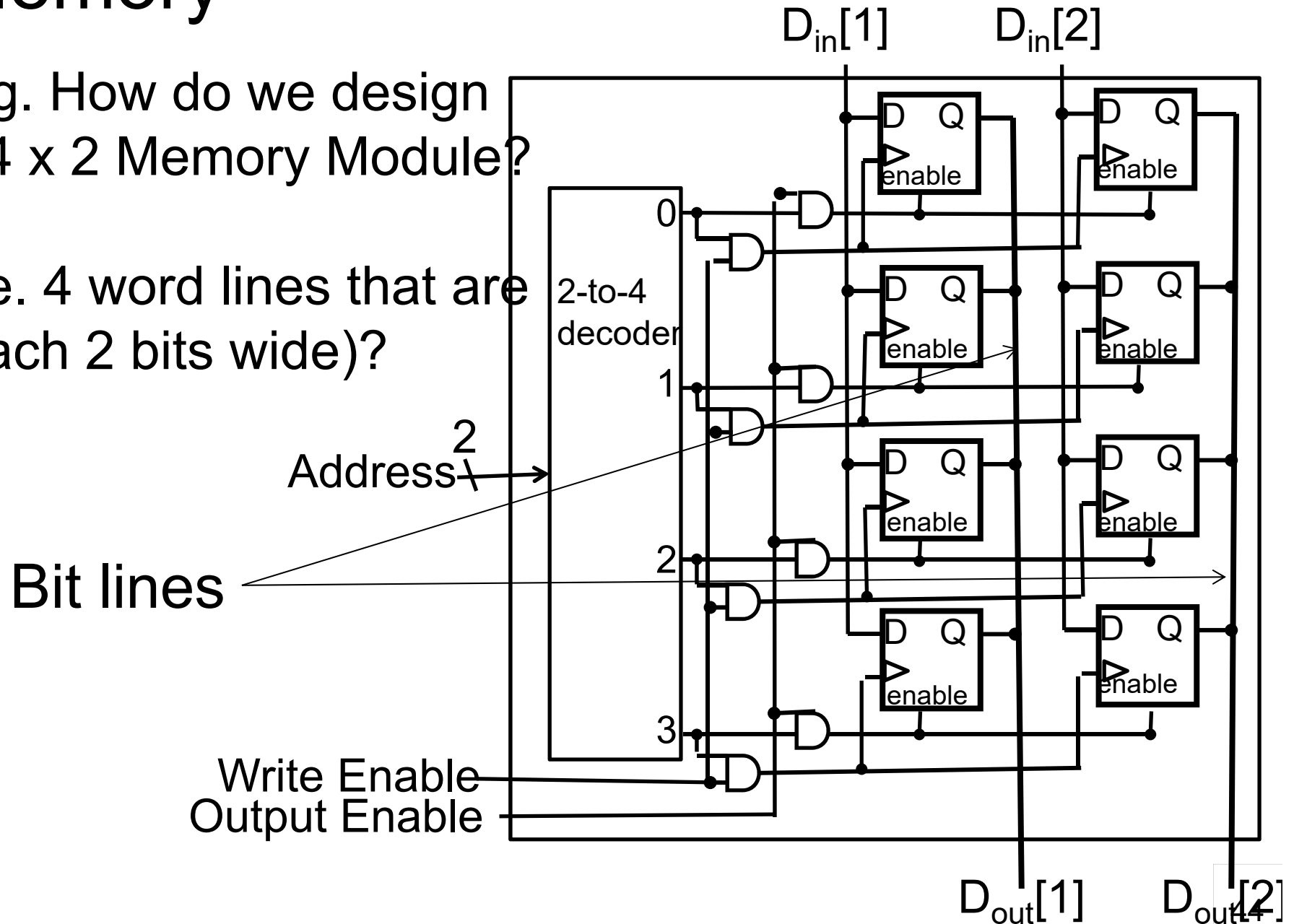(i.e. 4 word lines that are
each 2 bits wide)?




iClicker Question

What's your familiarity with memory (SRAM, DRAM)?

- A. I've never heard of any of this.
- B. I've heard the words SRAM and DRAM, but I have no idea what they are.
- C. I know that DRAM means main memory.
- D. I know the difference between SRAM and DRAM and where they are used in a computer system.

SRAM Cell


Typical SRAM Cell

 

Each cell stores one bit, and requires 4 – 8 transistors (6 is typical)

SRAM Cell

Typical SRAM Cell

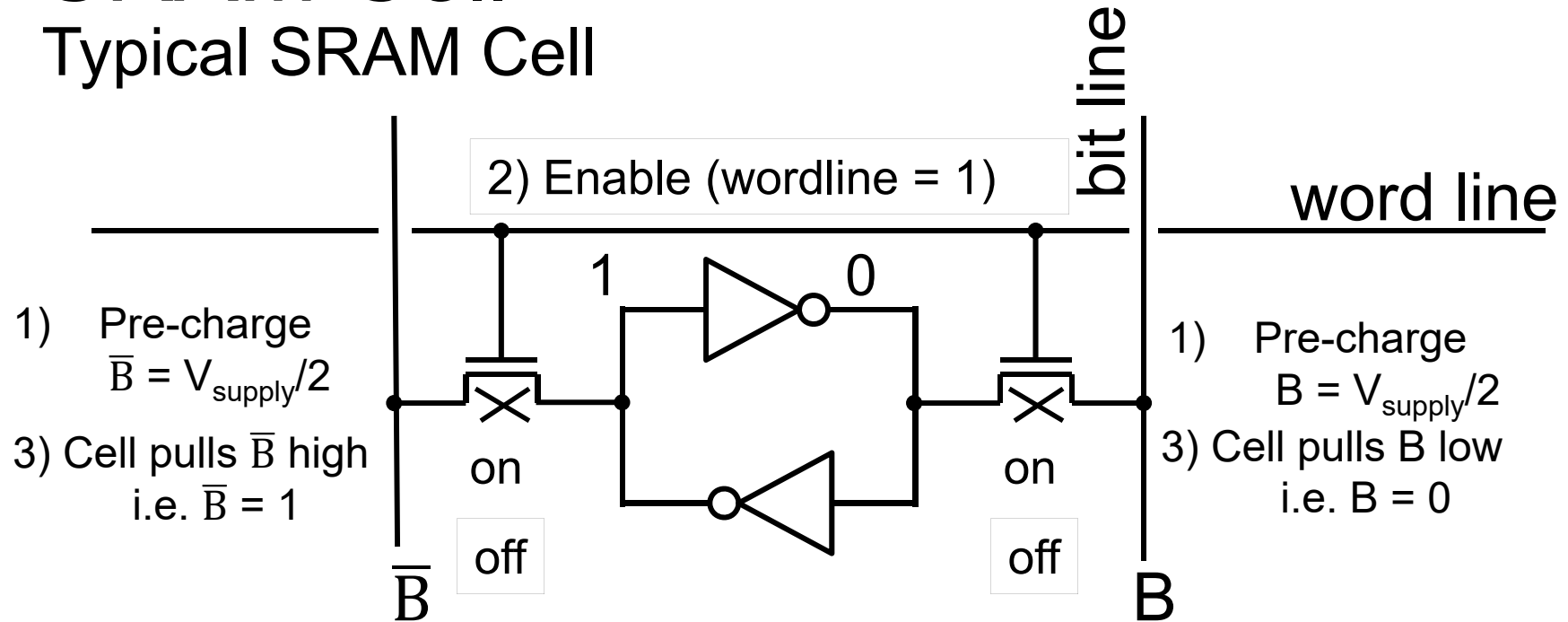


Each cell stores one bit, and requires 4 – 8 transistors (6 is typical)

Read:

- pre-charge B and \bar{B} to $V_{\text{supply}}/2$
- pull word line high
- cell pulls B or \bar{B} low, sense amp detects voltage difference

SRAM Cell

Typical SRAM Cell

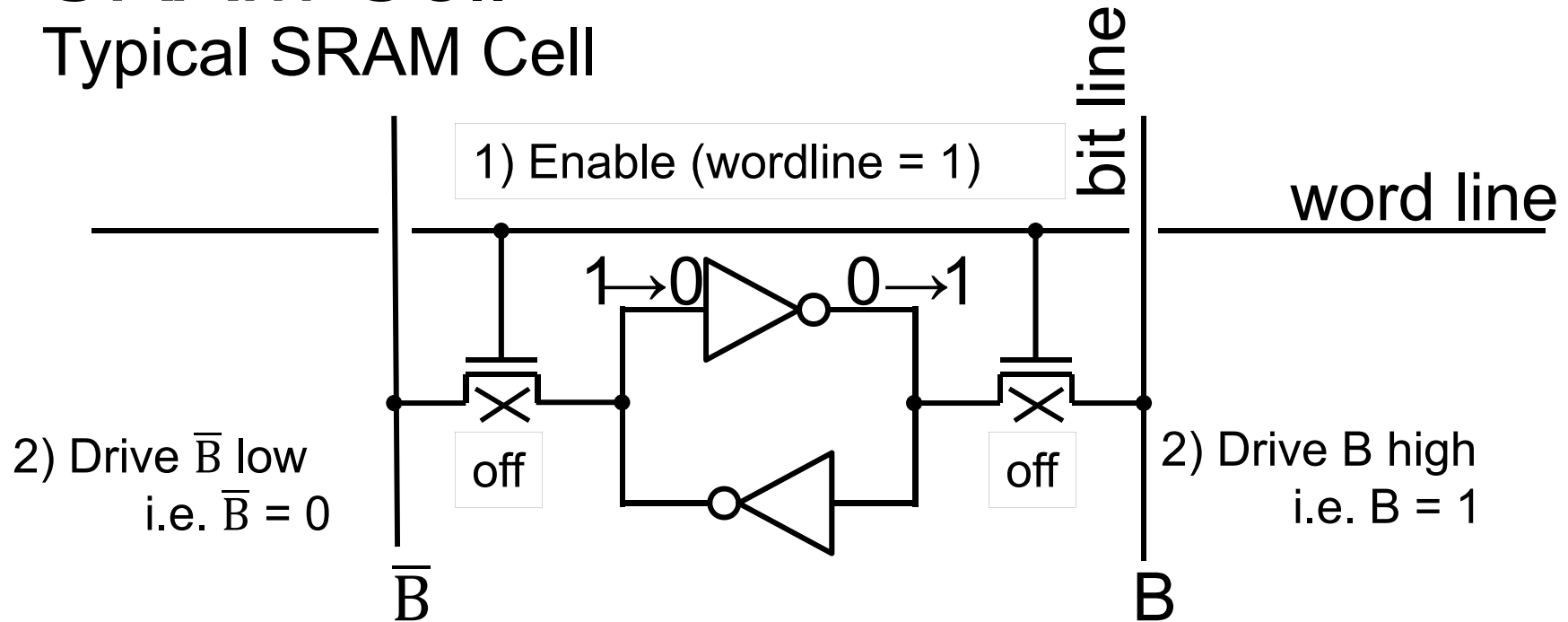

Each cell stores one bit, and requires 4 – 8 transistors (6 is typical)

Read:

- pre-charge B and \bar{B} to $V_{\text{supply}}/2$
- pull word line high
- cell pulls B or \bar{B} low, sense amp detects voltage difference

Write:

- pull word line high
- drive B and \bar{B} to flip cell

SRAM


E.g. How do we design
a 4 x 2 SRAM Module?

(i.e. 4 word lines that are
each 2 bits wide)?

Word lines

Write Enable
Output Enable


Address

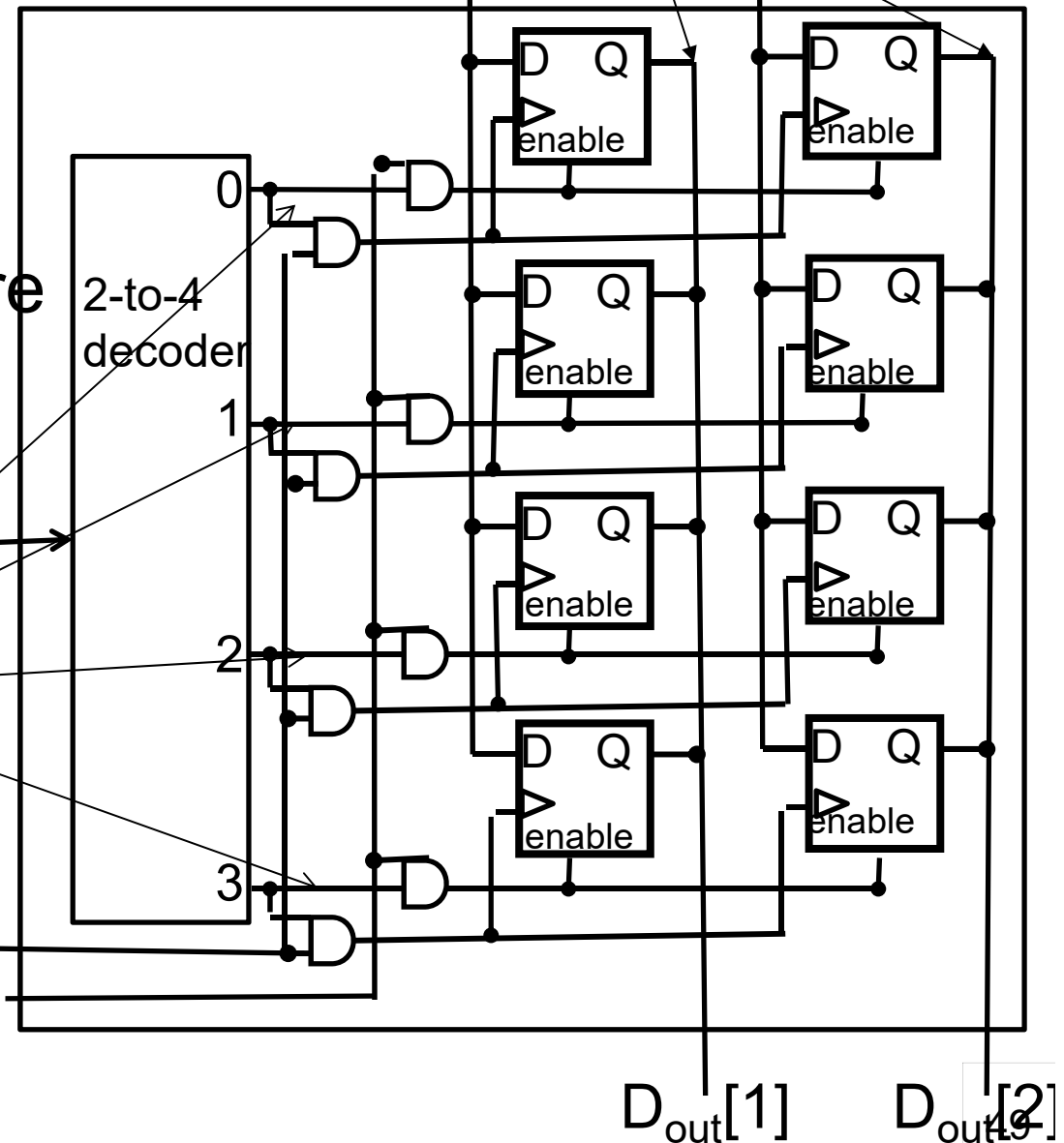

SRAM

E.g. How do we design
a 4 x 2 SRAM Module?

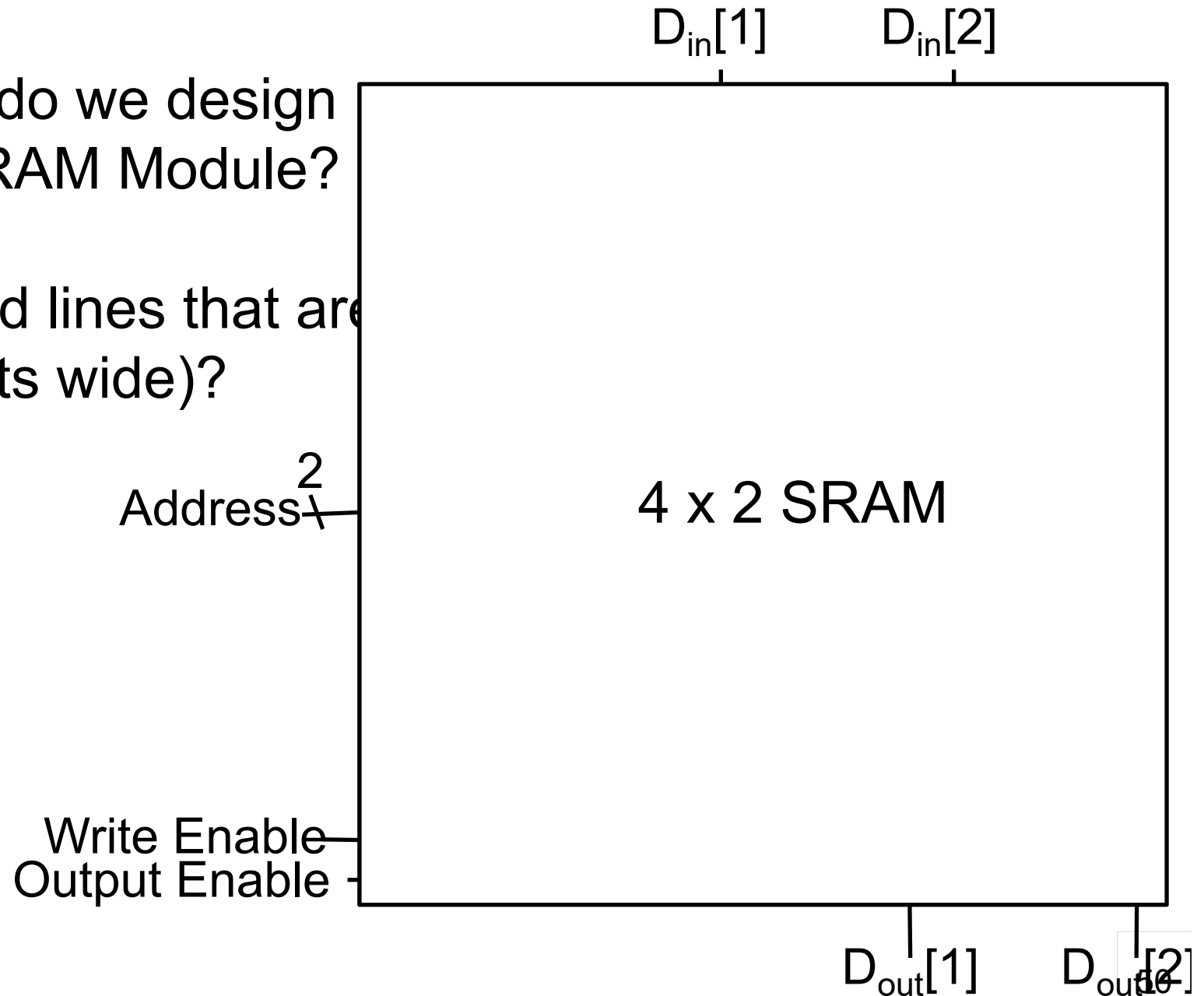
(i.e. 4 word lines that are
each 2 bits wide)?



SRAM


E.g. How do we design
a **4M x 8** SRAM Module?

 (i.e. 4M word lines that
are each 8 bits wide)?




SRAM

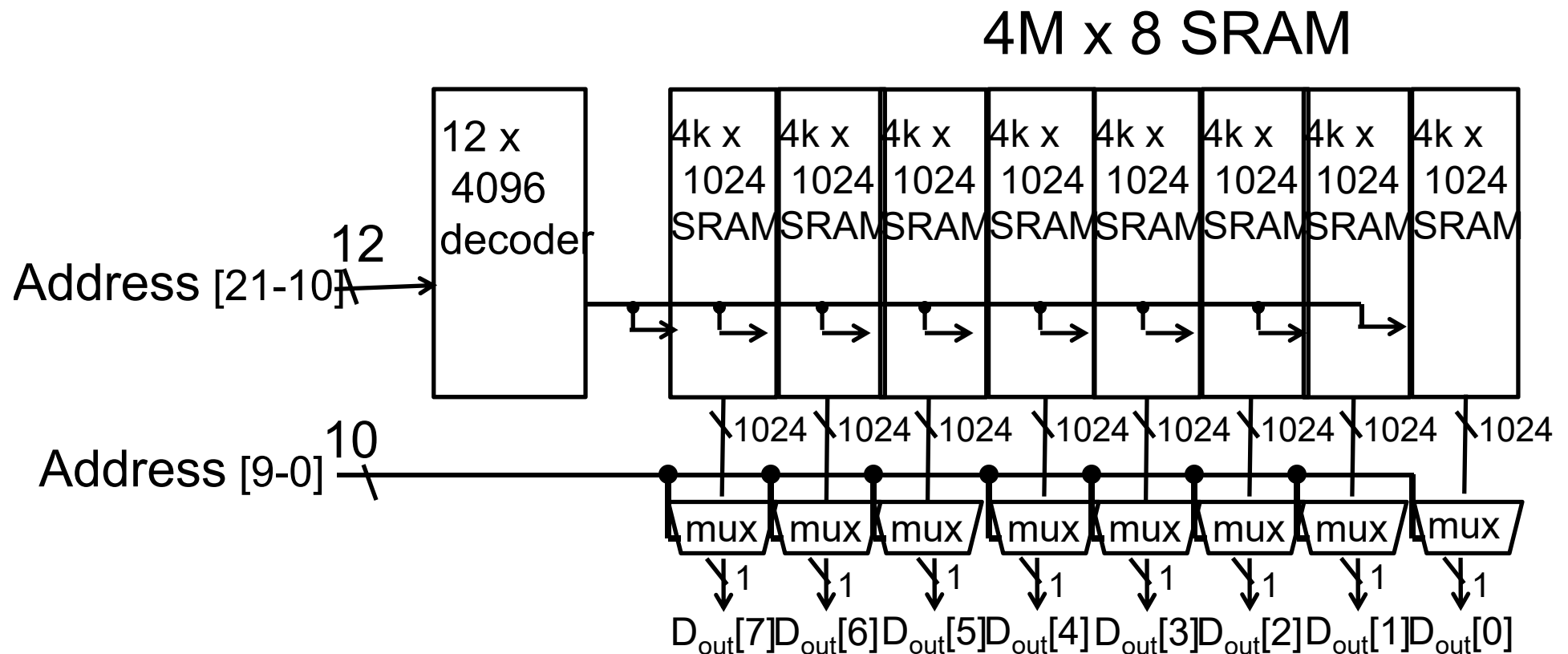E.g. How do we design
a **4M x 8** SRAM Module?




SRAM

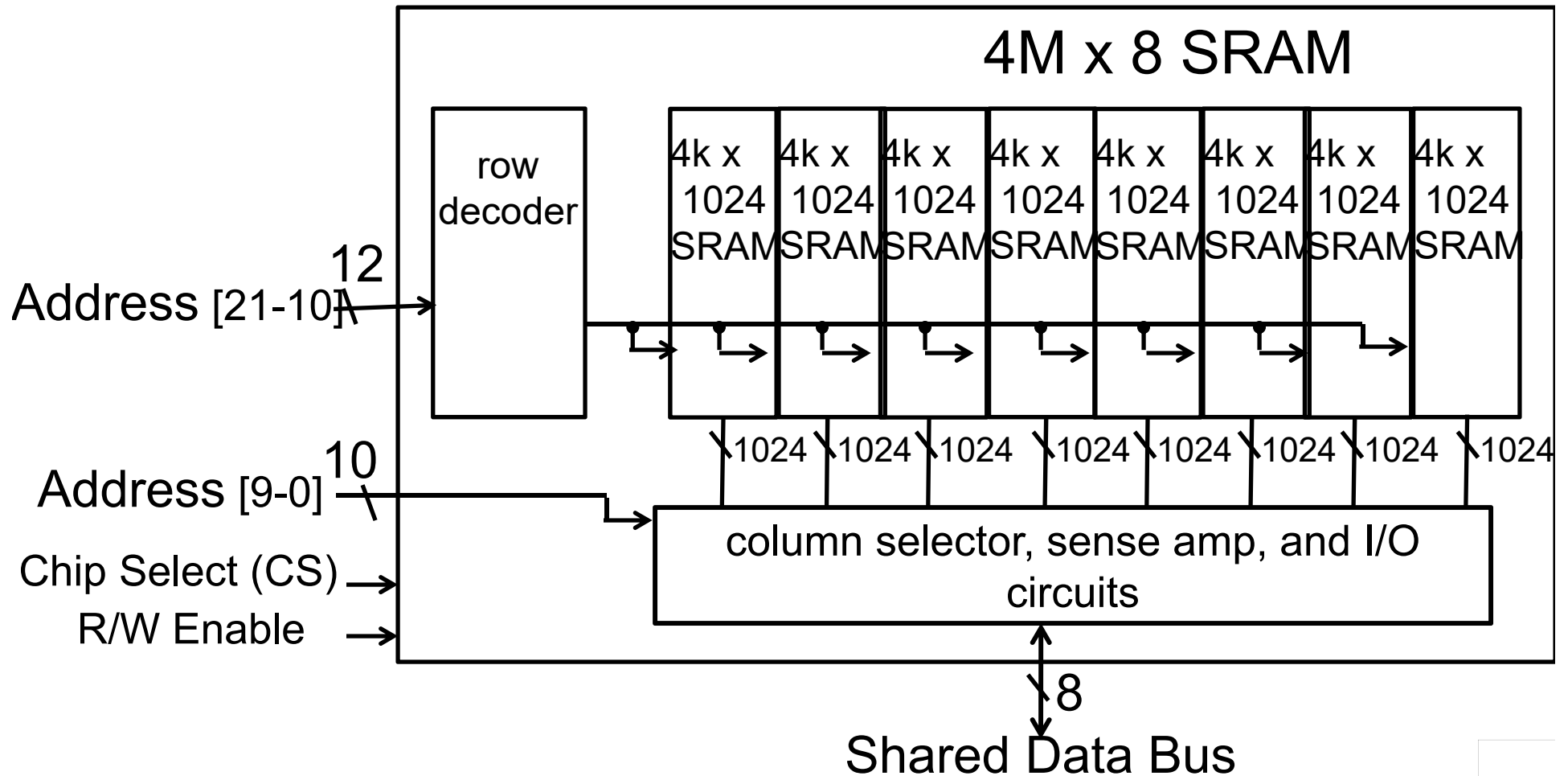E.g. How do we design
a **4M x 8** SRAM Module?



SRAM Modules and Arrays

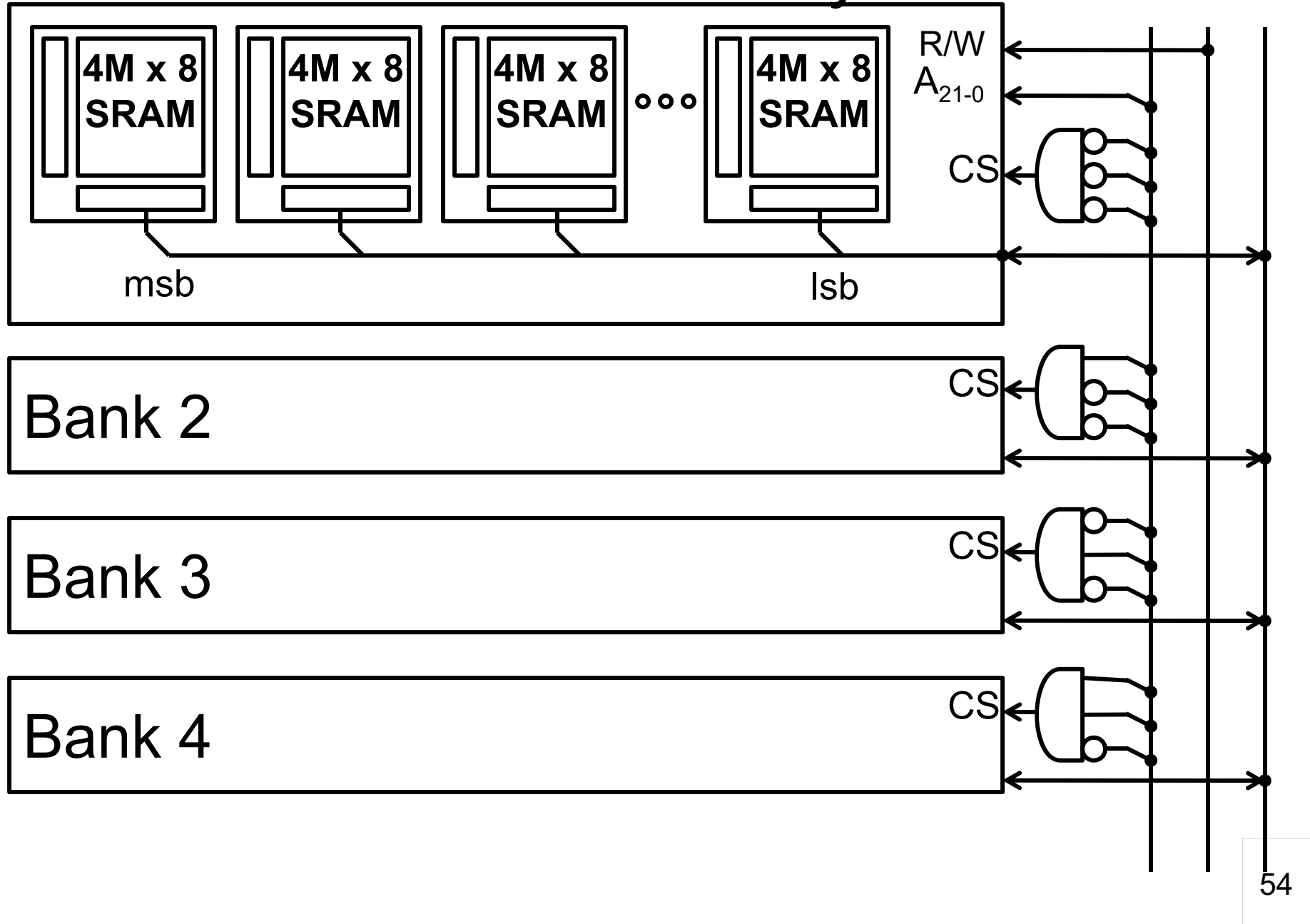

SRAM Summary

SRAM


- A few transistors (~ 6) per cell
- Used for working memory (caches)
- But for even higher density...



Dynamic RAM: DRAM

Dynamic-RAM (DRAM)

- Data values require constant refresh

 


Each cell stores one bit, and requires 1 transistors

Dynamic RAM: DRAM

Dynamic-RAM (DRAM)


- Data values require constant refresh

 

Each cell stores one bit, and requires 1 transistors

Dynamic RAM: DRAM

Dynamic-RAM (DRAM)

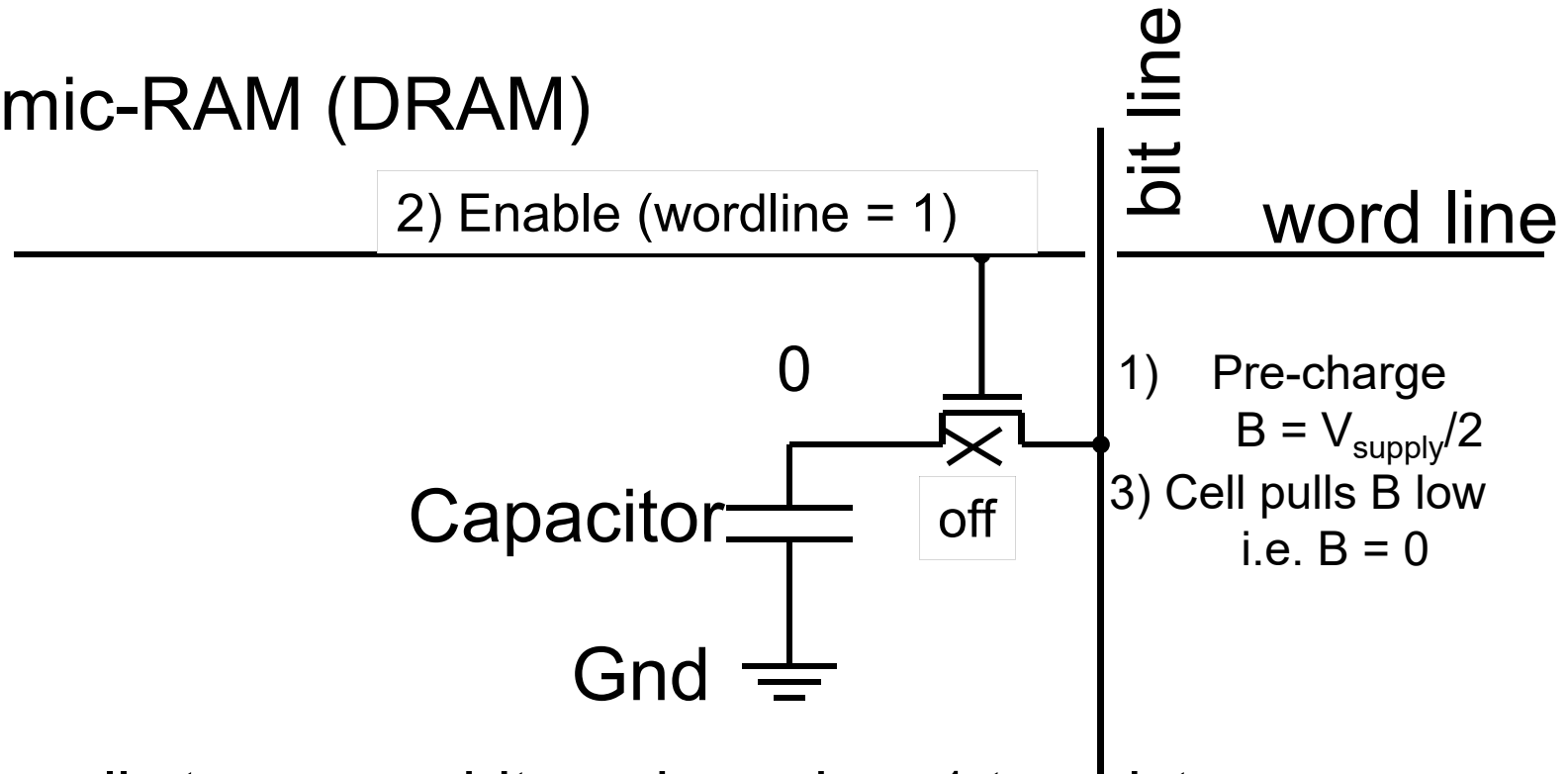


Each cell stores one bit, and requires 1 transistors

Read:

- pre-charge B and \bar{B} to $V_{\text{supply}}/2$
- pull word line high
- cell pulls B low, sense amp detects voltage difference

Dynamic RAM: DRAM

Dynamic-RAM (DRAM)

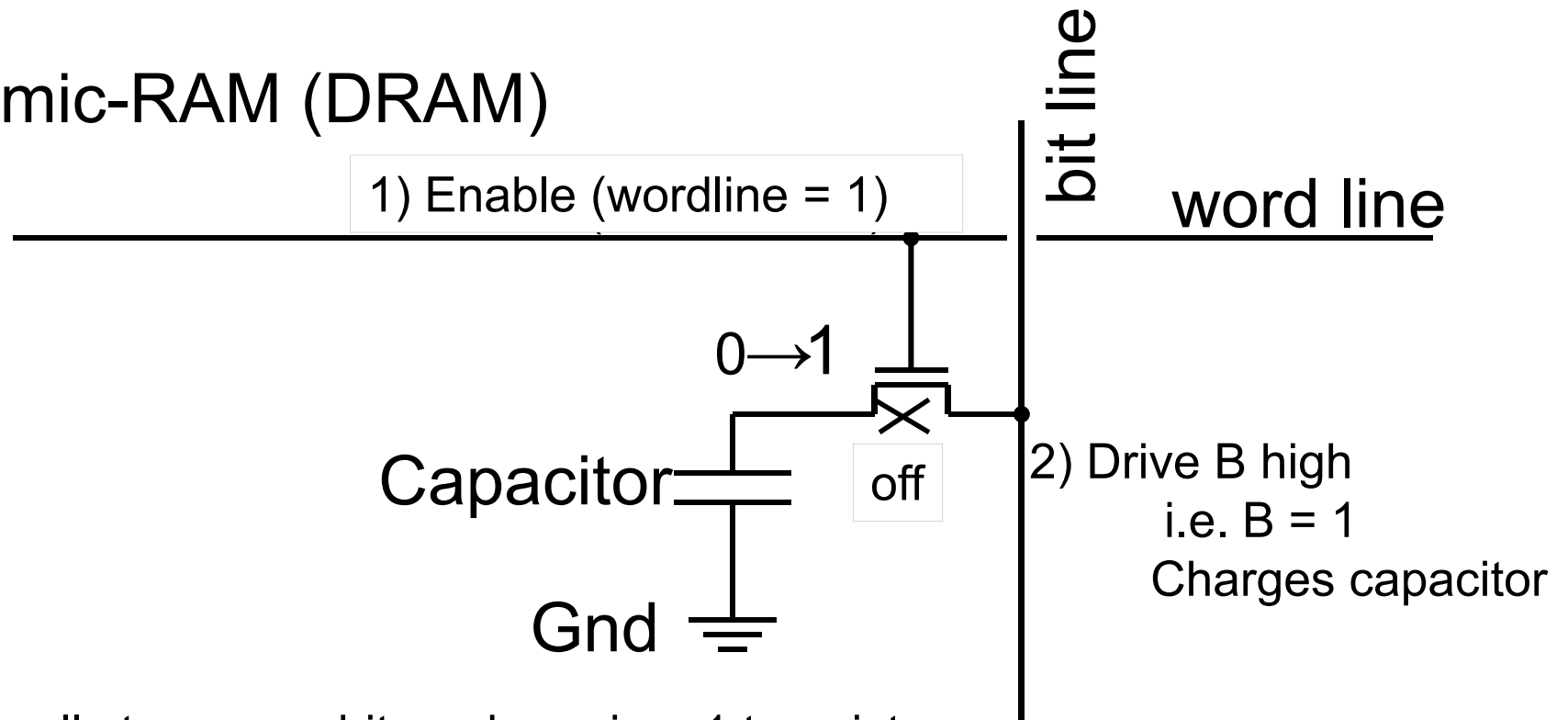

Each cell stores one bit, and requires 1 transistors

Read:

- pre-charge B and \bar{B} to $V_{\text{supply}}/2$
- pull word line high
- cell pulls B low, sense amp detects voltage difference

Write:

- pull word line high
- drive B charges capacitor

DRAM vs. SRAM

Single transistor vs. many gates

- Denser, cheaper (\$30/1GB vs. \$30/2MB)
- But more complicated, and has analog sensing

Also needs refresh

- Read and write back...
- ...every few milliseconds
- Organized in 2D grid, so can do rows at a time
- Chip can do refresh internally

Hence... slower and energy inefficient



Memory

Register File tradeoffs


- + Very fast (a few gate delays for both read and write)
- + Adding extra ports is straightforward
- Expensive, doesn't scale
- Volatile

Volatile Memory alternatives: SRAM, DRAM, ...

- Slower
- + Cheaper, and scales well
- Volatile

Non-Volatile Memory (NV-RAM): Flash, EEPROM, ...

 - + Scales well
- Limited lifetime; degrades after 100000 to 1M writes



Summary

We now have enough building blocks to build machines that can perform non-trivial computational tasks

Register File: Tens of words of working memory

SRAM: Millions of words of working memory

DRAM: Billions of words of working memory

NVRAM: long term storage

(usb fob, solid state disks, BIOS, ...)

Next time we will build a simple processor!

