


# Memory

**Prof. Hakim Weatherspoon**

**CS 3410**

Computer Science

Cornell University

 


**Cornell CIS**  
COMPUTING AND INFORMATION SCIENCE

[Weatherspoon, Bala, Bracy, and Sirer]
 
# Announcements

- Level Up (optional enrichment)
  - Teaches CS students tools and skills needed in their coursework as well as their career, such as Git, Bash Programming, study strategies, ethics in CS, and even applying to graduate school.
  - Thursdays at 7-8pm in 310 Gates Hall, starting this week
  - <http://www.cs.cornell.edu/courses/cs3110/2019sp/levelup/>



# Announcements

Make sure you are


- Registered for class, can access CMS
  - Have a Section you can go to.
  - *Lab Sections are required.*
- 
- Project partners are required for projects starting w/ project 2
    - Project partners will be assigned (from the same lab section, if possible)

# Announcements

- Make sure to go to [your](#) Lab Section this week
- Completed **Proj1** due Friday, Feb 15th
- Note, a Design Document is due when you submit Proj1 final circuit
- Work **alone**

**BUT** use your resources

 - Lab Section, Piazza.com, Office Hours
- Class notes, book, Sections, CSUGLab



# Announcements

## Check online syllabus/schedule


- <http://www.cs.cornell.edu/Courses/CS3410/2019sp/schedule>
- Slides and Reading for lectures
- Office Hours
- ***Pictures of all TAs***
- Project and Reading Assignments
- **Dates to keep in Mind**
  - Prelims: Tue Mar 5th and Thur May 2nd
  - ***Proj 1: Due next Friday, Feb 15th***
  - Proj3: Due before Spring break
  - Final Project: May 16th

Schedule is subject to change


# Goals for today
 
## Memory

- CPU: Register Files (i.e. Memory w/in the CPU)
- Scaling Memory: Tri-state devices
- Cache: SRAM (Static RAM—random access memory)
- Memory: DRAM (Dynamic RAM)




# Last time: How do we store one bit

 

D Flip Flop stores 1 bit

 
# Goal for today

How do we store results from ALU computations?






# Big Picture: Building a Processor

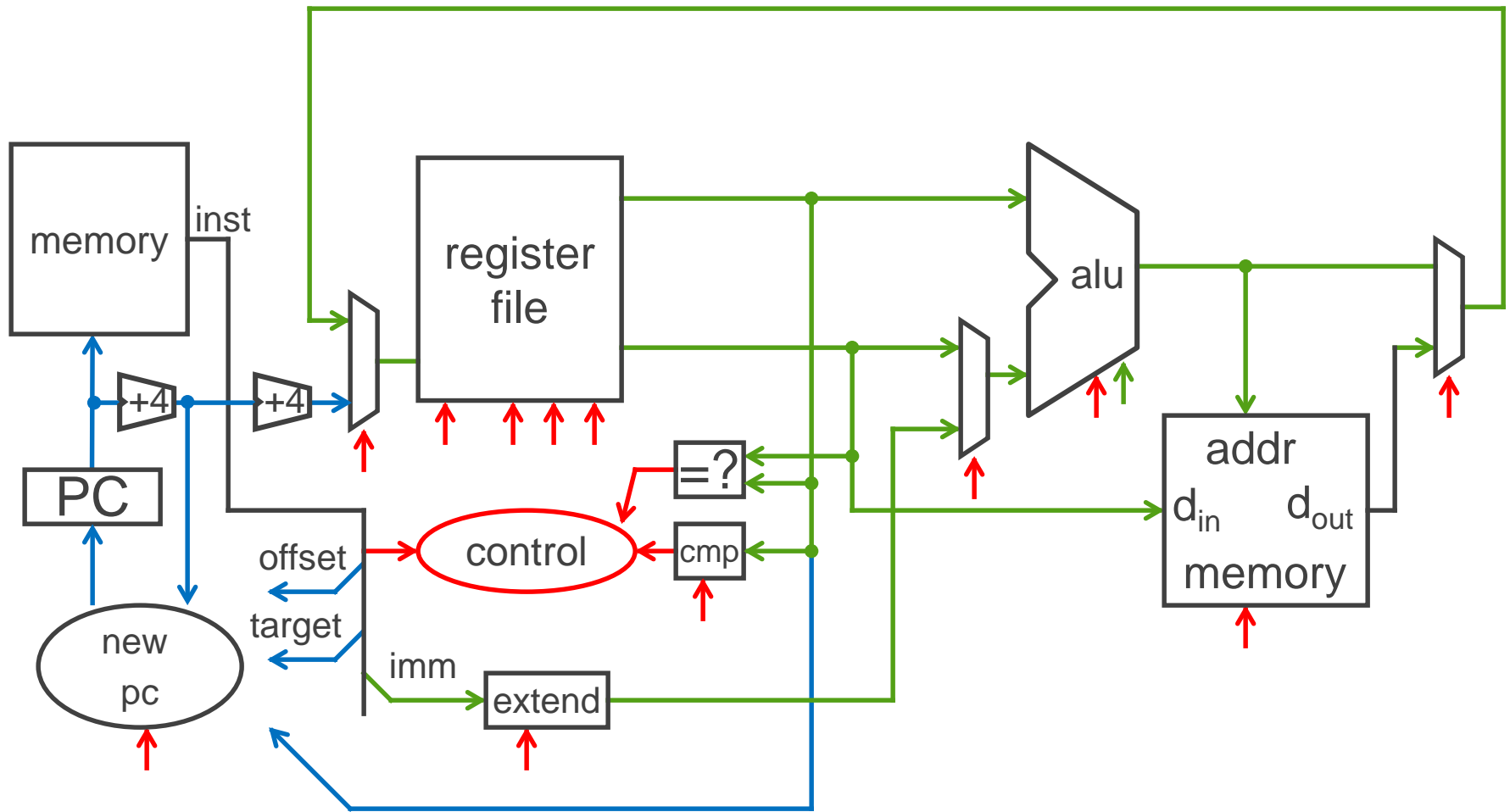

A Single cycle processor

# Big Picture: Building a Processor

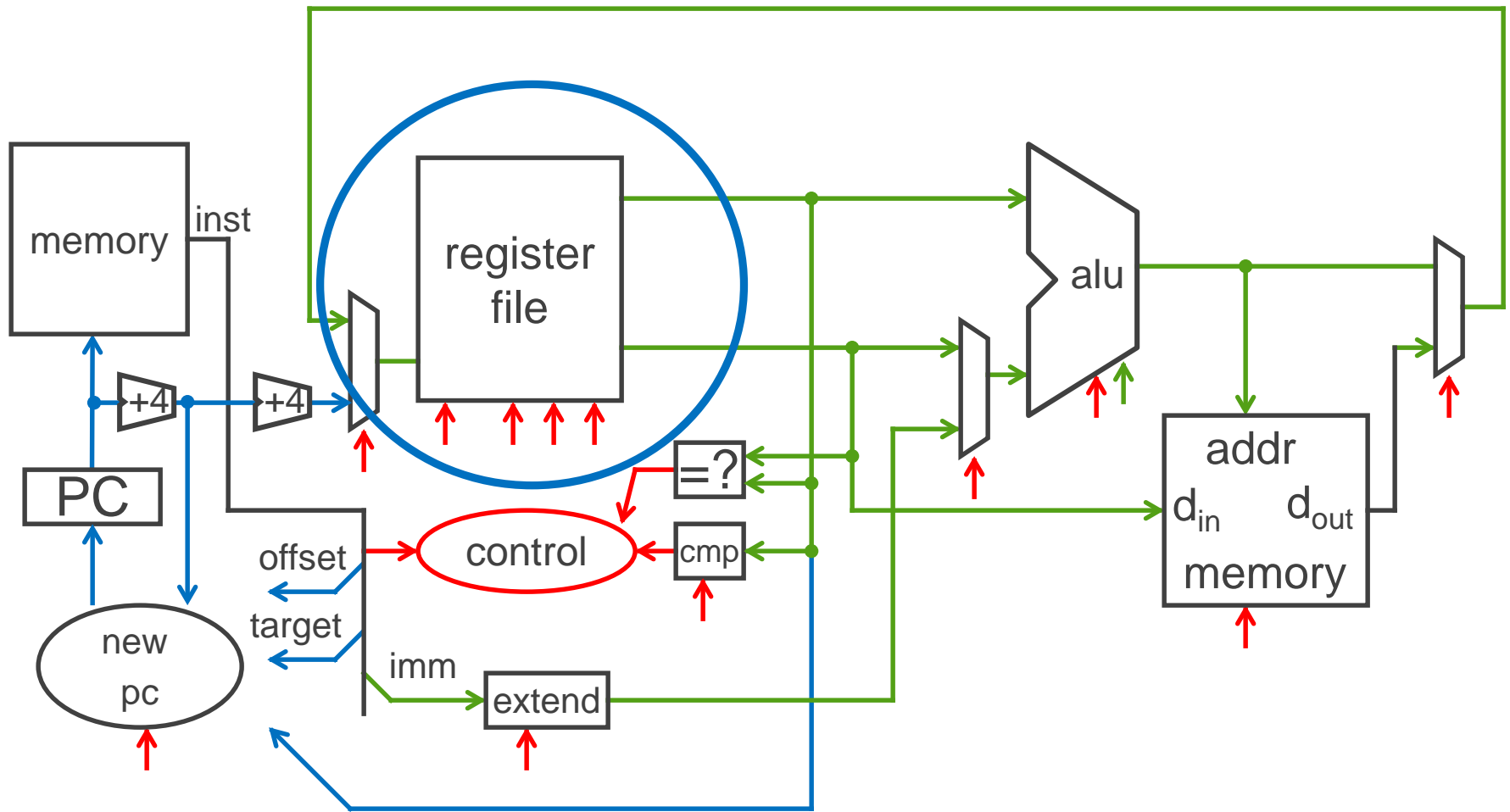

A Single cycle processor


# Goal for today

How do we store results from ALU computations?

How do we use stored results in subsequent operations?
 
## Register File


How does a Register File work? How do we design it?




# Register File
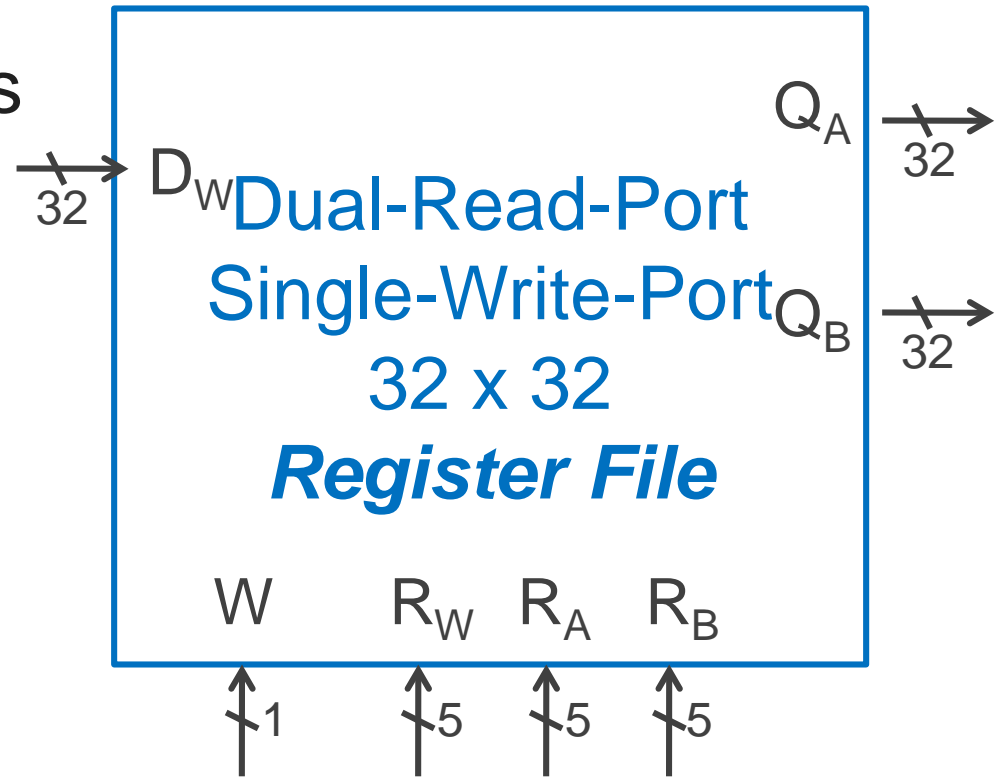
## Register File

- N read/write registers
- Indexed by register number




# Register File

 

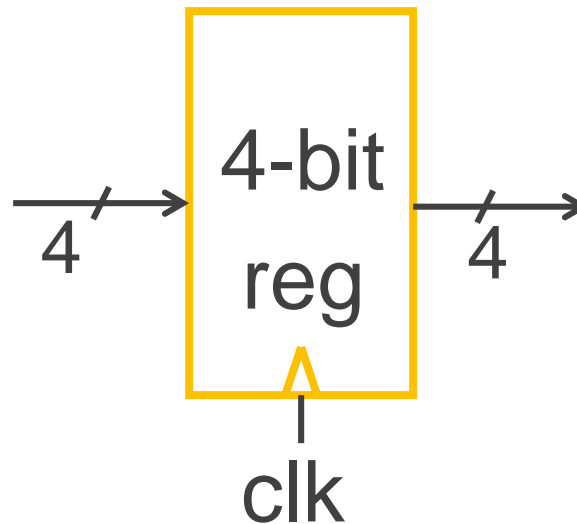
## Recall: Register

- D flip-flops in parallel
- shared clock
- extra clocked inputs: write\_enable, reset, ...




# Register File

 
 
## Recall: Register


- D flip-flops in parallel
- shared clock
- extra clocked inputs: write\_enable, reset, ...



# Register File
 
## Register File

- N read/write registers
- Indexed by register number




addi **x1**, x0, 10

**00001**

How to write to **one** register in the register file?

# 🏠 Aside: 3-to-8 decoder truth table & circuit

i2	i1	i0	o0	o1	o2	o3	o4	o5	o6	o7
0	0	0								
0	0	1								
0	1	0								
0	1	1								
1	0	0								
1	0	1								
1	1	0								
1	1	1								

 




# Register File

## Register File

- N read/write registers
- Indexed by register number

add x1, x0, x5

How to read from two registers?

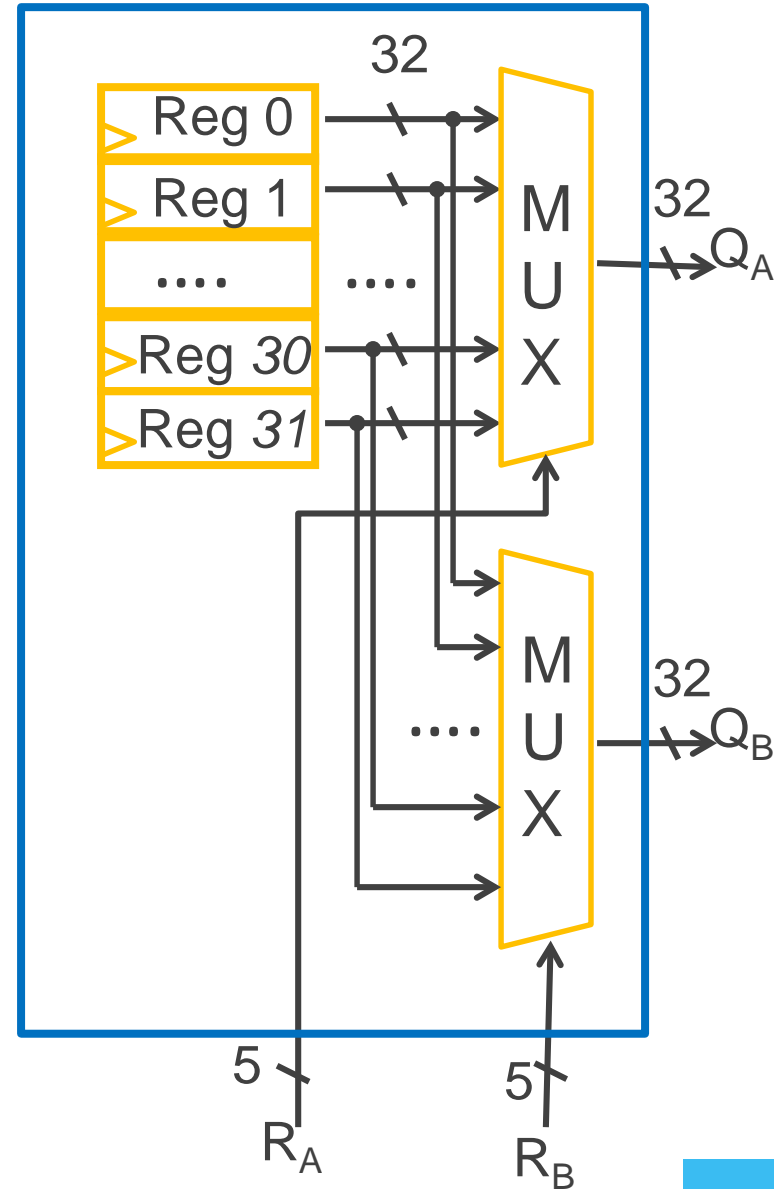


# Register File

## Register File

- N read/write registers
- Indexed by register number
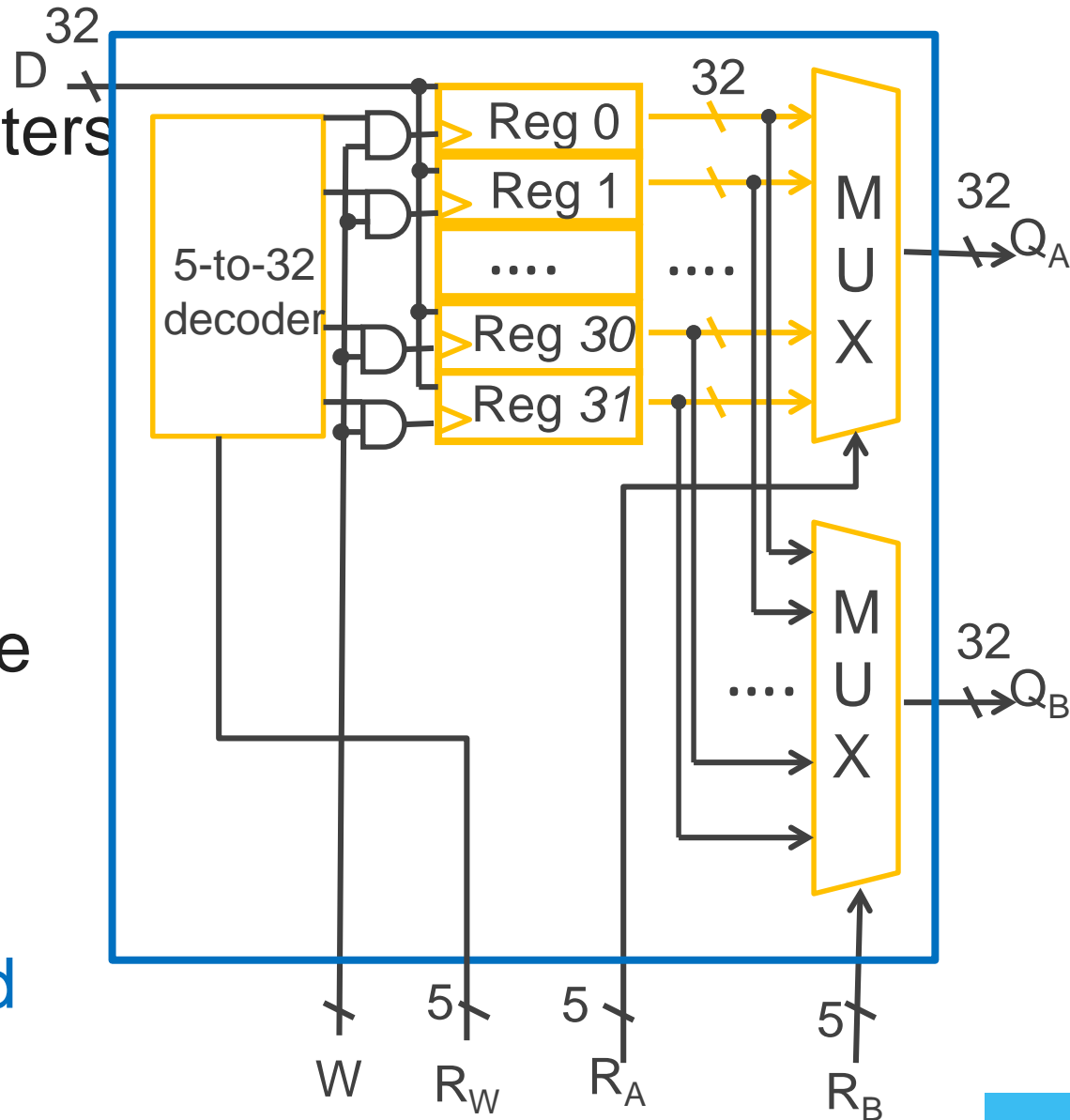
## Implementation:

- D flip flops to store bits
- Decoder for each write port
- Mux for each read port




# Register File

## Register File

- N read/write registers
- Indexed by register number
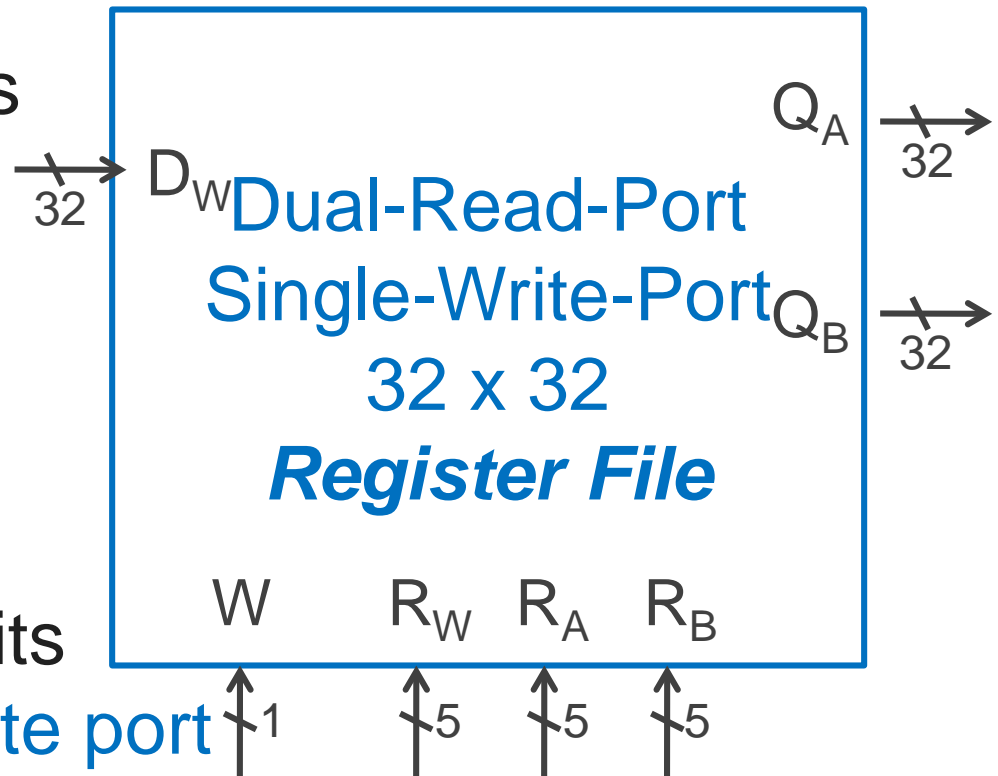
### Implementation:

- D flip flops to store bits
- Decoder for each **write port**
- Mux for each **read port**



# Register File

## Register File

- N read/write registers
- Indexed by register number

What happens if same register read and written during same clock cycle?

## Implementation:

- D flip flops to store bits
- Decoder for each write port
- Mux for each read port

# Tradeoffs


## Register File tradeoffs

- + Very fast (a few gate delays for both read and write)
- + Adding extra ports is straightforward
- Doesn't scale

e.g. 32Mb register file with  
32 bit registers


Need 32x 1M-to-1 multiplexor  
and 32x 20-to-1M decoder

How many logic gates/transistors?

 
 
# Takeway


Register files are very fast storage (only a few gate delays), but does not scale to large memory sizes.



# Goals for today

 
## Memory

- CPU: Register Files (i.e. Memory w/in the CPU)
- Scaling Memory: Tri-state devices
- Cache: SRAM (Static RAM—random access memory)
- Memory: DRAM (Dynamic RAM)



# Next Goal

How do we scale/build larger memories?

 



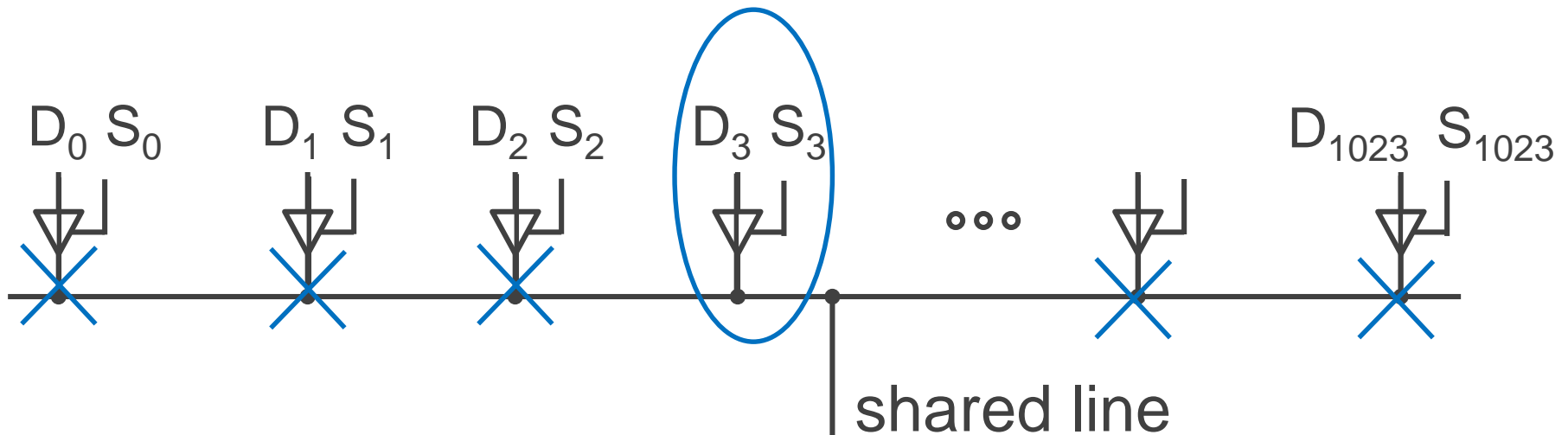
# Building Large Memories

Need a shared **bus** (or shared **bit line**)

- Many FlipFlops/outputs/etc. connected to single wire
- Only one output *drives* the bus at a time




- How do we build such a device?

# Tri-State Devices
 
## Tri-State Buffers

- If enabled ( $E=1$ ), then  $Q = D$
- Otherwise,  $Q$  is not connected ( $z = \text{high impedance}$ )




E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1


# Tri-State Devices
 
## Tri-State Buffers

- If enabled ( $E=1$ ), then  $Q = D$
- Otherwise,  $Q$  is not connected ( $z = \text{high impedance}$ )




E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

 


# Tri-State Devices
 
## Tri-State Buffers

- If enabled ( $E=1$ ), then  $Q = D$
- Otherwise,  $Q$  is not connected ( $z = \text{high impedance}$ )




E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

 

# Tri-State Devices
 
## Tri-State Buffers


- If enabled ( $E=1$ ), then  $Q = D$
- Otherwise,  $Q$  is not connected ( $z = \text{high impedance}$ )



E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

A	B	AND	NAND
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0


A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

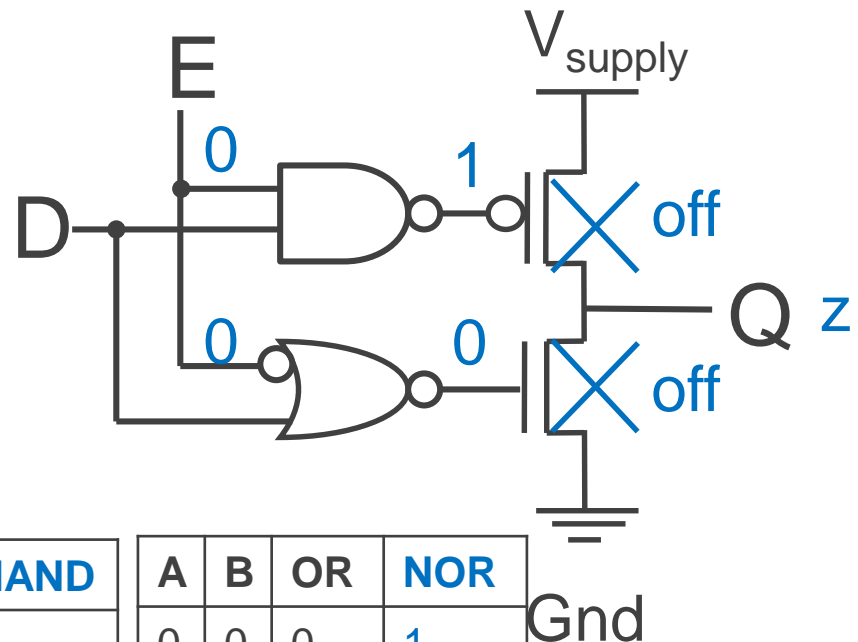

# Tri-State Devices
 
## Tri-State Buffers


- If enabled ( $E=1$ ), then  $Q = D$
- Otherwise,  $Q$  is not connected ( $z = \text{high impedance}$ )



E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

A	B	AND	NAND
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0


A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

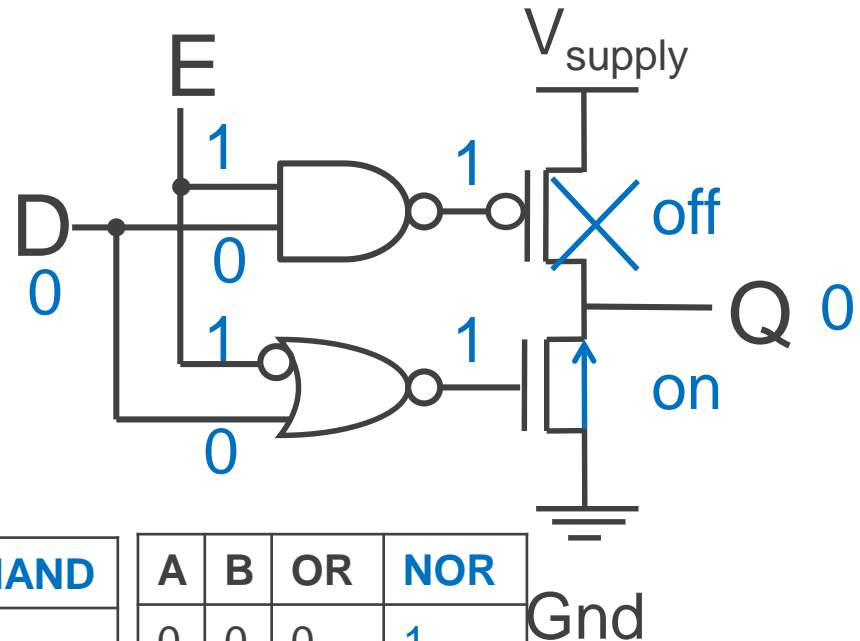

# Tri-State Devices
 
## Tri-State Buffers


- If enabled ( $E=1$ ), then  $Q = D$
- Otherwise,  $Q$  is not connected ( $z = \text{high impedance}$ )




E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

A	B	AND	NAND
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

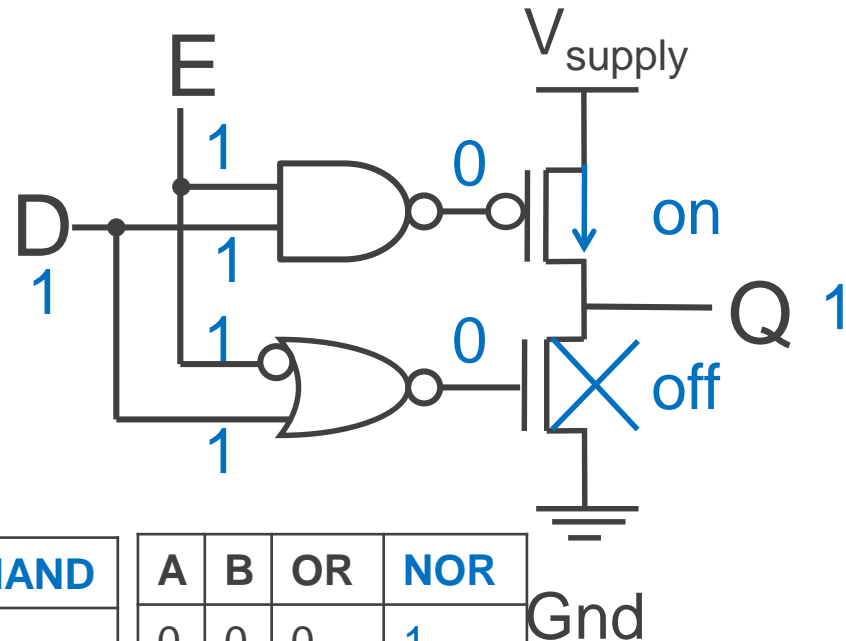

# Shared Bus

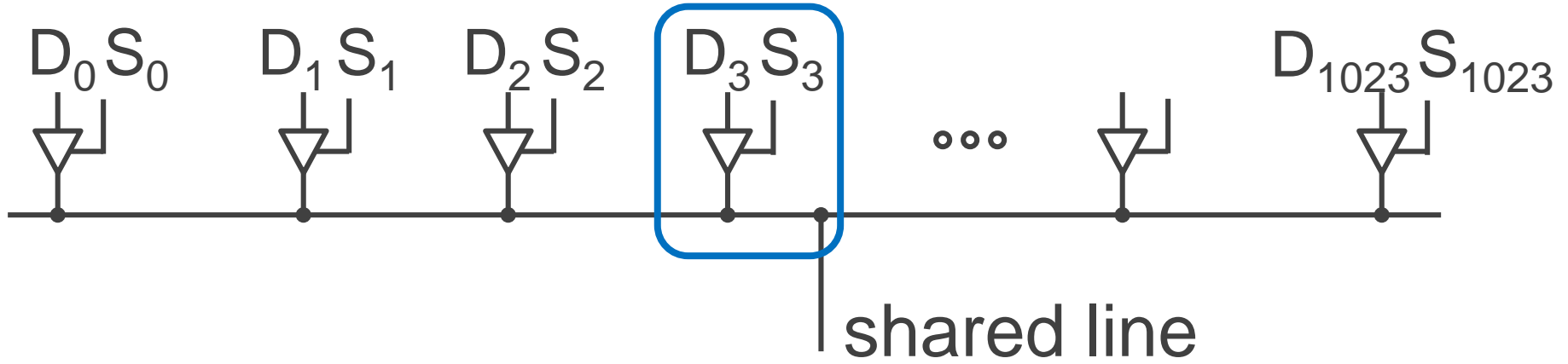



 
# Takeway

Register files are very fast storage (only a few gate delays), but does not scale to large memory sizes.


Tri-state Buffers allow scaling since multiple registers can be connected to a single output, while only one register actually drives the output.



# Goals for today
 
## Memory


- CPU: Register Files (i.e. Memory w/in the CPU)
- Scaling Memory: Tri-state devices
- Cache: SRAM (Static RAM—random access memory)
- Memory: DRAM (Dynamic RAM)


 
# Next Goal


How do we build large memories?

Use similar designs as Tri-state Buffers to connect multiple registers to output line. Only one register will drive output line.


 
# Memory


- Storage Cells + bus
- Inputs: Address, Data (for writes)
- Outputs: Data (for reads)
- Also need R/W signal (not shown)



- $N$  address bits  $\rightarrow 2^N$  words total
- $M$  data bits  $\rightarrow$  each word  $M$  bits

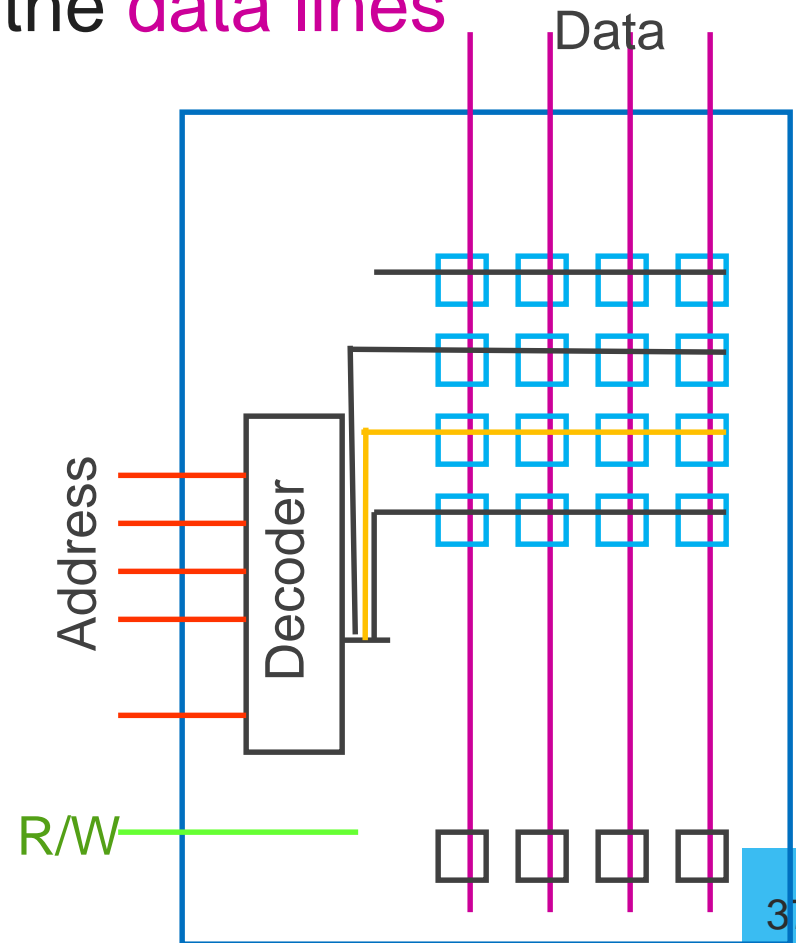
# Memory

- Storage Cells + bus
- Decoder selects a **word line**
- **R/W selector** determines access type
- Word line is then coupled to the **data lines**


 
# Memory


- Storage Cells + bus
- Decoder selects a **word line**
- **R/W selector** determines access type
- Word line is then coupled to the **data lines**


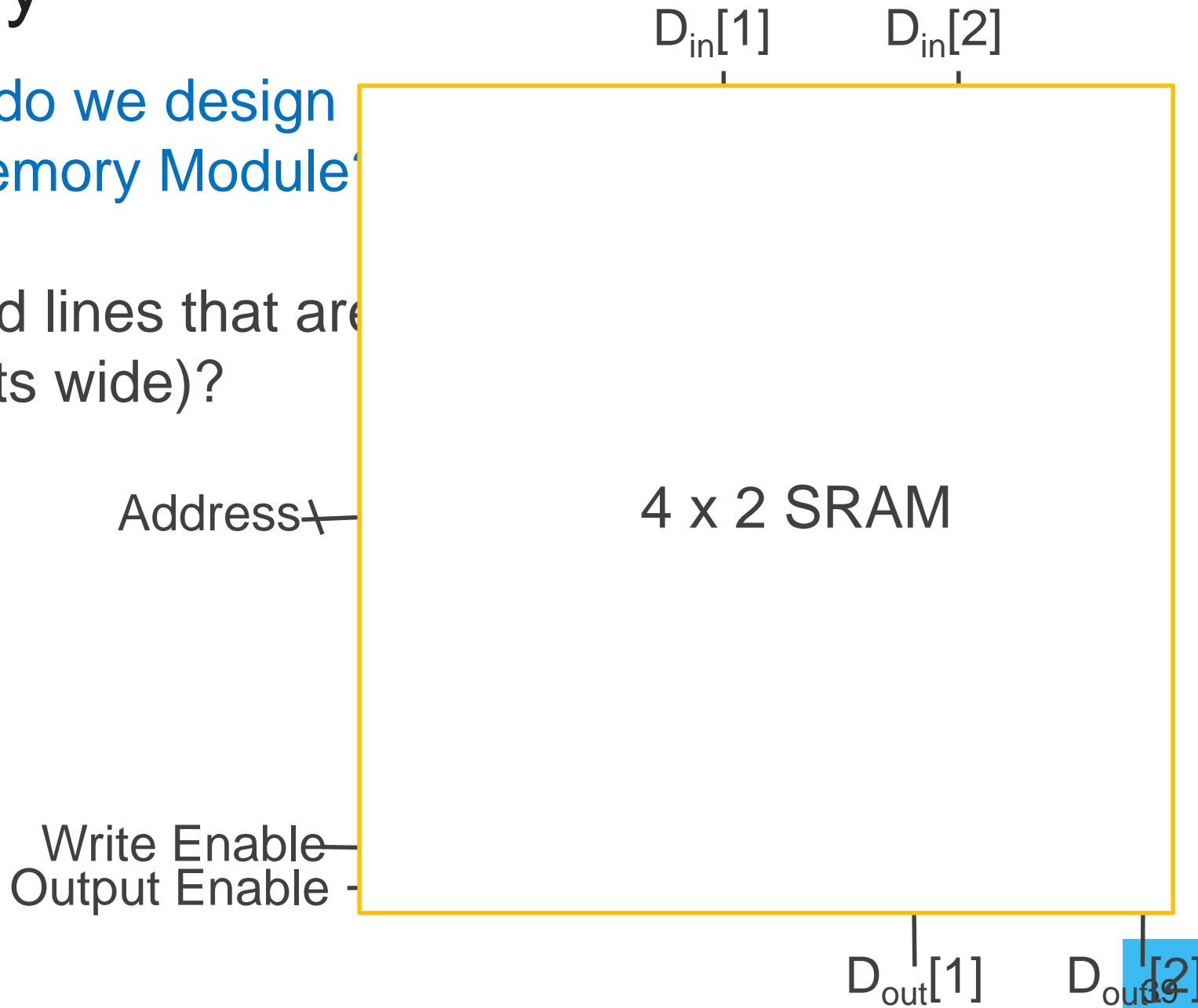
# Memory

E.g. How do we design  
a 4 x 2 Memory Module?


(i.e. 4 word lines that are  
each 2 bits wide)?


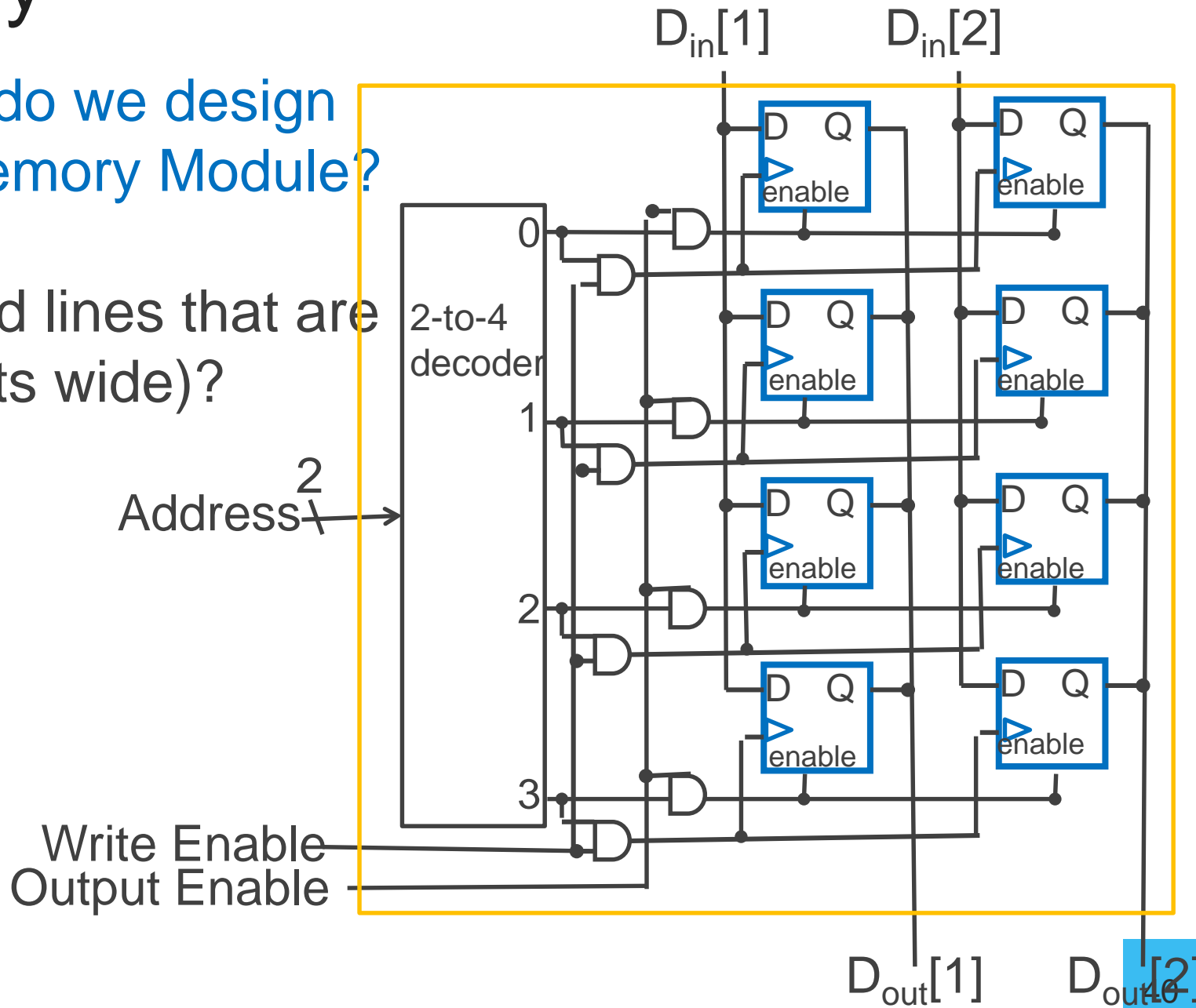
# Memory

E.g. How do we design a 4 x 2 Memory Module?

(i.e. 4 word lines that are each 2 bits wide)?






# Memory

E.g. How do we design a 4 x 2 Memory Module?

(i.e. 4 word lines that are each 2 bits wide)?

Word lines

Write Enable  
Output Enable

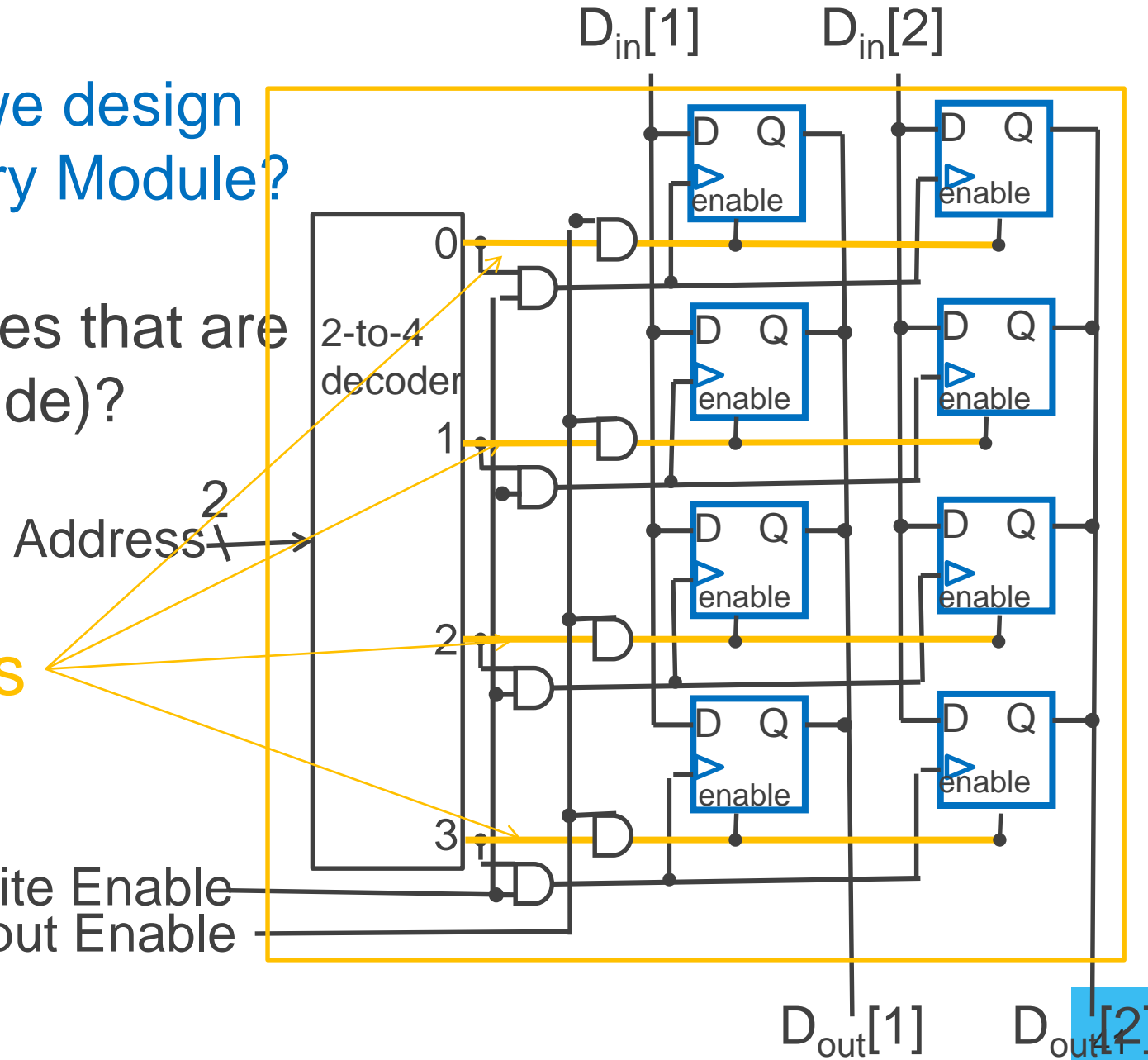


# Memory

E.g. How do we design a 4 x 2 Memory Module?


(i.e. 4 word lines that are each 2 bits wide)?

Bit lines

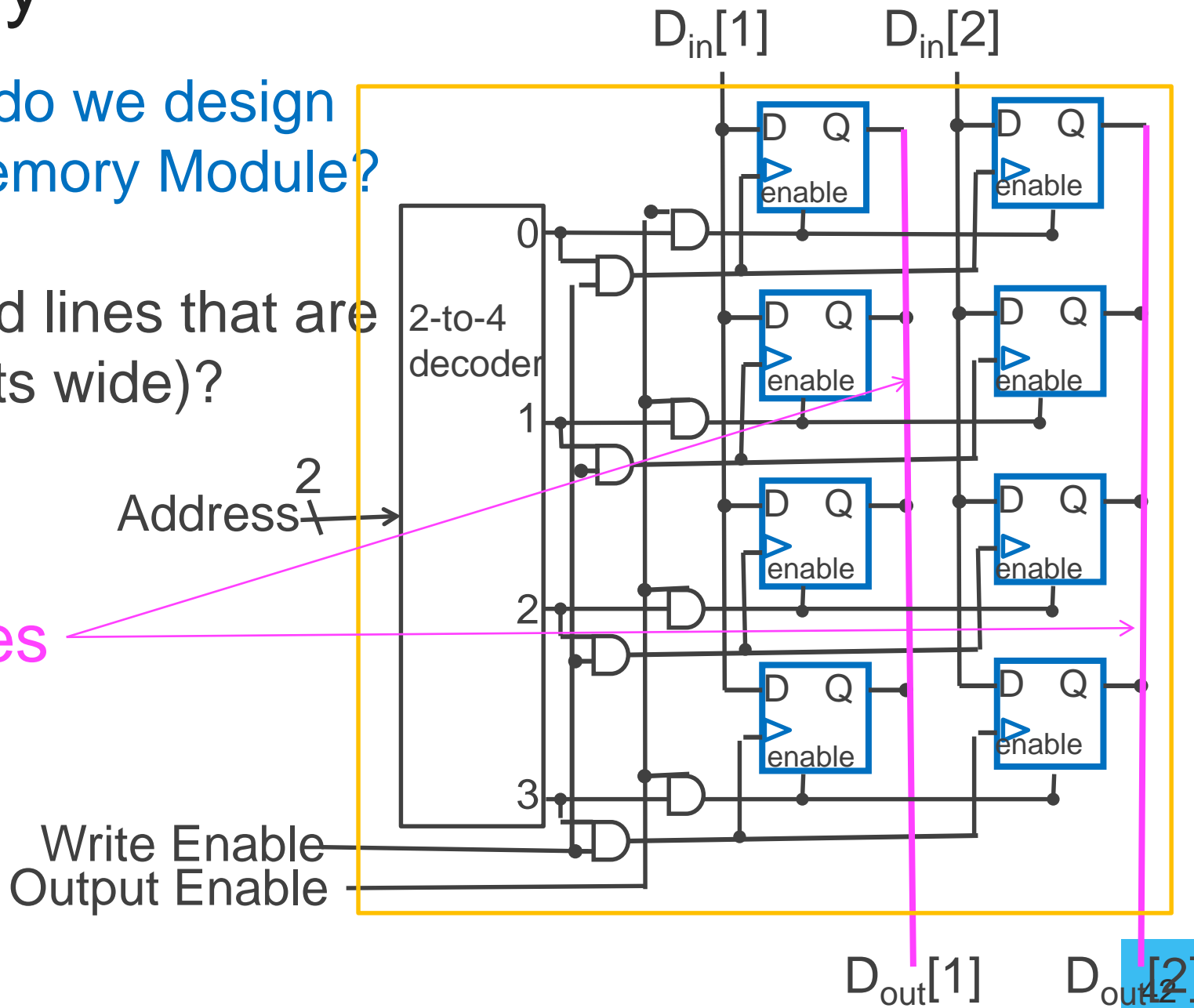

# SRAM Cell


Typical SRAM Cell

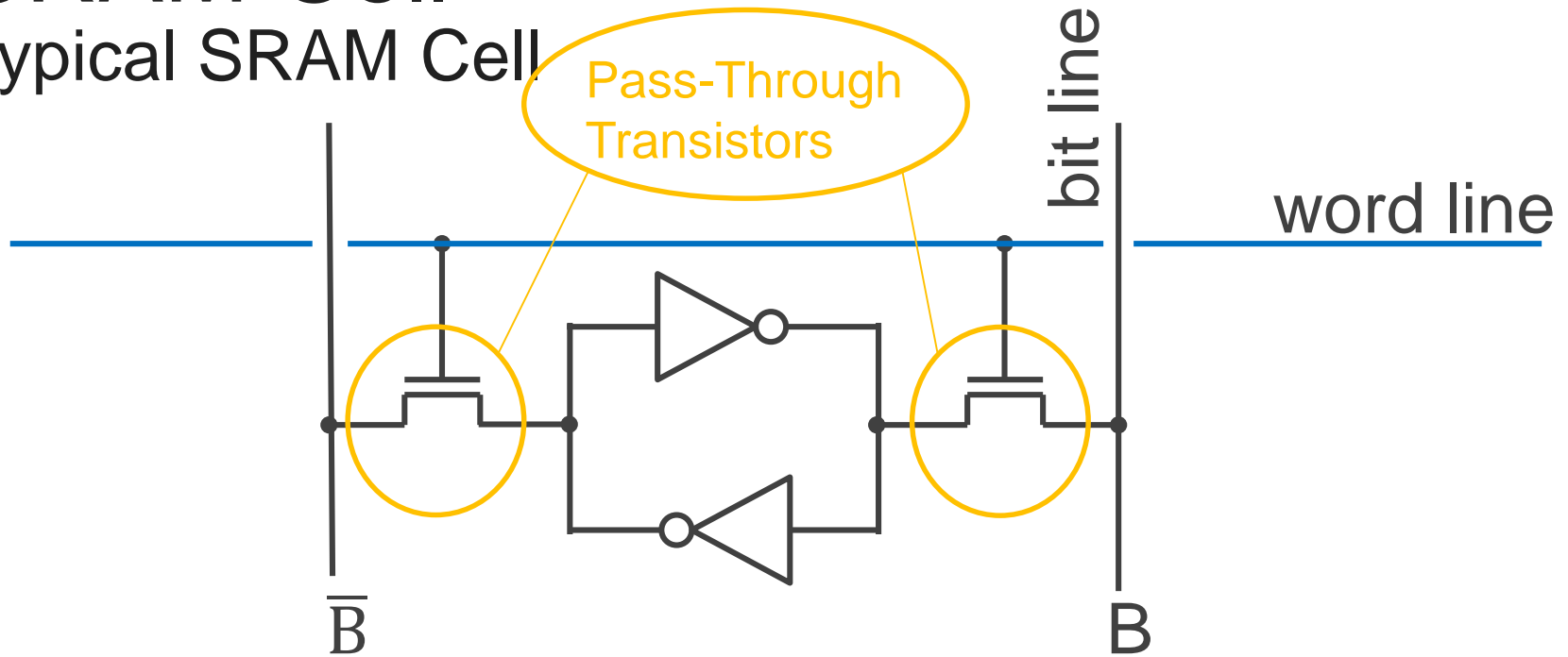

Each cell stores one bit, and requires 4 – 8 transistors (6 is typical)

# SRAM Cell

## Typical SRAM Cell

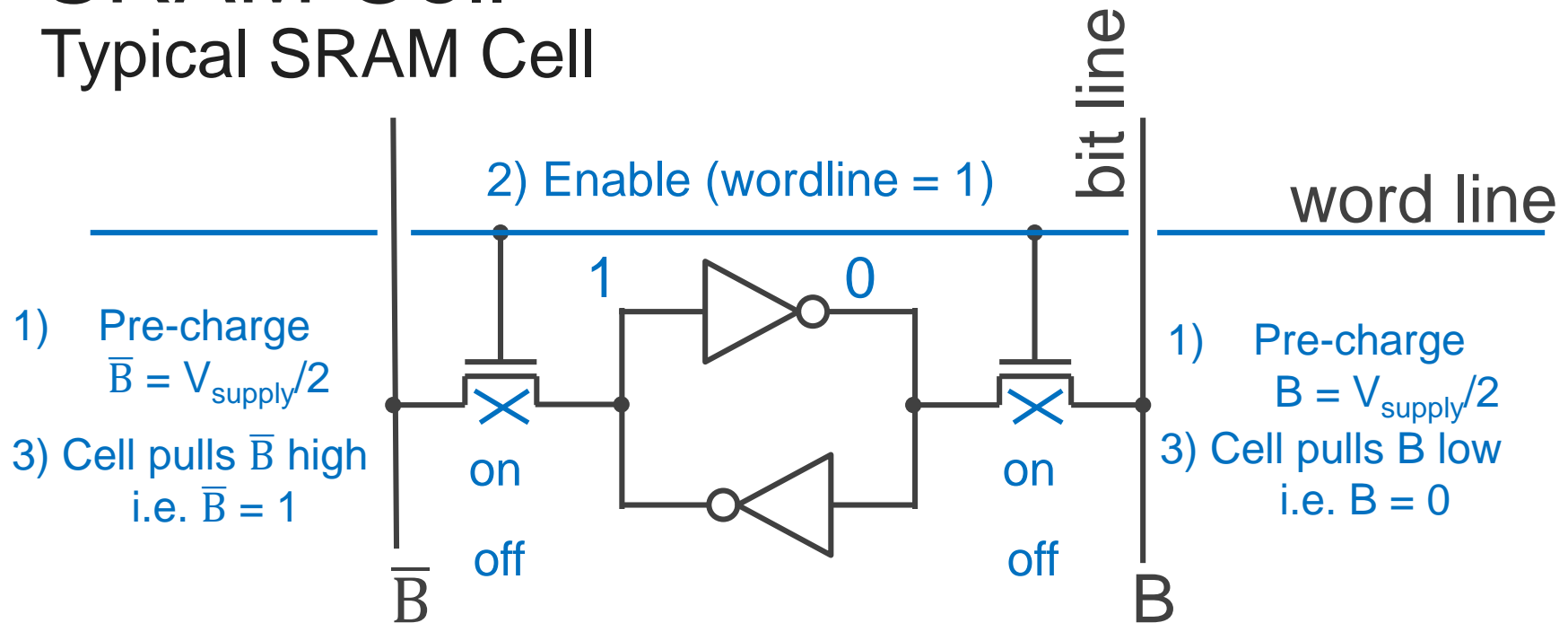


Each cell stores one bit, and requires 4 – 8 transistors (6 is typical)

### Read:

- pre-charge  $B$  and  $\bar{B}$  to  $V_{\text{supply}}/2$
- pull word line high
- cell pulls  $B$  or  $\bar{B}$  low, sense amp detects voltage difference

# SRAM Cell

## Typical SRAM Cell

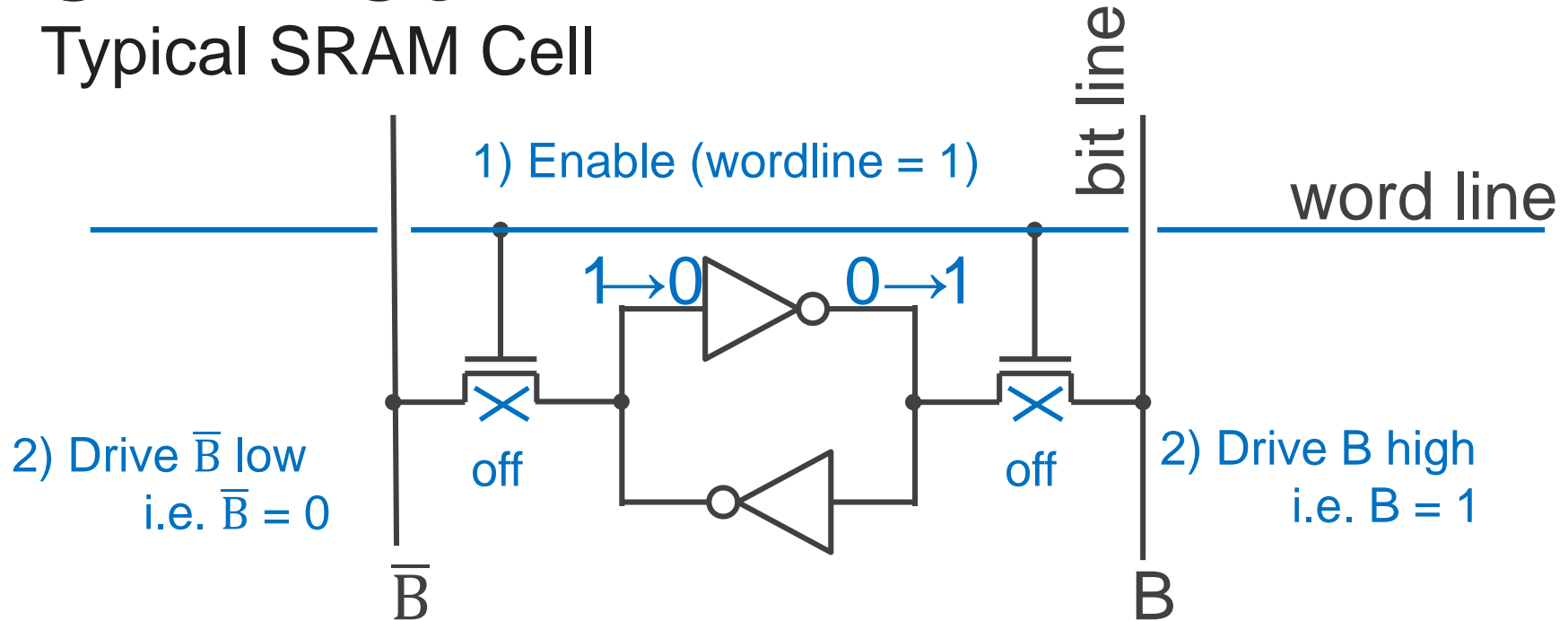

Each cell stores one bit, and requires 4 – 8 transistors (6 is typical)

### Read:

- pre-charge B and  $\bar{B}$  to  $V_{\text{supply}}/2$
- pull word line high
- cell pulls B or  $\bar{B}$  low, sense amp detects voltage difference

### Write:

- pull word line high
- drive


# SRAM

E.g. How do we design a 4 x 2 SRAM Module?

(i.e. 4 word lines that are each 2 bits wide)?

Word lines


Write Enable  
Output Enable

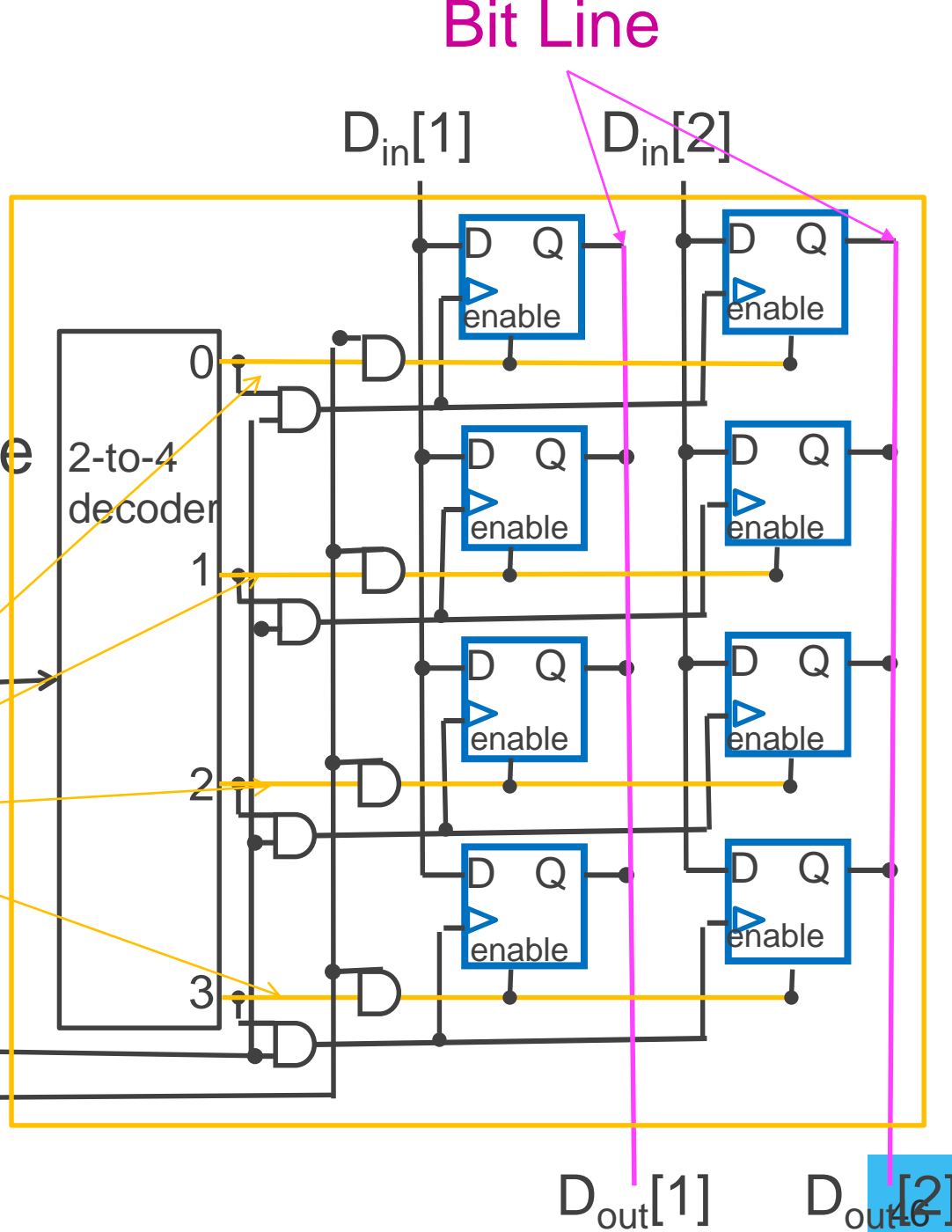
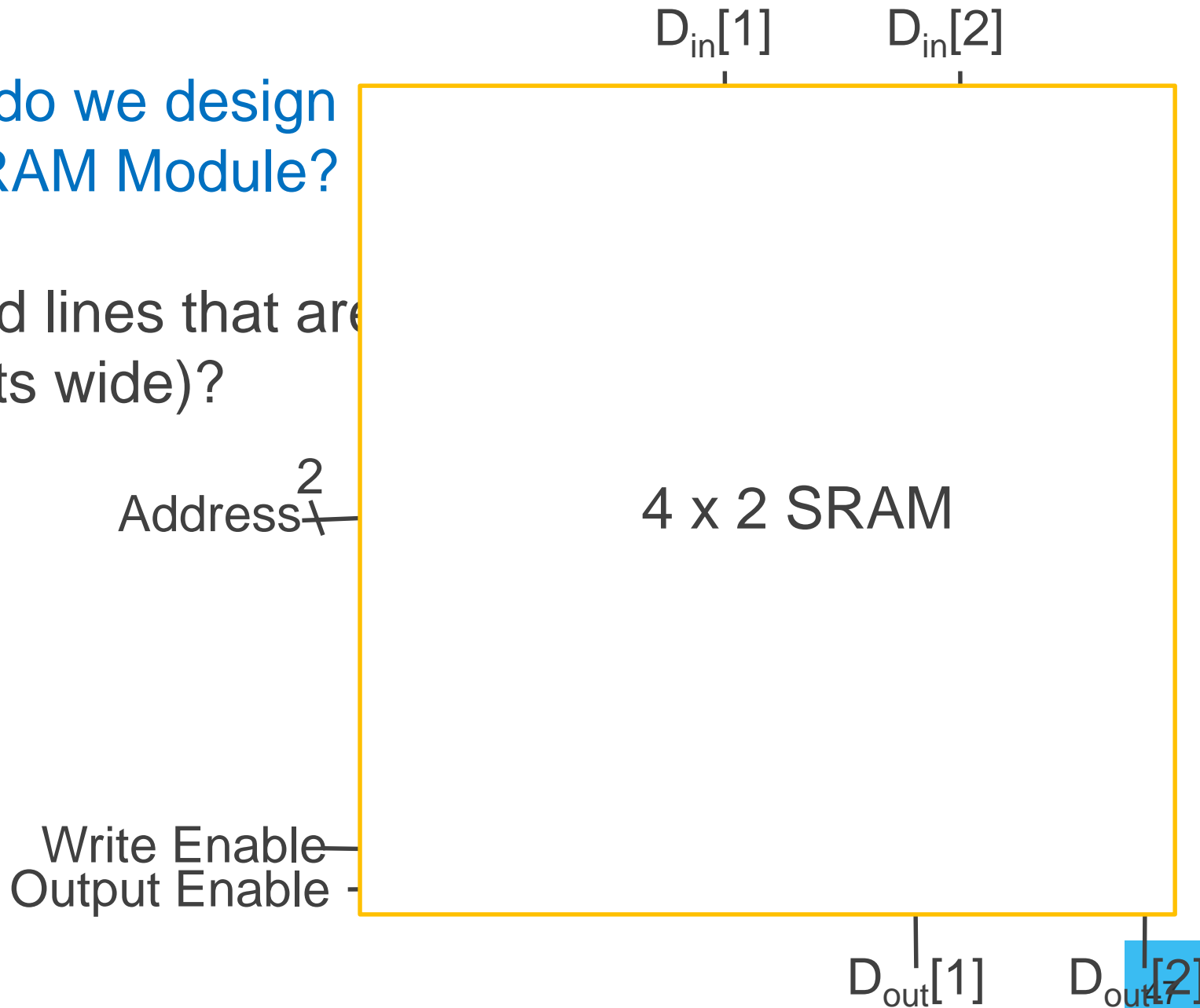
# SRAM

E.g. How do we design a 4 x 2 SRAM Module?


(i.e. 4 word lines that are each 2 bits wide)?


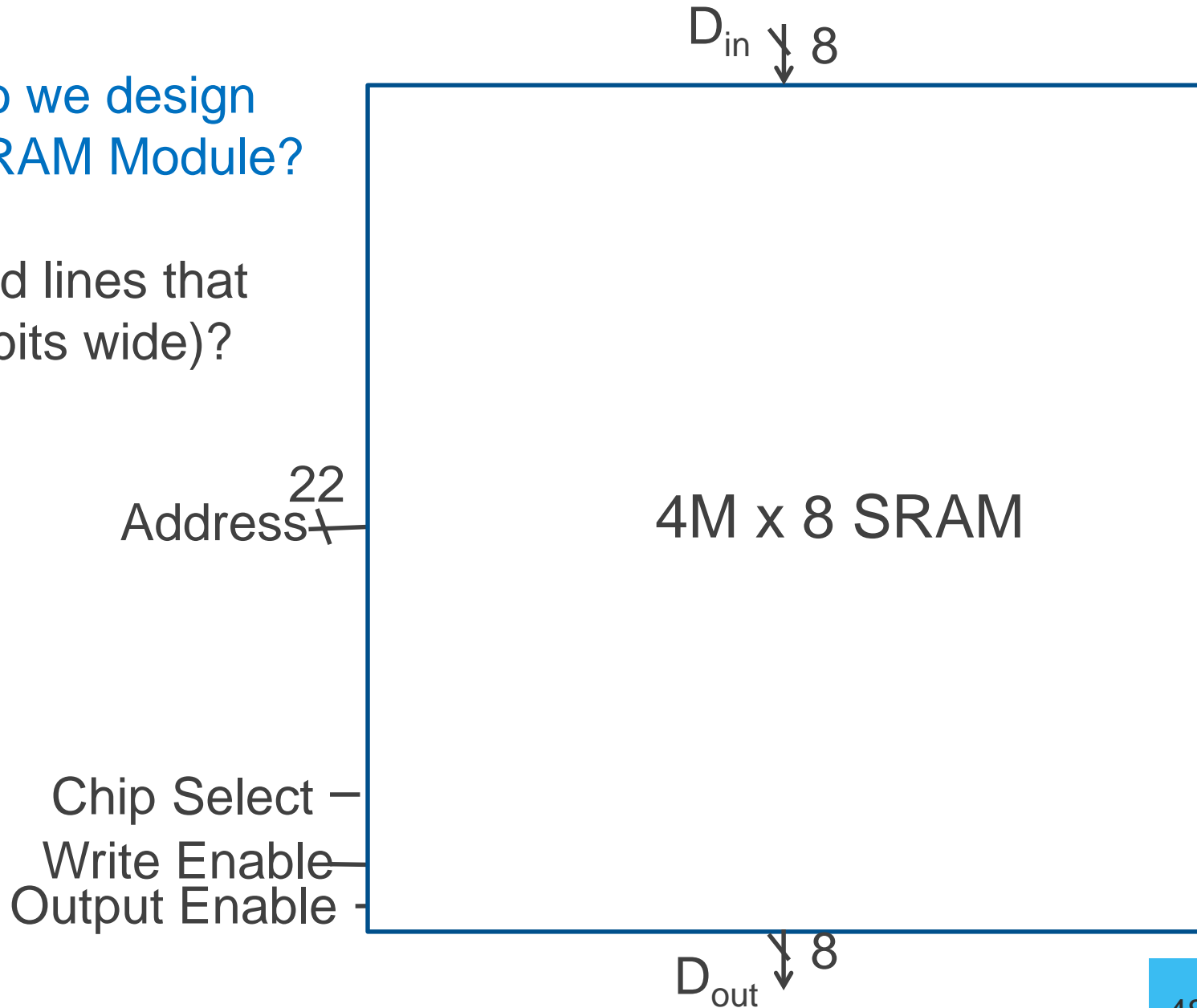
# SRAM

E.g. How do we design  
a **4M x 8** SRAM Module?


(i.e. 4M word lines that  
are each 8 bits wide)?





 
# SRAM

E.g. How do we design a **4M x 8** SRAM Module?



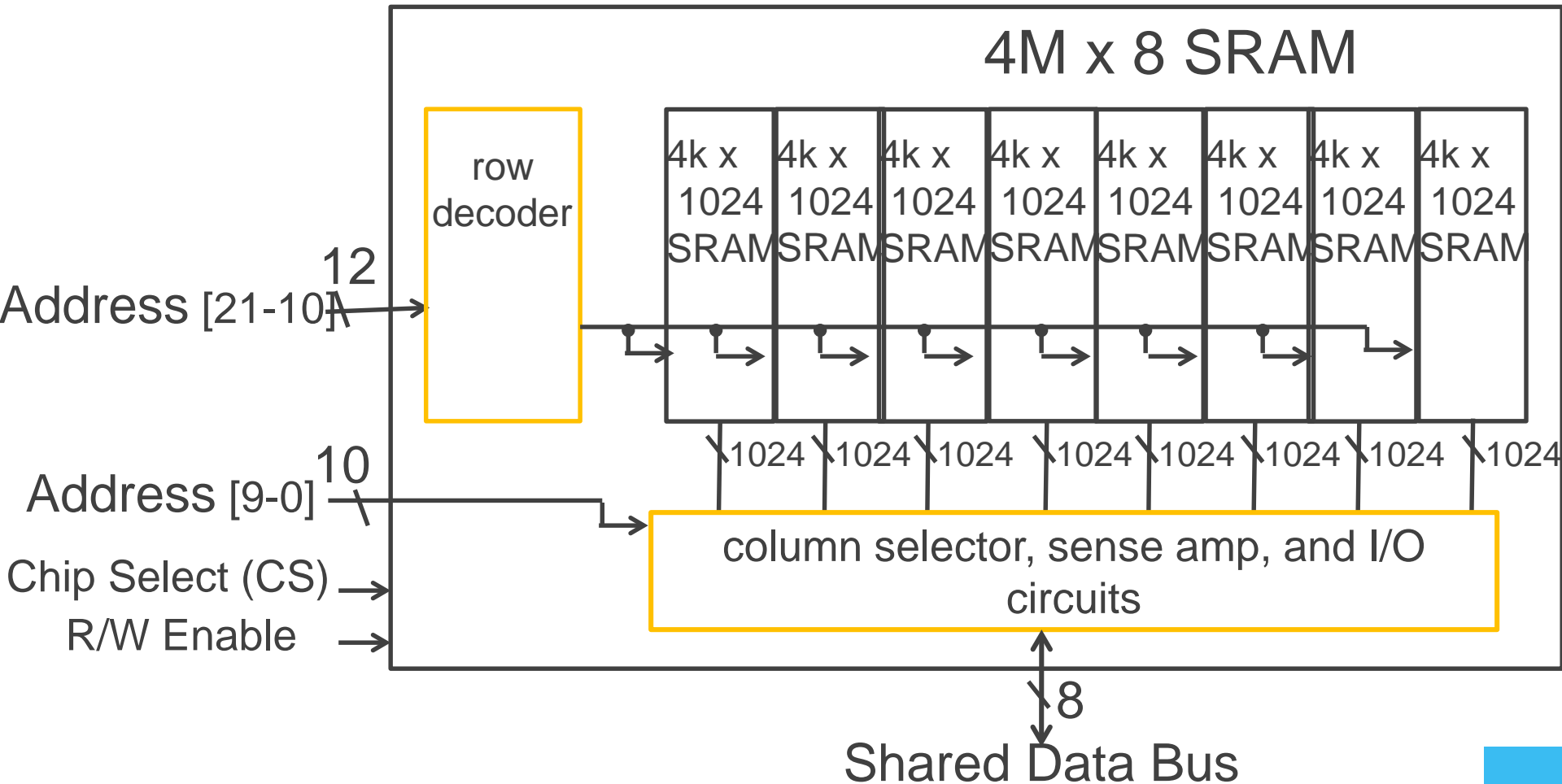
# SRAM

E.g. How do we design  
a **4M x 8** SRAM Module?




# SRAM Modules and Arrays

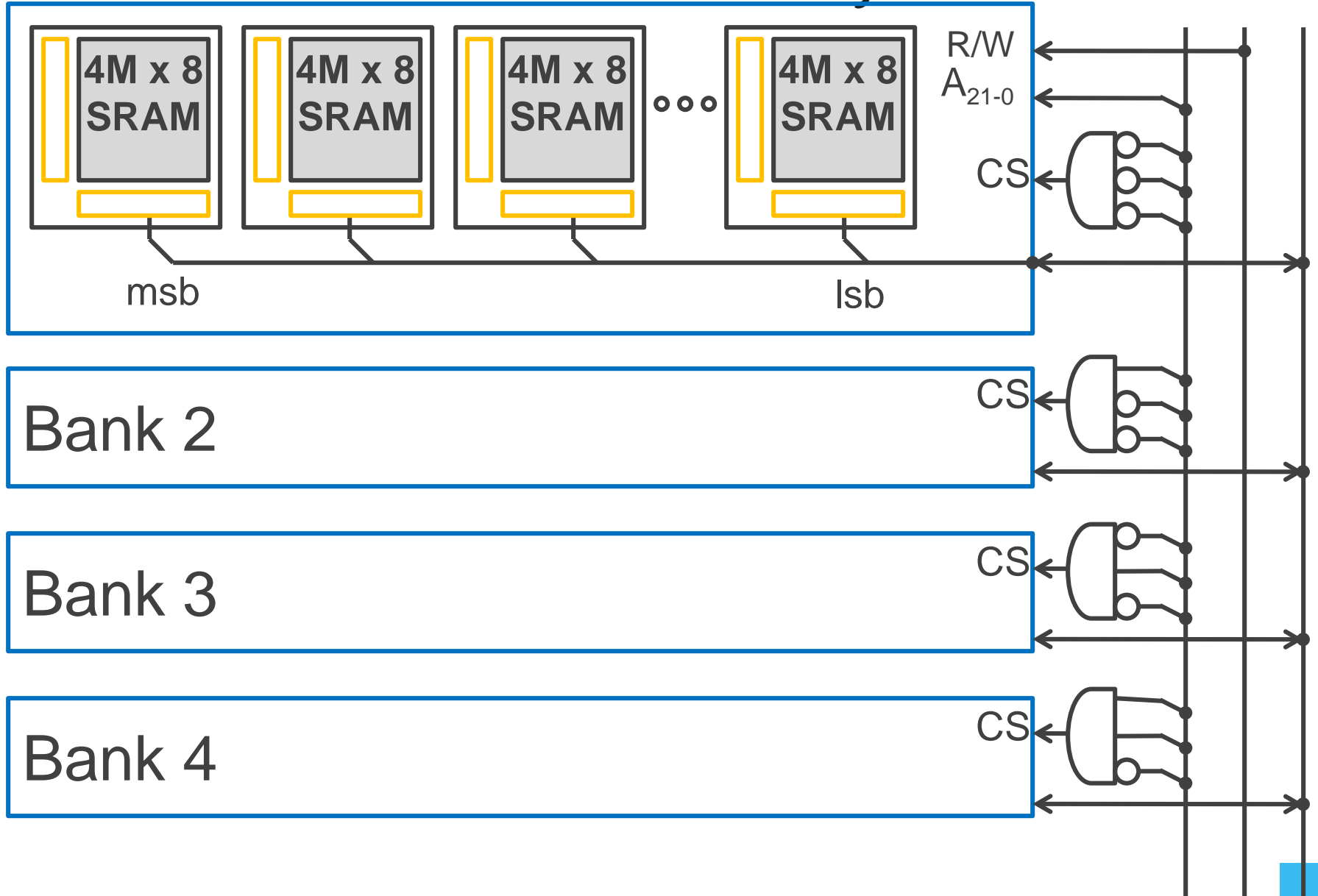

# SRAM Summary
 
## SRAM


- A few transistors ( $\sim 6$ ) per cell
- Used for working memory (caches)
- But for even higher density...



# Dynamic RAM: DRAM

## Dynamic-RAM (DRAM)

- Data values require constant refresh

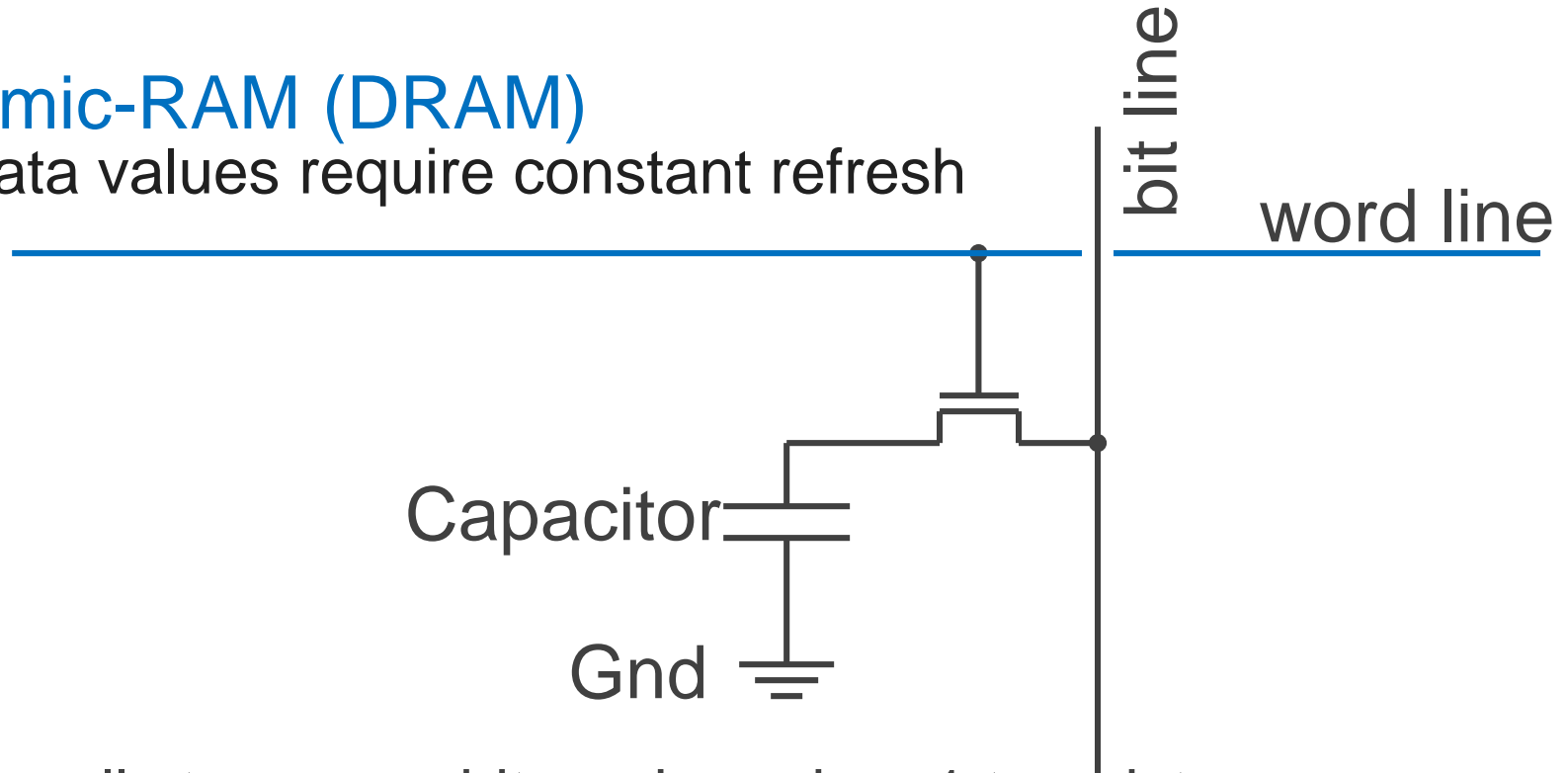


Each cell stores one bit, and requires 1 transistors

# Dynamic RAM: DRAM

## Dynamic-RAM (DRAM)


- Data values require constant refresh

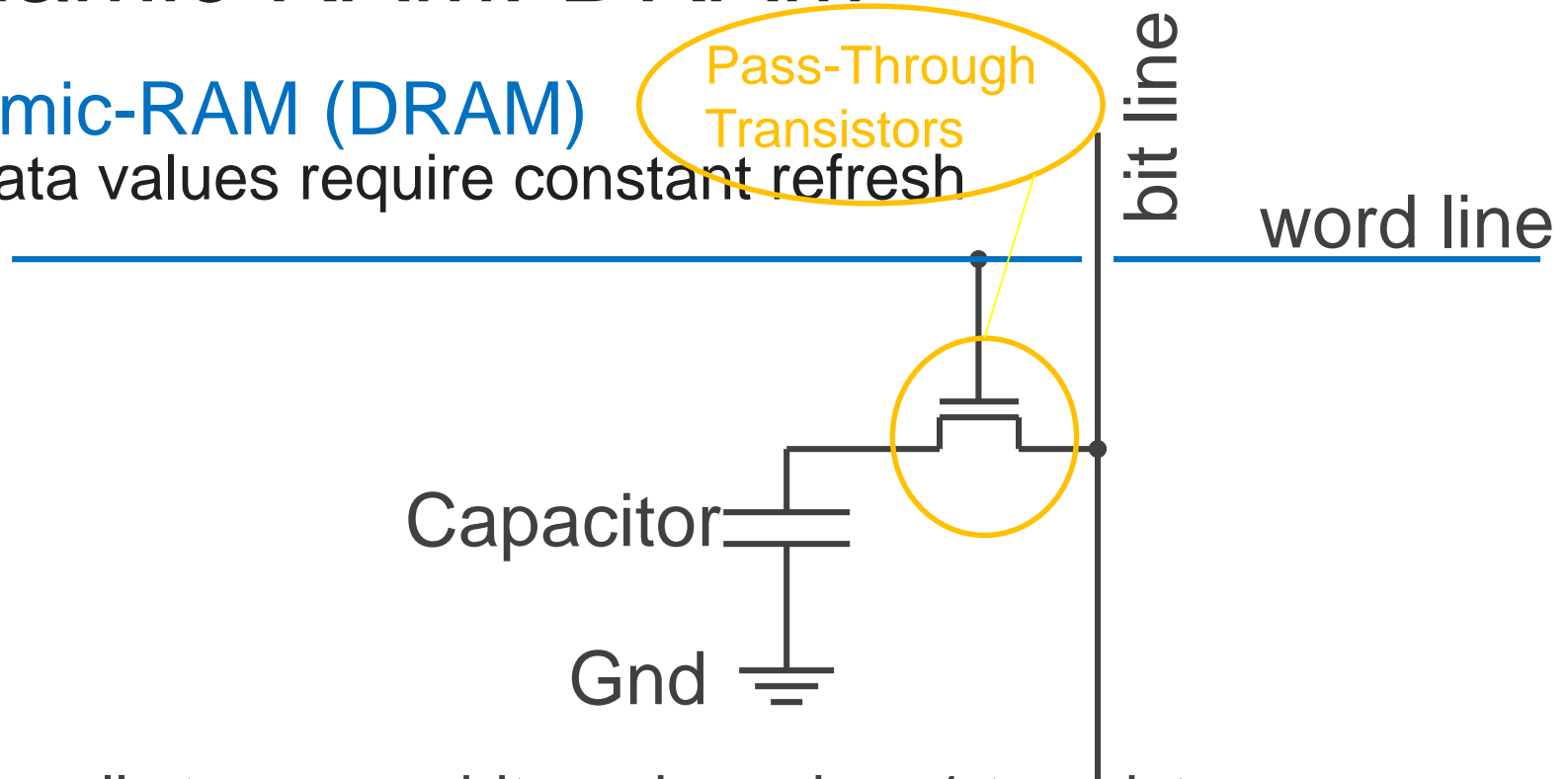

Each cell stores one bit, and requires 1 transistors

# Dynamic RAM: DRAM

## Dynamic-RAM (DRAM)

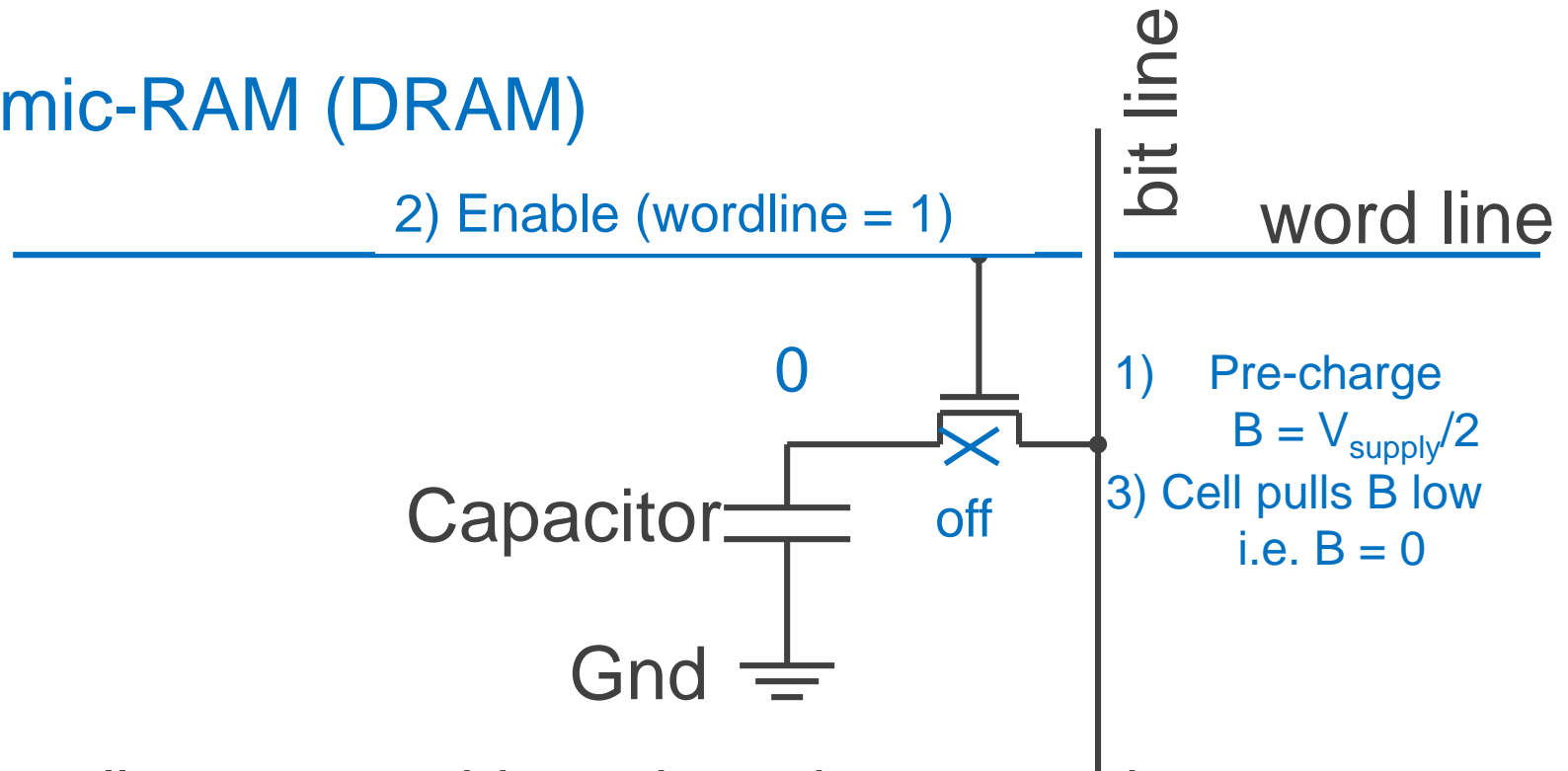


Each cell stores one bit, and requires 1 transistors

### Read:

- pre-charge B and  $\bar{B}$  to  $V_{\text{supply}}/2$
- pull word line high
- cell pulls B low, sense amp detects voltage difference

# Dynamic RAM: DRAM

## Dynamic-RAM (DRAM)

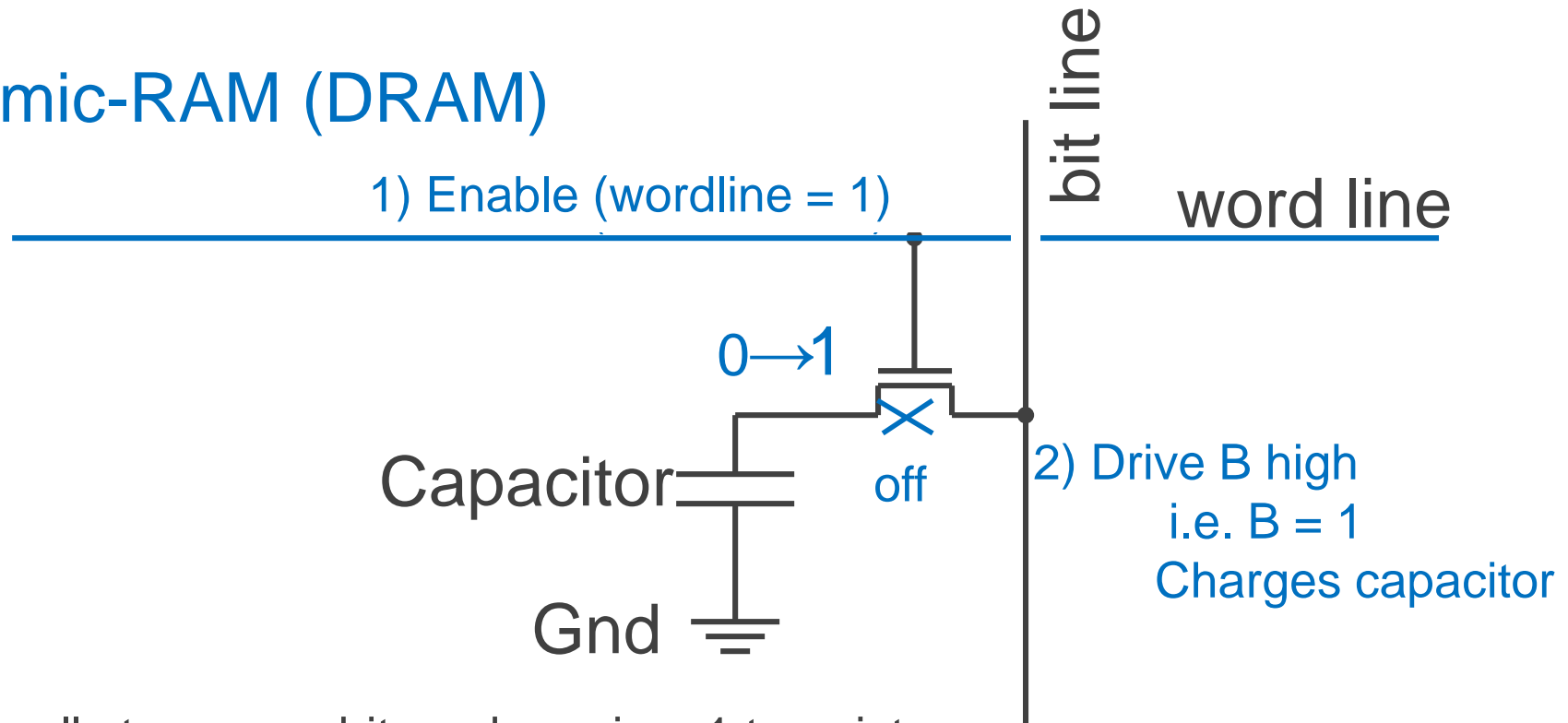

Each cell stores one bit, and requires 1 transistors

### Read:

- pre-charge B and  $\bar{B}$  to  $V_{\text{supply}}/2$
- pull word line high
- cell pulls B low, sense amp detects voltage difference

### Write:

- pull word line high
- drive B charges capacitor



# DRAM vs. SRAM


Single transistor vs. many gates

- Denser, cheaper (\$30/1GB vs. \$30/2MB)
- But more complicated, and has analog sensing

Also needs refresh

- Read and write back...
- ...every few milliseconds
- Organized in 2D grid, so can do rows at a time
- Chip can do refresh internally

Hence... slower and energy inefficient

 

# Memory

## Register File tradeoffs


- + Very fast (a few gate delays for both read and write)
- + Adding extra ports is straightforward
- Expensive, doesn't scale
- Volatile

## Volatile Memory alternatives: SRAM, DRAM, ...

- Slower
- + Cheaper, and scales well
- Volatile
 
## Non-Volatile Memory (NV-RAM): Flash, EEPROM, ...

- + Scales well
- Limited lifetime; degrades after 100000 to 1M writes



# Summary

We now have enough building blocks to build machines that can perform non-trivial computational tasks

Register File: Tens of words of working memory

SRAM: Millions of words of working memory

DRAM: Billions of words of working memory

NVRAM: long term storage

(usb fob, solid state disks, BIOS, ...)

Next time we will build a simple processor!

