



# Numbers & Arithmetic

Hakim Weatherspoon  
CS 3410, Spring 2011  
Computer Science  
Cornell University

See: P&H Chapter 2.4 - 2.6, 3.2, C.5 – C.6

# Announcements

---

Make sure you are

- Registered for class
- Can access CMS
- Have a Section you can go to
- Have a project partner

Sections are on this week

HW 1 out later today

- Due in one week, start early
- Work **alone**
- Use your resources
  - Class notes, book, Sections, office hours, newsgroup, CSUGLab<sub>2</sub>

# Announcements

---

Check online syllabus/schedule

- Slides and Reading for lectures
- Office Hours
- Homework and Programming Assignments
- Prelims: Thursday, March 11 and April 28<sup>th</sup>
- Schedule is subject to change

# Goals for today

---

## Review

- Circuit design (e.g. voting machine)
- Number representations
- Building blocks (encoders, decoders, multiplexors)

## Binary Operations

- One-bit and four-bit adders
- Negative numbers and two's complement
- Addition (two's complement)
- Subtraction (two's complement)
- Performance

# Logic Minimization

- How to implement a desired function?

a	b	c	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

$\bar{a}\bar{b}\bar{c}$

$\bar{a}\bar{b}c$

$\bar{a}bc$

$a\bar{b}c$


# Logic Minimization

- How to implement a desired function?

a	b	c	out	minterm
0	0	0	0	$\bar{a}\bar{b}\bar{c}$
0	0	1	1	$\bar{a}\bar{b}c$
0	1	0	0	$\bar{a}b\bar{c}$
0	1	1	1	$\bar{a}bc$
1	0	0	0	$a\bar{b}\bar{c}$
1	0	1	1	$a\bar{b}c$
1	1	0	0	$abc$
1	1	1	0	$abc$

sum of products:

- OR of all minterms where out=1

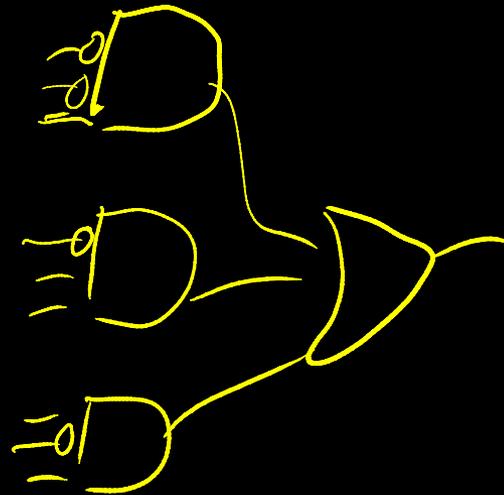

corollary: *any* combinational circuit *can be* implemented in two levels of logic (ignoring inverters)

# Karnaugh Maps

---

How does one find the most efficient equation?

- Manipulate algebraically until...?
- Use Karnaugh maps (optimize visually)
- Use a software optimizer

For large circuits


- Decomposition & reuse of building blocks

# Voting machine

- Voting Machine!
  - optical scan (thanks FL)
- Assume:
  - vote is recorded on paper by filling a circle
  - fixed number of choices
  - don't worry about "invalids"

Al Franken	<input type="radio"/>
Bill Clinton	<input type="radio"/>
Condi Rice	<input type="radio"/>
Dick Cheney	<input type="radio"/>
Eliot Spitzer	<input type="radio"/>
Fred Upton	<input type="radio"/>
Write-in Lizard People	<input checked="" type="radio"/>

# Voting Machine Components

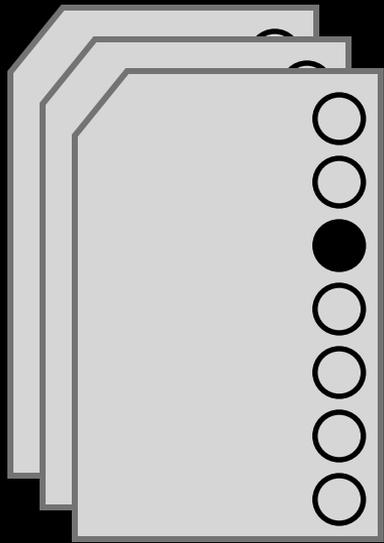

Ballots



The 3410 optical scan  
vote counter reader  
machine


## 5 Essential Components?

- **Input:** paper with at exactly one mark
- **Datapath:** process current ballot
- **Output:** a number the supervisor can record
- **Memory & control:** none for now
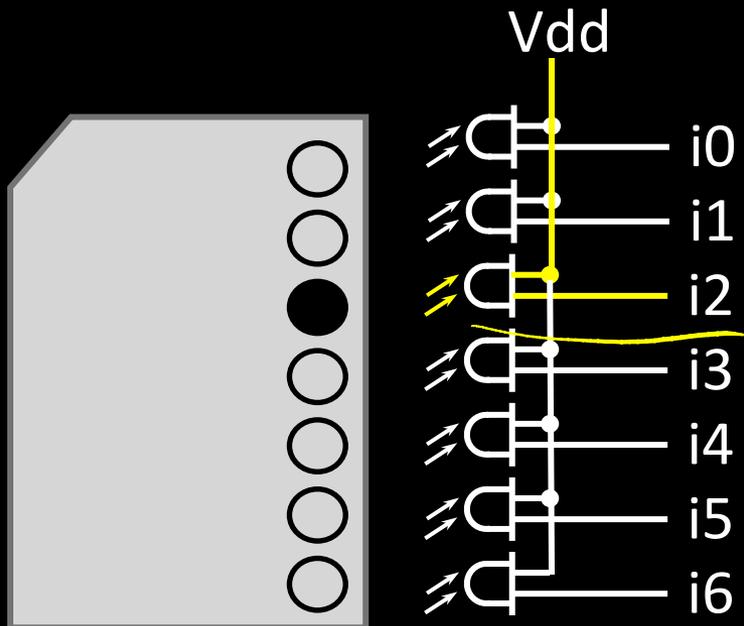
# Input




- **Photo-sensitive transistor**
  - photons replenish gate depletion region
  - can distinguish dark and light spots on paper




- Use array of N sensors for voting machine input
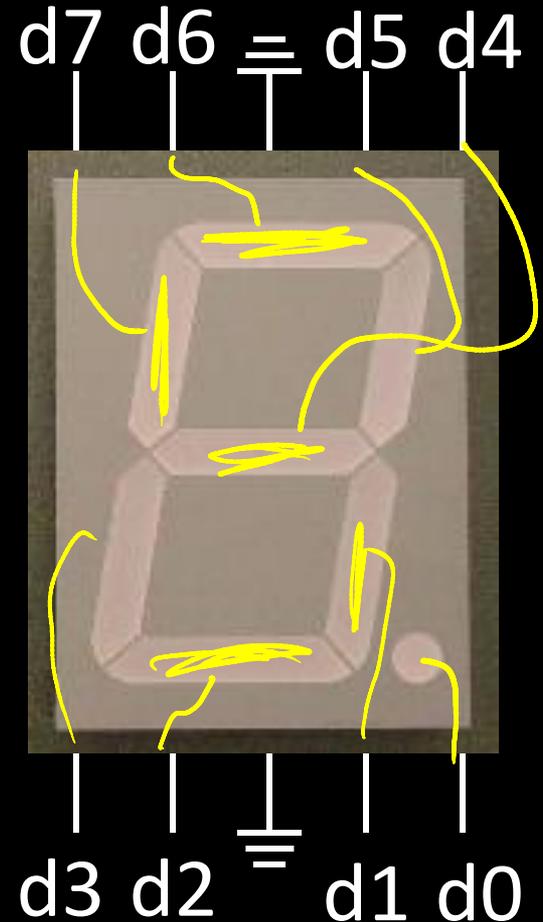
# Output


- 7-Segment LED
  - photons emitted when electrons fall into holes



# Block Diagram

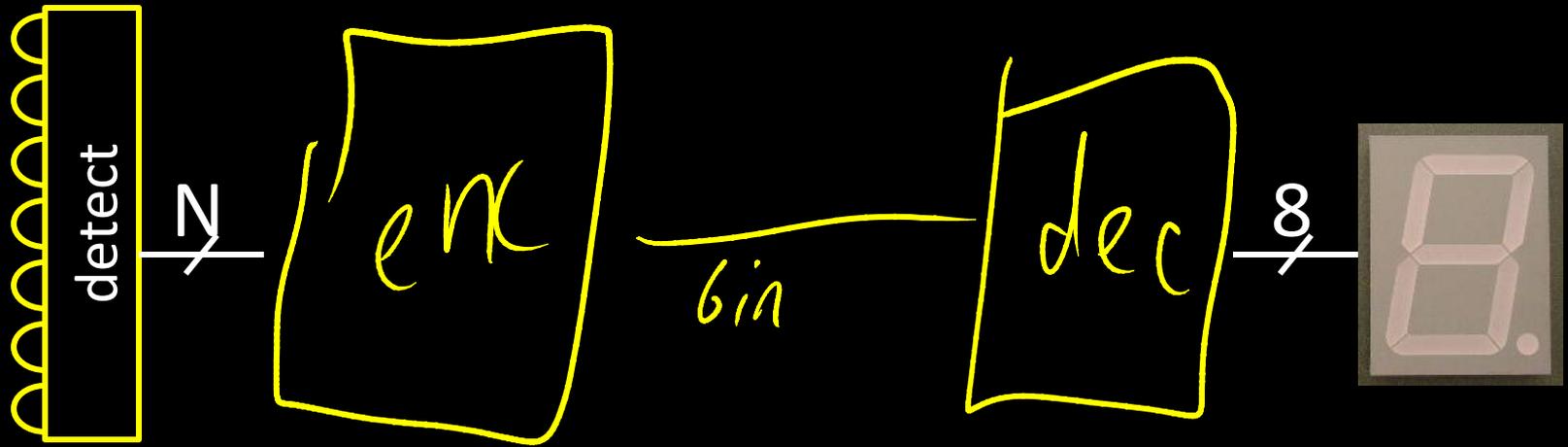

# Encoders

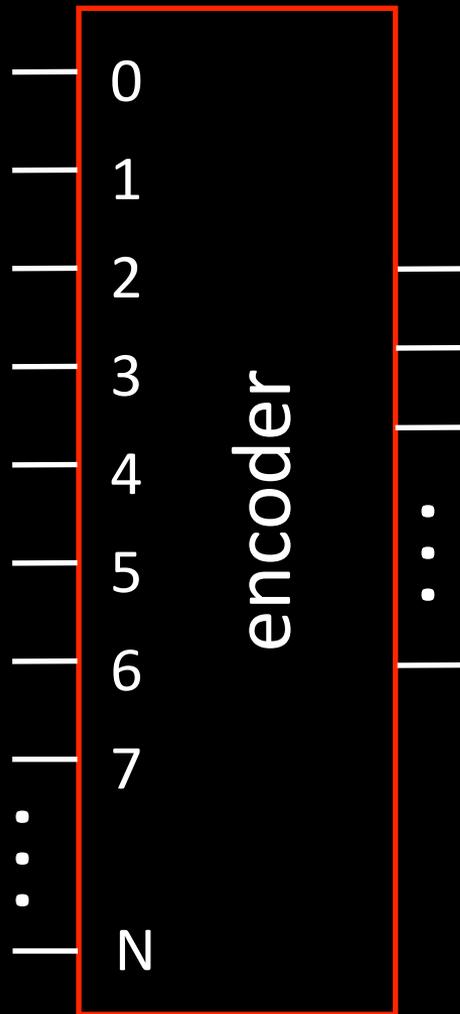

- N might be large
- Routing wires is expensive
- More efficient encoding?

$$\log_2(N)$$

# Number Representations

---

- Base 10 - **Decimal**

6 3 7  
 $10^2$   $10^1$   $10^0$

- Just as easily use other bases
  - Base 2 - **Binary**
  - Base 8 - **Octal**
  - Base 16 - **Hexadecimal**

# Counting

---

- Counting

dec	oct
0	0
1	1
2	2
3	3
4	4
5	5
6	6
7	7
8	...
9	...
10	77
...	...
100	100

# Base Conversion

- Base conversion via repetitive division
  - Divide by base, write remainder, move left with quotient

$$\begin{array}{l} 637 \div 10 = 63 \text{ rem } 7 \\ \quad \div 10 = 6 \text{ rem } 3 \\ \quad \div 10 = 0 \text{ rem } 6 \end{array}$$

LSB


637

MSB
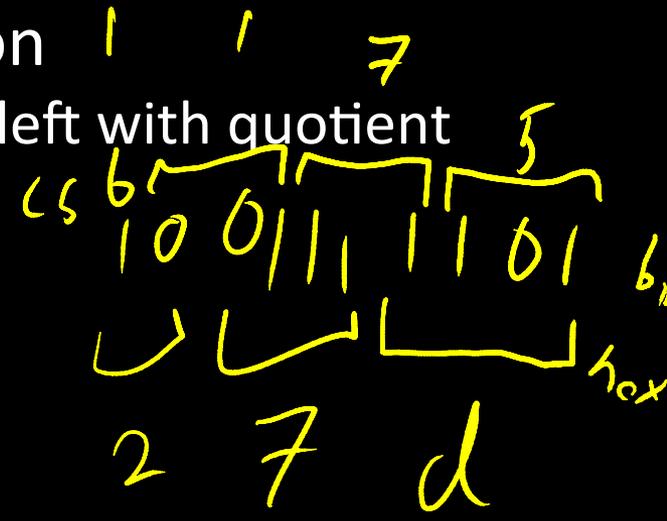
# Base Conversion

- Base conversion via repetitive division
  - Divide by base, write remainder, move left with quotient

$$\begin{array}{r} 637 \div 2 = 318 \text{ rem } 1 \\ \div 2 = 159 \text{ rem } 0 \\ \div 2 = 79 \text{ rem } 1 \\ \div 2 = 39 \text{ rem } 1 \\ \div 2 = 19 \text{ rem } 1 \\ \div 2 = 9 \text{ rem } 1 \\ \div 2 = 4 \text{ rem } 0 \\ \div 2 = 2 \text{ rem } 1 \\ \div 2 = 1 \text{ rem } 0 \end{array}$$



0x27d

# Base Conversion

- Base conversion via repetitive division
  - Divide by base, write remainder, move left with quotient

$$\begin{array}{l} 637 \div 16 = 39 \text{ rem } 13 \\ \div 16 = 2 \text{ rem } 7 \\ \div 16 = 0 \text{ rem } 2 \end{array} \quad \left[ \begin{array}{l} \text{lsb} \\ 13 \\ 7 \\ 2 \\ \text{msb} \end{array} \right]$$


$$\begin{array}{r} 27 \quad 13 \\ 27 \quad d \\ 0x27d \end{array}$$

# Hexadecimal, Binary, Octal Conversions
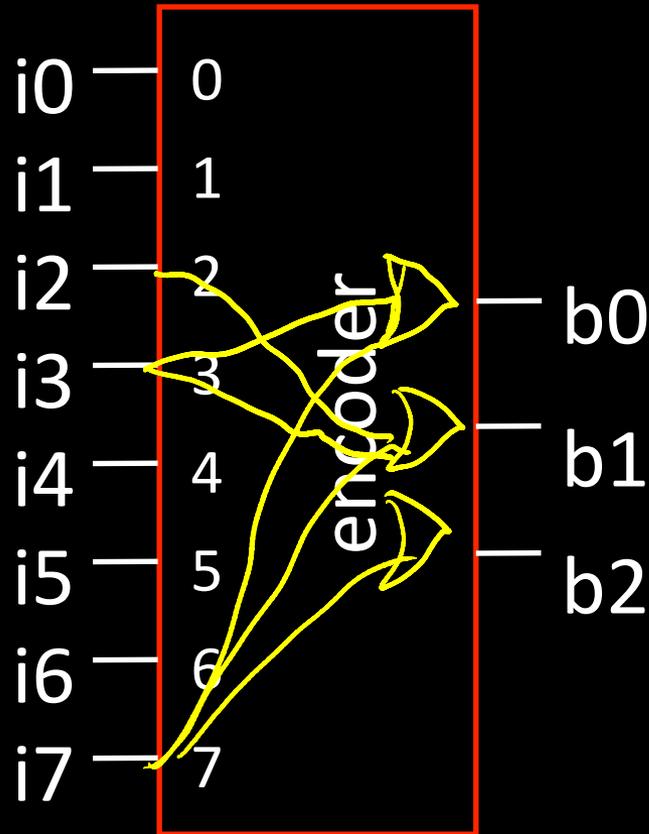
# Encoder Implementation

- Implementation . . .


- assume 8 choices, exactly one mark detected



3-bit encoder  
(8-to-3)


	msb	lsb
0	0	00
1	0	01
2	0	10
3	0	11
4	1	00
5	1	01
6	1	10
7	1	11

# Ballot Reading

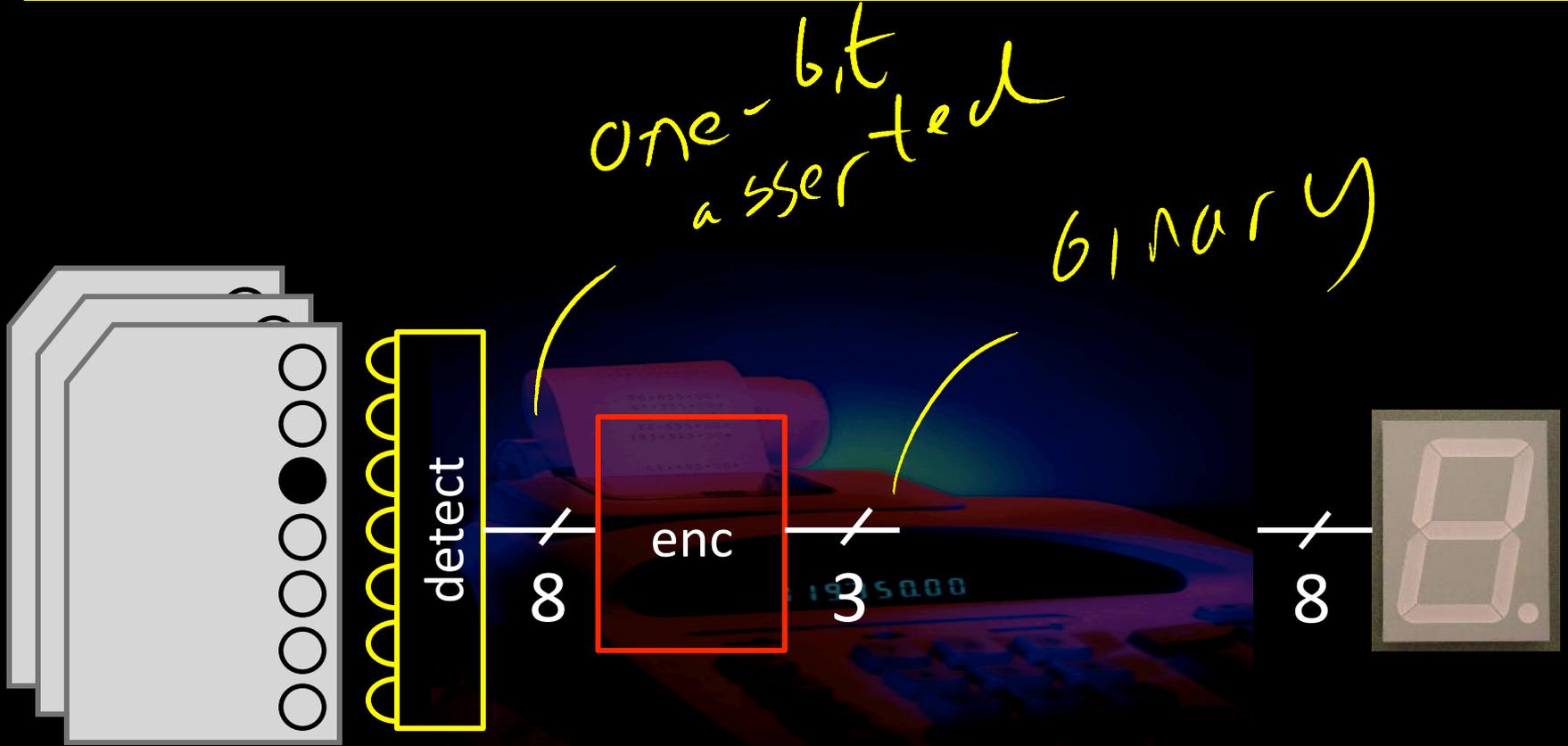

# 7-Segment LED Decoder


---

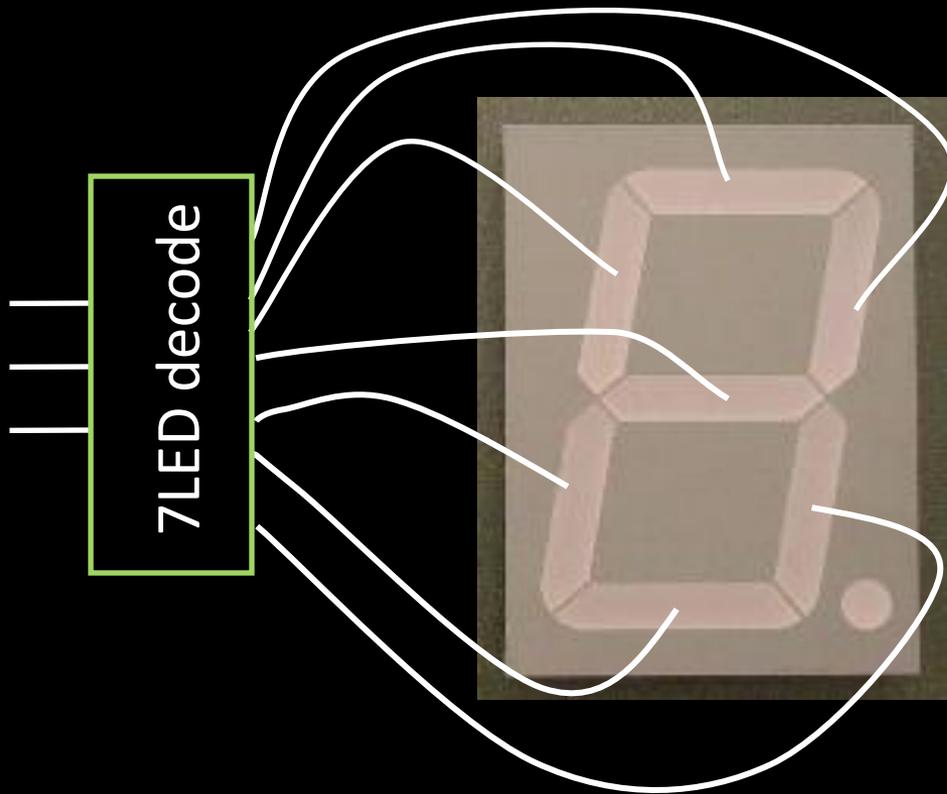

- 3 inputs
- encode 0 – 7 in binary
- 7 outputs
- one for each LED


# 7 Segment LED Decoder Implementation

b2	b1	b0	d6	d5	d4	d3	d2	d1	d0
0	0	0							
0	0	1							
0	1	0							
0	1	1							
1	0	0							
1	0	1							
<u>1</u>	<u>1</u>	<u>0</u>	1	0	0	0	0	1	1
1	1	1							

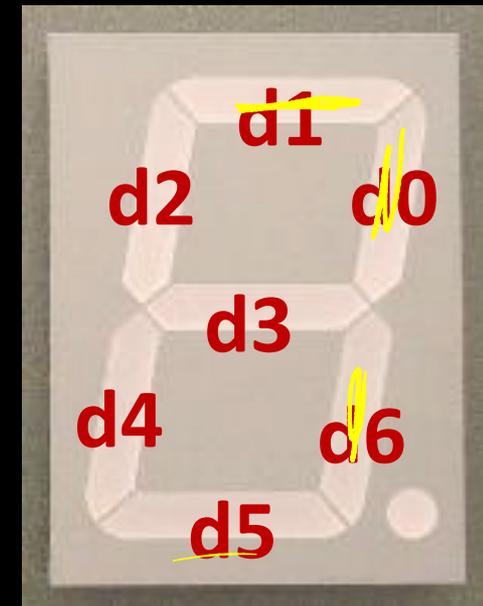


# 7 Segment LED Decoder Implementation

b2	b1	b0	d6	d5	d4	d3	d2	d1	d0
0	0	0	1	1	1	0	1	1	1
0	0	1	1	0	0	0	0	0	1
0	1	0	0	1	1	1	0	1	1
0	1	1	1	1	0	1	0	1	1
1	0	0	1	0	0	1	1	0	1
1	0	1	1	1	0	1	1	1	0
1	1	0	1	1	1	1	1	1	0
1	1	1	1	0	0	0	0	1	1

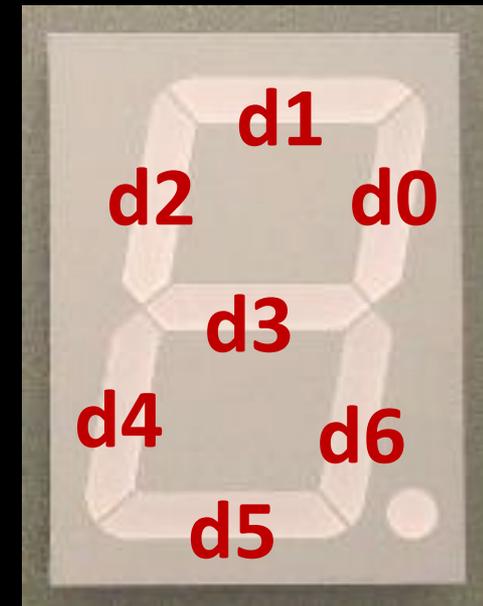


# Ballot Reading and Display

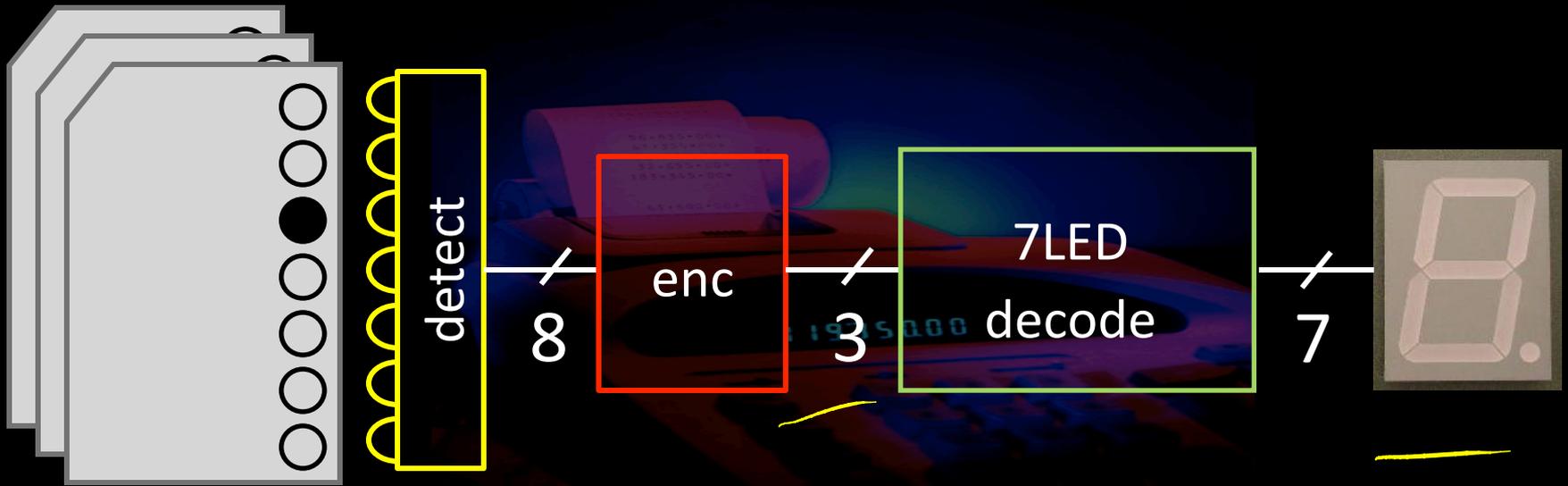

Ballots

The 3410 optical scan  
vote counter reader  
machine

# Building Blocks

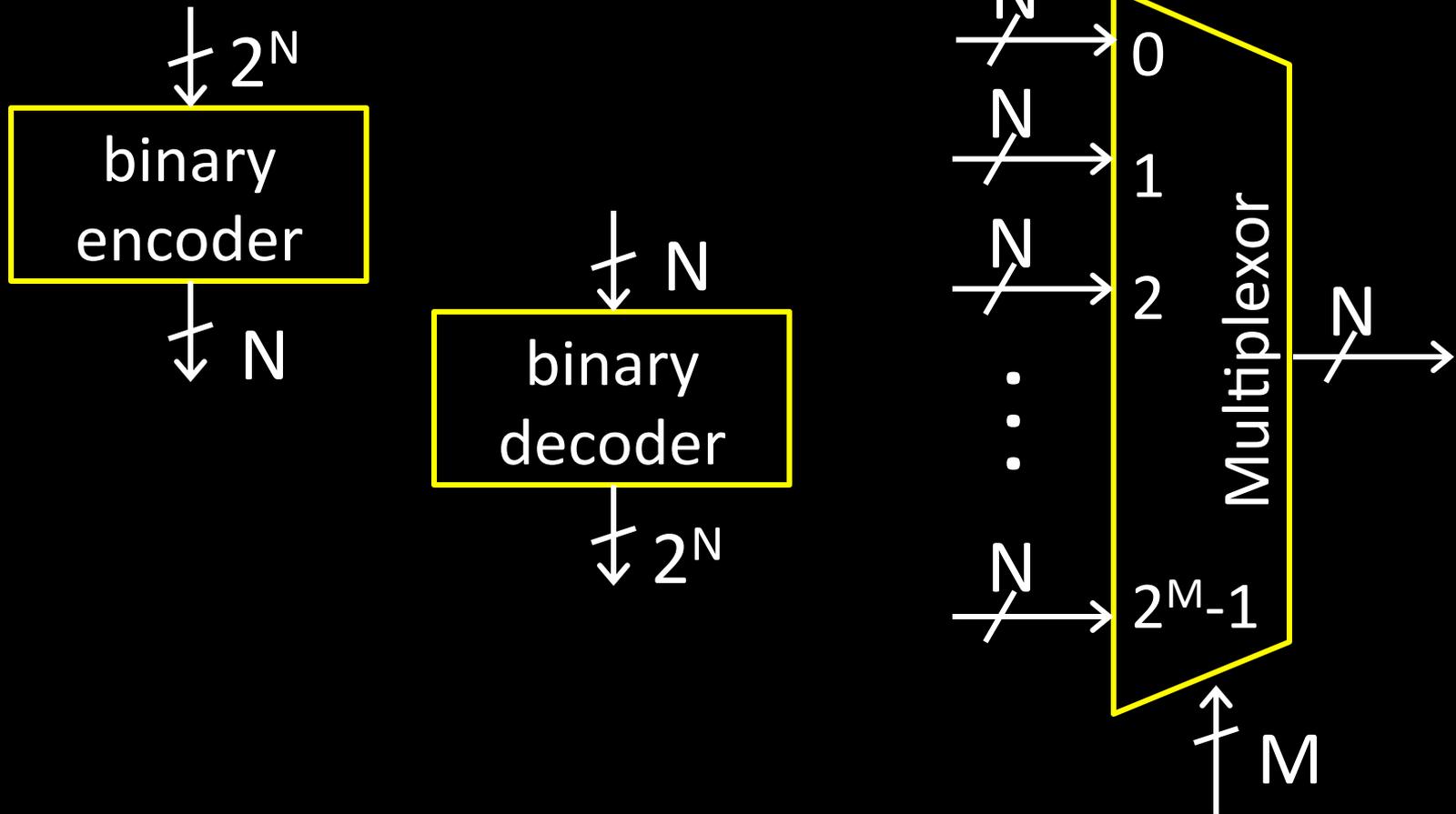

# Goals for today

---

## Review

- Circuit design (e.g. voting machine)
- Number representations
- Building blocks (encoders, decoders, multiplexors)

## Binary Operations

- One-bit and four-bit adders
- Negative numbers and two's complement
- Addition (two's complement)
- Subtraction (two's complement)
- Performance

# Binary Addition

---


$$\begin{array}{r} | \\ 183 \\ + 254 \\ \hline \end{array}$$

437

$$\begin{array}{r} 001110 \\ + 011100 \\ \hline 101010 \end{array}$$

- Addition works the same way regardless of base
- Add the digits in each position
- Propagate the carry

# 1-bit Adder

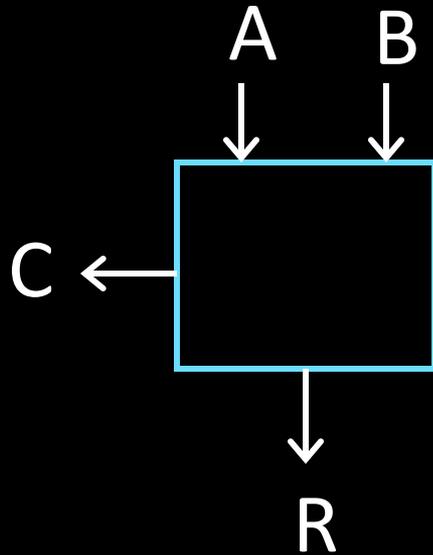


## Half Adder

- Adds two 1-bit numbers
- Computes 1-bit result and 1-bit carry

A	B	C	R
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

# 1-bit Adder with Carry

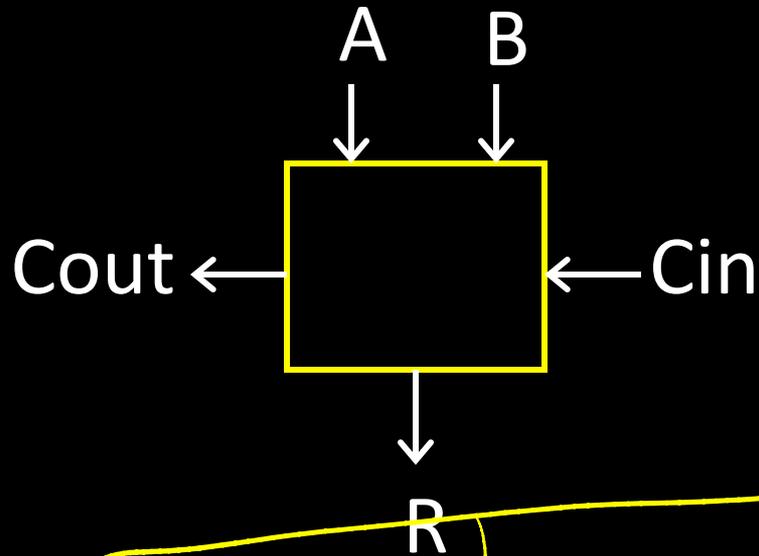


## Full Adder

- Adds three 1-bit numbers
- Computes 1-bit result and 1-bit carry
- Can be cascaded

A	B	C <sub>in</sub>	C <sub>out</sub>	R
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

# 4-bit Adder


---

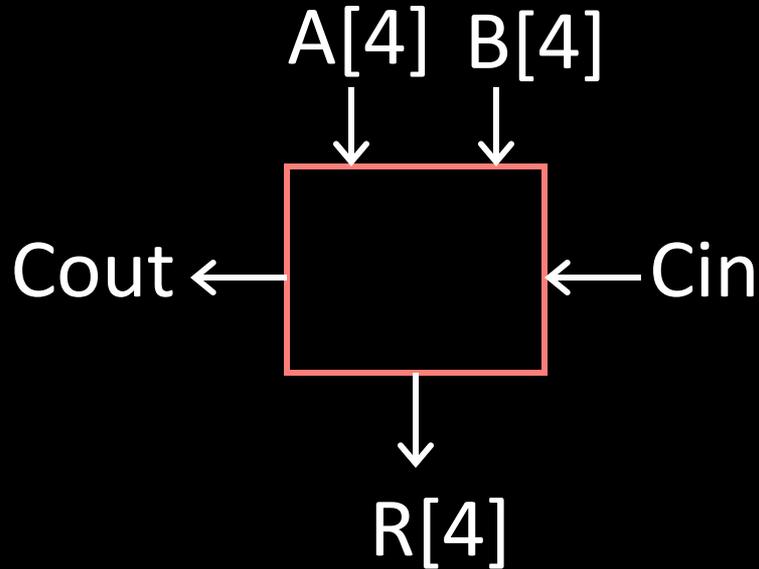


## 4-Bit Full Adder

- Adds two 4-bit numbers and carry in
- Computes 4-bit result and carry out
- Can be cascaded

# 4-bit Adder

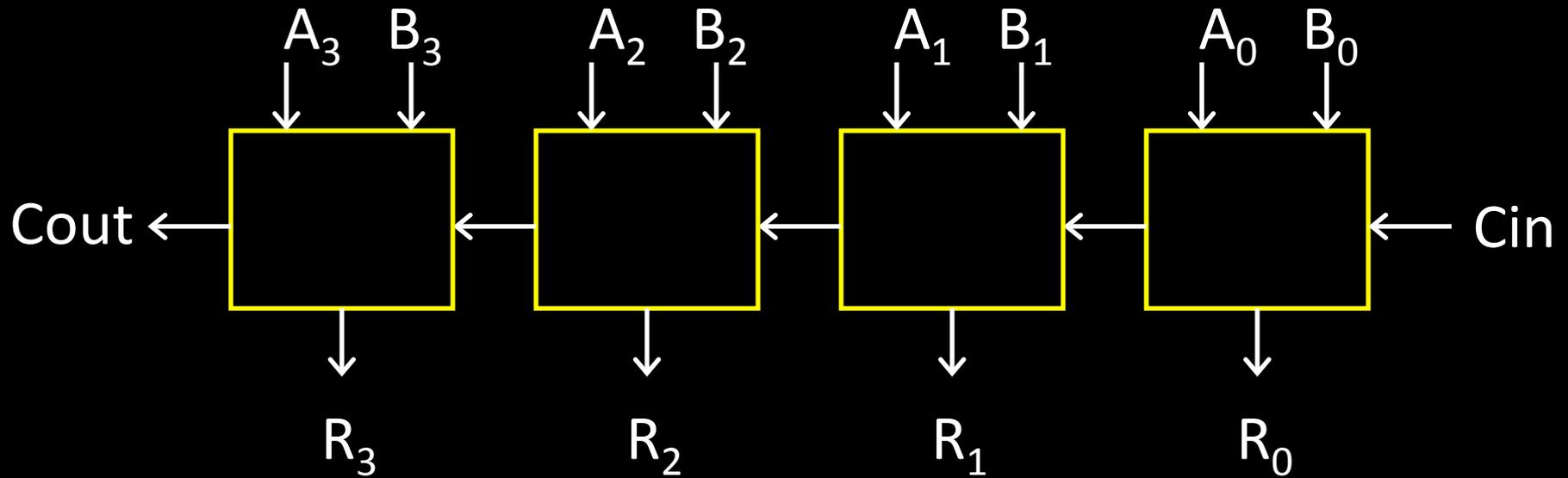

# 4-bit Adder

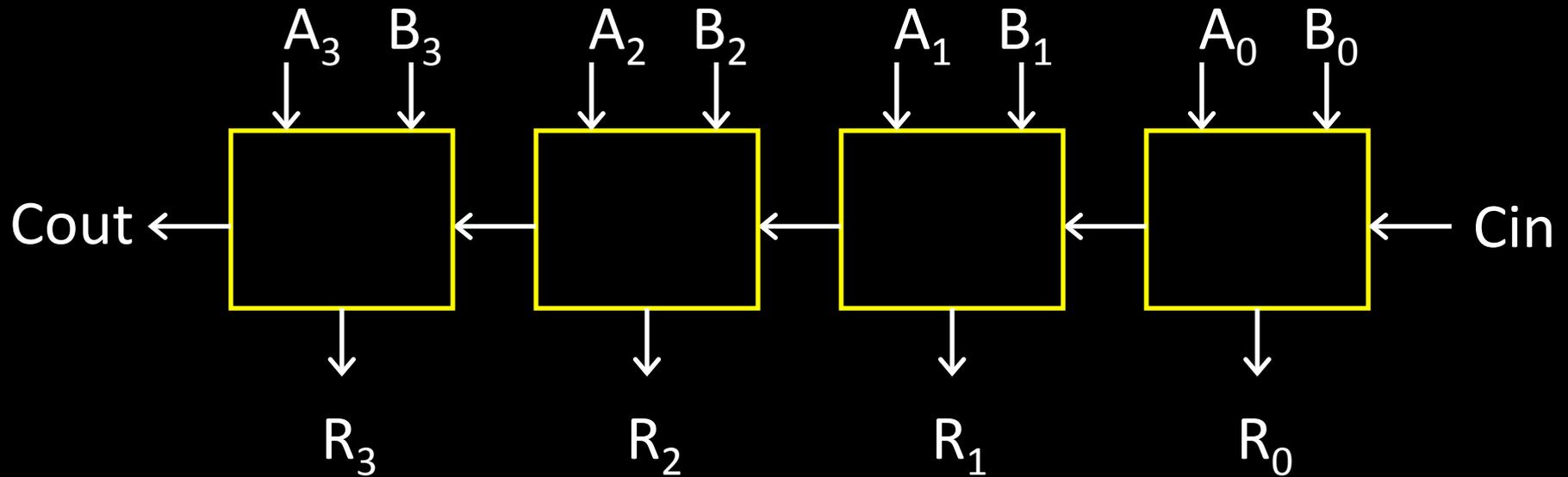

- Adds two 4-bit numbers, along with carry-in
- Computes 4-bit result and carry out

# Arithmetic with Negative Numbers

- Addition with negatives:  $0111 = 7$
- $pos + pos \rightarrow$  add magnitudes, result positive  $1111 = -7$
- $neg + neg \rightarrow$  add magnitudes, result negative
- $pos + neg \rightarrow$  subtract smaller magnitude, keep sign of bigger magnitude  
result neg
- $pos + neg \rightarrow$  subtract smaller  
Keep the sign of the bigger mag

# First Attempt: Sign/Magnitude Representation

- First Attempt: Sign/Magnitude Representation
- 1 bit for sign (0=positive, 1=negative)
- N-1 bits for magnitude

$$0 \ 111 = 7$$
$$1 \ 111 = -7$$

# Two's Complement Representation

- Better: Two's Complement Representation
- Leading 1's for negative numbers
- To negate **any** number:

– complement *all* the bits

– then add 1

$$\begin{array}{r} 6 = 0110 \\ \hline \bar{6} = 1001 \\ \quad + 1 \\ \hline -6 = 1010 \end{array} \quad \begin{array}{r} 20 = 00010100 \\ \bar{20} = 11101011 \\ \quad + 1 \\ \hline -20 = 11101100 \end{array}$$

# Two's Complement

- Non-negatives Negatives

*Ignore last carry*

- (as usual): (two's complement: flip then add 1):

• +0 = 0000	$\sim 0 = 1111$	$-0 = 0000$
• +1 = 0001	$\sim 1 = 1110$	$-1 = 1111$
• +2 = 0010	$\sim 2 = 1101$	$-2 = 1110$
• +3 = 0011	$\sim 3 = 1100$	$-3 = 1101$
• +4 = 0100	$\sim 4 = 1011$	$-4 = 1100$
• +5 = 0101	$\sim 5 = 1010$	$-5 = 1101$
• +6 = 0110	$\sim 6 = 1001$	$-6 = 1100$
• +7 = 0111	$\sim 7 = 1000$	$-7 = 1001$
• <del>+8 = 1000</del>	$\sim 8 = 0111$	<del>-8 = 1000</del>

*4 bits = [-8, 7]*

# Two's Complement Facts

- Signed two's complement
  - Negative numbers have leading 1's
  - zero is unique:  $+0 = -0$
  - wraps from largest positive to largest negative
- N bits can be used to represent

- unsigned:

– eg: 8 bits  $\Rightarrow$

$$0 \dots 2^N - 1$$
$$0 \dots 2^8 - 1 = 255$$

- signed (two's complement):

– ex: 8 bits  $\Rightarrow$

$$-128 \dots 0 \dots +127$$
$$-\left(\frac{2^N}{2}\right) \dots \left(\frac{2^N}{2}\right) - 1$$

# Sign Extension & Truncation

- Extending to larger size


- Truncate to smaller size

$$\begin{array}{r} 6 = \underline{0110} \\ - 1 = \underline{1111} \\ \hline \end{array} \quad \begin{array}{r} \underline{0000} \quad \underline{0110} \\ \underline{1111} \quad \underline{1111} \end{array}$$

~~$$\begin{array}{r} 0000 \quad 1111 = 15 \\ 0111 = 7 \end{array}$$~~
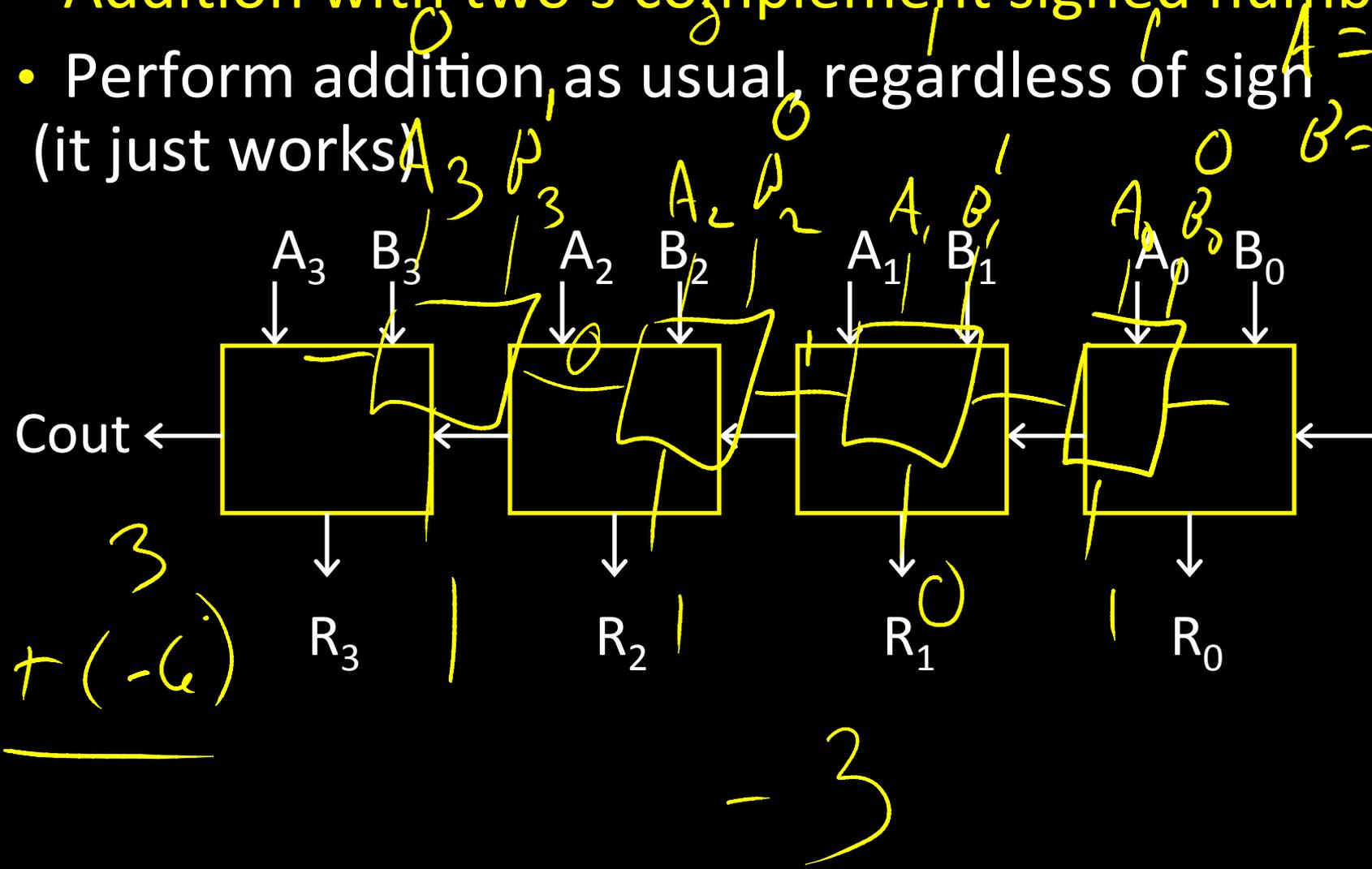
# Two's Complement Addition

- Addition with two's complement signed numbers
- Perform addition as usual, regardless of sign (it just works)



# Diversion: 10's Complement

---

- How does that work?

$$\begin{array}{r} -154 \\ +283 \\ \hline \end{array}$$

# Overflow

---

- **Overflow**

- adding a negative and a positive?

- adding two positives?


- adding two negatives?

- **Rule of thumb!**  $msb \neq carry\ in$   $msb$

- Overflow happened iff  
carry into msb  $\neq$  carry out of msb
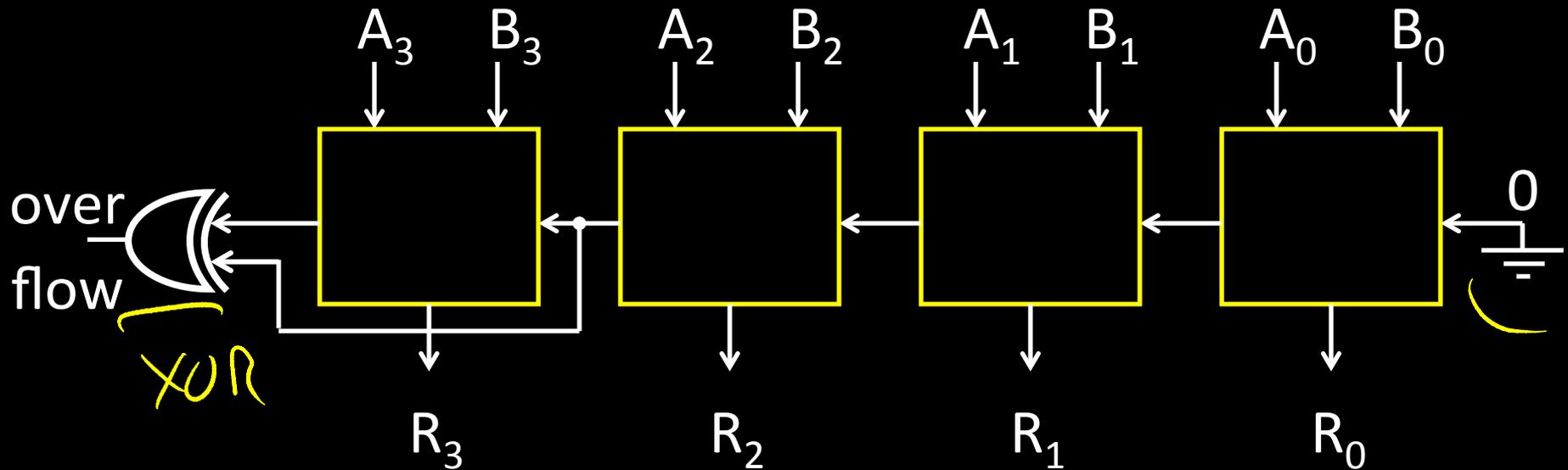
# Two's Complement Adder

- Two's Complement Adder with overflow detection




# Binary Subtraction

- Two's Complement Subtraction

- $A - B = A + (-B) = A + (B + 1)$   
Lazy approach


$A = 7$   
 $B = -8$

- $A - B = A + (-B) = A + (B + 1)$

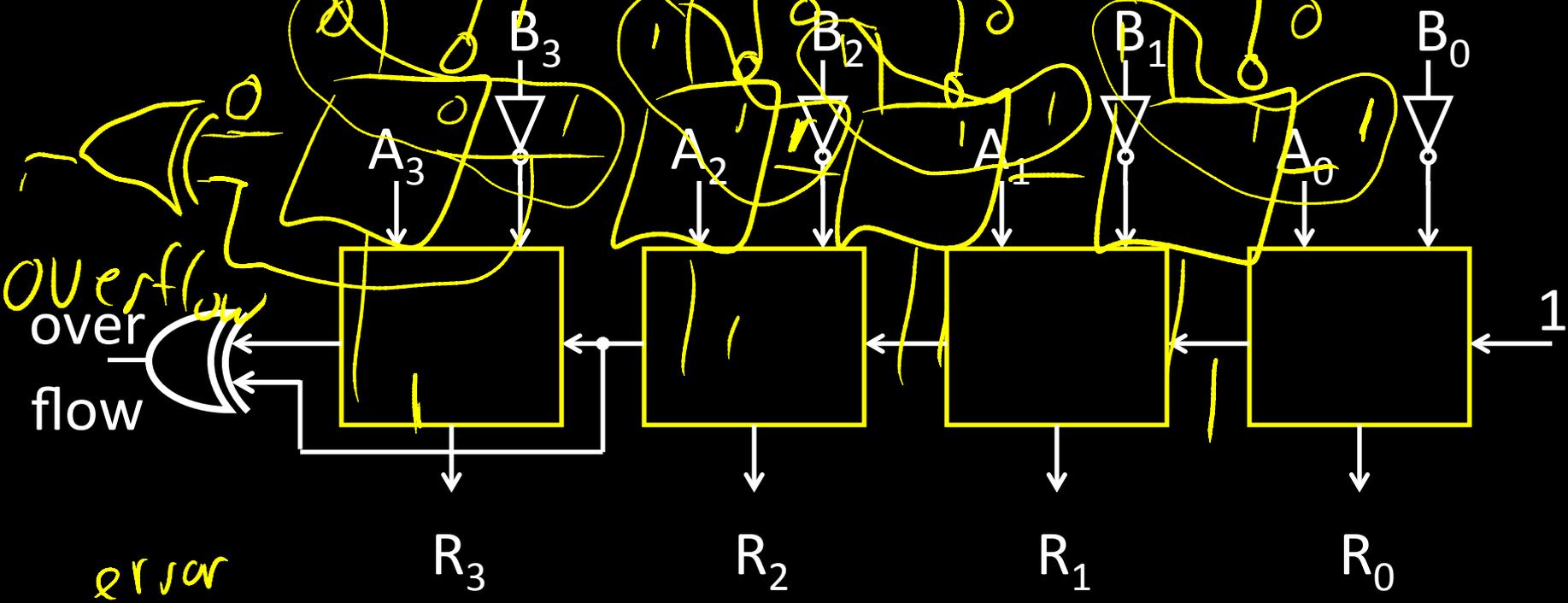


Q: What if (-B) overflows?

# A Calculator

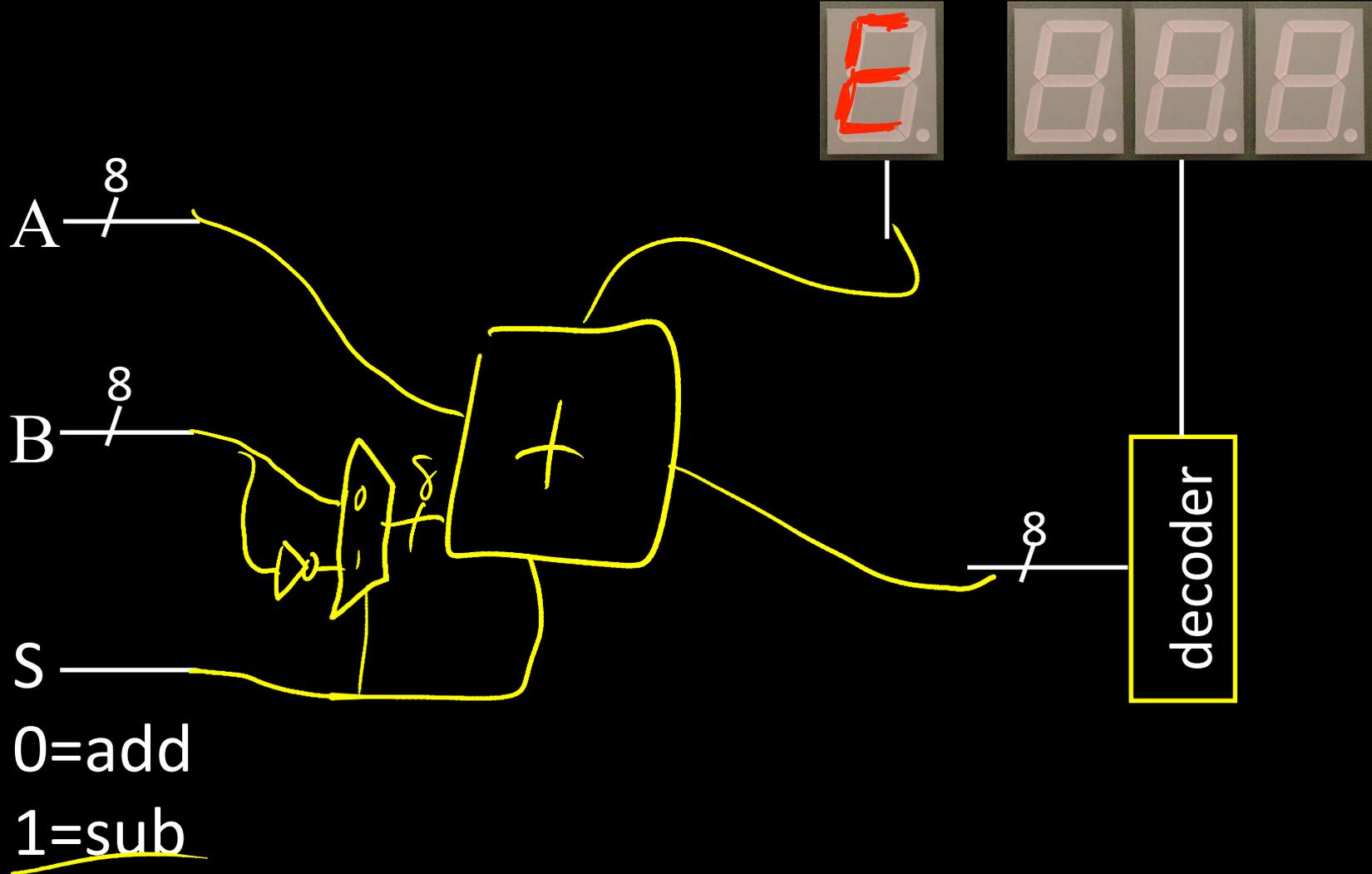


# A Calculator

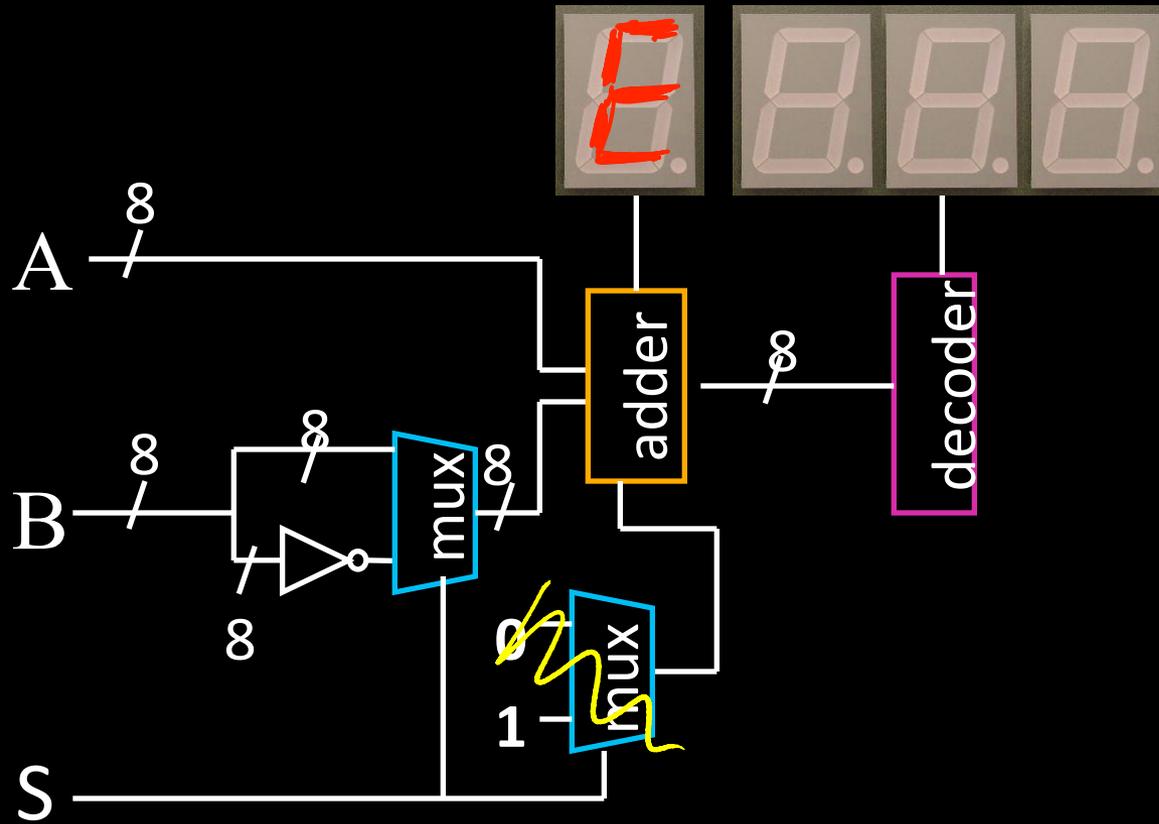

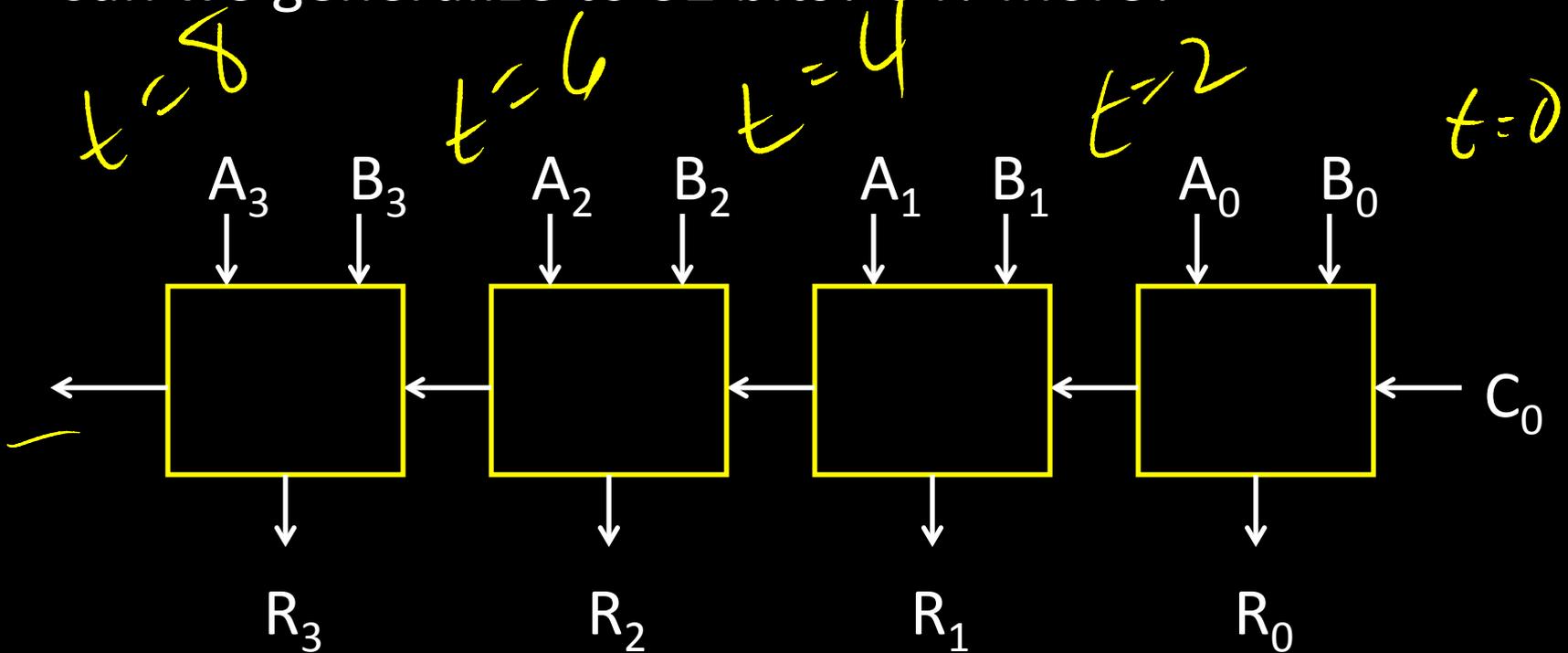
# Efficiency and Generality

- Is this design fast enough?
- Can we generalize to 32 bits? 64? more?



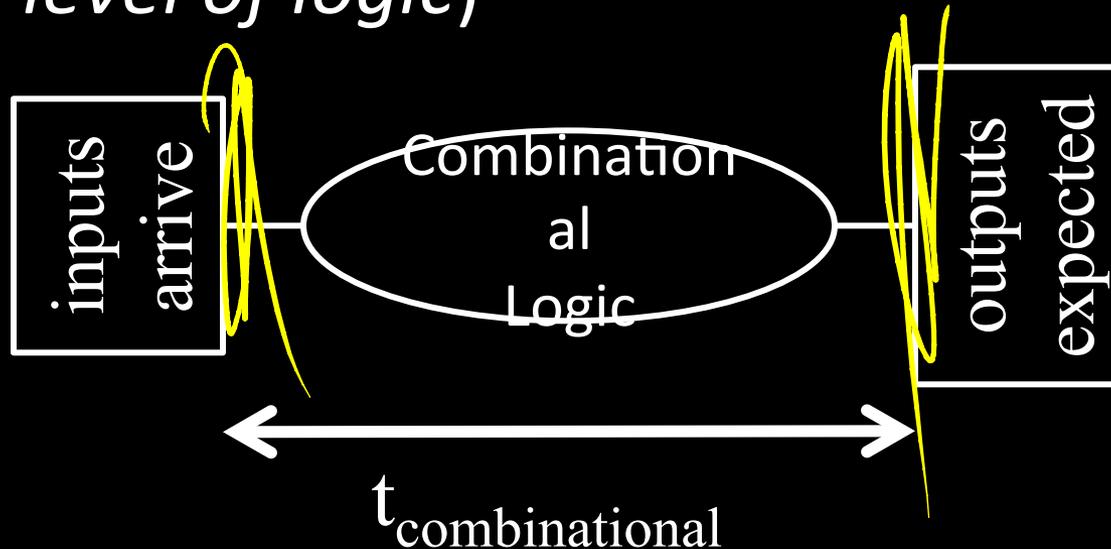
# Performance

- Speed of a circuit is affected by the number of gates in series (on the *critical path* or the *deepest level of logic*)



# 4-bit Ripple Carry Adder

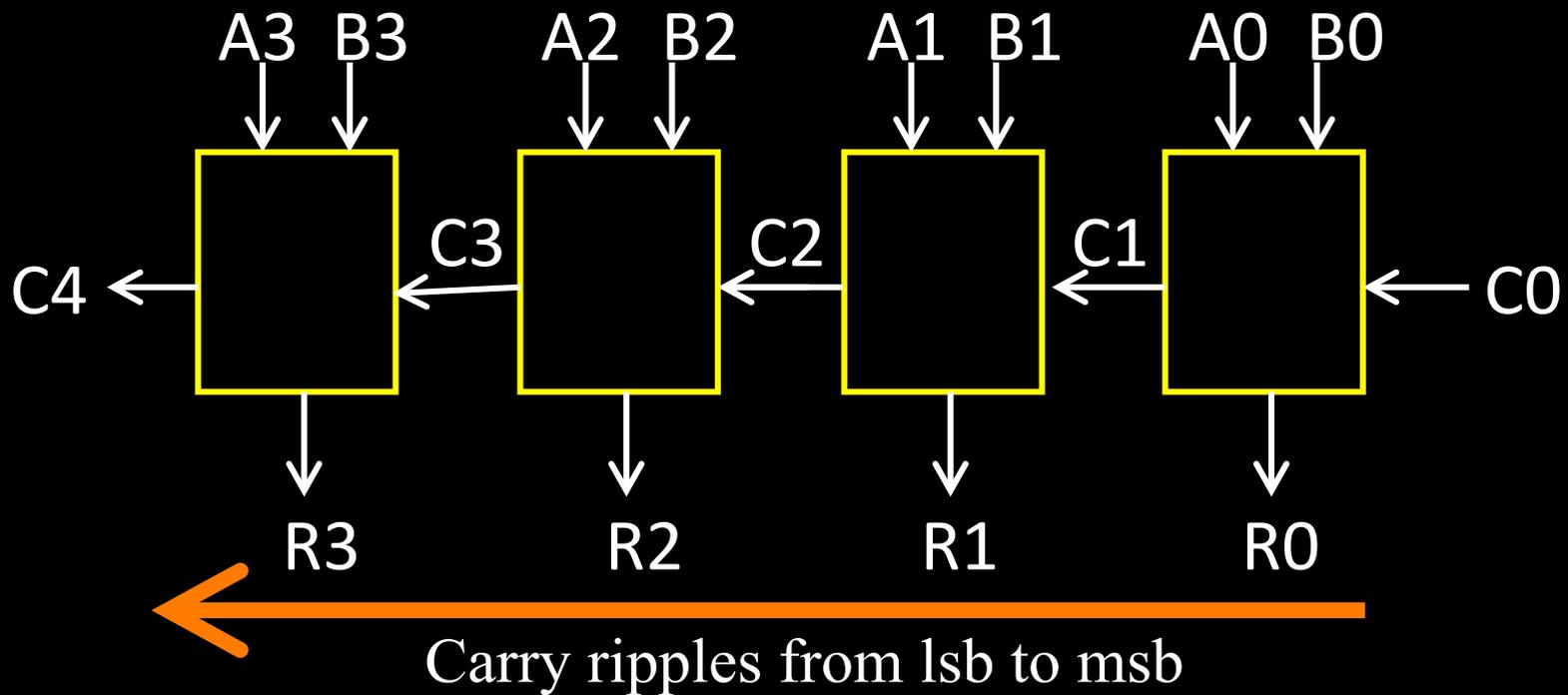

- First full adder, 2 gate delay
- Second full adder, 2 gate delay
- ...

# Summary

---

- We can now implement any combinational (combinatorial) logic circuit
  - Decompose large circuit into manageable blocks
    - Encoders, Decoders, Multiplexors, Adders, ...
  - Design each block
    - Binary encoded numbers for compactness
  - Can implement circuits using NAND or NOR gates
  - Can implement gates using use P- and N-transistors
  - **And can add and subtract numbers (in two's compliment)!**
  - Next time, state and finite state machines...