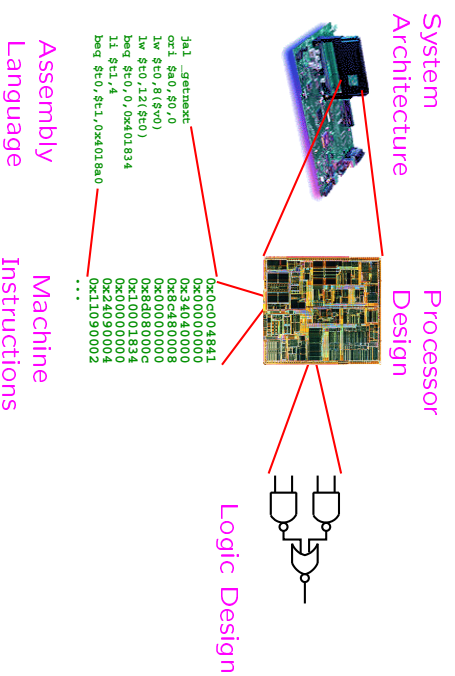


What 314 Is About



Building A Computer

Information is encoded with bits: 0's and 1's.
(we've already seen 2's complement numbers)

These are encoded using *voltages*...

- + well understood
- + easy to generate, detect
- affected by environment

But why 1's and 0's only?



Digital Representation

Example: representing a B&W picture:

- Black = 0 V
- White = 1 V
- 80% grey = 0.8 V
- ...

Represent by scanning picture in fixed order.


Let's try doing some computation with the voltages...




Digital Representation

Flip image:

Flip back and forth...

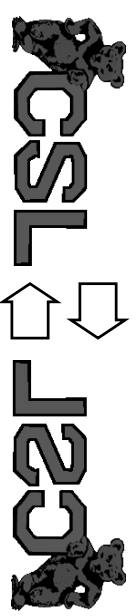

What really happens...

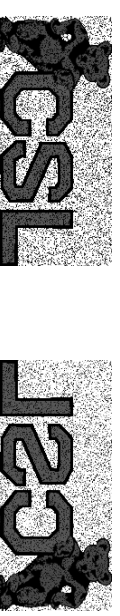


Have to build system to tolerate some error (noise).



Logic Levels

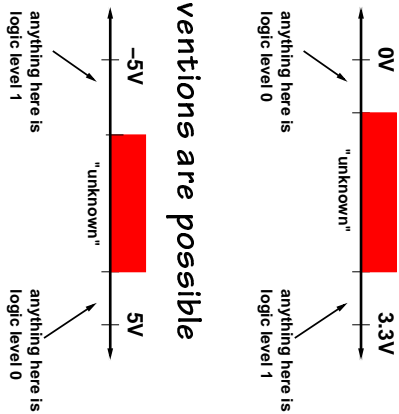- Store just one bit on a wire...
- Gain reliability



Different conventions are possible




Combinational Devices

A **combinational device**:


- Output is a function of inputs only ("memoryless")
- Takes input to valid, stable outputs

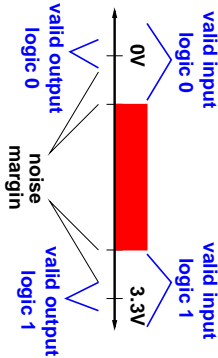Combinational devices **restore** marginally valid signals!



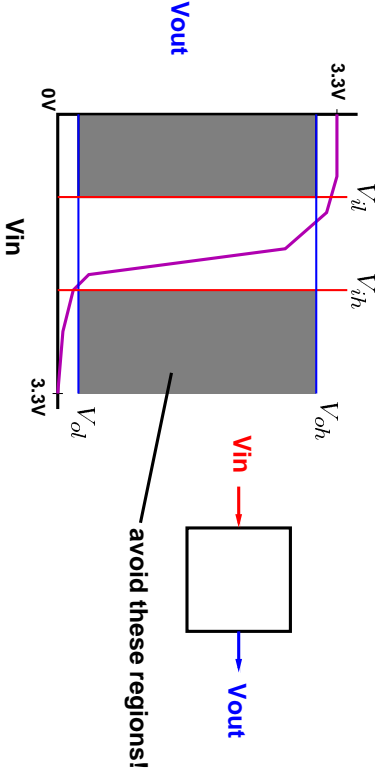Example

- Input: logic 0 if $V_{in} < V_{il}$, logic 1 if $V_{in} > V_{ih}$
- Output logic 0 if $V_{out} < V_{ol}$, logic 1 if $V_{out} > V_{oh}$



Digital View

- If input is 0, output is 1
- If input is 1, output is 0

Normally written in a table, like this:

| In | Out |
|----|-----|
| 0 | 1 |
| 1 | 0 |

Called a "truth-table".




Implementation: Switching Networks

Lots of ways to build switches...


- relays
- vacuum tubes
- transistors
- ...

P-transistor

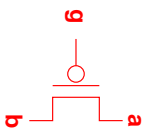

Connect a and b
if $g = 0$.


N-transistor

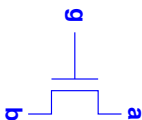

Connect a and b
if $g = 1$.



Switching Networks: Inverter

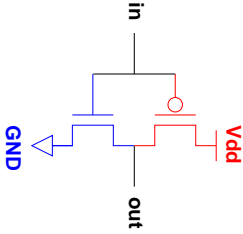


| in | out |
|----|-----|
| 0 | 1 |
| 1 | 0 |

- Function: NOT
- Called an inverter
- Symbol:




Switching Networks: NAND

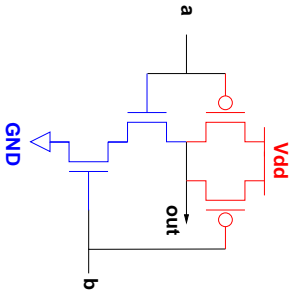


| a | b | out |
|---|---|-----|
| 0 | 0 | 1 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 0 |

- Function: NAND
- Symbol:

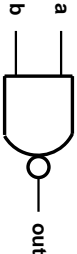

Switching Networks: NOR

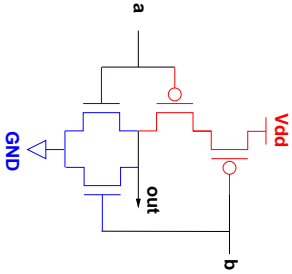


| a | b | out |
|---|---|-----|
| 0 | 0 | 1 |
| 1 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 1 | 0 |

- Function: NOR
- Symbol:



Building Functions From Gates

- AND:

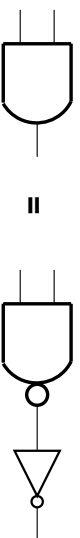

- OR:



Can specify function by describing gates, truth table, or **logic equations**.



Logic Equations

AND:

$$\begin{aligned} out &= a \cdot b \\ out &= ab \\ out &= a \wedge b \end{aligned}$$

OR:

$$\begin{aligned} out &= a + b \\ out &= a \vee b \end{aligned}$$

NOT:

$$\begin{aligned} out &= \neg in \\ out &= \overline{in} \end{aligned}$$



Logic Equations

Fun with identities:

$$\begin{aligned} a + \bar{a} &= 1 \\ a + 0 &= a \\ a + 1 &= 1 \end{aligned}$$

$$\begin{aligned} a\bar{a} &= 0 \\ a \cdot 0 &= 0 \\ a \cdot 1 &= a \end{aligned}$$

$$\begin{aligned} a(b + c) &= ab + ac \\ \overline{(a + b)} &= \bar{a} \cdot \bar{b} \\ \overline{(a \cdot b)} &= \bar{a} + \bar{b} \\ a + \bar{a}b &= a + b \end{aligned}$$

Check by writing truth tables, or by manipulating logic equations.



Let's Build An Adder

Write down function:

- Two 1-bit inputs, a and b
- Two 1-bit outputs, sum and $carry$

Truth-table:

| a | b | carry | sum |
|-----|-----|-------|-----|
| 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |




Let's Build An Adder

Sum output:

| a | b | sum | Logic term |
|---|---|-----|-------------------------|
| 0 | 0 | 0 | $\bar{a} \cdot \bar{b}$ |
| 1 | 0 | 1 | $a \cdot \bar{b}$ |
| 0 | 1 | 1 | $\bar{a} \cdot b$ |
| 1 | 1 | 0 | $a \cdot b$ |

Logic equation: $a \cdot \bar{b} + \bar{a} \cdot b$

Circuit:

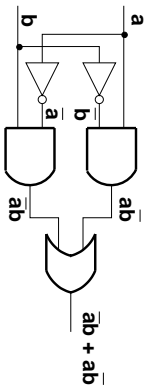

Let's Build An Adder

Carry output:

| a | b | carry | Logic term |
|---|---|-------|-------------------------|
| 0 | 0 | 0 | $\bar{a} \cdot \bar{b}$ |
| 1 | 0 | 0 | $a \cdot \bar{b}$ |
| 0 | 1 | 0 | $\bar{a} \cdot b$ |
| 1 | 1 | 1 | $a \cdot b$ |


Logic equation: $a \cdot b$

Circuit:



Let's Build An Adder

Final Circuit:

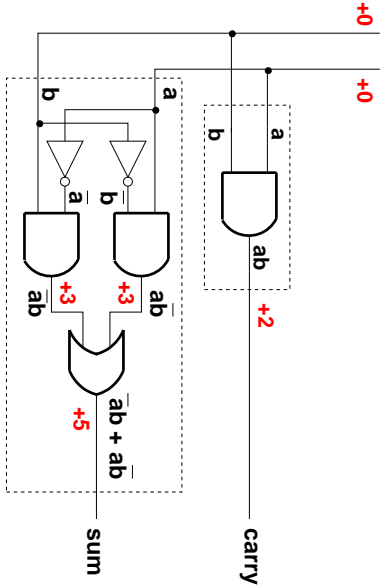

Numbers indicate the number of sequential steps from input to output (worst-case).

