

# Processor Implementation

---

## Overview

- Start with common datapath design concepts
- Simple processor implementation
- Move to more complex implementation
- Finally, pipelined implementation

We'll look at how modern hardware works:

- Clocking, combinational logic, etc
- Pipelining
- **Dealing with complexity**

a.k.a. how do they build those 10 million transistor chips??



# Designing Complex FSMs

---

How many states do we need for a MIPS CPU?

- MIPS has 32 32-bit registers
- Each register could be in one of  $2^{32}$  states
- We need at least  $31 \times 2^{32}$  states!  
(register 0 is 0)

... so we clearly don't want to draw the FSM or write the truth-table!

*Idea: exploit FSM structure*



# Datapath Concepts

---

## Datapath:

- Part of an architecture that manipulates data
- Tends to be “regular”

Example: ALU, MUX, etc.

## Control:

- Tells datapath what to do

Example: alu opcode, MUX select input, etc.



# Datapath Design

---

Steps in designing a processor:  
(or any other piece of hardware)

- *Start with high-level specification*  
processor: the ISA
- *Identify major storage elements and signals*  
processor: registers, memory, ...
- *Translate specification*  
determine operations on storage elements  
(RTL, register transfer language)



# Datapath Design

---

More steps...

- Pick computation blocks  
processor: alu
- Determine connections  
data-dependencies among different blocks  
i.e., the *datapath*
- Determine control inputs to datapath blocks

... and then put everything together.

Cross-cutting issue: **clocking strategy**  
when do storage elements get updated?



# Datapath Design Example

---

Example: (unsigned integers)

```
x = 0;  
for (i=1; i <= N; i++)  
    x = x + i;
```

Here  $N$  is an input and we should produce the result that is stored in  $x$ .

First step: make the specification precise in terms of signals and clocks.



# Datapath Design Example

---

## Better specification of I/O behavior:

- Input  $N$  arrives on a bus that is 4 bits wide and  $N$  is non-zero
- Output  $x$  is 7 bits wide
- Output  $xdone$  (1 bit) is set to 1 when the  $x$  output holds the correct data
- $xdone$  stays high for 1 cycle, after which the next  $N$  input is read and the computation proceeds as before
- Signals change at the positive edge of the clock



# Pick Storage Elements

---

There is normally a choice here. For our example:

- i: 4 bit storage element
- N: 4 bit storage element
- x: 7 bit storage element
- xdone: 1 bit output signal

Another option: rewrite the loop and eliminate one of the storage elements!

```
x = 0;  
for (i=N; i >= 1; i--)  
    x = x + i;
```





# Translate Specification

---

Pick states, and determine operations in each state.

A systematic way: translate program using `gotos...`

`initial:`

`xdone = 0; x = 0; i = N;`

`goto loop;`

`loop:`

`xdone = 0; x = x + i; i = i - 1;`

`if (i == 0) goto done;`

`else goto loop;`

`done:`

`xdone = 1;`

`goto initial`



# Translate Specification

---

Idea:

- Each label is a state
- Advance from one state to the next every cycle
- End of program fragment at each label is a goto  
all paths lead to a goto!  
no intervening labels

RTL: normally uses “<-” for assignment



# What about Concurrency?

---

Everything happens in parallel in hardware...

loop:

```
xdone = 0; x = x + i; i = i - 1;  
if (i == 0) goto done;  
else goto loop;
```

- variables are updated when the *state changes*
- the state-holding element for *i* holds the value of *i* at the beginning of the state
- computation blocks have to handle this



# Computation Blocks

---

Operations on storage elements/signals:

- *i*

- $i \leftarrow N, i \leftarrow i - 1, i == 0$

- *x*

- $x \leftarrow 0, x \leftarrow x + i$

- *xdone*


- $xdone \leftarrow 0, xdone \leftarrow 1$

You can see why *x* and *i* are state-holding elements...


Blocks: “subtract 1,” adder, compare to zero



# Computation Blocks

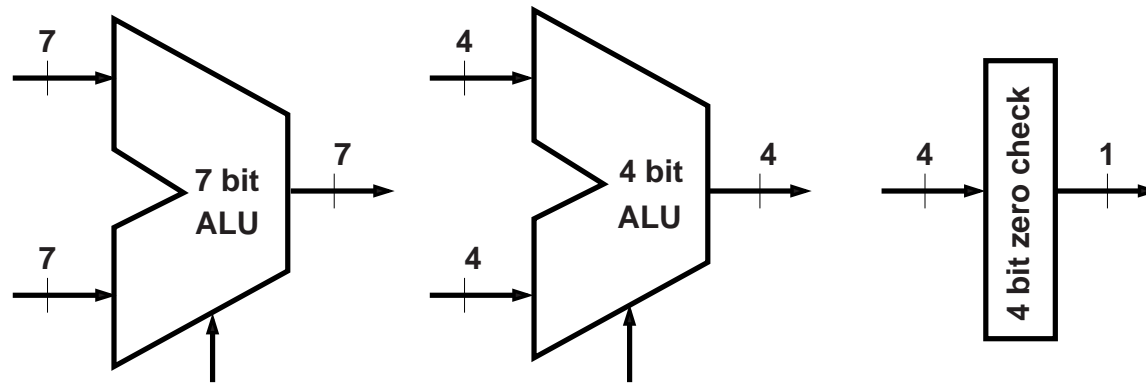

or...

 

Reduce, reuse, recycle...



# Data Dependencies

---

For each storage element, find dependencies.




- *i*
  - set to *N*, output of sub1 block
  - used by sub1 block, adder
- *x*
  - set to 0, output of adder
  - used by adder

(In general case, determine how computation blocks are interconnected too.)

What is the data flow?



# Data Dependencies

  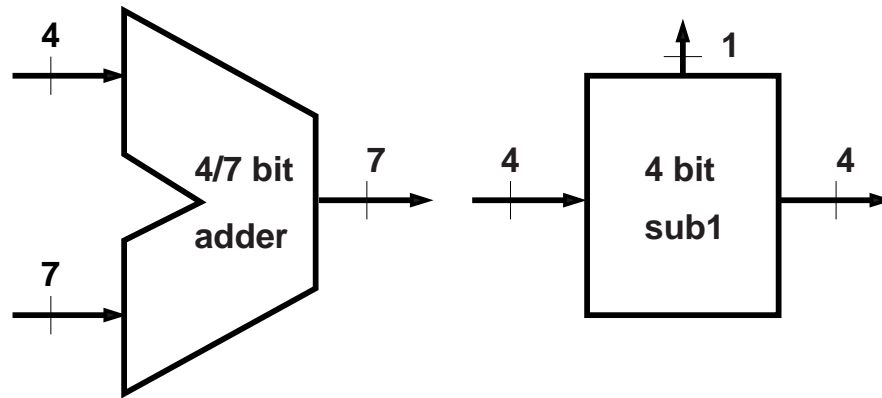



blue: state-holding  
elements that are  
implemented with  
posflops.

red: write control

*i can be set in two different ways...*



# Data Dependencies

  

blue: state-holding  
elements that are  
implemented with  
posflops.


red: control

Use MUXes...






# Data Dependencies

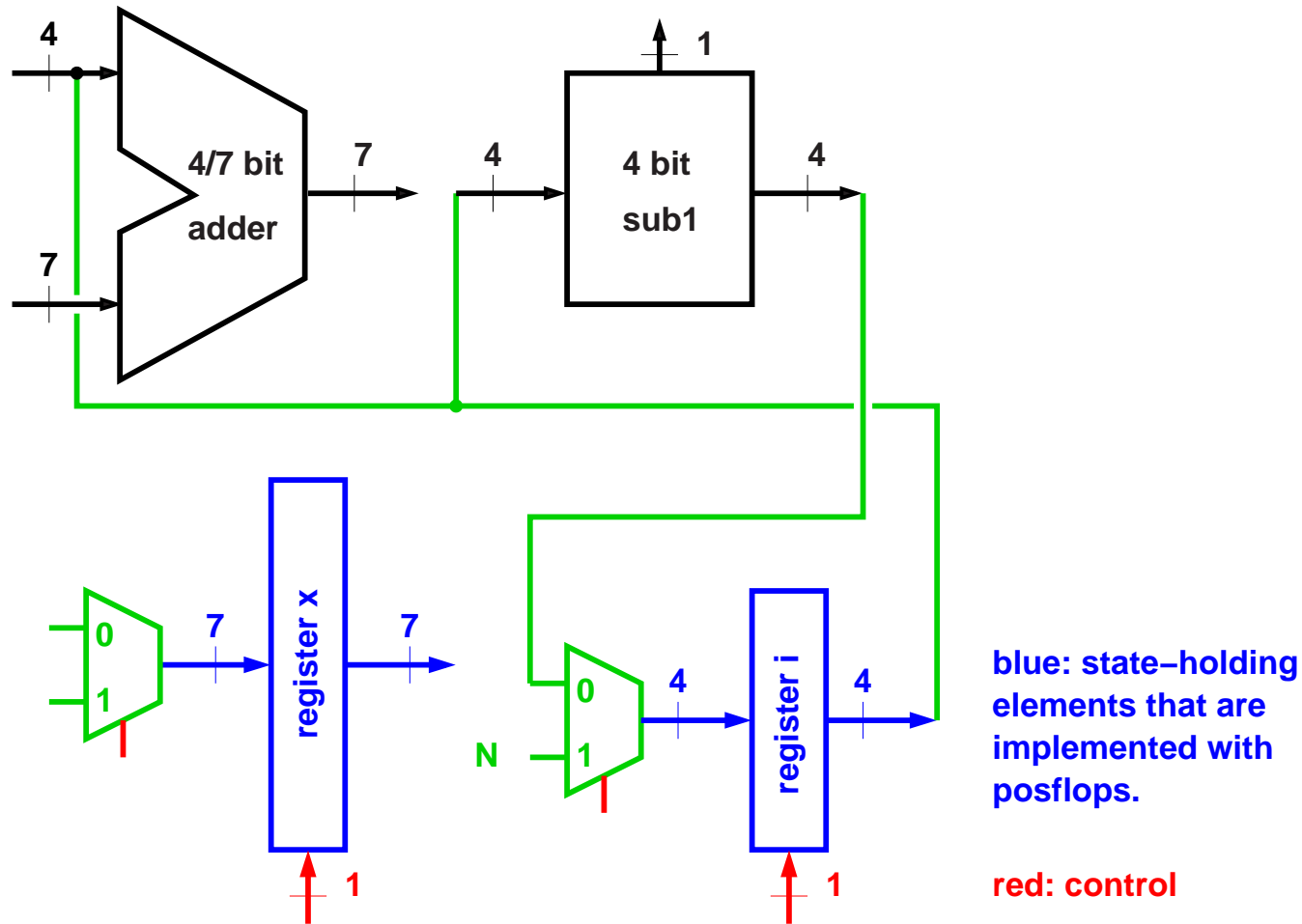

Connections for i.




# Data Dependencies

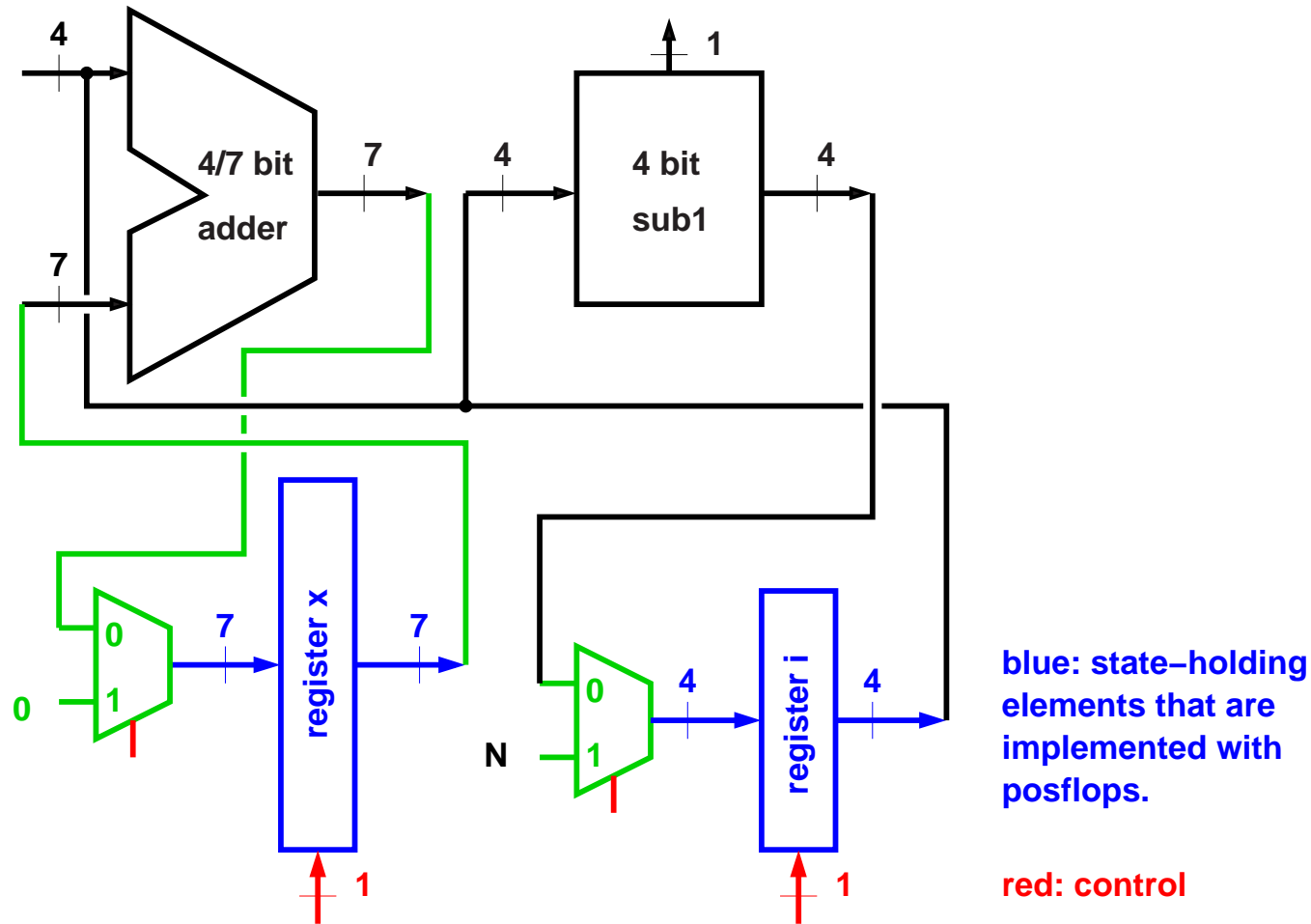

Connections for x.



# Data Dependencies

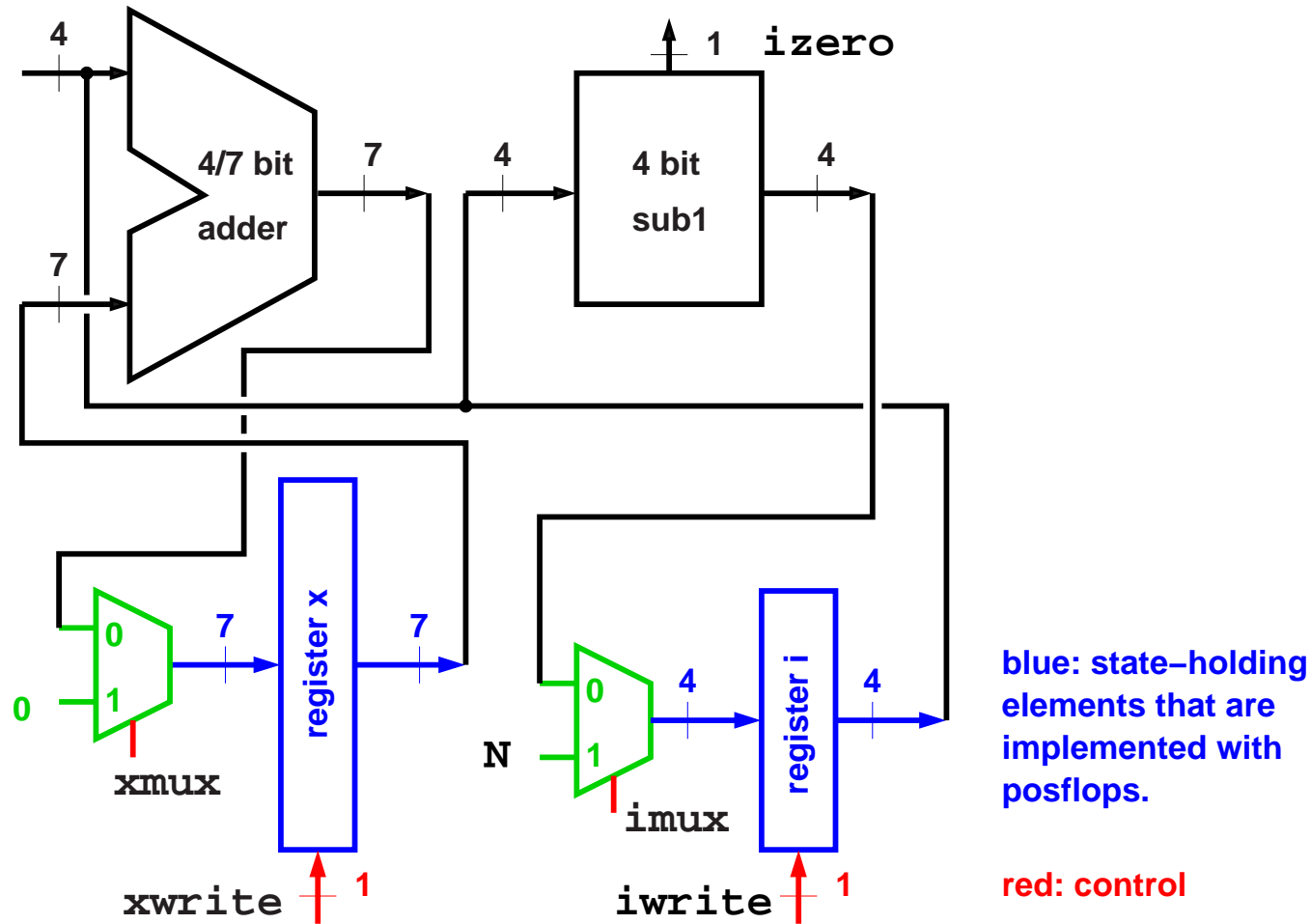

Finally: control



# Control

---

```
initial:
    xdone <- 0;
    x <- 0;
    i <- N;
    goto loop;
loop:
    xdone <- 0;    x <- x + i;
    i <- i - 1;
    if (i == 0) goto done;
    else goto loop;
done:
    xdone <- 1;
    goto initial
```

*Specify operations on data by using control signals!*



# Control

---

```
initial:
    xdone <- 0;
    xwrite <- 1; xmux <- 1;
    iwrite <- 1; imux <- 1;
    goto loop;
loop:
    xdone <- 0; xwrite <- 1; xmux <- 0;
    iwrite <- 1; imux <- 0;
    if (izero == 1) goto done;
    else goto loop;
done:
    xdone <- 1; xwrite <- 0; iwrite <- 0;
    goto initial
```

*Specify operations on data by using control signals!*



# Control

---

## Important points:


- What about `xmux`, `imux` in the done state?  
⇒ `iwrite`, `xwrite` are 0, so don't cares.
- **Note:** *each signal is set in each state!*  
⇒ we can generate them using combinational logic!
- If this is not the case, need a state-holding element to remember what the old value of the variable was...  
(sometimes referred to as an *implied flop/latch*)


 
# Control

---

Format: izero/xdone xwrite xmux iwrite imux




Next step: state assignment/state table



# Control

Format: izero/xdone xwrite xmux iwrite imux

s0 s1

 

Next: state tables, logic design





# Control

---

After some logic synthesis...

- $x_{done} = s_0$
- $x_{write} = \overline{s_0}$
- $i_{mux} = \overline{s_0} \cdot \overline{s_1}$
- $x_{mux} = \overline{s_0} \cdot \overline{s_1}$
- $i_{write} = 1$
- $News_0 = \overline{s_0} \cdot s_1 \cdot i_{zero} \cdot \overline{Reset}$
- $News_1 = (\overline{s_0} \cdot \overline{s_1} + s_1 \cdot \overline{i_{zero}}) \cdot \overline{Reset}$

