 


The Design So Far ...



The Logic Equations ...

- $x_{done} = s_0$
- $x_{write} = \overline{s_0}$
- $i_{mux} = \overline{s_0} \cdot \overline{s_1}$
- $x_{mux} = \overline{s_0} \cdot \overline{s_1}$
- $i_{write} = 1$
- $News_0 = \overline{s_0} \cdot s_1 \cdot i_{zero} \cdot \overline{Reset}$
- $News_1 = (\overline{s_0} \cdot \overline{s_1} + s_1 \cdot \overline{i_{zero}}) \cdot \overline{Reset}$



The CAST Language

A Circuit Description Language
(looks a lot like a programming language)

CAST objects:

NODES: connection points / wires
(look a lot like variables)

BLOCKS: gates connected together through nodes
(look a lot like procedures)



The Initial Parts List ...

node CLK, _CLK;
node Reset;
node Vdd, GND;
node TRUE = Vdd;
node FALSE = GND;

global clock
global reset
supply and ground
source of logical 1
source of logical 0

Nand2()(node a, b; node out)
Nor2()(node a, b; node out)
Inv()(node in; node out)

2-input NAND gate
2-input NOR gate
Inverter

posFLOP()(node in, out)
negFLOP()(node in, out)

pos edge-triggered Flip-Flop
neg edge-triggered Flip-Flop
(clock is implicit)
(no complemented output)



A CAST Header

Looks like a C function prototype:

```
define Negater (int N) (node[N] in, out; node sel) {  
    ...  
}
```

*numeric parameters
control size of circuit
i.e. replication of parts*

*interface -- nodes and
arrays of nodes that
connect this block
to the rest of the
circuit*


definition of the Negater block



Defining a Logic Block


```
define And2( ) (node a, b; node out)
{
  node _and;

   Nand2() (a,b,_and);
  Inv() (_and,out);
}
```



The Header defines the Interface ...
 
```
define And2( ) (node a, b; node out)
{
  ...
}
```




The structure inside is hidden.




Another Style ...
 
```
define And4( ) (node a,b,c,d; node out)
{
  Nand2 x(a,b);
  Nand2 y(c,d);
  Nor2 z(x.out,y.out,out);
}
```




Again with OR ...
 
```
define Or2() (node a, b; node out)
{
  node _or;
  Nor2() (a,b,_or);
  Inv () (_or, out);
}
```




Nested Instantiations ...
 
```
define Or3() (node a, b, c; node out)
{
  Or2 x(a,b);
  Or2() (x.out,c,out);
}
```



Nested Instantiations Again ...

```
define Xor2() (node a, b; node out)
{
  node _a, _b;
  Inv() (a, _a);
  Inv() (b, _b);
  And2 a1(a, _b);
  And2 a2(b, _a);
  Or2() (a1.out, a2.out, out);
}
```

 

The 1-bit Full Adder

```
define onebitadd() (node a, b, cin; node sum, cout)
{
  node x0,x1,x2;

  And2() (a,b,x0);
  And2() (a,cin,x1);
  And2() (b,cin,x2);
  Or3() (x0,x1,x2,cout);

  Xor2 x(a,b);
  Xor2() (x.out,cin,sum);
}
```

Verify these match the FA we defined earlier ...



Arrays of Nodes & Parts and Iteration

```
define Adder(int N) (node[N] a,b; node cin;  
                    node[N] sum; node cout)
```

```
{  
  onebitadd[N] o;  ← Array of FA parts
```

```
<i:N: o[i].a=a[i]; o[i].b=b[i]; o[i].sum=sum[i];>
```


```
<i:N-1: o[i].cout=o[i+1].cin;> ← Loops
```

```
o[0].cin=cin; ← Simple connections  
o[N-1].cout=cout; ← Simple connections
```

```
}
```



Here's the Diagram

 

A (Wasteful) 4 + 7 bit Adder

```
define Add47() (node[4] a; node[7] b; node[7] out)
{
  Adder(7) x;

  x.b=b;
  x.cin=GND;
  x.sum=out;

  x.a[0..3]=a;
  x.a[4]=GND;
  x.a[5]=GND;
  x.a[6]=GND;
}
```

Array assignment
connection


Just connect the unused inputs to 0.



The 1-bit Mux

```
define Mux() (node[2] a; node sel; node out)
{
  node _sel;
  Inv () (sel,_sel);
  And2 x(a[1],sel);
  And2 y(a[0],_sel);
  Or2() (x.out,y.out,out);
}
```

 
Note specification of two inputs
as node[2] array rather than
two scalar nodes



An N-bit Mux

```
define MuxN(int N) (node[N] a, b; node sel; node[N] out)
{
  <i:N:Mux() ({a[i],b[i]},sel,out[i]);>
}
```

 Note use of $\{a[i],b[i]\}$
to construct a 2-element array



Subtract-1 Unit

```
define sub1 () (node[4] in, out; node izezero)
{
  Adder(4) a;

  a.a = in;
  a.b[0] = GND;
  <i:1..3:a.b[i]=Vdd;>
  a.cin=Vdd;
  out=a.sum;
  Or2 x1(out[0],out[1]);
  Or2 x2(out[2],out[3]);
  Or2 x(x1.out,x2.out);
  Inv() (x.out,izezero);
}
```


Another correct but wasteful part!



A FLOP that is Cleared on Reset

```
define rposFLOP() (node in, out)
{
  node _r;
  Inv () (Reset,_r);
  And2 x(_r,in);
  posFLOP() (x.out,out);
}
```

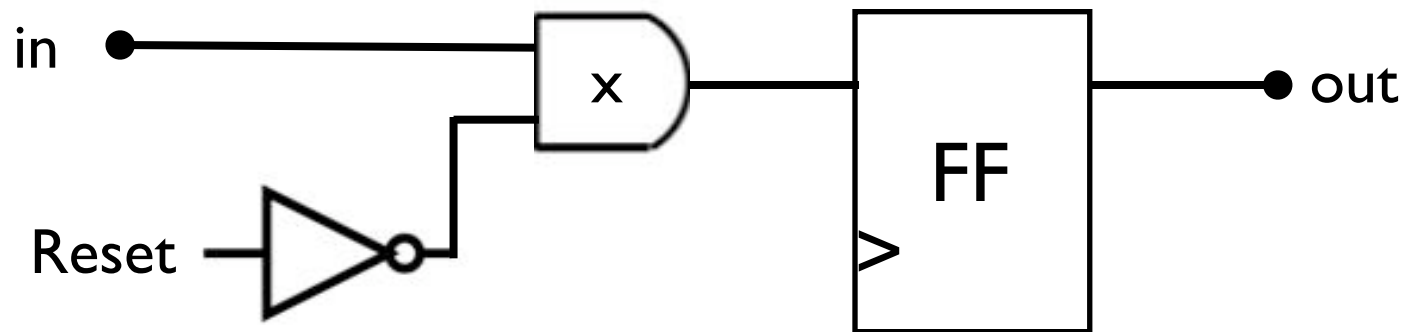Reset will be high for several clock periods



N-bit Register with Write Enable

```
define WReg(int N) (node[N] in, out; node we)
{
  Mux[N] m;


  <i:N:rposFLOP() (m[i].out,out[i]);>

  <i:N:m[i].sel = we;>
  <i:N:m[i].a[0] = out[i];>
  <i:N:m[i].a[1] = in[i];>
}
```


Create the FLOPs inside loop
rather than as array



Here's the Diagram ...

 

The Design So Far ...

 

Text



Declaring the Signals ...

```
define myckt() (node[4] N; node[7] X; node xdone)
{
  node[7] xval;
  node[4] ival;
  node xmux, xwrite, imux, iwrite, izero;
  node s0,s1,news0,news1;
  MuxN(7) mx;
  MuxN(4) mi;
  WReg(7) xreg(mx.out, xval, xwrite);
  WReg(4) ireg(mi.out, ival, iwrite);
  WReg(2) sreg({news0,news1},{s0,s1},Vdd);
  Add47 a1(ival,xval,mx.a);
  sub1 sub(ival,mi.a,izero);
}
```



Remaining Datapath Connections ...

```
mi.sel = imux;  
mx.sel = xmux;  
xval = X;  
<i:7:mx.b[i]=GND;>  
mi.b=N;
```



State Transitions ...

node _s0, _r, _izero;

Inv() (Reset, _r);

Inv() (s0, _s0);

Inv() (izero, _izero);

And4() (_r, _s0, s1, izero, news0);

Nor2 n1(s0, s1);

And2 n2(_izero, s1);

Or2 o(n1.out, n2.out);

And2 () (_r, o.out, news1);

- $News0 = \overline{s0} \cdot s1 \cdot izero \cdot \overline{Reset}$
- $News1 = (\overline{s0} \cdot \overline{s1} + s1 \cdot \overline{izero}) \cdot \overline{Reset}$



Control ...

```
xdone = s0;  
Inv() (s0,xwrite);  
Nor2() (s0,s1,imux);  
imux=xmux;  
iwrite=Vdd;  
}
```

- $x_{done} = s_0$
- $x_{write} = \overline{s_0}$
- $i_{mux} = \overline{s_0} \cdot \overline{s_1}$
- $x_{mux} = \overline{s_0} \cdot \overline{s_1}$
- $i_{write} = 1$



Finally, Instantiate the Circuit

... using the myckt block we just defined

```
node[4] N;  
node[7] X;  
node xdone;  
  
myckt m(N,X,xdone);
```

