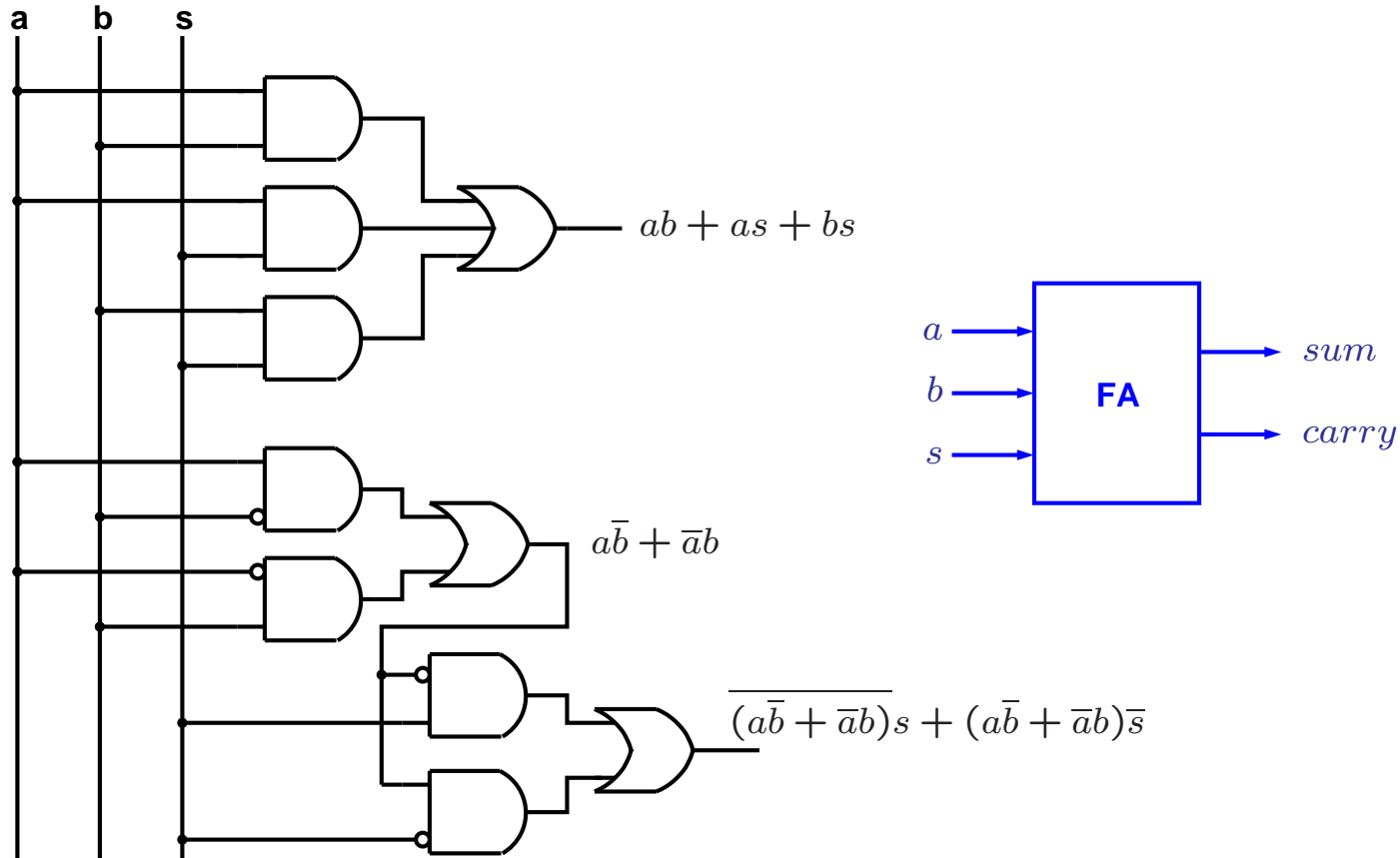


Building Blocks For Arithmetic

Binary Addition: recall the full-adder design.



Integer Addition

Full-adder:

- Three input bits a, b, s
- Output: two bits sum and $carry$

Logic equations and gate diagram derived from truth-tables.

What about 4-bit addition?



Integer Addition

Solution 1: write truth-table, derive logic equations, draw gate diagram.


Solution 2:

$$\begin{array}{rcccc} & 1 & 1 & 0 & 0 \\ & 1 & 0 & 1 & 0 \\ + & 0 & 1 & 1 & 1 \\ \hline 1 & 0 & 0 & 0 & 1 \end{array}$$

Use a number of full-adders!



Integer Addition

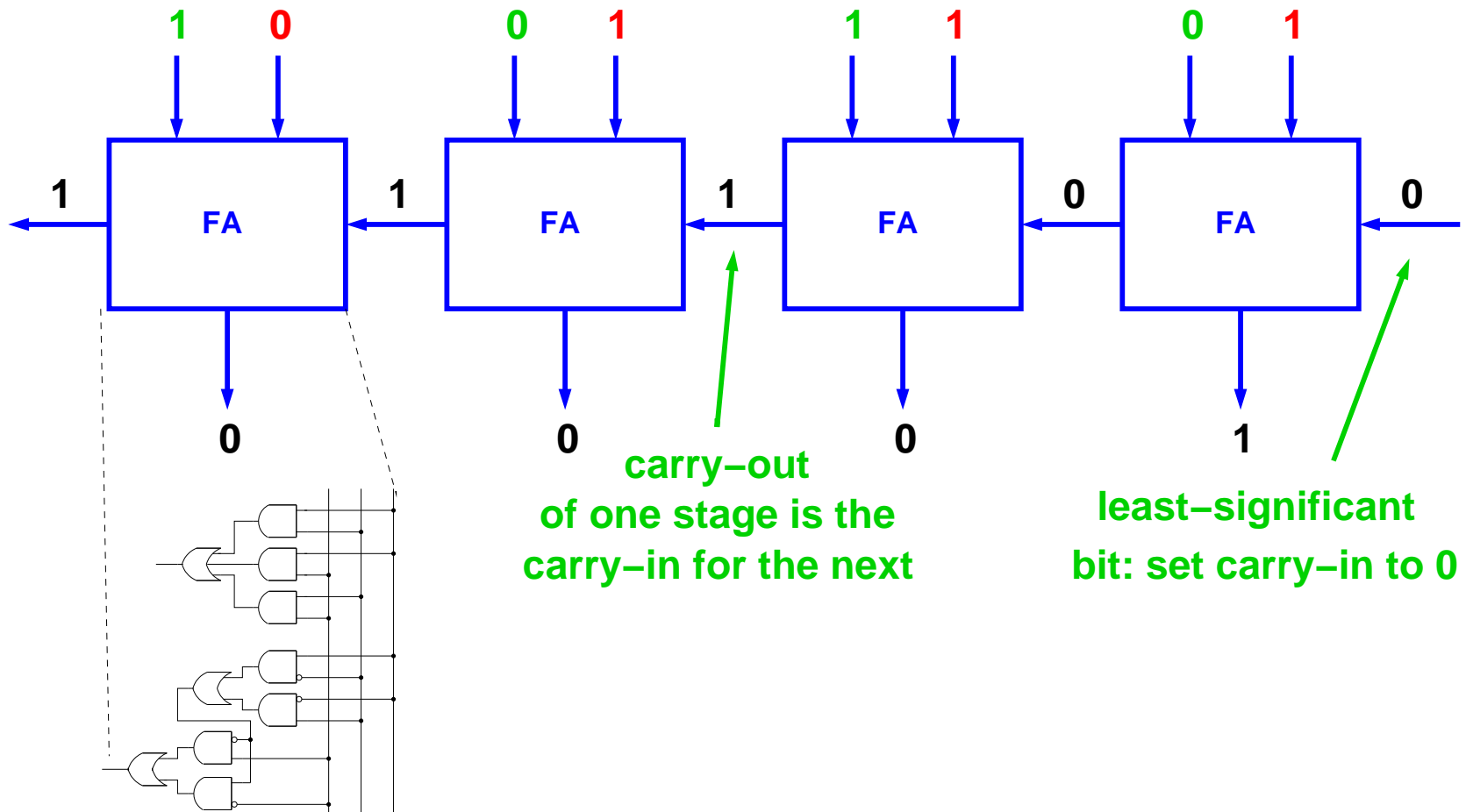

2's complement? Addition time for N bits?



Integer Addition

Observation: all we need is the carry-out...

⇒ compute carry-out *cout* for blocks

- input: 0 0, *cout* = 0 *kill*
- input: 1 1, *cout* = 1 *generate*
- input: 0 1 or 1 0, *cout*=carry-in (*cin*) *propagate*

$$cout = cin \cdot P + G$$

$$G = a \cdot b$$

$$P = a + b$$

Block codes:


$$G_{01} = G_1 + G_0P_1$$

$$P_{01} = P_0P_1$$



Integer Addition

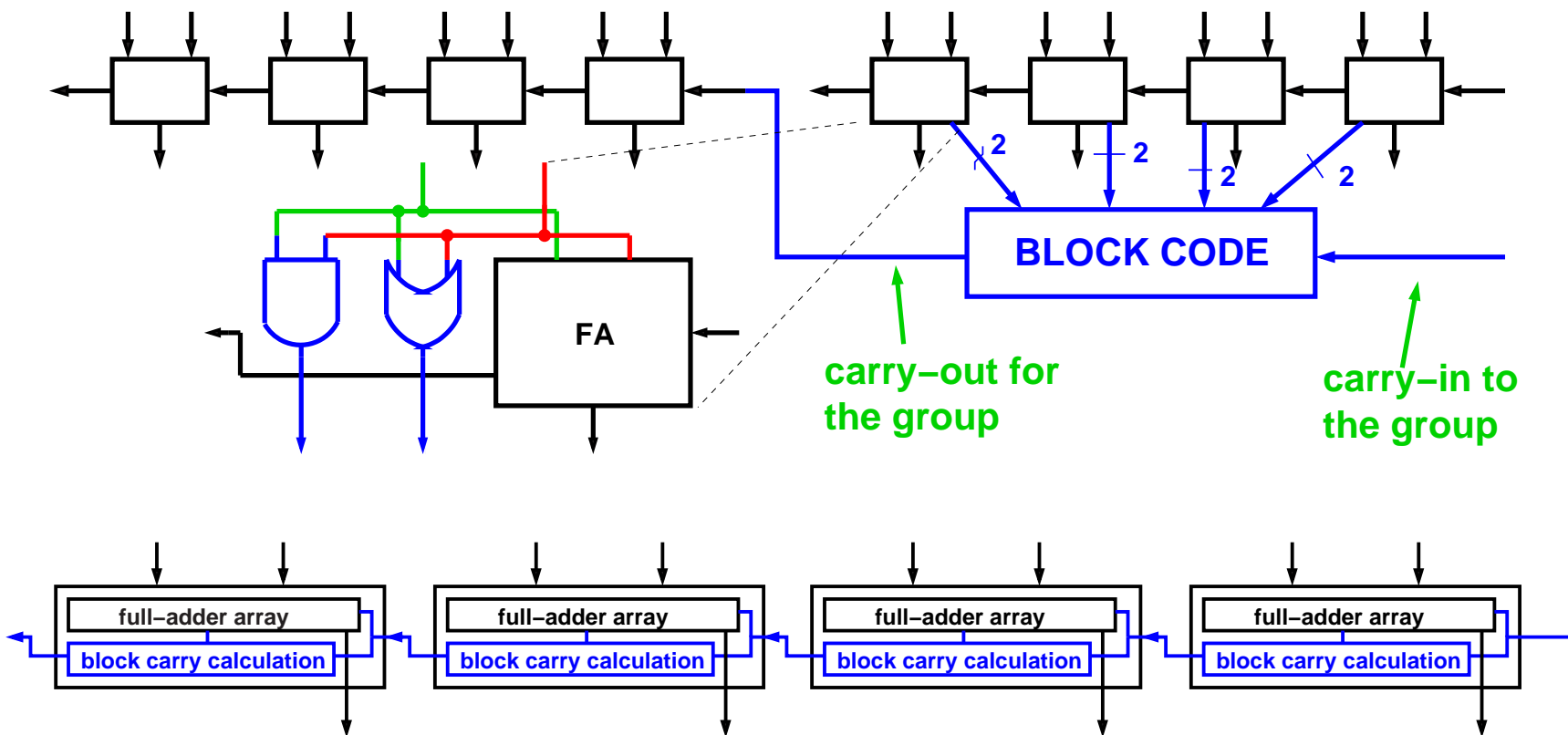Carry Lookahead adder: compute block codes to speed up carry computation.




Subtraction

To calculate $a - b$, use $a + (-b)$.

To calculate $-b$, flip all the bits and add 1.

⇒ build it using an adder

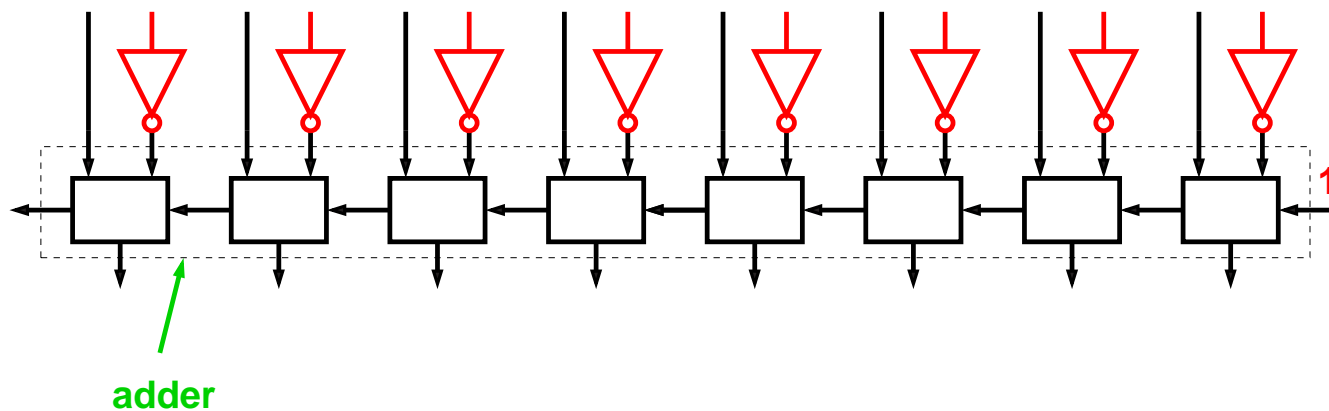


Combined Add/Subtract Unit


Given: one bit of control c , two N bit inputs a and b .
compute $a + b$ if $c = 0$, $a - b$ if $c = 1$.

- Carry-in to the adder is c
- one input: a
- other input: b if $c = 0$, complement of b if $c = 1$.

Standard element: MUX (multiplexor)

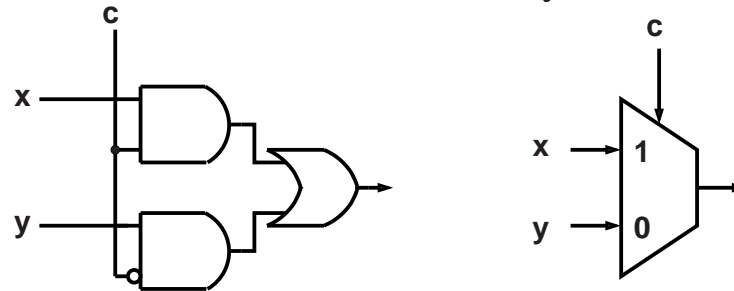

Combined Add/Subtract Unit

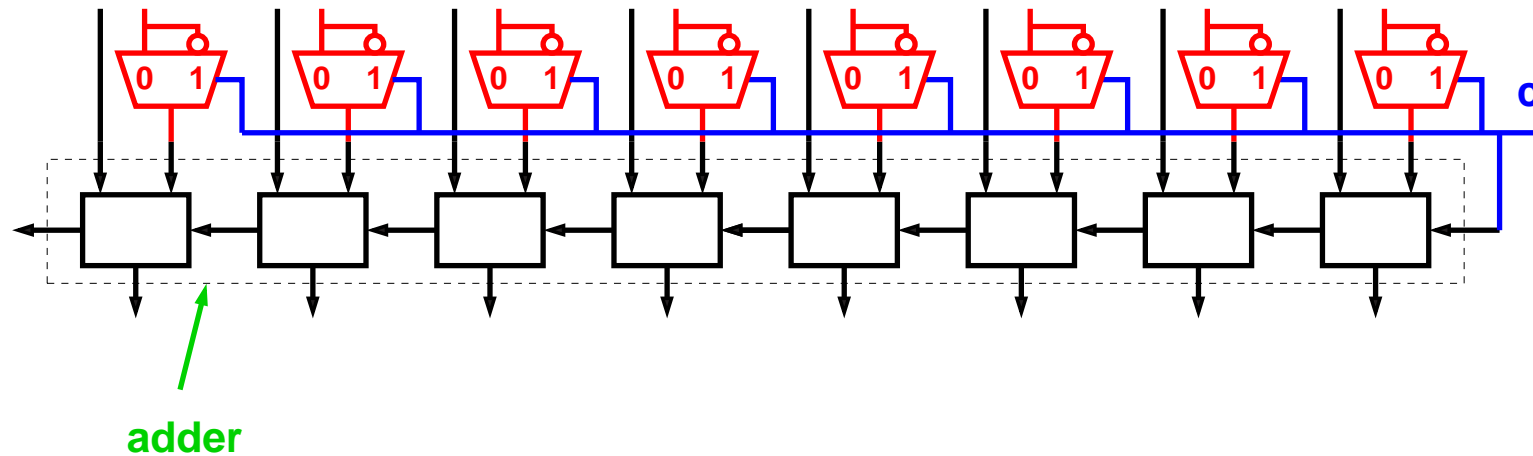


- Hierarchical design
- Reuse components
- Replication



Shifter

4-input MUX?

Simple shifter:

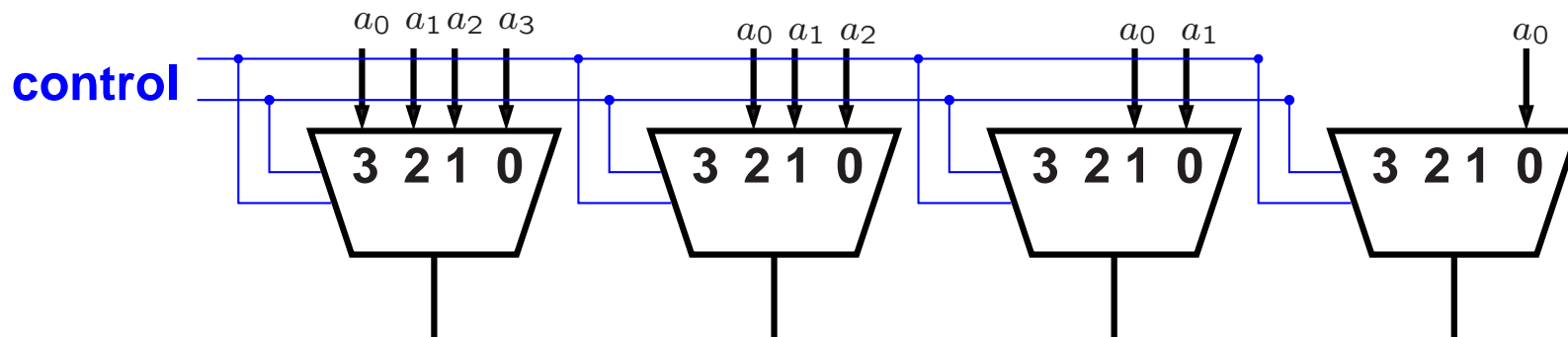

Arithmetic Logic Unit (ALU)

Example ALU: given inputs a and b , and an operation code, produce output.

Operation code:

- 000: AND
- 001: OR
- 010: NOR
- 011: ADD
- 111: SUB


How do we implement this ALU?



Selecting An Operation


2-bit decoder: 2 bit input, 4 bit output

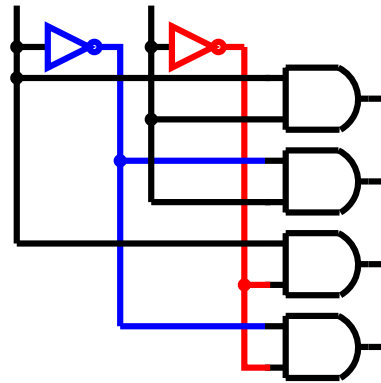- input: 00, output: 0001
- input: 01, output: 0010
- input: 10, output: 0100
- input: 11, output: 1000




ALU: One Bit

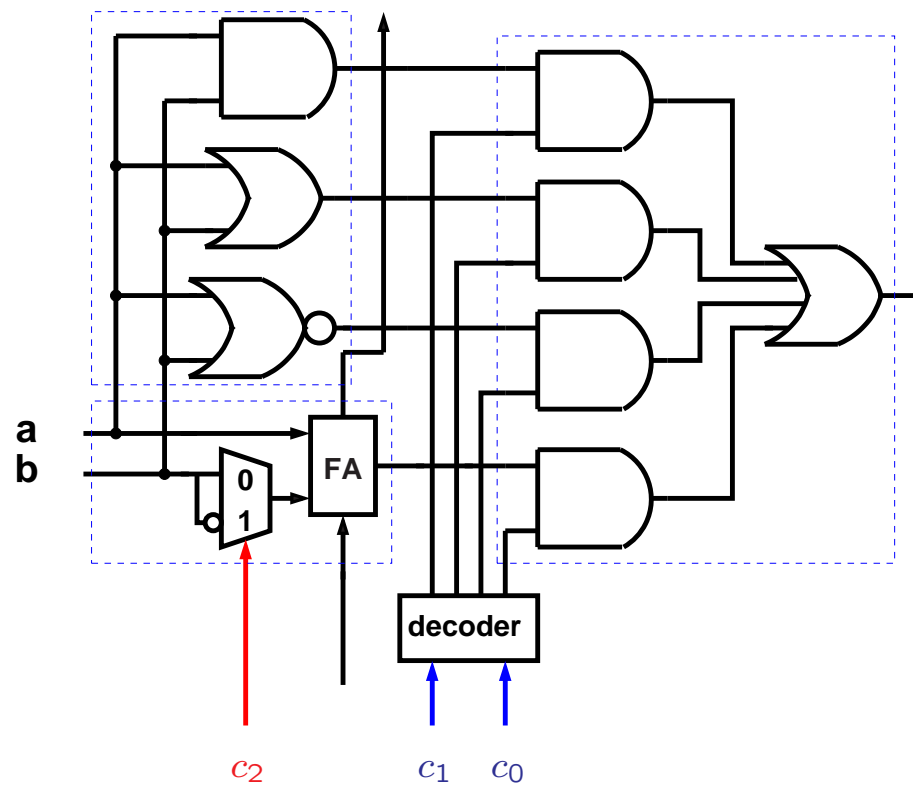Use decoder to select operation, and use combined add/subtract unit.



ALU: Multiple Bits

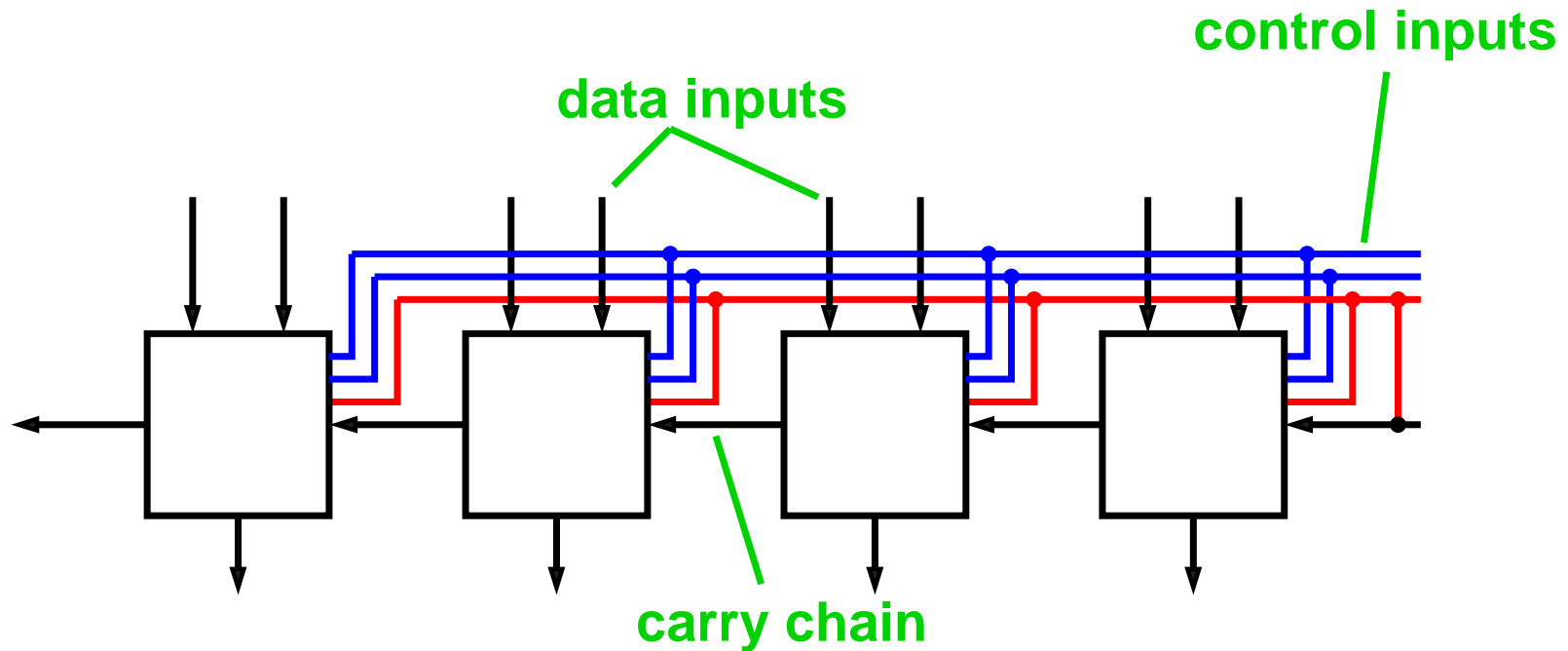Chain ALU *bit slices* to get an N bit ALU:



How can we use a better adder in the ALU?



Overflow Detection

Overflow = result of operation cannot be represented

Unsigned N -bit addition:

- Overflow = result requires more than N bits
⇒ carry-out of MSB is 1

Signed addition:

- Adding two positive numbers
- Adding two negative numbers

Overflow \equiv carry-in to MSB \neq carry-out of MSB



Comparison

When is $a < b$?

- $a < b \equiv a - b < 0$
- Subtract b from a , check sign of result
- Sign bit is MSB

When is $a = b$?

- $a = b \equiv a - b = 0$
- Subtract b from a , check if all bits are zero
- Use NOR gate

