
 




Gates and Logic

 

See: P&H Appendix C.2, C.3




  
- Acts as a *conductor* or *insulator*
- Can be used to build amazing things...






 
- One current controls another (larger) current
- Static Power:
 - Keeps consuming power when in the *ON* state
- Dynamic Power:
 - Jump in power consumption when switching



 


 

Boron

 


Silicon

 


Phosphorus

Silicon

 


N-Type: Silicon + Phosphorus

 



mobile electrons $\Rightarrow$ conductor
 $n_e + v_h \Rightarrow$ depleted $\Rightarrow$ ins.


P-Type: Silicon + Boron

 


 mobile holes $\Rightarrow$ Cond.
 $\Rightarrow$ depleted $\Rightarrow$ Ins.






 

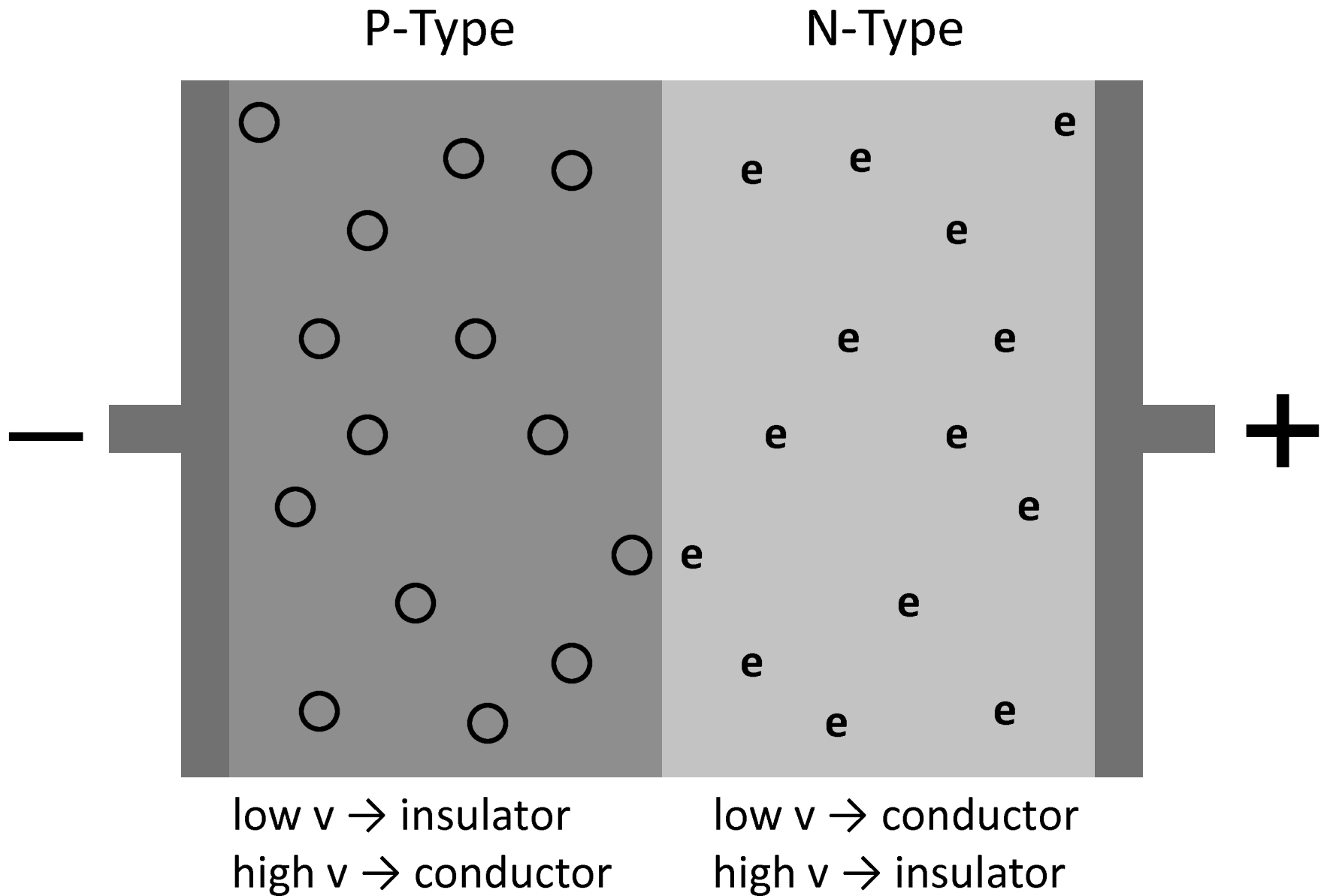

 



PN Junction “Diode”

   


Conventions:

$v_{dd} = v_{cc} = +1.2v = +5v = hi$

$v_{ss} = v_{ee} = 0v = gnd$

 
 


 



- Solid-state switch: The most amazing invention of the 1900s

Emitter = “input”, Base = “switch”, Collector = “output”


PNP Transistor

  

NPN Transistor

  


P-type FET

 


- Connect Source to Drain when Gate = lo
- Drain must be vdd, or connected to source of another P-type transistor

N-type FET

 


 - Connect Source to Drain when Gate = hi
- Source must be vss, or connected to drain of another N-type transistor



In	Out
5V	0V
0V	5V

voltage

 


Gate delay

- transistor switching time
- voltage, propagation, fanout, temperature, ...

CMOS design


(complementary-symmetry metal–oxide–semiconductor)

- Power consumption = dynamic + leakage

 

In	Out
+5v	0v
0v	+5v

voltage

 


In	Out
T	F
F	T

truth table

Conventions:


vdd = vcc = +1.2v = +5v = hi = true = 1

vss = vee = 0v = gnd = false = 0

 


Function: NOT

- Symbol:

 


In	Out
0	1
1	0

Truth table

 


Function: NAND

- Symbol:

 


A	B	out
0	0	1
0	1	1
1	0	1
1	1	0

 




Function: NOR

- Symbol:

 

A	B	out
0	0	1
0	1	0
1	0	0
1	1	0

  
 
$$\boxed{\text{NOT } (A \text{ and } B) = (\text{NOT } A) \text{ or } (\text{NOT } B)}$$



NAND is universal (so is NOR)

- Can implement any function with just NAND gates
 - De Morgan's laws are helpful (pushing bubbles)
- useful for manufacturing

  E.g.: XOR (A, B) = A or B but not both (“exclusive or”)



Proof: ?

Some notation:

- constants: true = 1, false = 0
- variables: a, b, out, ...
- operators:

$$\bullet \text{ AND}(a, b) = a \cdot b$$

$$\bullet \text{ OR}(a, b) = a + b$$

$$\bullet \text{ NOT}(a) = \bar{a}$$

$= a \& b$	$= a \wedge b$
$= a b$	$= a \vee b$
$= !a$	$= \neg a$

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

Identities useful for manipulating logic equations

– For optimization & ease of implementation

$$a + 0 = a$$

$$a + 1 = 1$$

$$a + \bar{a} = 1$$

$$a 0 = 0$$

$$a 1 = a$$

$$a \bar{a} = 0$$

$$\overline{(a + b)} = \bar{a} \bar{b}$$

$$\overline{(a b)} = \bar{a} + \bar{b}$$

$$a + a b = a$$

$$a(b+c) = ab + ac$$

$$\overline{a(b+c)} = \bar{a} + \overline{bc}$$

- functions: gates $\leftrightarrow$ truth tables $\leftrightarrow$ equations
- Example: $(a+b)(a+c) = a + bc$

a	b	c	a+b	a+c	LHS	bc	RHS
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

$$(a+b)(a+c)$$

$$\begin{array}{r} a \cdot a + a \cdot c + b \cdot \underline{a} + b \cdot c \\ \hline a \cdot 1 \end{array}$$

$$a(1 + c + b) + b \cdot c$$

$$\begin{array}{c} \underbrace{\hspace{10em}} \\ | \end{array}$$

$$\begin{array}{r} a \cdot 1 \\ \hline a \end{array} + b \cdot c + b \cdot c$$