 



Gates and Logic



See: P&H Appendix C.2, C.3




 
- Acts as a *conductor* or *insulator*
- Can be used to build amazing things...






 
- One current controls another (larger) current
- **Static Power:**
 - Keeps consuming power when in the *ON* state
- **Dynamic Power:**
 - Jump in power consumption when switching



 


 

Boron

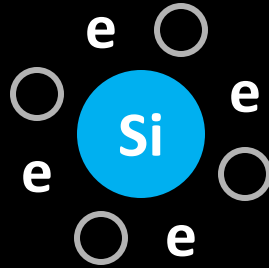


Silicon

 


Phosphorus


Silicon

 


N-Type: Silicon + Phosphorus

 

P-Type: Silicon + Boron

 

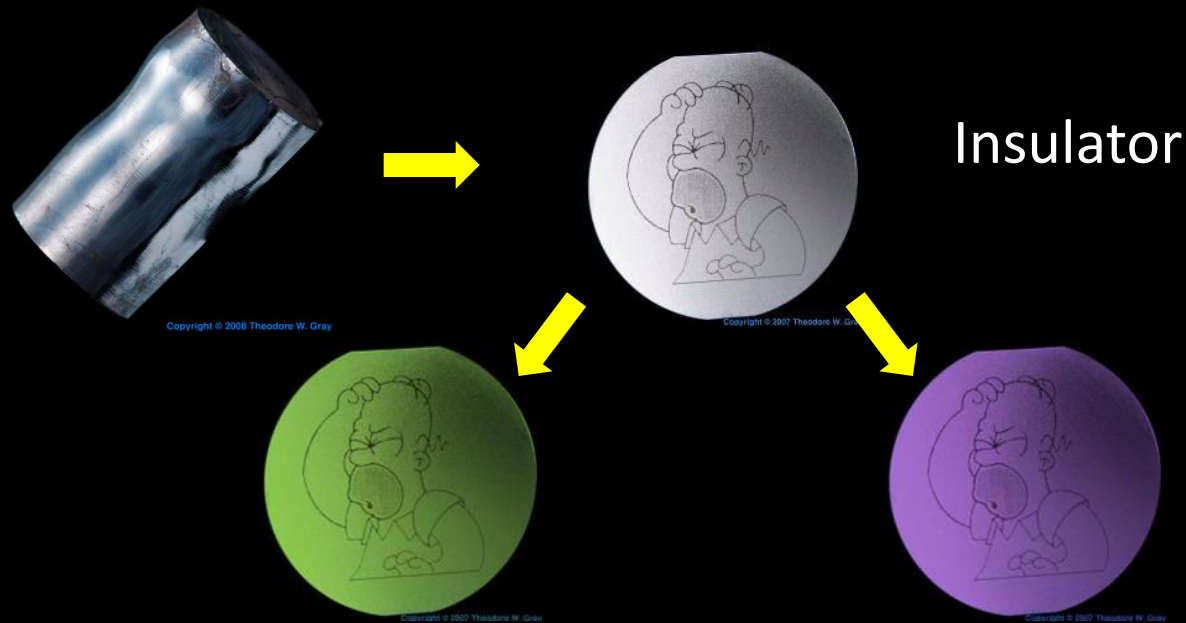



p-type (Si+Boron)
has mobile holes:


low voltage (depleted)
→ insulator
high voltage (mobile holes)
→ conductor

n-type (Si+Phosphorus)
has mobile electrons:


 
low voltage (mobile electrons)
→ conductor
high voltage (depleted)
→ insulator



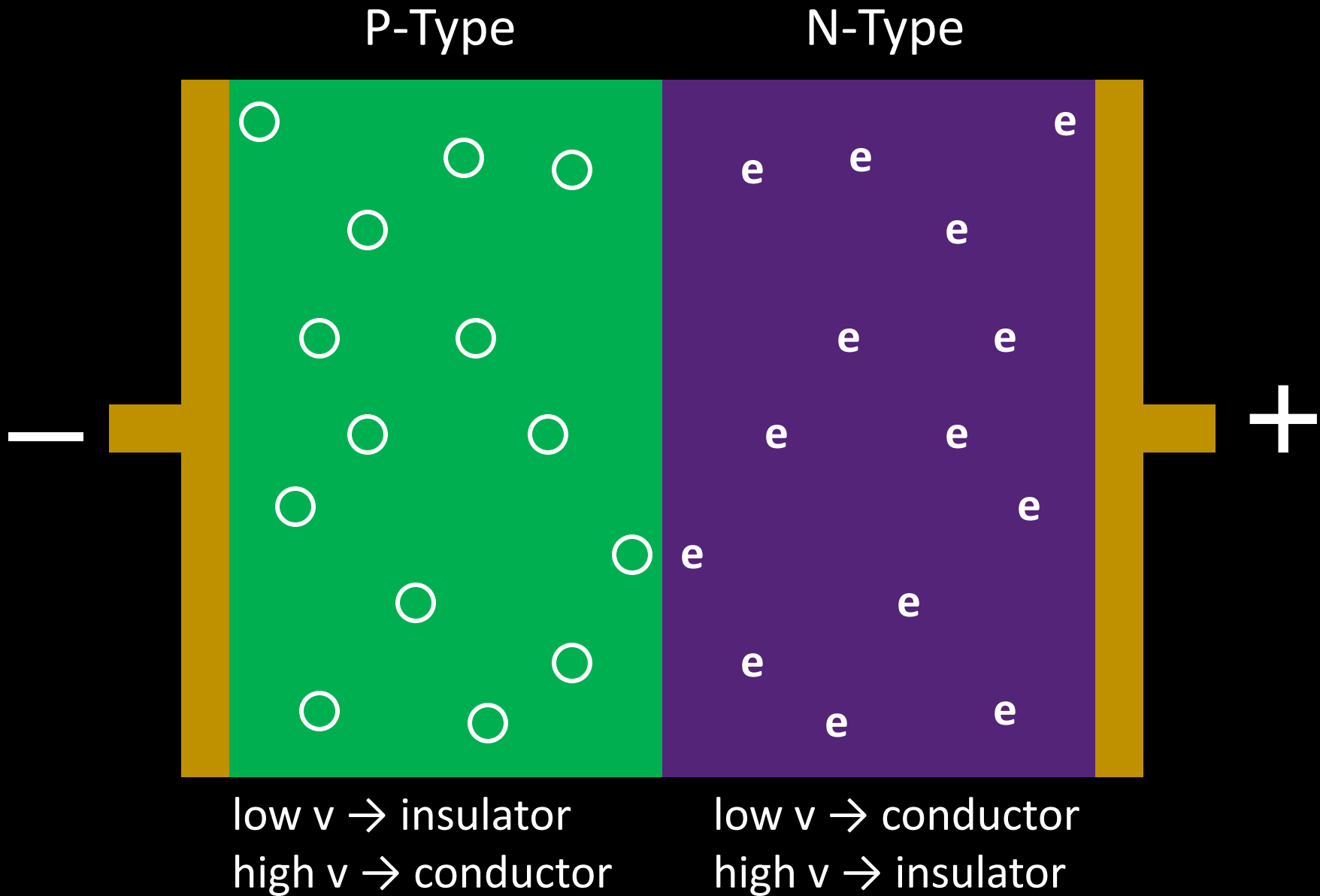

 


PN Junction “Diode”

  


Conventions:

$v_{dd} = v_{cc} = +1.2v = +5v = hi$

$v_{ss} = v_{ee} = 0v = gnd$


 


 



- Solid-state switch: The most amazing invention of the 1900s

Emitter = “input”, Base = “switch”, Collector = “output”


PNP Transistor

  

NPN Transistor

  


P-type FET

 


- Connect Source to Drain when Gate = lo
- Drain must be vdd, or connected to source of another P-type transistor

N-type FET

 


 - Connect Source to Drain when Gate = hi
- Source must be vss, or connected to drain of another N-type transistor



In	Out

voltage

 



Gate delay

- transistor switching time
- voltage, propagation, fanout, temperature, ...

CMOS design

(complementary-symmetry metal–oxide–semiconductor)

- Power consumption = dynamic + leakage

  

In	Out
+5v	0v
0v	+5v

voltage


In	Out

truth table

Conventions:


vdd = vcc = +1.2v = +5v = hi = true = 1

vss = vee = 0v = gnd = false = 0

 


Function: NOT

- Symbol:

 


In	Out
0	1
1	0

Truth table

 


Function: NAND

- Symbol:

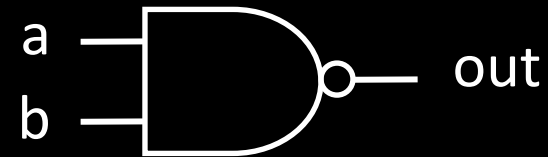


A	B	out
0	0	1
0	1	1
1	0	1
1	1	0

 



Function: NOR


- Symbol:

 

A	B	out
0	0	1
0	1	0
1	0	0
1	1	0

 - AND: 

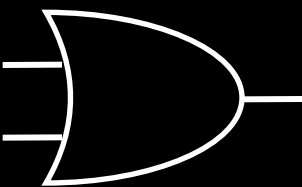
- OR: 

 - NOT: 

NAND is universal (so is NOR)

- Can implement any function with just NAND gates
 - De Morgan's laws are helpful (pushing bubbles)
- useful for manufacturing

 E.g.: XOR (A, B) = A or B but not both (“exclusive or”)



Proof: ?

Some notation:

- constants: true = 1, false = 0
- variables: a, b, out, ...
- operators:
 - $\text{AND}(a, b) = a b = a \& b = a \wedge b$
 - $\text{OR}(a, b) = a + b = a | b = a \vee b$
 - $\text{NOT}(a) = \bar{a} = !a = \neg a$

Identities useful for manipulating logic equations

— For optimization & ease of implementation

$$a + 0 = a$$

$$a + 1 = 1$$

$$a + \bar{a} = 1$$

$$a 0 = 0$$

$$a 1 = a$$

$$a \bar{a} = 0$$

$$\overline{(a + b)} = \bar{a} \bar{b}$$

$$\overline{(a b)} = \bar{a} + \bar{b}$$

$$a + a b = a$$

$$a(b+c) = ab + ac$$

$$\overline{a(b+c)} = \bar{a} + \overline{bc}$$

- functions: gates $\leftrightarrow$ truth tables $\leftrightarrow$ equations
- Example: $(a+b)(a+c) = a + bc$

a	b	c	a+b	a+c	LHS	bc	RHS
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

