

Circuits & Numbers


Kevin Walsh
CS 3410, Spring 2010
Computer Science
Cornell University

See: P&H Chapter 2.4, 2.5, 3.2, C.5

Office Hours

HW1

CSUGLab

 


How to implement a desired function?

a	b	c	out	minterm
0	0	0	0	$\bar{a} \bar{b} \bar{c}$
0	0	1	1	$\bar{a} \bar{b} c$
0	1	0	0	$\bar{a} b \bar{c}$
0	1	1	1	$\bar{a} b c$
1	0	0	0	$a \bar{b} \bar{c}$
1	0	1	1	$a \bar{b} c$
1	1	0	0	$a b \bar{c}$
1	1	1	0	$a b c$

sum of products:

- OR of all minterms where out=1

 

corollary: *any* combinational circuit *can be* implemented in two levels of logic (ignoring inverters)

How does one find the most efficient equation?


- Manipulate algebraically until...?
- Use Karnaugh maps (optimize visually)
- Use a software optimizer

For large circuits


- Decomposition & reuse of building blocks

- Voting Machine!
 - optical scan (thanks FL)
- Assume:
 - vote is recorded on paper by filling a circle
 - fixed number of choices
 - don't worry about "invalids"

Al Franken	☐
Bill Clinton	☐
Condi Rice	☐
Dick Cheney	☐
Eliot Spitzer	☐
Fred Upton	☐
Lizard People Write-in	☐

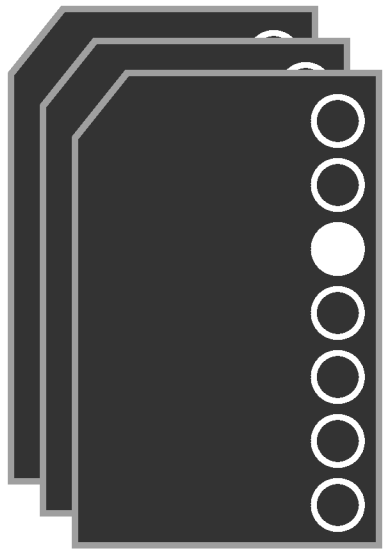

Ballots

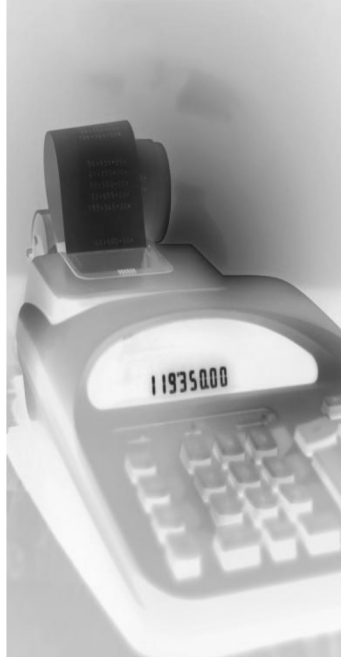

The 3410 optical scan
vote counter reader
machine

5 Essential Components?

- Input: paper with at exactly one mark
- Datapath: process current ballot
- Output: a number the supervisor can record
- Memory & control: none for now


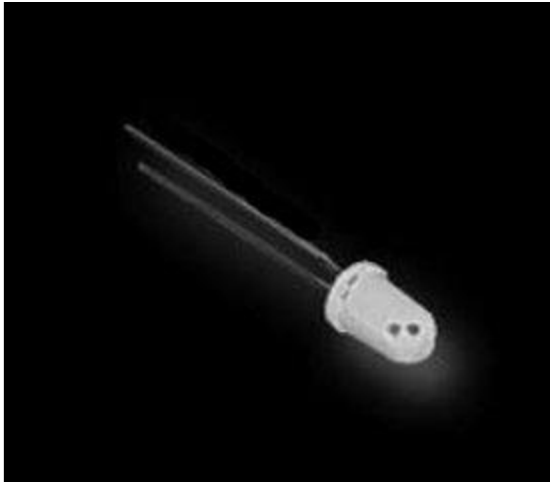


Photo-sensitive transistor

 
- photons replenish gate depletion region
- can distinguish dark and light spots on paper





- Use array of N sensors for voting machine input

7-Segment LED

 - photons emitted when electrons fall into holes



 

 

N might be large

- Routing wires is expensive

More efficient encoding?

$$\log_2(N)$$

- Base 10 - Decimal

$$\begin{array}{ccc} \underline{6} & \underline{3} & \underline{7} \\ 10^2 & 10^1 & 10^0 \end{array}$$

- Just as easily use other bases
 - Base 2 - Binary
 - Base 8 - Octal
 - Base 16 - Hexadecimal

$$10110 = 1 \times 2^4 + 0 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 + 0 \times 2^0$$


Counting

0
1
2
3
:
9
10
:
99
100
:
1

Output

0
1
3
4
:
7
10
11
12
:
77
100

- Base conversion via repetitive division
 - Divide by base, write remainder, move left with quotient
 
$$\begin{array}{l} 637_{10} \div 10 = 63 \text{ rem } 7 \\ \quad \div 10 = 6 \text{ rem } 3 \\ \quad \quad \div 10 = 0 \text{ rem } 6 \end{array}$$


- Base conversion via repetitive division
 - Divide by base, write remainder, move left with quotient


$637 \div 2 = 318 \text{ rem } 1$
 $\div 2 = 159 \text{ rem } 0$
 $\div 2 = 79 \text{ rem } 1$
 $\div 2 = 39 \text{ rem } 1$
 $\div 2 = 19 \text{ rem } 1$
 $\div 2 = 9 \text{ rem } 1$
 $\div 2 = 4 \text{ rem } 1$
 $\div 2 = 2 \text{ rem } 0$
 $\div 2 = 1 \text{ rem } 0$
 $\div 2 = 0 \text{ rem } 1$

1001111012
 27d₁₆

- Base conversion via repetitive division
 - Divide by base, write remainder, move left with quotient



$$\begin{array}{rcl}
 637 \div 16 & = & 39 \text{ rem } 13 \\
 \div 16 & = & 2 \text{ rem } 7 \\
 \div 16 & = & 0 \text{ rem } 2
 \end{array}$$

 
$$\begin{aligned}
 637_{10} &= 27d_{16} \\
 &= 0x27d
 \end{aligned}$$




Implementation . . .

  - assume 8 choices, exactly one mark detected



 

 


3 inputs


- encode 0 – 7 in binary

7 outputs

- one for each LED




b2	b1	b0	d6	d5	d4	d3	d2	d1	d0
0	0	0	1	1	1	0	1	1	1
0	0	1	1	0	0	0	0	0	1
0	1	0	0	1	1	1	0	1	1
0	1	1	1	1	0	1	0	1	1
1	0	0	1	0	0	1	1	0	1
1	0	1	1	1	0	1	1	1	0
1	1	0	1	1	1	1	1	1	0
1	1	1	1	0	0	0	0	1	1

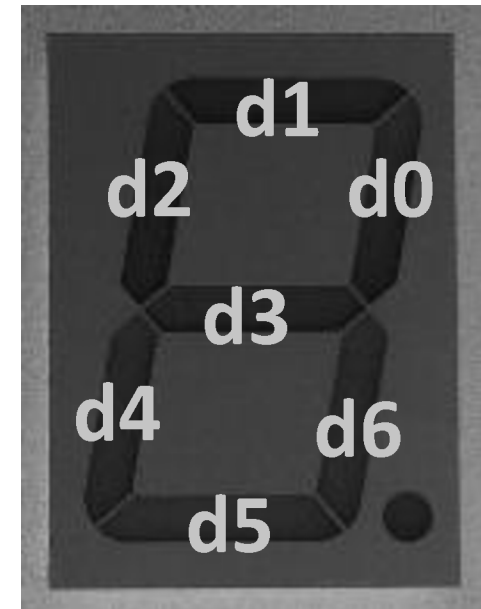

 

Ballots

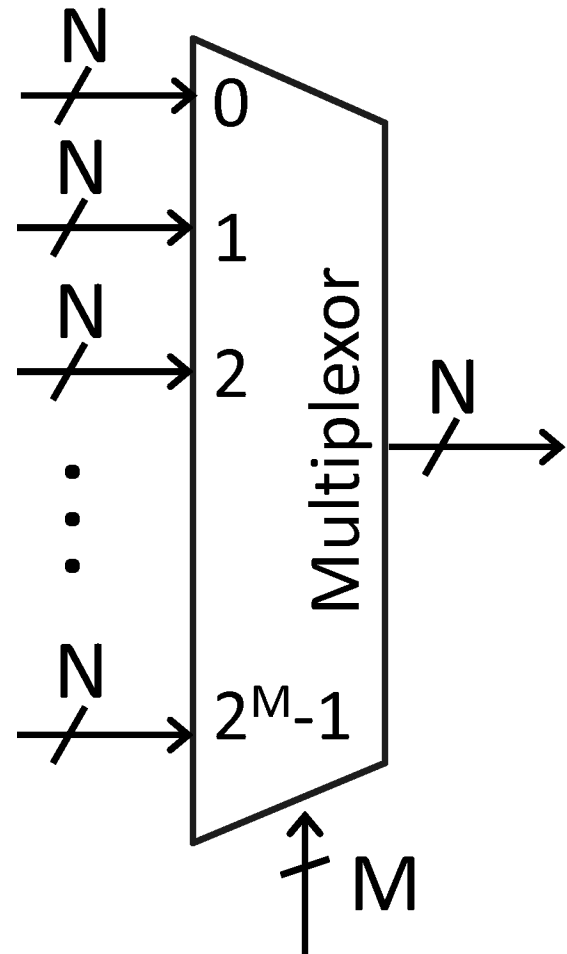 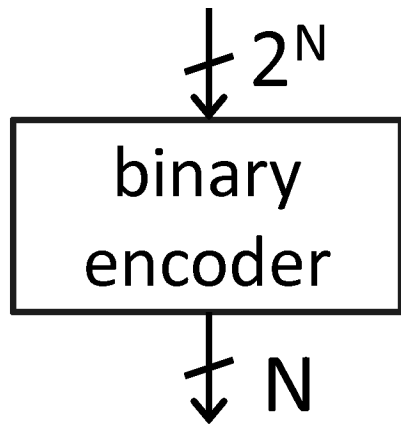The 3410 optical scan
vote counter reader
machine




$$\begin{array}{r}
 183 \\
 + 254 \\
 \hline
 437
 \end{array}$$


decimal

$$\begin{array}{r}
 001110 \\
 + 011100 \\
 \hline
 0
 \end{array}$$

Addition works the same way regardless of base

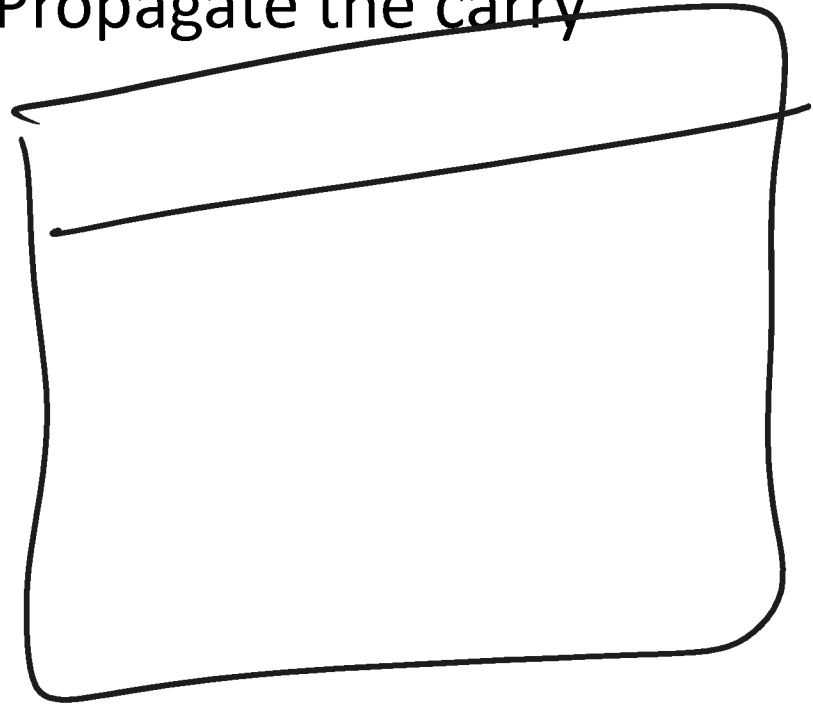- Add the digits in each position
- Propagate the carry




 

Half Adder


- Adds two 1-bit numbers
- Computes 1-bit result and 1-bit carry

A	B	C	R
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 


Full Adder

 - Adds three 1-bit numbers
- Computes 1-bit result and 1-bit carry
- Can be cascaded



4-Bit Full Adder

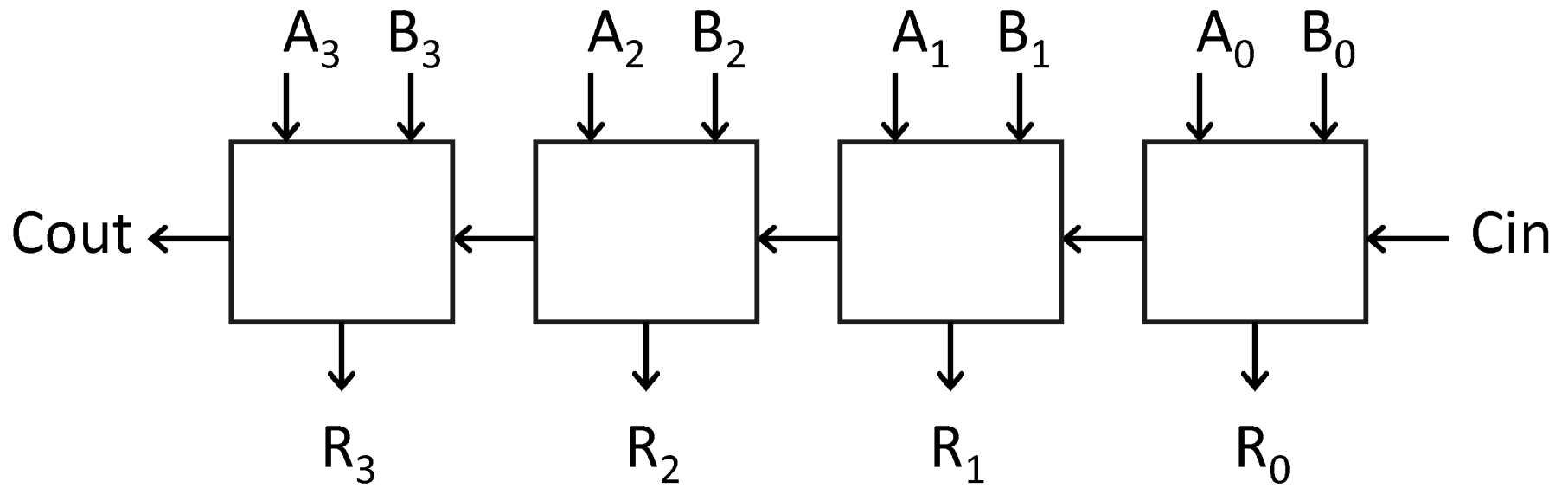- Adds two 4-bit numbers and carry in
- Computes 4-bit result and carry out
- Can be cascaded



We can now implement any combinational (combinatorial) logic circuit

- Decompose large circuit into manageable blocks
 - Encoders, Decoders, Multiplexors, Adders, ...
- Design each block
 - Binary encoded numbers for compactness
- Can implement circuits using NAND or NOR gates
- Can implement gates using use P- and N-transistors