

Circuits & Numbers

Kevin Walsh
CS 3410, Spring 2010
Computer Science
Cornell University

See: P&H Chapter 2.4, 2.5, 3.2, C.5

Office Hours

HW1

CSUGLab

How to implement a desired function?

a	b	c	out	minterm
0	0	0	0	$\bar{a} \bar{b} \bar{c}$
0	0	1	1	$\bar{a} \bar{b} c$
0	1	0	0	$\bar{a} b \bar{c}$
0	1	1	1	$\bar{a} b c$
1	0	0	0	$a \bar{b} \bar{c}$
1	0	1	1	$a \bar{b} c$
1	1	0	0	$a b \bar{c}$
1	1	1	0	$a b c$

sum of products:

- OR of all minterms where out=1

corollary: *any* combinational circuit *can be* implemented in two levels of logic (ignoring inverters)

How does one find the most efficient equation?


- Manipulate algebraically until...?
- Use Karnaugh maps (optimize visually)
- Use a software optimizer

For large circuits


- Decomposition & reuse of building blocks

- Voting Machine!
 - optical scan (thanks FL)
- Assume:
 - vote is recorded on paper by filling a circle
 - fixed number of choices
 - don't worry about "invalids"

Al Franken	☐
Bill Clinton	☐
Condi Rice	☐
Dick Cheney	☐
Eliot Spitzer	☐
Fred Upton	☐
Lizard People Write-in	☐

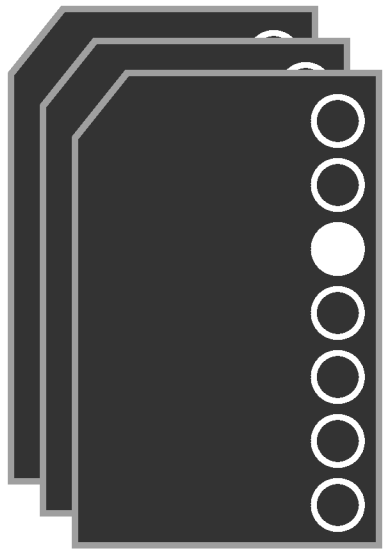

Ballots

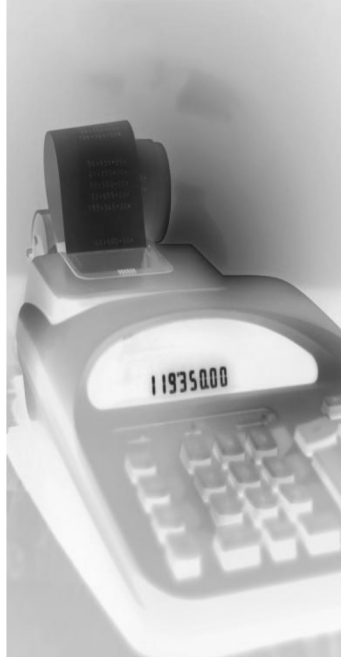

The 3410 optical scan
vote counter reader
machine

5 Essential Components?

- Input: paper with at exactly one mark
- Datapath: process current ballot
- Output: a number the supervisor can record
- Memory & control: none for now


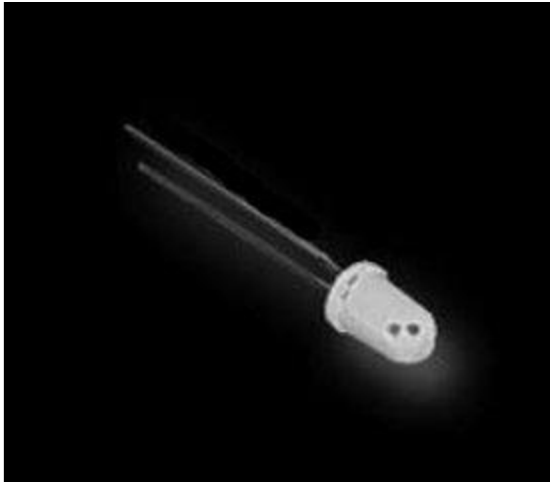


Photo-sensitive transistor

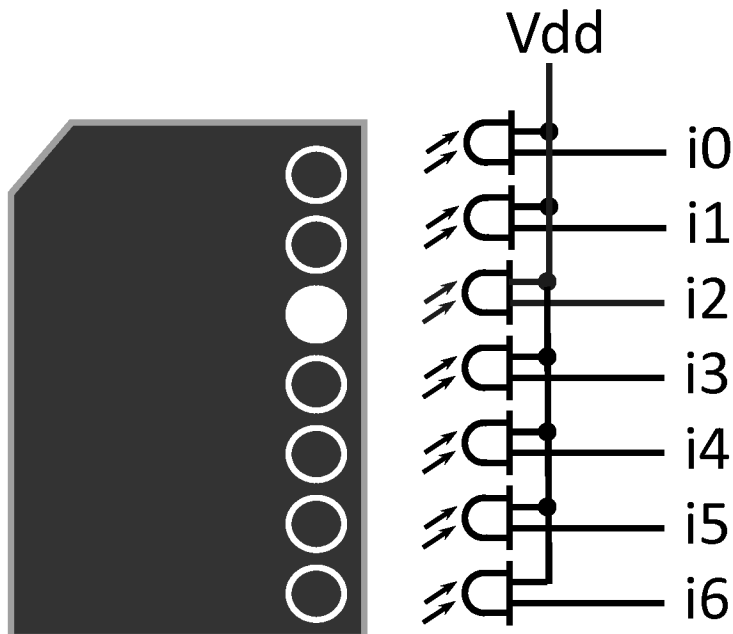- photons replenish gate depletion region
- can distinguish dark and light spots on paper






- Use array of N sensors for voting machine input

7-Segment LED

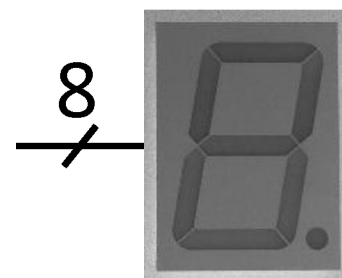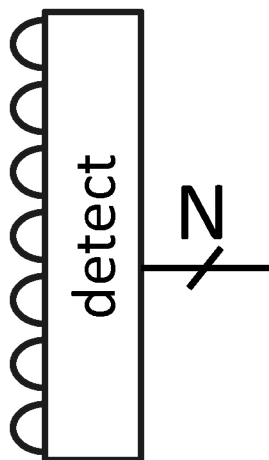- photons emitted when electrons fall into holes





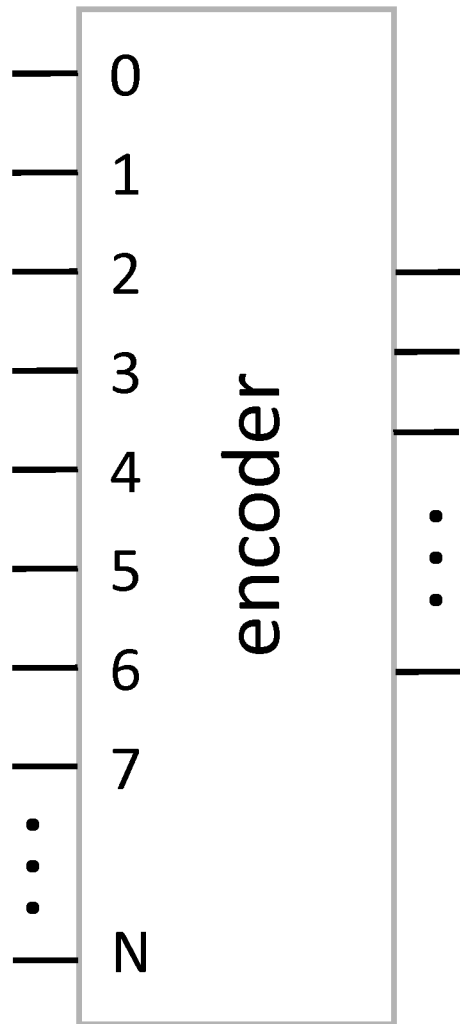

N might be large

- Routing wires is expensive

More efficient encoding?

6 3 7
 10^2 10^1 10^0

- Base 10 - Decimal
- Just as easily use other bases
 - Base 2 - Binary
 - Base 8 - Octal
 - Base 16 - Hexadecimal

Counting


- Base conversion via repetitive division
 - Divide by base, write remainder, move left with quotient

- Base conversion via repetitive division
 - Divide by base, write remainder, move left with quotient


- Base conversion via repetitive division
 - Divide by base, write remainder, move left with quotient


Implementation . . .

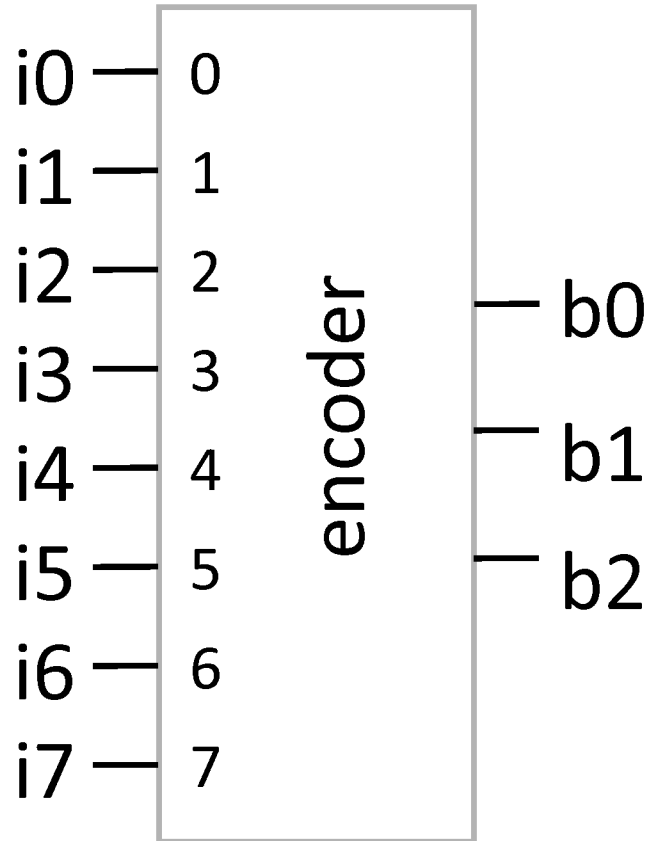- assume 8 choices, exactly one mark detected



3-bit encoder
(8-to-3)

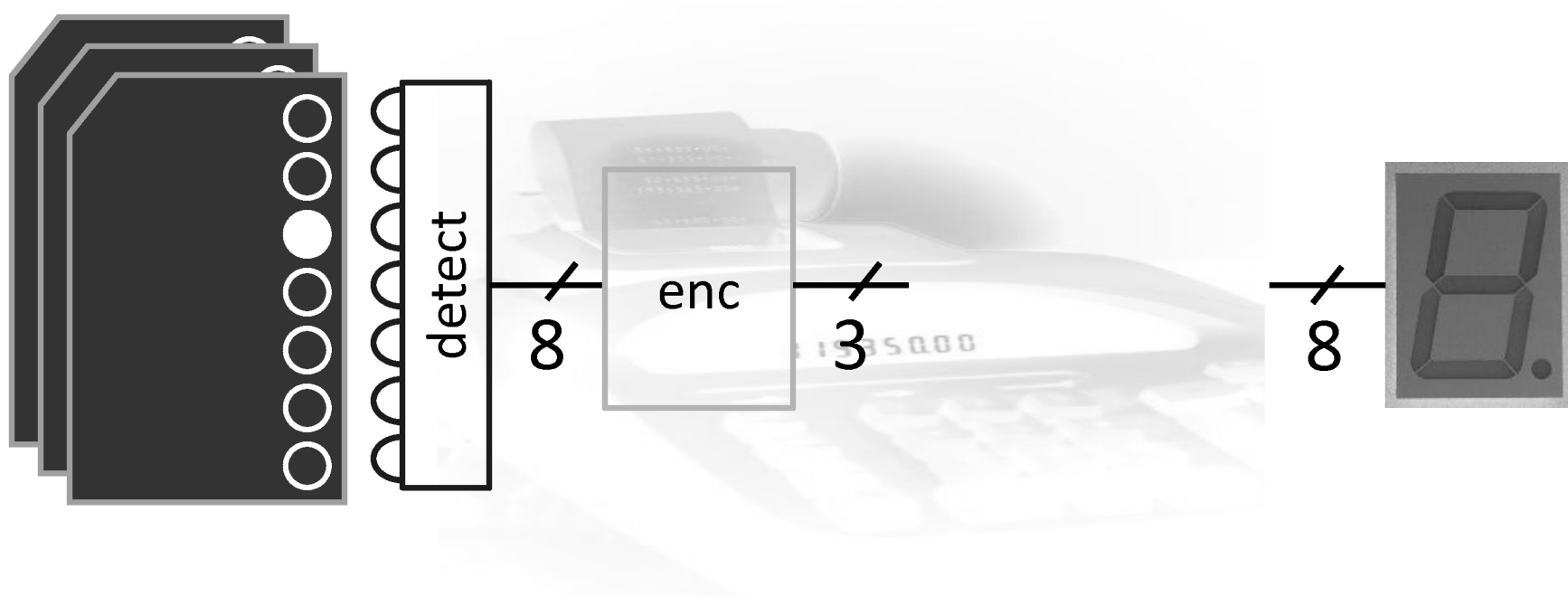

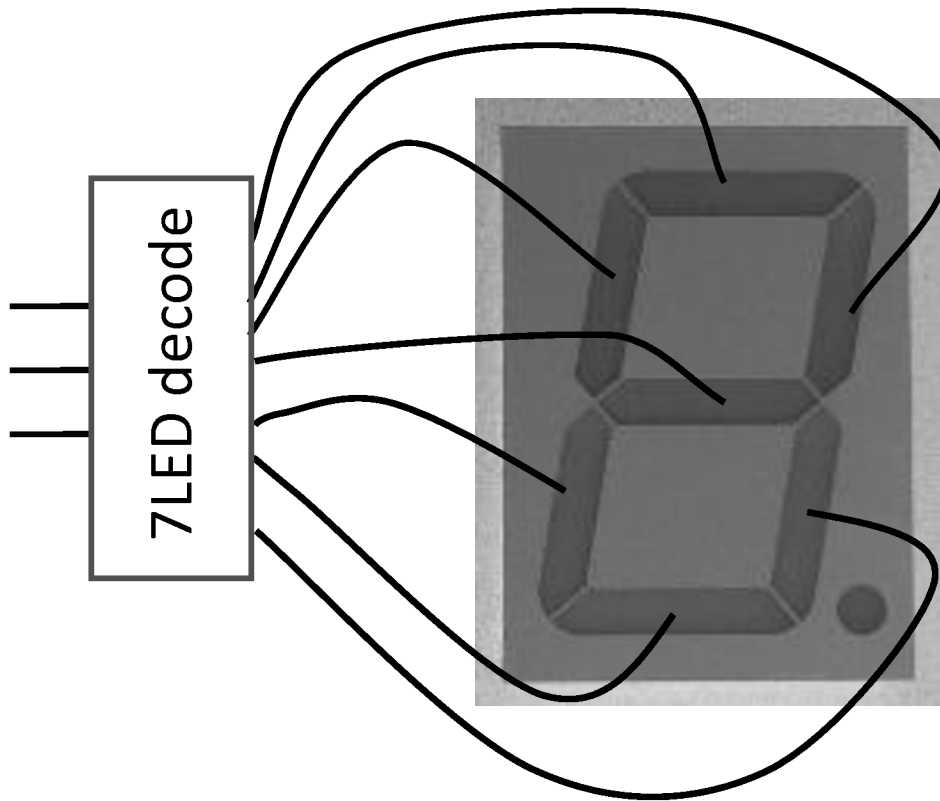


3 inputs


- encode 0 – 7 in binary

7 outputs

- one for each LED




b2	b1	b0	d6	d5	d4	d3	d2	d1	d0
0	0	0	1	1	1	0	1	1	1
0	0	1	1	0	0	0	0	0	1
0	1	0	0	1	1	1	0	1	1
0	1	1	1	1	0	1	0	1	1
1	0	0	1	0	0	1	1	0	1
1	0	1	1	1	0	1	1	1	0
1	1	0	1	1	1	1	1	1	0
1	1	1	1	0	0	0	0	1	1

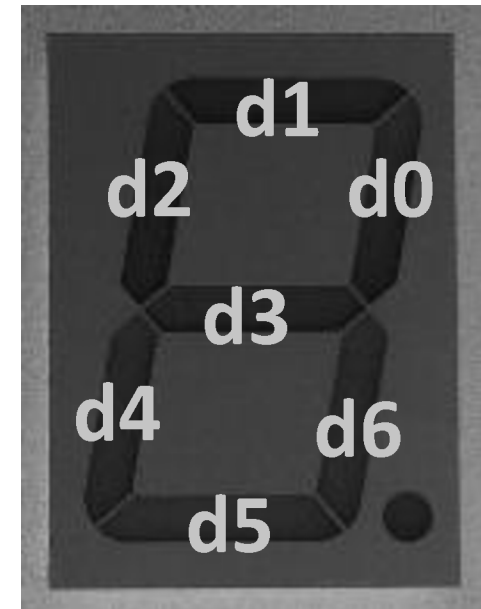

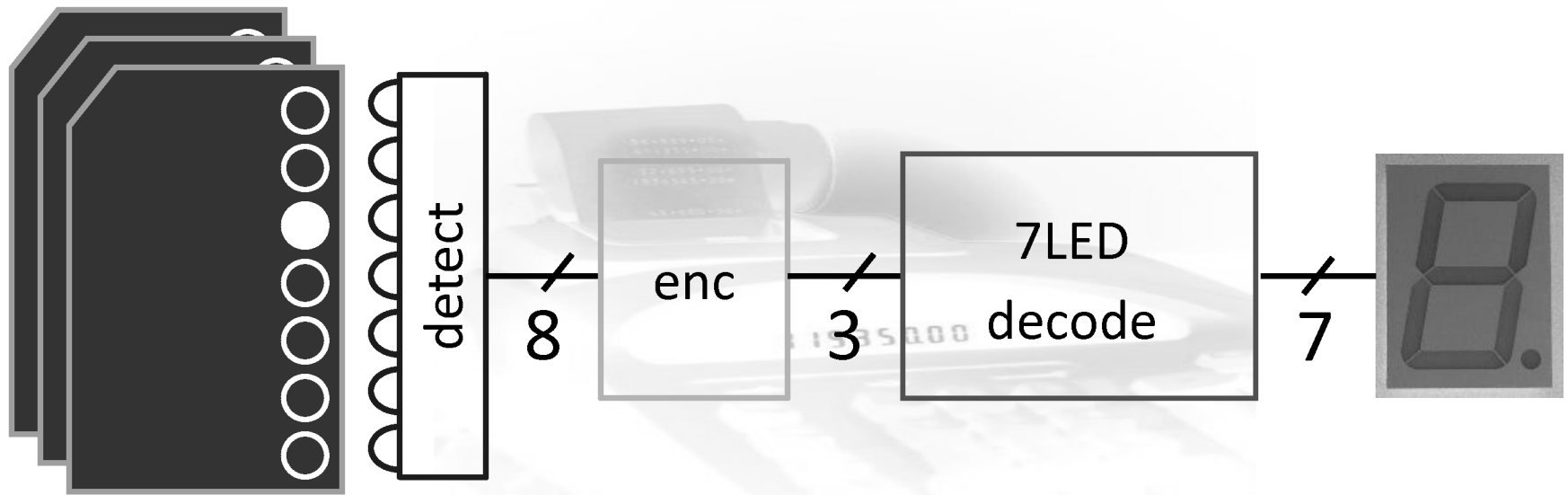

Ballots

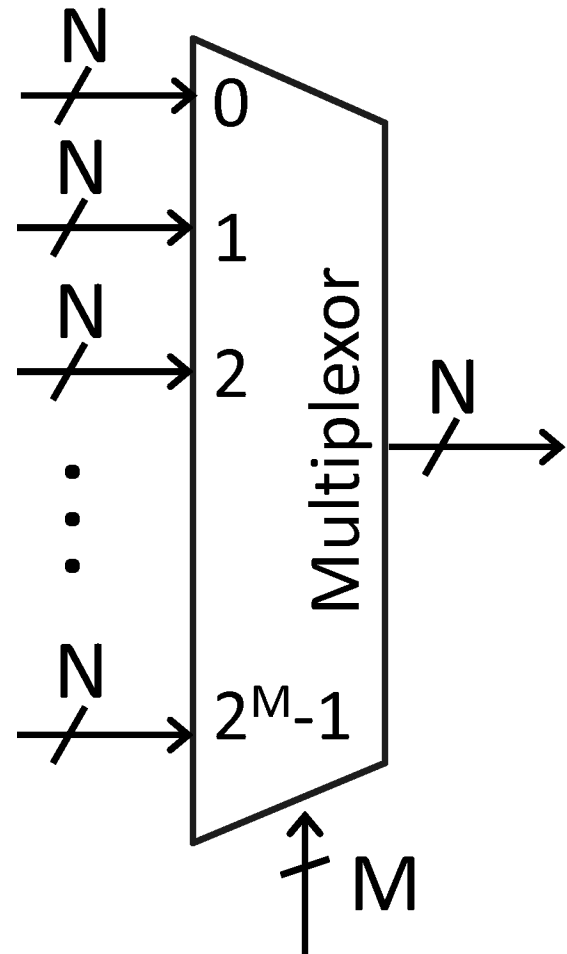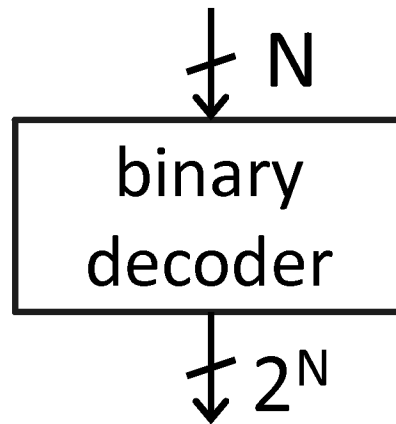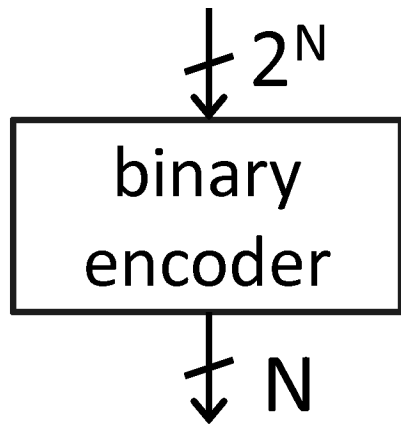The 3410 optical scan
vote counter reader
machine




$$\begin{array}{r} 183 \\ + 254 \\ \hline \end{array}$$

$$\begin{array}{r} 001110 \\ + 011100 \\ \hline \end{array}$$


Addition works the same way
regardless of base

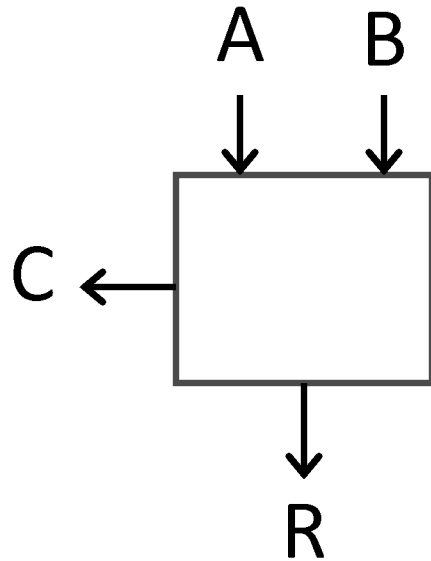- Add the digits in each position
- Propagate the carry




Half Adder

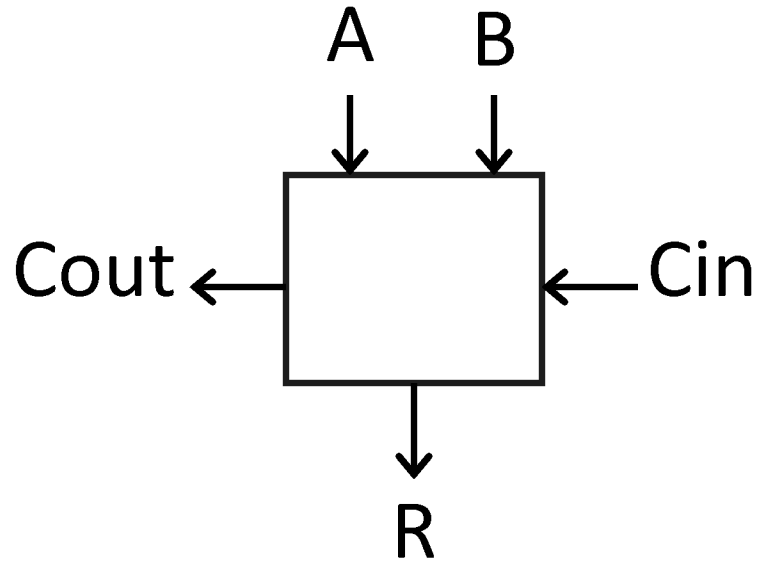- Adds two 1-bit numbers
- Computes 1-bit result and 1-bit carry




Full Adder

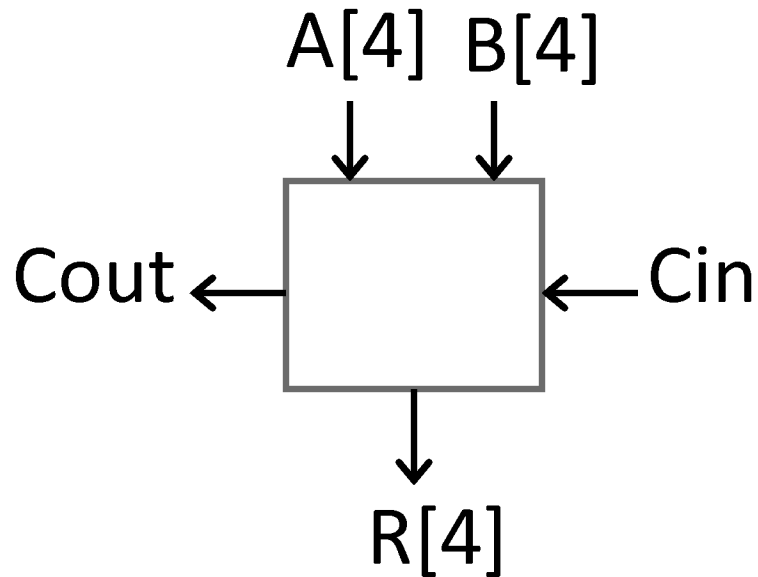- Adds three 1-bit numbers
- Computes 1-bit result and 1-bit carry
- Can be cascaded



4-Bit Full Adder

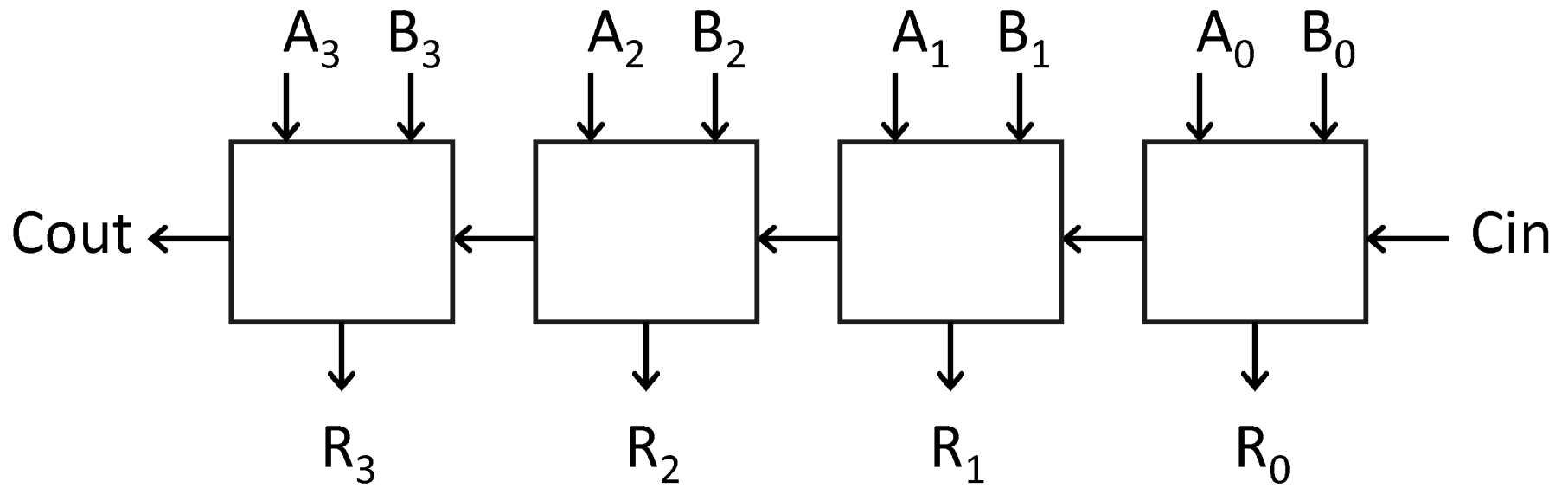- Adds two 4-bit numbers and carry in
- Computes 4-bit result and carry out
- Can be cascaded



We can now implement any combinational (combinatorial) logic circuit

- Decompose large circuit into manageable blocks
 - Encoders, Decoders, Multiplexors, Adders, ...
- Design each block
 - Binary encoded numbers for compactness
- Can implement circuits using NAND or NOR gates
- Can implement gates using use P- and N-transistors