 


Arithmetic

Kevin Walsh
CS 3410, Spring 2010
Computer Science
Cornell University

See: P&H Chapter 3.1-3, C.5-6



- Adds two 4-bit numbers, along with carry-in
- Computes 4-bit result and carry out

Addition with negatives:

- $\text{pos} + \text{pos} \rightarrow$ add magnitudes, result positive
- $\text{neg} + \text{neg} \rightarrow$ add magnitudes, result negative
- $\text{pos} + \text{neg} \rightarrow$ subtract smaller magnitude, keep sign of bigger magnitude

$\text{pos} + \text{neg} \Rightarrow$ larger minus smaller
Sign of larger



First Attempt: Sign/Magnitude Representation

- 1 bit for sign (0=positive, 1=negative)
- N-1 bits for magnitude

$$0111 = +7$$

$$1111 = -7$$

Better: Two's Complement Representation

- Leading 1's for negative numbers
- To negate any number:
 - complement *all* the bits
 - then add 1, *ignore carry out.*

$$\begin{array}{r}
 +6 = 0110 \\
 \sim 6 \quad 1001 \\
 \quad \quad +1 \\
 \hline
 -6 = 1010
 \end{array}$$

$$\begin{array}{r}
 +20 = 00010100 \\
 \quad \quad 11101011 \\
 \quad \quad \quad +1 \\
 \hline
 -20 = 11101100
 \end{array}$$

$$\begin{array}{r}
 \hline
 -20 = 11101100
 \end{array}$$

Non-negatives Negatives

(as usual):

(two's complement: flip then add 1):

$$+0 = 0000$$

$$\sim 0 = 1111$$

$$-0 = 0000$$

$$+1 = 0001$$

$$\sim 1 = 1110$$

$$-1 = 1111$$

$$+2 = 0010$$

$$\sim 2 = 1101$$

$$-2 = 1110$$

$$+3 = 0011$$

$$\sim 3 = 1100$$

$$-3 = 1101$$

$$+4 = 0100$$

$$\sim 4 = 1011$$

$$-4 = 1100$$

$$+5 = 0101$$

$$\sim 5 = 1010$$

$$-5 = 1011$$

$$+6 = 0110$$

$$\sim 6 = 1001$$

$$-6 = 1010$$

$$+7 = 0111$$

$$\sim 7 = 1000$$

$$-7 = 1001$$

$$+8 = 1000$$

$$\sim 8 = 0111$$

$$-8 = 1000$$

Signed two's complement

- Negative numbers have leading 1's
- zero is unique: $+0 = -0$
- wraps from largest positive to largest negative

N bits can be used to represent

- unsigned: $0 \dots (2^N) - 1$
 - eg: 8 bits $\Rightarrow 0 \dots 2^8 - 1 = 255$
- signed (two's complement):
 - ex: 8 bits $\Rightarrow -128 \dots 0 \dots +127$
 - $-\left(\frac{2^N}{2}\right) \dots \left(\frac{2^N}{2}\right) - 1$

Extending to larger size

$$\begin{array}{r} 0110 \\ - 1 = 1111 \end{array}$$

$$\begin{array}{r} 000010110 \\ 111111111 \end{array}$$


Truncate to smaller size

Drop leading sign bits, as long as sign doesn't change

$$\begin{array}{r} 00001111 = 15 \\ 0111 = 7 \end{array}$$

Addition with two's complement signed numbers

 - Perform addition as usual, regardless of sign (it just works)



How does that work?

$$\begin{array}{r} -154 \\ +283 \\ \hline \end{array}$$

ten's complement

$$\begin{array}{r} 999 \\ -154 \\ \hline 845 \end{array}$$

$$\begin{array}{r} 845 \\ +283 \\ \hline 1128 \end{array}$$

1128 - 1000 = 128

Overflow

- adding a negative and a positive?


Can't happen

- adding two positives?


- adding two negatives?

Rule of thumb:

 ✓ Overflow happened iff
carry into msb $\neq$ carry out of msb



 Two's Complement Adder with overflow detection



$$\begin{array}{r}
 0111 \\
 + 1 \\
 \hline
 1000
 \end{array}$$


Two's Complement Subtraction

Lazy approach


$$A - B = A + (-B) = A + (\bar{B} + 1)$$


$$B \equiv -8 = \boxed{1000}$$

$$(7) - (-8)$$

 

Q: What if $(-B)$ overflows?

 


 


if (b ~~is~~ true)
then ~


- Is this design fast enough?
- Can we generalize to 32 bits? 64? more?

delay = 8

 

 Speed of a circuit is affected by the number of gates in series (on the *critical path* or the *deepest level of logic*)



 

- First full adder, 2 gate delay
- Second full adder, 2 gate delay
- ...