

# RISC Pipeline

Kevin Walsh
CS 3410, Spring 2010
Computer Science

**Cornell University** 

See: P&H Chapter 4.6

 

 


# Five stage "RISC" load-store architecture

- 1. Instruction fetch (IF)
  - get instruction from memory, increment PC
- 2. Instruction Decode (ID)
  - translate opcode into control signals and read registers
- 3. Execute (EX)
  - perform ALU operation, compute jump/branch targets
- 4. Memory (MEM)
  - access memory if needed
- 5. Writeback (WB)
  - update register file
 
# Break instructions across multiple clock cycles (five, in this case)

Design a separate stage for the execution performed during each clock cycle

Add pipeline registers to isolate signals between different stages




## Stage 1: Instruction Fetch

## Fetch a new instruction every cycle

- Current PC is index to instruction memory
- Increment the PC at end of cycle (assume no branches for now)
 
## Write values of interest to pipeline register (IF/ID)

- Instruction bits (for later decoding)
- PC+4 (for later computing branch targets)




#### Stage 2: Instruction Decode

#### On every cycle:

- Read IF/ID pipeline register to get instruction bits
- Decode instruction, generate control signals
- Read from register file
 
# Write values of interest to pipeline register (ID/EX)

- Control information, Rd index, immediates, offsets, ...
- Contents of Ra, Rb
- PC+4 (for computing branch targets later)




#### Stage 3: Execute

#### On every cycle:

- Read ID/EX pipeline register to get values and control bits
- Perform ALU operation
- Compute targets (PC+4+offset, etc.) in case this is a branch
- Decide if jump/branch should be taken
 
## Write values of interest to pipeline register (EX/MEM)

- Control information, Rd index, ...
- Result of ALU operation
- Value in case this is a memory store instruction




#### Stage 4: Memory

#### On every cycle:

- Read EX/MEM pipeline register to get values and control bits
- Perform memory load/store if needed
  - address is ALU result
 
## Write values of interest to pipeline register (MEM/WB)


- Control information, Rd index, ...
- Result of memory operation
- Pass result of ALU operation




# Stage 5: Write-back

 
# On every cycle:


- Read MEM/WB pipeline register to get values and control bits
- Select value and write to register file



 
 
```
add r3, r1, r2;
nand r6, r4, r5;
lw r4, 20(r2);
add r5, r2, r5;
sw r7, 12(r3);
```



 

# Powerful technique for masking latencies

- Logically, instructions execute one at a time
- Physically, instructions execute in parallel
  - Instruction level parallelism

# Abstraction promotes decoupling

Interface (ISA) vs. implementation (Pipeline)