

Gates and Logic

Hakim Weatherspoon


CS 3410, Spring 2011

Computer Science

Cornell University

See: P&H Appendix C.0, C.1, C.2

Gates and Logic

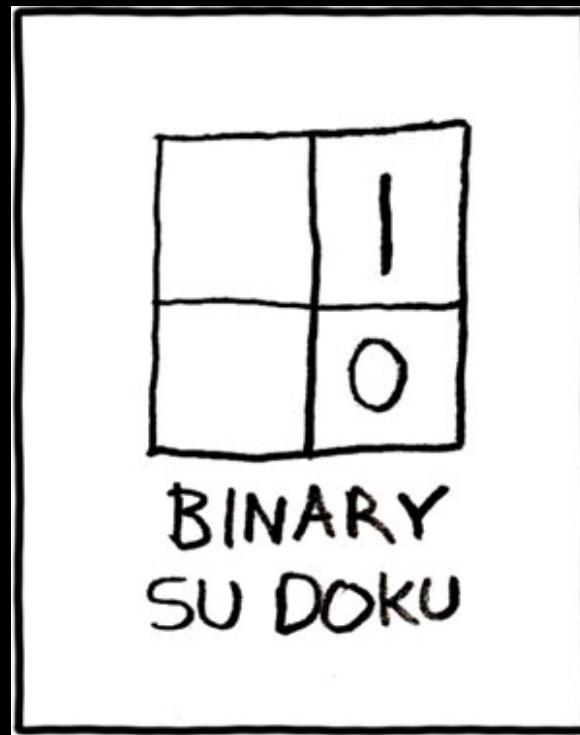

See: P&H Appendix C.0, C.1, C.2

<http://www.xkcd.com/74/>

Announcements

Class newsgroup created

- Posted on web-page
- Use it for partner finding

First assignment is to find partners


Sections start next week

- Use this weeks section to find a partner


Note about class

- No Verilog or VHDL
- Clickers not required, but will use them from time-to-time


A switch

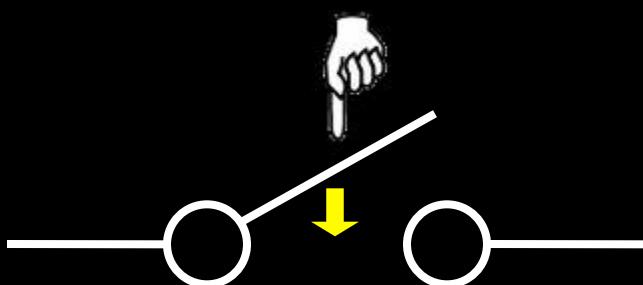

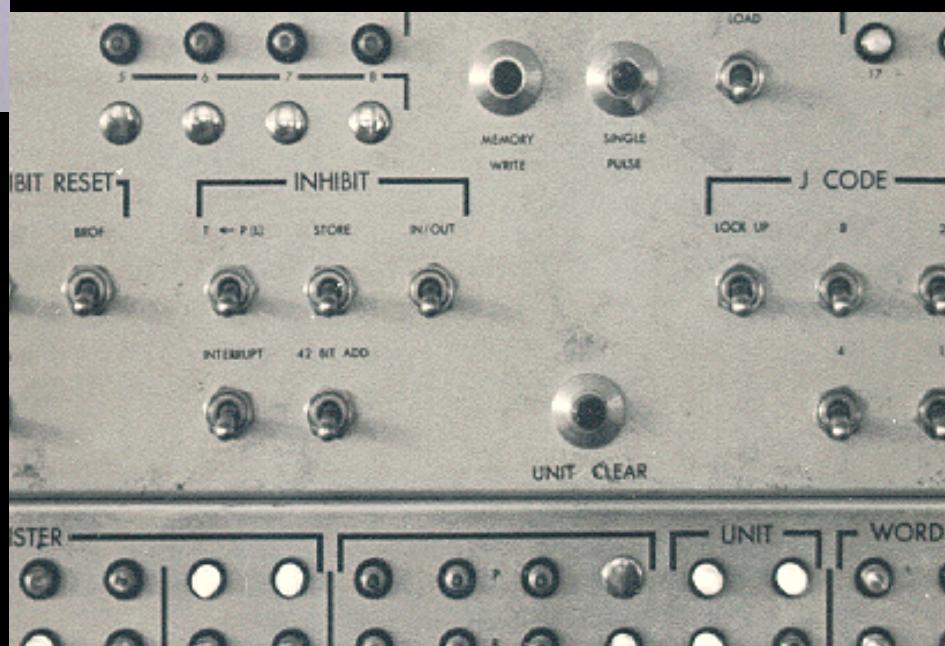- Acts as a *insulator*
- or
- Can be used to build amazing things...




Better Switch

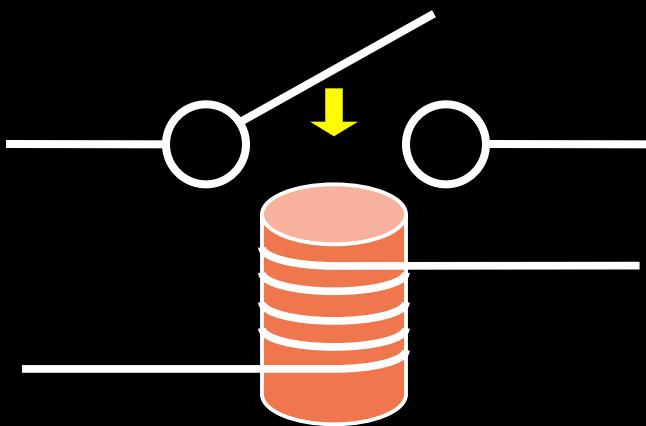


- One current controls another (larger) current
- Static Power:
 - Keeps consuming power when in the *ON* state
- Dynamic Power:
 - Jump in power consumption when switching

Atoms

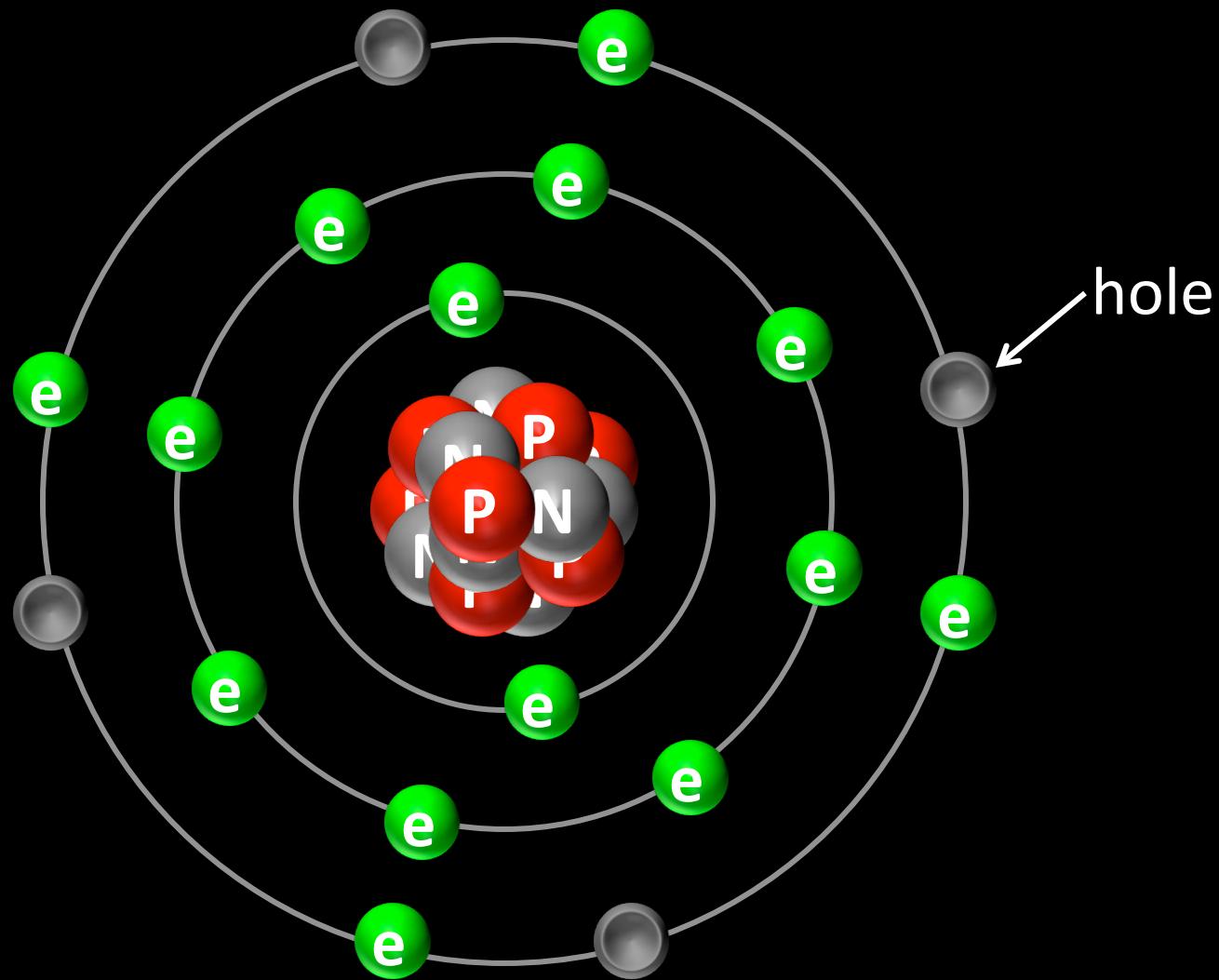


Elements

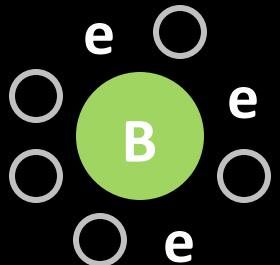

Boron




Silicon

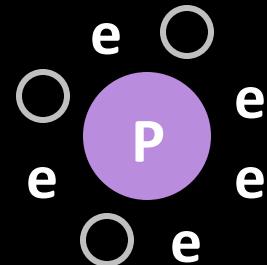

Phosphorus


Silicon Crystal

Silicon

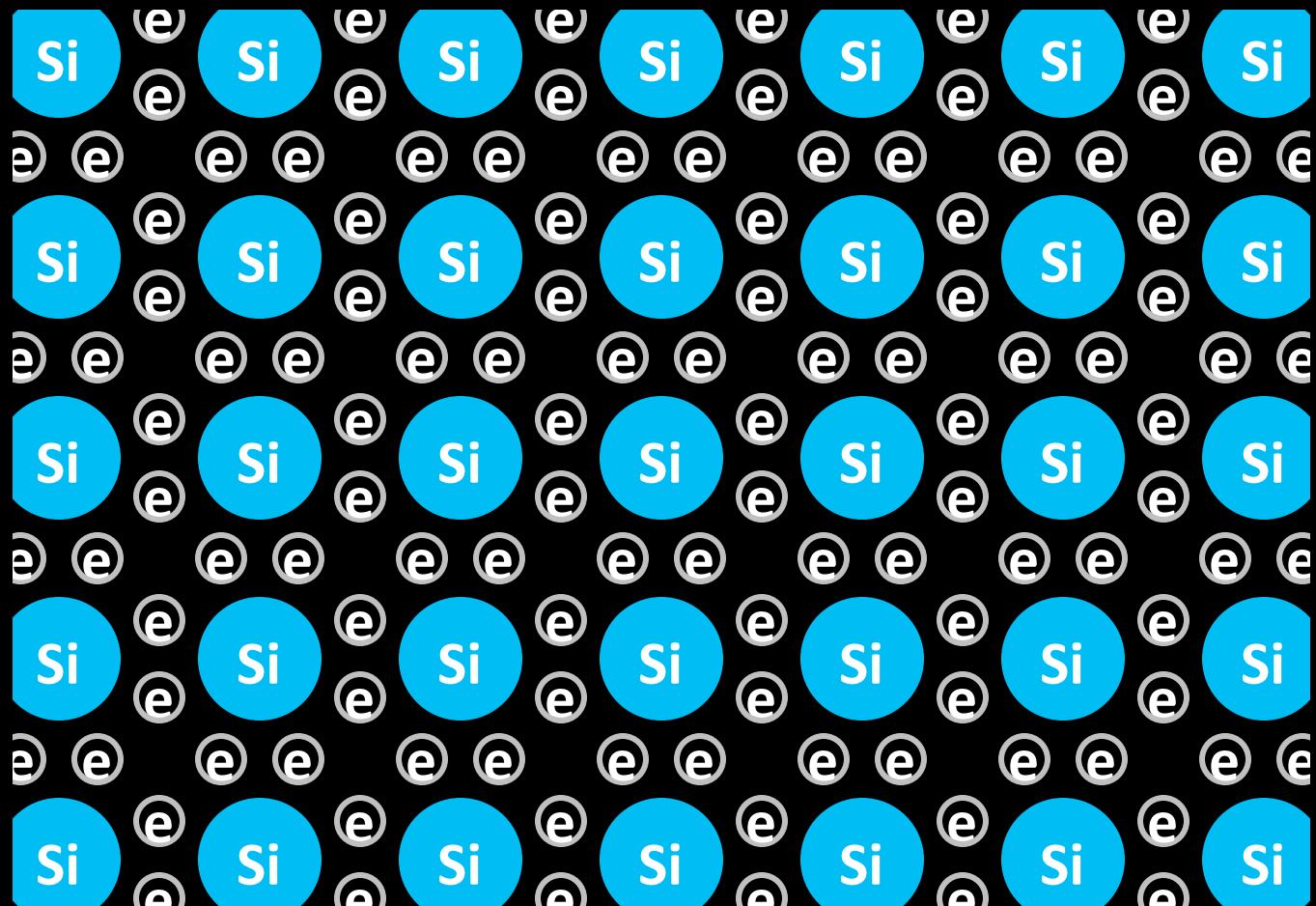


Phosphorus Doping

N-Type: Silicon + Phosphorus

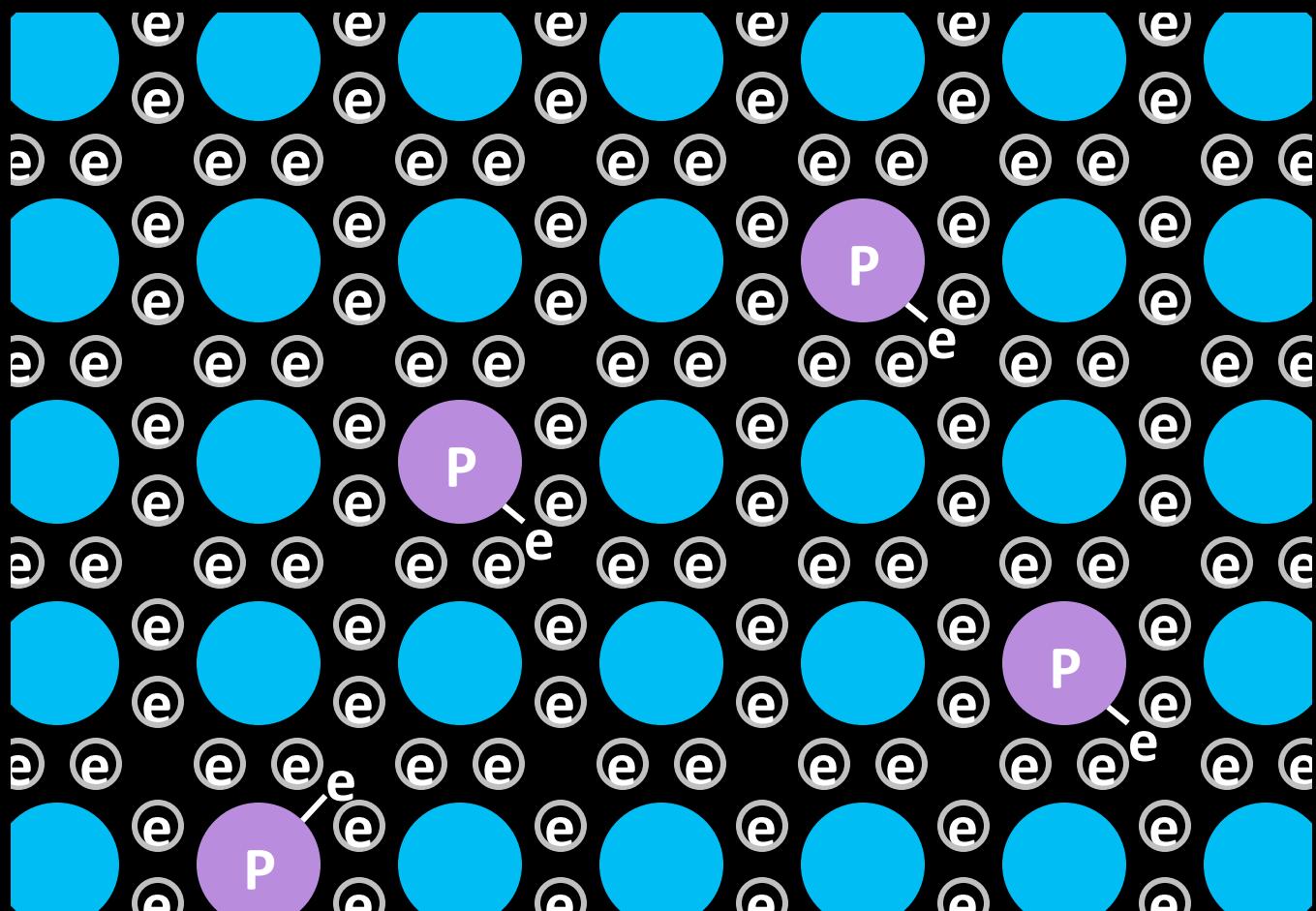


Boron Doping

P-Type: Silicon + Boron

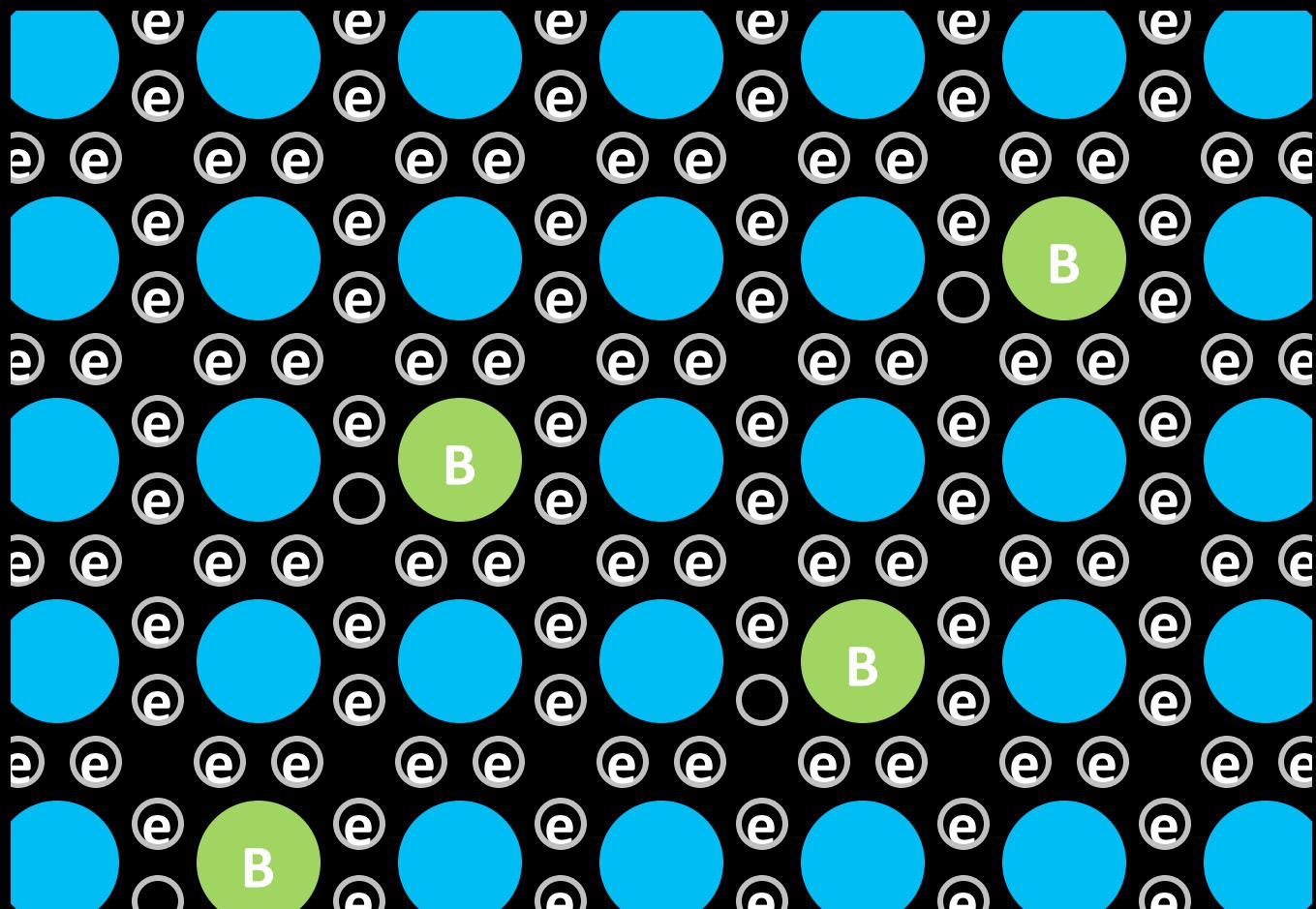

Semiconductors

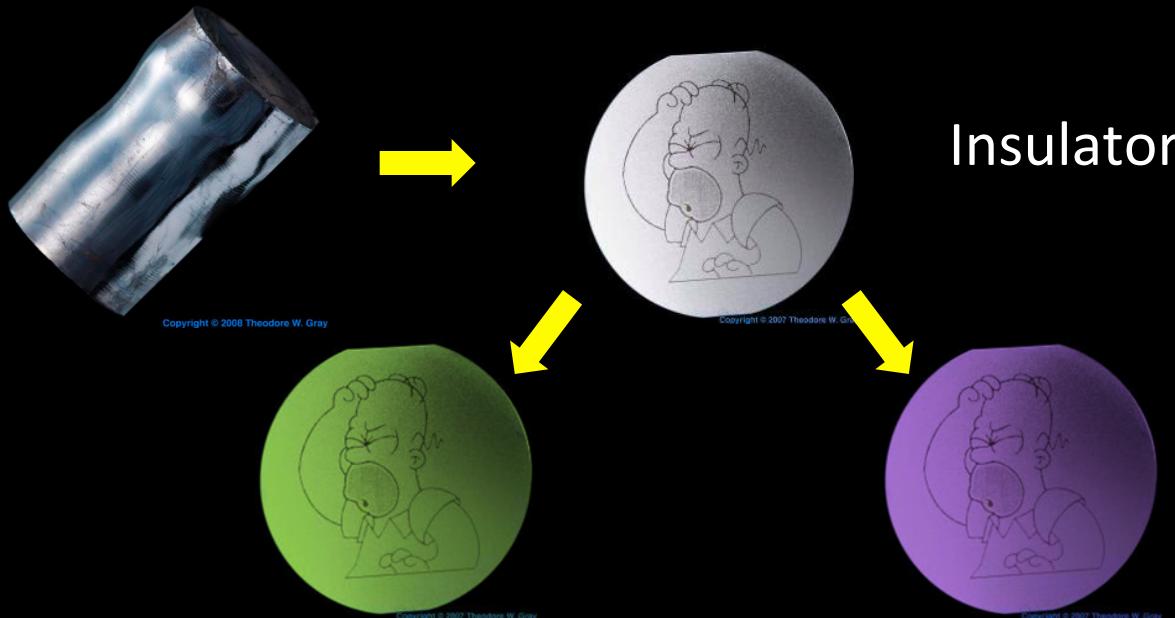

p-type (Si+Boron)
has mobile holes:

low voltage (depleted)
→ insulator


high voltage (mobile holes)
→ conductor

n-type (Si+Phosphorus)
has mobile electrons:

low voltage (mobile electrons)
→ conductor

high voltage (depleted)
→ insulator


Bipolar Junction

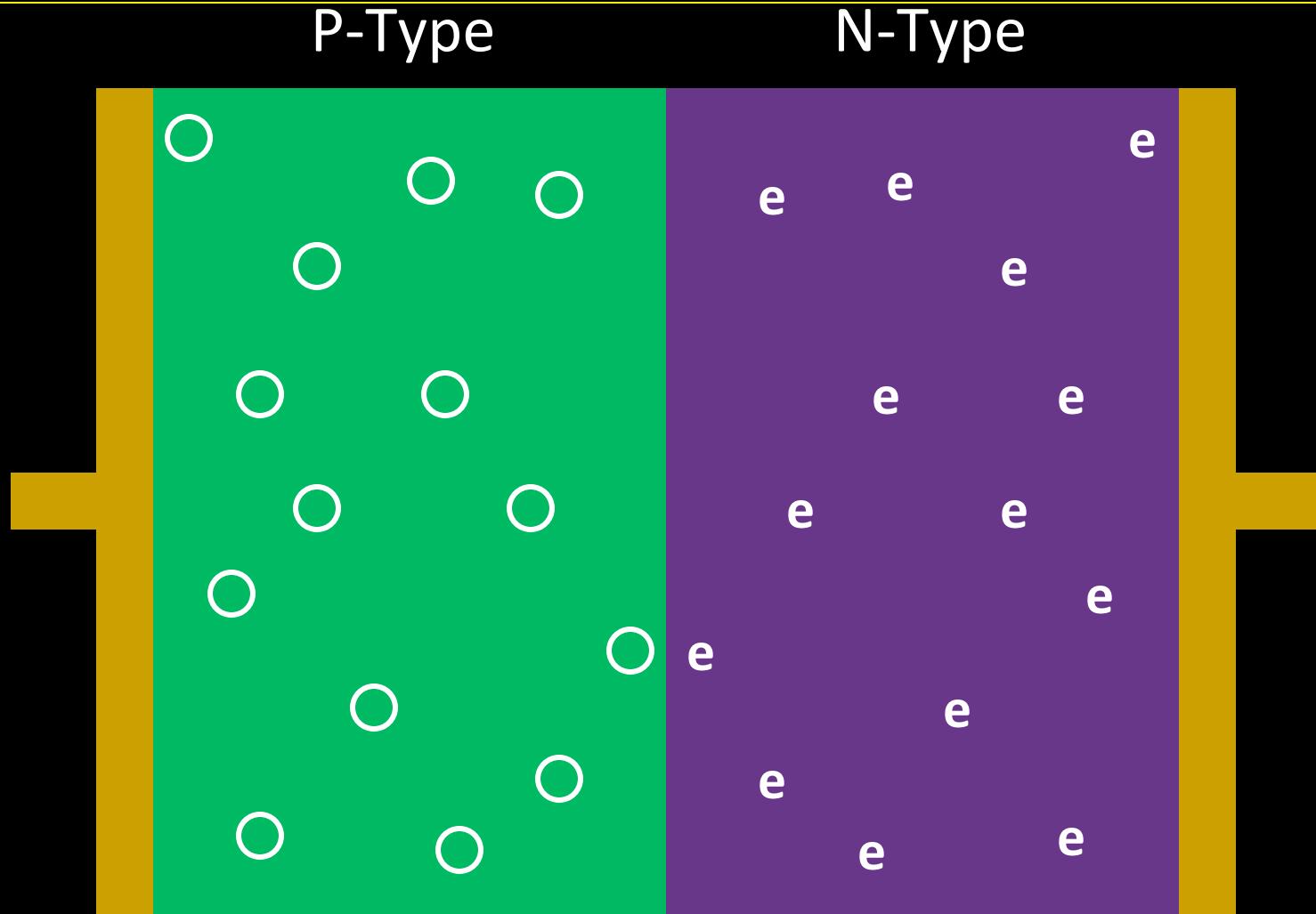


low $v \rightarrow$ insulator
high $v \rightarrow$ conductor

low $v \rightarrow$ conductor
high $v \rightarrow$ insulator

Reverse Bias


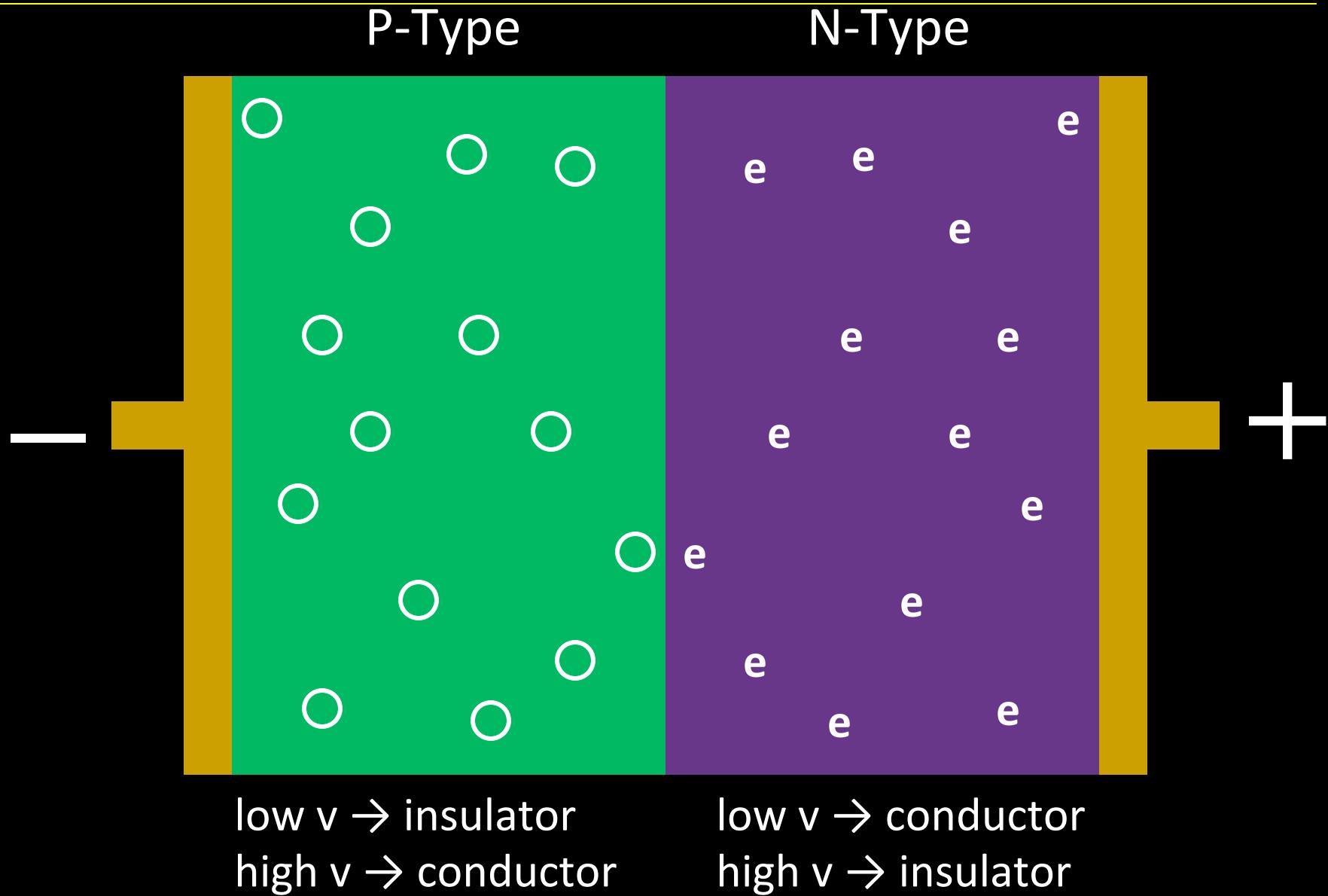


Forward Bias

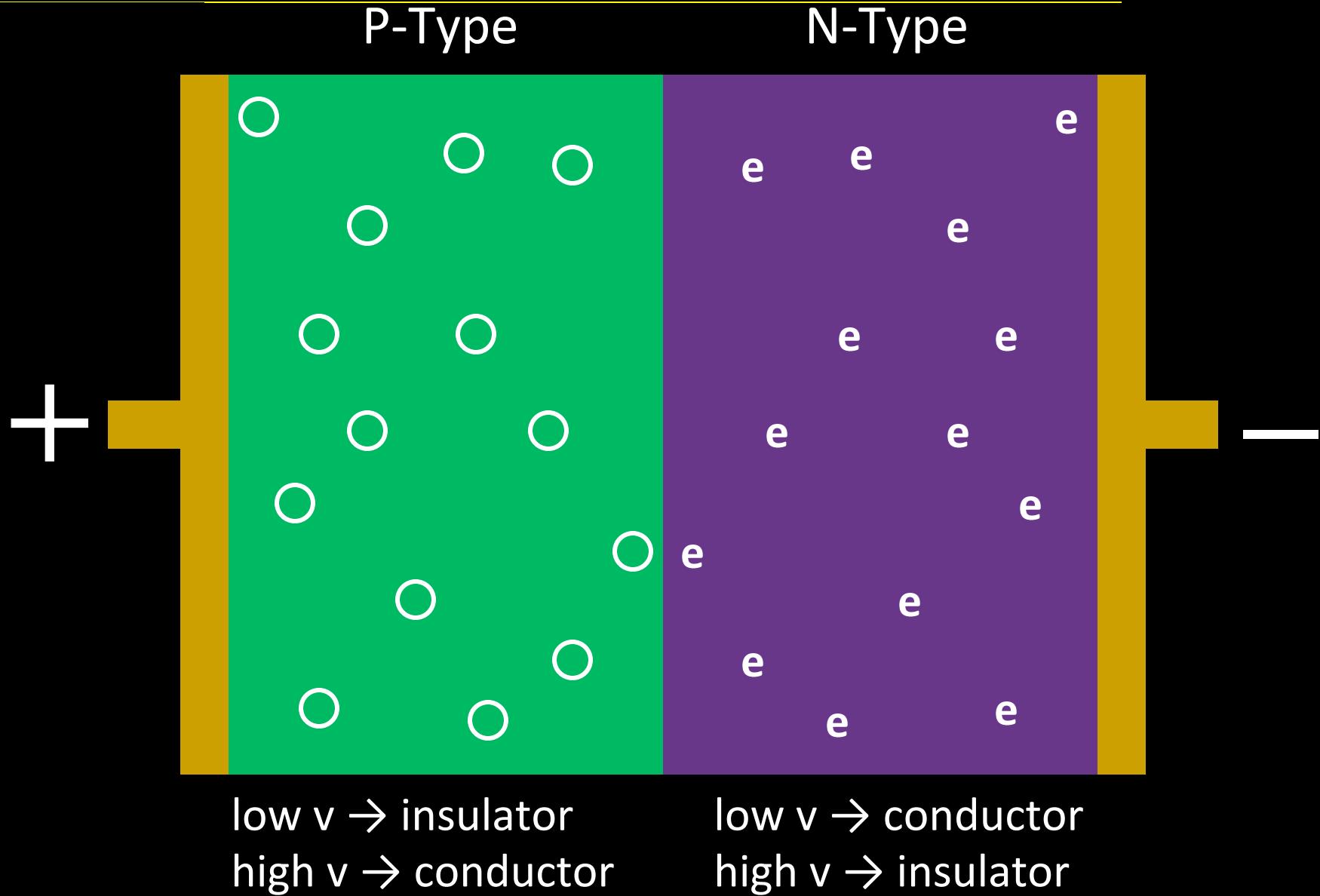

Diodes

PN Junction “Diode”

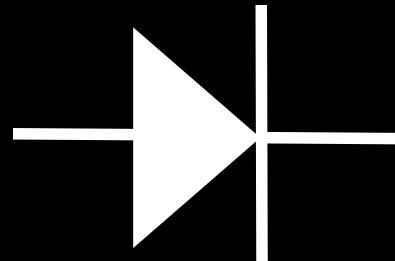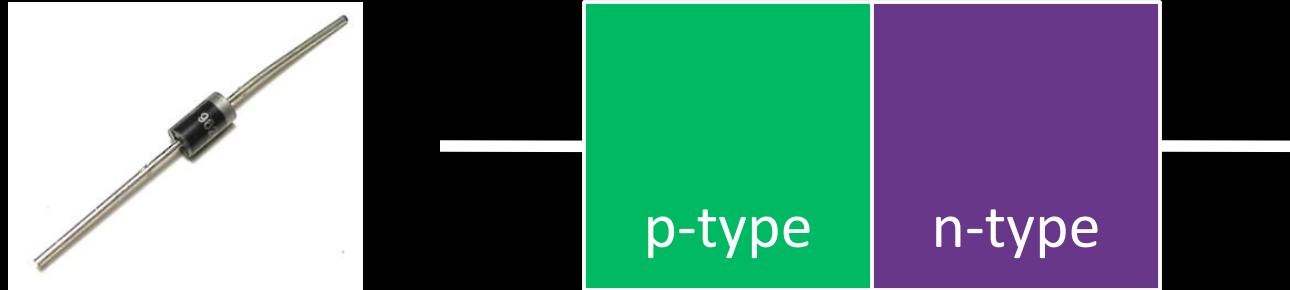


Conventions:


$v_{dd} = v_{cc} = +1.2v = +5v = hi$

$v_{ss} = v_{ee} = 0v = gnd$

PNP Junction

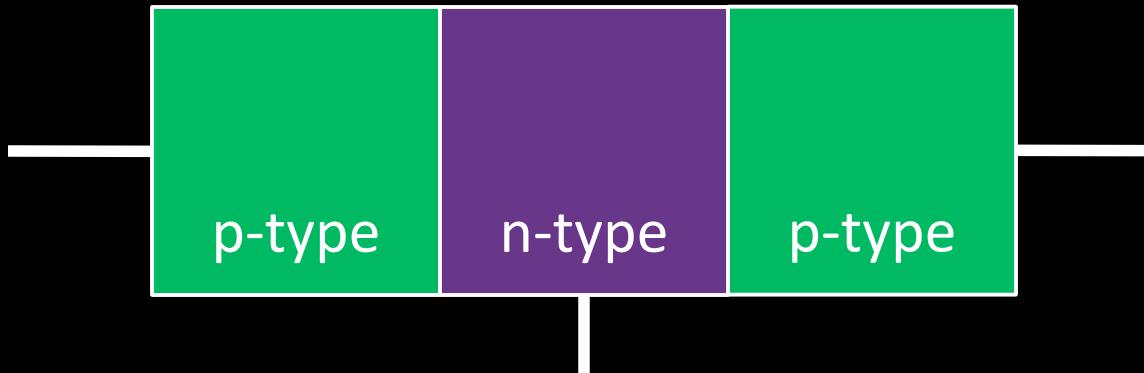


Bipolar Junction Transistors



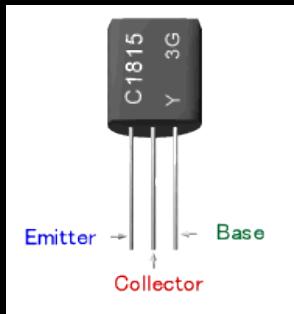


- Solid-state switch: The most amazing invention of the 1900s
Emitter = “input”, Base = “switch”, Collector = “output”

PNP Transistor

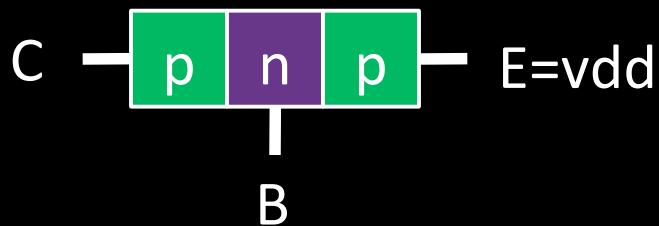


NPN Transistor

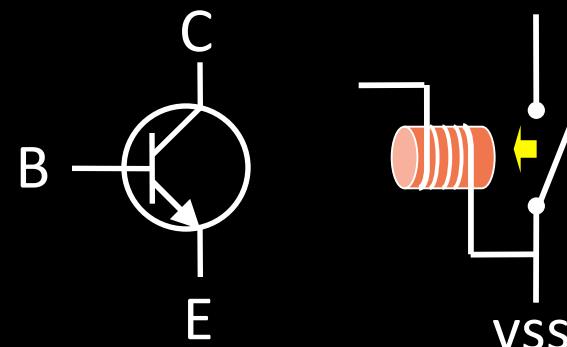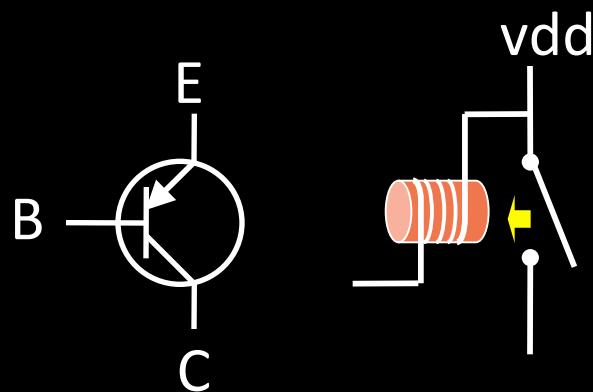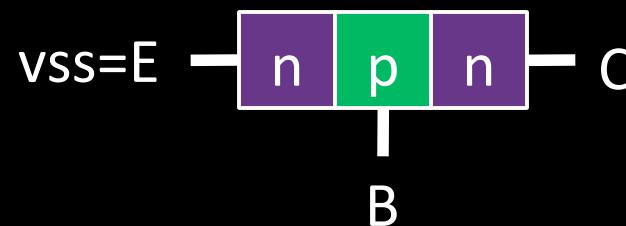


Field Effect Transistors

P-type FET

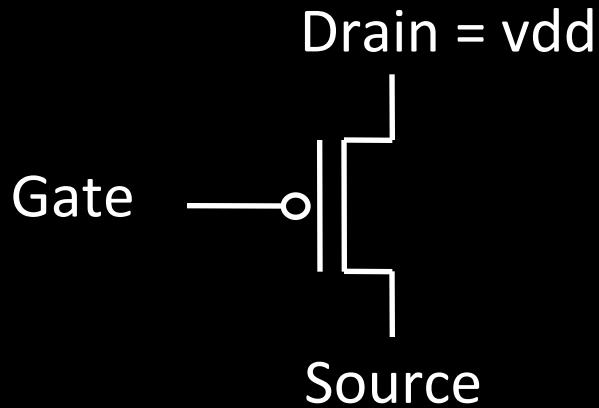



N-type FET

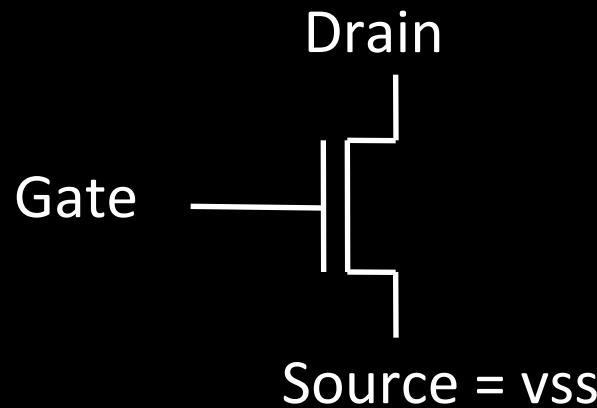

- Connect Source to Drain when Gate = lo
- Drain must be vdd, or connected to source of another P-type transistor

- Connect Source to Drain when Gate = hi
- Source must be vss, or connected to drain of another N-type transistor

Multiple Transistors

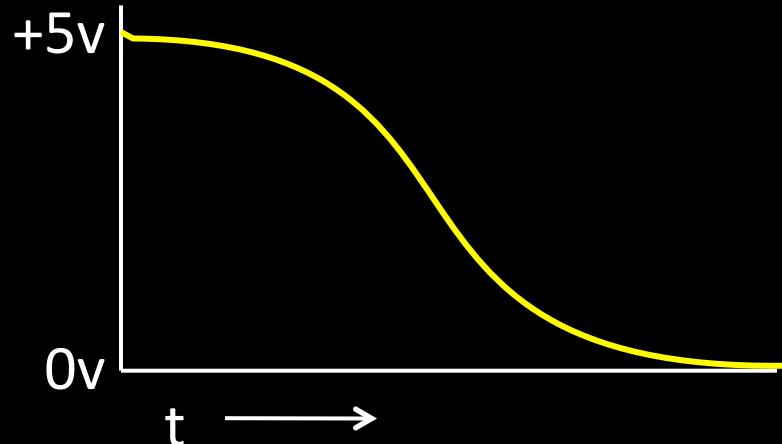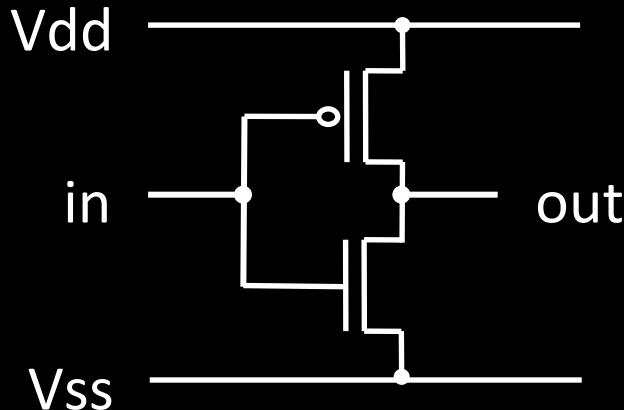

In	Out

voltage

Gate delay



- transistor switching time
- voltage, propagation, fanout, temperature, ...

CMOS design

(complementary-symmetry metal–oxide semiconductor)

- Power consumption = dynamic + leakage

Digital Logic

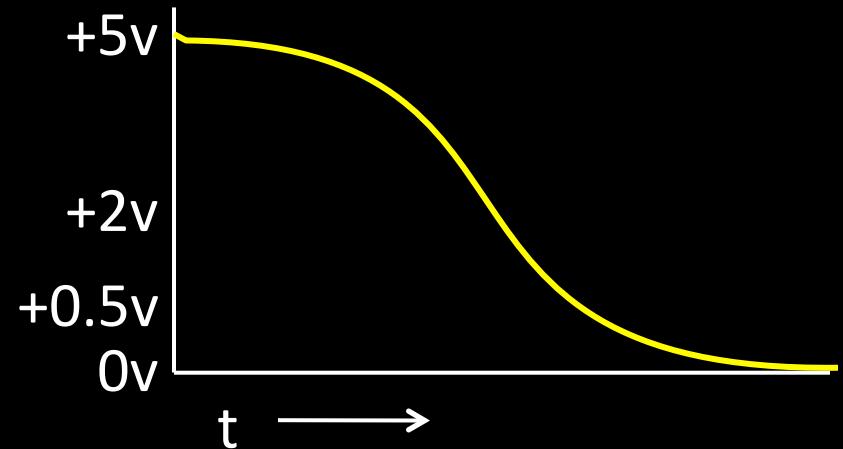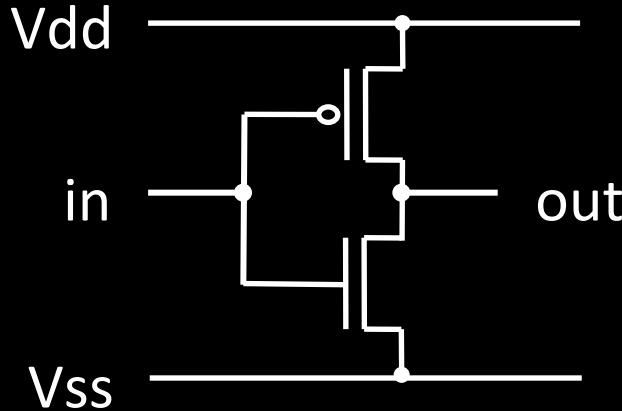

In	Out
+5v	0v
0v	+5v

voltage

In	Out


truth table

Conventions:

vdd = **vcc** = **+1.2v** = **+5v** = **hi** = **true** = **1**


vss = **vee** = **0v** = **gnd** = **false** = **0**

NOT Gate (Inverter)

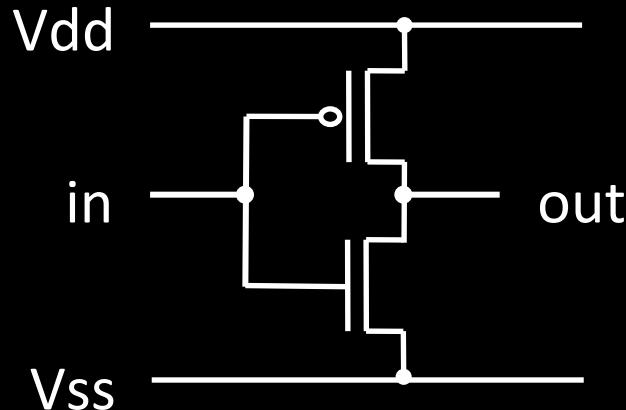

Function: NOT


- Symbol:

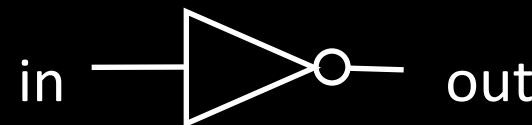

In	Out
0	1
1	0


Truth table

NAND Gate

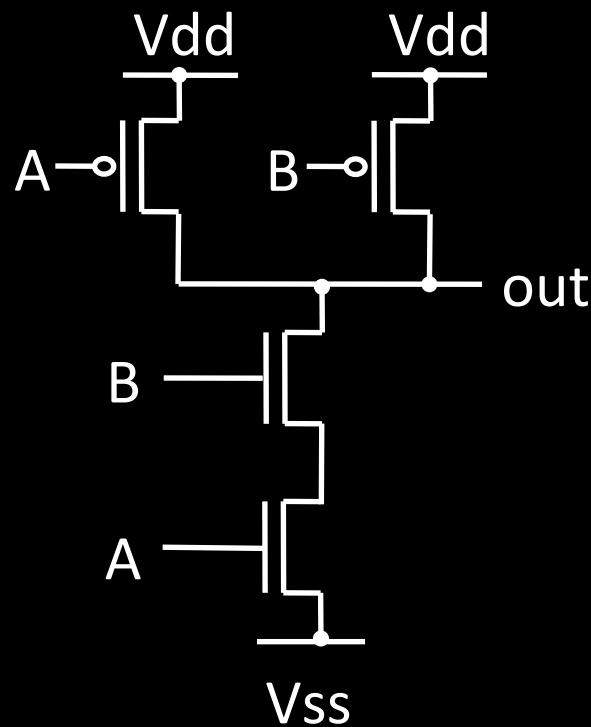


Function: NAND

- Symbol:

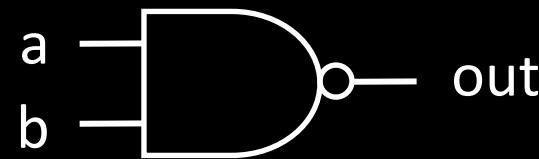


A	B	out
0	0	1
0	1	1
1	0	1
1	1	0

NOR Gate

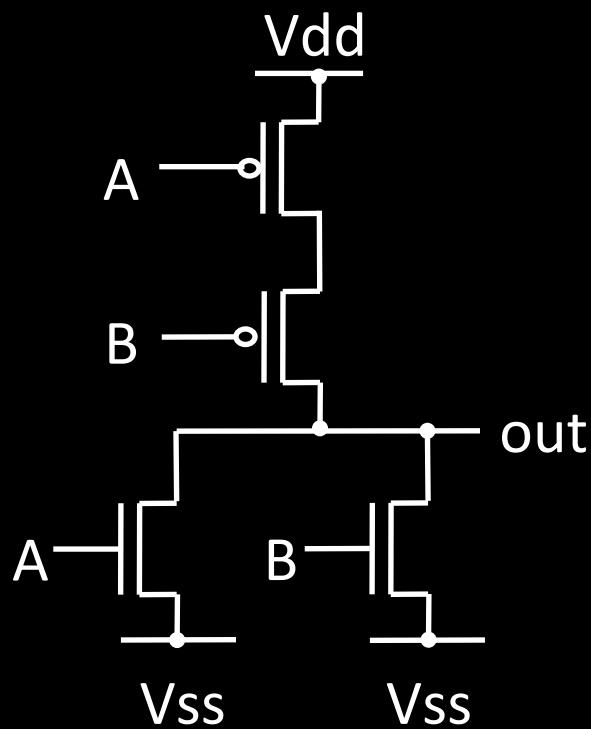

Function: NOR


- Symbol:

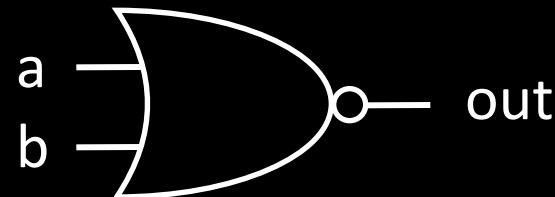


A	B	out
0	0	1
0	1	0
1	0	0
1	1	0

Building Functions


- AND:

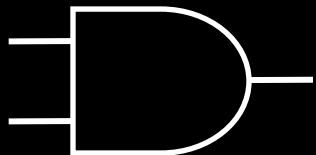

- OR:

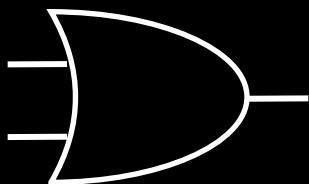

- NOT:

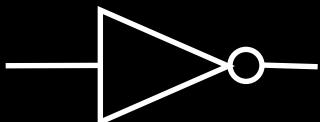


Universal Gates

NAND is universal (so is NOR)

- Can implement any function with just NAND gates
 - De Morgan's laws are helpful (pushing bubbles)
- useful for manufacturing

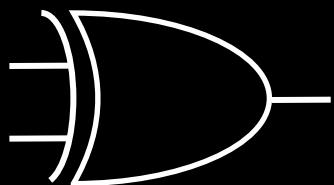E.g.: XOR (A, B) = A or B but not both ("exclusive or")



Proof: ?

Logic Equations

Some notation:

- constants: true = 1, false = 0
- variables: a, b, out, ...
- operators:
 - $\text{AND}(a, b) = a \cdot b = a \& b = a \wedge b$
 - $\text{OR}(a, b) = a + b = a | b = a \vee b$
 - $\text{NOT}(a) = \bar{a} = !a = \neg a$

Identities

Identities useful for manipulating logic equations

- For optimization & ease of implementation

$$a + 0 = a$$

$$a + 1 = 1$$

$$a + \bar{a} = 1$$

$$a \cdot 0 = 0$$

$$a \cdot 1 = a$$

$$a \cdot \bar{a} = 0$$

$$\overline{(a + b)} = \bar{a} \bar{b}$$

$$\overline{(a \cdot b)} = \bar{a} + \bar{b}$$

$$a + a \cdot b = a$$

$$a(b+c) = ab + ac$$

$$\overline{a(b+c)} = \bar{a} + \bar{b}\bar{c}$$

Logic Manipulation

- functions: gates \leftrightarrow truth tables \leftrightarrow equations
- Example: $(a+b)(a+c) = a + bc$

a	b	c					
0	0	0					
0	0	1					
0	1	0					
0	1	1					
1	0	0					
1	0	1					
1	1	0					
1	1	1					

Logic Manipulation

- functions: gates \leftrightarrow truth tables \leftrightarrow equations
- Example: $(a+b)(a+c) = a + bc$

a	b	c	a+b	a+c	LHS	bc	RHS
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

Logic Minimization


- A common problem is how to implement a desired function most efficiently
- One can derive the equation from the truth table

a	b	c	minterm
0	0	0	\overline{abc}
0	0	1	\overline{abc}
0	1	0	$\overline{ab}\bar{c}$
0	1	1	$\overline{a}\overline{bc}$
1	0	0	$\overline{a}\overline{b}\overline{c}$
1	0	1	$\overline{a}\overline{b}c$
1	1	0	$\overline{a}bc$
1	1	1	abc

for all outputs
that are 1,
take the corresponding
minterm
Obtain the result in
“sum of products” form


- How does one find the most efficient equation?
 - Manipulate algebraically until satisfied
 - Use Karnaugh maps (or K maps)

Multiplexer

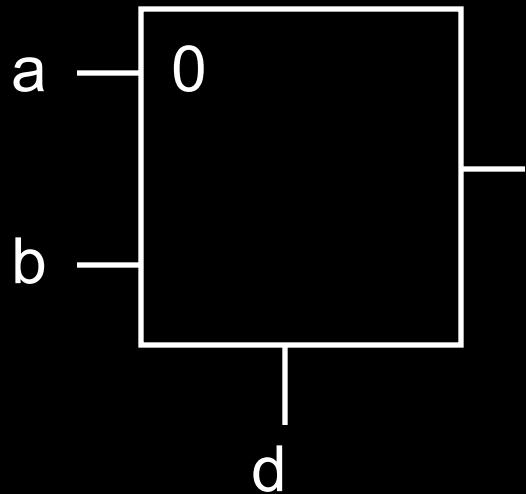

- A multiplexer selects between multiple inputs
 - $\text{out} = a$, if $d = 0$
 - $\text{out} = b$, if $d = 1$
- Build truth table
- Minimize diagram
- Derive logic diagram


Multiplexer Implementation

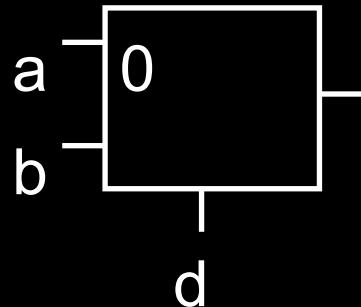

a	b	d	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

- Build a truth table
 $= abd + ab\bar{d} + \bar{a} b d + a \bar{b} \bar{d}$
 $= a\bar{d} + bd$


Multiplexer Implementation

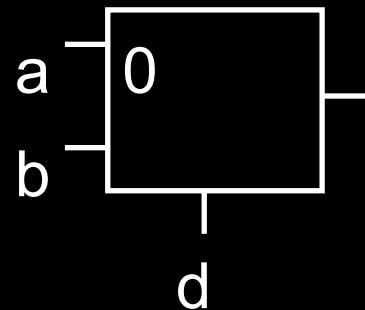


- Draw the circuit

a	b	d	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

– $\text{out} = ad\bar{b} + bd$

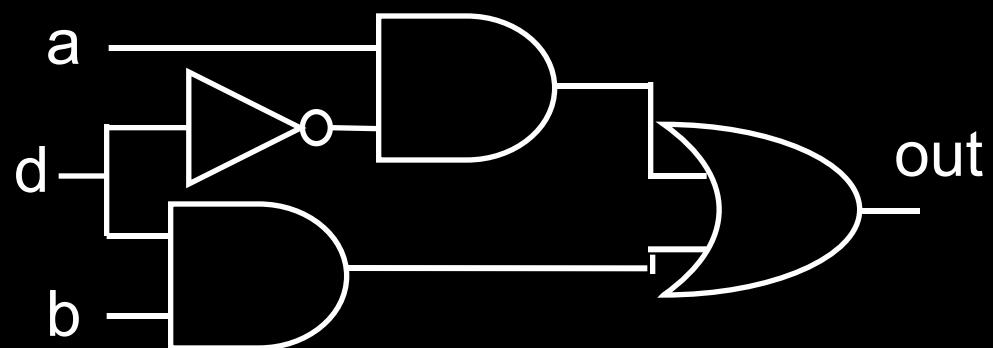


Logic Gates

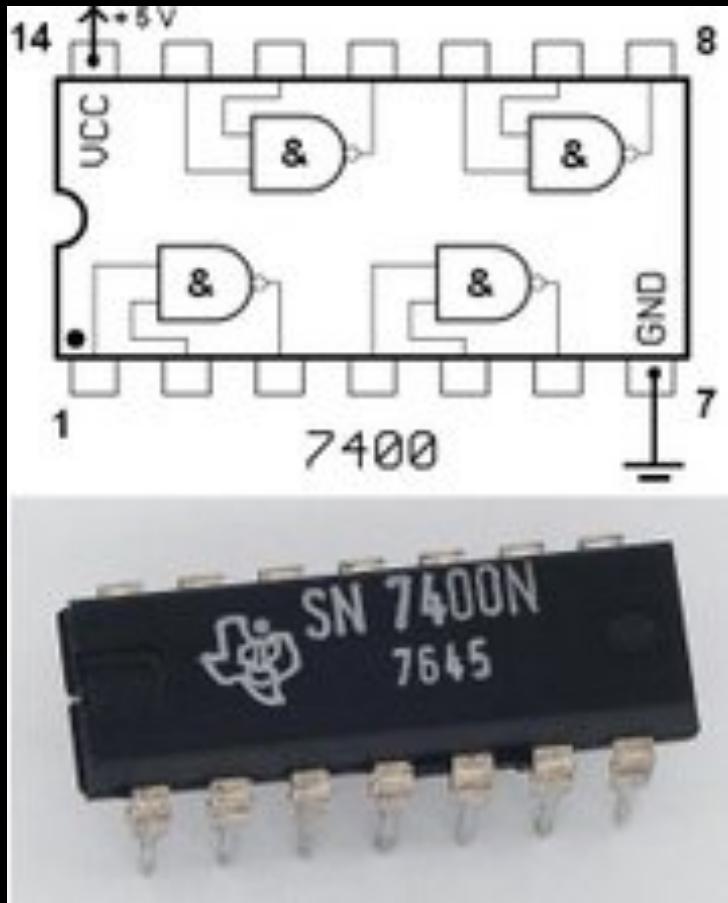

- One can buy gates separately
 - ex. 74xxx series of integrated circuits
 - cost ~\$1 per chip, mostly for packaging and testing
- Cumbersome, but possible to build devices using gates put together manually

Integrated Circuits

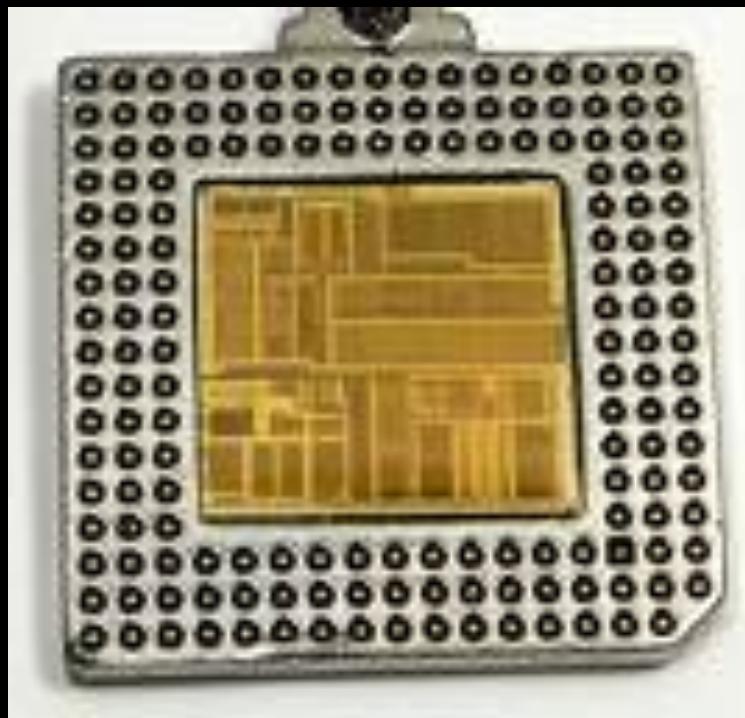

- Or one can manufacture a complete design using a custom mask
- Intel Nehalem has approximately 731 million transistors

Voting machine

- Build something interesting
- A voting machine
- Assume:
 - A vote is recorded on a piece of paper,
 - by punching out a hole,
 - there are at most 7 choices
 - we will not worry about hanging chads or “invalids”


Voting machine

- For now, let's just display the numerical identifier to the ballot supervisor
 - we won't do counting yet, just decoding
 - we can use four photo-sensitive transistors to find out which hole is punched out



- A photo-sensitive transistor detects the presence of light
- Photo-sensitive material triggers the gate

Ballot Reading

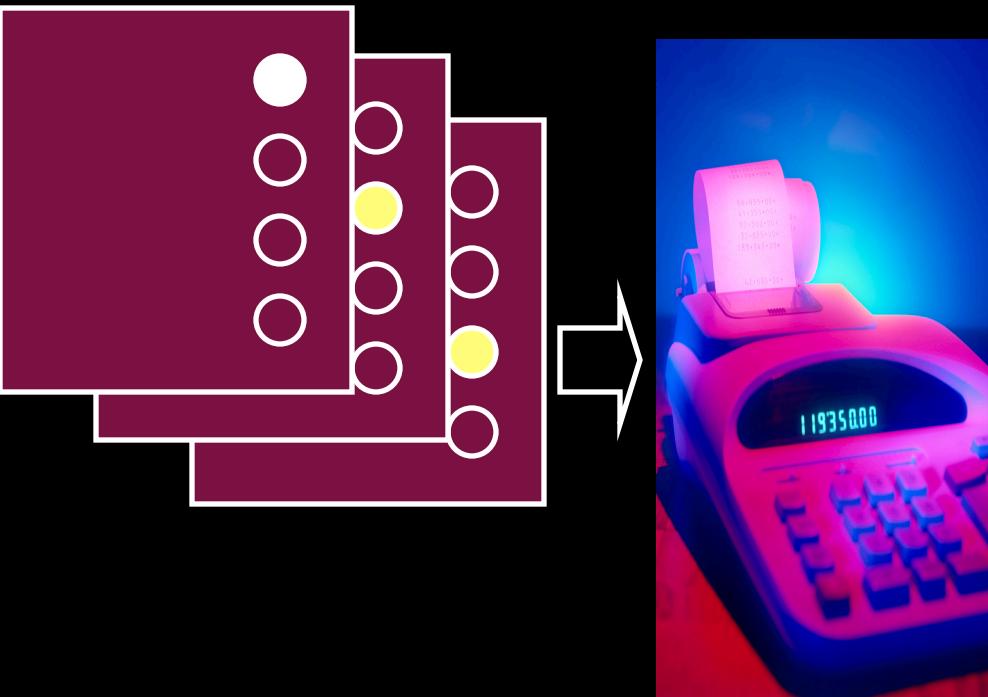


Ballots

The 3410 vote recording
machine

- Input: paper with a hole in it
- Out: number the ballot supervisor can record

Encoders

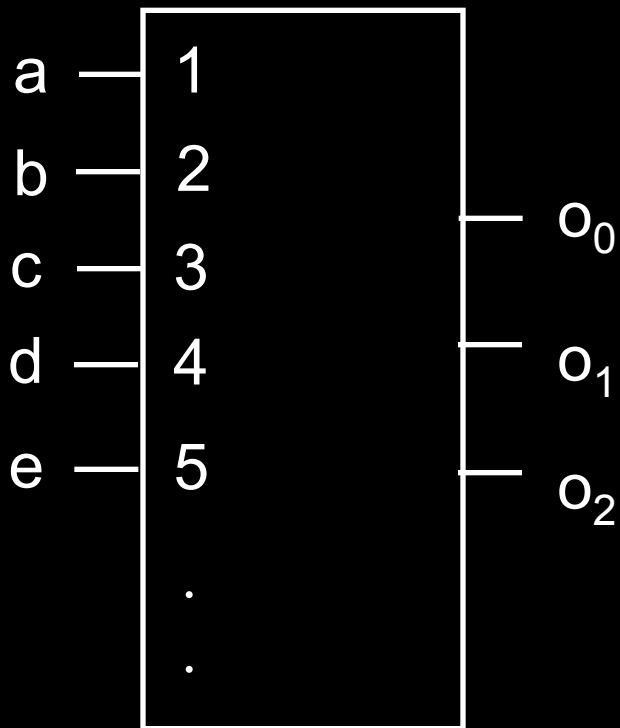

A 3-bit encoder
(7-to-3)
(5 inputs shown)

- N sensors in a row
- Want to distinguish which of the N sensors has fired
- Want to represent the firing sensor number in compact form
 - N might be large
 - Only one wire is on at any time
 - Silly to route N wires everywhere, better to encode in $\log N$ wires

Number Representations

37
10¹ 10⁰

- Decimal numbers are written in base 10
 - $3 \times 10^1 + 7 \times 10^0 = 37$
- Just as easily use other bases
 - Base 2 - “Binary”
 - Base 8 - “Octal”
 - Base 16 – “Hexadecimal”

Number Representations

$$\begin{array}{r} 3 \quad 7 \\ \hline 10^1 \quad 10^0 \end{array}$$

- Base conversion via repetitive division
 - Divide by base, write remainder, move left with quotient
 - Sanity check with 37 and base 10

Binary Representation

- Check 37 and base 2
- $37 = 32 + 4 + 1$


0	1	0	0	1	0	1
—	—	—	—	—	—	—
2^6	2^5	2^4	2^3	2^2	2^1	2^0
64	32	16	8	4	2	1

Hexadecimal Representation

$$\begin{array}{r} 25 \\ \hline 16^1 \ 16^0 \end{array}$$

- 37 decimal = $(25)_{16}$
- Convention
 - Base 16 is written with a leading 0x
 - 37 = 0x25
- Need extra digits!
 - 0, 1, 2, 3, 4, 5, 6, 7,
8, 9, A, B, C, D, E, F
- Binary to hexadecimal is easy
 - Divide into groups of 4, translate groupwise into hex digits

Encoder Truth Table

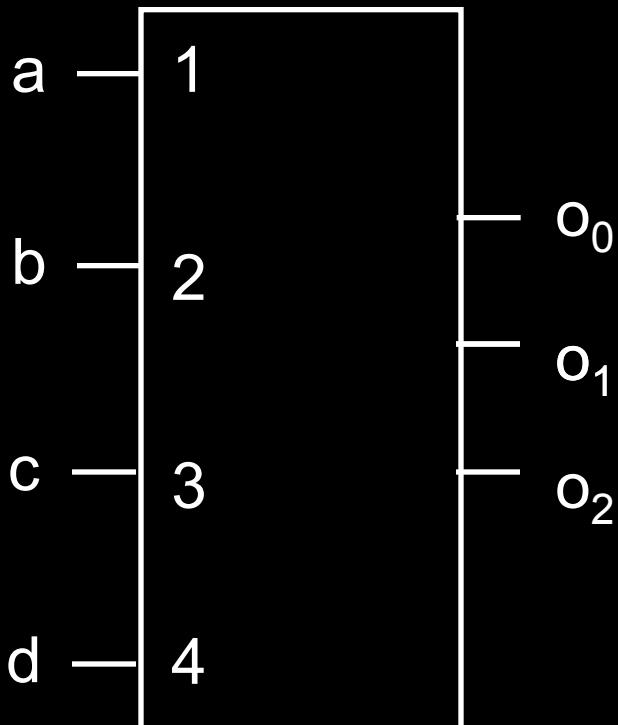


A 3-bit
encoder
with 4 inputs
for simplicity

a	b	c	d			o ₂	o ₁	o ₀
0	0	0	0			0	0	0
1	0	0	0			0	0	1
0	1	0	0			0	1	0
0	0	1	0			0	1	1
0	0	0	1			1	0	0

- o₂ = \overline{abcd}
- o₁ = $\overline{\underline{a}}\overline{\underline{b}}\overline{\underline{c}}\overline{\underline{d}}$ + $\overline{\underline{a}}\overline{\underline{b}}\overline{\underline{c}}\underline{d}$
- o₀ = $a\overline{bcd}$ + $\overline{a}\overline{bcd}$

Ballot Reading

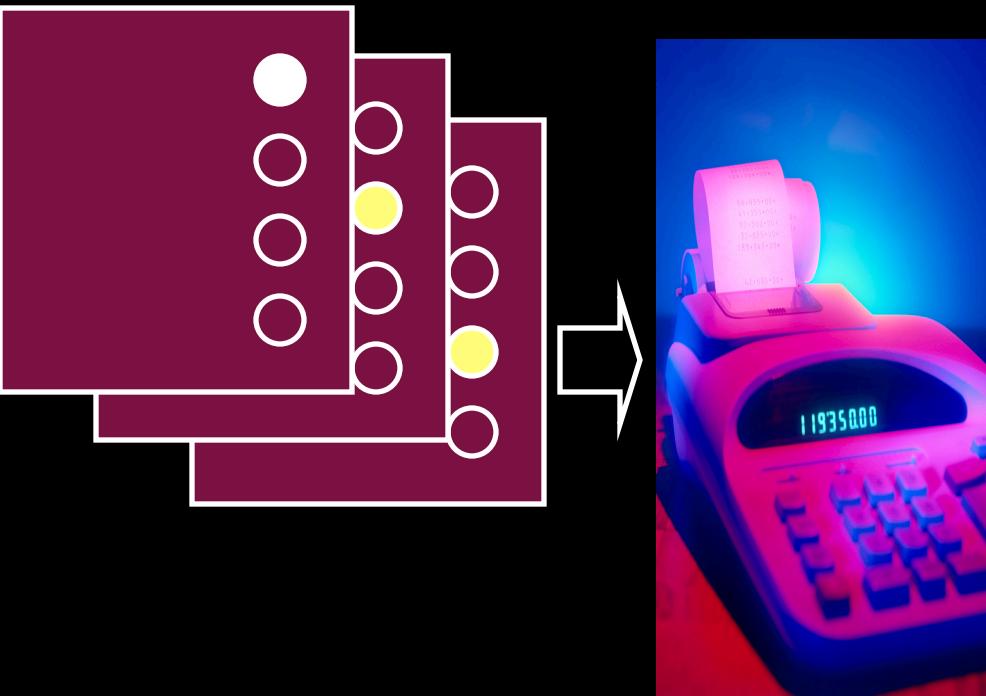


Ballots

The 3410 voting
machine


- Ok, we built first half of the machine
- Need to display the result

7-Segment LED Decoder

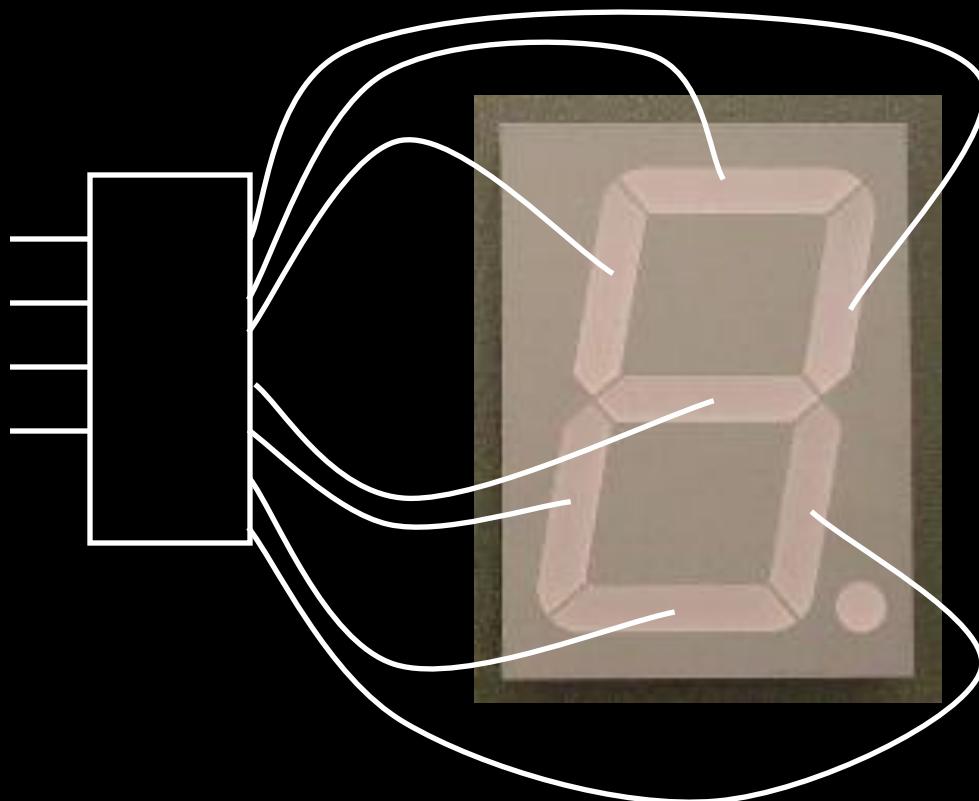


- Just a simple logic circuit
- Write the truth table
- 4 inputs encoded in binary
- 8 outputs, each driving an independent, rectangular LED
- Can display numbers

7-Segment LED Decoder

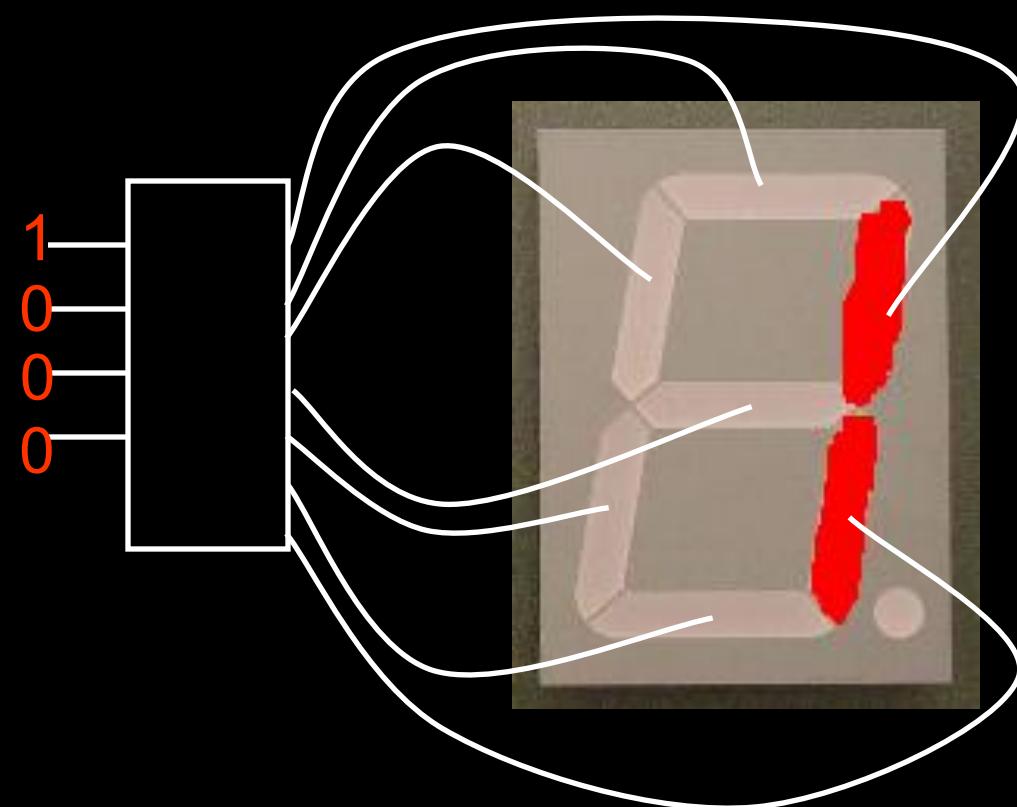

- 4 inputs encoded in binary
- 8 outputs, each driving an independent, rectangular LED
- Can display numbers


7-Segment LED Decoder

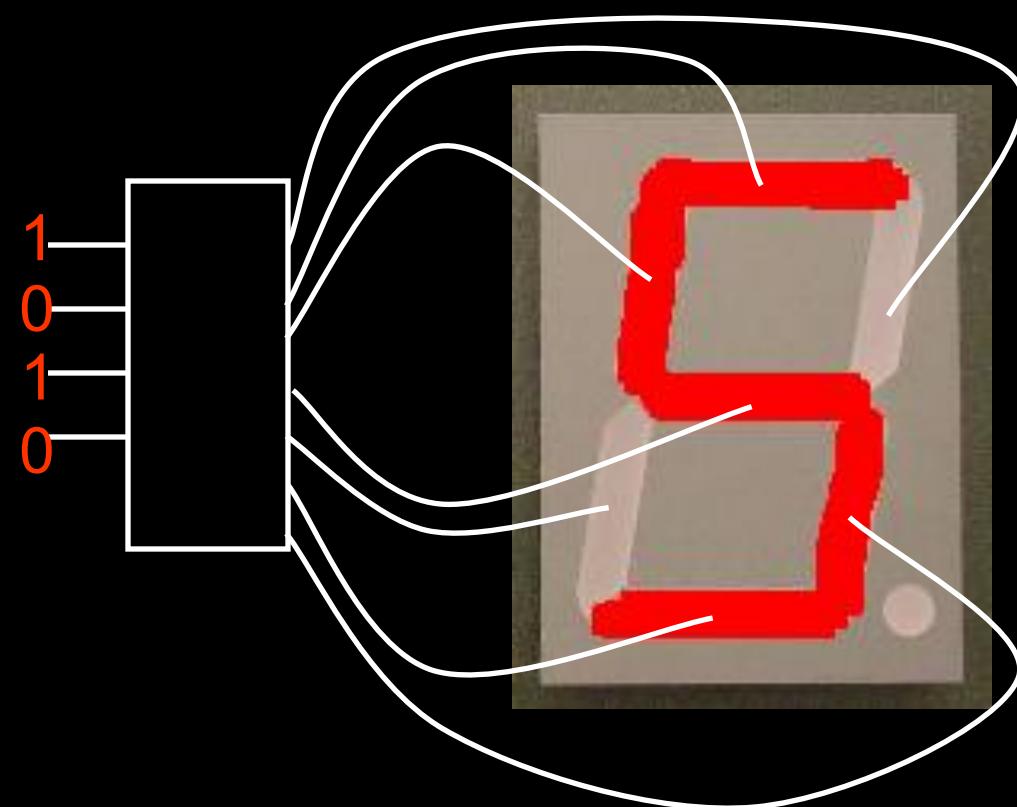

- 4 inputs encoded in binary
- 8 outputs, each driving an independent, rectangular LED
- Can display numbers

7-Segment Decoder Truth Table


i_3	i_2	i_1	i_0		o_0	o_1	o_2	o_3	o_4	o_5	o_6
0	0	0	0		1	1	1	0	1	1	1
0	0	0	1		1	0	0	0	0	0	1
0	0	1	0		1	1	0	1	1	1	0
0	0	1	1		1	1	0	1	0	1	1
0	1	0	0		1	0	1	1	0	0	1
0	1	0	1		0	1	1	1	0	1	1
0	1	1	0		0	0	1	1	1	1	1
0	1	1	1		1	1	0	0	0	0	0
1	0	0	0		1	1	1	1	1	1	1
1	0	0	1		1	1	1	1	0	1	1

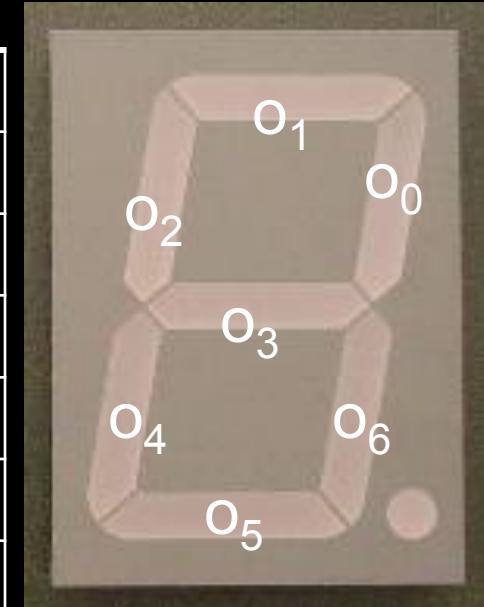

Exercise: find the error(s) in this truth table

7-Segment Decoder Truth Table


i_3	i_2	i_1	i_0		o_0	o_1	o_2	o_3	o_4	o_5	o_6
0	0	0	0		1	1	1	0	1	1	1
0	0	0	1		1	0	0	0	0	0	1
0	0	1	0		1	1	0	1	1	1	0
0	0	1	1		1	1	0	1	0	1	1
0	1	0	0		1	0	1	1	0	0	1
0	1	0	1		0	1	1	1	0	1	1
0	1	1	0		0	0	1	1	1	1	1
0	1	1	1		1	1	0	0	0	0	0
1	0	0	0		1	1	1	1	1	1	1
1	0	0	1		1	1	1	1	0	1	1

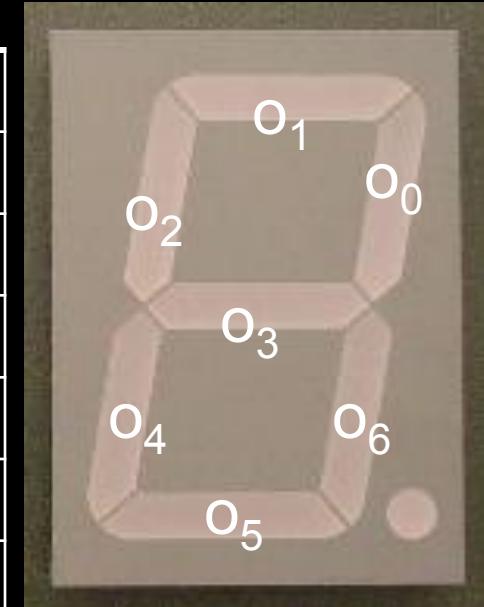

Exercise: find the error(s) in this truth table

Ballot Reading

- Done!

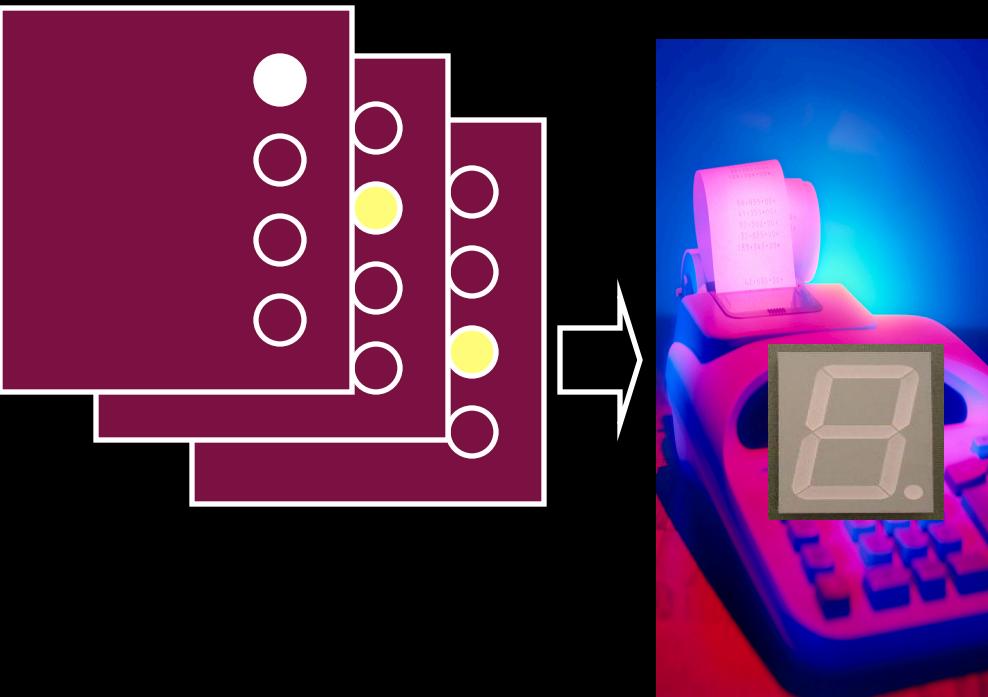

Ballots

The 3410 voting
machine

Summary

- We can now implement any logic circuit
 - Can do it efficiently, using Karnaugh maps to find the minimal terms required
 - Can use either NAND or NOR gates to implement the logic circuit
 - Can use P- and N-transistors to implement NAND or NOR gates