

Numbers & Arithmetic

Hakim Weatherspoon
CS 3410, Spring 2011
Computer Science
Cornell University

See: P&H Chapter 2.4 - 2.6, 3.2, C.5 – C.6

Announcements

Make sure you are

- Registered for class
- Can access CMS
- Have a Section you can go to
- Have a project partner

Sections are on this week

HW 1 out later today

- Due in one week, start early
- Work **alone**
- Use your resources
 - Class notes, book, Sections, office hours, newsgroup, CSUGLab₂

Announcements

Check online syllabus/schedule

- Slides and Reading for lectures
- Office Hours
- Homework and Programming Assignments
- Prelims: Thursday, March 11 and April 28th
- Schedule is subject to change

Goals for today

Review

- Circuit design (e.g. voting machine)
- Number representations
- Building blocks (encoders, decoders, multiplexors)

Binary Operations

- One-bit and four-bit adders
- Negative numbers and two's complement
- Addition (two's complement)
- Subtraction (two's complement)
- Performance

Logic Minimization

- How to implement a desired function?

a	b	c	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

Logic Minimization

- How to implement a desired function?

a	b	c	out	minterm
0	0	0	0	$\bar{a} \bar{b} \bar{c}$
0	0	1	1	$\bar{a} \bar{b} c$
0	1	0	0	$\bar{a} b \bar{c}$
0	1	1	1	$\bar{a} b c$
1	0	0	0	$a \bar{b} \bar{c}$
1	0	1	1	$a \bar{b} c$
1	1	0	0	$a b \bar{c}$
1	1	1	0	$a b c$

sum of products:

- OR of all minterms where out=1

corollary: *any* combinational circuit *can be* implemented in two levels of logic (ignoring inverters)

Karnaugh Maps

How does one find the most efficient equation?

- Manipulate algebraically until...?
- Use Karnaugh maps (optimize visually)
- Use a software optimizer

For large circuits


- Decomposition & reuse of building blocks

Voting machine


- Voting Machine!
 - optical scan (thanks FL)
- Assume:
 - vote is recorded on paper by filling a circle
 - fixed number of choices
 - don't worry about "invalids"

Al Franken	<input type="radio"/>
Bill Clinton	<input type="radio"/>
Condi Rice	<input type="radio"/>
Dick Cheney	<input type="radio"/>
Eliot Spitzer	<input type="radio"/>
Fred Upton	<input type="radio"/>
Write-in Lizard People	<input checked="" type="radio"/>

Voting Machine Components

 

Ballots

 

The 3410 optical scan
vote counter reader
machine


5 Essential Components?

- **Input:** paper with at exactly one mark
- **Datapath:** process current ballot
- **Output:** a number the supervisor can record
- **Memory & control:** none for now

Input



 - **Photo-sensitive transistor**
 - photons replenish gate depletion region
 - can distinguish dark and light spots on paper




- Use array of N sensors for voting machine input

Output


- **7-Segment LED**
 - photons emitted when electrons fall into holes



Block Diagram

 

Encoders

 

- N might be large
- Routing wires is expensive
- More efficient encoding?

Number Representations

- Base 10 - **Decimal**

6 3 7
 10^2 10^1 10^0

- Just as easily use other bases
 - Base 2 - **Binary**
 - Base 8 - **Octal**
 - Base 16 - **Hexadecimal**

Counting

- Counting

Base Conversion

- Base conversion via repetitive division
 - Divide by base, write remainder, move left with quotient

Base Conversion

- Base conversion via repetitive division
 - Divide by base, write remainder, move left with quotient


Base Conversion

- Base conversion via repetitive division
 - Divide by base, write remainder, move left with quotient

Hexadecimal, Binary, Octal Conversions


Encoder Implementation

 - Implementation . . .
 - assume 8 choices, exactly one mark detected




3-bit encoder
(8-to-3)

Ballot Reading

 


7-Segment LED Decoder

 

- 3 inputs
- encode 0 – 7 in binary
- 7 outputs
- one for each LED


7 Segment LED Decoder Implementation

b2	b1	b0	d6	d5	d4	d3	d2	d1	d0
0	0	0							
0	0	1							
0	1	0							
0	1	1							
1	0	0							
1	0	1							
1	1	0							
1	1	1							

 


7 Segment LED Decoder Implementation

b2	b1	b0	d6	d5	d4	d3	d2	d1	d0
0	0	0	1	1	1	0	1	1	1
0	0	1	1	0	0	0	0	0	1
0	1	0	0	1	1	1	0	1	1
0	1	1	1	1	0	1	0	1	1
1	0	0	1	0	0	1	1	0	1
1	0	1	1	1	0	1	1	1	0
1	1	0	1	1	1	1	1	1	0
1	1	1	1	0	0	0	0	1	1

 




Ballot Reading and Display

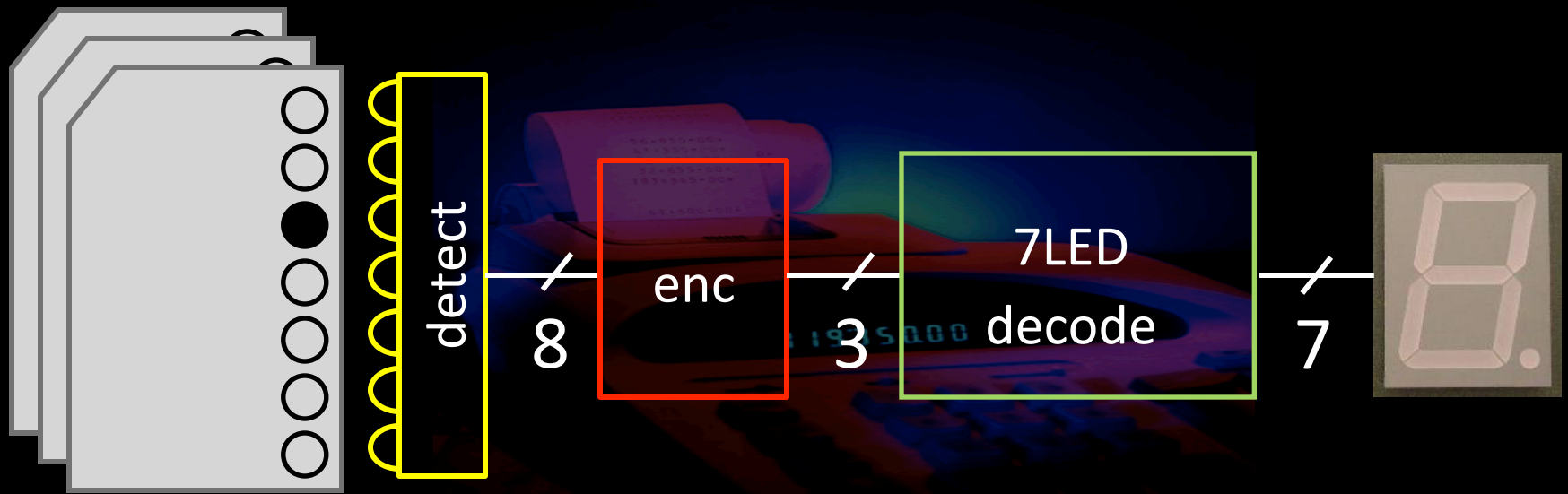

Ballots

The 3410 optical scan
vote counter reader
machine

Building Blocks

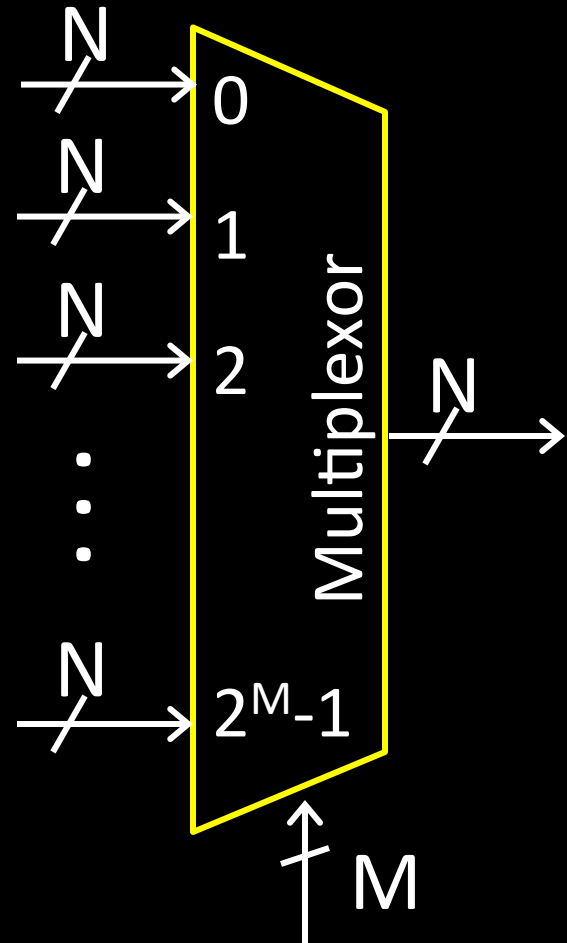  

Goals for today

Review

- Circuit design (e.g. voting machine)
- Number representations
- Building blocks (encoders, decoders, multiplexors)

Binary Operations

- One-bit and four-bit adders
- Negative numbers and two's complement
- Addition (two's complement)
- Subtraction (two's complement)
- Performance


Binary Addition

$$\begin{array}{r} 183 \\ + 254 \\ \hline \end{array}$$

$$\begin{array}{r} + 011100 \\ \hline \end{array}$$

- Addition works the same way regardless of base
 - Add the digits in each position
 - Propagate the carry


1-bit Adder

 

Half Adder

- Adds two 1-bit numbers
- Computes 1-bit result and 1-bit carry


1-bit Adder with Carry

 

Full Adder

- Adds three 1-bit numbers
- Computes 1-bit result and 1-bit carry
- Can be cascaded


4-bit Adder

 


4-Bit Full Adder

- Adds two 4-bit numbers and carry in
- Computes 4-bit result and carry out
- Can be cascaded

4-bit Adder

 

4-bit Adder

 

- Adds two 4-bit numbers, along with carry-in
- Computes 4-bit result and carry out

Arithmetic with Negative Numbers

- Addition with negatives:
 - pos + pos \rightarrow add magnitudes, result positive
 - neg + neg \rightarrow add magnitudes, result negative
 - pos + neg \rightarrow subtract smaller magnitude,
keep sign of bigger magnitude

First Attempt: Sign/Magnitude Representation

- First Attempt: Sign/Magnitude Representation
- 1 bit for sign (0=positive, 1=negative)
- N-1 bits for magnitude

Two's Complement Representation

- Better: Two's Complement Representation
- Leading 1's for negative numbers
- To negate **any** number:
 - complement *all* the bits
 - then add 1

Two's Complement

- **Non-negatives** **Negatives**

- (as usual): (two's complement: flip then add 1):

- +0 = 0000

- +1 = 0001 1110 -1 = 1111

- +2 = 0010 ~2 =

- +3 = 0011 ~3 = 1100 -3 = 1101

- +4 = 0100

- +5 = 0101

- +6 = 0110

- +7 = 0111 ~7 = 1000 -7 = 1001

- +8 = 1000 ~8 = 0111 -8 = 1000

Two's Complement Facts

- Signed two's complement
 - Negative numbers have leading 1's
 - zero is unique: $+0 = -0$
 - wraps from largest positive to largest negative
- N bits can be used to represent
 - unsigned:
 - eg: 8 bits \Rightarrow
 - signed (two's complement):
 - ex: 8 bits \Rightarrow


Sign Extension & Truncation

- Extending to larger size

- Truncate to smaller size

Two's Complement Addition

 - Addition with two's complement signed numbers
- Perform addition as usual, regardless of sign (it just works)



Diversion: 10's Complement

- How does that work?


$$\begin{array}{r} -154 \\ +283 \\ \hline \end{array}$$

Overflow

- **Overflow**
 - adding a negative and a positive?
 - adding two positives?
 - adding two negatives?
- **Rule of thumb:**
 - Overflow happened iff
carry into msb \neq carry out of msb


Two's Complement Adder

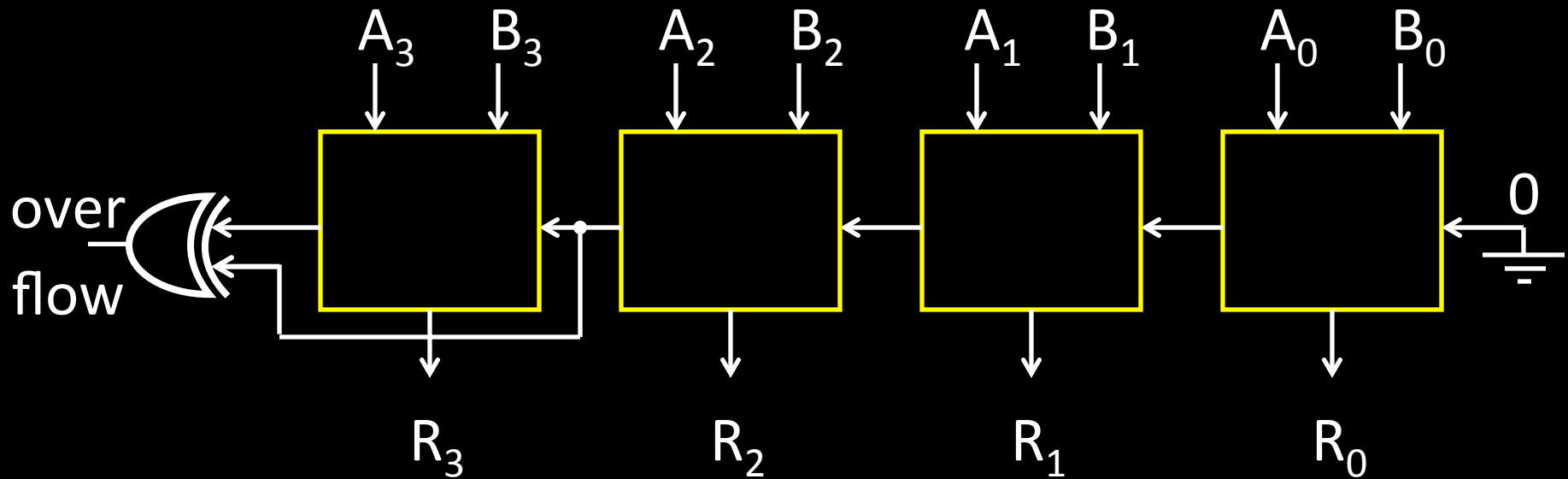- Two's Complement Adder with overflow detection



Binary Subtraction

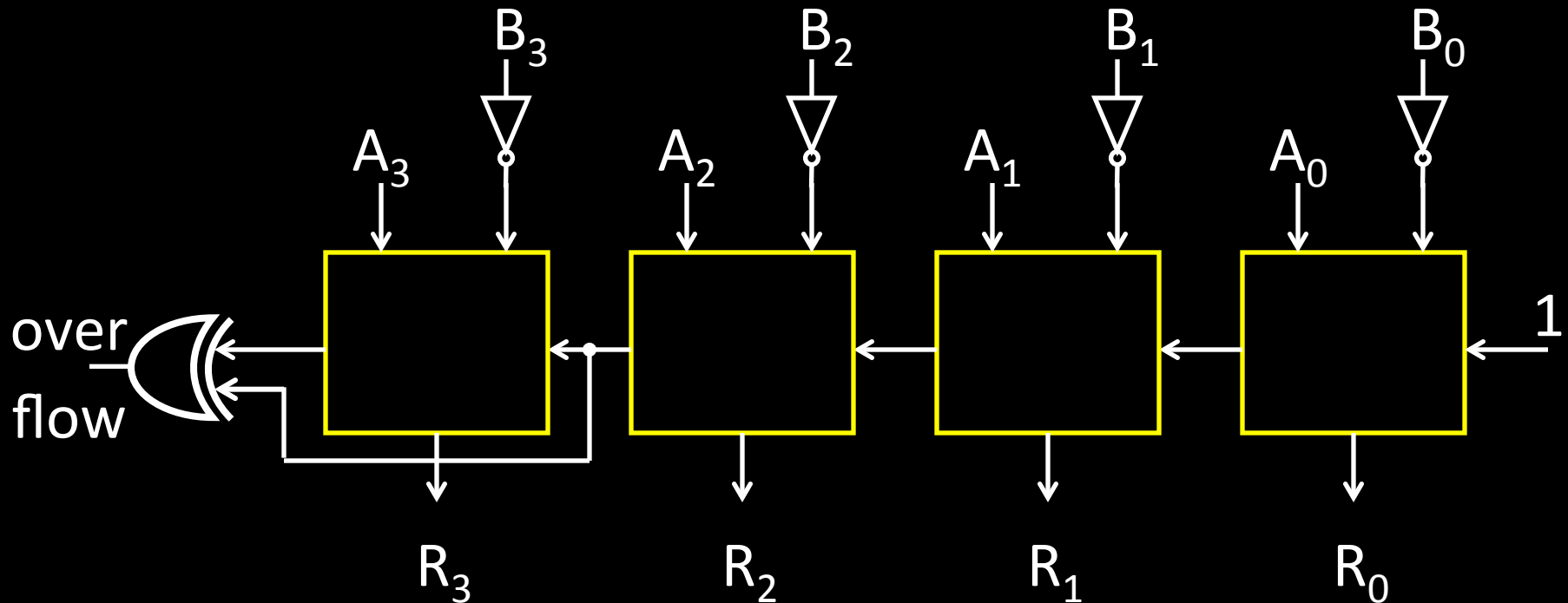- Two's Complement Subtraction
- Lazy approach —
- $A - B = A + (-B) = A + (B + 1)$



Q: What if $(-B)$ overflows?

A Calculator


A $\xrightarrow{8}$ _____

B $\xrightarrow{8}$ _____


S _____

0=add

1=sub

 


A Calculator

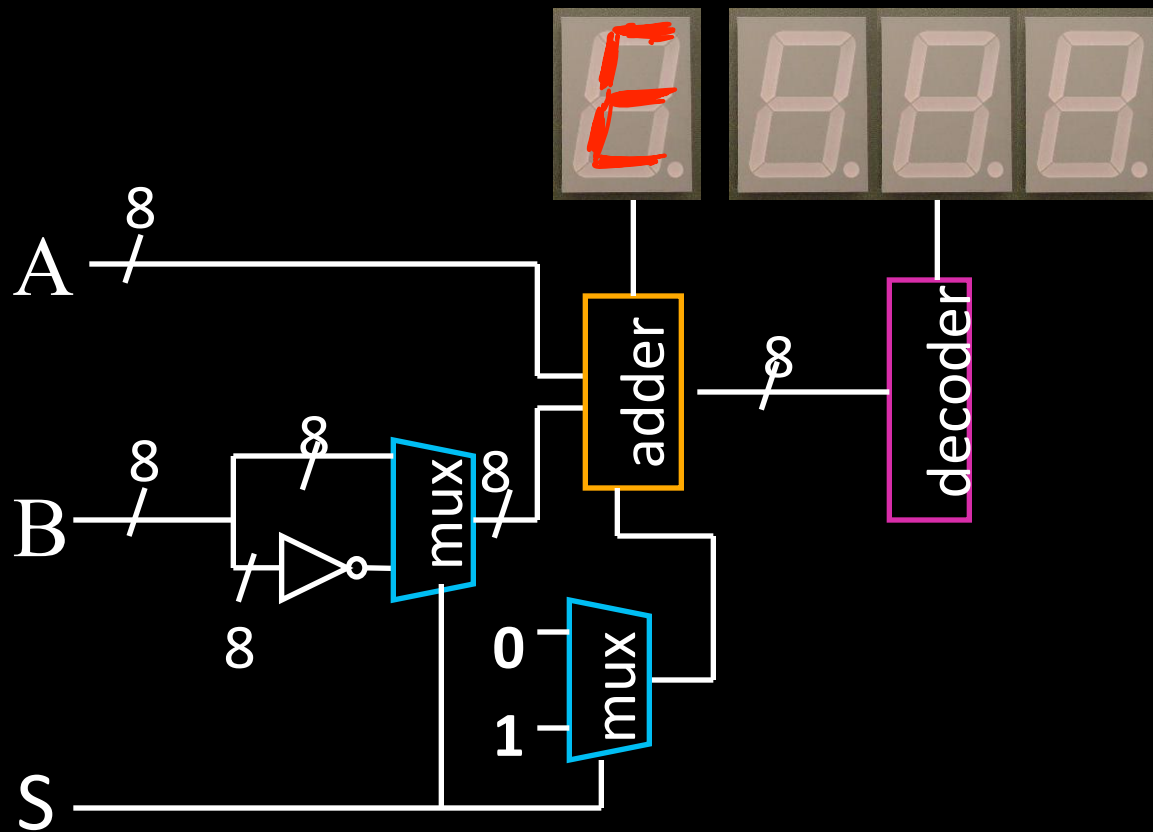


Efficiency and Generality

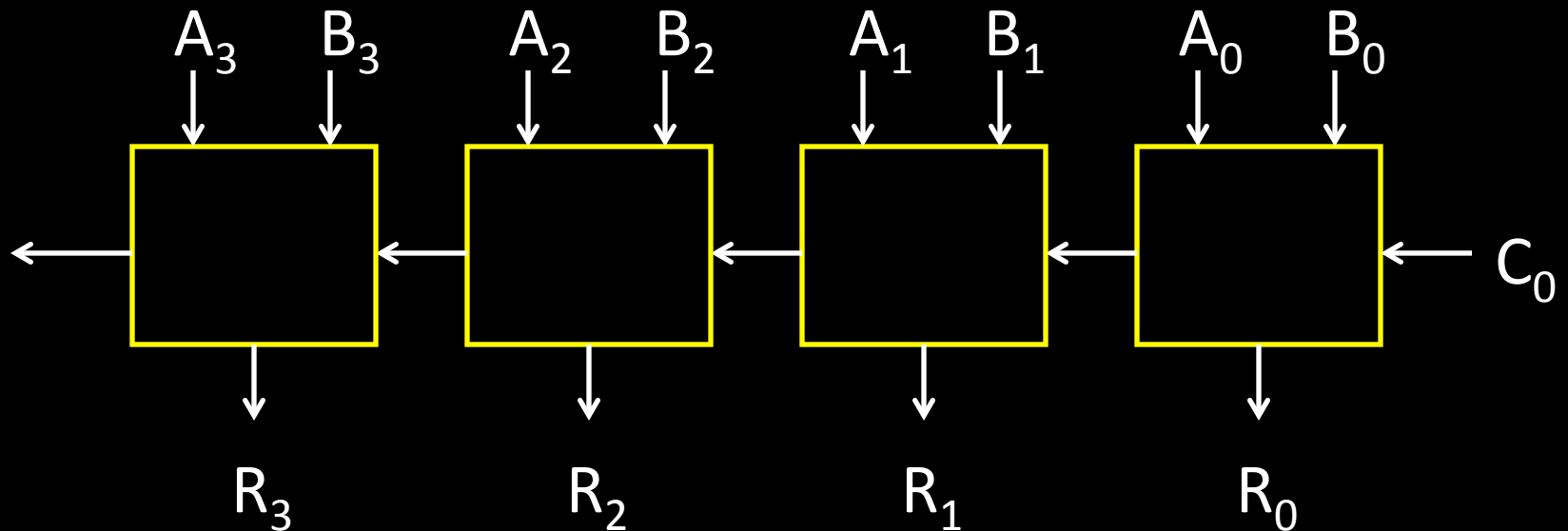- Is this design fast enough?
- Can we generalize to 32 bits? 64? more?




Performance

 - Speed of a circuit is affected by the number of gates in series (on the *critical path* or the *deepest level of logic*)



4-bit Ripple Carry Adder

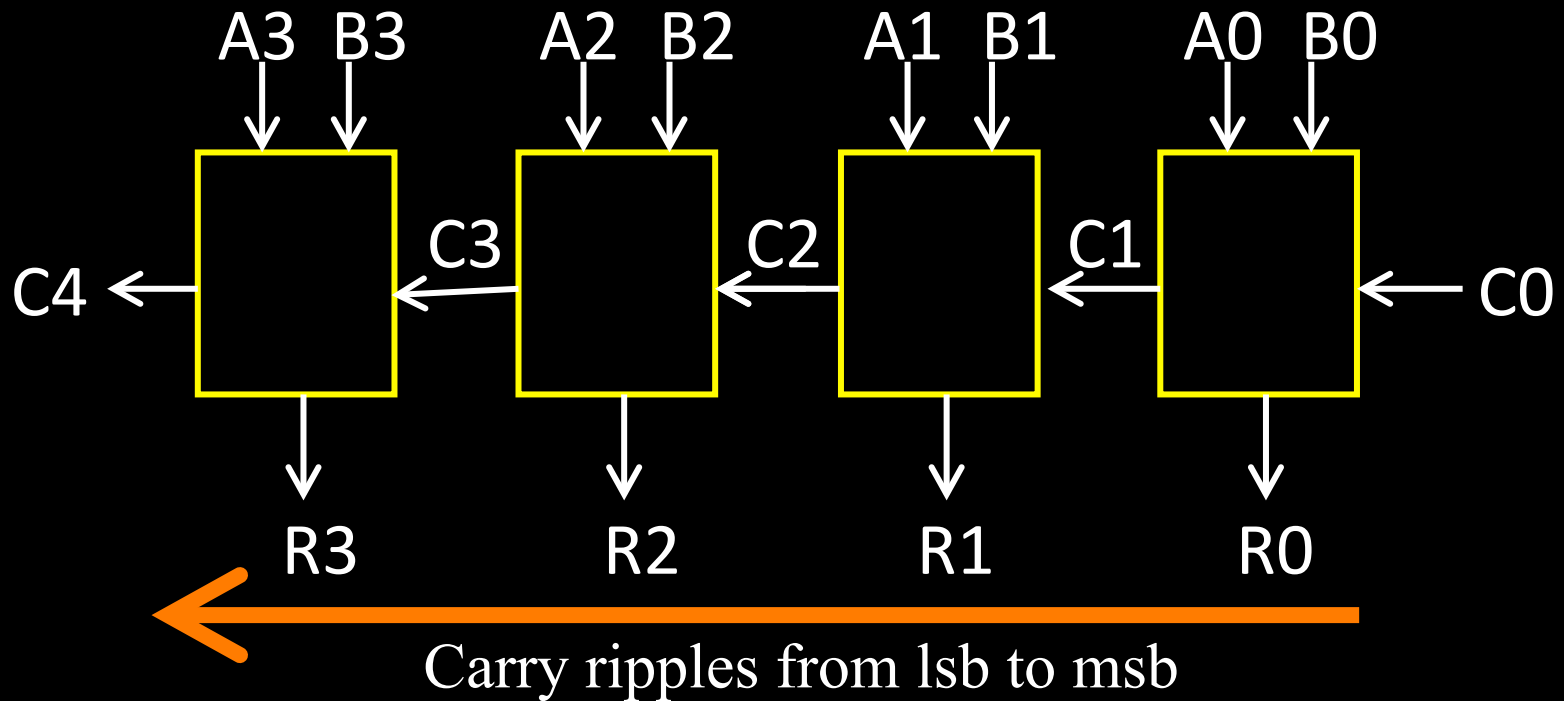

- First full adder, 2 gate delay
- Second full adder, 2 gate delay
- ...

Summary

- We can now implement any combinational (combinatorial) logic circuit
 - Decompose large circuit into manageable blocks
 - Encoders, Decoders, Multiplexors, Adders, ...
 - Design each block
 - Binary encoded numbers for compactness
 - Can implement circuits using NAND or NOR gates
 - Can implement gates using use P- and N-transistors
 - **And can add and subtract numbers (in two's compliment)!**
 - Next time, state and finite state machines...