

State & Finite State Machines

Hakim Weatherspoon

CS 3410, Spring 2011

Computer Science

Cornell University

See P&H Appendix C.7, C.8, C.10, C.11

Announcements

Make sure you are
Registered for class
Can access CMS
Have a Section you can go to
Have a project partner

Sections are on this week

HW 1 out later today
Due in one week, start early
Work alone
Use your resources

- Class notes, book, Sections, office hours, newsgroup, CSUG₂Lab

Announcements

Check online syllabus/schedule

Slides and Reading for lectures

Office Hours

Homework and Programming Assignments

Prelims: Evening of Thursday, March 10 and April 28th

Schedule is subject to change

HW1 Correction:


Hint 1: Your ALU should use your adder and left shifter as components. But, as in class, your ALU should only use a single adder component to implement both addition and subtraction. Similarly, your ALU should use only a single left shifter component to implement all of the shift

operations. For instance, **left right** shifting can be accomplished by transforming the inputs and outputs to your left shifter. You will be penalized if your final ALU circuit uses more than one adder or left shifter. Of course, always strive to make your implementation clear, but do not duplicate components in an effort to do so.

Goals for Today: Stateful Components

Until now is combinatorial logic

 - Output is computed when inputs are present
- System has no internal state
- Nothing computed in the present can depend on what happened in the past!




Need a way to record data

Need a way to build stateful circuits

Need a state-holding device


Finite State Machines

Unstable Devices

 

Bistable Devices


- Stable and unstable equilibria?

 



A Simple Device

Bistable Devices

- Stable and unstable equilibria?

 

- In stable state, $\bar{A} = B$

  


- How do we change the state?


SR Latch

Set-Reset (SR) Latch

 Stores a value Q and its complement \bar{Q}




S	R	Q	\bar{Q}
0	0	hold state	
0	1	0	1
1	0	1	0
1	1	forbidden	forbidden

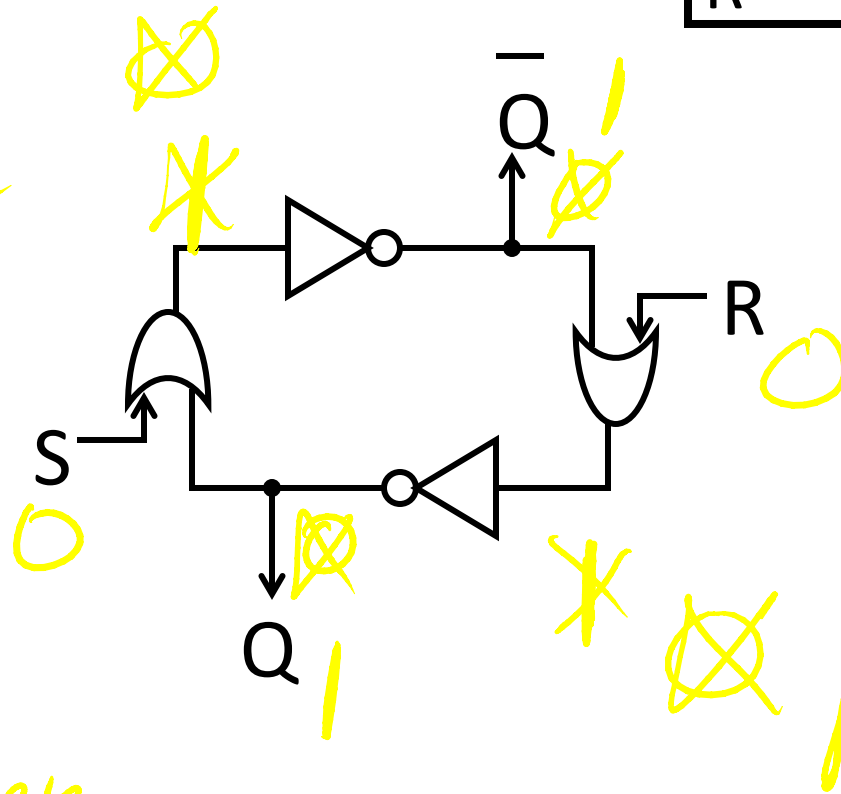

forbidden


Unclocked D Latch

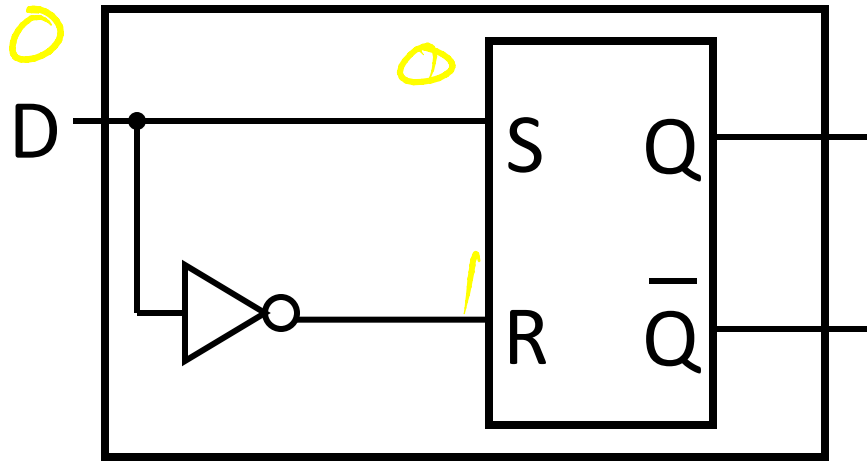

Data (D) Latch

D	Q	\bar{Q}
0	0	1
1	1	0

Unclocked D Latch

 

Data (D) Latch

D	Q	\bar{Q}
0	0	1
1	1	0

Data Latch

- Easier to use than an SR latch
- No possibility of entering an undefined state

When D changes, Q changes

– ... immediately (after a delay of 2 Ors and 2 NOTs)

Need to control when the output changes

D Latch with Clock



Level Sensitive D Latch

Clock high:

set/reset (according to D)

Clock low:


keep state (ignore D)

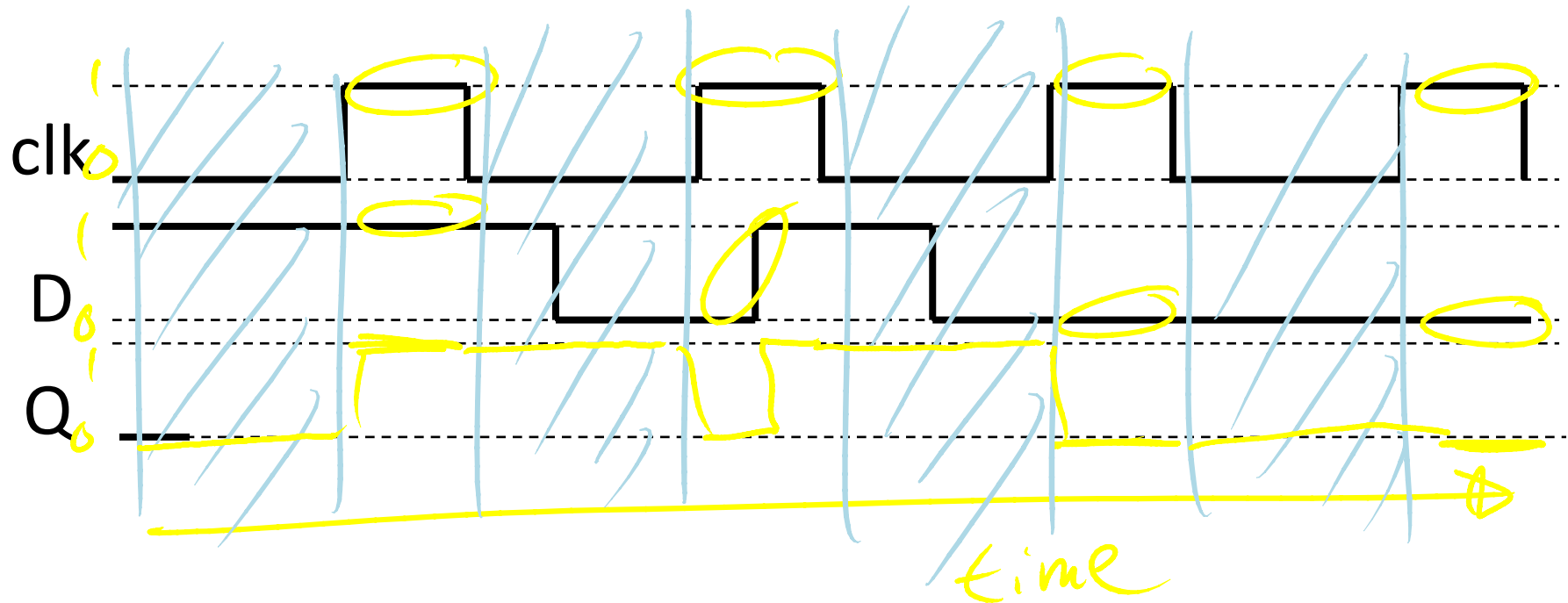 



Clocks


Clock helps coordinate state changes

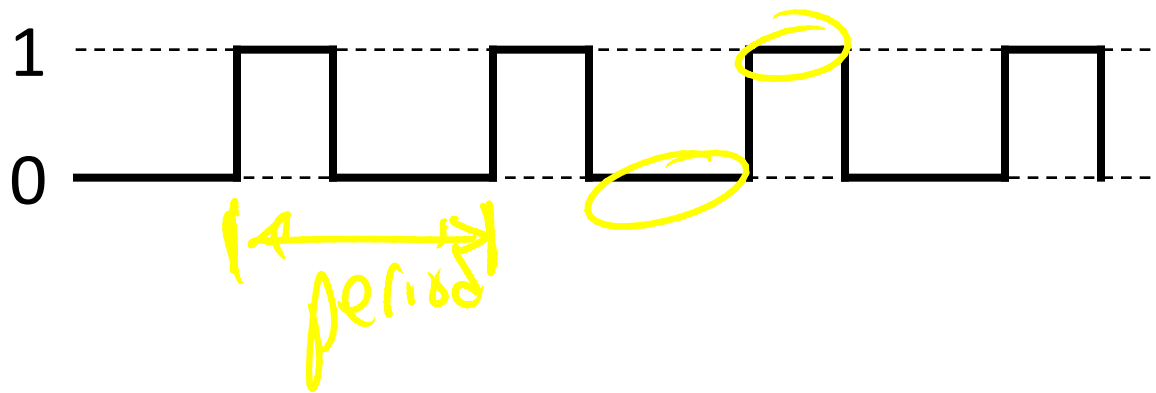- Usually generated by an oscillating crystal
- Fixed period; frequency = $1/\text{period}$



Edge-triggering

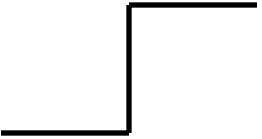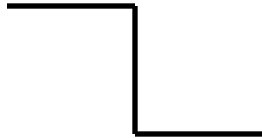
 
- Can design circuits to change on the rising or falling edge
- Trigger on rising edge = positive edge-triggered 
- Trigger on falling edge = negative edge-triggered 
- Inputs must be stable just before the triggering edge



Edge-Triggered D Flip-Flop

D Flip-Flop

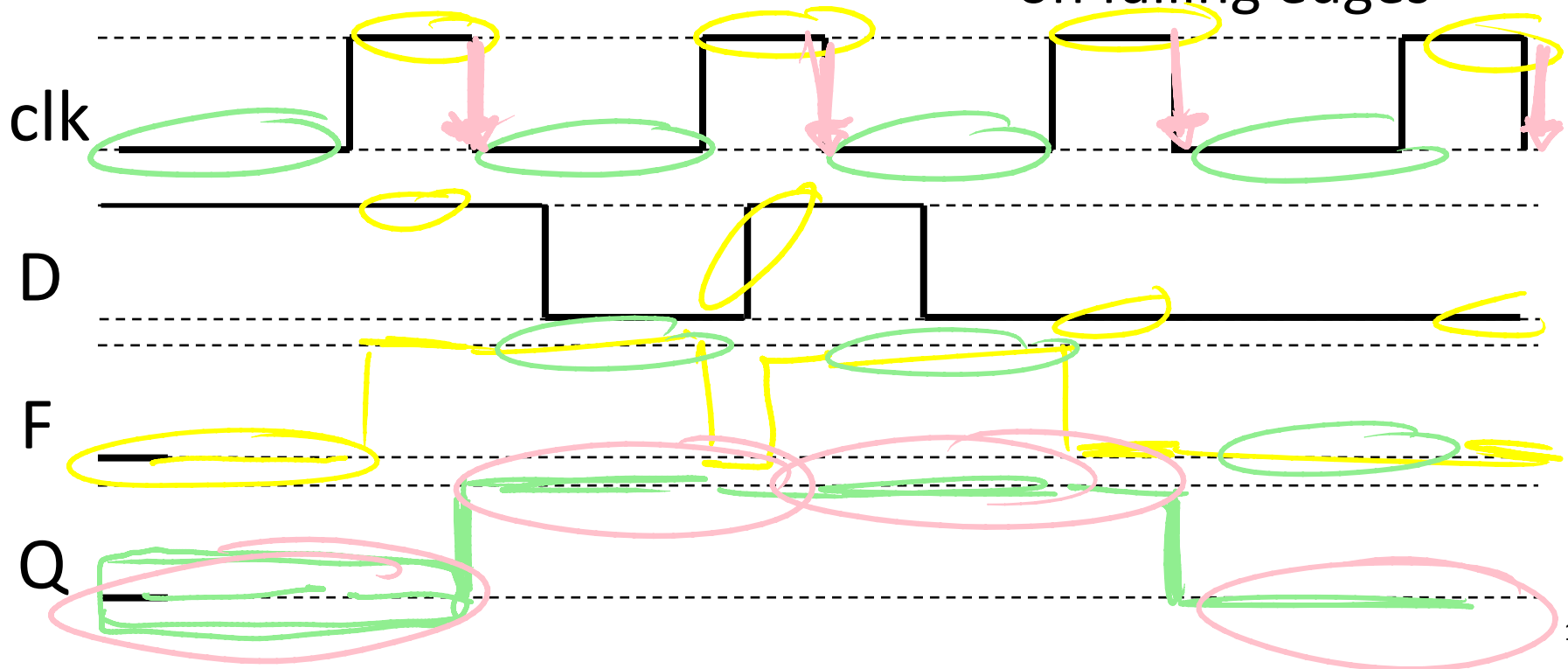 - Edge-Triggered
- Data is captured when clock is high
- Outputs change only on falling edges



Clock Disciplines


Level sensitive

- State changes when clock is high (or low)


Edge triggered

- State changes at clock edge


positive edge-triggered

 

negative edge-triggered

 


Registers

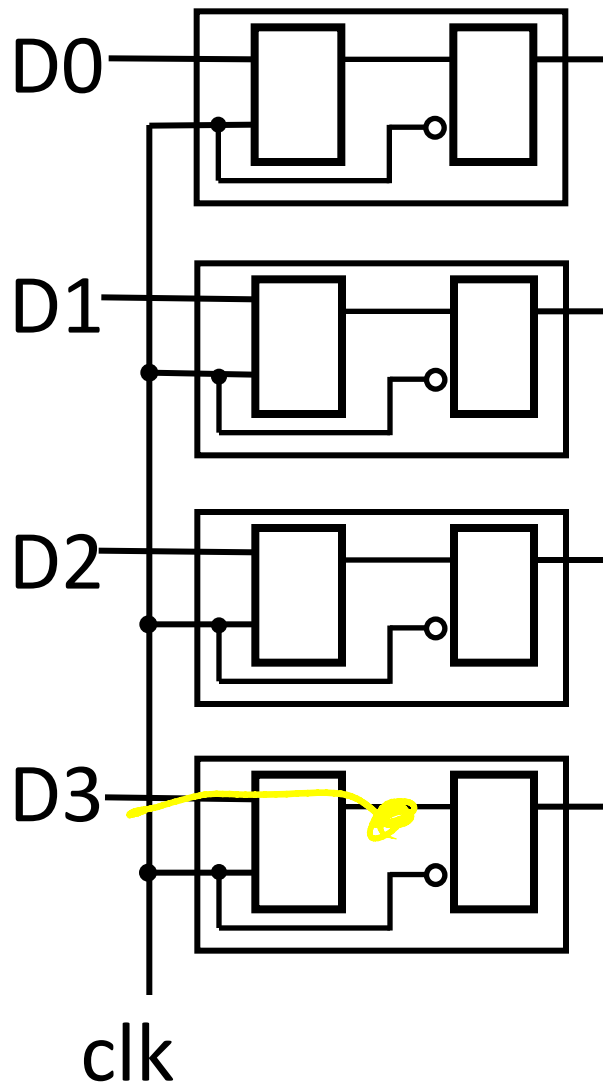


Register

 - D flip-flops in parallel
- shared clock
- extra clocked inputs: write_enable, reset, ...




Metastability and Asynchronous Inputs

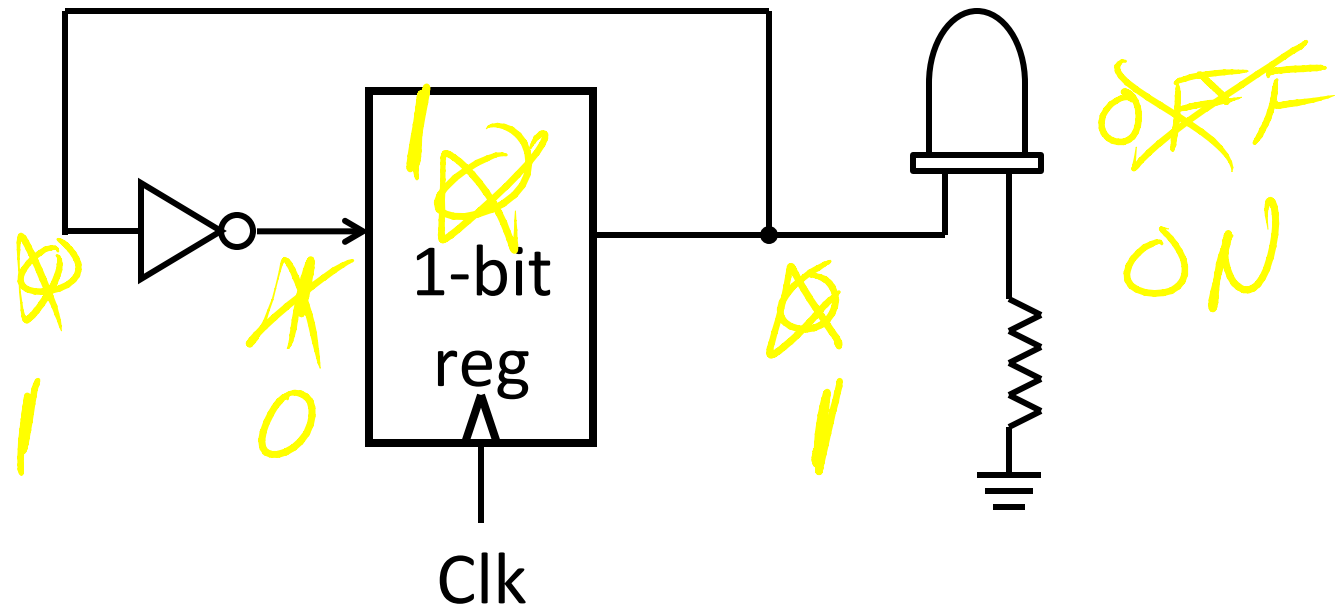


Metastability and Asynchronous Inputs

Q: What happens if input ~~changes~~ changes near clock edge?

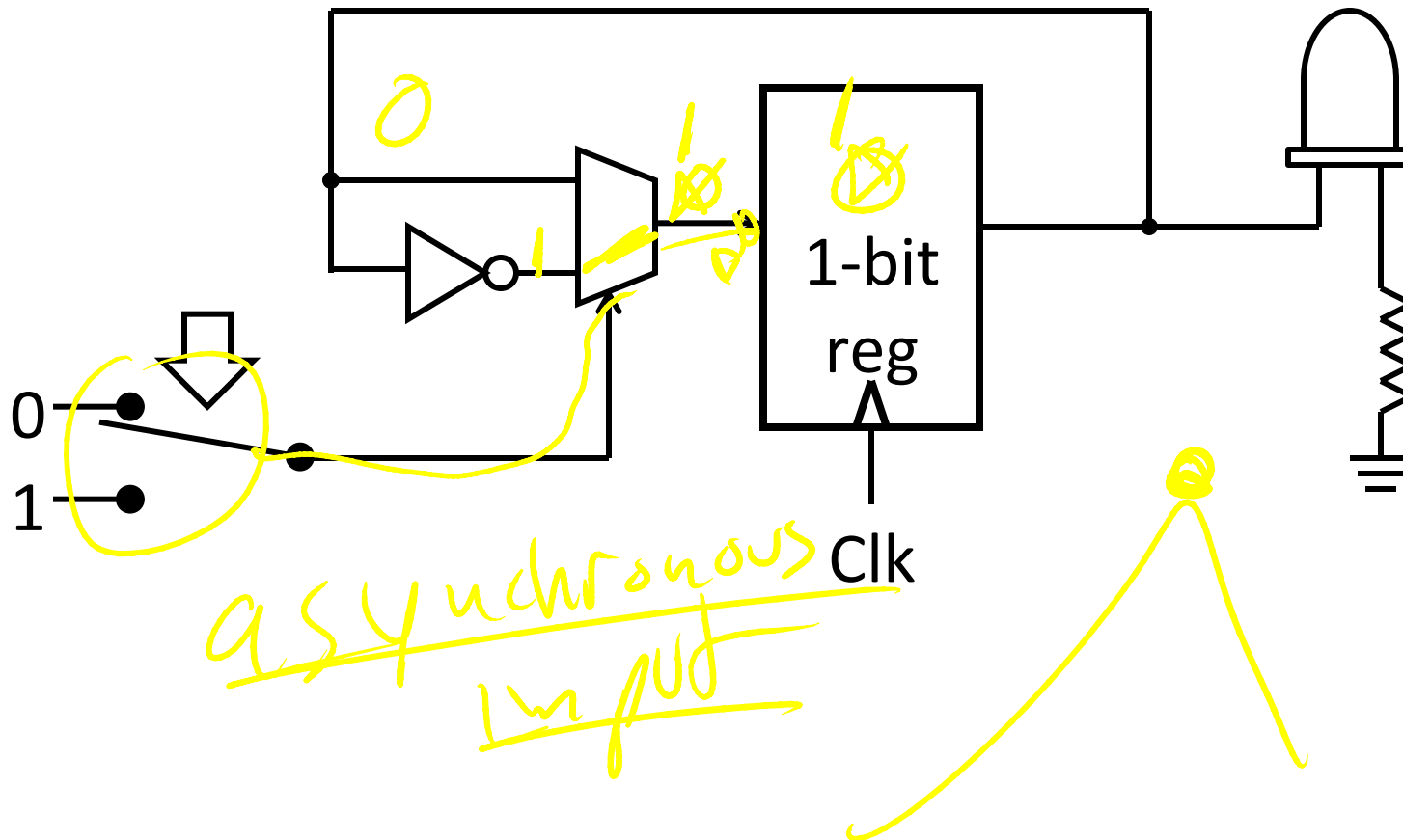A: Google “Buridan’s Principle” by Leslie Lamport




An Example

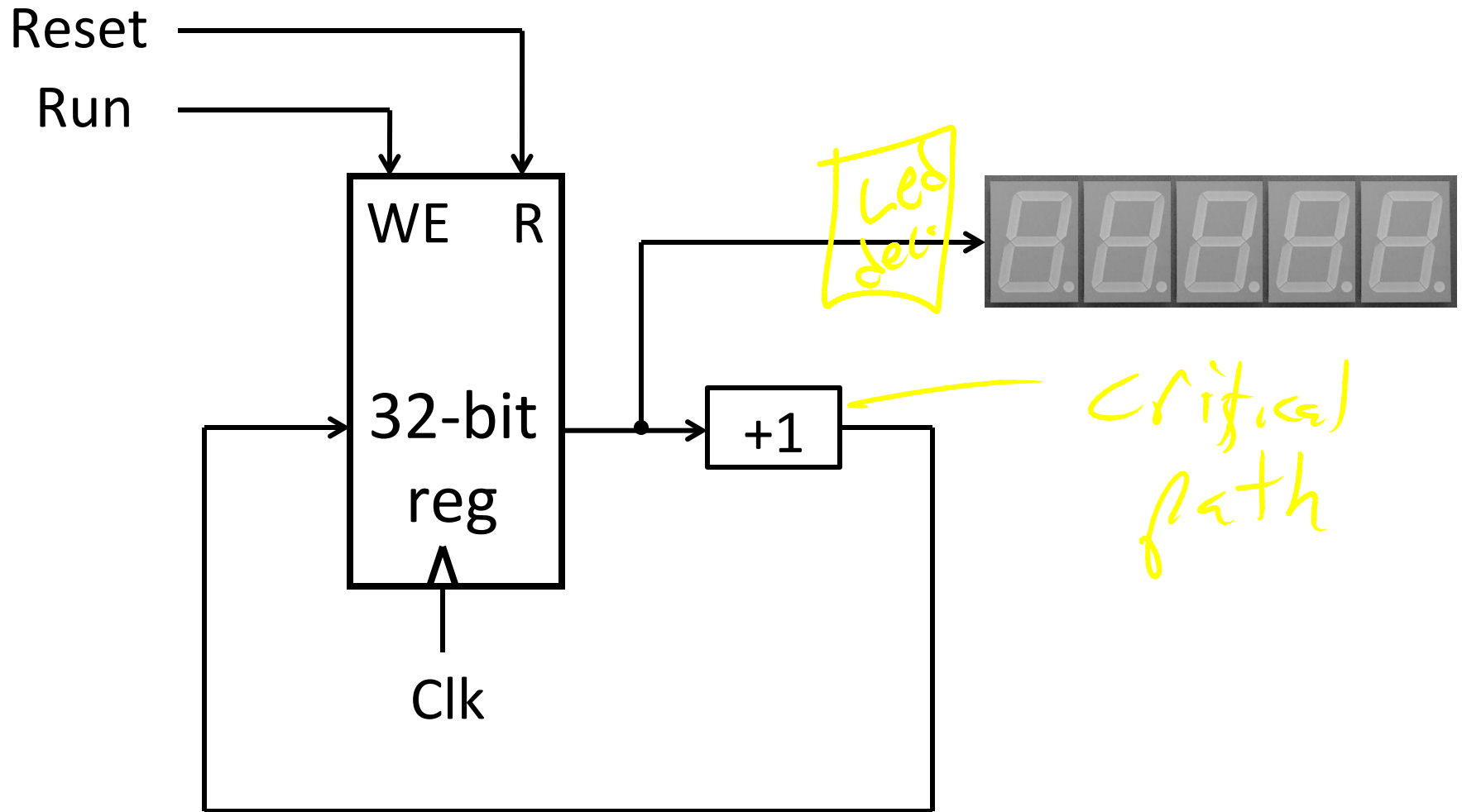

Clock Methodology

Clock Methodology

- Negative edge, synchronous

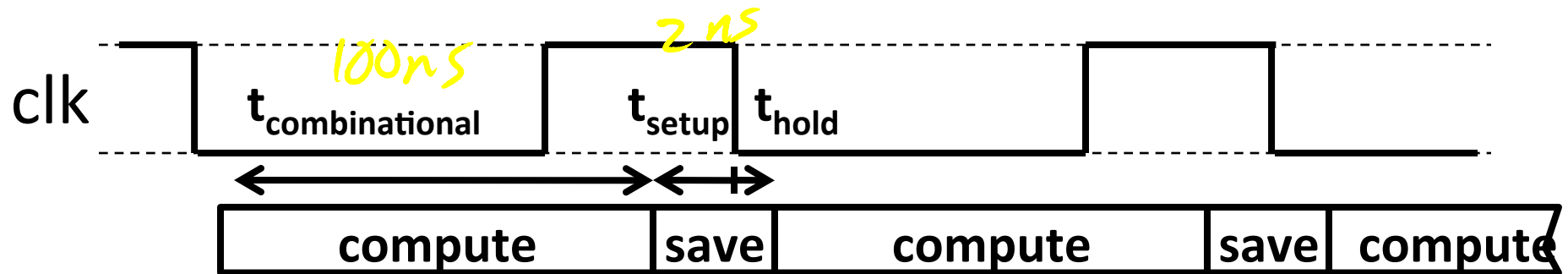

– Signals must be stable near falling clock edge

- Positive edge synchronous
- Asynchronous, multiple clocks, . . .

Finite State Machines

Finite State Machines

An electronic machine which has

- external inputs
- externally visible outputs
- internal state

Output and next state depend on

- inputs
- current state

Abstract Model of FSM

Machine is

$$M = (S, I, O, \delta)$$

S : Finite set of states


I : Finite set of inputs

O : Finite set of outputs

δ : State transition function


Next state depends on present input *and*
present state

Voting Machine

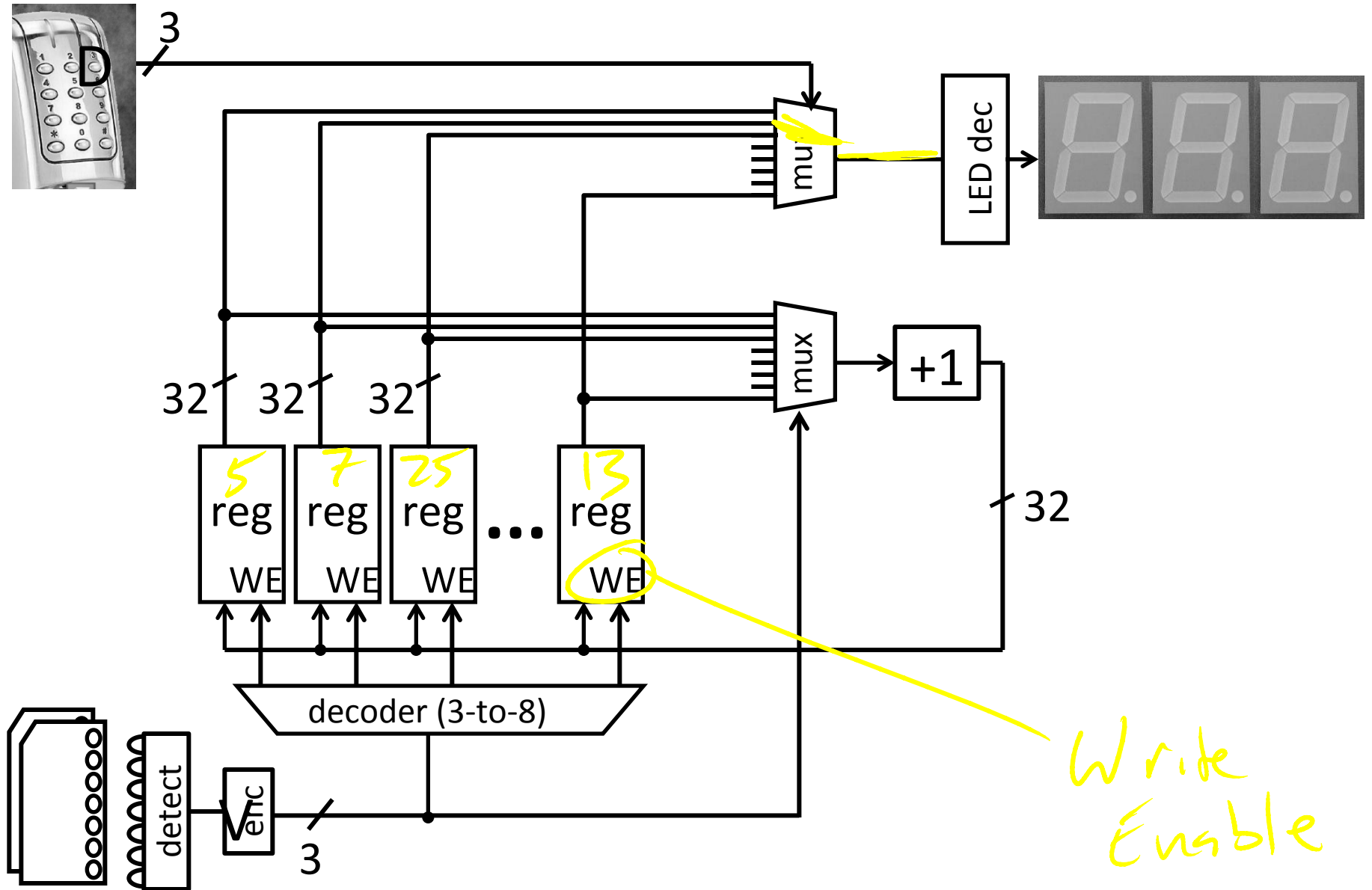



Automata Model

Finite State Machine

 

- inputs from external world
- outputs to external world
- internal state
- combinational logic

FSM Example

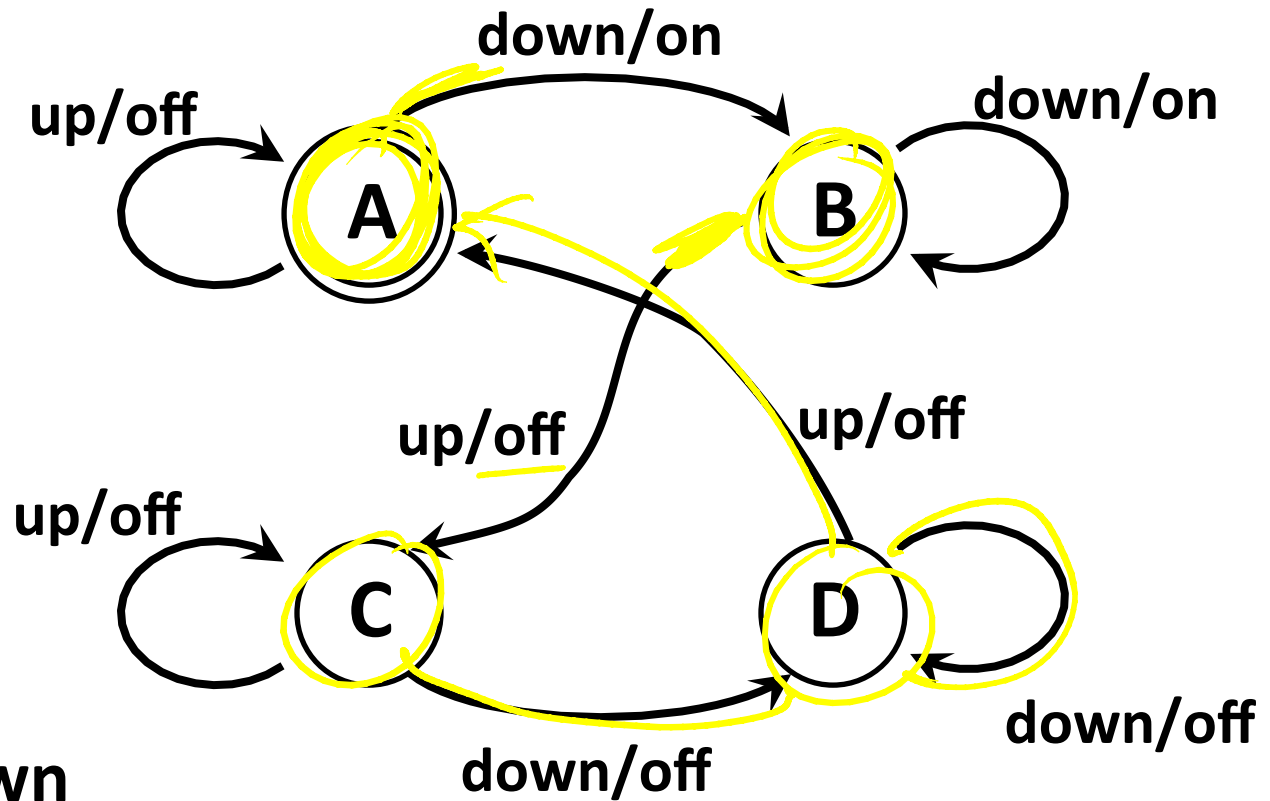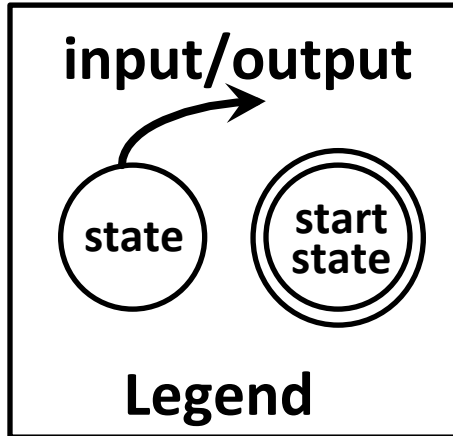



Input: **up** or **down**

Output: **on** or **off**

States: **A**, **B**, **C**, or **D**

In: D U D D U
 State: B C D D A
 Out: ON OFF OFF OFF OFF

FSM Example Details

 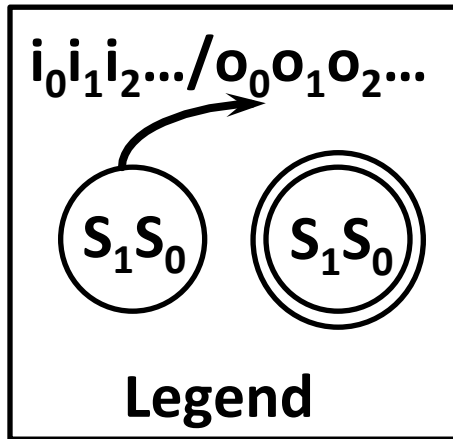


Input: **0**=up or **1**=down

Output: **1**=on or **1**=off

States: **00**=A, **01**=B, **10**=C, or **11**=D

Mealy Machine


General Case: Mealy Machine

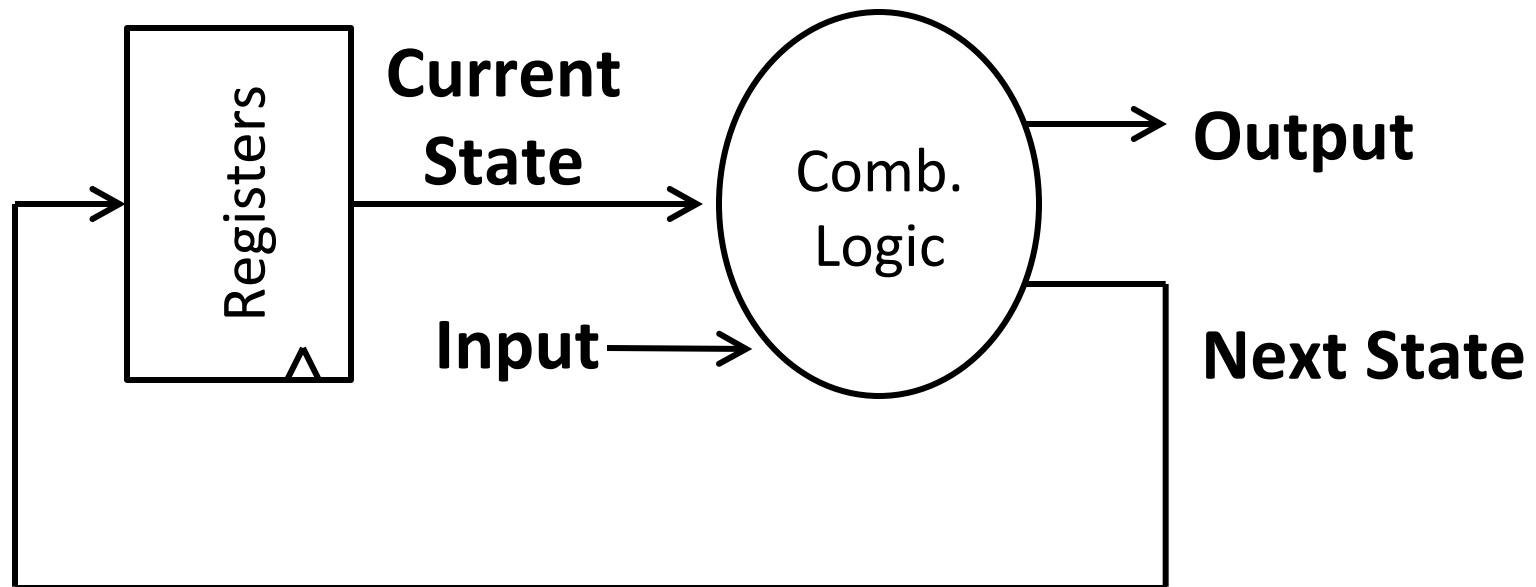

Outputs and next state depend on both current state and input



Moore Machine

Special Case: Moore Machine

 

Outputs depend only on current state

Moore Machine Example

  

Input: **up** or **down**

Output: **on** or **off**

States: **A**, **B**, **C**, or **D**

Digital Door Lock



Digital Door Lock

Inputs:

- keycodes from keypad
- clock

Outputs:

- “unlock” signal
- display how many keys pressed so far

Door Lock: Inputs

Assumptions:

- signals are synchronized to clock
- Password is B-A-B




K
A
B

K	A	B	Meaning
0	0	0	∅ (no key)
1	1	0	'A' pressed
1	0	1	'B' pressed


Door Lock: Outputs

Assumptions:


- High pulse on U unlocks door

 


Door Lock: Simplified State Diagram

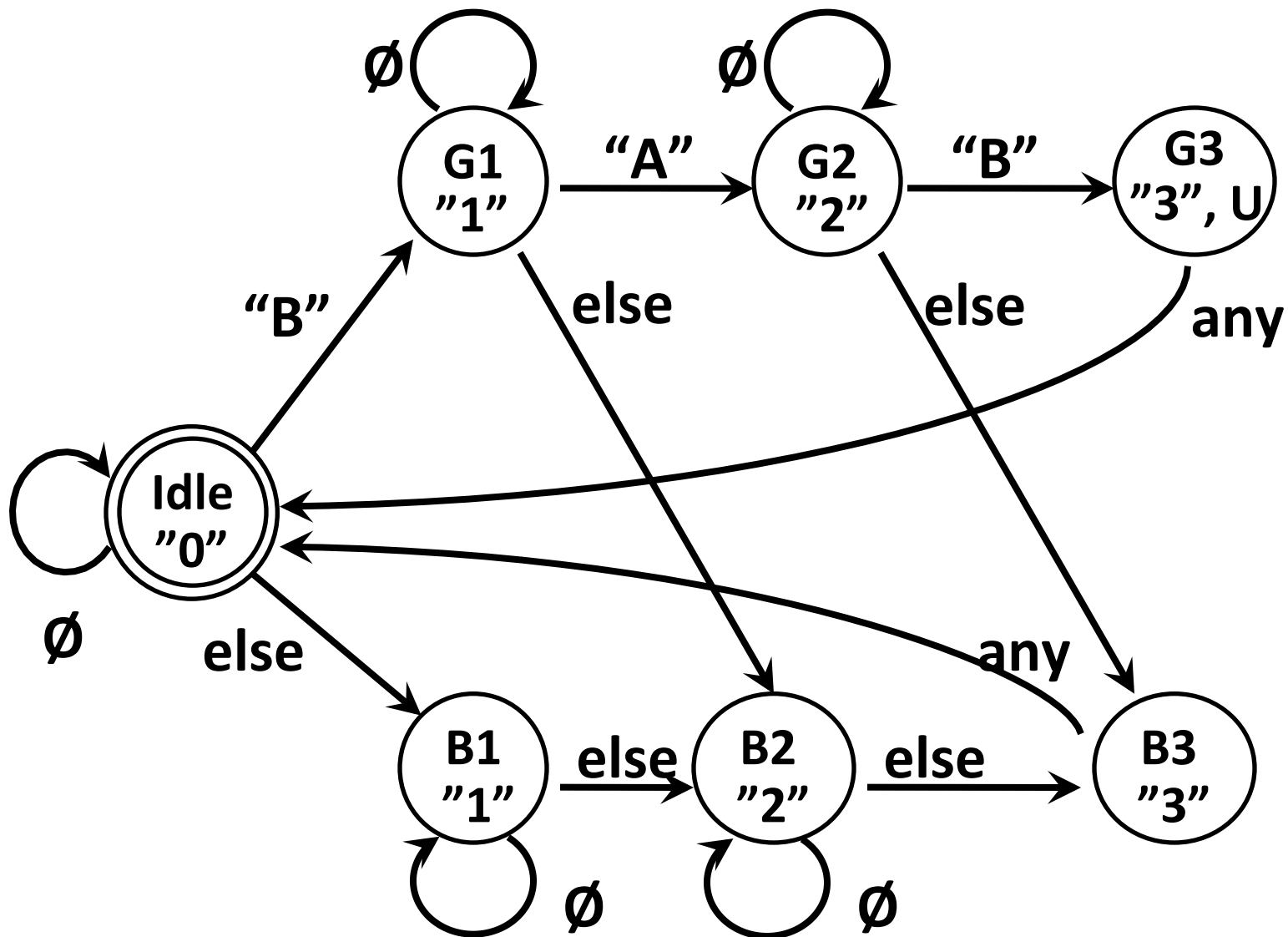


Door Lock: Simplified State Diagram

 

Door Lock: Simplified State Diagram

 

Door Lock: Simplified State Diagram

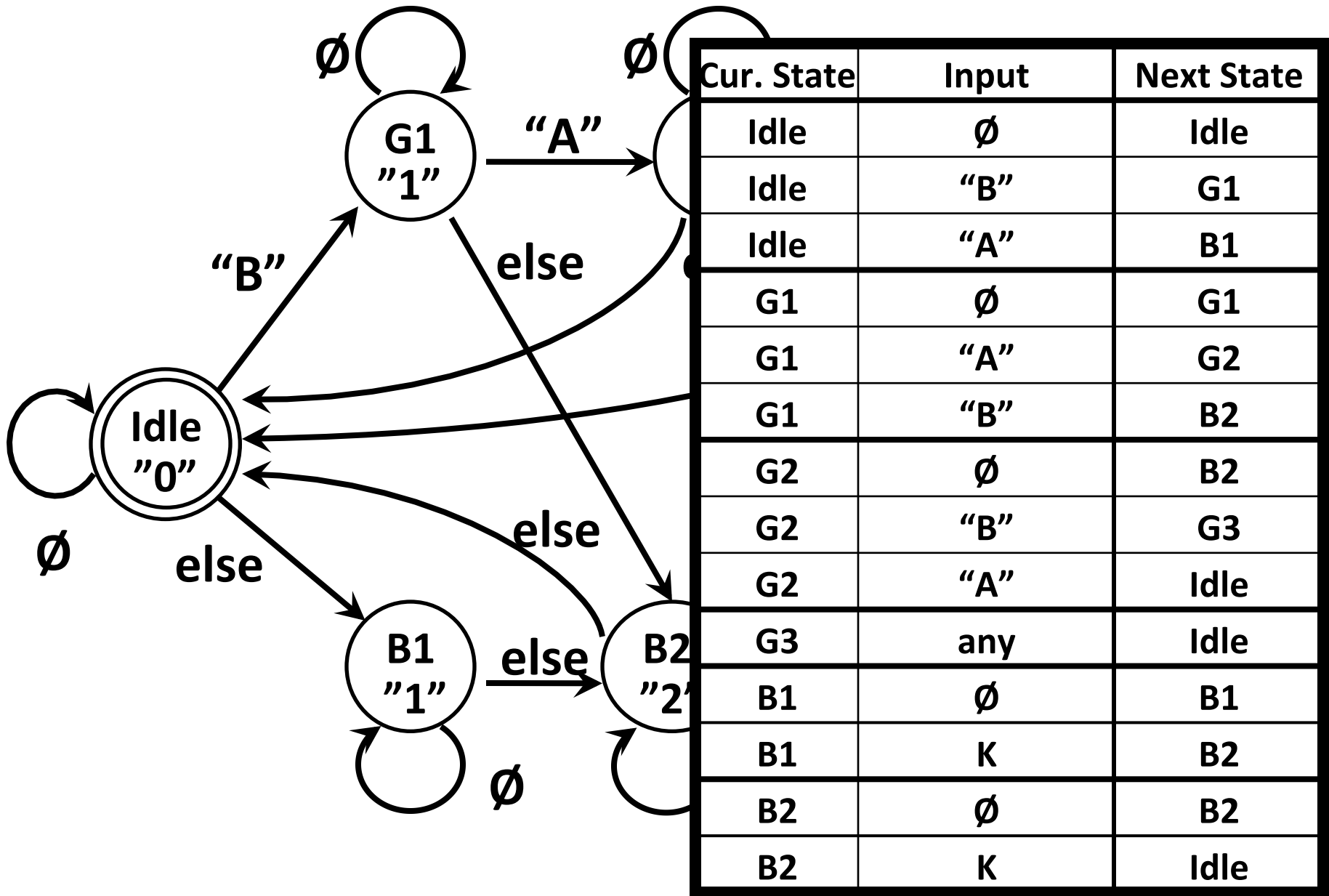

Cur. State	Input	Next State
Idle	\emptyset	Idle
Idle	"B"	G1
Idle	"A"	B1
G1	\emptyset	G1
G1	"A"	G2
G1	"B"	B2
G2	\emptyset	B2
G2	"B"	G3
G2	"A"	Idle
G3	any	Idle
B1	\emptyset	B1
B1	K	B2
B2	\emptyset	B2
B2	K	Idle

State Table Encoding


S ₂	S ₁	S ₀	D ₃	D ₂	D ₁	D ₀	U
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	0	0	1	1	1
1	0	0	0	0	0	1	0
1	0	1	0	0	1	0	0

D

State	S ₂	S ₁	S ₀
Idle	0	0	0
G1	0	0	1
G2	0	1	0
G3	0	1	1
B1	1	0	0
B2	1	0	1

S ₂	S ₁	S ₀	K	A	B	S' ₂	S' ₁	S' ₀
0	0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	0	1
0	0	0	1	1	0	1	0	0
0	0	1	0	0	0	0	0	1
0	0	1	1	1	0	0	1	0
0	0	1	1	0	1	1	0	1
0	1	0	0	0	0	0	1	0
0	1	0	1	0	1	0	1	1
0	1	0	1	1	0	0	0	0
0	1	1	x	x	x	0	0	0
1	0	0	0	0	0	1	0	0
1	0	0	1	x	x	1	0	1
1	0	1	0	0	0	1	0	1
1	0	1	1	x	x	0	0	0

Door Lock: Implementation

 

Strategy:

- (1) Draw a state diagram (e.g. Moore Machine)
- (2) Write output and next-state tables
- (3) Encode states, inputs, and outputs as bits
- (4) Determine logic equations for next state and outputs

Summary

We can now build interesting devices with sensors

- Using combinational logic

We can also store data values

- Stateful circuit elements (D Flip Flops, Registers, ...)
- Clock to synchronize state changes
- But be wary of asynchronous (un-clocked) inputs
- State Machines or Ad-Hoc Circuits