
Memory

Hakim Weatherspoon
CS 3410, Spring 2011
Computer Science
Cornell University

See: P&H Appendix C.8, C.9

Announcements

HW1 due today

HW2 available later today

HW2 due in one week and a half

Work **alone**

Use your resources

- FAQ, class notes, book, Sections, office hours, newsgroup, CSUGLab

Make sure you

- Registered for class, can access CMS, have a Section, and have a project partner
- Check online syllabus/schedule, review slides and lecture notes, Office Hours, early homework and programming assignments

Announcements

Prelims: Evening of Thursday, March 10 and April 28th


Late Policy

- 1) Each person has a total of **four “slip days”**
- 2) For projects, slip days are deducted from all partners
- 3) 10% deducted per day late after slip days are exhausted

Critical Path

Which operation is the critical path?


- A) AND
- B) OR
- C) ADD/SUB
- D) LT

 

Critical Path

What is the length of the critical path (in gates)?


- A) 3
- B) 5
- C) 8
- D) 11

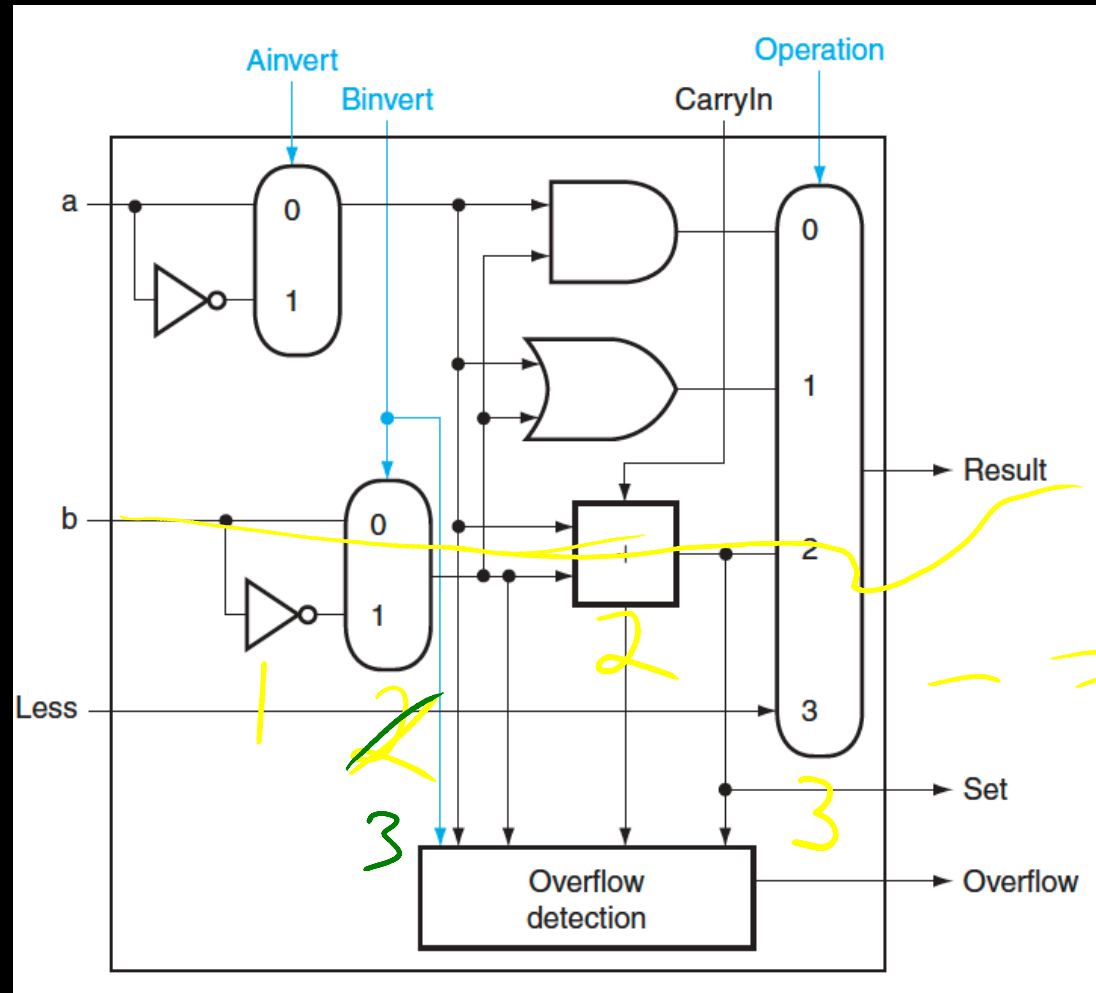



Critical Path

What is the length of the critical path for a 32-bit ALU (in gates)?

- A) 11
- B) 32
- C) 64
- D) 70

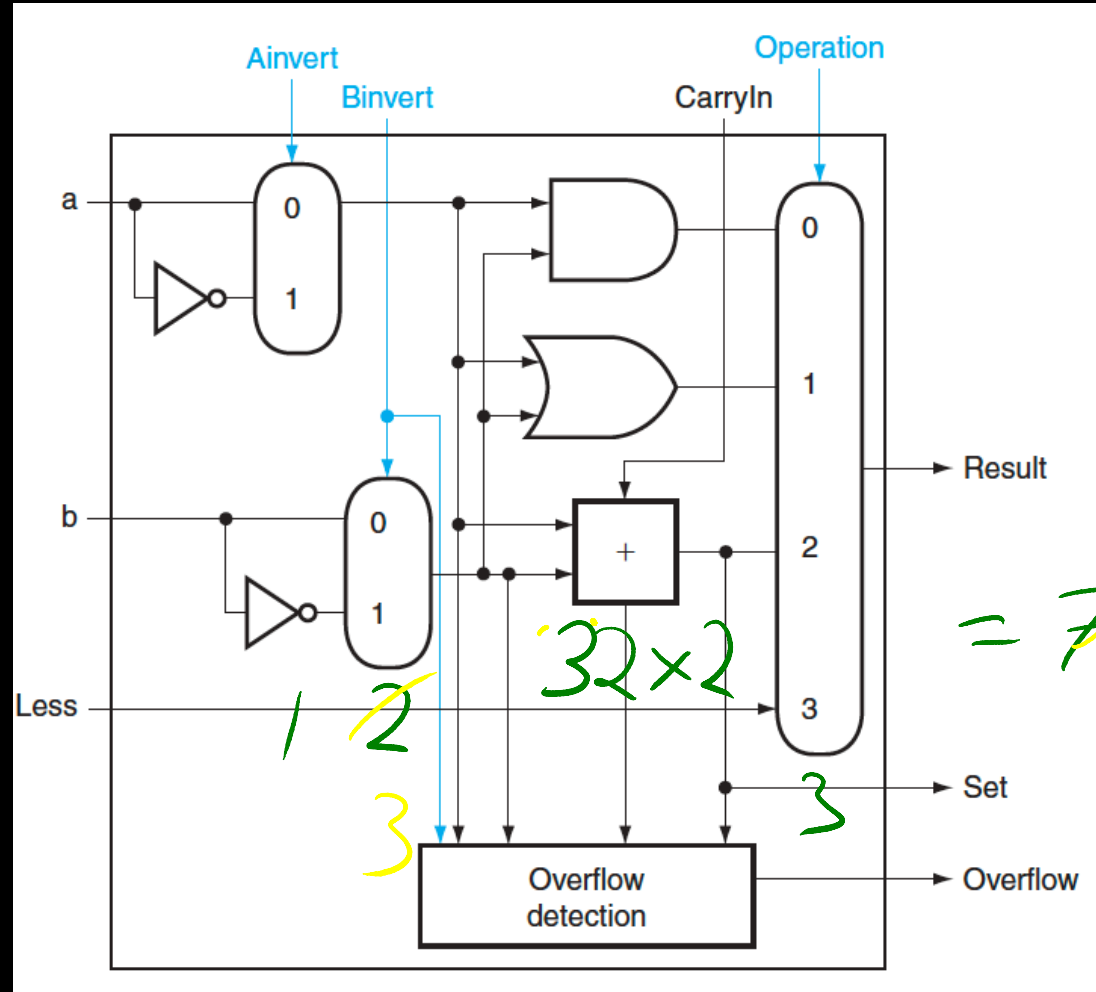


Multiplexor

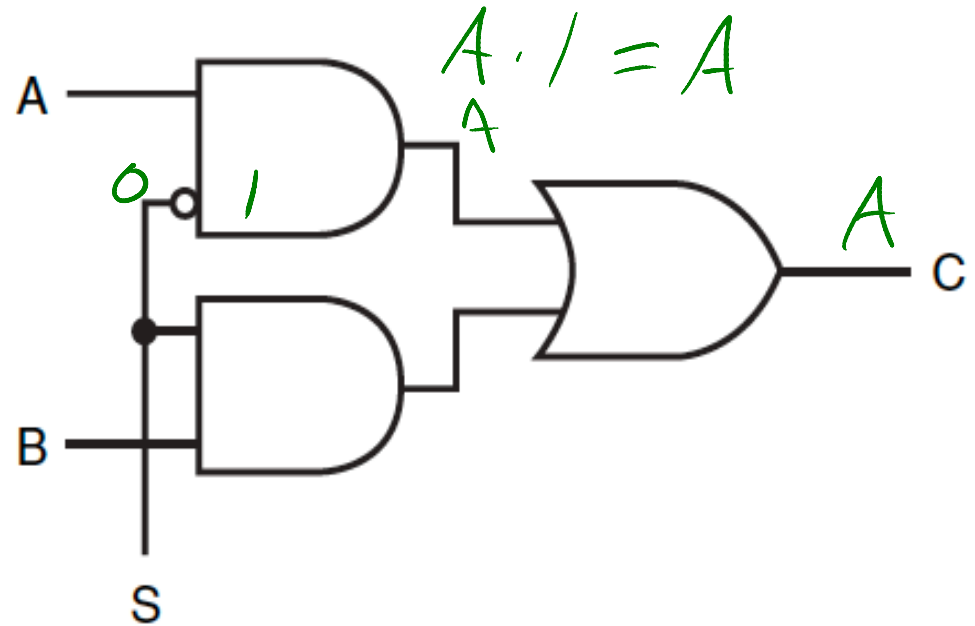 

Multiplexor

A-0
B-1
C-2
D-3
S-2
S

 

Goals for today

Review


- SR Latches, D Latches, D Flip Flips, and Registers

Memory

- Register Files
- Tri-state devices
- SRAM (Static RAM—random access memory)
- DRAM (Dynamic RAM)

Bistable Devices

- Stable and unstable equilibria?

 


A Simple Device

How to change?



Bistable Devices

- Stable and unstable equilibria?

 


A Simple Device

- In stable state, $\bar{A} = B$

  

- How do we change the state?

SR Latch

 


SR Latch

Set-Reset (SR) Latch

Stores a value Q and its complement \bar{Q}

S	R	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	1	0
1	0	0	1
1	1	---	---

 


forbidden

SR Latch

Set-Reset (SR) Latch


Stores a value Q and its complement \bar{Q}

S	R	Q	\bar{Q}
0	0	Q	Q
0	1	0	1
1	0	1	0
1	1	forbidden	

 

Unclocked D Latch

Data (D) Latch

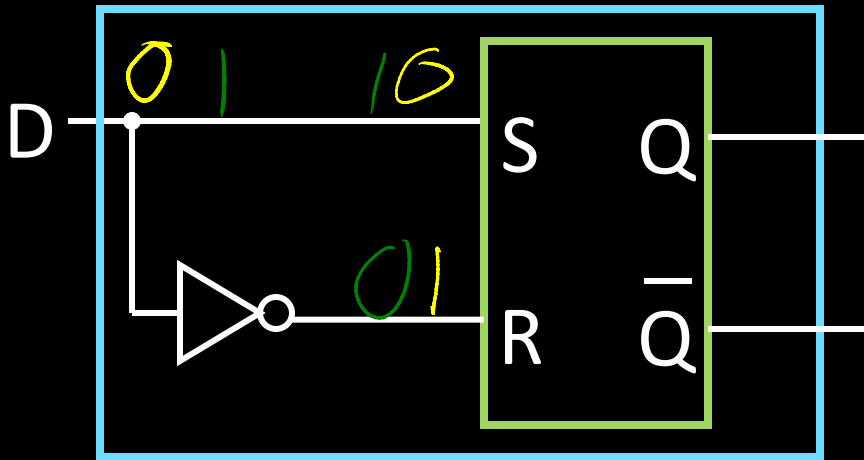


D	Q	\bar{Q}
0	0	1
1	1	0

Problem
cannot control
when output
changes
Q is always same as D

Unclocked D Latch

Data (D) Latch

 

D	Q	\bar{Q}
0	0	1
1	1	0

Data Latch


- Easier to use than an SR latch
- No possibility of entering an undefined state

When D changes, Q changes

- ... immediately (after a delay of 2 Ors and 2 NOTs)

Need to control when the output changes

D Latch with Clock

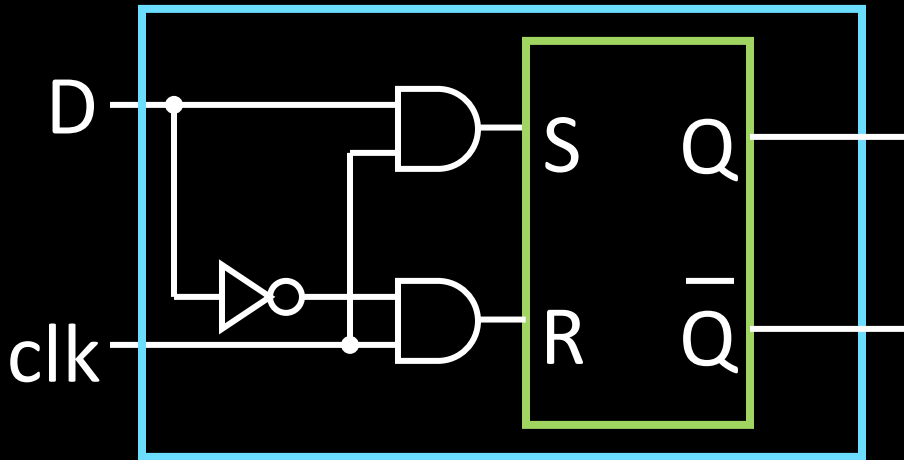

D	Q	\bar{Q}
0	0	1
1	1	0

Level Sensitive D Latch

Clock high:


set/reset (according to D)

Clock low:

keep state (ignore D)

D Latch with Clock

$$D \cdot 1 = D$$

 


D	Q	\bar{Q}
0	0	1
1	1	0


S	R	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	0	1
1	0	1	0
1	1	forbidden	

clk	D	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	Q	\bar{Q}
1	0	0	1
1	1	1	0

D Latch with Clock

 


D	Q	\bar{Q}
0	0	1
1	1	0

 


clk	D	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	Q	\bar{Q}
1	0	0	1
1	1	1	0

Edge-Triggered D Flip-Flop

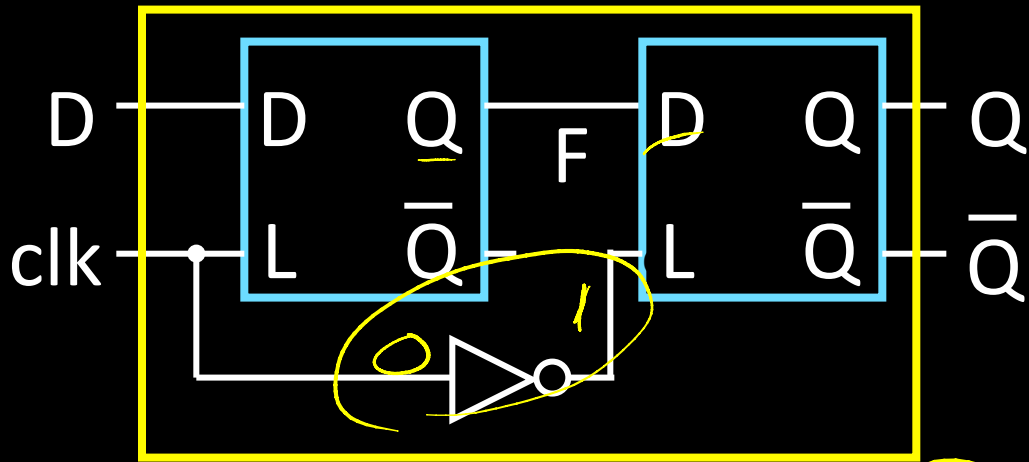

D Flip-Flop


 
- Edge-Triggered
- Data is captured when clock is high
- Outputs change only on falling edges




Registers

Register

  - D flip-flops in parallel
- shared clock
- extra clocked inputs: write_enable, reset, ...



Voting Machine

 

Goals for today

Review

- SR Latches, D Latches, D Flip Flips, and Registers

Memory

- Register Files
- Tri-state devices
- SRAM (Static RAM—random access memory)
- DRAM (Dynamic RAM)


Register File

Register File

- N read/write registers
- Indexed by register number

Implementation:

 - D flip flops to store bits
- Decoder for each **write port**
- Mux for each **read port**



$$2^5 = 32$$


Register File

Register File

- N read/write registers
- Indexed by register number

Implementation:

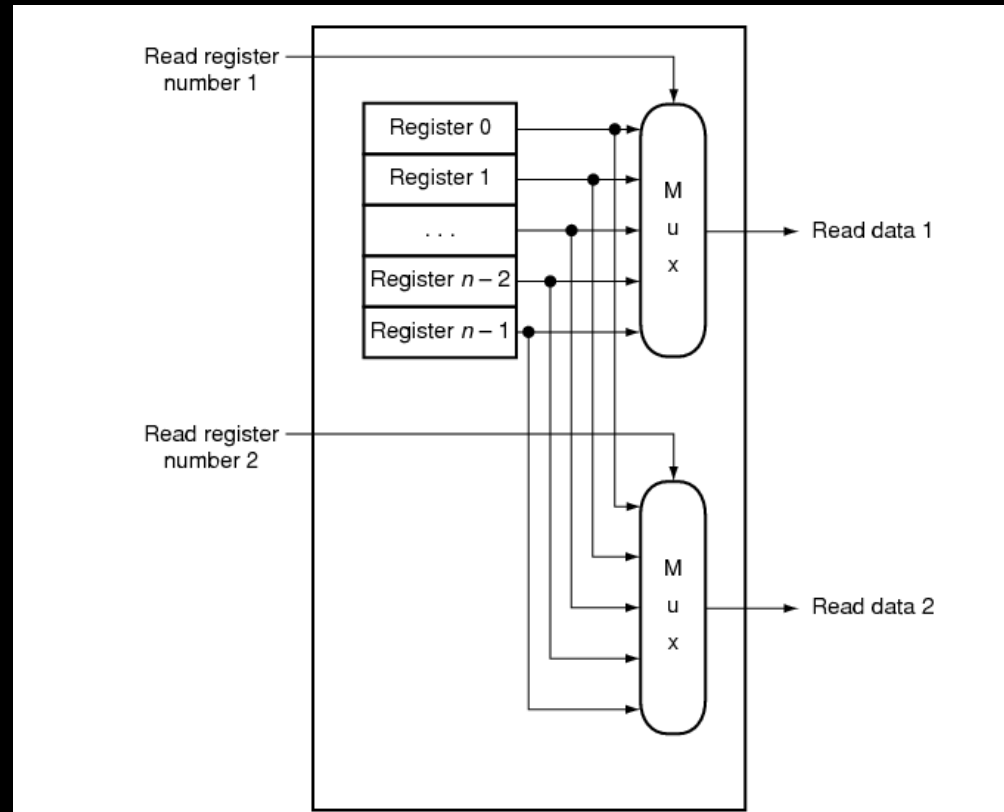- D flip flops to store bits
- Decoder for each write port
- Mux for each read port




Register File

Register File

- N read/write registers
- Indexed by register number

Implementation:

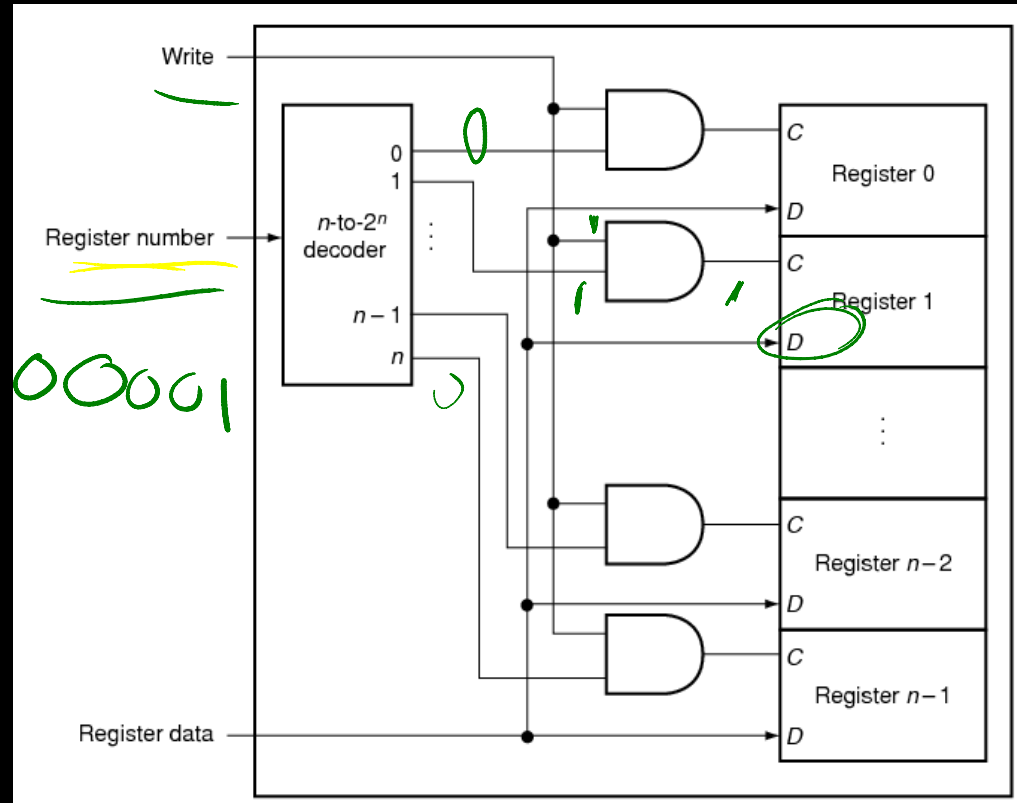- D flip flops to store bits
- Decoder for each write port
- Mux for each read port



Tradeoffs

Register File tradeoffs


- + Very fast (a few gate delays for both read and write)
- + Adding extra ports is straightforward
- Doesn't scale

21 to 2 million
2 M lines

Building Large Memories

Need a shared **bus** (or shared **bit line**)

 
- Many FFs/outputs/etc. connected to single wire
- Only one output *drives* the bus at a time




only one device / reg
drives bus at a time

Tri-State Devices

Tri-State Buffers

 


E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

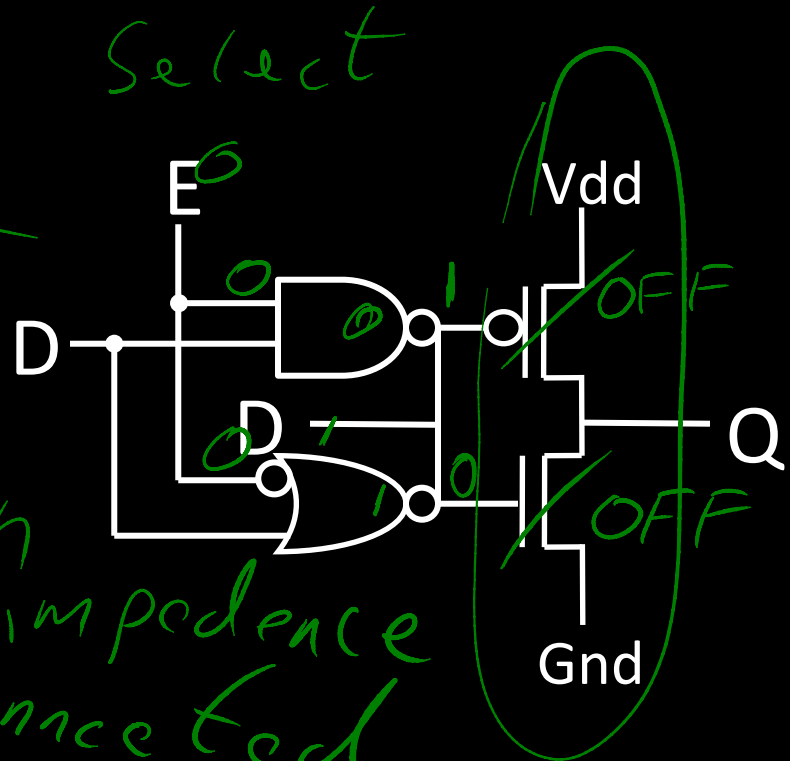


Tri-State Devices


Tri-State Buffers

 

E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

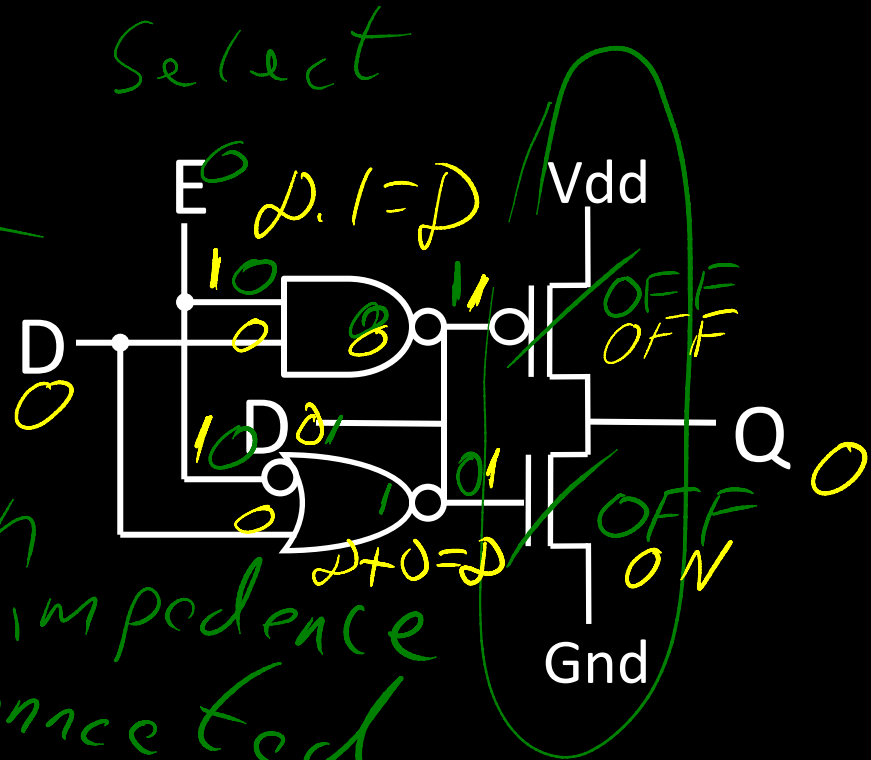

Shared Bus

 

SRAM


Static RAM (SRAM)

- cache

Static?

Cache?

 - Essentially just SR Latches + tri-states buffers



SRAM Chip

12-to 4K decoder
Rows x 1024 wide


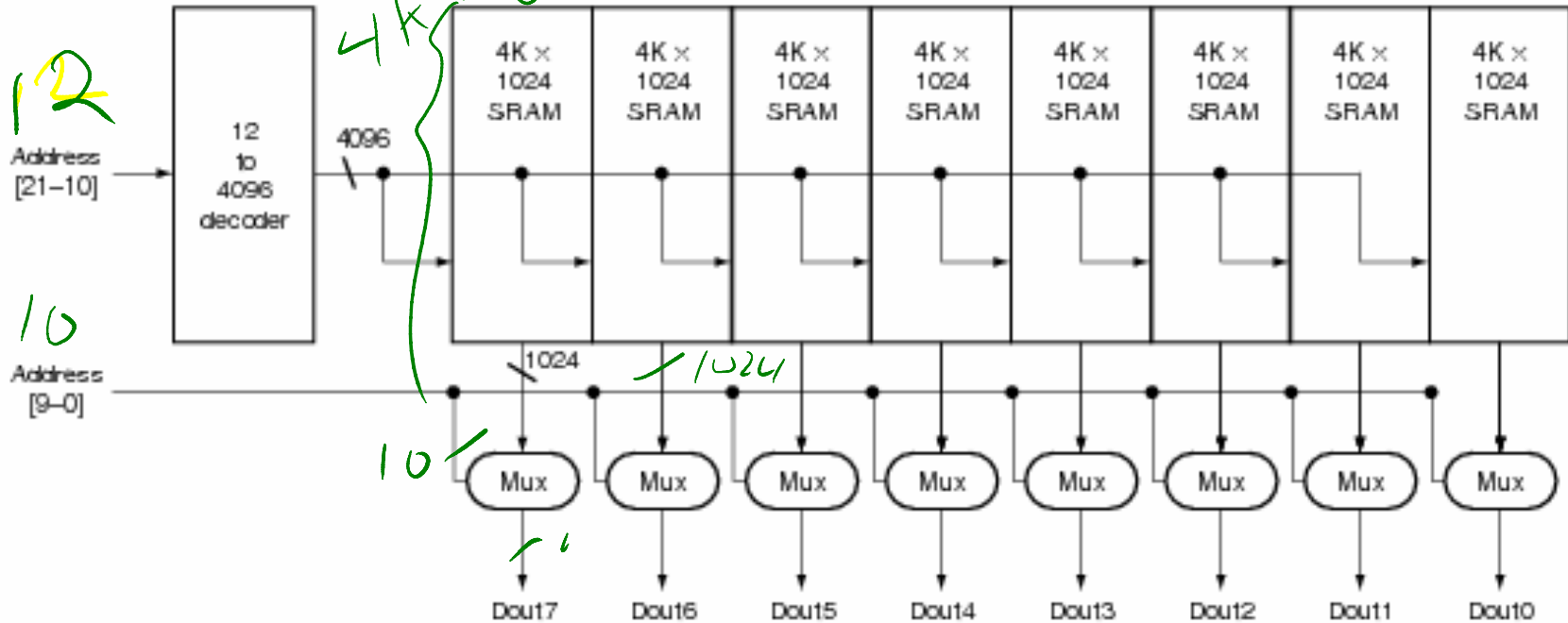



FIGURE B.9.4 Typical organization of a 4M x 8 SRAM as an array of 4K x 1024 arrays. The first decoder generates the addresses for eight 4K x 1024 arrays; then a set of multiplexers is used to select 1 bit from each 1024-bit-wide array. This is a much easier design than a single-level decode that would need either an enormous decoder or a gigantic multiplexor. In practice, a modern SRAM of this size would probably use an even larger number of blocks, each somewhat smaller.

SRAM Chip

 

SRAM Cell

Typical SRAM Cell

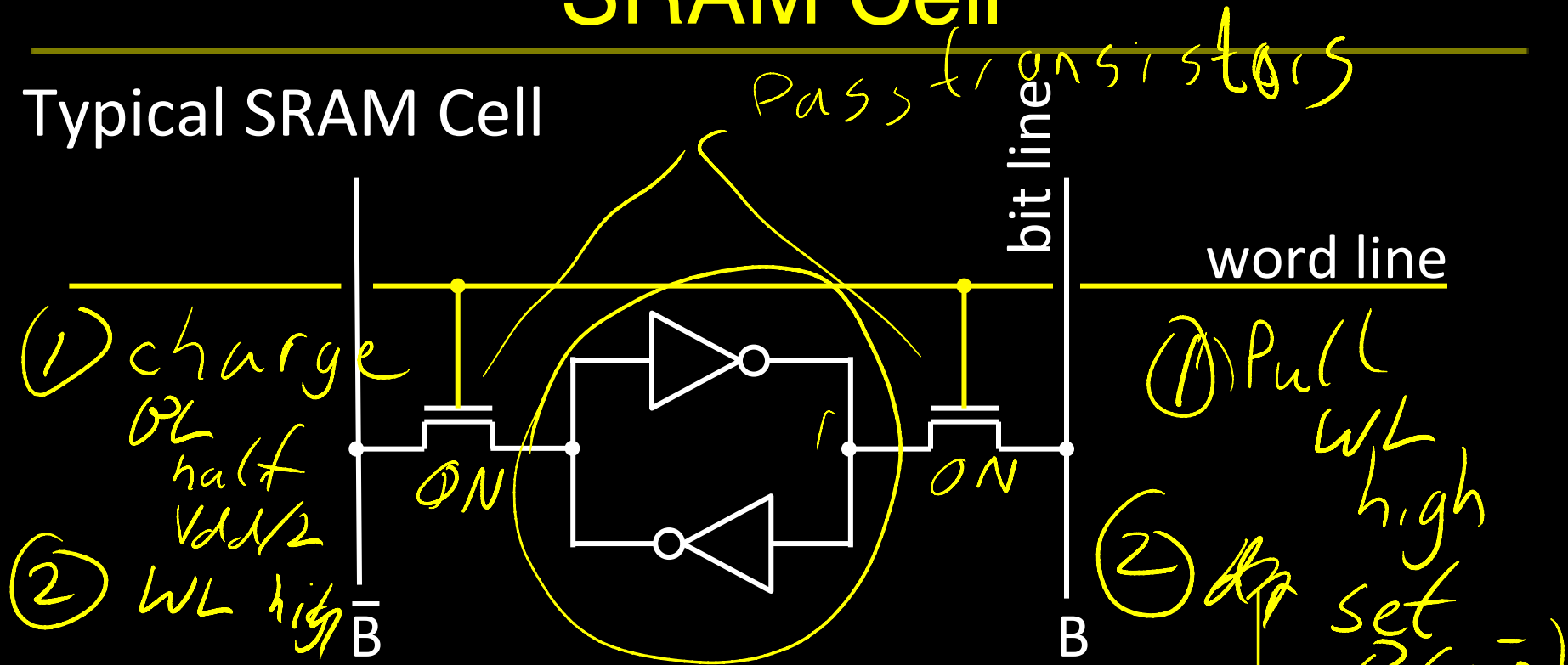

Each cell stores one bit, and requires 4 – 8 transistors (6 is typical)


Read:

- pre-charge B and \bar{B} to $V_{dd}/2$
- pull word line high
- cell pulls B or \bar{B} low, sense amp detects voltage difference

Write:

- pull word line high
- drive B and \bar{B} to flip cell

SRAM Modules and Arrays

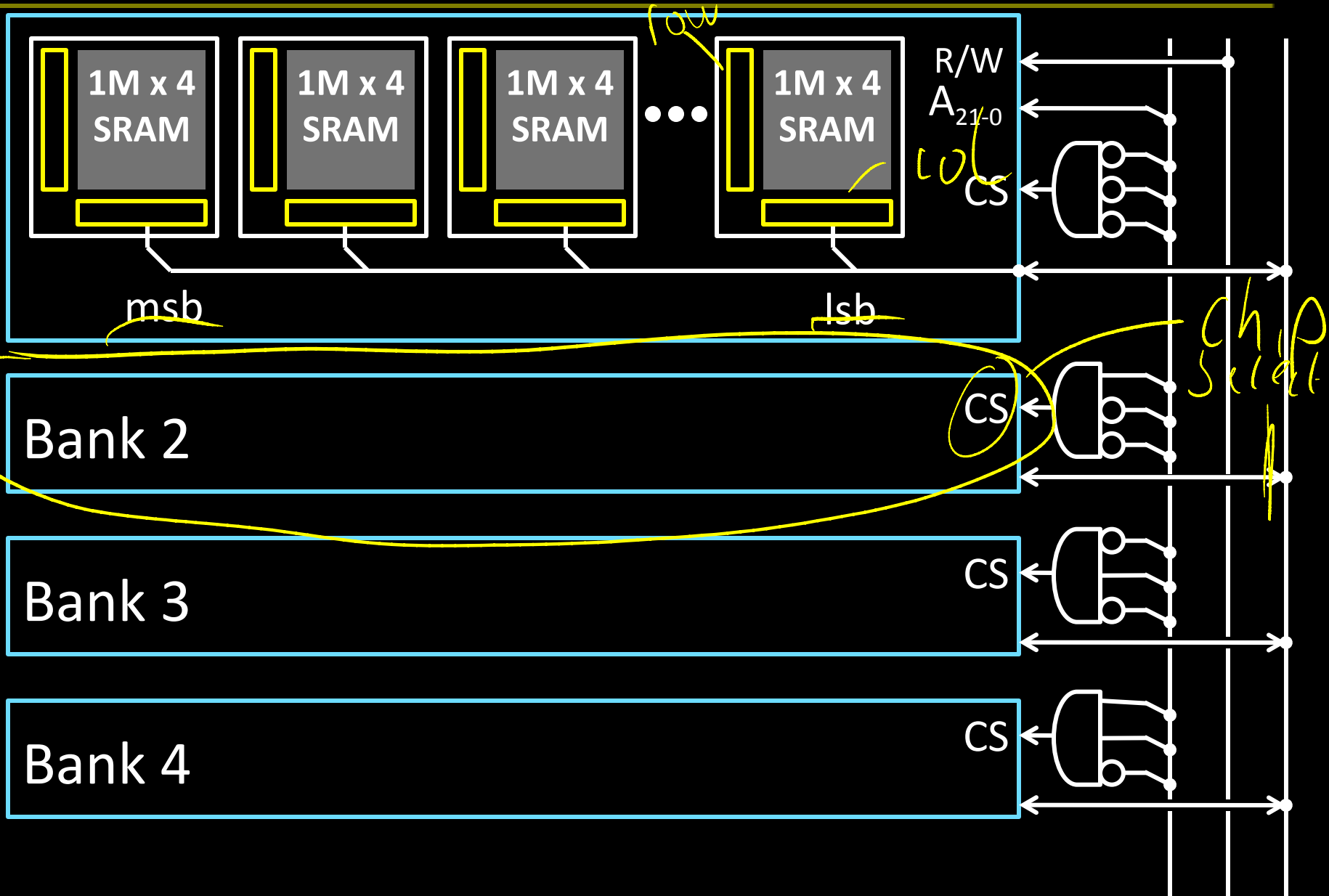

SRAM Summary

SRAM

- A few transistors (~ 6) per cell
- Used for working memory (caches)
- But for even higher density...


Dynamic RAM: DRAM

Dynamic-RAM (DRAM)

- Data values require constant refresh

Refresh ωR

*1 = charge
0 = discharge*

 

bit line

word line

Pass Transistor

*R_d
 $O_L = V_{dd}/2$*

★ 1 transistor

DRAM vs. SRAM

Single transistor vs. many gates

- Denser, cheaper (\$30/1GB vs. \$30/2MB)
- But more complicated, and has analog sensing

Also needs refresh

- Read and write back...
- ...every few milliseconds
- Organized in 2D grid, so can do rows at a time
- Chip can do refresh internally

Hence... slower and energy inefficient

Memory

Register File tradeoffs

- + Very fast (a few gate delays for both read and write)
- + Adding extra ports is straightforward
- Expensive, doesn't scale
- Volatile

Volatile Memory alternatives: SRAM, DRAM, ...

- Slower
- + Cheaper, and scales well
- Volatile

Non-Volatile Memory (NV-RAM): Flash, EEPROM, ...

- + Scales well
- Limited lifetime; degrades after 100000 to 1M writes

Summary

We now have enough building blocks to build machines that can perform non-trivial computational tasks

Register File: Tens of words of working memory

SRAM: Millions of words of working memory

DRAM: Billions of words of working memory

NVRAM: long term storage

(usb fob, solid state disks, BIOS, ...)