
Memory

Hakim Weatherspoon
CS 3410, Spring 2011
Computer Science
Cornell University

See: P&H Appendix C.8, C.9

Announcements

HW1 due today

HW2 available later today

HW2 due in one week and a half

Work alone

Use your resources

- FAQ, class notes, book, Sections, office hours, newsgroup, CSUGLab

Make sure you

- Registered for class, can access CMS, have a Section, and have a project partner
- Check online syllabus/schedule, review slides and lecture notes, Office Hours, early homework and programming assignments

Announcements

Prelims: Evening of Thursday, March 10 and April 28th


Late Policy

- 1) Each person has a total of four “slip days”
- 2) For projects, slip days are deducted from all partners
- 3) 10% deducted per day late after slip days are exhausted

Critical Path

Which operation is the critical path?


- A) AND
- B) OR
- C) ADD/SUB
- D) LT

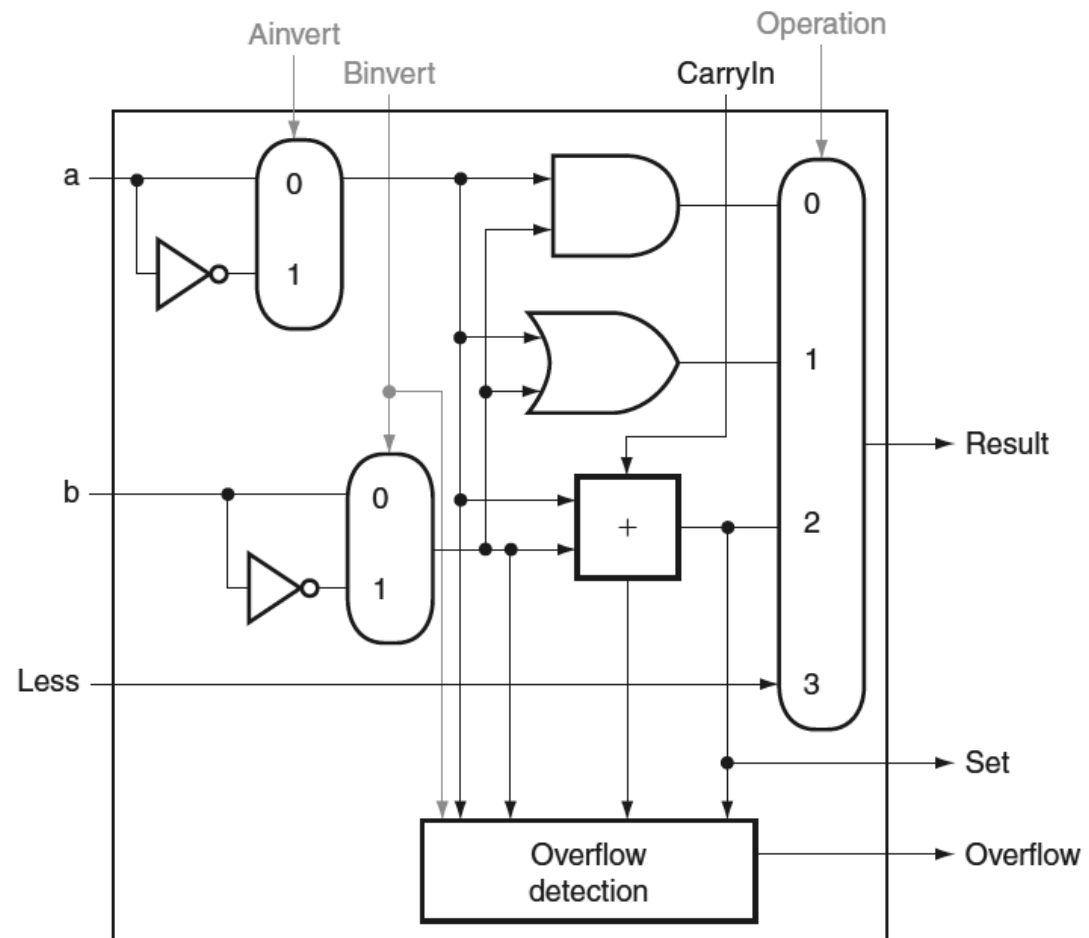

Critical Path

What is the length of the critical path (in gates)?


- A) 3
- B) 5
- C) 7
- D) 9

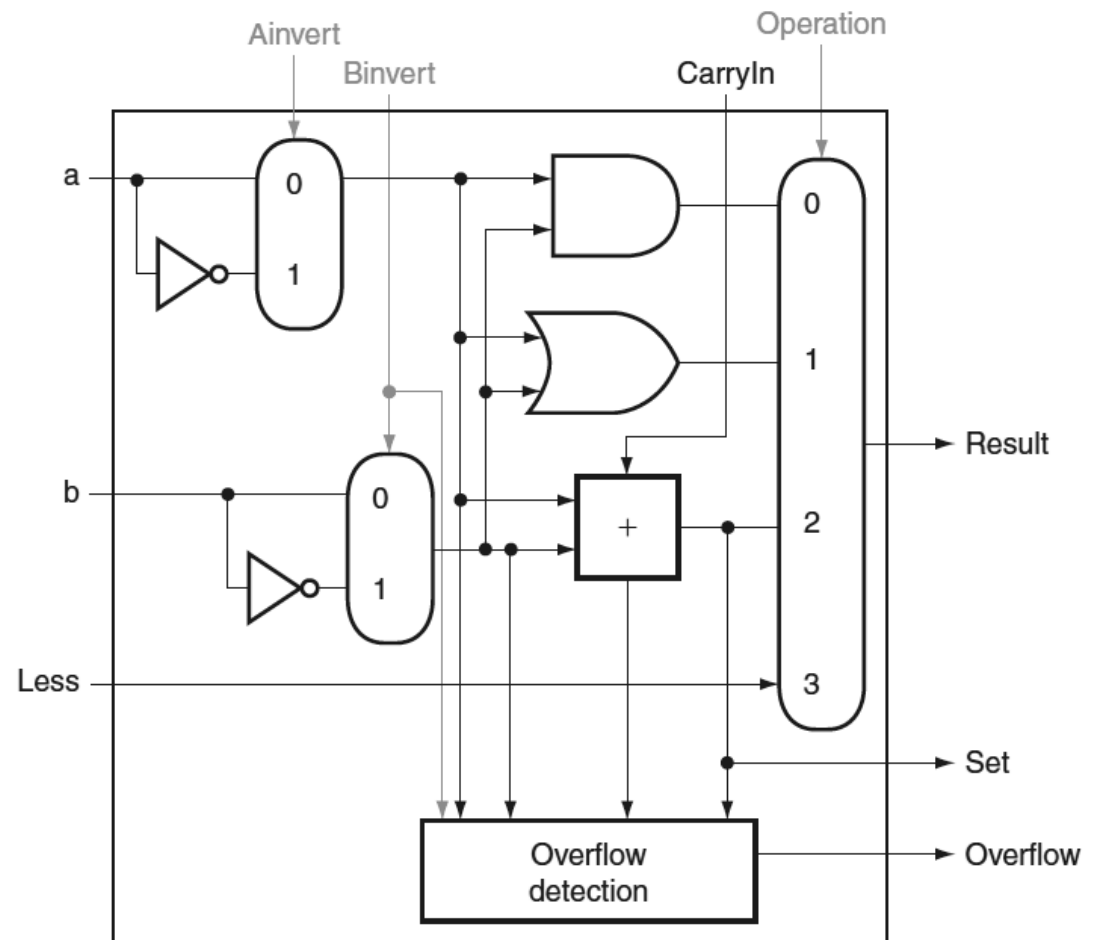



Critical Path

What is the length of the critical path for a 32-bit ALU (in gates)?


- A) 9
- B) 32
- C) 64
- D) 69

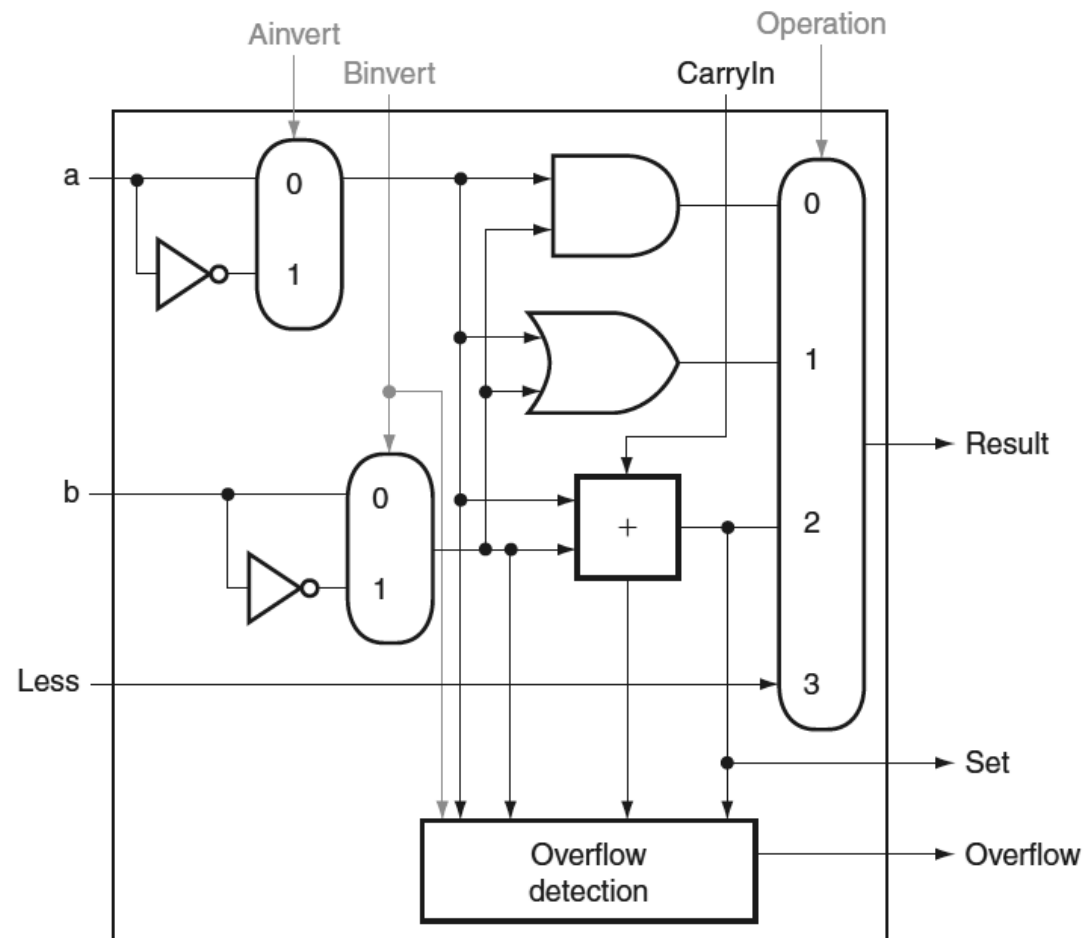

Multiplexor

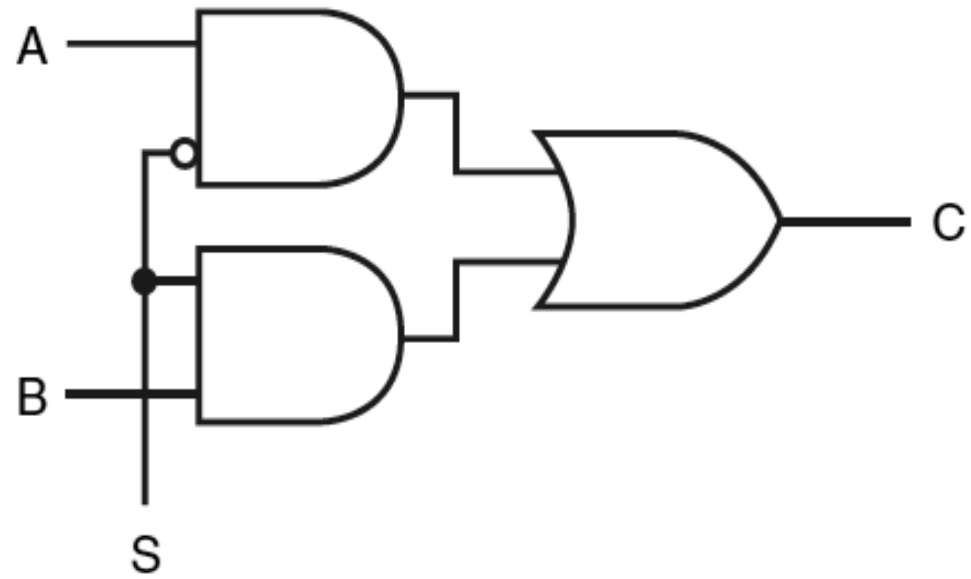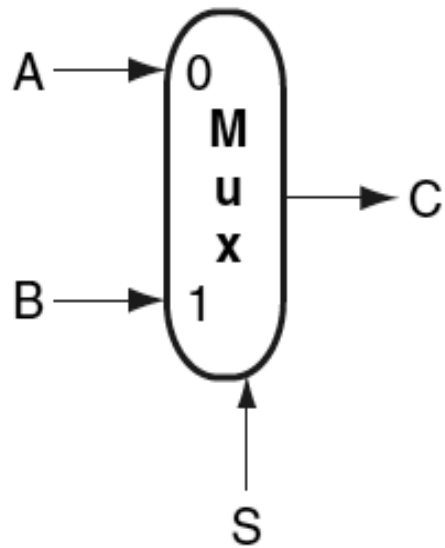

Multiplexor

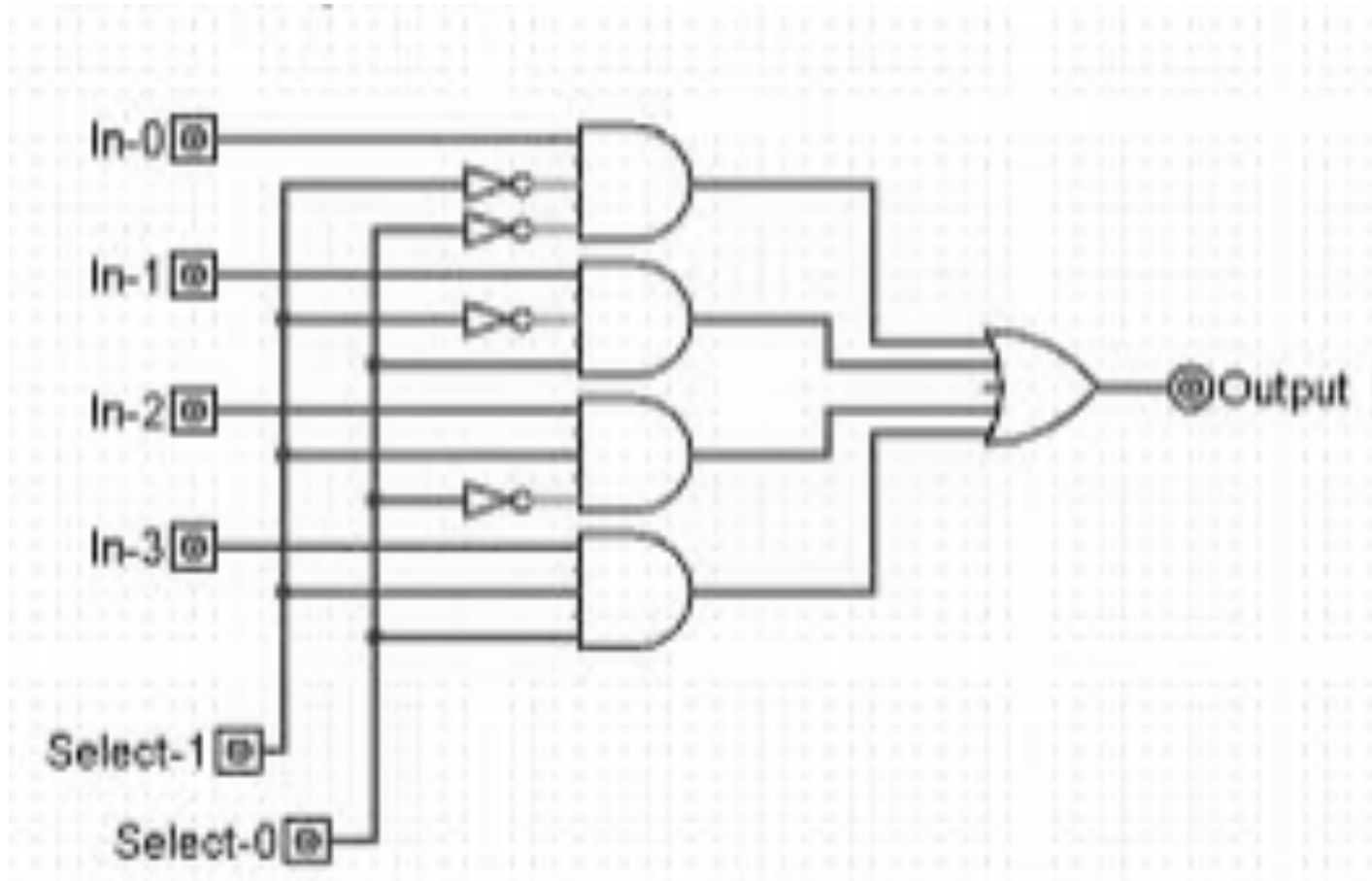

Goals for today

Review


- SR Latches, D Latches, D Flip Flips, and Registers

Memory

- Register Files
- Tri-state devices
- SRAM (Static RAM—random access memory)
- DRAM (Dynamic RAM)

Bistable Devices


- Stable and unstable equilibria?

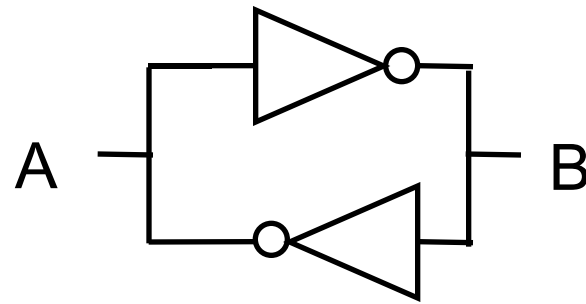

A Simple Device



Bistable Devices

- Stable and unstable equilibria?

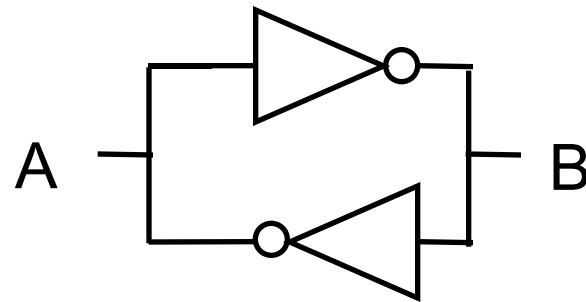


A Simple Device

- In stable state, $\bar{A} = B$

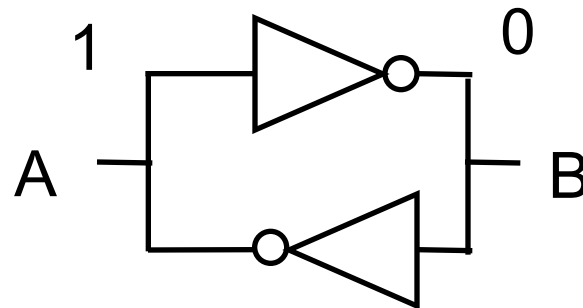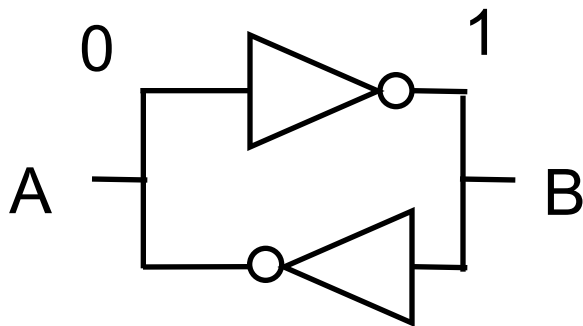

- How do we change the state?

SR Latch

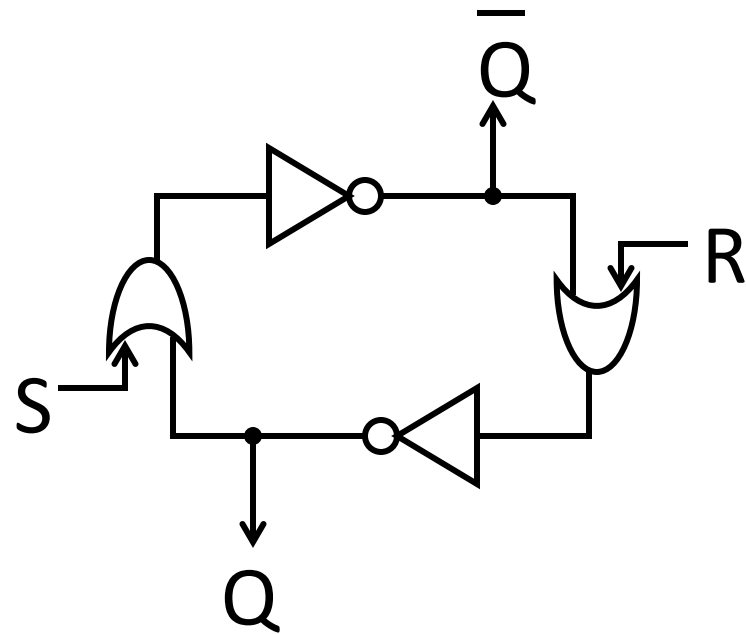


SR Latch

Set-Reset (SR) Latch

Stores a value Q and its complement \bar{Q}


S	R	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		

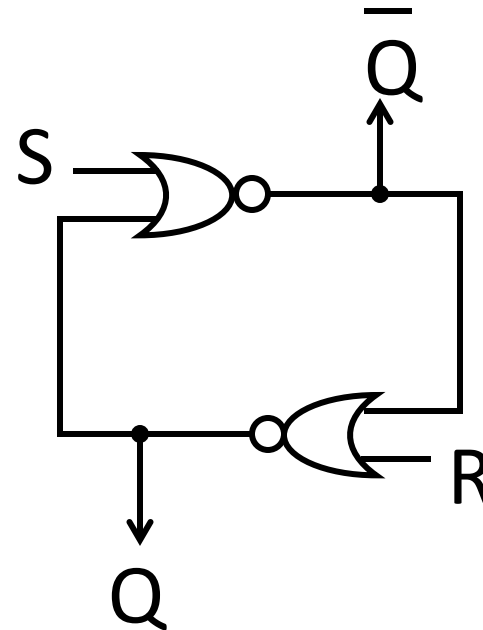


SR Latch

Set-Reset (SR) Latch

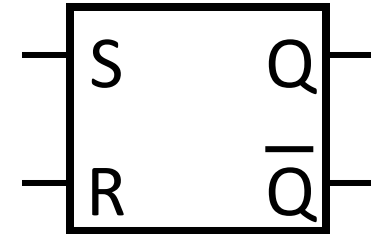
Stores a value Q and its complement \bar{Q}



S	R	Q	\bar{Q}
0	0	Q	Q
0	1	0	1
1	0	1	0
1	1	forbidden	

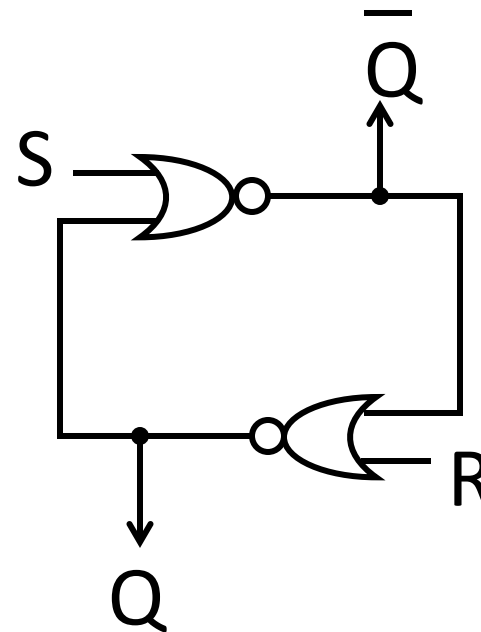


Unclocked D Latch

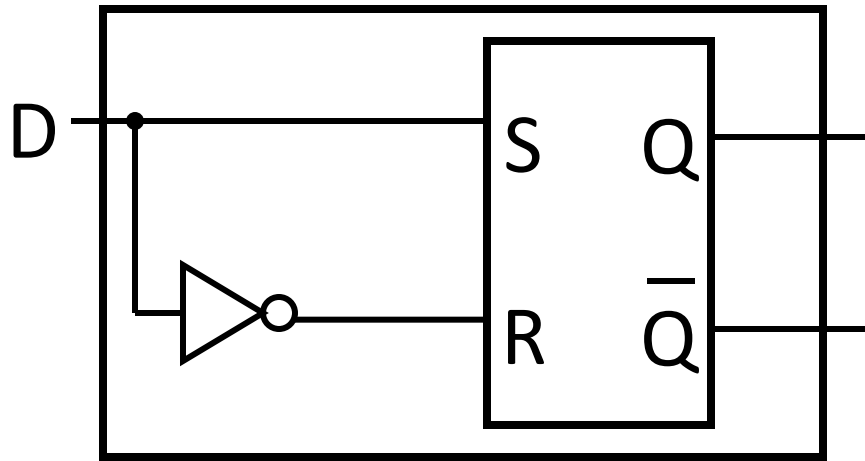

Data (D) Latch

D	Q	\bar{Q}
0		
1		

Unclocked D Latch

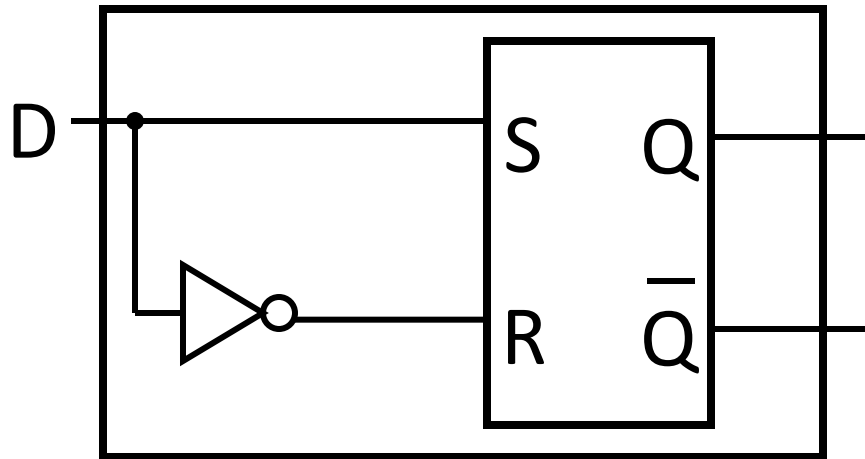

Data (D) Latch

D	Q	\bar{Q}
0	0	1
1	1	0

Data Latch


- Easier to use than an SR latch
- No possibility of entering an undefined state

When D changes, Q changes

– ... immediately (after a delay of 2 Ors and 2 NOTs)

Need to control when the output changes

D Latch with Clock

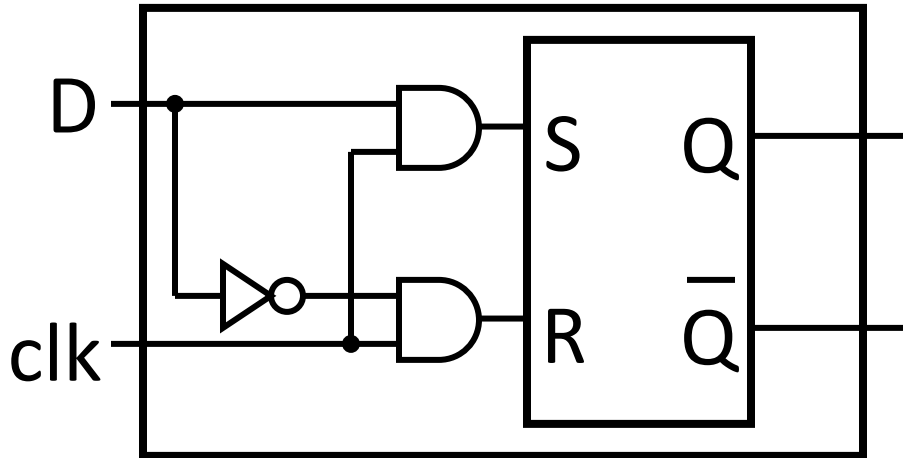

D	Q	\bar{Q}
0	0	1
1	1	0

Level Sensitive D Latch


Clock high:

set/reset (according to D)

Clock low:

keep state (ignore D)

D Latch with Clock

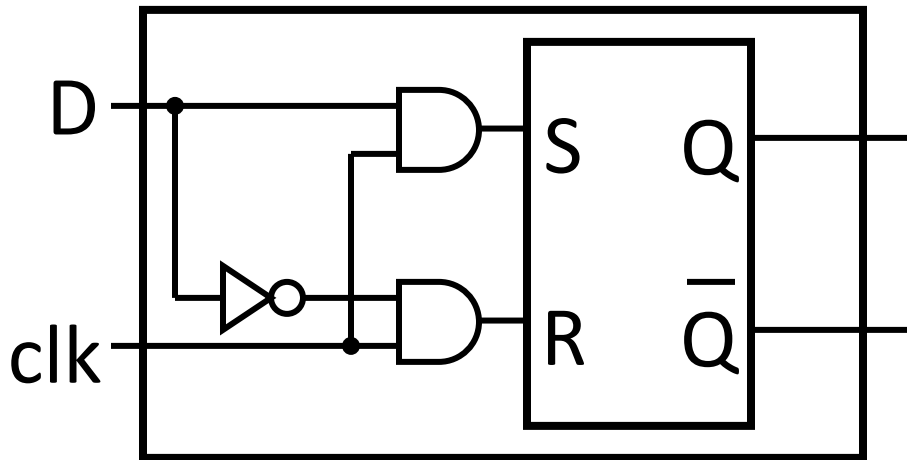


D	Q	\bar{Q}
0	0	1
1	1	0


S	R	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	0	1
1	0	1	0
1	1	forbidden	

clk	D	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	Q	\bar{Q}
1	0	0	1
1	1	1	0

D Latch with Clock

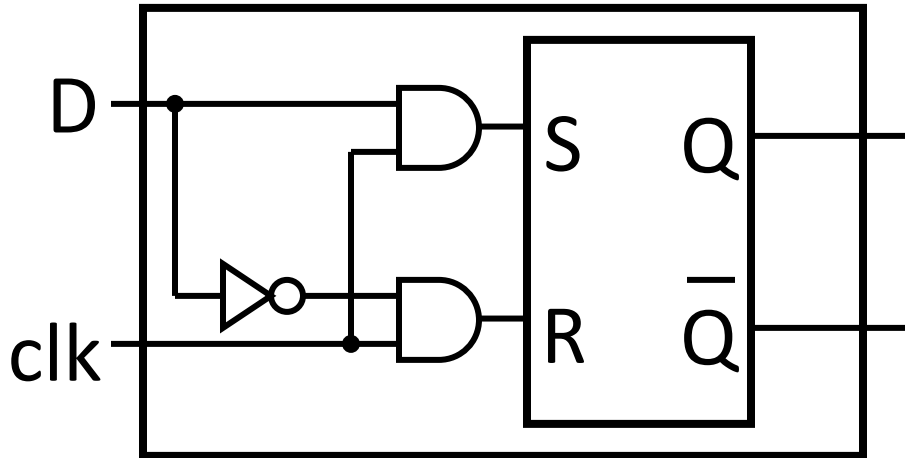

D	Q	\bar{Q}
0	0	1
1	1	0


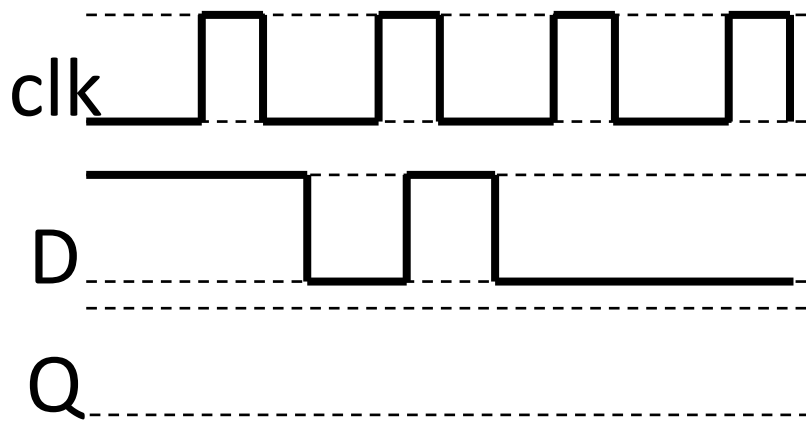


clk	D	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	Q	\bar{Q}
1	0	0	1
1	1	1	0


Edge-Triggered D Flip-Flop

D Flip-Flop

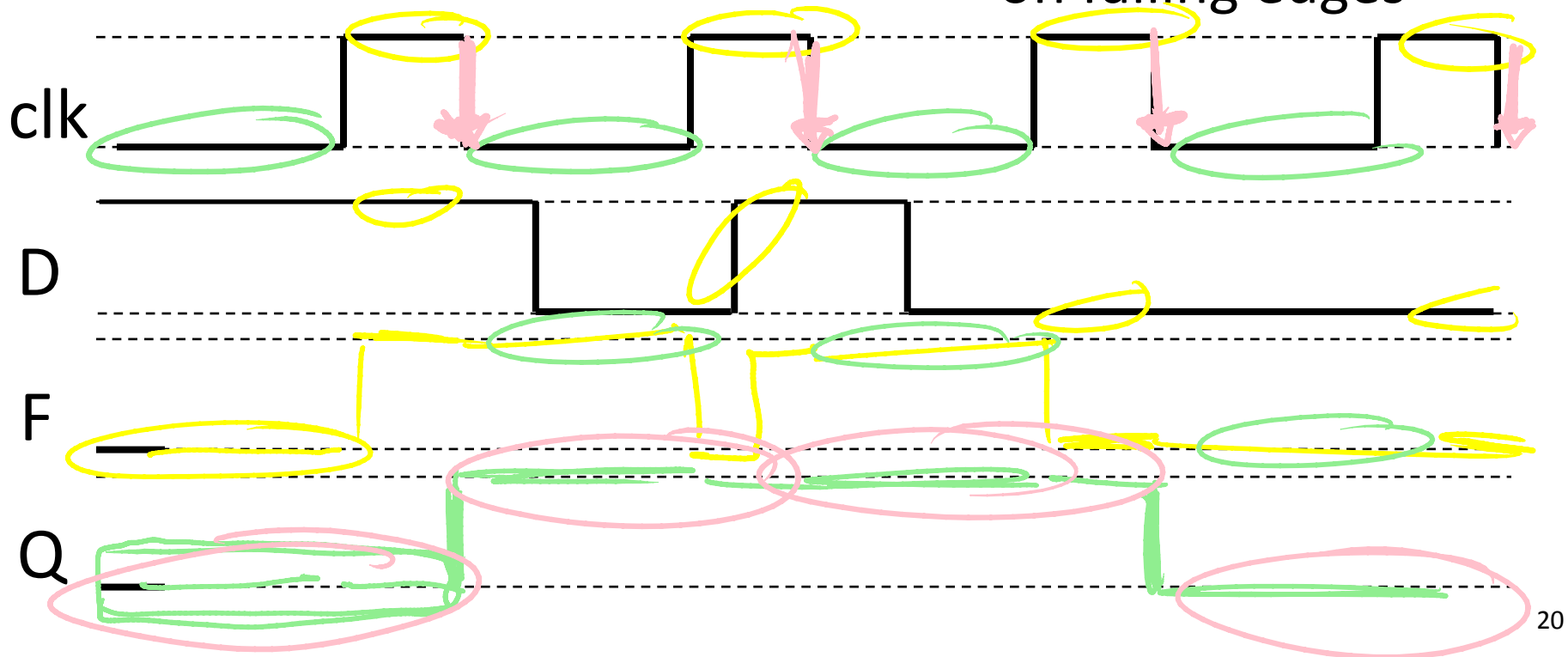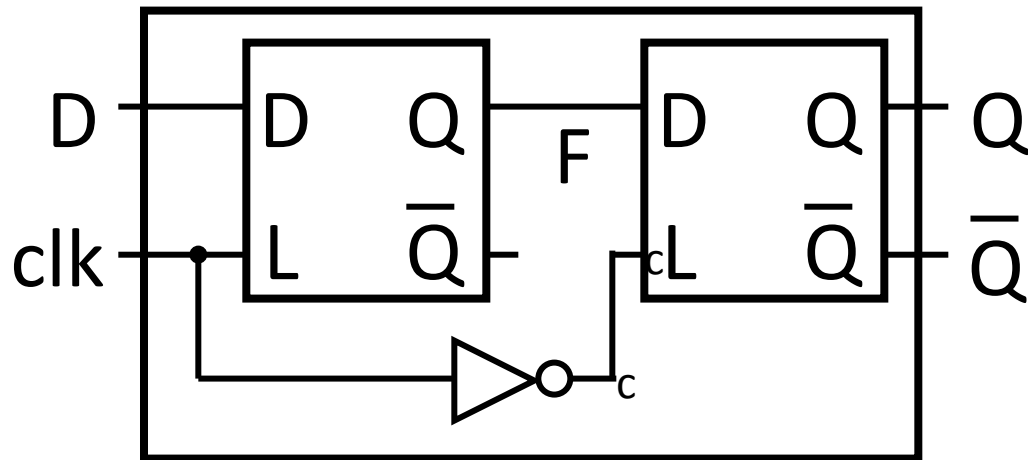- Edge-Triggered
- Data is captured when clock is high
- Outputs change only on falling edges




Registers

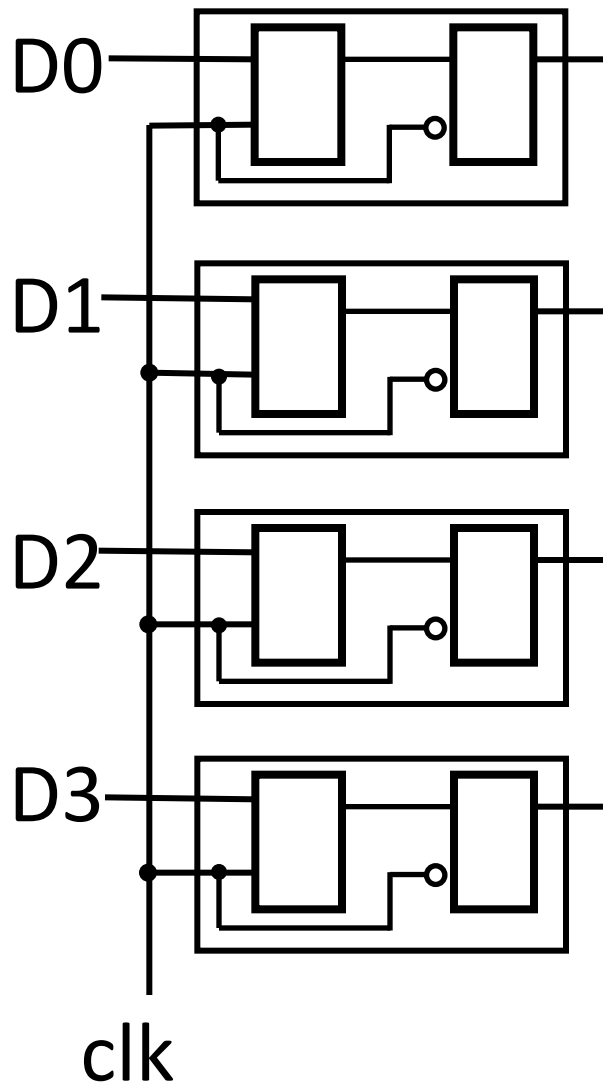


Register

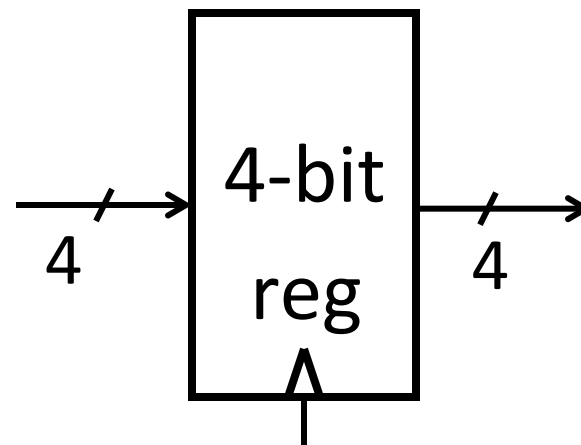- D flip-flops in parallel
- shared clock
- extra clocked inputs: write_enable, reset, ...



Voting Machine

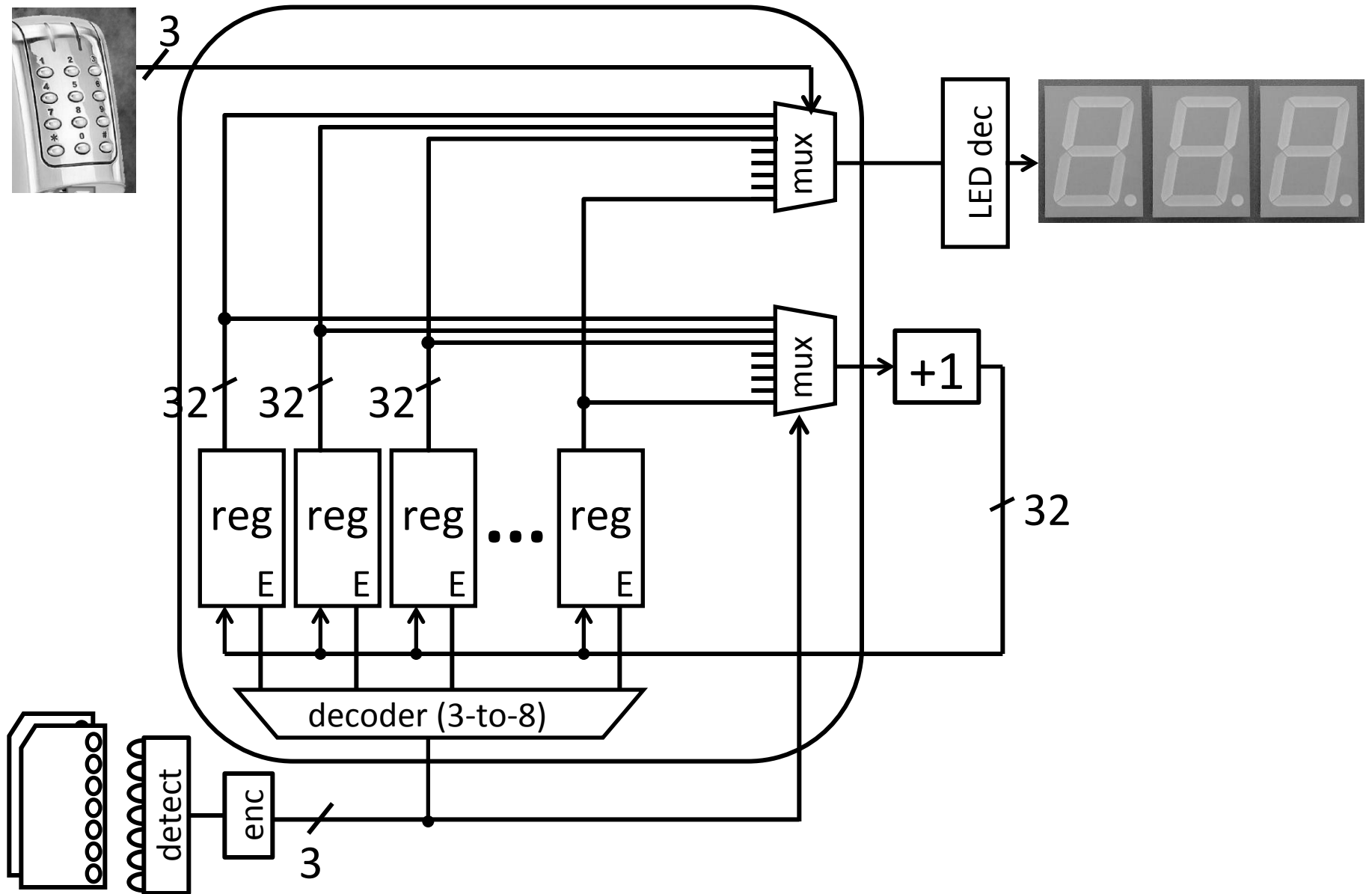

Goals for today

Review

- SR Latches, D Latches, D Flip Flips, and Registers


Memory

- Register Files
- Tri-state devices
- SRAM (Static RAM—random access memory)
- DRAM (Dynamic RAM)

Register File

Register File

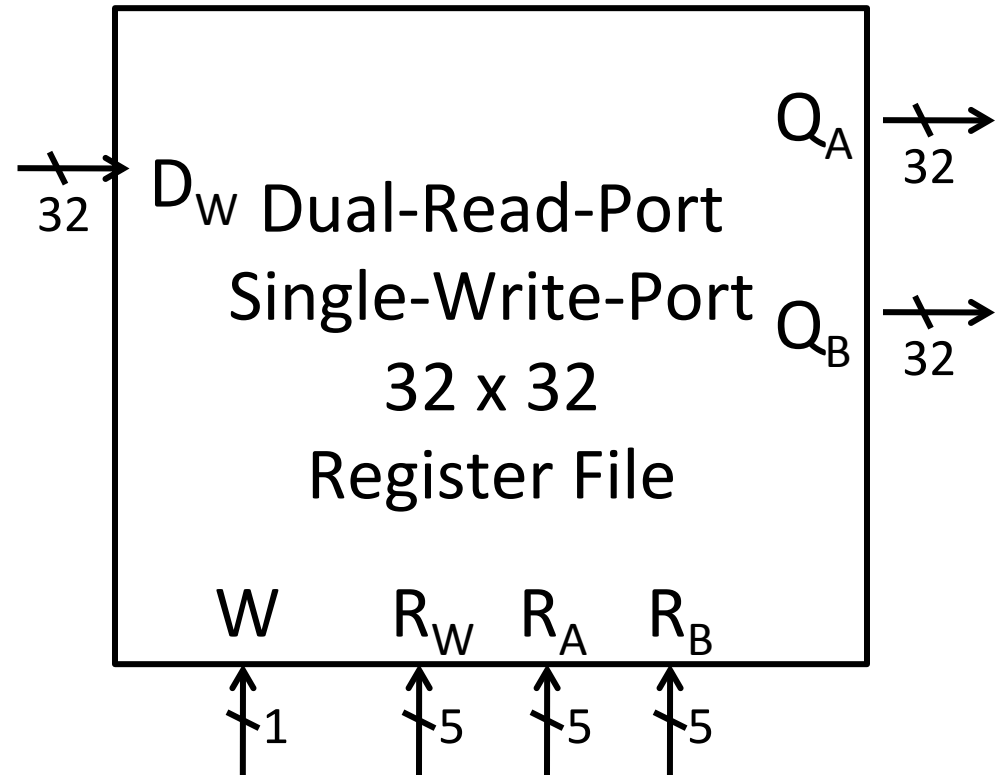- N read/write registers
- Indexed by register number



Implementation:

- D flip flops to store bits
- Decoder for each write port
- Mux for each read port


Register File

Register File

- N read/write registers
- Indexed by register number

Implementation:

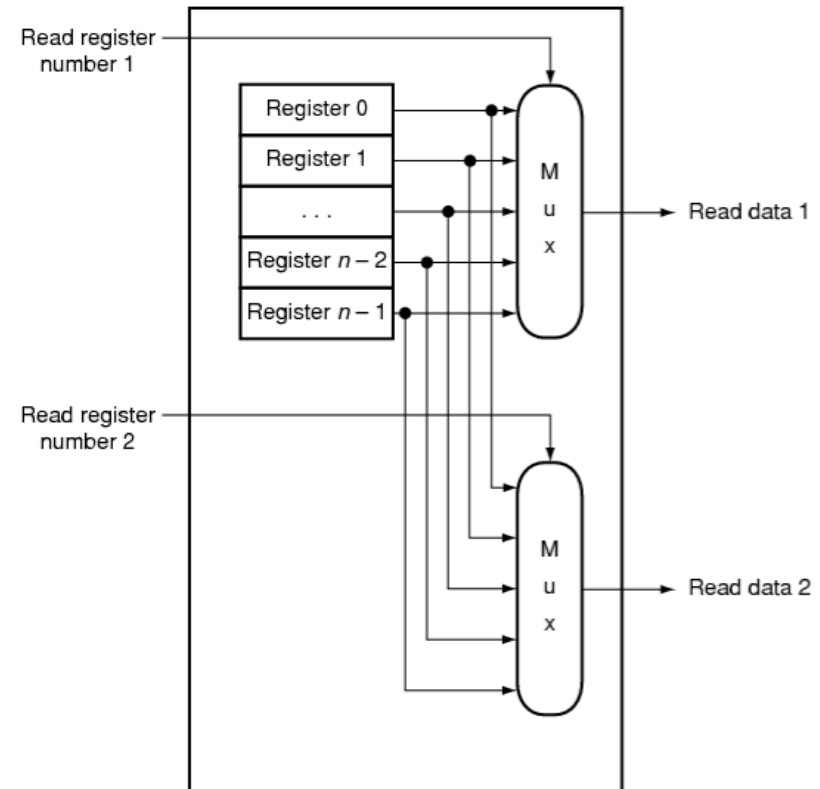- D flip flops to store bits
- Decoder for each write port
- Mux for each read port




Register File

Register File

- N read/write registers
- Indexed by register number

Implementation:

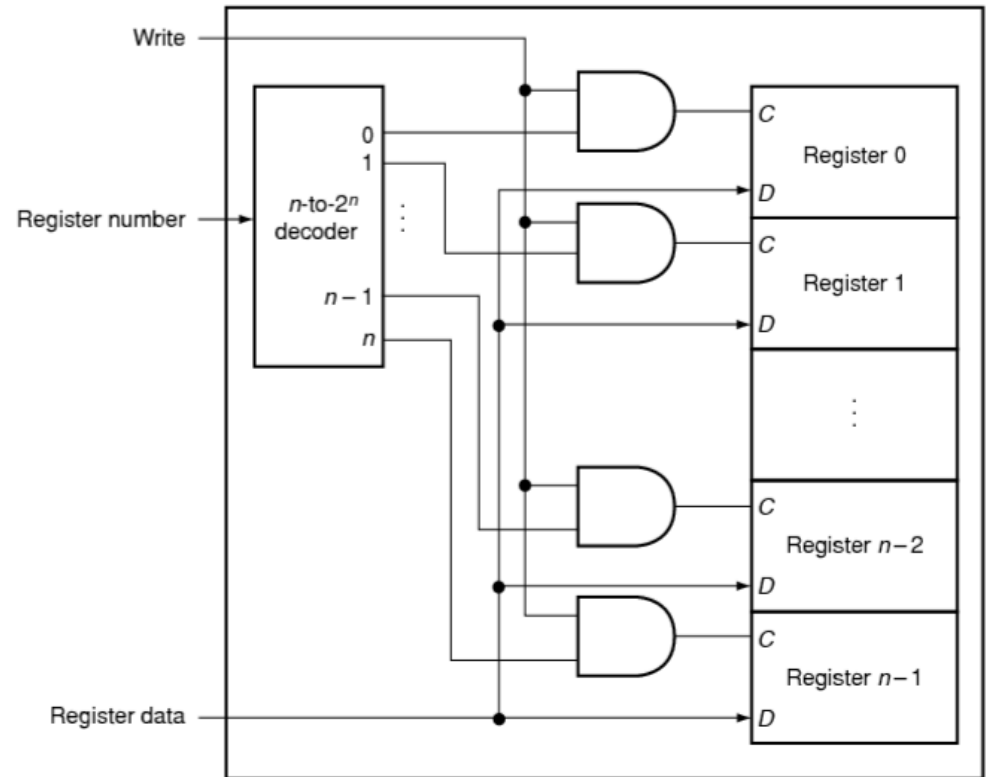- D flip flops to store bits
- Decoder for each write port
- Mux for each read port



Tradeoffs

Register File tradeoffs

- + Very fast (a few gate delays for both read and write)
- + Adding extra ports is straightforward
- Doesn't scale


Building Large Memories

Need a shared bus (or shared bit line)


- Many FFs/outputs/etc. connected to single wire
- Only one output *drives* the bus at a time

Tri-State Devices


Tri-State Buffers

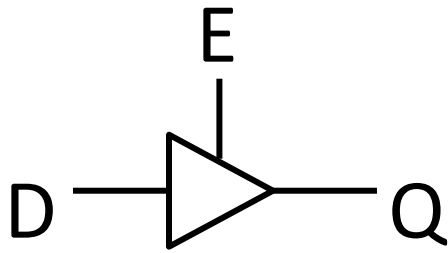

E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

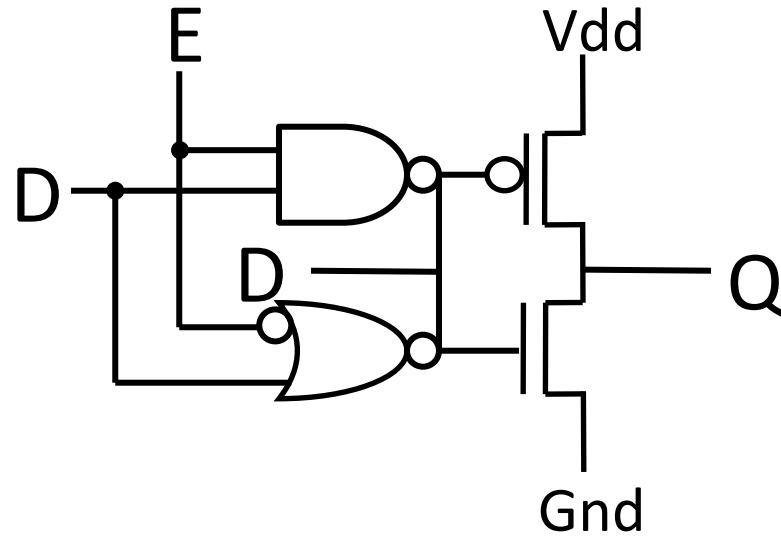


Shared Bus

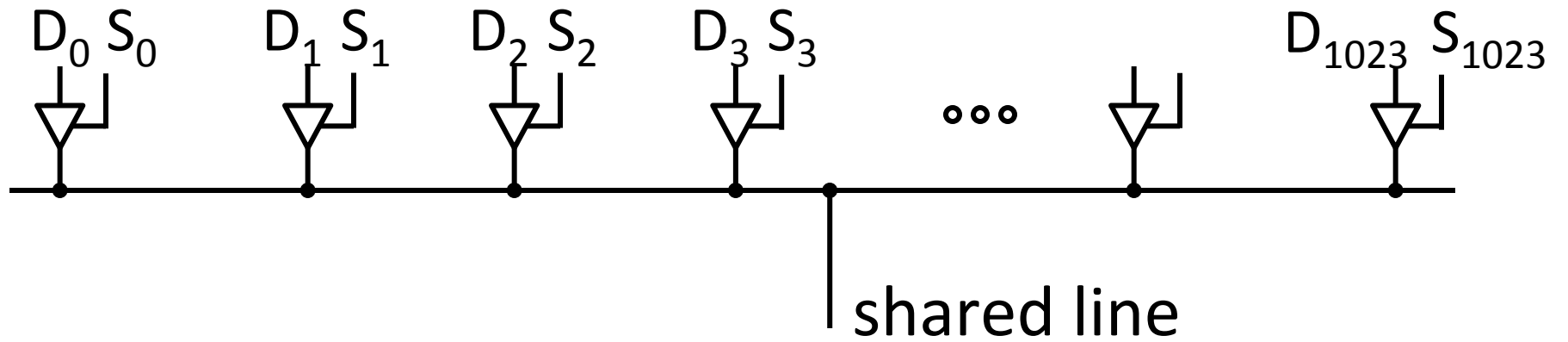

SRAM

Static RAM (SRAM)

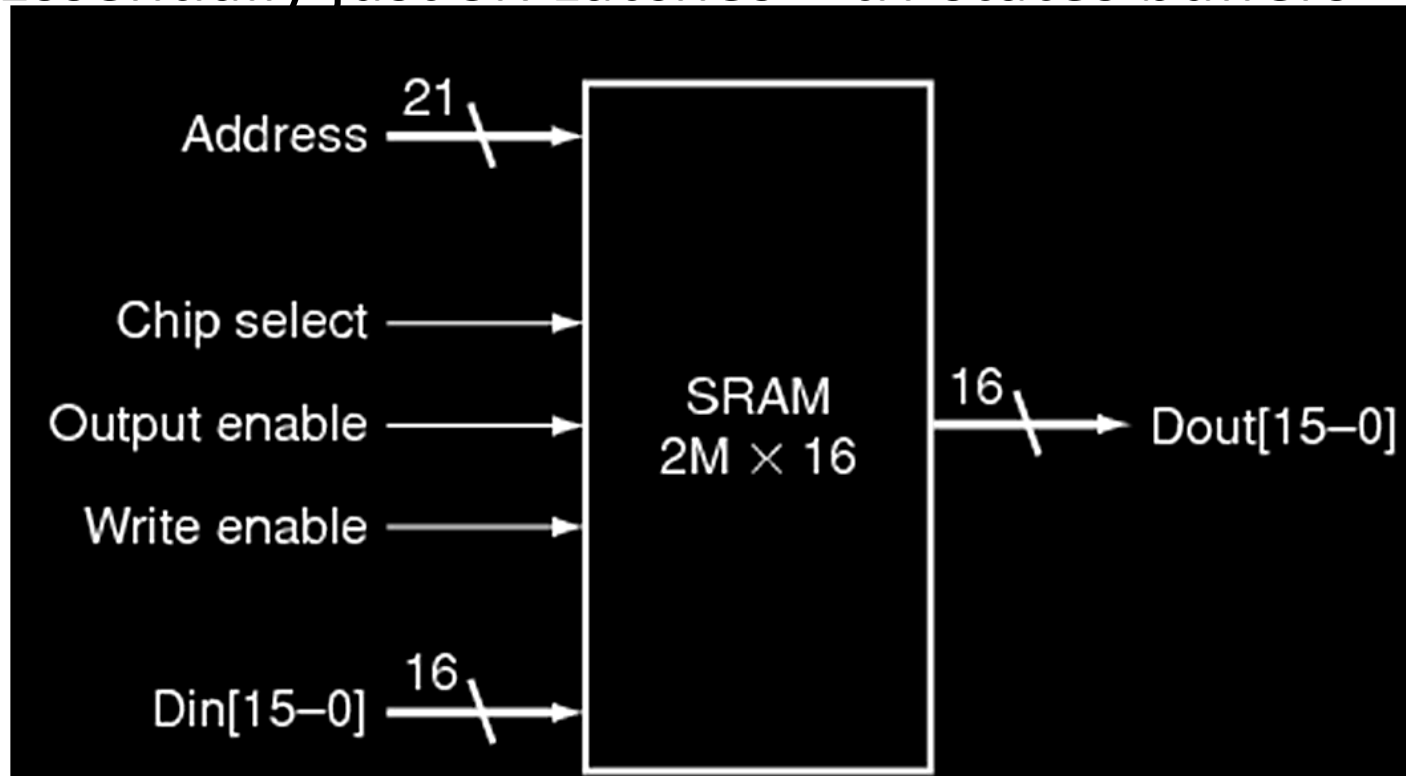- Essentially just SR Latches + tri-states buffers



SRAM Chip


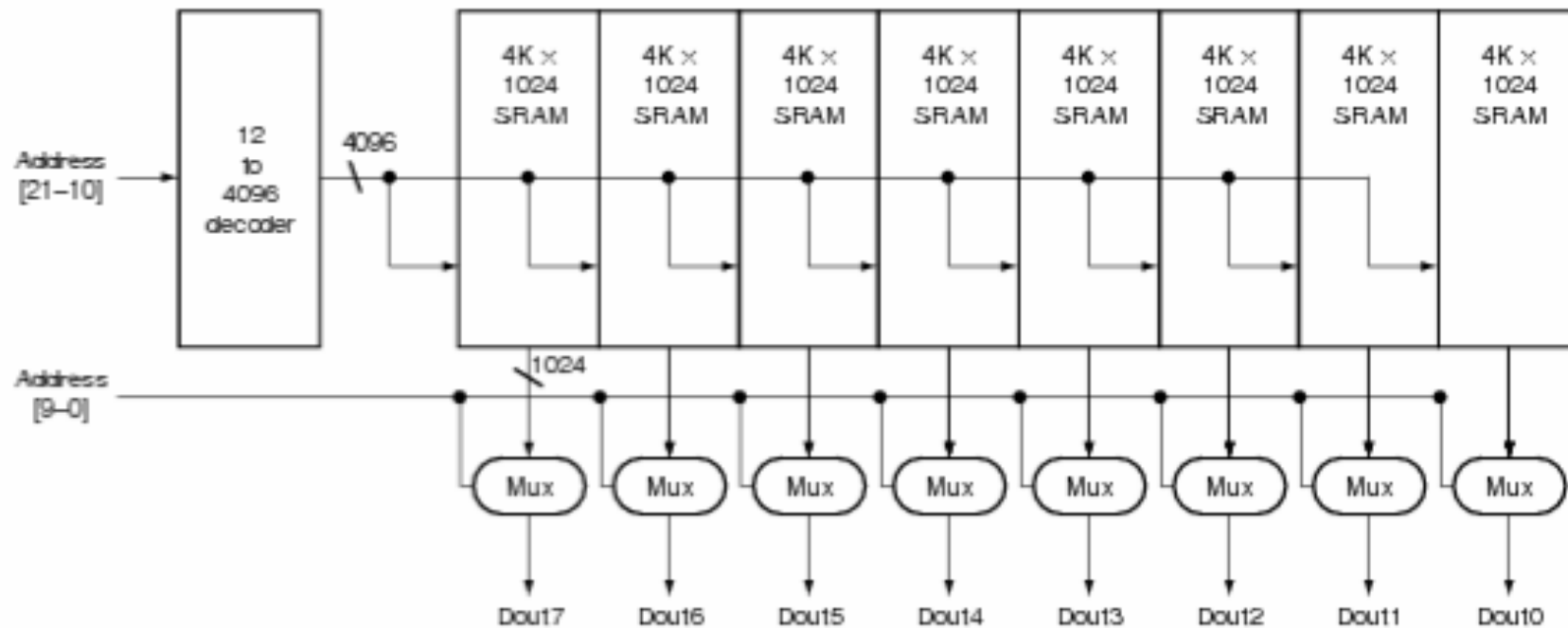



FIGURE B.9.4 Typical organization of a 4M x 8 SRAM as an array of 4K x 1024 arrays. The first decoder generates the addresses for eight 4K x 1024 arrays; then a set of multiplexers is used to select 1 bit from each 1024-bit-wide array. This is a much easier design than a single-level decode that would need either an enormous decoder or a gigantic multiplexer. In practice, a modern SRAM of this size would probably use an even larger number of blocks, each somewhat smaller.

SRAM Chip

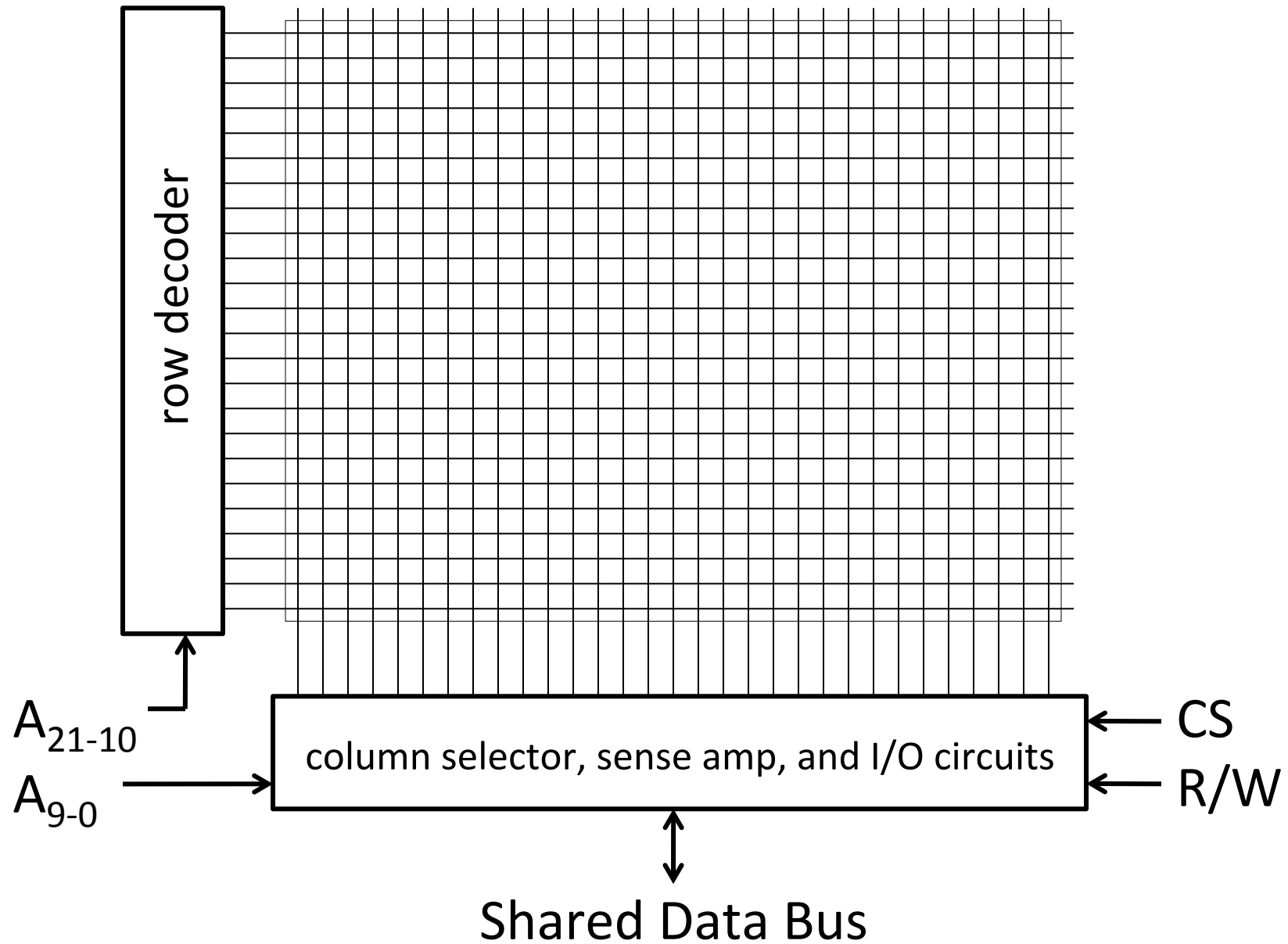

SRAM Cell

Typical SRAM Cell

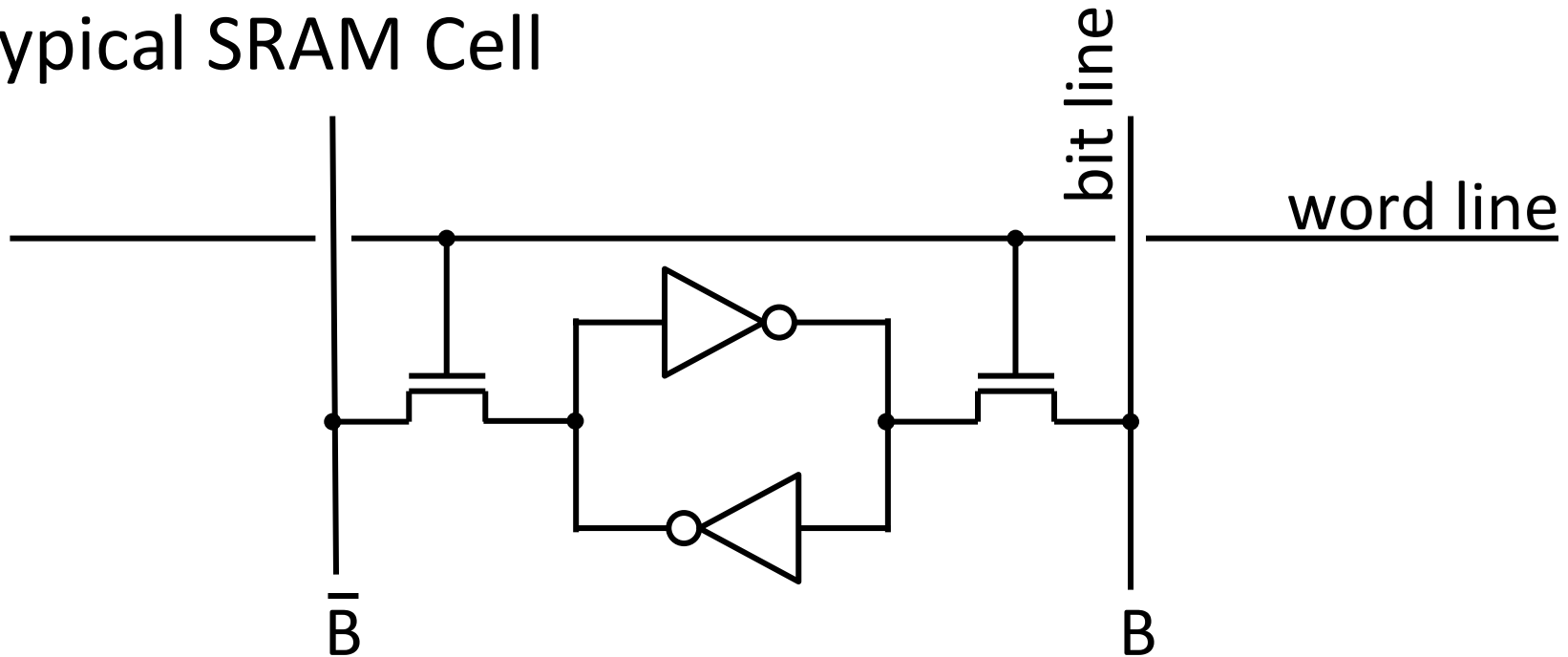

Each cell stores one bit, and requires 4 – 8 transistors (6 is typical)


Read:

- pre-charge B and \bar{B} to $V_{dd}/2$
- pull word line high
- cell pulls B or \bar{B} low, sense amp detects voltage difference

Write:

- pull word line high
- drive B and \bar{B} to flip cell

SRAM Modules and Arrays

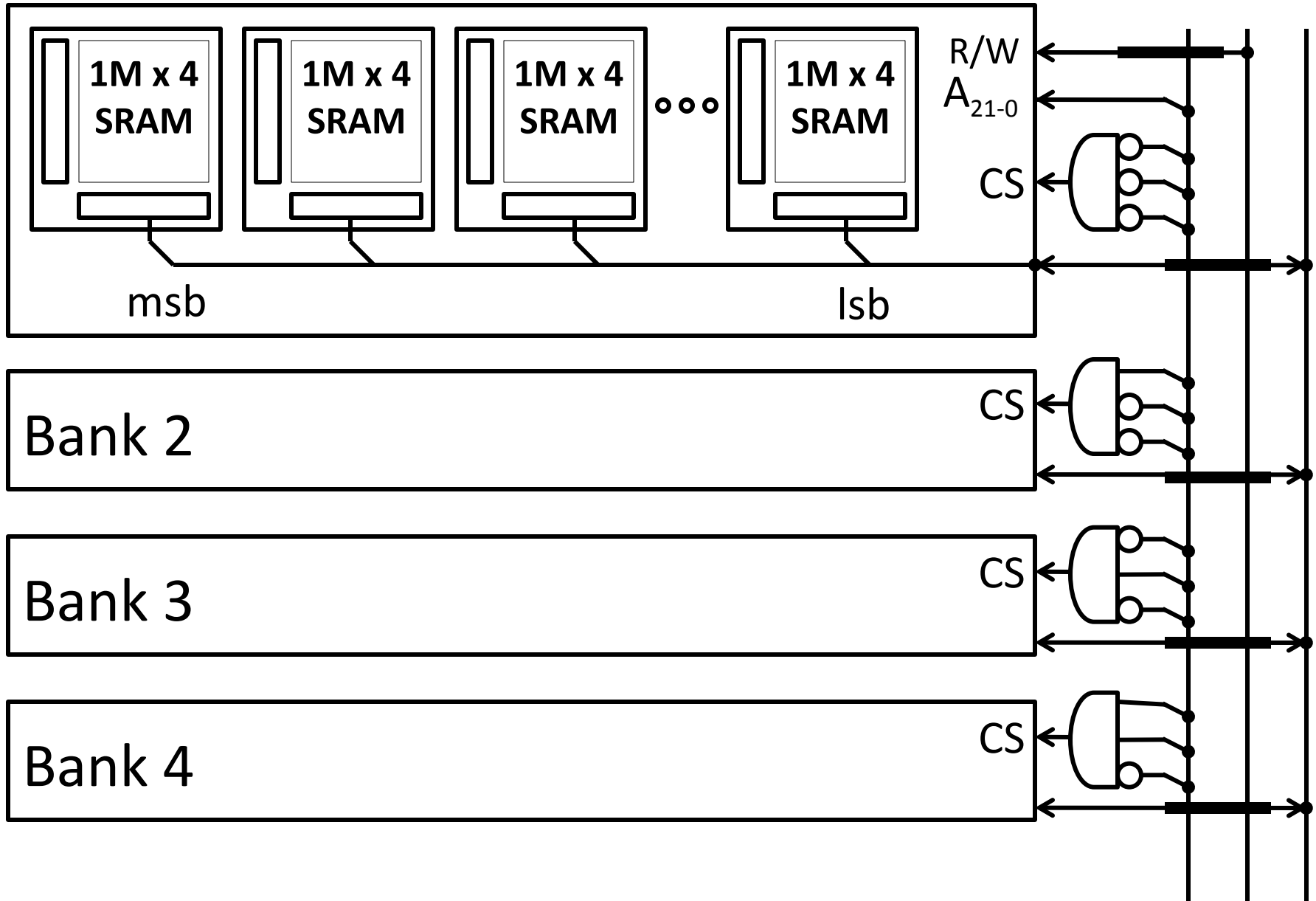

SRAM Summary


SRAM

- A few transistors (~ 6) per cell
- Used for working memory (caches)
- But for even higher density...

Dynamic RAM: DRAM

Dynamic-RAM (DRAM)

- Data values require constant refresh

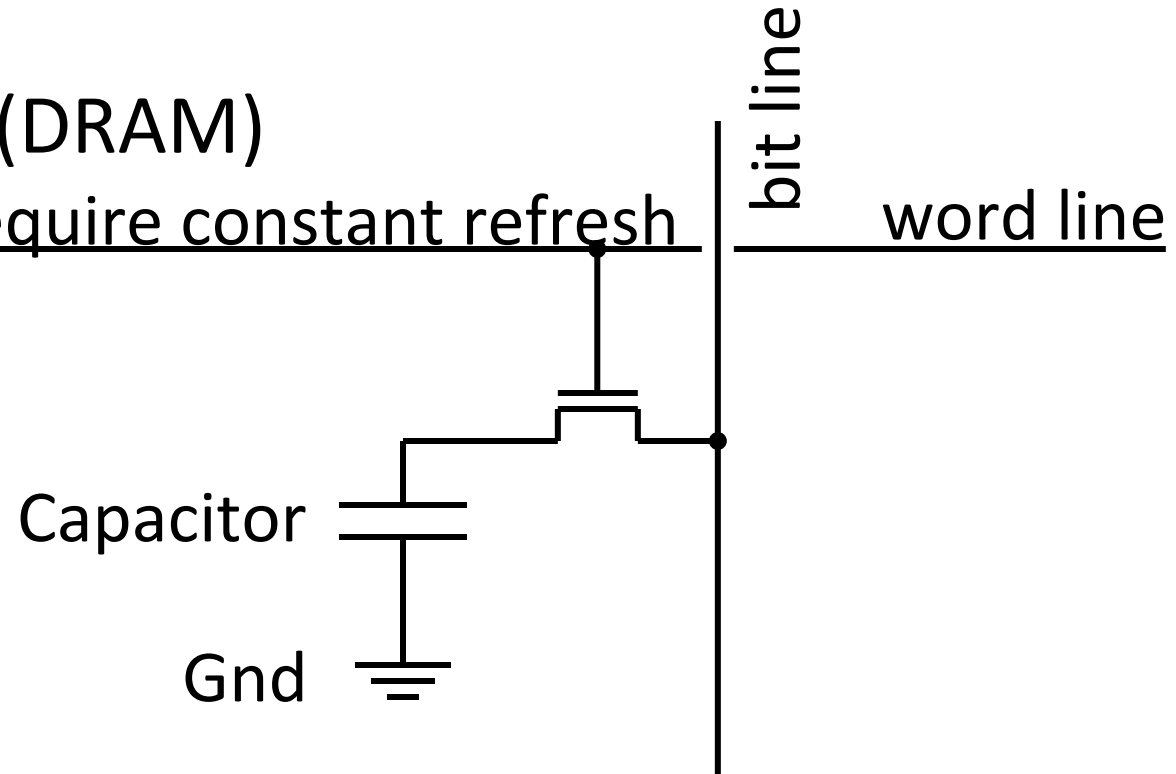

DRAM vs. SRAM

Single transistor vs. many gates

- Denser, cheaper (\$30/1GB vs. \$30/2MB)
- But more complicated, and has analog sensing

Also needs refresh

- Read and write back...
- ...every few milliseconds
- Organized in 2D grid, so can do rows at a time
- Chip can do refresh internally

Hence... slower and energy inefficient

Memory

Register File tradeoffs

- + Very fast (a few gate delays for both read and write)
- + Adding extra ports is straightforward
- Expensive, doesn't scale
- Volatile

Volatile Memory alternatives: SRAM, DRAM, ...

- Slower
- + Cheaper, and scales well
- Volatile

Non-Volatile Memory (NV-RAM): Flash, EEPROM, ...

- + Scales well
- Limited lifetime; degrades after 100000 to 1M writes

Summary

We now have enough building blocks to build machines that can perform non-trivial computational tasks

Register File: Tens of words of working memory

SRAM: Millions of words of working memory

DRAM: Billions of words of working memory

NVRAM: long term storage

(usb fob, solid state disks, BIOS, ...)