

---

# Memory

**Hakim Weatherspoon**  
**CS 3410, Spring 2011**  
Computer Science  
Cornell University

See: P&H Appendix C.8, C.9

# Announcements

---

HW1 due today

*HW2 available later today*

HW2 due in one week and a half

Work **alone**

Use your resources

- FAQ, class notes, book, Sections, office hours, newsgroup, CSUGLab

Make sure you

- Registered for class, can access CMS, have a Section, and have a project partner
- Check online syllabus/schedule, review slides and lecture notes, Office Hours, early homework and programming assignments

# Announcements

---

Prelims: Evening of Thursday, March 10 and April 28<sup>th</sup>


## Late Policy

- 1) Each person has a total of **four “slip days”**
- 2) For projects, slip days are deducted from all partners
- 3) 10% deducted per day late after slip days are exhausted

# Critical Path

Which operation is the critical path?


- A) AND
- B) OR
- C) ADD/SUB
- D) LT

 

# Critical Path

What is the length of the critical path (in gates)?


- A) 3
- B) 5
- C) 7
- D) 9

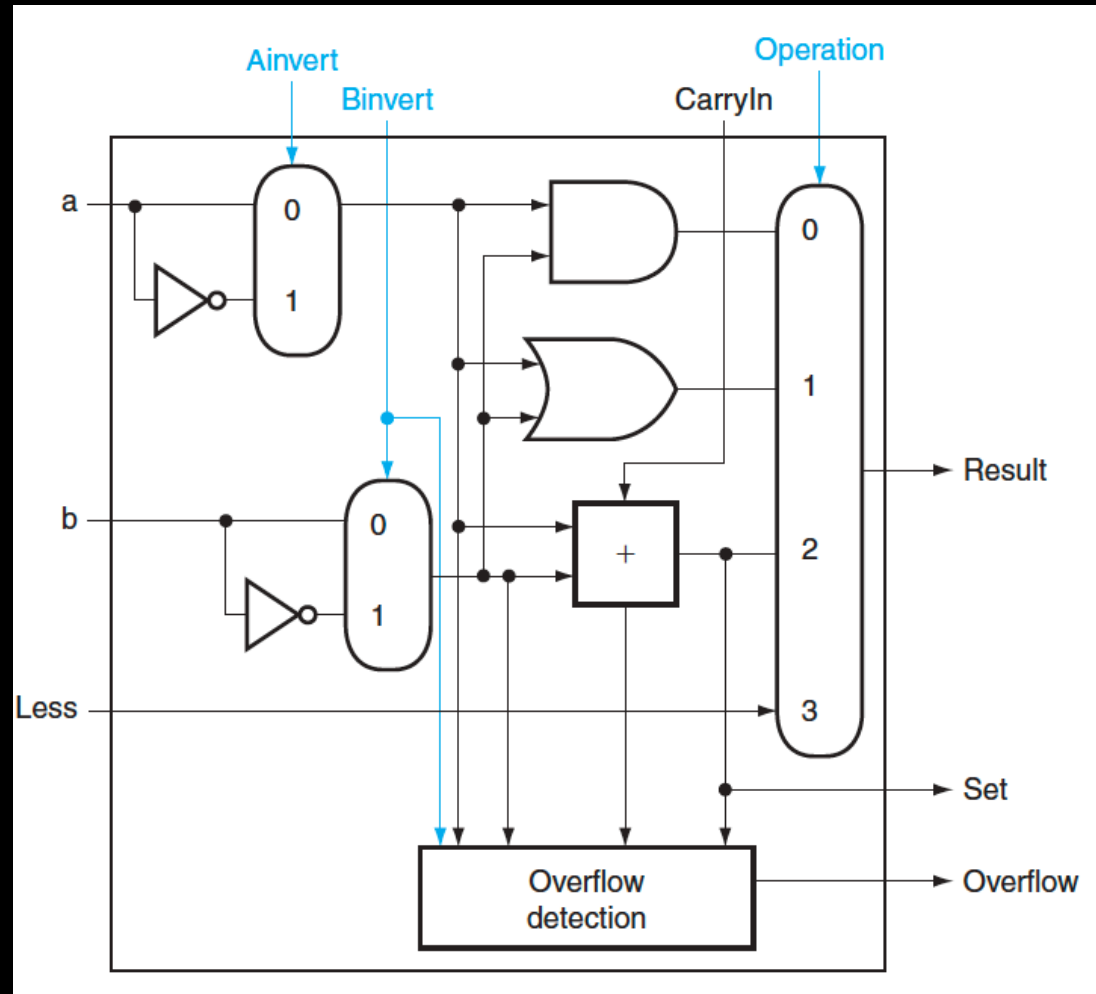



# Critical Path

What is the length of the critical path for a 32-bit ALU (in gates)?


- A) 9
- B) 32
- C) 64
- D) 69

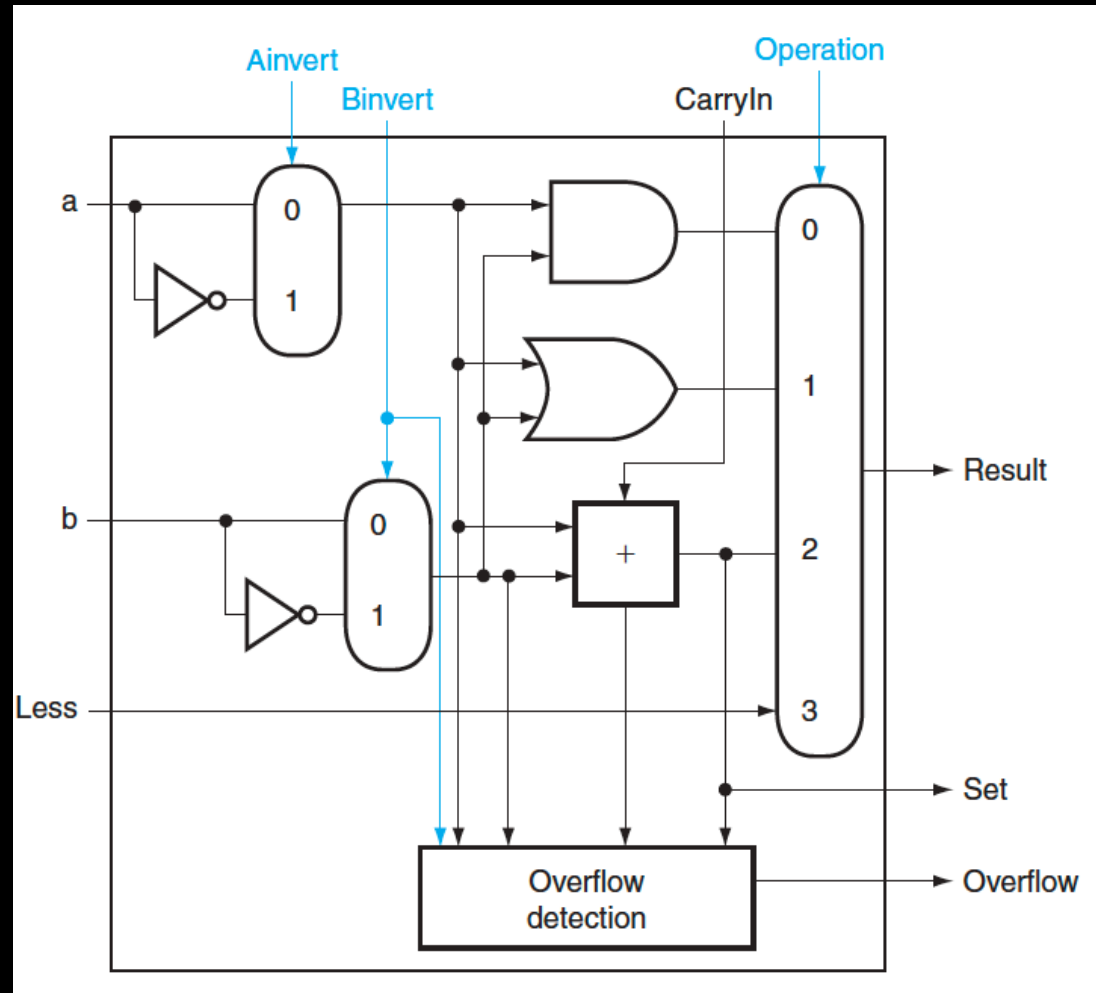

# Multiplexor

  

# Multiplexor

 



# Goals for today

---

## Review

- SR Latches, D Latches, D Flip Flips, and Registers


## Memory

- Register Files
- Tri-state devices
- SRAM (Static RAM—random access memory)
- DRAM (Dynamic RAM)

# Bistable Devices

---


- Stable and unstable equilibria?

 

A Simple Device



# Bistable Devices

- Stable and unstable equilibria?

 

A Simple Device


- In stable state,  $\bar{A} = B$

  

- How do we change the state?

# SR Latch

---

 


# SR Latch

## Set-Reset (SR) Latch

Stores a value  $Q$  and its complement  $\bar{Q}$

S	R	Q	$\bar{Q}$
0	0		
0	1		
1	0		
1	1		

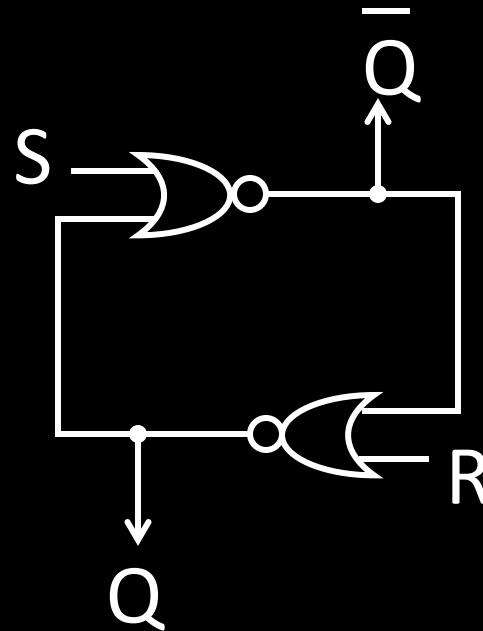


# SR Latch


## Set-Reset (SR) Latch

Stores a value  $Q$  and its complement  $\bar{Q}$

S	R	Q	$\bar{Q}$
0	0	Q	Q
0	1	0	1
1	0	1	0
1	1	forbidden	

 

# Unclocked D Latch

 


Data (D) Latch

D	Q	$\bar{Q}$
0		
1		

# Unclocked D Latch

## Data (D) Latch

 

D	Q	$\bar{Q}$
0	0	1
1	1	0

## Data Latch

- Easier to use than an SR latch
- No possibility of entering an undefined state


## When D changes, Q changes

- ... immediately (after a delay of 2 Ors and 2 NOTs)

## Need to control when the output changes



# D Latch with Clock

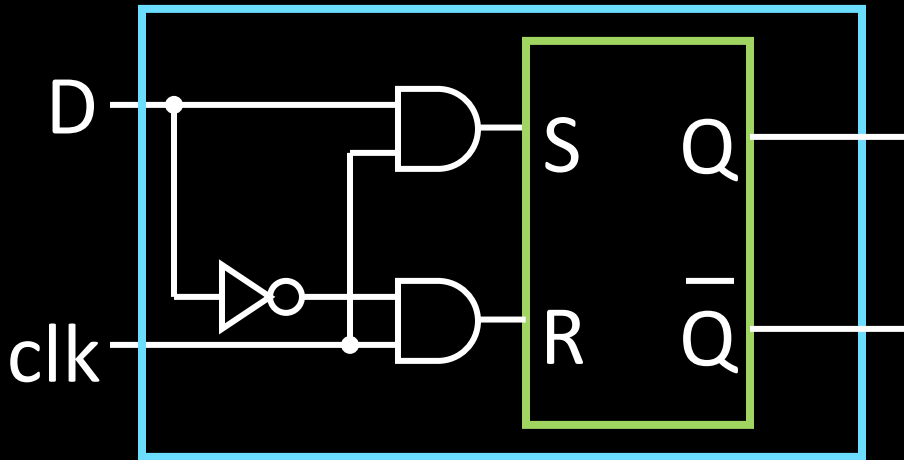

D	Q	$\bar{Q}$
0	0	1
1	1	0

## Level Sensitive D Latch


Clock high:

set/reset (according to D)

Clock low:

keep state (ignore D)

# D Latch with Clock

 


D	Q	$\bar{Q}$
0	0	1
1	1	0


S	R	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	0	1
1	0	1	0
1	1	forbidden	

clk	D	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	Q	$\bar{Q}$
1	0	0	1
1	1	1	0

# D Latch with Clock

 


D	Q	$\bar{Q}$
0	0	1
1	1	0

 


clk	D	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	Q	$\bar{Q}$
1	0	0	1
1	1	1	0

# Edge-Triggered D Flip-Flop

 
 
## D Flip-Flop



- Edge-Triggered
- Data is captured when clock is high
- Outputs change only on falling edges




# Registers
  
## Register

- D flip-flops in parallel
- shared clock
- extra clocked inputs: write\_enable, reset, ...



# Voting Machine

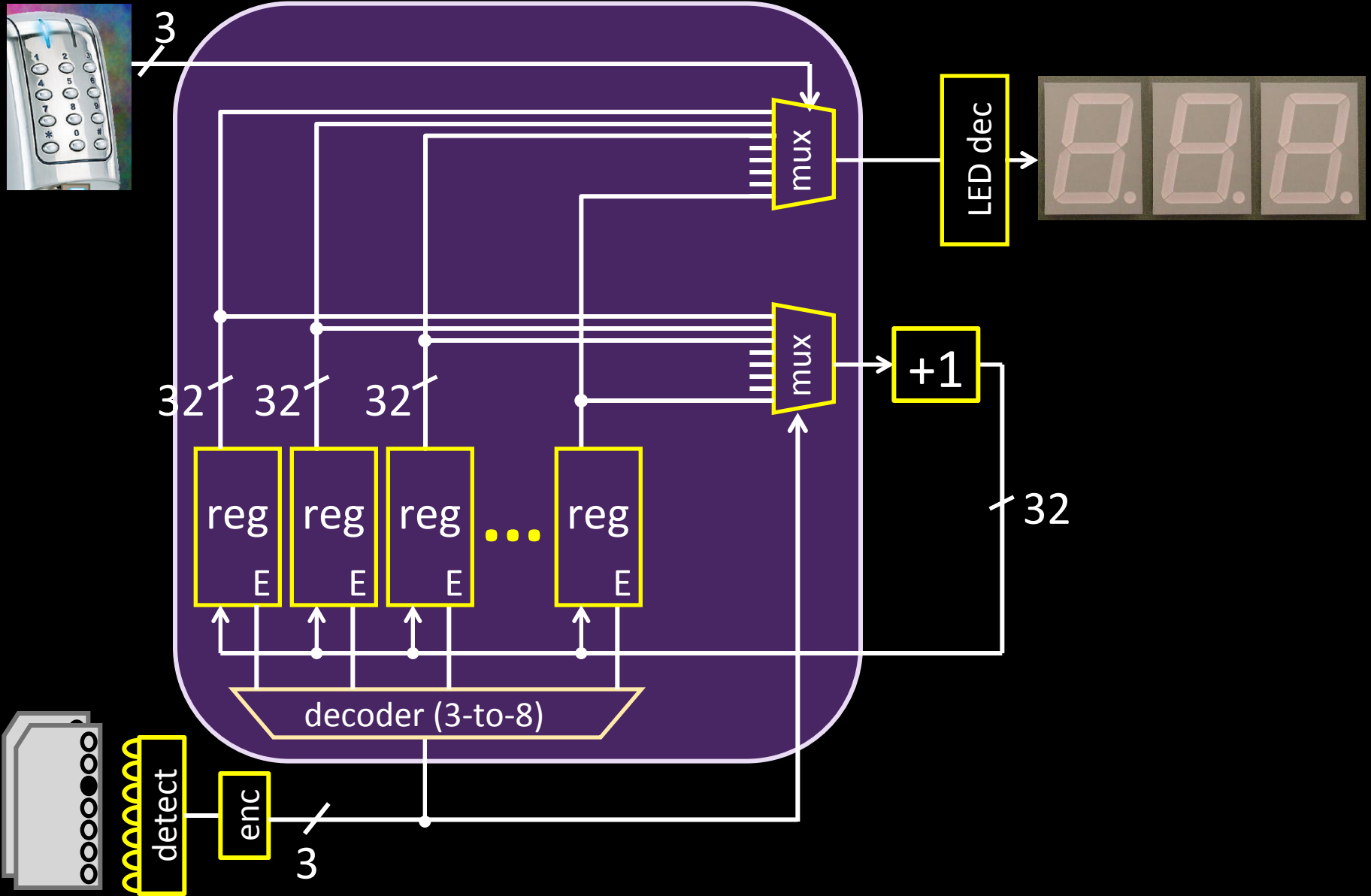

# Goals for today

---

## Review

- SR Latches, D Latches, D Flip Flips, and Registers


## Memory

- Register Files
- Tri-state devices
- SRAM (Static RAM—random access memory)
- DRAM (Dynamic RAM)

# Register File
 
## Register File

- N read/write registers
- Indexed by register number



## Implementation:

- D flip flops to store bits
- Decoder for each **write port**
- Mux for each **read port**




# Register File

## Register File

- N read/write registers
- Indexed by register number
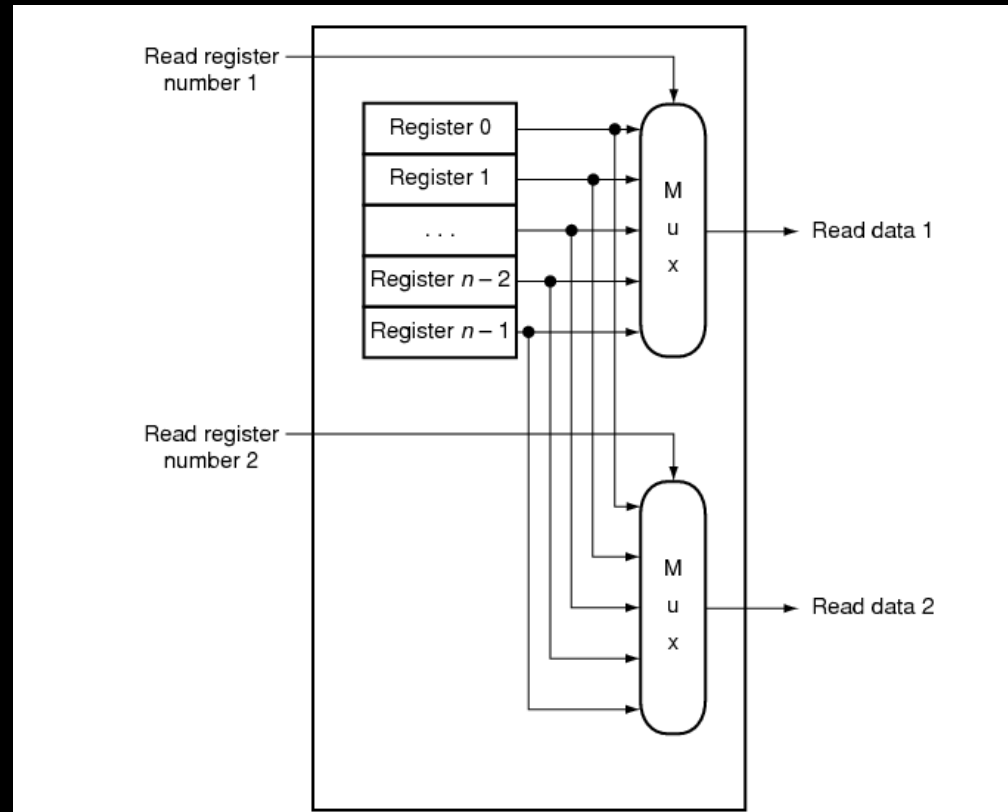
## Implementation:

- D flip flops to store bits
- Decoder for each **write port**
- Mux for each **read port**




# Register File

## Register File

- N read/write registers
- Indexed by register number
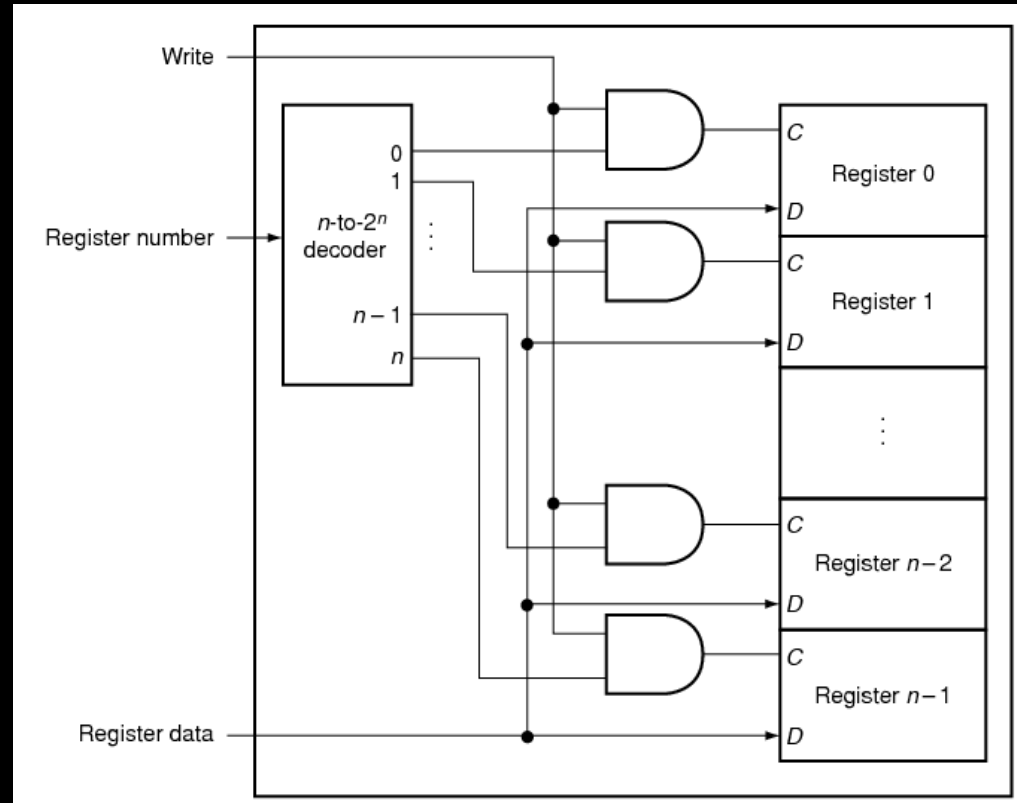
## Implementation:

- D flip flops to store bits
- Decoder for each **write port**
- Mux for each **read port**



# Tradeoffs

---

## Register File tradeoffs

- + Very fast (a few gate delays for both read and write)
- + Adding extra ports is straightforward
- Doesn't scale

# Building Large Memories


---

Need a shared **bus** (or shared **bit line**)


- Many FFs/outputs/etc. connected to single wire
- Only one output *drives* the bus at a time

# Tri-State Devices


## Tri-State Buffers

 

E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

 


# Shared Bus

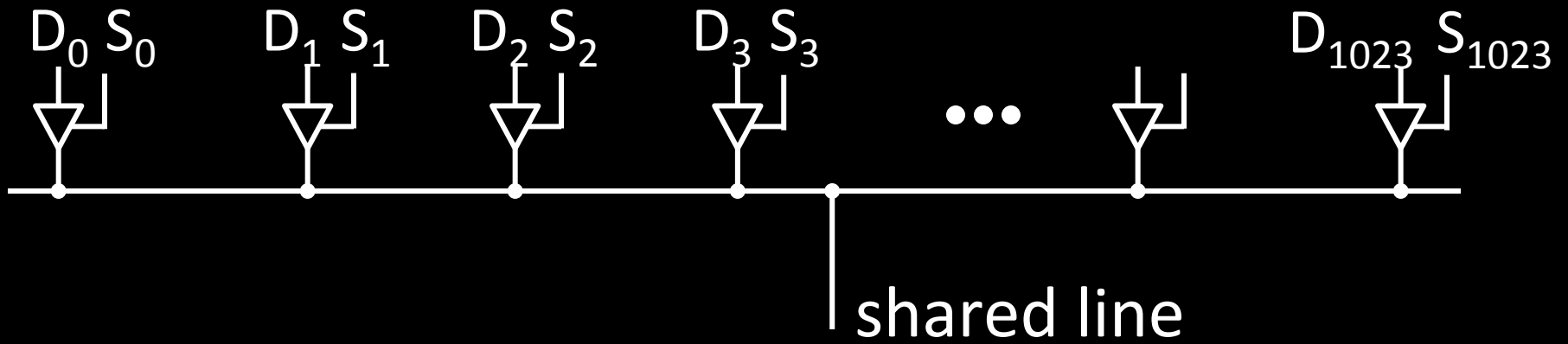


# SRAM
 
## Static RAM (SRAM)

- Essentially just SR Latches + tri-states buffers




# SRAM Chip

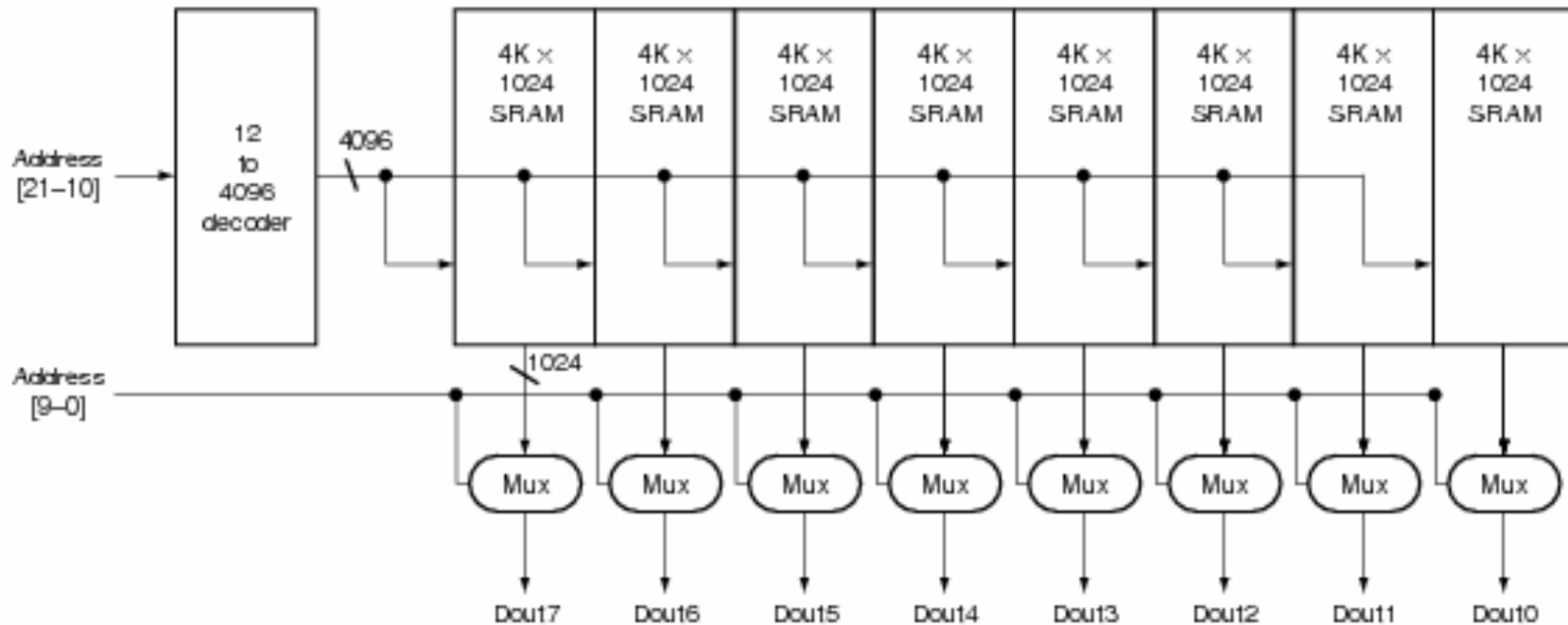

**FIGURE B.9.4 Typical organization of a 4M x 8 SRAM as an array of 4K x 1024 arrays.** The first decoder generates the addresses for eight 4K x 1024 arrays; then a set of multiplexers is used to select 1 bit from each 1024-bit-wide array. This is a much easier design than a single-level decode that would need either an enormous decoder or a gigantic multiplexer. In practice, a modern SRAM of this size would probably use an even larger number of blocks, each somewhat smaller.




# SRAM Chip

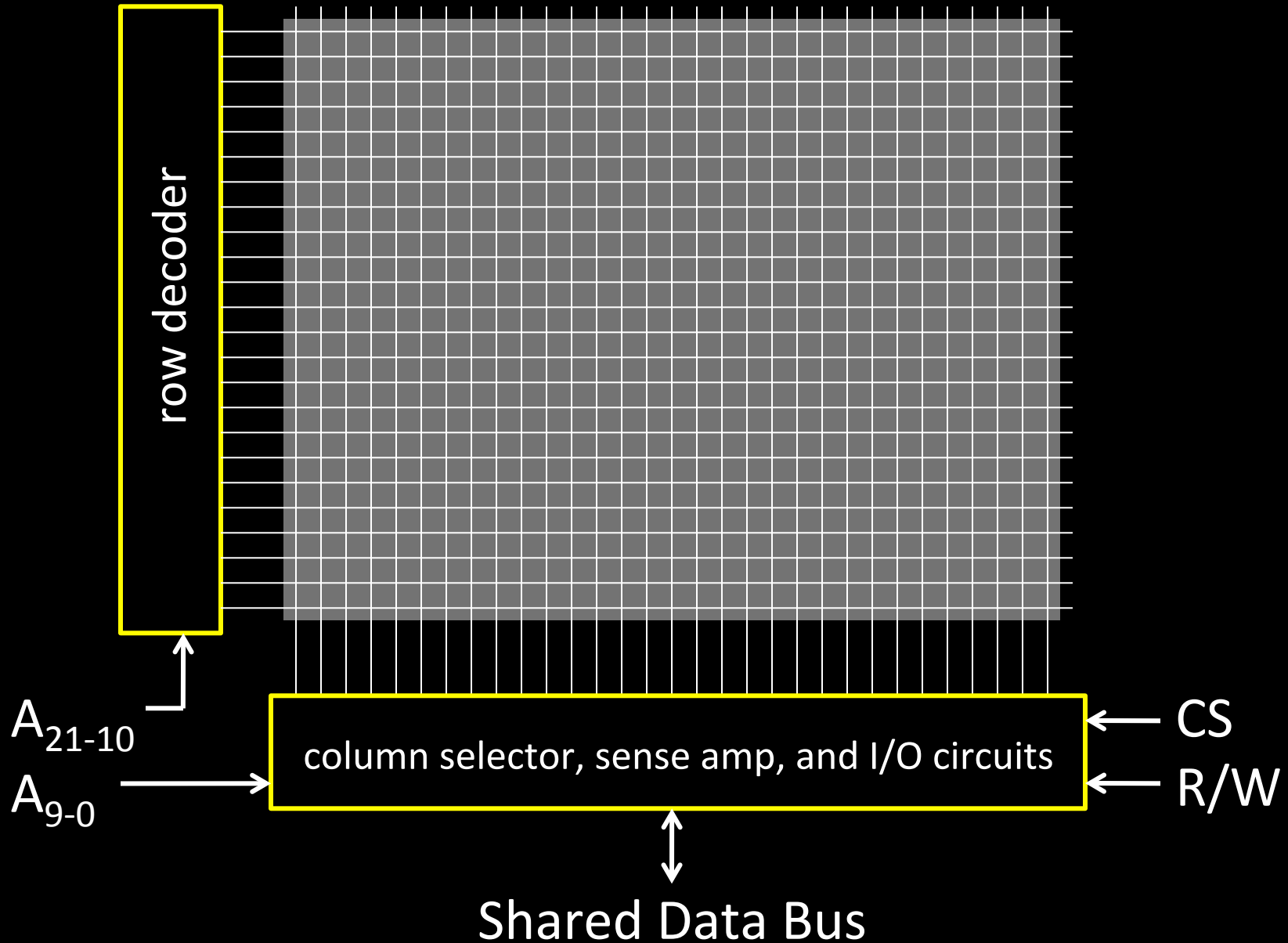

# SRAM Cell

## Typical SRAM Cell

 

Each cell stores one bit, and requires 4 – 8 transistors (6 is typical)


### Read:

- pre-charge  $B$  and  $\overline{B}$  to  $V_{dd}/2$
- pull word line high
- cell pulls  $B$  or  $\overline{B}$  low, sense amp detects voltage difference

### Write:

- pull word line high
- drive  $B$  and  $\overline{B}$  to flip cell

# SRAM Modules and Arrays

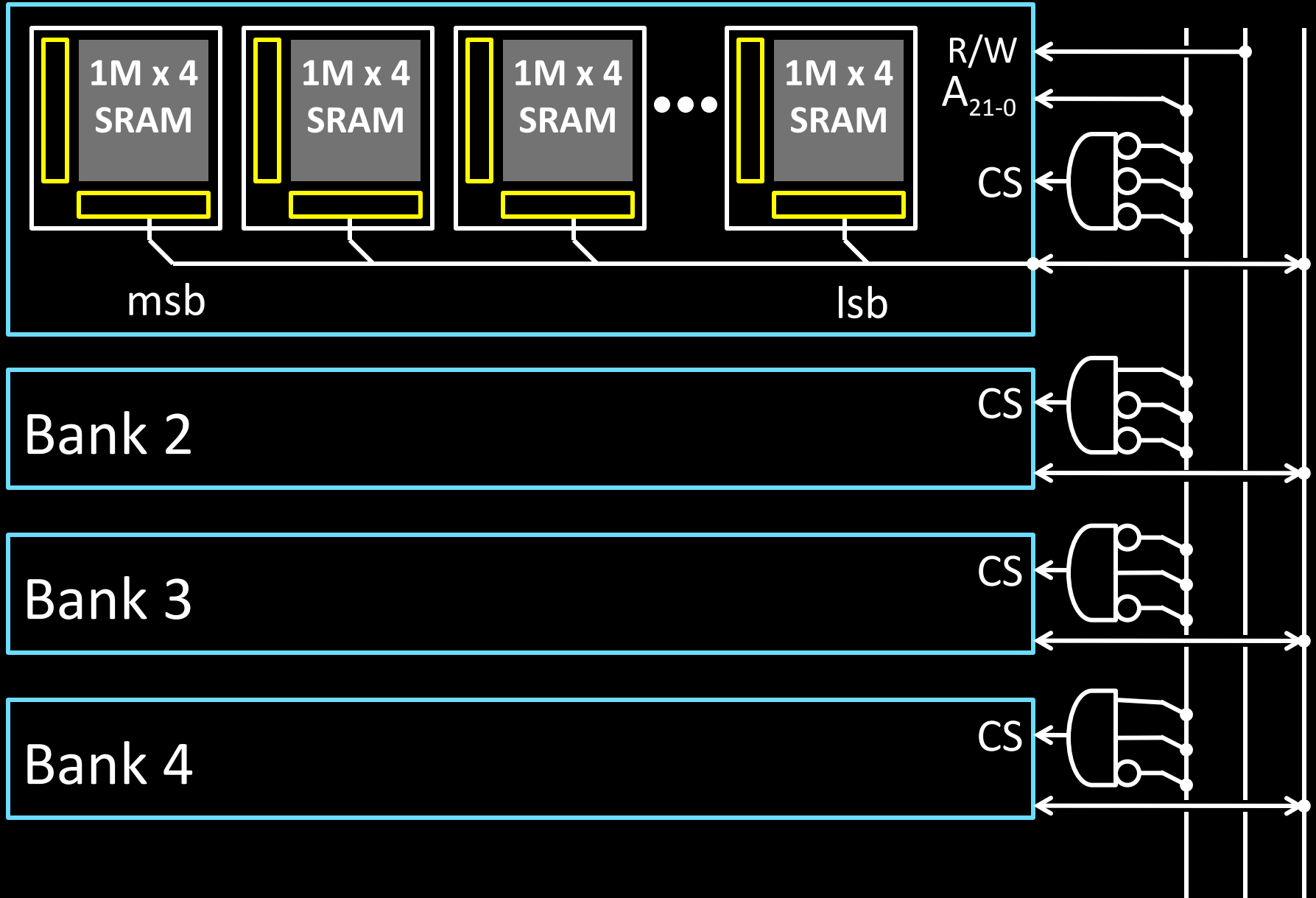

# SRAM Summary

---


## SRAM

- A few transistors ( $\sim 6$ ) per cell
- Used for working memory (caches)
- But for even higher density...

# Dynamic RAM: DRAM

## Dynamic-RAM (DRAM)

- Data values require constant refresh

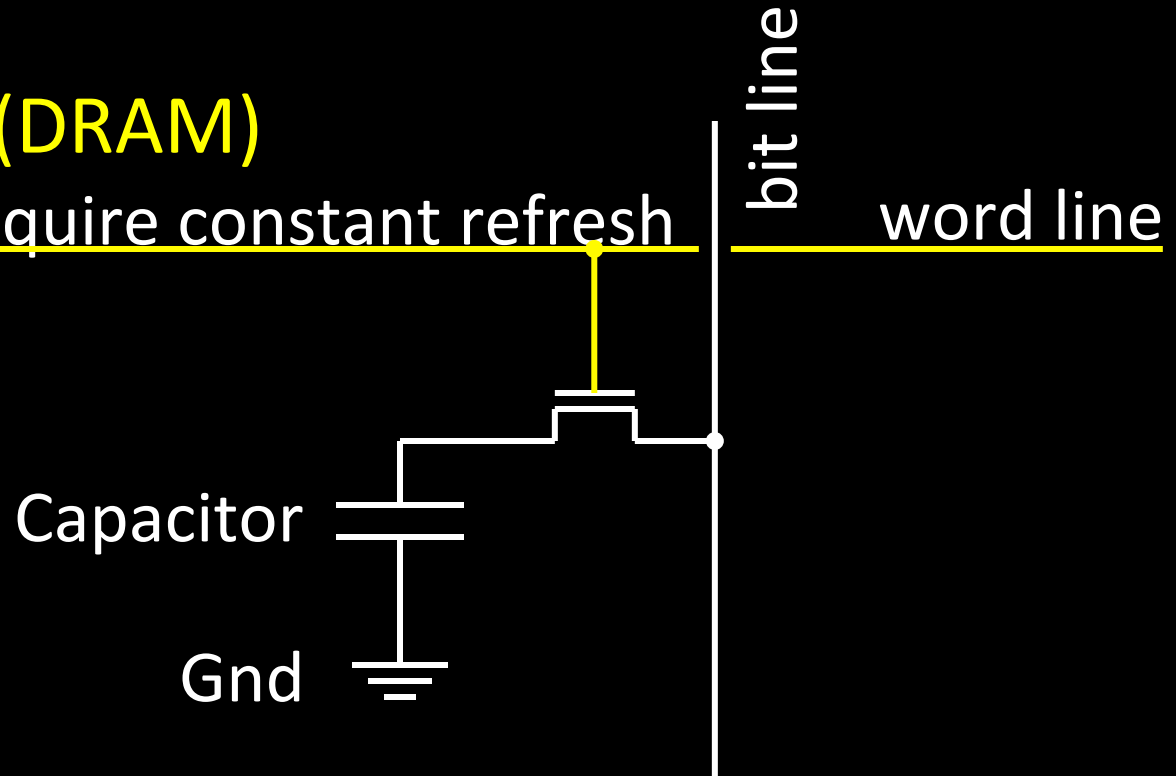

# DRAM vs. SRAM

---

Single transistor vs. many gates

- Denser, cheaper (\$30/1GB vs. \$30/2MB)
- But more complicated, and has analog sensing

Also needs refresh

- Read and write back...
- ...every few milliseconds
- Organized in 2D grid, so can do rows at a time
- Chip can do refresh internally

Hence... slower and energy inefficient

# Memory

---

## Register File tradeoffs

- + Very fast (a few gate delays for both read and write)
- + Adding extra ports is straightforward
- Expensive, doesn't scale
- Volatile

## Volatile Memory alternatives: SRAM, DRAM, ...

- Slower
- + Cheaper, and scales well
- Volatile

## Non-Volatile Memory (NV-RAM): Flash, EEPROM, ...

- + Scales well
- Limited lifetime; degrades after 100000 to 1M writes

# Summary

---

We now have enough building blocks to build machines that can perform non-trivial computational tasks

Register File: Tens of words of working memory

SRAM: Millions of words of working memory

DRAM: Billions of words of working memory

NVRAM: long term storage

(usb fob, solid state disks, BIOS, ...)