

# Memory

**Anne Bracy**

**CS 3410**


Computer Science

Cornell University

The slides are the product of many rounds of teaching CS 3410 by Professors Weatherspoon, Bala, Bracy, and Sirer.

See P&H Appendix B.8 (register files) and B.9

# Big Picture: Building a Processor

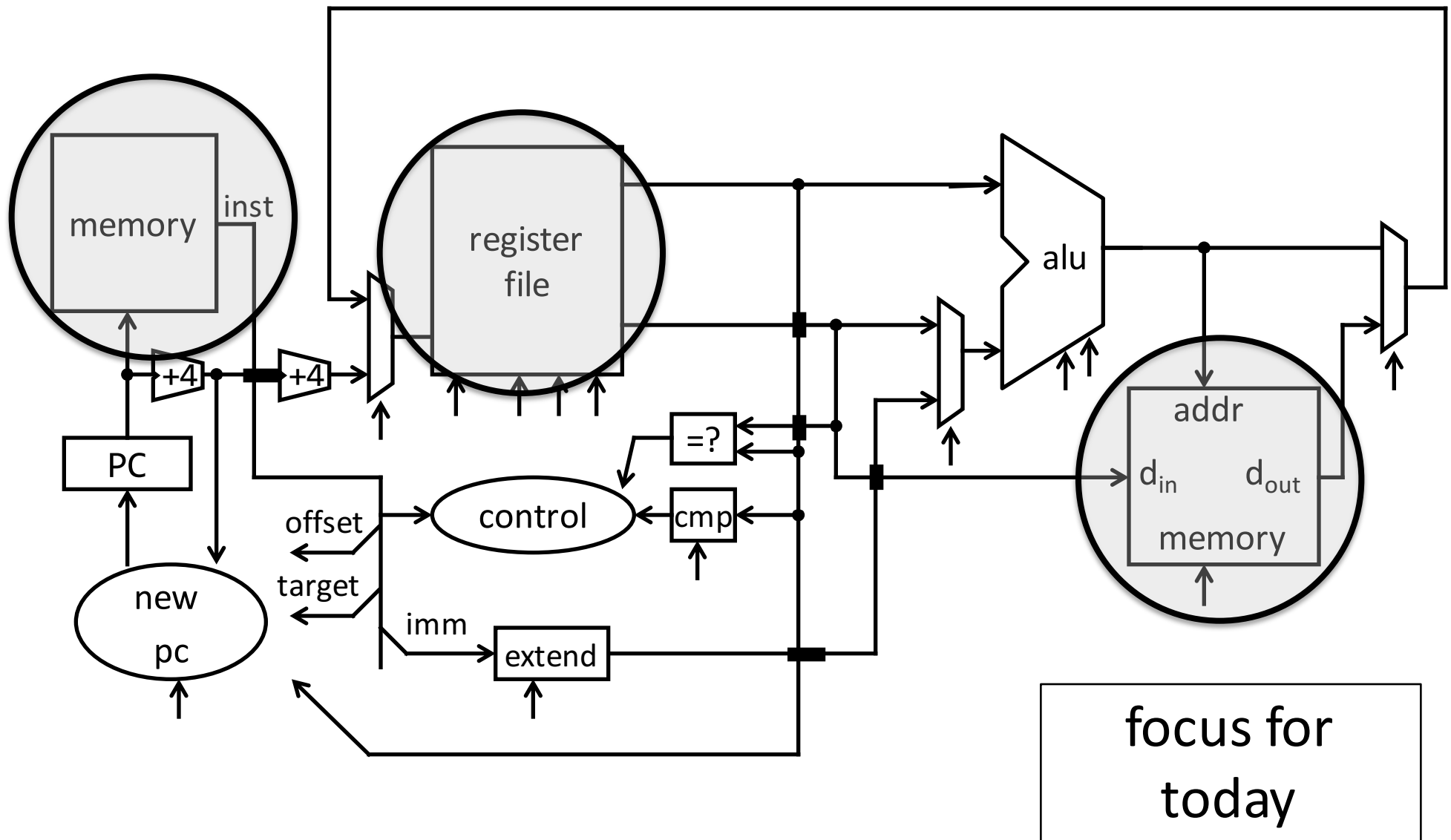

A Single cycle processor

# Goals for today


## Memory

- Register Files
- Tri-state devices
- SRAM (Static RAM—random access memory)
- DRAM (Dynamic RAM)

# Register File
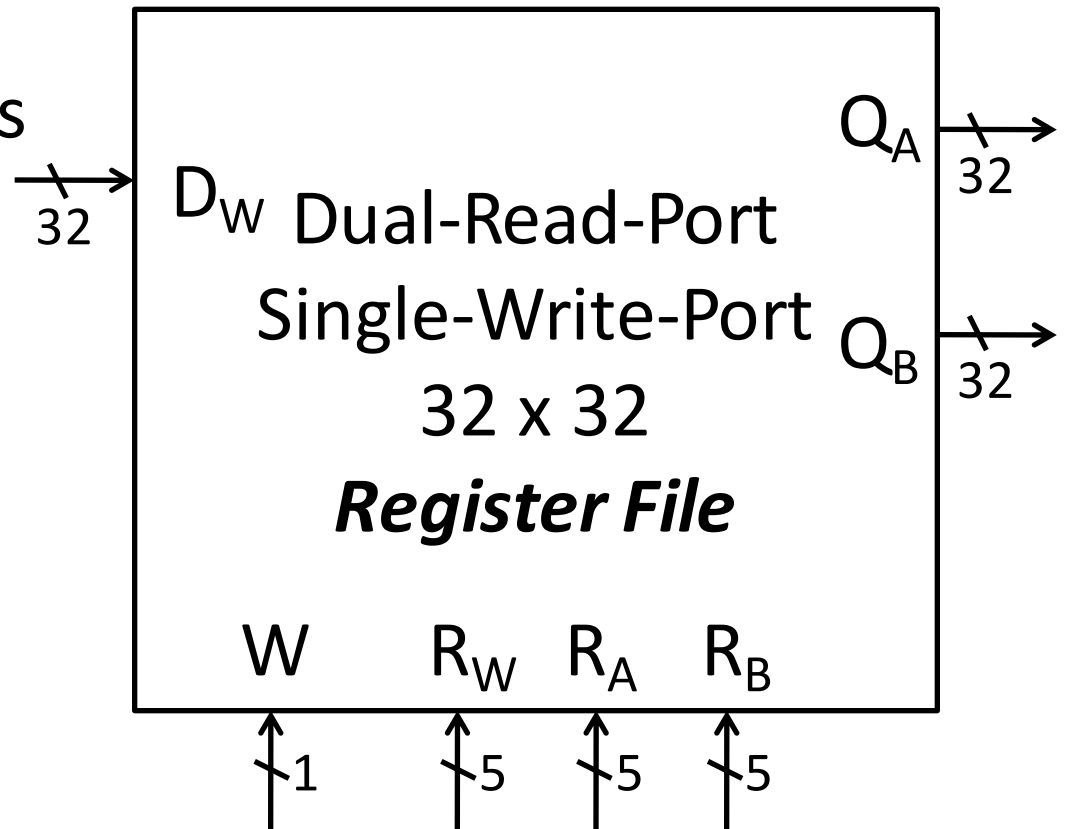
## Register File



- N read/write registers
- Indexed by register number


  
# Register File

Recall: Register

- D flip-flops in parallel
- shared clock
- extra clocked inputs: write\_enable, reset, ...




# Writing to the Register File (1)

## Register File

- N read/write registers
- Indexed by register number

```
addi r5, r0, 10
```

 


How to write to **one** register in the register file?

- Need a decoder

# Activity: 3-to-8 decoder truth table & circuit

i2	i1	i0	o0	o1	o2	o3	o4	o5	o6	o7
0	0	0								
0	0	1								
0	1	0								
0	1	1								
1	0	0								
1	0	1								
1	1	0								
1	1	1								

 


# Writing to the Register File (2)

## Register File

- N read/write registers
- Indexed by register number

```
addi r5, r0, 10
```

 

How to write to **one** register in the register file?

- Need a decoder




# Reading from the Register File

## Register File

- N read/write registers
- Indexed by register number

## How to read from two registers?

- Need a multiplexor

 


# Register File

## Register File

- N read/write registers
- Indexed by register number
 
## Implementation:


- D flip flops to store bits
- Decoder for each write port
- Mux for each read port



# Register File
 
## Register File

- N read/write registers
- Indexed by register number



## Implementation:

- D flip flops to store bits
- Decoder for each write port
- Mux for each read port

# Tradeoffs


## Register File tradeoffs

- + Very fast (a few gate delays for both read and write)
- + Adding extra ports is straightforward
- Doesn't scale

e.g. 32Mb register file with  
32 bit registers

Need 32x 1M-to-1 multiplexor  
and 32x 20-to-1M decoder

How many logic gates/transistors?

 

# Goals for today


## Memory

- CPU: Register Files (i.e. Memory w/in the CPU)
- Scaling Memory: Tri-state devices
- Cache: SRAM (Static RAM—random access memory)
- Memory: DRAM (Dynamic RAM)
 
# Building Large Memories

Need a shared bus (or shared bit line)

- Many FlipFlops/outputs/etc. connected to single wire
- Only one output *drives* the bus at a time




- How do we build such a device?

# Tri-State Devices

 
## Tri-State Buffers

- If enabled ( $E=1$ ), then  $Q = D$
- Otherwise,  $Q$  is not connected ( $z = \text{high impedance}$ )



E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

# Shared Bus

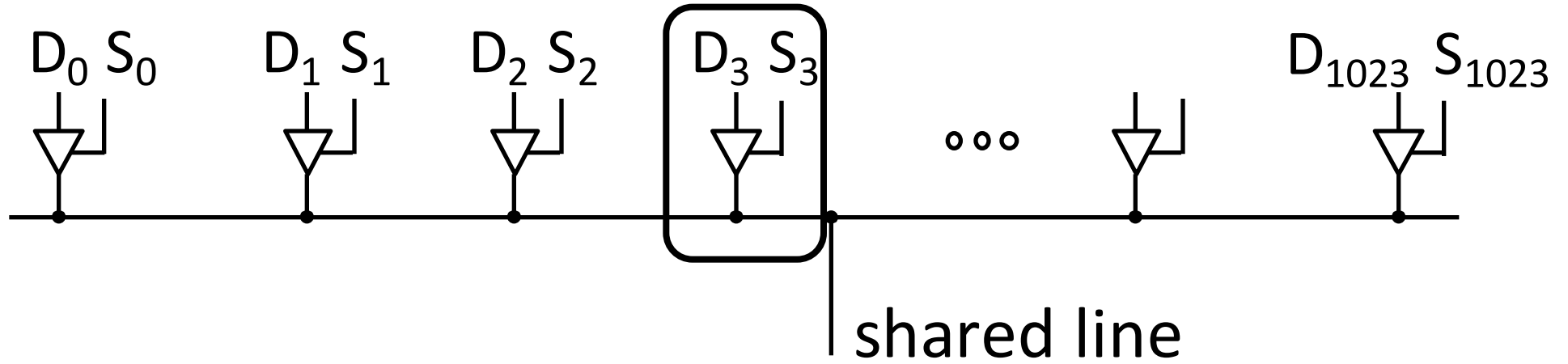



# Takeways

Register files are very fast storage (only a few gate delays), but does not scale to large memory sizes.

Tri-state Buffers allow scaling since multiple registers can be connected to a single output, while only one register actually drives the output.


# Goals for today

## Memory

- CPU: Register Files (i.e. Memory w/in the CPU)
- Scaling Memory: Tri-state devices
- Cache: SRAM (Static RAM—random access memory)
- Memory: DRAM (Dynamic RAM)
 
# Memory


- Storage Cells + plus Tri-State Buffers
- Inputs: Address, Data (for writes)
- Outputs: Data (for reads)
- Also need R/W signal (not shown)



- N address bits  $\rightarrow 2^N$  words total
- M data bits  $\rightarrow$  each word M bits
 
# Memory


- Storage Cells + plus Tri-State Buffers
- Decoder selects a word line
- R/W selector determines access type
- Word line is then coupled to the data lines


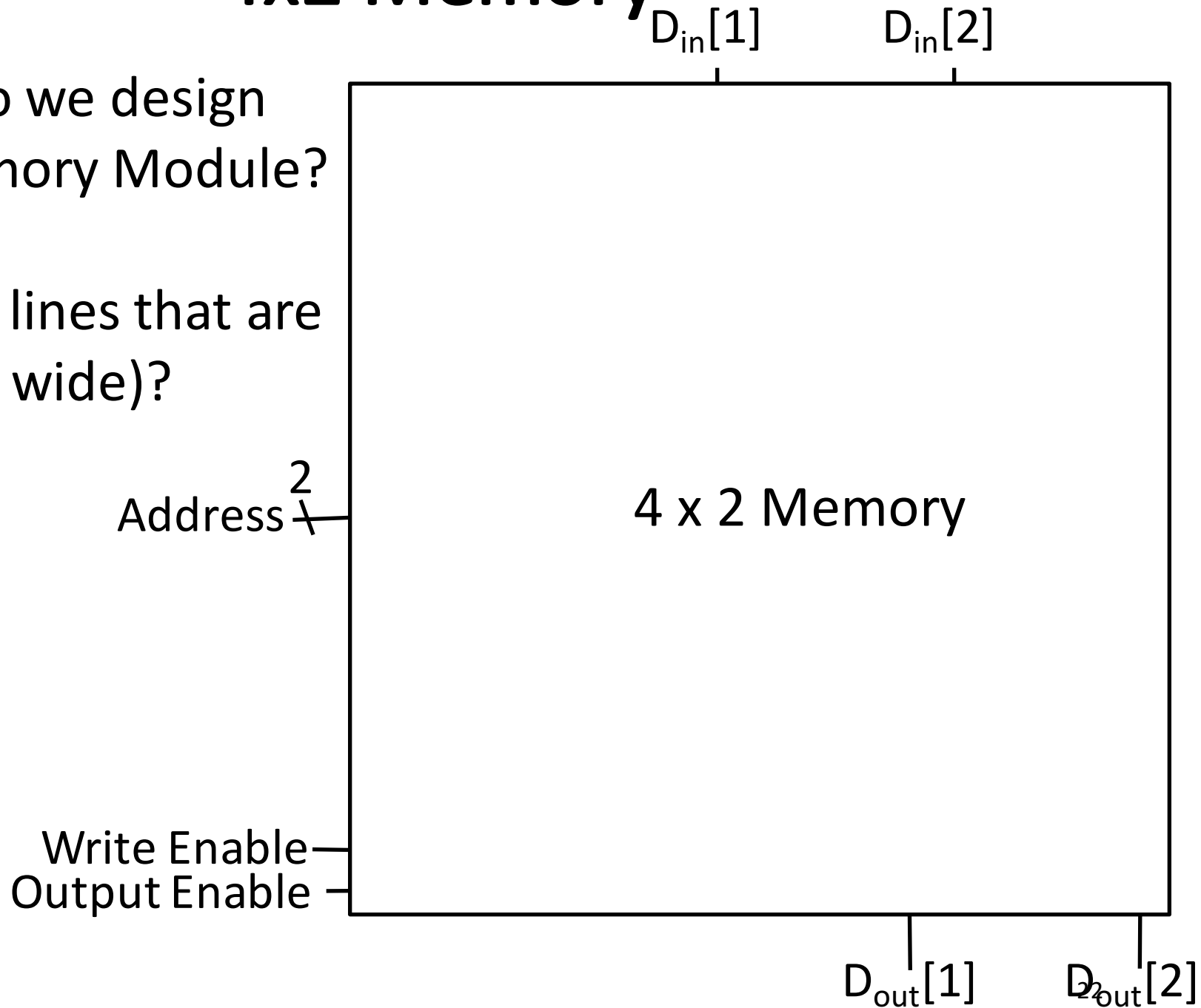
# 4x2 Memory

E.g. How do we design  
a 4 x 2 Memory Module?


(i.e. 4 word lines that are  
each 2 bits wide)?


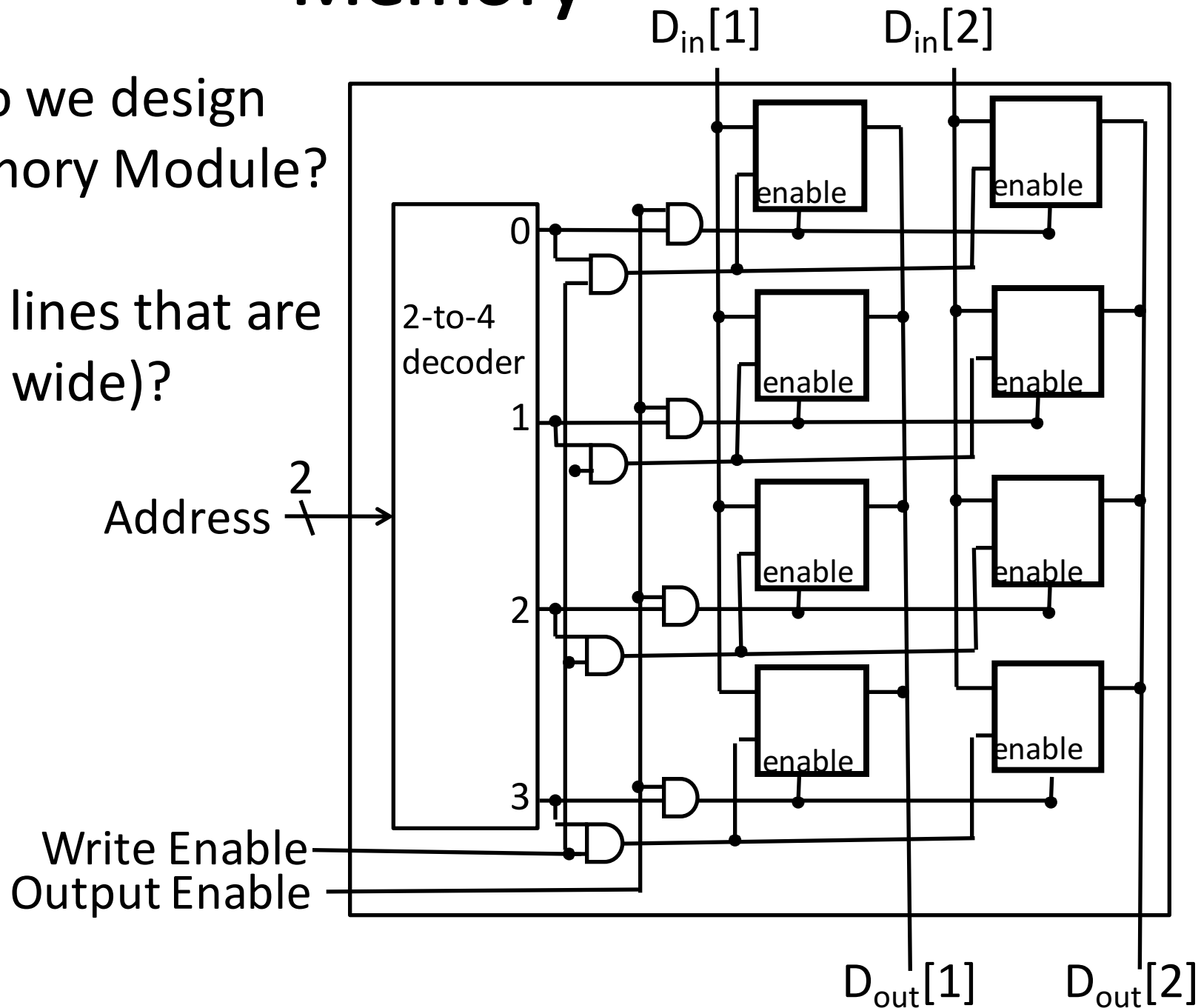
# Memory

E.g. How do we design  
a 4 x 2 Memory Module?


(i.e. 4 word lines that are  
each 2 bits wide)?


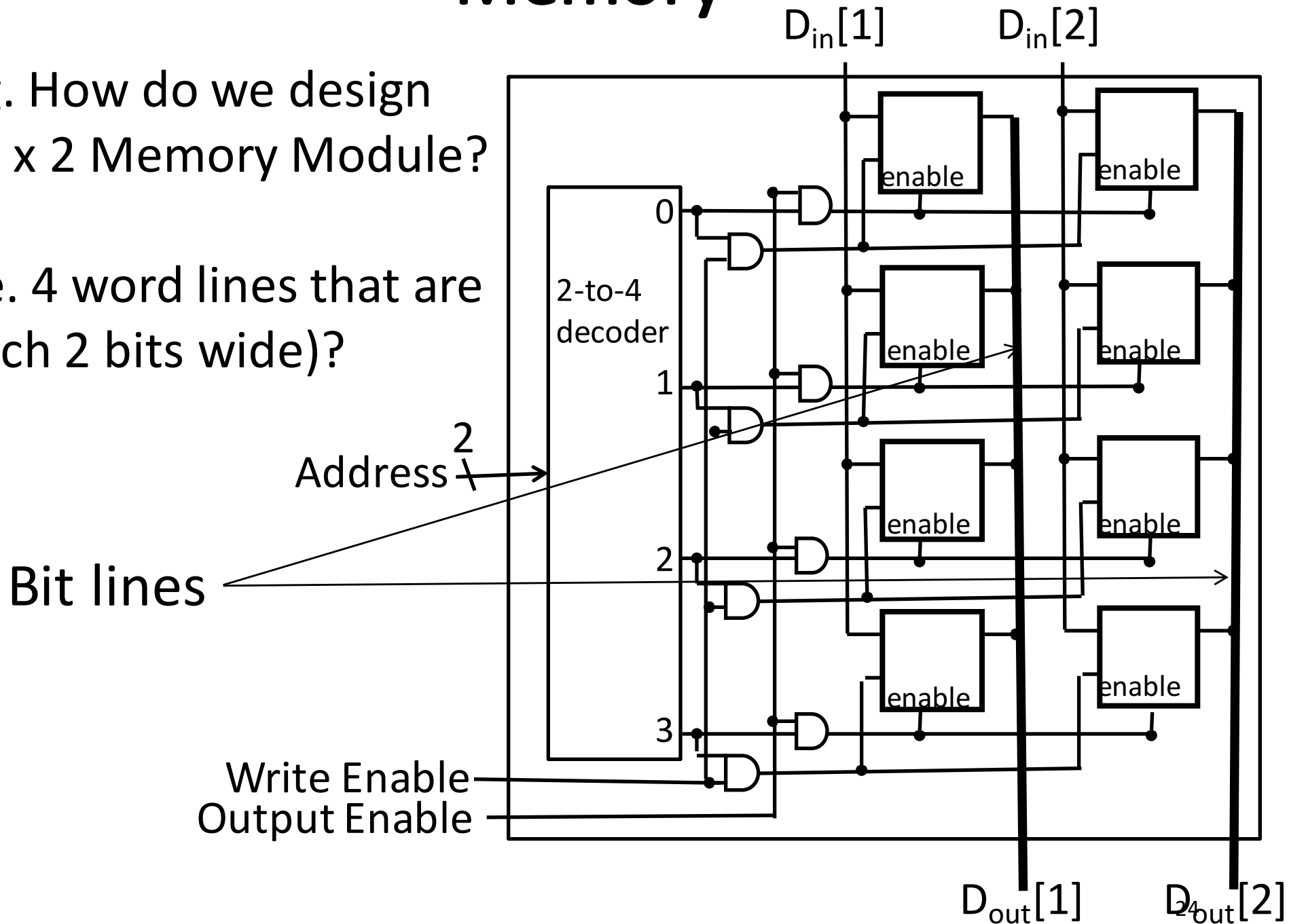
# Memory

E.g. How do we design  
a 4 x 2 Memory Module?


(i.e. 4 word lines that are  
each 2 bits wide)?


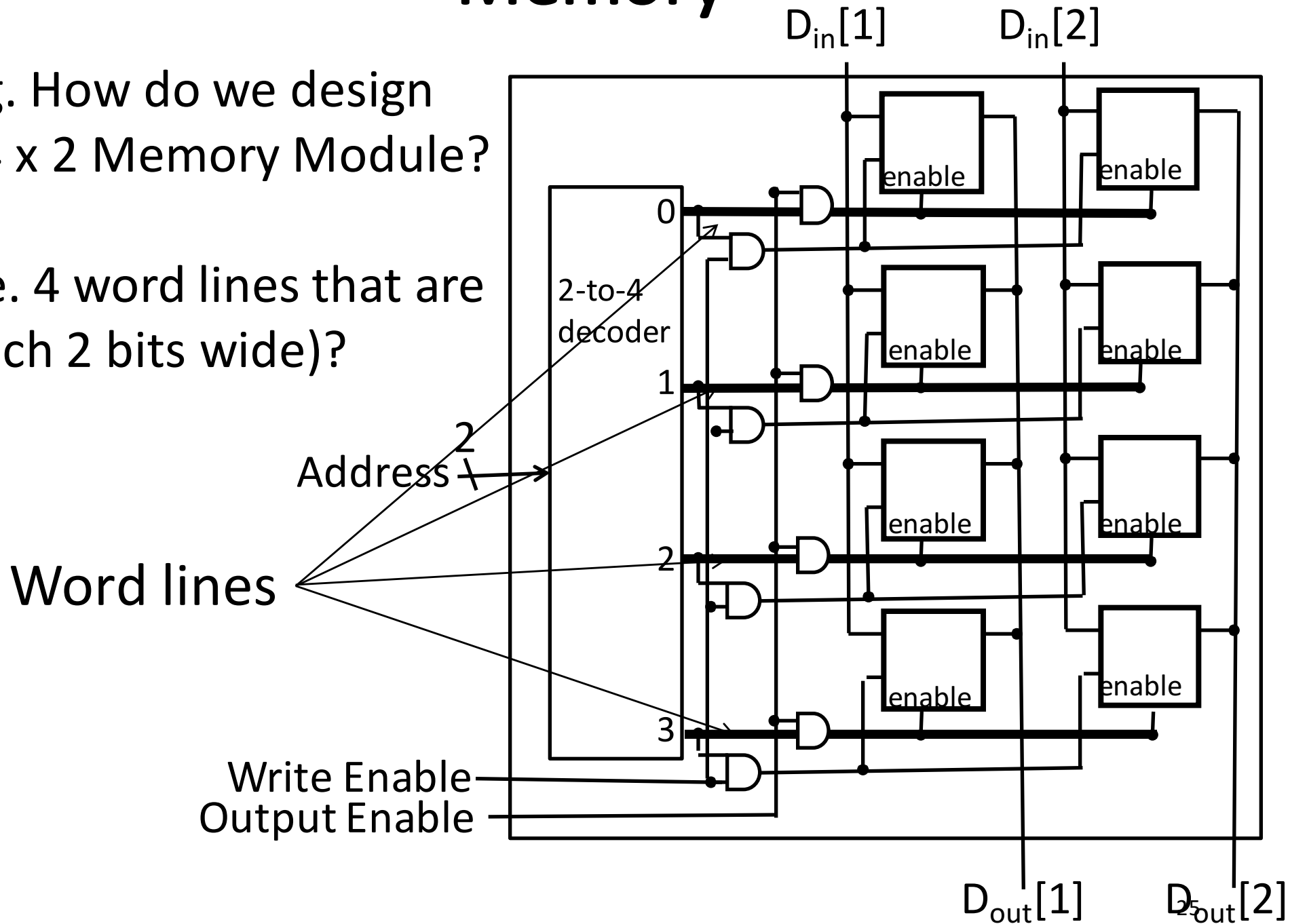
# Memory

E.g. How do we design  
a 4 x 2 Memory Module?


(i.e. 4 word lines that are  
each 2 bits wide)?





# SRAM Cell

## Typical SRAM Cell

 

Each cell stores one bit, and requires 4 – 8 transistors (6 is typical)

Pass-Through  
Transistors

# SRAM Summary


## SRAM

- A few transistors ( $\sim 6$ ) per cell
- Used for working memory (caches)
- But for even higher density...

# Dynamic RAM: DRAM

## Dynamic-RAM (DRAM)

- Data values require constant refresh

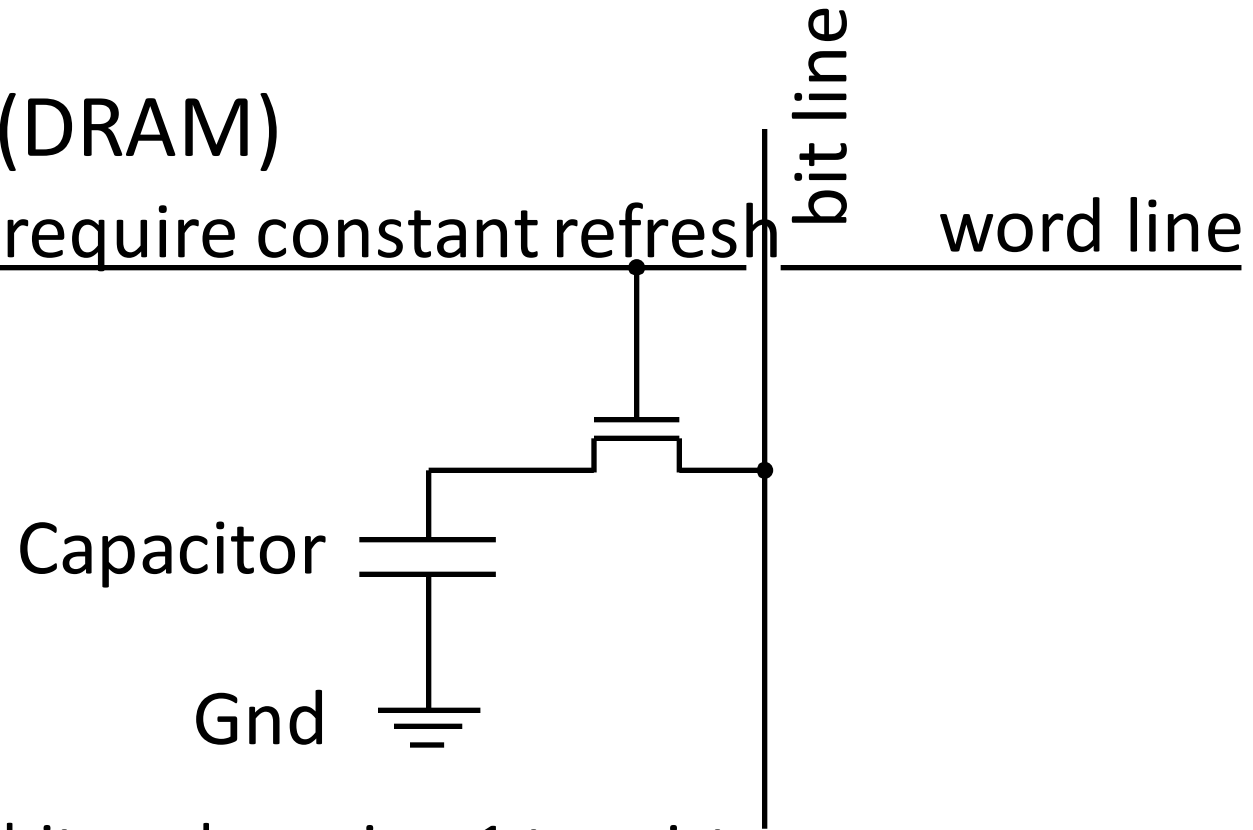


Each cell stores one bit, and requires 1 transistors

# Dynamic RAM: DRAM

## Dynamic-RAM (DRAM)

- Data values require constant refresh

 

Each cell stores one bit, and requires 1 transistors

# DRAM vs. SRAM

Single transistor vs. many gates

- Denser, cheaper (\$30/1GB vs. \$30/2MB)
- But more complicated, and has analog sensing

Also needs refresh

- Read and write back...
- ...every few milliseconds
- Organized in 2D grid, so can do rows at a time
- Chip can do refresh internally

Hence... slower and energy inefficient

# Memory

## Register File tradeoffs

- + Very fast (a few gate delays for both read and write)
- + Adding extra ports is straightforward
- Expensive, doesn't scale
- Volatile

## Volatile Memory alternatives: SRAM, DRAM, ...

- Slower
- + Cheaper, and scales well
- Volatile

## Non-Volatile Memory (NV-RAM): Flash, EEPROM, ...

- + Scales well
- Limited lifetime; degrades after 100000 to 1M writes

# Summary

Finally have the building blocks to build machines that can perform non-trivial computational tasks

Register File: Tens of words of working memory

SRAM: Millions of words of working memory

DRAM: Billions of words of working memory

NVRAM: long term storage

(usb fob, solid state disks, BIOS, ...)

Next time we will build a simple processor!