

State

Hakim Weatherspoon

CS 3410

Computer Science

Cornell University

The slides are the product of many rounds of teaching CS 3410 by Professors Weatherspoon, Bala, Bracy, and Sirer.

Announcements

Make sure you are

- Registered for class, can access CMS
- Have a Section you can go to.
- *Lab Sections are required.*
 - “Make up” lab sections **only Friday 11:40am or 1:25pm**
 - Bring laptop to Labs
- Project partners are required for projects starting w/
project 2
 - Have project partner in same Lab Section, if possible
 - WICC hosting a partner finding event Feb 12 @ 6pm in 3rd floor lounge of Gates

Announcements

Make sure to go to your Lab Section this week

Completed **Proj1** due *before* winter break, Friday, Feb 16th

Note, a Design Document is due when you submit Proj1 final circuit

Work **alone**

Work alone, **BUT** use your resources

- Lab Section, Piazza.com, Office Hours
- Class notes, book, Sections, CSUGLab

Announcements

Check online syllabus/schedule

- <http://www.cs.cornell.edu/Courses/CS3410/2018sp/schedule>
- Slides and Reading for lectures
- Office Hours
- *Pictures of all TAs*
- Project and Reading Assignments
- **Dates to keep in Mind**
 - Prelims: Thur Mar 15th and Thur May 3rd
 - ***Proj 1: Due next Friday, Feb 16th before Winter break***
 - Proj3: Due before Spring break
 - Final Project: May 15th

Schedule is subject to change

Collaboration, Late, Re-grading Policies

“White Board” Collaboration Policy

- Can discuss approach together on a “white board”
- Leave , watch a movie (e.g. Strange Things), and write up solution independently
- Do not copy solutions

Late Policy

- Each person has a total of **four** “slip days”
- Max of **two** slip days for any individual assignment
- Slip days deducted first for *any* late assignment, cannot selectively apply slip days
- For projects, slip days are deducted from all partners
- 25% deducted per day late after slip days are exhausted

Regrade policy

- Submit regrade within a week of receiving score

Goals for Today

State

- How do we store *one* bit?
- Attempts at storing (and changing) one bit
 - Set-Reset Latch
 - D Latch
 - D Flip-Flops
 - Master-Slave Flip-Flops
- Register: storing more than one bit, N-bits


Basic Building Blocks

- Decoders and Encoders

Goal


How do we store store *one* bit?

First Attempt: Unstable Devices

 


Second Attempt: Bistable Devices

- Stable and unstable equilibria?

 


A Simple Device

Third Attempt: Set-Reset Latch

 

Third Attempt: Set-Reset Latch

 



S	R	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		

Set-Reset (S-R) Latch

Stores a value Q and its complement

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

Third Attempt: Set-Reset Latch

  

S	R	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		

Set-Reset (S-R) Latch

Stores a value Q and its complement


Takeaway

Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But, SR Latch has a forbidden state.


Next Goal

How do we avoid the forbidden state of S-R Latch?

Fourth Attempt: (Unclocked) D Latch

 

Fill in the truth table?

 

D	Q	\bar{Q}
0		
1		

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

Takeaway

Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But, SR Latch has a forbidden state.

(Unclocked) D Latch can store and change a bit like an SR Latch while avoiding the forbidden state.


Next Goal

How do we coordinate state changes to a D Latch?

Aside: Clocks

Clock helps coordinate state changes

 - Usually generated by an oscillating crystal
- Fixed period
- Frequency = $1/\text{period}$



Clock Disciplines

Level sensitive


- State changes when clock is high (or low)




Edge triggered

- State changes at clock edge

positive edge-triggered

 


negative edge-triggered

 

Clock Methodology

Clock Methodology

- Negative edge, synchronous

 


Edge-Triggered → signals must be stable near falling edge

“near” = before and after


t_{setup} t_{hold}

Round 2: D Latch (1)

 


- Inverter prevents SR Latch from entering 1,1 state

D	Q	\bar{Q}	
0			<i>Reset</i>
1			<i>Set</i>

 


Round 2: D Latch (1)

 

- Level sensitive
- Inverter prevents SR Latch from entering 1,1 state
- C enables changes

C = 1, D Latch *transparent*:
set/reset (according to D)

 C = 0, D Latch *opaque*:
keep state (ignore D)




C	D	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		

No
Change

Reset

Set

Round 2: D Latch (1)

 


- Level sensitive
- Inverter prevents SR Latch from entering 1,1 state
- C enables changes

C = 1, D Latch *transparent*:
set/reset (according to D)

C = 0, D Latch *opaque*:
keep state (ignore D)

S	R	Q	\bar{Q}	
0	0	Q	\bar{Q}	hold
0	1	0	1	reset
1	0	1	0	set
1	1	forbidden		

 

C	D	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		


No
Change

Reset

Set

Round 2: D Latch (1)

Level Sensitive D Latch

 


Clock high:

set/reset (according to D)


Clock low:

keep state (ignore D)

 

clk	D	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		

Round 3: D Flip-Flop

 


- Edge-Triggered
- Data captured when clock high
- Output changes only on falling edges

Round 3: D Flip-Flop


Clock = 1: L1 *transparent*
L2 *opaque*

 When CLK rises (0→1),
now X can change,
Q does not change




Clock = 0: L1 *opaque*
L2 *transparent*

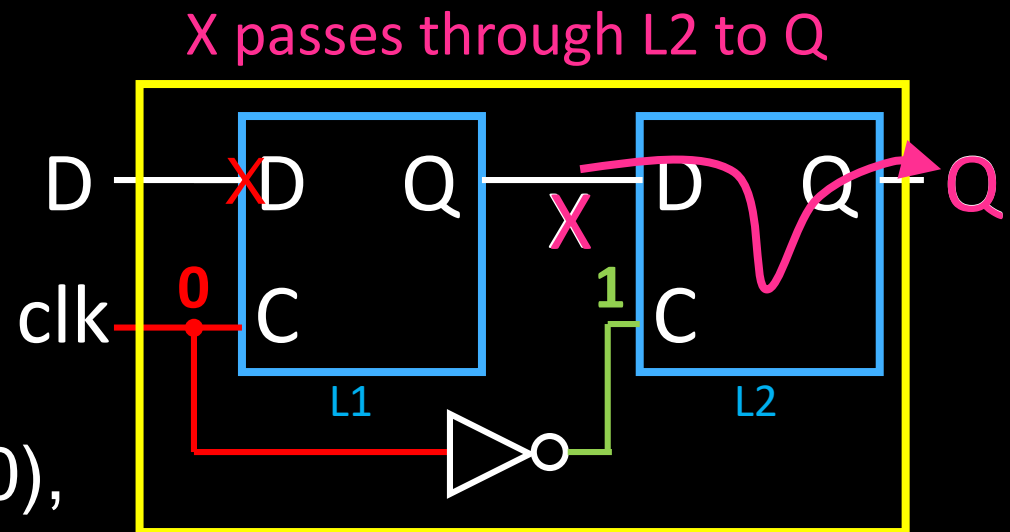When **CLK falls** (1→0),
Q gets X, X cannot change




Edge-Triggered D Flip-Flop

D Flip-Flop

 

 - Edge-Triggered
- Data captured when clock is high
- Output changes only on falling edges



Takeaway

Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But, SR Latch has a forbidden state.

(Unclocked) D Latch can store and change a bit like an SR Latch while avoiding a forbidden state.

An Edge-Triggered D Flip-Flop (aka Master-Slave D Flip-Flop) stores one bit. The bit can be changed in a synchronized fashion on the edge of a clock signal.



Next Goal

How do we store more than one bit, N bits?

Registers

Register

  - D flip-flops in parallel
- shared clock
- extra clocked inputs: write_enable, reset, ...



Takeaway


Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But, SR Latch has a forbidden state.

(Unclocked) D Latch can store and change a bit like an SR Latch while avoiding a forbidden state.

An Edge-Triggered D Flip-Flop (aka Master-Slave D Flip-Flop) stores one bit. The bit can be changed in a synchronized fashion on the edge of a clock signal.

An N -bit **register** stores N -bits. It is created with N D-Flip-Flops in parallel along with a shared clock.

An Example: What will this circuit do?

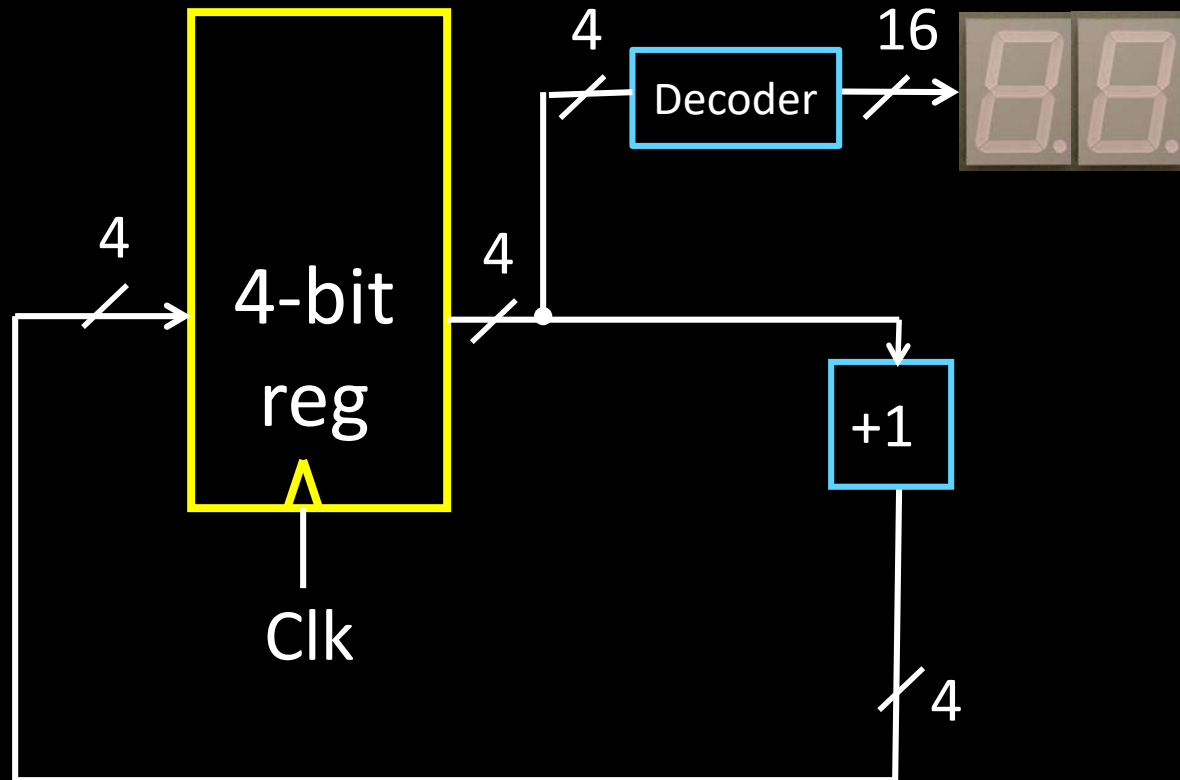


Decoder Example: 7-Segment LED

7-Segment LED

- photons emitted when electrons fall into holes



Decoder Example: 7-Segment LED Decoder

 

3 inputs


- encode 0 – 7 in binary

7 outputs


- one for each LED

7 Segment LED Decoder Implementation


b2	b1	b0	d6	d5	d4	d3	d2	d1	d0
0	0	0							
0	0	1							
0	1	0							
0	1	1							
1	0	0							
1	0	1							
1	1	0							
1	1	1							

 

Basic Building Blocks We have Seen

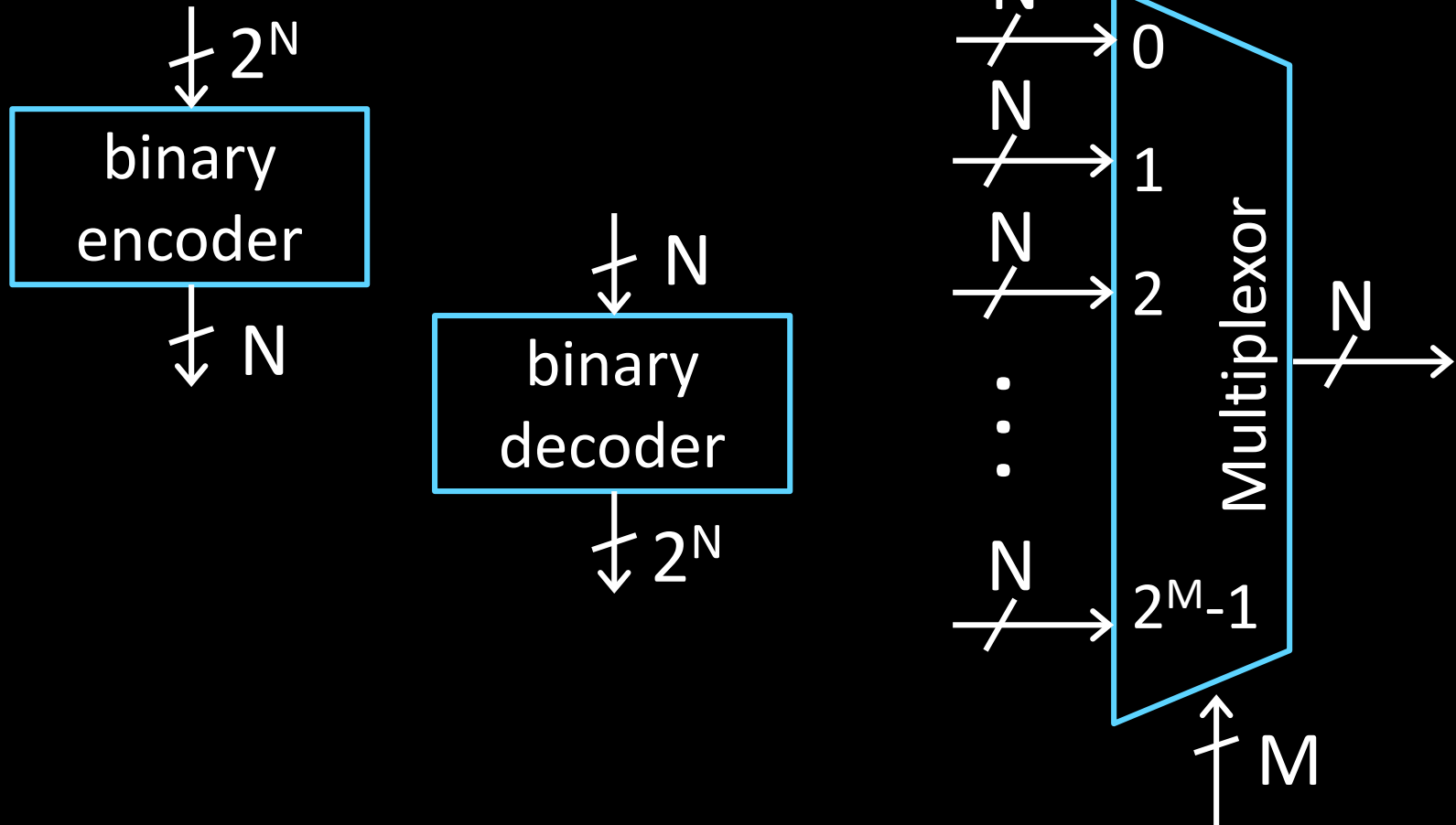

Encoders

 


e.g. Voting:

Can only vote for one out of N candidates, so N inputs.

But can encode vote efficiently with binary encoding.


Example Encoder Truth Table

 

A 3-bit
encoder
with 4 inputs
for simplicity

a	b	c	d				
0	0	0	0				
1	0	0	0				
0	1	0	0				
0	0	1	0				
0	0	0	1				

Basic Building Blocks Example: Voting

 

Recap

We can now build interesting devices with sensors

- Using combinational logic

We can also store data values (aka Sequential Logic)

- In state-holding elements
- Coupled with clocks

Summary

We can now build interesting devices with sensors

- Using combinational logic

We can also store data values

- Stateful circuit elements (D Flip Flops, Registers, ...)
- Clock to synchronize state changes