

Finite State Machines

Hakim Weatherspoon

CS 3410

Computer Science

Cornell University

The slides are the product of many rounds of teaching CS 3410 by Professors Weatherspoon, Bala, Bracy, and Sirer.

Goals for Today

Finite State Machines (FSM)

- How do we design logic circuits with state?
- Types of FSMs: Mealy and Moore Machines
- Examples: Serial Adder and a Digital Door Lock

Finite State Machines

Next Goal

How do we design logic circuits with state?

Finite State Machines

An electronic machine which has

- external inputs
- externally visible outputs
- internal state

Output and next state depend on

- inputs
- current state

Abstract Model of FSM

Machine is

$$M = (S, I, O, \delta)$$

S : Finite set of states

I : Finite set of inputs


O : Finite set of outputs

δ : State transition function

Next state depends on present input *and* present state



Automata Model

Finite State Machine

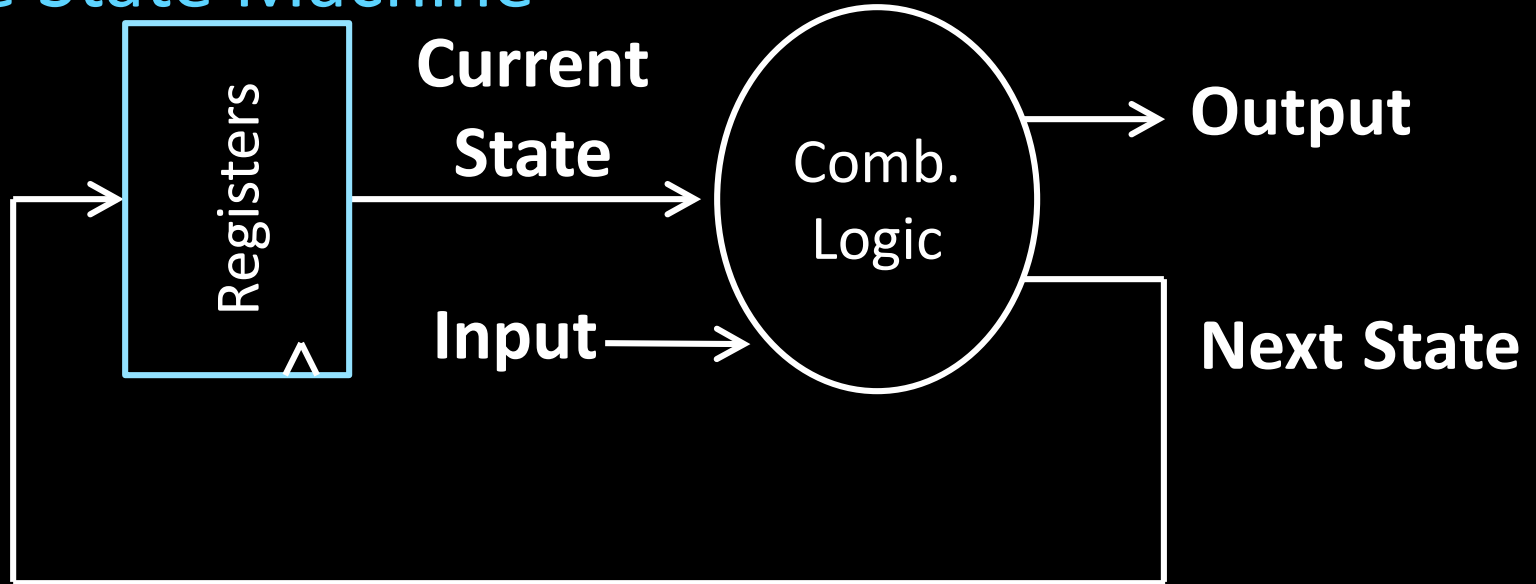

- inputs from external world
- outputs to external world
- internal state
- combinational logic

FSM Example

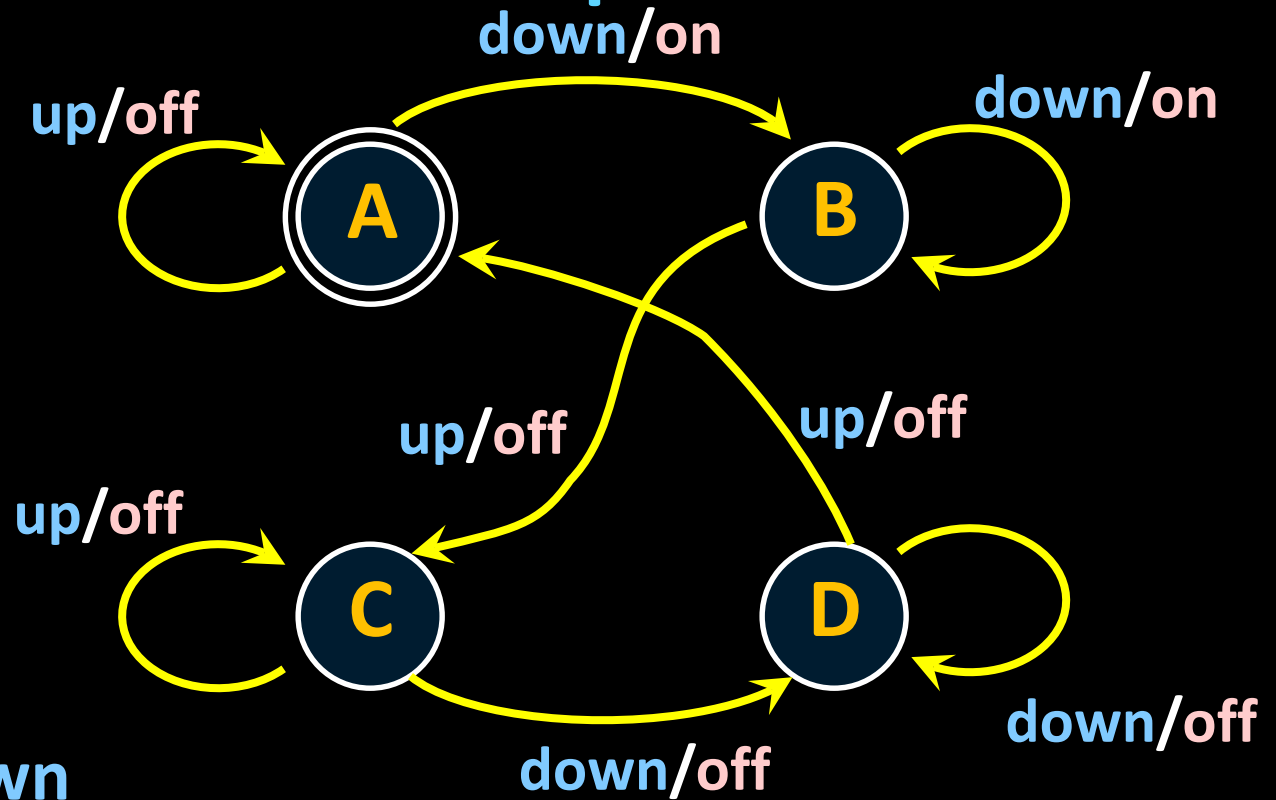
 


Input: **up** or **down**

Output: **on** or **off**

States: **A**, **B**, **C**, or **D**

FSM Example

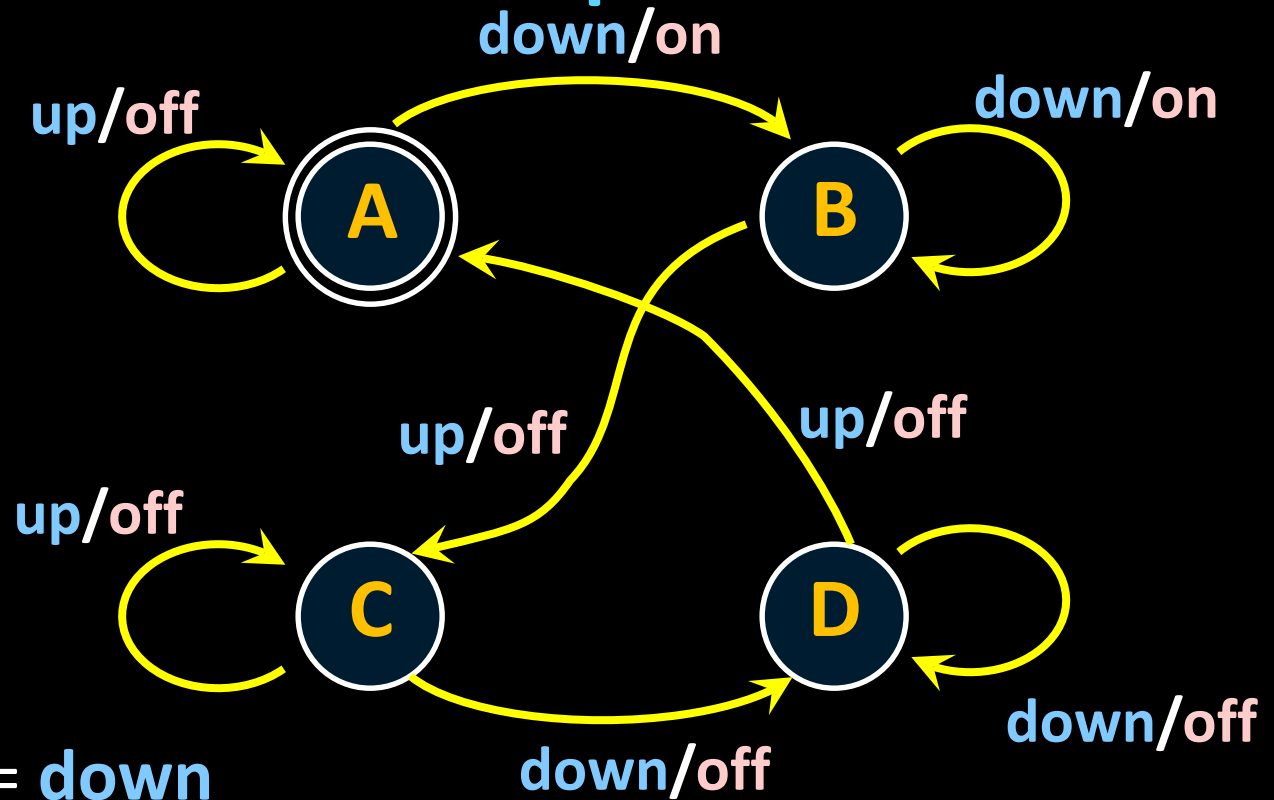
 


Input: = **up** or = **down**

Output: = **on** or = **off**

States: = **A**, = **B**, = **C**, or = **D**

FSM Example

  


Input: **0**=up or **1**=down

Output: **1**=on or **0**=off

States: **00**=A, **01**=B, **10**=C, or **11**=D

Mealy Machine


General Case: Mealy Machine

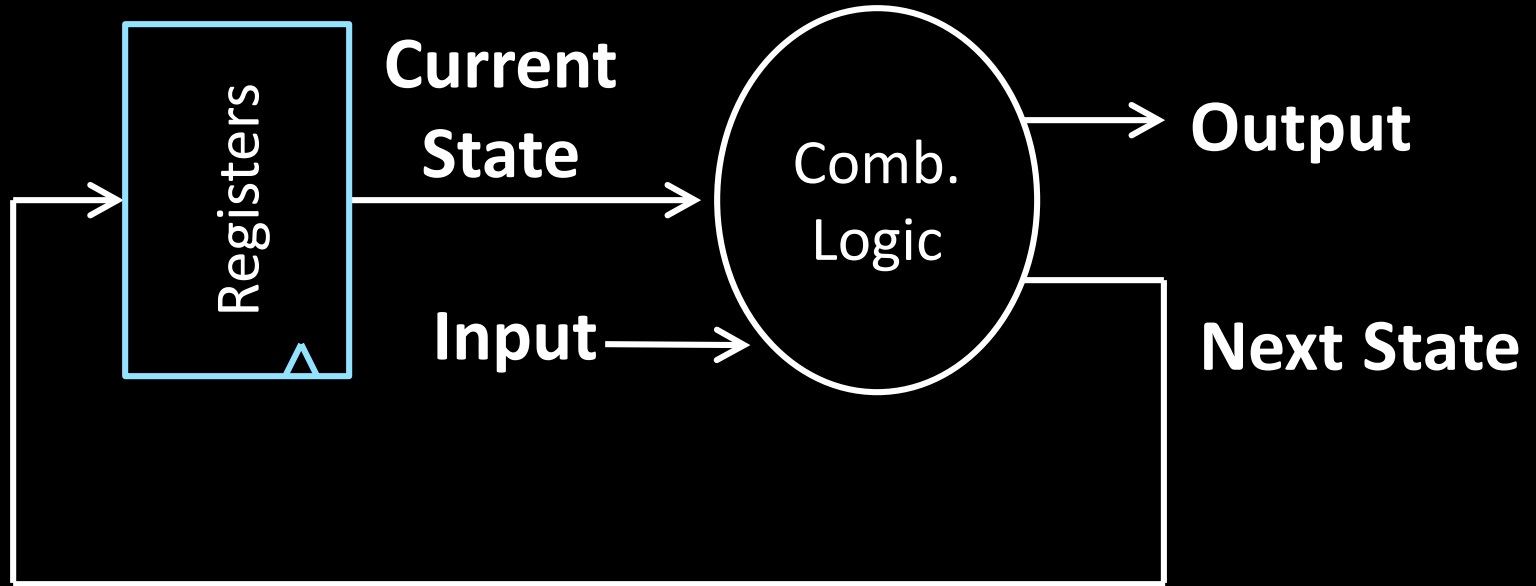

Outputs and next state depend on both current state and input



Moore Machine

Special Case: Moore Machine

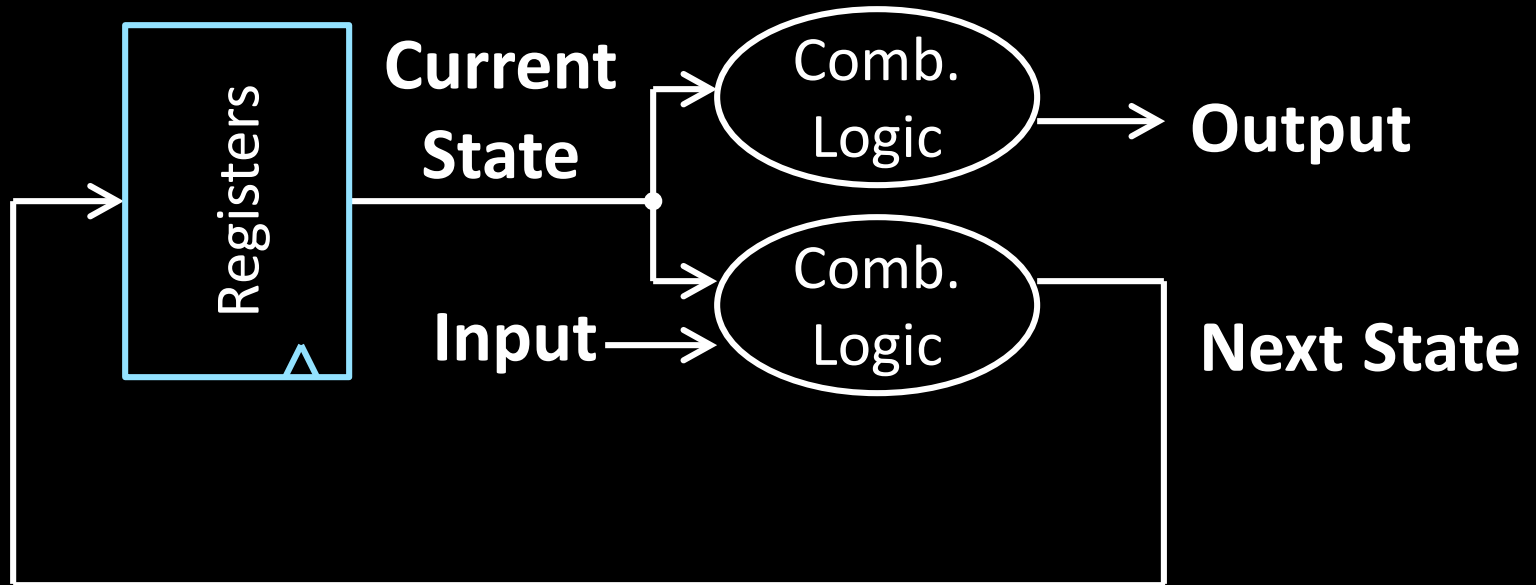

Outputs depend only on current state

Moore Machine FSM Example

 
 


Input: **up** or **down**

Output: **on** or **off**

States: **A**, **B**, **C**, or **D**

Mealy Machine FSM Example

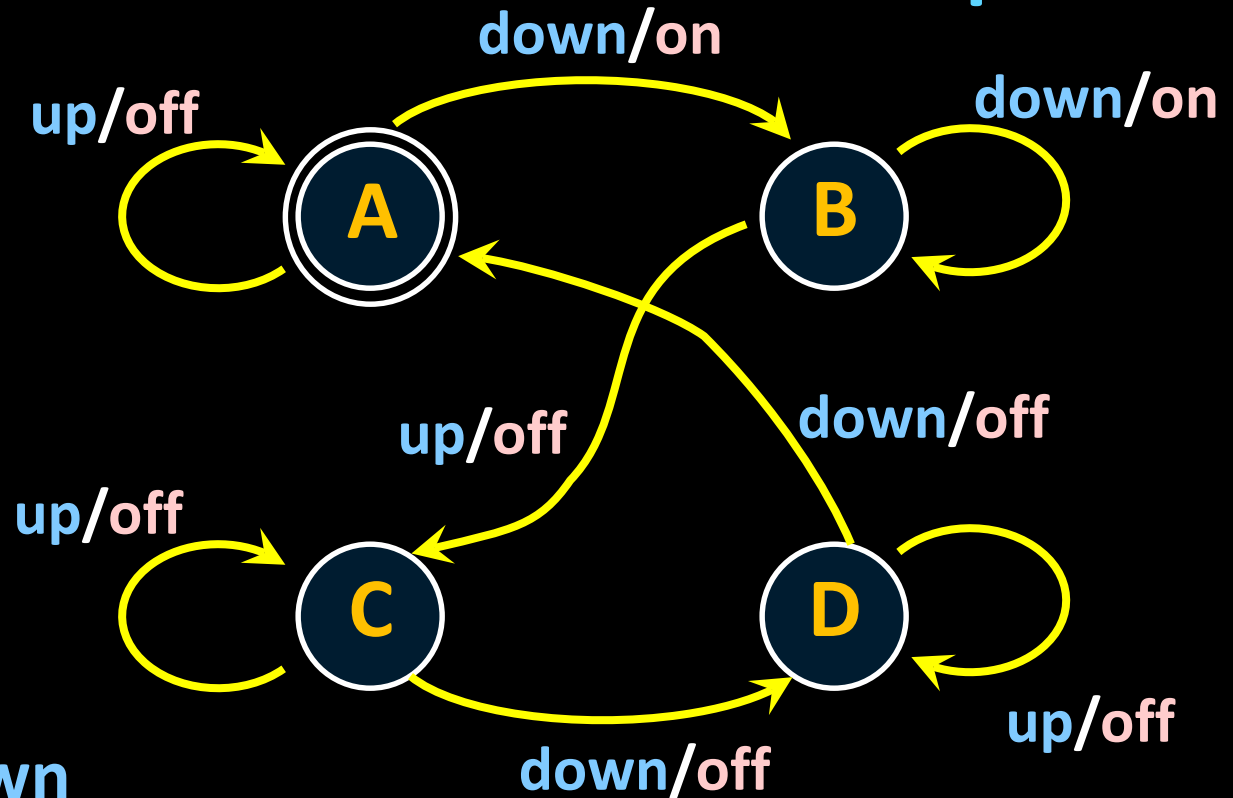 

Input: **up** or **down**


Output: **on** or **off**

States: **A**, **B**, **C**, or **D**

Activity#2: Create a Logic Circuit for a Serial Adder

Add two infinite input bit streams

 
- streams are sent with least-significant-bit (lsb) first
- How many states are needed to represent FSM?
- Draw and Fill in FSM diagram



Strategy:

- (1) Draw a state diagram (e.g. Mealy Machine)
- (2) Write output and next-state tables
- (3) Encode states, inputs, and outputs as bits
- (4) Determine logic equations for next state and outputs

FSM: State Diagram


 


 states:

Inputs: ??? and ???

Output: ???

FSM: State Diagram

  


___ states:

Inputs: ??? and ???

Output: ???


FSM: State Diagram

 

??	??	Current state	?	Next state

(2) Write down all input and state combinations

FSM: State Diagram

 

??	??	Current state	?	Next state

(3) Encode states, inputs, and outputs as bits

FSM: State Diagram

??	??	Current state	?	Next state

(4) Determine logic equations for next state and outputs

Example: Digital Door Lock



Digital Door Lock

Inputs:

- keycodes from keypad
- clock

Outputs:

- “unlock” signal
- display how many keys pressed so far

Door Lock: Inputs

Assumptions:

- signals are synchronized to clock
- Password is B-A-B




K	A	B	Meaning
0	0	0	∅ (no key)
1	1	0	'A' pressed
1	0	1	'B' pressed

Door Lock: Outputs

Assumptions:


- High pulse on U unlocks door

 

Strategy:


- (1) Draw a state diagram (e.g. Moore Machine)
- (2) Write output and next-state tables
- (3) Encode states, inputs, and outputs as bits
- (4) Determine logic equations for next state and outputs

Door Lock: Simplified State Diagram

 

(1) Draw a state diagram (e.g. Moore Machine)


Door Lock: Simplified State Diagram

 

Cur. State	Output

(2) Write output and next-state tables


Door Lock: Simplified State Diagram

 

Cur. State	Input	Next State


(2) Write output and next-state tables

Door Lock: Implementation

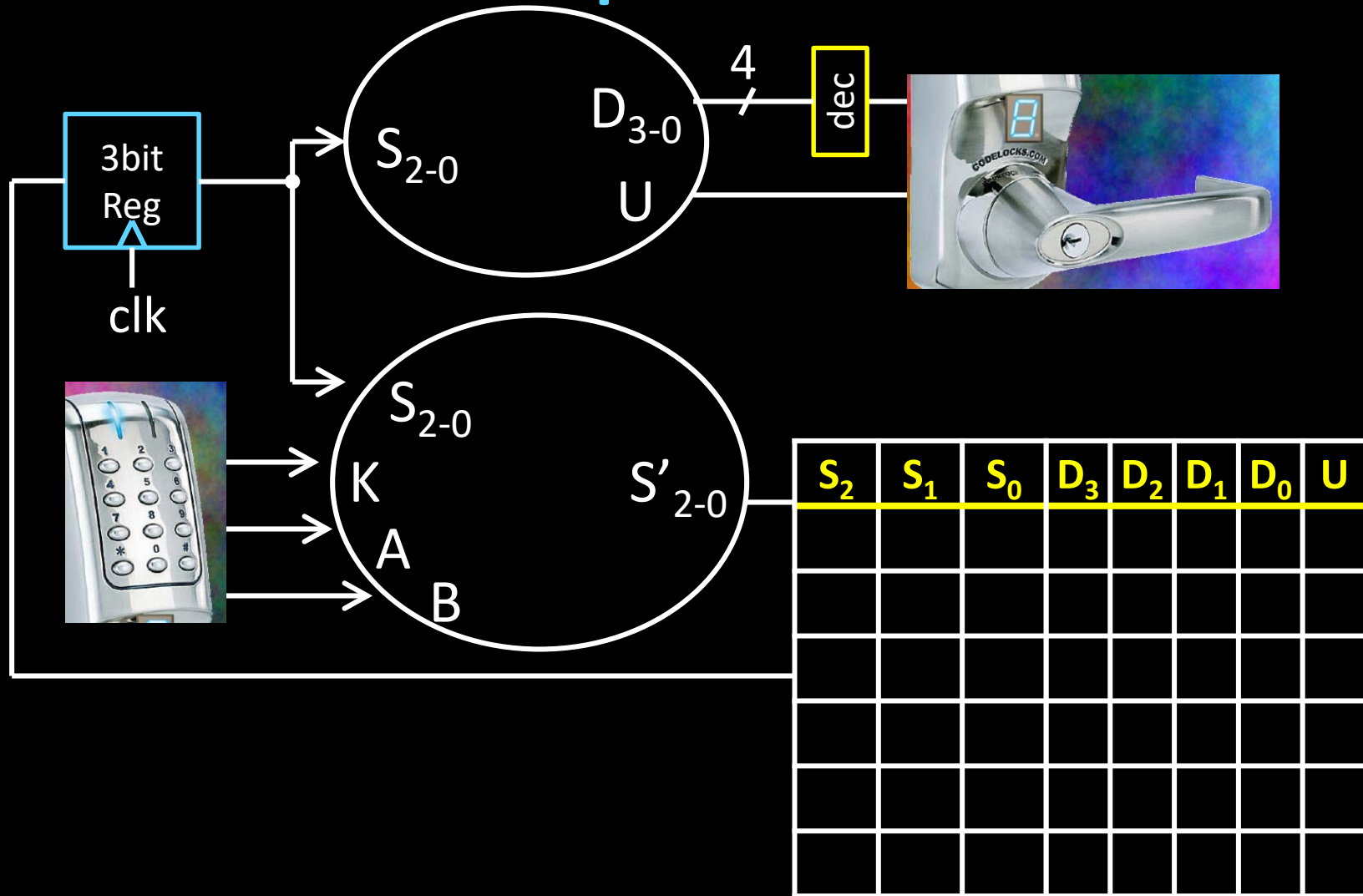


(4) Determine logic equations for next state and outputs

The diagram illustrates a 3-bit register (Reg) that receives a clock signal (clk) and outputs a 3-bit value. This value is connected to two state machines, both labeled S_{2-0} . The first state machine has inputs S_{2-0} and K . The second state machine has inputs S_{2-0} , A , and B . The output of the second state machine is connected back to the clock signal (clk).

 [illegible]

(4) Determine logic equations for next state and outputs


Door Lock: Implementation

 

Strategy:

- (1) Draw a state diagram (e.g. Moore Machine)
- (2) Write output and next-state tables
- (3) Encode states, inputs, and outputs as bits
- (4) Determine logic equations for next state and outputs

Door Lock: Implementation

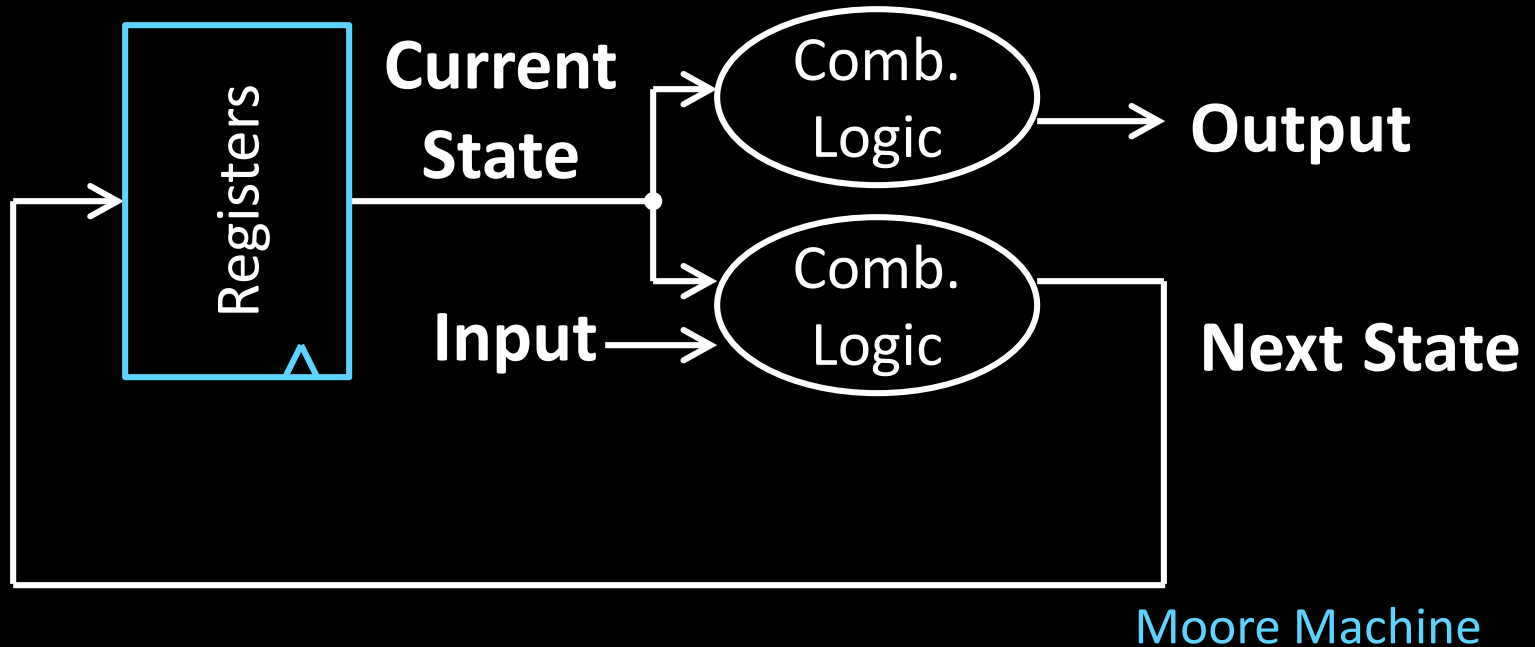

Strategy:

- (1) Draw a state diagram (e.g. Moore Machine)
- (2) Write output and next-state tables
- (3) Encode states, inputs, and outputs as bits
- (4) Determine logic equations for next state and outputs

Goals for today

Review

- Finite State Machines

Summary

We can now build interesting devices with sensors

- Using combinational logic

We can also store data values

- Stateful circuit elements (D Flip Flops, Registers, ...)
- State Machines or Ad-Hoc Circuits