

# Memory

**Hakim Weatherspoon**

**CS 3410**

Computer Science

Cornell University

The slides are the product of many rounds of teaching CS 3410 by Professors Weatherspoon, Bala, Bracy, and Sirer.

# Memory

**Hakim Weatherspoon**


**CS 3410**

Computer Science

Cornell University

The slides are the product of many rounds of teaching CS 3410 by Professors Weatherspoon, Bala, Bracy, and Sirer.

# Big Picture: Building a Processor

 

A Single cycle processor

# Goals for today

## Memory

- CPU: Register Files (i.e. Memory w/in the CPU)
- Scaling Memory: Tri-state devices
- Cache: SRAM (Static RAM—random access memory)
- Memory: DRAM (Dynamic RAM)

# Goal:


How do we store results from ALU computations?

How do we use stored results in subsequent operations?

## Register File

How does a Register File work? How do we design it?

# Big Picture: Building a Processor

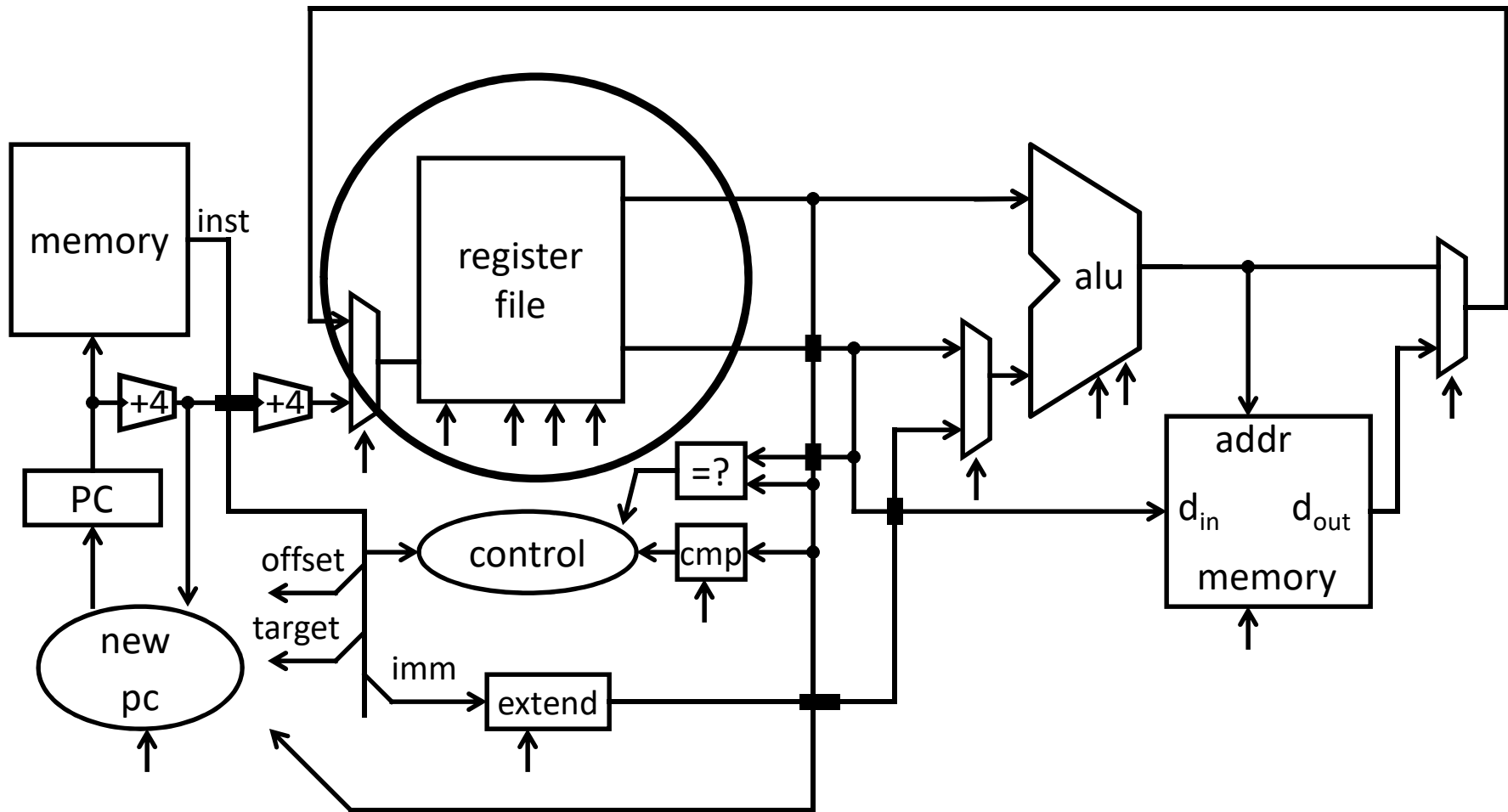


A Single cycle processor

# Register File
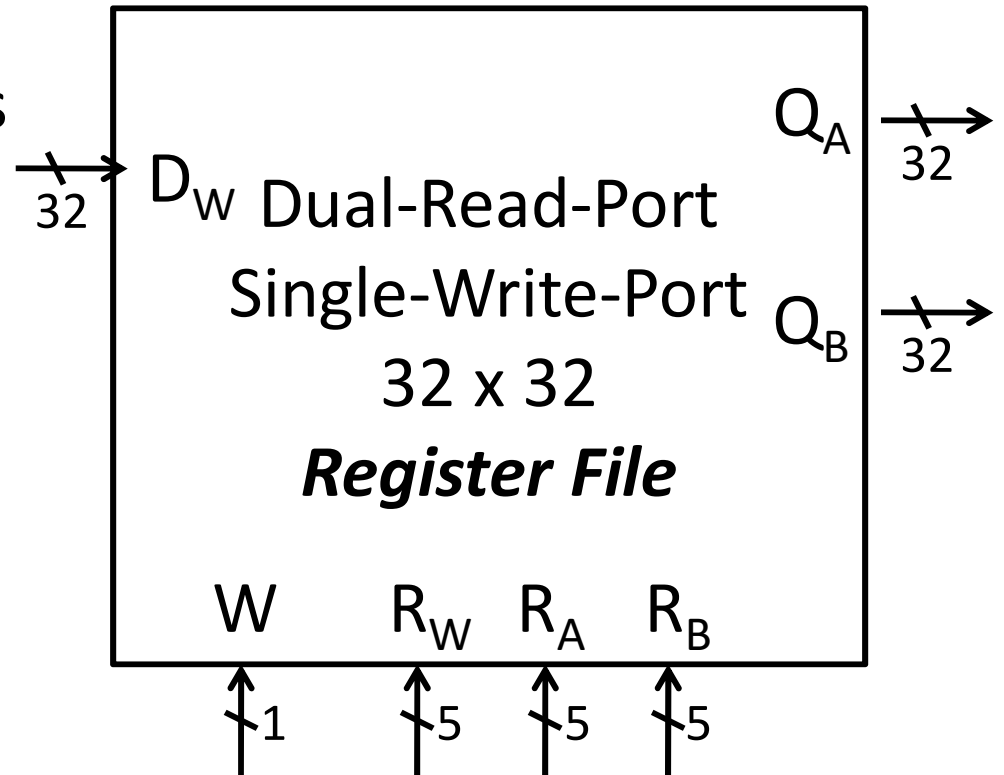
## Register File



- N read/write registers
- Indexed by register number


  
# Register File

Recall: Register

- D flip-flops in parallel
- shared clock
- extra clocked inputs: write\_enable, reset, ...






  
# Register File

Recall: Register


- D flip-flops in parallel
- shared clock
- extra clocked inputs: write\_enable, reset, ...



# Register File
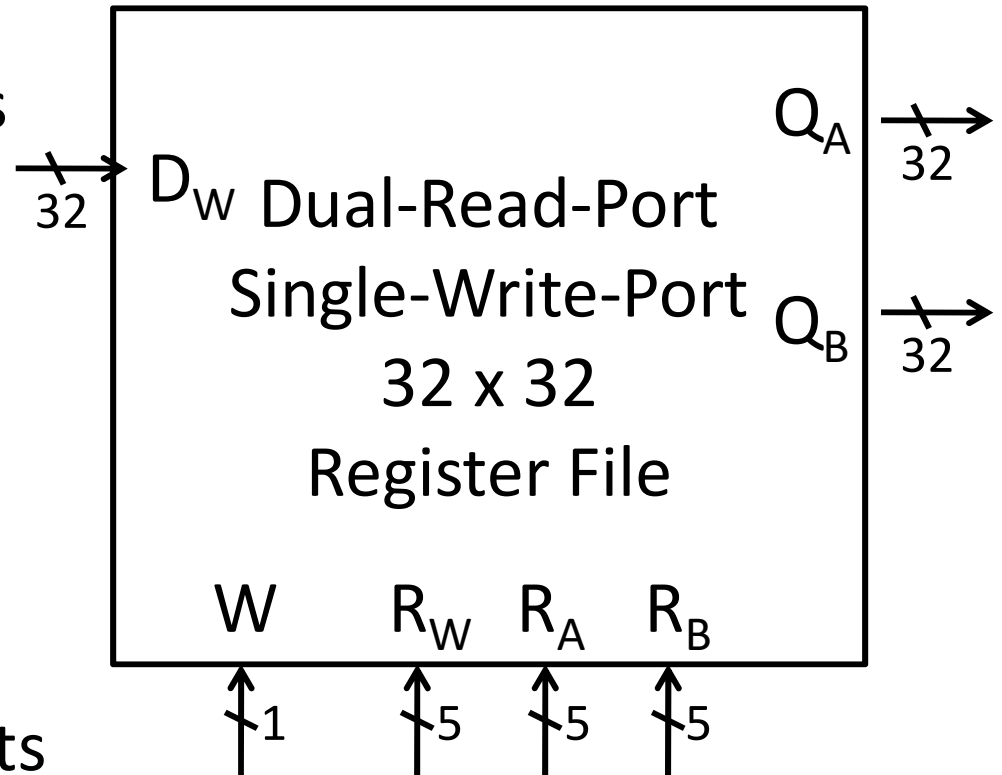
## Register File

- N read/write registers
- Indexed by register number



## Implementation:

- D flip flops to store bits
- Decoder for each write port
- Mux for each read port

# Tradeoffs


## Register File tradeoffs

- + Very fast (a few gate delays for both read and write)
- + Adding extra ports is straightforward
- Doesn't scale

e.g. 32Mb register file with  
32 bit registers

Need 32x 1M-to-1 multiplexor  
and 32x 20-to-1M decoder

How many logic gates/transistors?

 

# Takeaway

Register files are very fast storage (only a few gate delays), but does not scale to large memory sizes.

# Goals for today

## Memory

- CPU: Register Files (i.e. Memory w/in the CPU)
- Scaling Memory: Tri-state devices
- Cache: SRAM (Static RAM—random access memory)
- Memory: DRAM (Dynamic RAM)


# Next Goal

How do we scale/build larger memories?
 
# Building Large Memories

Need a shared bus (or shared bit line)

- Many FlipFlops/outputs/etc. connected to single wire
- Only one output *drives* the bus at a time




- How do we build such a device?

# Tri-State Devices
 
## Tri-State Buffers

- If enabled ( $E=1$ ), then  $Q = D$
- Otherwise,  $Q$  is not connected ( $z = \text{high impedance}$ )




E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1




# Tri-State Devices
 
## Tri-State Buffers

- If enabled ( $E=1$ ), then  $Q = D$
- Otherwise,  $Q$  is not connected ( $z = \text{high impedance}$ )




E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

 


# Tri-State Devices
 
## Tri-State Buffers


- If enabled ( $E=1$ ), then  $Q = D$
- Otherwise,  $Q$  is not connected ( $z = \text{high impedance}$ )



E	D	Q
0	0	z
0	1	z
1	0	0
1	1	1

 

# Shared Bus

 

# Takeaway

Register files are very fast storage (only a few gate delays), but does not scale to large memory sizes.

Tri-state Buffers allow scaling since multiple registers can be connected to a single output, while only one register actually drives the output.

# Goals for today

## Memory

- CPU: Register Files (i.e. Memory w/in the CPU)
- Scaling Memory: Tri-state devices
- Cache: SRAM (Static RAM—random access memory)
- Memory: DRAM (Dynamic RAM)

# Next Goal


How do we build large memories?

Use similar designs as Tri-state Buffers to connect multiple registers to output line. Only one register will drive output line.

# SRAM
 
## Static RAM (SRAM)—Static Random Access Memory


- Essentially just D-Latches plus Tri-State Buffers
- A decoder selects which line of memory to access (i.e. word line)
- A R/W selector determines the type of access
- That line is then coupled to the data lines



# SRAM
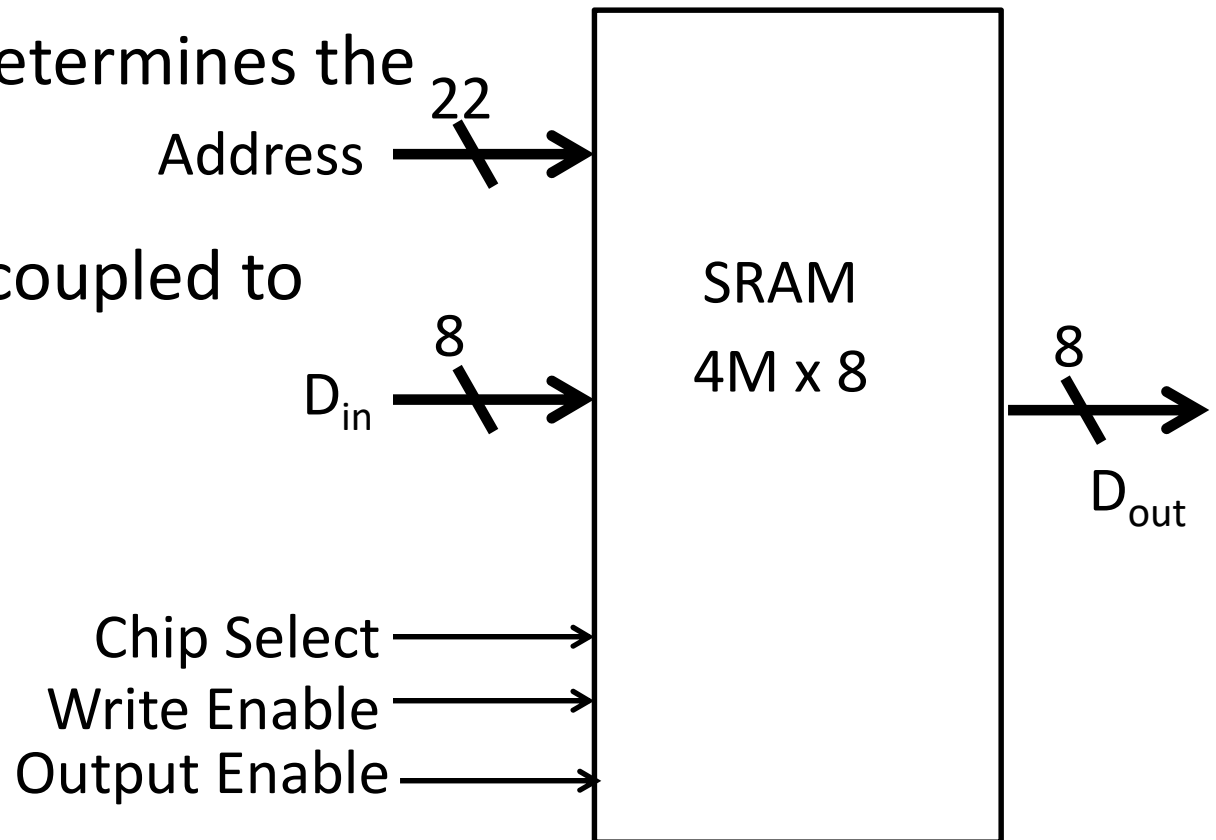
## Static RAM (SRAM)—Static Random Access Memory

- Essentially just D-Latches plus Tri-State Buffers
- A decoder selects which line of memory to access (i.e. word line)
- A R/W selector determines the type of access
- That line is then coupled to the data lines





 
# SRAM

E.g. How do we design  
a 4 x 2 SRAM Module?


(i.e. 4 word lines that are  
each 2 bits wide)?



# SRAM

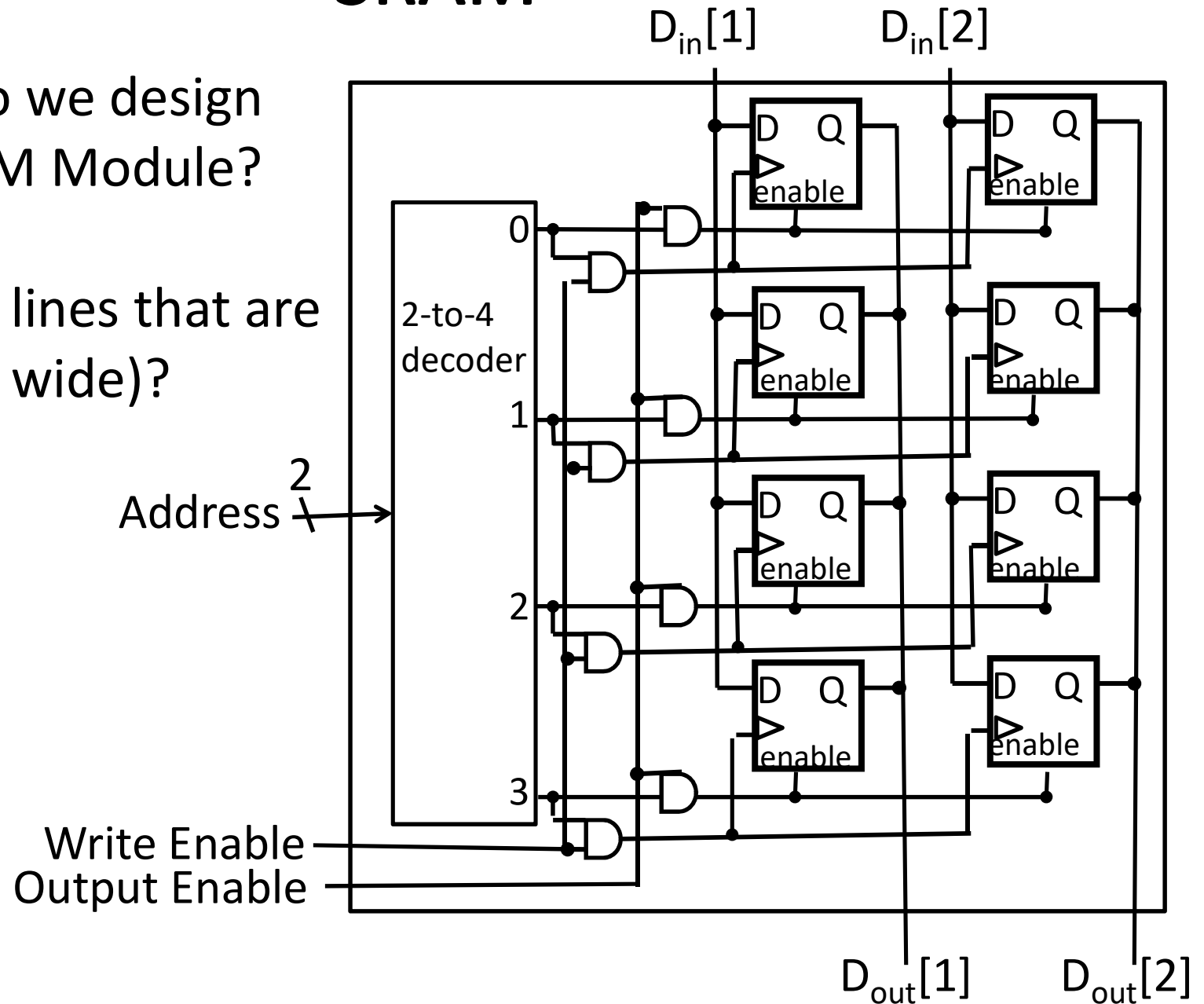
## E.g. How do we design a 4 x 2 SRAM Module?

(i.e. 4 word lines that are each 2 bits wide)?




The diagram illustrates a 2-to-4 decoder-based SRAM array. On the left, a 2-to-4 decoder takes two address inputs (labeled 0 and 1) and produces four word lines (labeled 0, 1, 2, and 3). Each word line is connected to the enable input of a 2x4 grid of D flip-flops. The flip-flops are organized into two columns. The first column's D inputs are connected to a common data input line,  $D_{in}[1]$ , and its Q outputs are connected to a common data output line,  $D_{out}[1]$ . The second column's D inputs are connected to a common data input line,  $D_{in}[2]$ , and its Q outputs are connected to a common data output line,  $D_{out}[2]$ . The word lines are also connected to the D inputs of the flip-flops in the first column via AND gates. The bit lines are connected to the Q outputs of the flip-flops in the second column via AND gates. The word lines are also connected to the D inputs of the flip-flops in the second column via AND gates. The bit lines are connected to the Q outputs of the flip-flops in the first column via AND gates. The word lines are also connected to the D inputs of the flip-flops in the first column via AND gates. The bit lines are connected to the Q outputs of the flip-flops in the second column via AND gates.

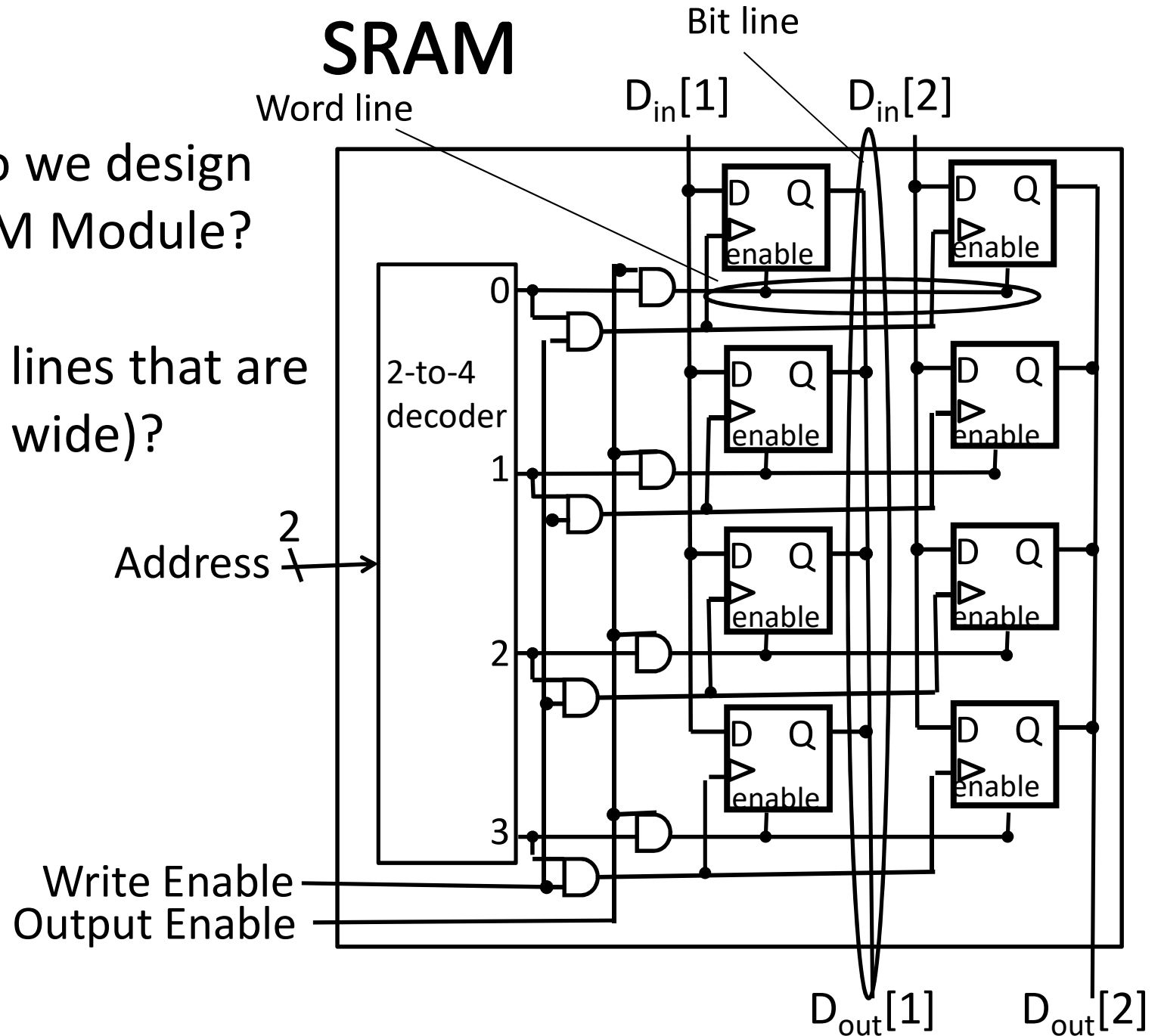(i.e. 4 word lines that are each 2 bits wide)?



# SRAM Cell

Typical SRAM Cell

 


Each cell stores one bit, and requires 4 – 8 transistors (6 is typical)
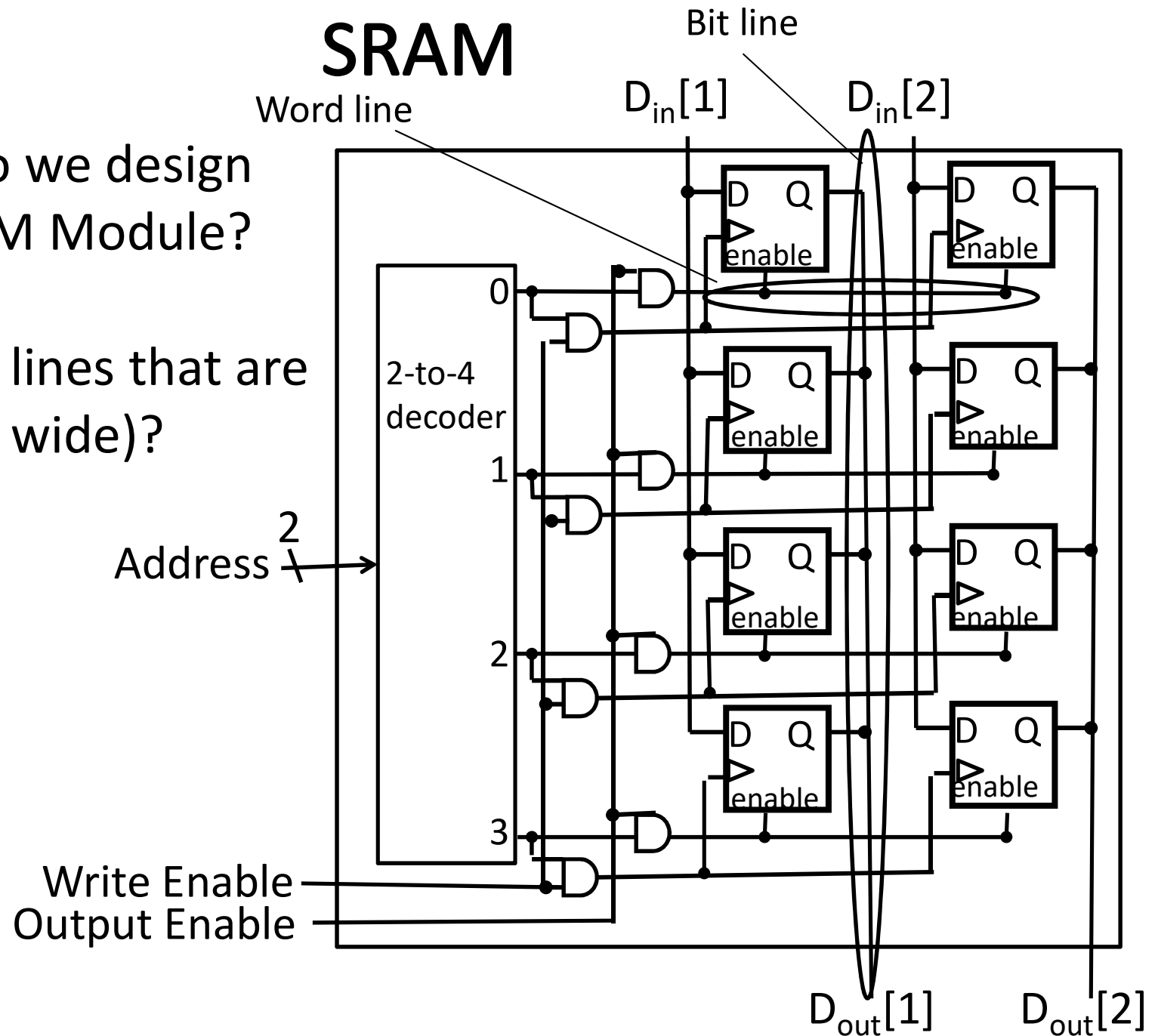
# SRAM

E.g. How do we design  
a 4 x 2 SRAM Module?


(i.e. 4 word lines that are  
each 2 bits wide)?


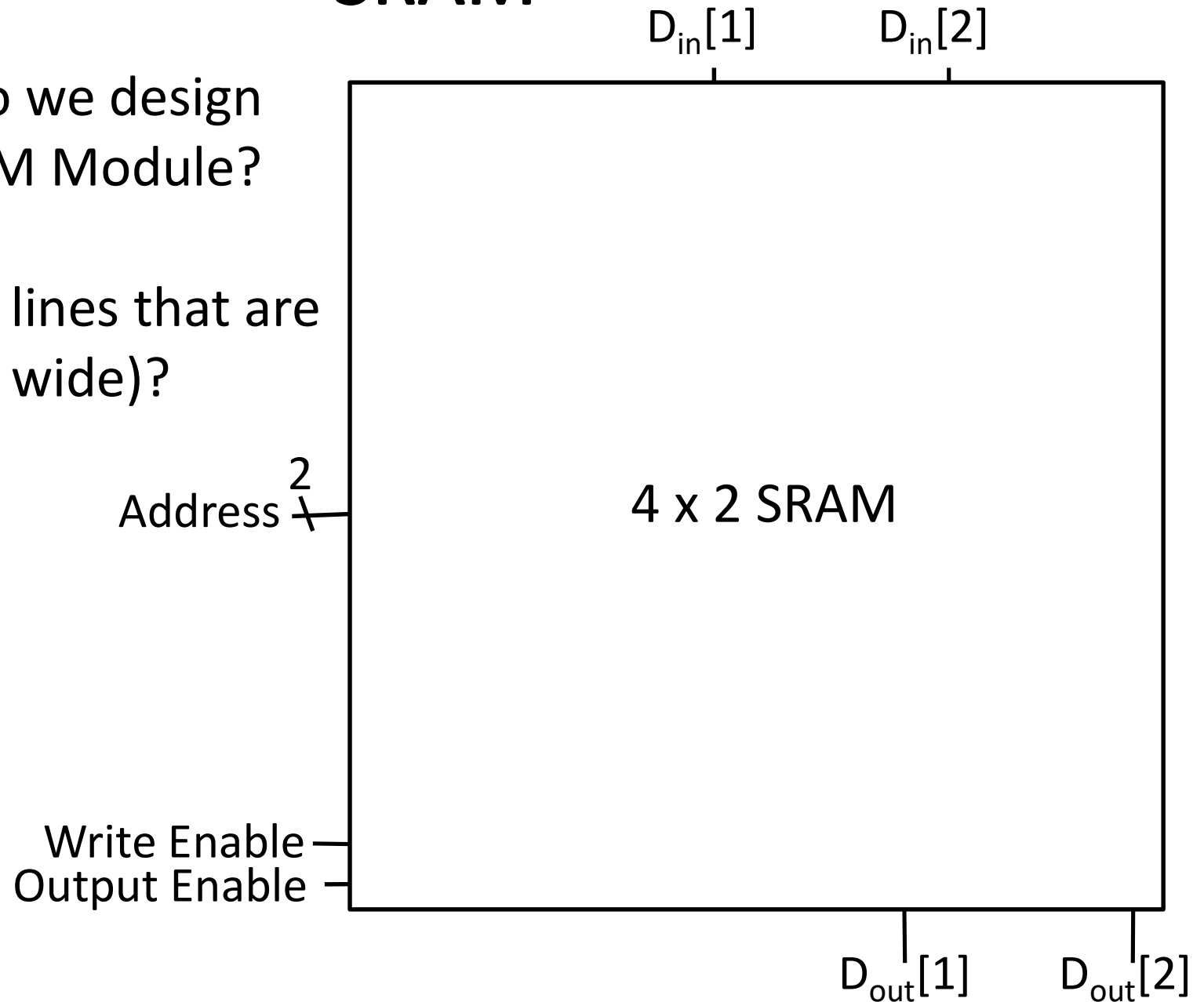
# SRAM

E.g. How do we design  
a 4 x 2 SRAM Module?


(i.e. 4 word lines that are  
each 2 bits wide)?


 
# SRAM


E.g. How do we design  
a **4M x 8** SRAM Module?

(i.e. 4M word lines that  
are each 8 bits wide)?


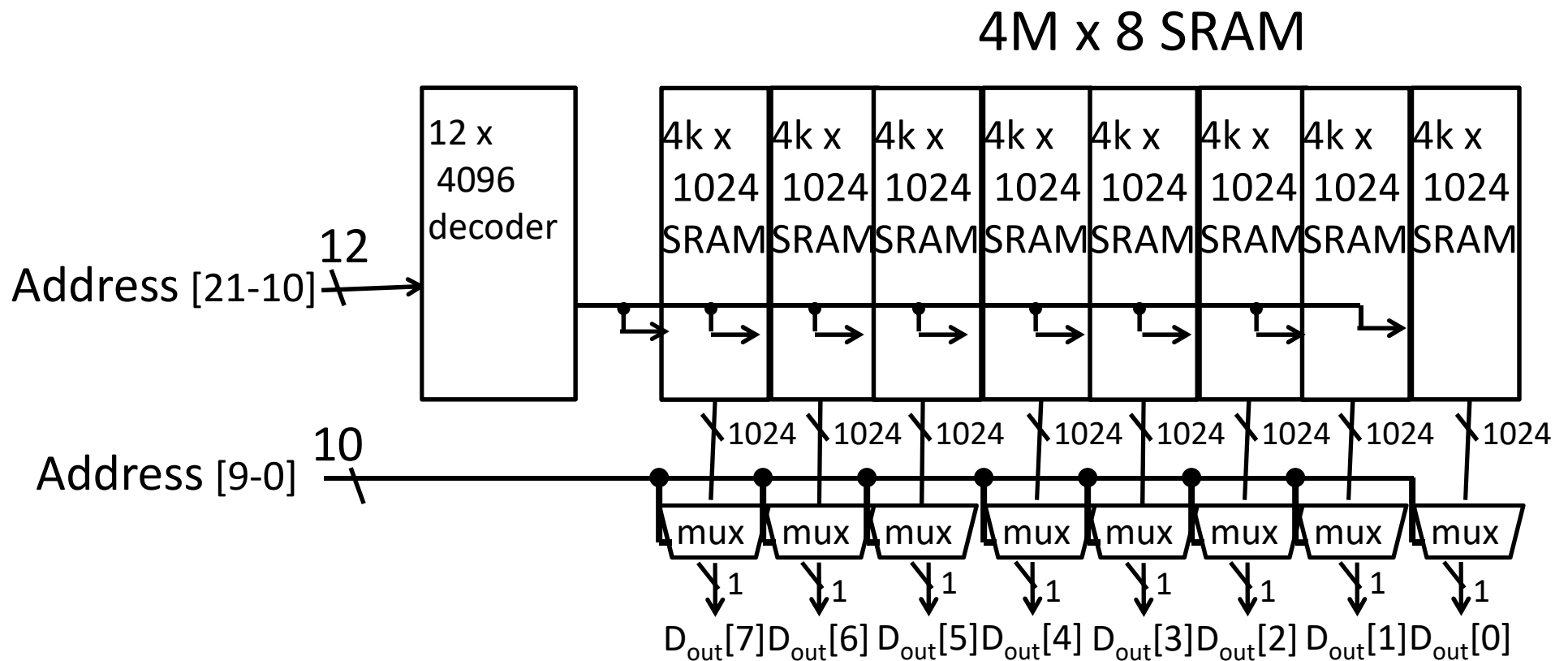
# SRAM


E.g. How do we design  
a **4M x 8** SRAM Module?





 
# SRAM

E.g. How do we design  
a **4M x 8** SRAM Module?



# SRAM Modules and Arrays

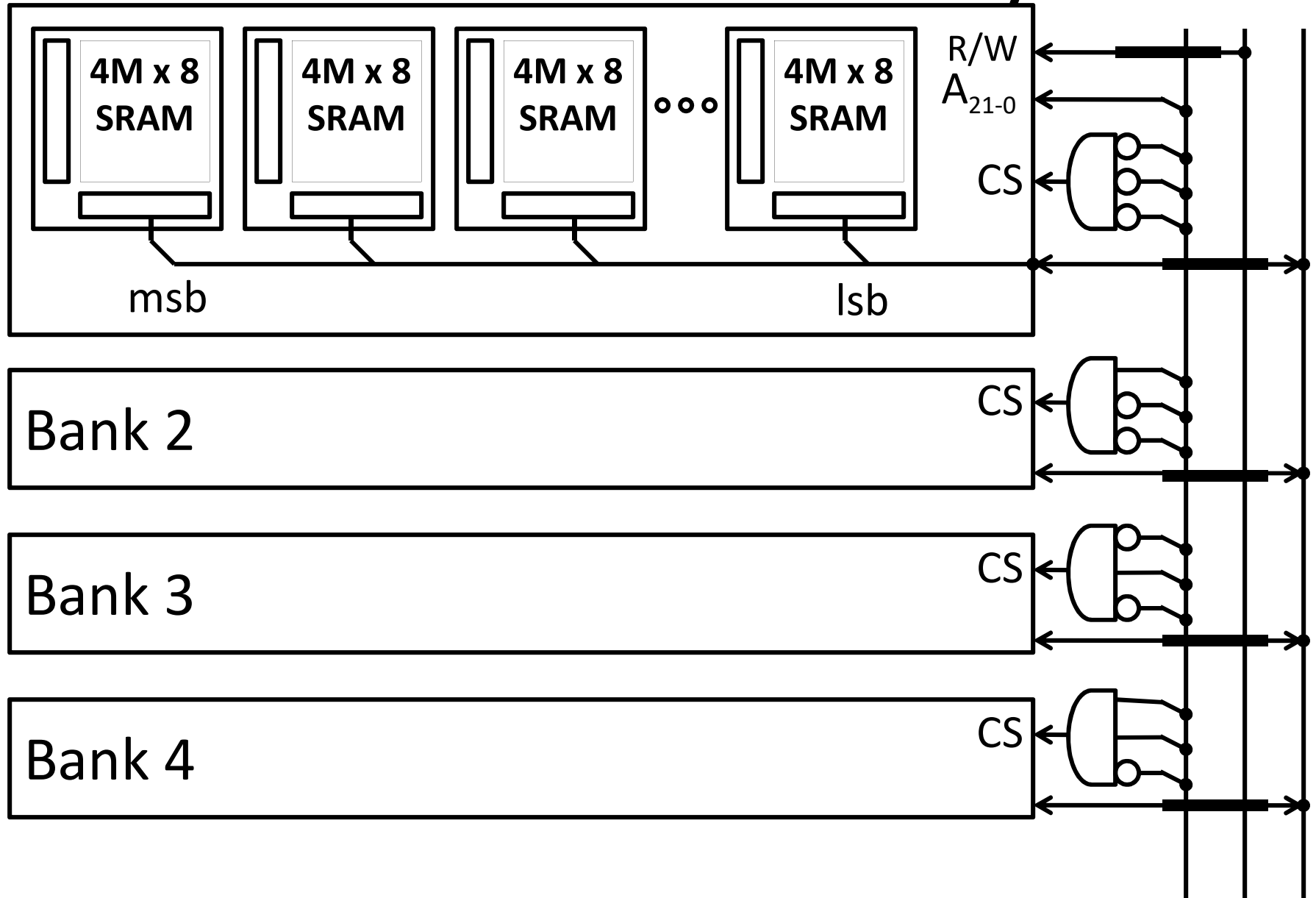

# SRAM Summary


## SRAM

- A few transistors ( $\sim 6$ ) per cell
- Used for working memory (caches)
- But for even higher density...

# Dynamic RAM: DRAM

## Dynamic-RAM (DRAM)

- Data values require constant refresh

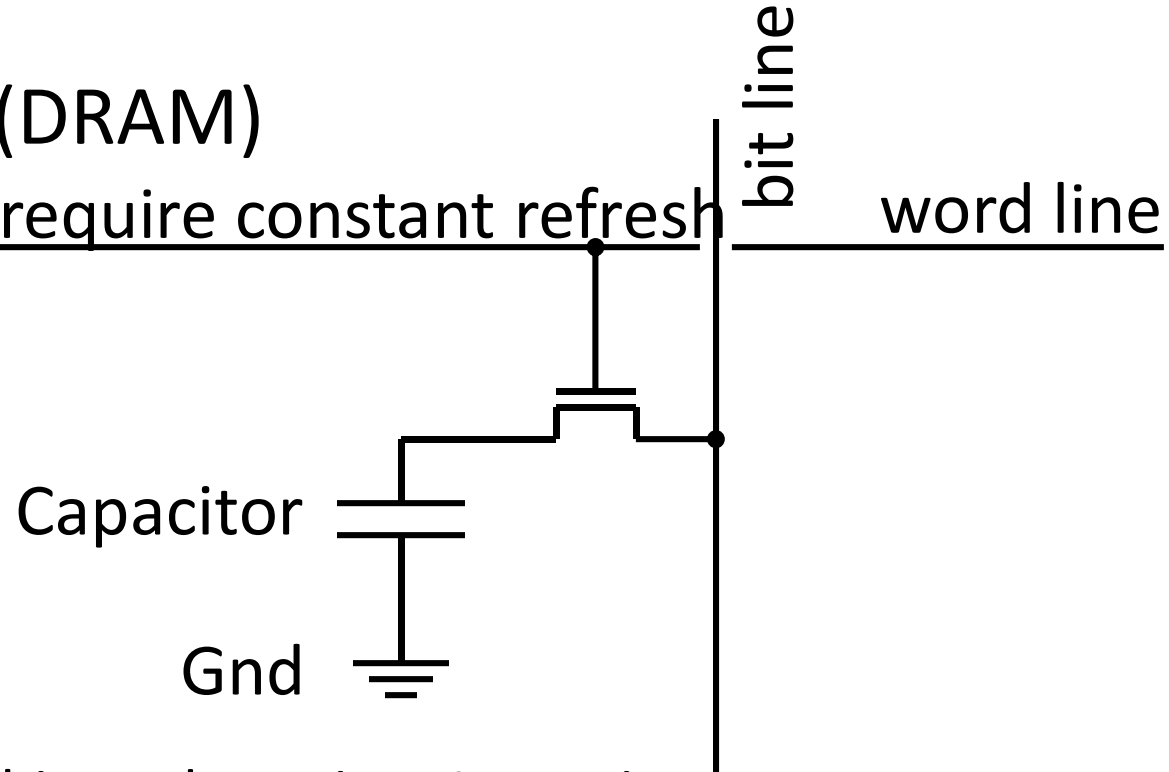


Each cell stores one bit, and requires 1 transistors

# Dynamic RAM: DRAM

Dynamic-RAM (DRAM)

- Data values require constant refresh

 

Each cell stores one bit, and requires 1 transistors

# DRAM vs. SRAM

Single transistor vs. many gates

- Denser, cheaper (\$30/1GB vs. \$30/2MB)
- But more complicated, and has analog sensing

Also needs refresh

- Read and write back...
- ...every few milliseconds
- Organized in 2D grid, so can do rows at a time
- Chip can do refresh internally

Hence... slower and energy inefficient

# Memory

## Register File tradeoffs

- + Very fast (a few gate delays for both read and write)
- + Adding extra ports is straightforward
- Expensive, doesn't scale
- Volatile

## Volatile Memory alternatives: SRAM, DRAM, ...

- Slower
- + Cheaper, and scales well
- Volatile

## Non-Volatile Memory (NV-RAM): Flash, EEPROM, ...

- + Scales well
- Limited lifetime; degrades after 100000 to 1M writes

# Summary

We now have enough building blocks to build machines that can perform non-trivial computational tasks

Register File: Tens of words of working memory

SRAM: Millions of words of working memory

DRAM: Billions of words of working memory

NVRAM: long term storage

(usb fob, solid state disks, BIOS, ...)

Next time we will build a simple processor!