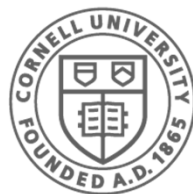


# Gates and Logic: From Transistors to Logic Gates and Logic Circuits

**Prof. Hakim Weatherspoon**  
**CS 3410**

Computer Science  
Cornell University



**Cornell CIS**  
COMPUTING AND INFORMATION SCIENCE

[Weatherspoon, Bala, Bracy, and Sirer]

# Goals for Today

- From Switches to Logic Gates to Logic Circuits
- Logic Gates
  - From switches
  - Truth Tables
- Logic Circuits
  - From Truth Tables to Circuits (Sum of Products)
  - Identity Laws
- Logic Circuit Minimization
  - Algebraic Manipulations
  - Truth Tables (Karnaugh Maps)
- Transistors (electronic switch)




# A switch




Acts as a *conductor* or *insulator*.

Can be used to build amazing things...

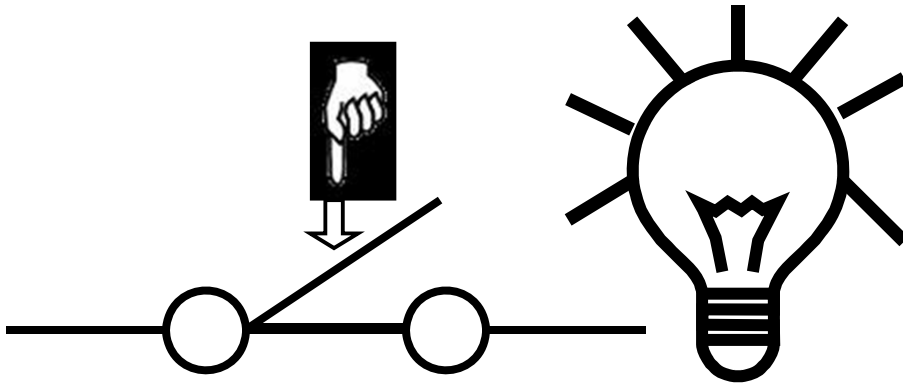


The Bombe used to break the German Enigma machine during World War II
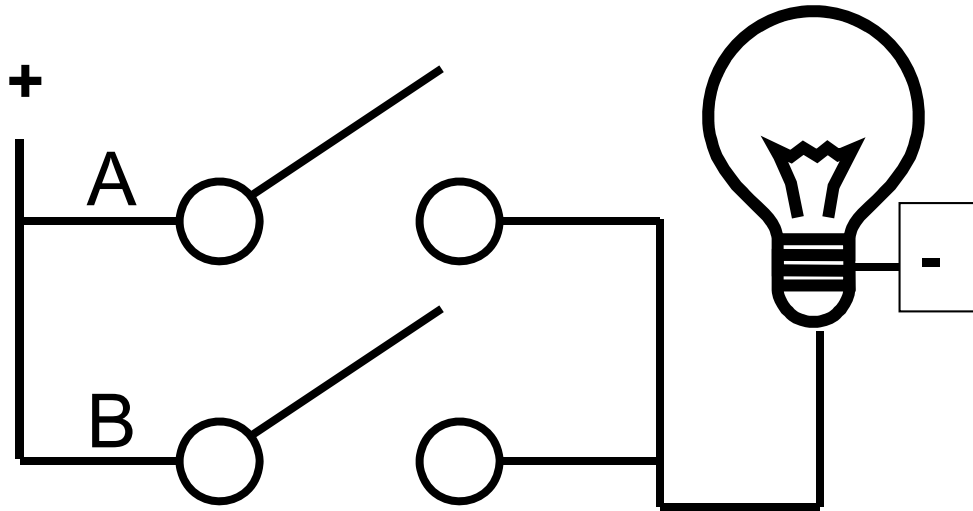
# Basic Building Blocks: Switches to Logic Gates




Truth Table

A	B	Light
OFF	OFF	
OFF	ON	
ON	OFF	
ON	ON	

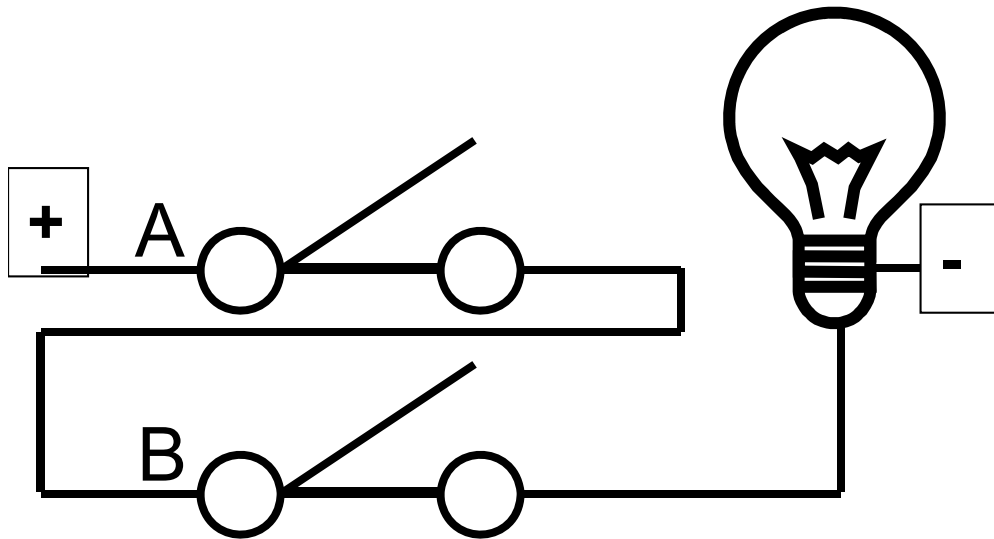

A	A	B	B	Light	Light
OFF	OFF	OFF	OFF		
OFF	OFF	ON	ON		
ON	ON	OFF	OFF		
ON	ON	ON	ON		

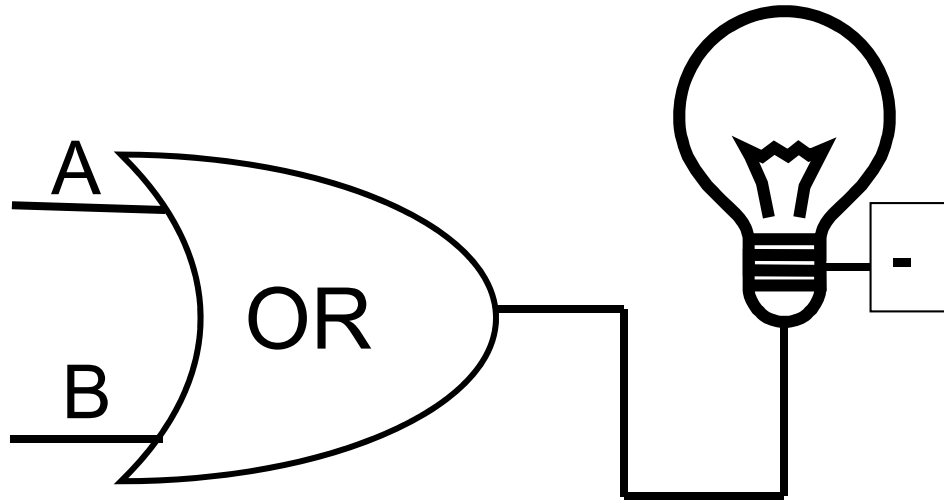
# Basic Building Blocks: Switches to Logic Gates



- Either (OR)

Truth Table


A	B	Light
OFF	OFF	
OFF	ON	
ON	OFF	
ON	ON	

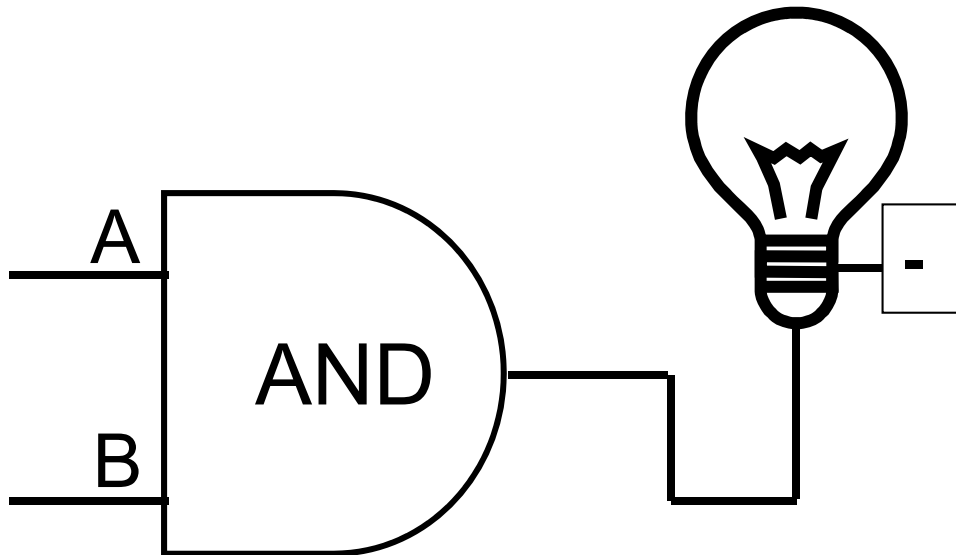

- Both (AND)

A	A	B	B	Light	Light
OFF	OFF	OFF	OFF		
OFF	OFF	ON	ON		
ON	ON	OFF	OFF		
ON	ON	ON	ON		
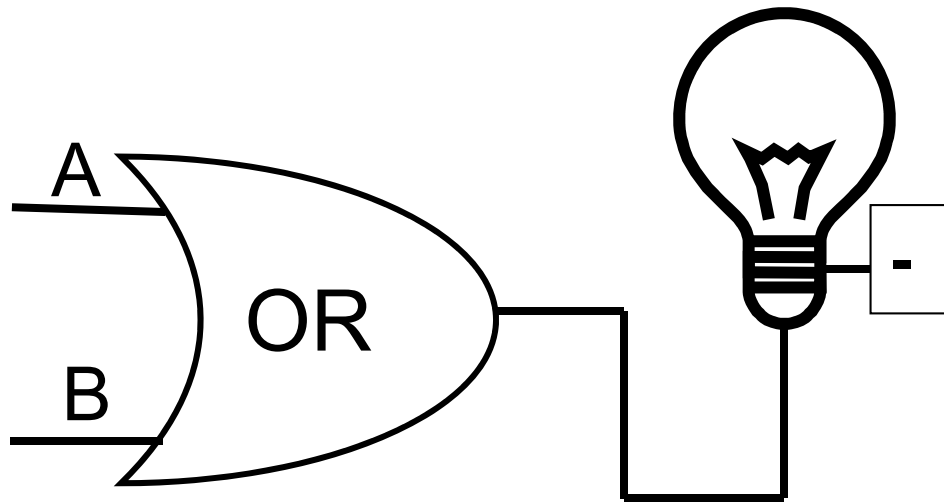
# Basic Building Blocks: Switches to Logic Gates




- Either (OR)

Truth Table

A	B	Light
OFF	OFF	
OFF	ON	
ON	OFF	
ON	ON	


0 = OFF  
1 = ON

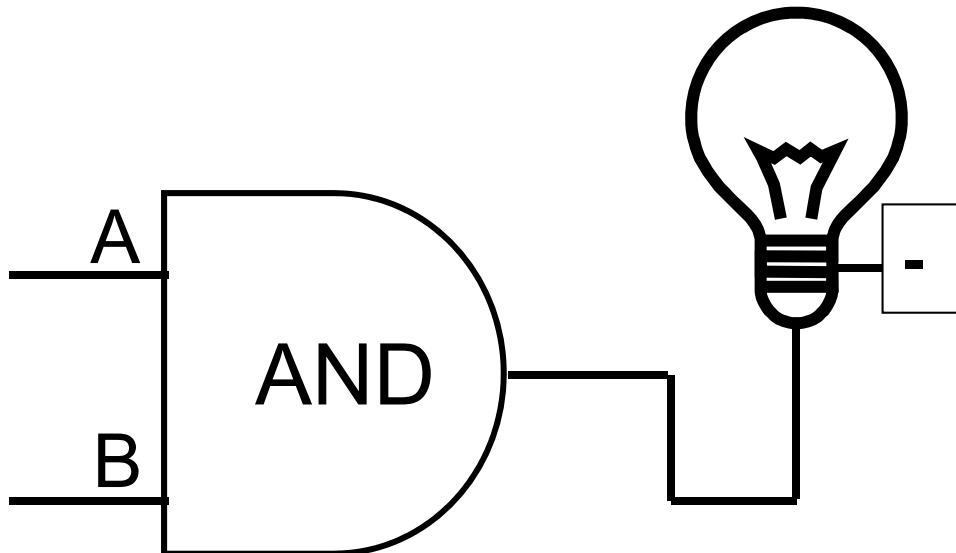


- Both (AND)

A	B	Light
0	0	
0	1	
1	0	
1	1	
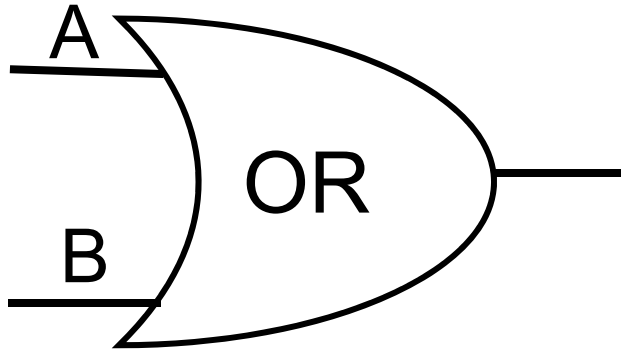
# Basic Building Blocks: Switches to Logic Gates



**George Boole (1815-1864)**

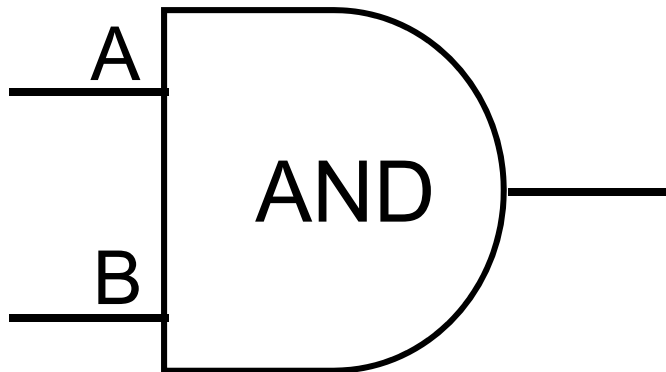

- Did you know?
- George Boole: Inventor of the idea of logic gates. He was born in Lincoln, England and he was the son of a shoemaker in a low class family.

# Takeaway


- Binary (two symbols: true and false) is the basis of Logic Design






# Building Functions: Logic Gates

- NOT:

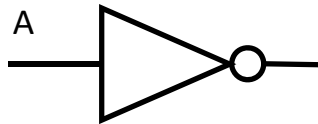


A	Out
0	1
1	0

- AND:

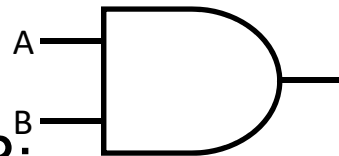


A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1

- OR:

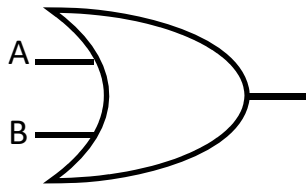


A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1

NAND:

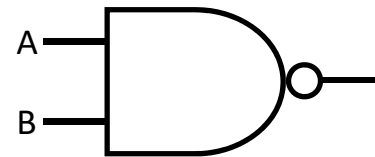

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

NOR:

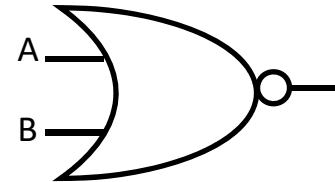

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

- Logic Gates

- digital circuit that either allows a signal to pass through it or not.
- Used to build logic functions
- There are seven basic logic gates:

AND, OR, **NOT**,

NAND (not AND), NOR (not OR), XOR, and XNOR (not XOR) [later]

# Goals for Today

- From Switches to Logic Gates to Logic Circuits
- Logic Gates
  - From switches
  - Truth Tables
- Logic Circuits
  - From Truth Tables to Circuits (Sum of Products)
  - Identity Laws
- Logic Circuit Minimization
  - Algebraic Manipulations
  - Truth Tables (Karnaugh Maps)
- Transistors (electronic switch)




# Next Goal

- Given a Logic function, create a Logic Circuit that implements the Logic Function...
- ...and, *with the minimum number of logic gates*
- Fewer gates: A cheaper (\$\$\$) circuit!




# Logic Gates

NOT:

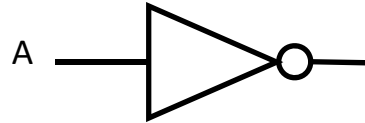


A	Out
0	1
1	0

AND:

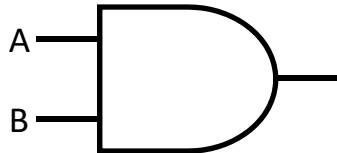


A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1

NAND:

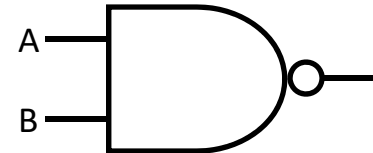


A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

OR:

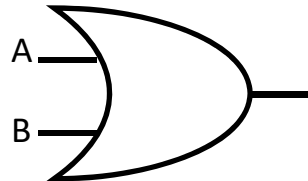


A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1

NOR:

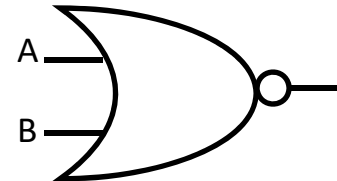


A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

XOR:

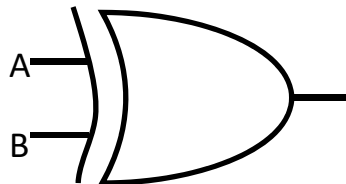

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0

XNOR:

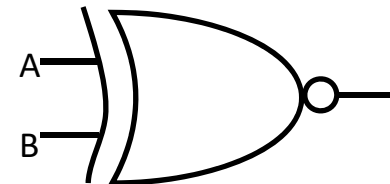

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	1

# Logic Implementation

- How to implement a desired logic function?

a	b	c	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

# Logic Implementation

- How to implement a desired logic function?

a	b	c	out	minterm
0	0	0	0	$\bar{a} \bar{b} \bar{c}$
0	0	1	1	$\bar{a} \bar{b} c$
0	1	0	0	$\bar{a} b \bar{c}$
0	1	1	1	$\bar{a} b c$
1	0	0	0	$a \bar{b} \bar{c}$
1	0	1	1	$a \bar{b} c$
1	1	0	0	$a b \bar{c}$
1	1	1	0	$a b c$

1) Write minterms

2) sum of products:

- OR of all minterms where out=1

# Logic Equations

- NOT:

- $\text{out} = \bar{a} = !a = \neg a$

- AND:

- $\text{out} = a \cdot b = a \& b = a \wedge b$

- NAND:

- $\text{out} = \overline{a \cdot b} = !(a \& b) = \neg (a \wedge b)$

- OR:

- $\text{out} = a + b = a | b = a \vee b$

- NOR:

- $\text{out} = \overline{a + b} = !(a | b) = \neg (a \vee b)$

- XOR:

- $\text{out} = a \oplus b = a\bar{b} + \bar{a}b$

- XNOR:

- $\text{out} = \overline{a \oplus b} = ab + \bar{a}\bar{b}$

- Logic Equations

- Constants: true = 1, false = 0
  - Variables: a, b, out, ...
  - Operators (above): AND, OR, NOT, etc.

# Identities

Identities useful for manipulating logic equations

- For optimization & ease of implementation

$$a + 0 =$$

$$a + 1 =$$

$$a + \bar{a} =$$

$$a \cdot 0 =$$

$$a \cdot 1 =$$

$$a \cdot \bar{a} =$$



# Identities

Identities useful for manipulating logic equations

- For optimization & ease of implementation

$$\overline{(a + b)} =$$

$$\overline{(a \cdot b)} =$$

$$a + a b =$$

$$a(b+c) =$$

$$\overline{a(b + c)} =$$

# Goals for Today

- From Switches to Logic Gates to Logic Circuits
- Logic Gates
  - From switches
  - Truth Tables
- Logic Circuits
  - From Truth Tables to Circuits (Sum of Products)
  - Identity Laws
- **Logic Circuit Minimization – *why?***
  - Algebraic Manipulations
  - Truth Tables (Karnaugh Maps)
- Transistors (electronic switch)



# Checking Equality w/Truth Tables

circuits  $\leftrightarrow$  truth tables  $\leftrightarrow$  equations

Example:  $(a+b)(a+c) = a + bc$

<b>a</b>	<b>b</b>	<b>c</b>					
<b>0</b>	<b>0</b>	<b>0</b>					
<b>0</b>	<b>0</b>	<b>1</b>					
<b>0</b>	<b>1</b>	<b>0</b>					
<b>0</b>	<b>1</b>	<b>1</b>					
<b>1</b>	<b>0</b>	<b>0</b>					
<b>1</b>	<b>0</b>	<b>1</b>					
<b>1</b>	<b>1</b>	<b>0</b>					
<b>1</b>	<b>1</b>	<b>1</b>					

# Takeaway

- Binary (two symbols: true and false) is the basis of Logic Design
- More than one Logic Circuit can implement same Logic function. Use Algebra (Identities) or Truth Tables to show equivalence.



# Goals for Today

- From Switches to Logic Gates to Logic Circuits
- Logic Gates
  - From switches
  - Truth Tables
- Logic Circuits
  - From Truth Tables to Circuits (Sum of Products)
  - Identity Laws
- Logic Circuit Minimization
  - Algebraic Manipulations
  - Truth Tables (Karnaugh Maps)
- Transistors (electronic switch)



# Karnaugh Maps

How does one find the most efficient equation?

- Manipulate algebraically until...?
- Use Karnaugh Maps (optimize visually)
- Use a software optimizer

For large circuits

- Decomposition & reuse of building blocks

# Minimization with Karnaugh maps (1)

◆ Sum of minterms yields

■ out =

a	b	c	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

# Minimization with Karnaugh maps (2)

a	b	c	out
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

		ab			
		00	01	11	10
c	0	0	0	0	1
	1	1	1	0	1

◆ Sum of minterms yields

- $out = \overline{a}\overline{b}c + \overline{a}b\overline{c} + a\overline{b}\overline{c} + a\overline{b}c$

◆ Karnaugh map minimization

- Cover all 1's
- Group adjacent blocks of  $2^n$  1's that yield a rectangular shape
- Encode the common features of the rectangle
  - ◆  $out = a\overline{b} + \overline{a}c$



# Karnaugh Minimization Tricks (1)

		ab			
		00	01	11	10
c	0	0	1	1	1
	1	0	0	1	0

◆ Minterms can overlap

■ out =

		ab			
		00	01	11	10
c	0	1	1	1	1
	1	0	0	1	0

◆ Minterms can span 2, 4, 8 or more cells

■ out =

# Karnaugh Minimization Tricks (2)

		ab			
cd		00	01	11	10
	00	0	0	0	0
	01	1	0	0	1
	11	1	0	0	1
	10	0	0	0	0

- The map wraps around
  - out =

		ab			
cd		00	01	11	10
	00	1	0	0	1
	01	0	0	0	0
	11	0	0	0	0
	10	1	0	0	1



# Karnaugh Minimization Tricks (3)

		ab			
		00	01	11	10
cd	00	0	0	0	0
	01	1	x	x	x
	11	1	x	x	1
	10	0	0	0	0

		ab			
		00	01	11	10
cd	00	1	0	0	x
	01	0	x	x	0
	11	0	x	x	0
	10	1	0	0	1

- “Don’t care” values can be interpreted individually in whatever way is convenient
  - assume all x’s = 1
  - out =
  - assume middle x’s = 0
  - assume 4<sup>th</sup> column x = 1
  - out =

# Minimization with K-Maps

		ab			
		00	01	11	10
c	0	0	0	0	1
	1	1	1	0	1

(1) Circle the 1's (see below)


(2) Each circle is a logical component of the final equation

$$= a\bar{b} + \bar{a}c$$

## Rules:

- Use fewest circles necessary to cover all 1's
- Circles must cover *only* 1's
- Circles span rectangles of size power of 2 (1, 2, 4, 8...)
- Circles should be as large as possible (all circles of 1?)
- Circles may wrap around edges of K-Map
- 1 may be circled multiple times *if* that means fewer circles

# Multiplexer

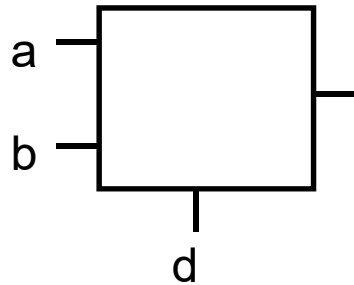

a	b	d	out
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

- A multiplexer selects between multiple inputs
  - $\text{out} = a$ , if  $d = 0$
  - $\text{out} = b$ , if  $d = 1$
- Build truth table
- Minimize diagram
- Derive logic diagram

# Takeaway

- Binary (two symbols: true and false) is the basis of Logic Design
- More than one Logic Circuit can implement same Logic function. Use Algebra (Identities) or Truth Tables to show equivalence.
- Any logic function can be implemented as “sum of products”. Karnaugh Maps minimize number of gates.



# Goals for Today

- From Switches to Logic Gates to Logic Circuits
- Logic Gates
  - From switches
  - Truth Tables
- Logic Circuits
  - From Truth Tables to Circuits (Sum of Products)
  - Identity Laws
- Logic Circuit Minimization
  - Algebraic Manipulations
  - Truth Tables (Karnaugh Maps)
- Transistors (electronic switch)




# Silicon Valley & the Semiconductor Industry


- Transistors:
- Youtube video “How does a transistor work”  
<https://www.youtube.com/watch?v=lcrBqCFLHIY>
- Break: show some Transistor, Fab, Wafer photos



# Transistors 101

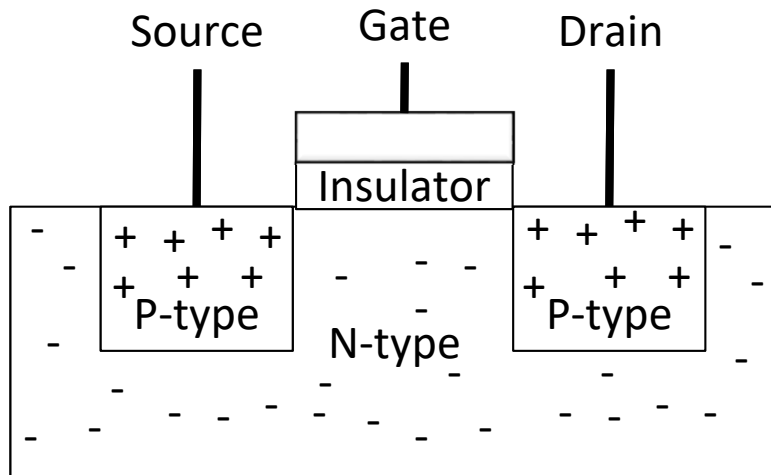

**P-Transistor Off**

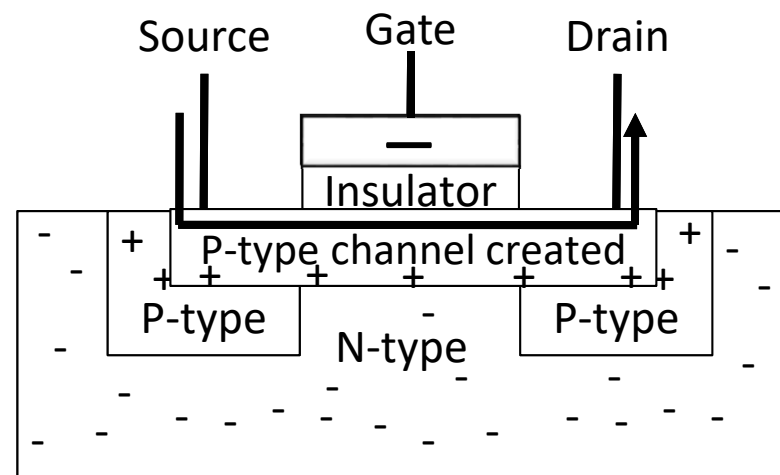

**P-Transistor On**

**N-Type Silicon:** negative free-carriers (electrons)

**P-Type Silicon:** positive free-carriers (holes)

**P-Transistor:** negative charge on gate generates electric field that creates a (+ charged) p-channel connecting source & drain


**N-Transistor:** works the opposite way

Metal-Oxide Semiconductor (Gate-Insulator-Silicon)


- Complementary MOS = **CMOS** technology uses both p- & n-type transistors

# CMOS Notation

N-type

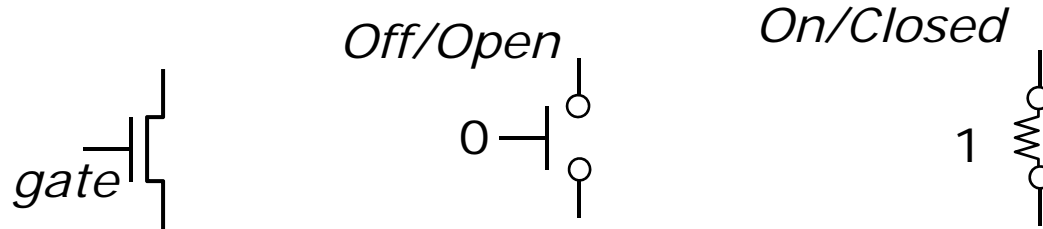

P-type

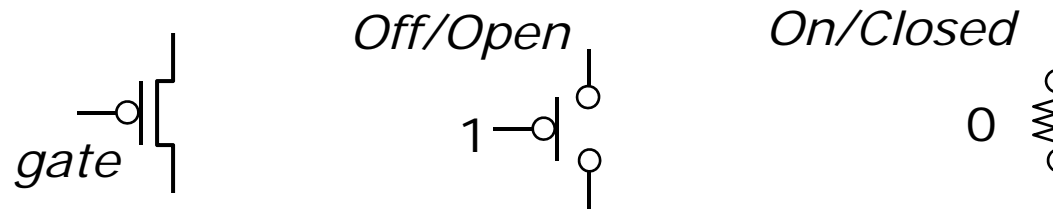


Gate input controls whether current can flow between the other two terminals or not.

*Hint:* the “o” bubble of the p-type tells you that this gate wants a 0 to be turned on


# 2-Transistor Combination: NOT

- Logic gates are constructed by combining transistors in complementary arrangements
- Combine p&n transistors to make a NOT gate:

*CMOS Inverter :*

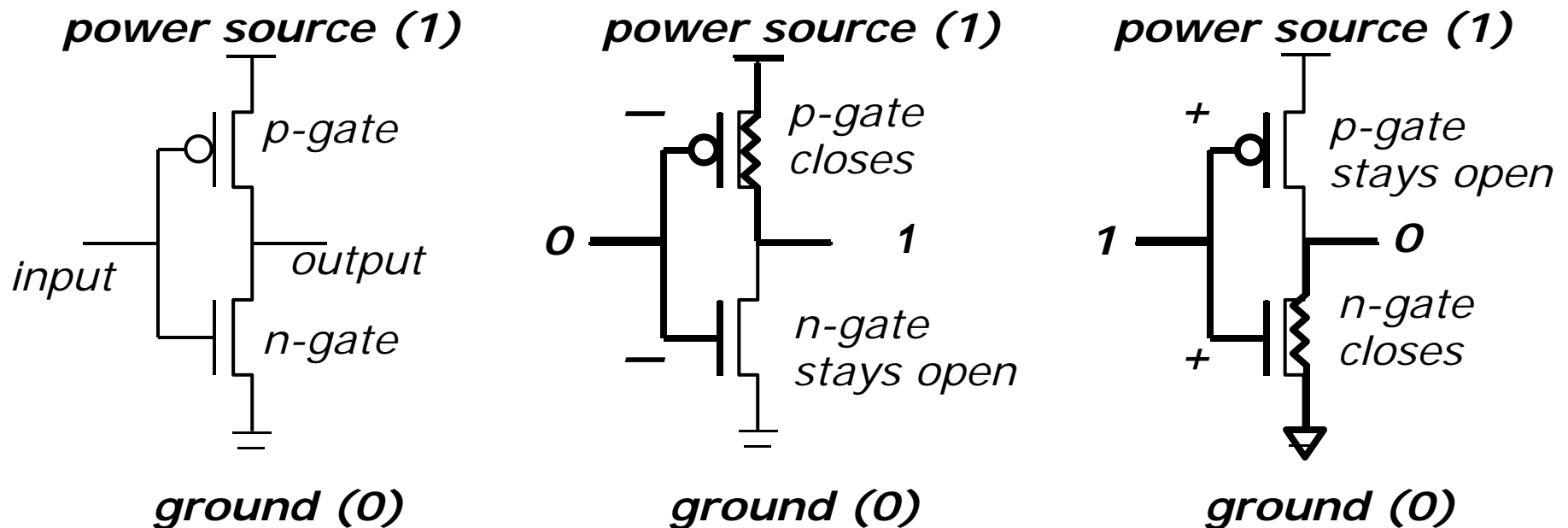


# Inverter

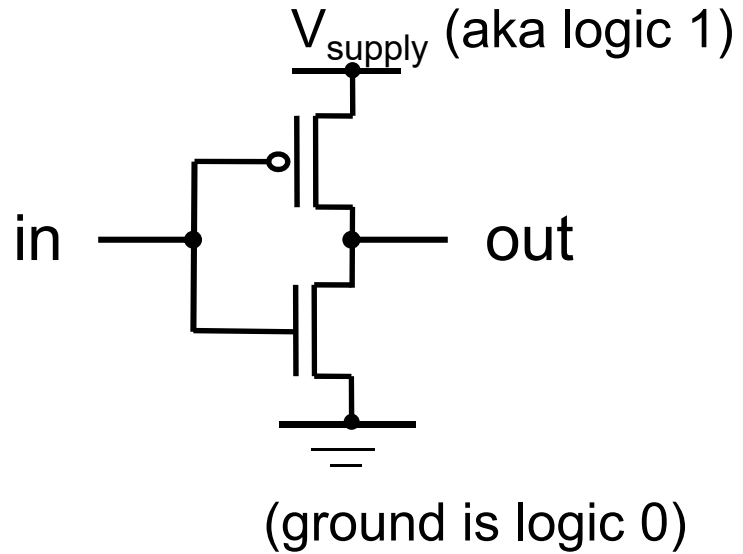

Function: NOT


Symbol:

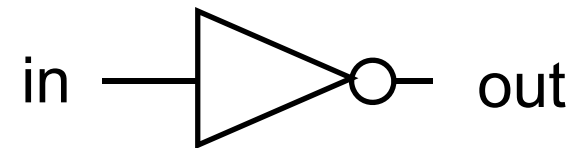

Truth Table:


In	Out
0	1
1	0

# NOR Gate

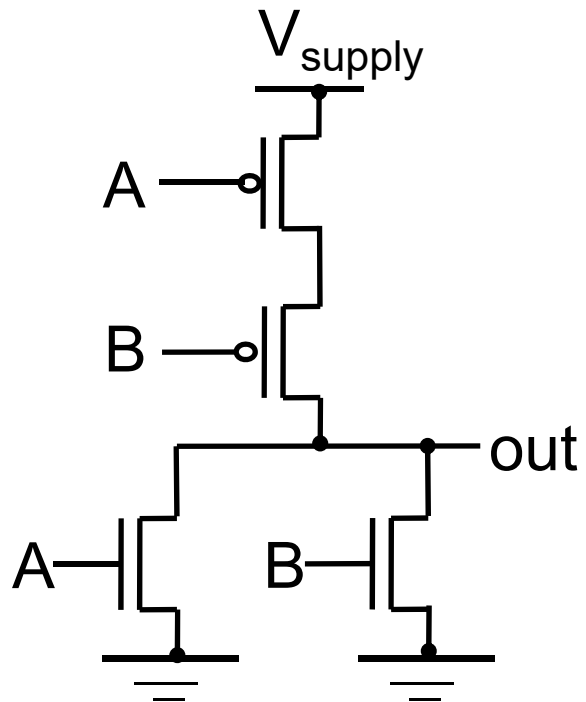

Function: NOR

Symbol:


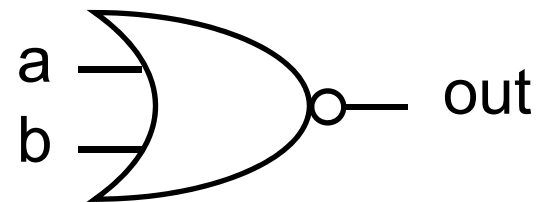


Truth Table:



A	B	out
0	0	1
0	1	0
1	0	0
1	1	0

# Building Functions (Revisited)



- NOT:

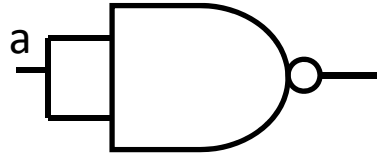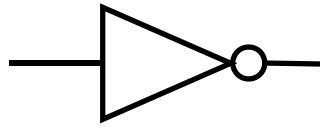

- AND:

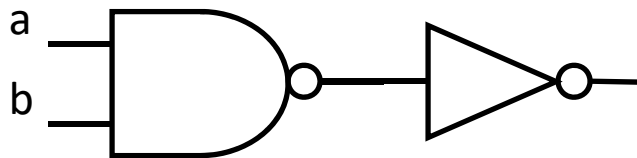
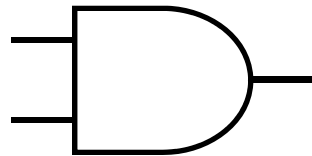


- OR:

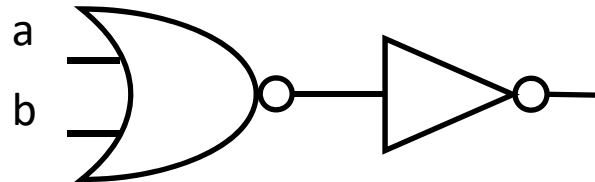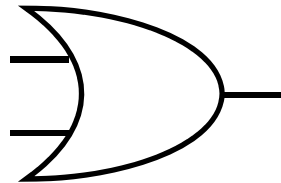



- NAND and NOR are universal
  - Can implement **any** function with NAND or just NOR gates
  - useful for manufacturing

# Logic Gates

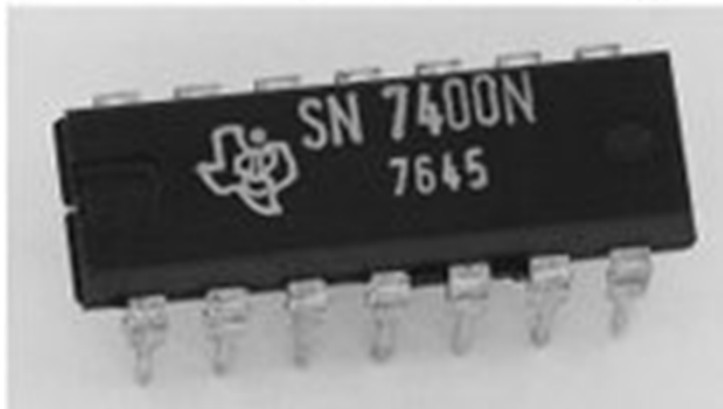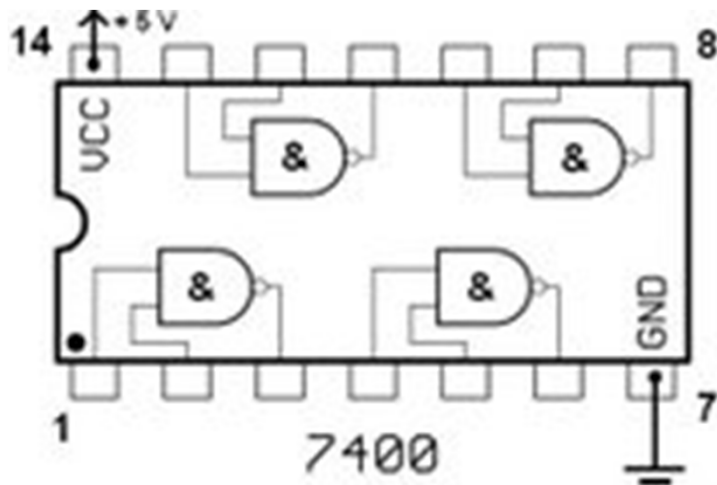

- One can buy gates separately
  - ex. 74xxx series of integrated circuits
  - cost ~\$1 per chip, mostly for packaging and testing
- Cumbersome, but possible to build devices using gates put together manually

# Then and Now

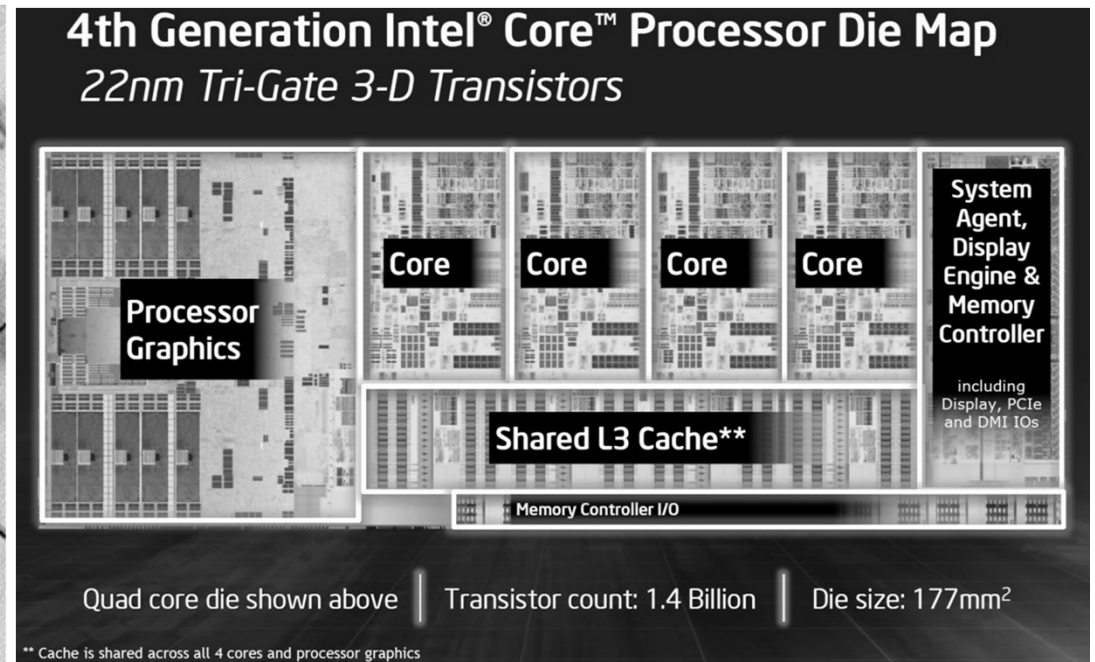
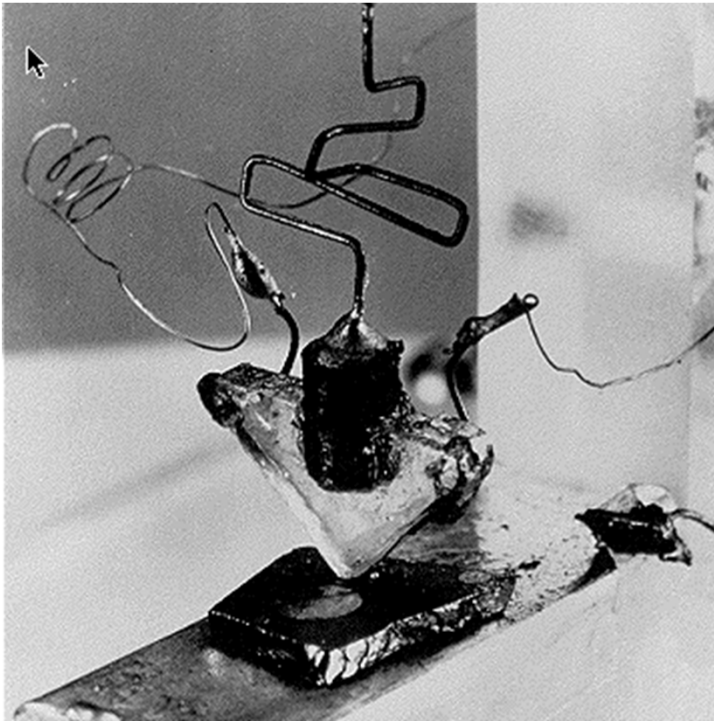


<http://techguru3d.com/4th-gen-intel-haswell-processors-architecture-and-lineup/>

- The first transistor
  - One workbench at AT&T Bell Labs
  - 1947
  - Bardeen, Brattain, and Shockley
- Intel Haswell
  - 1.4 billion transistors, 22nm
  - 177 square millimeters
  - Four processing cores



# Then and Now



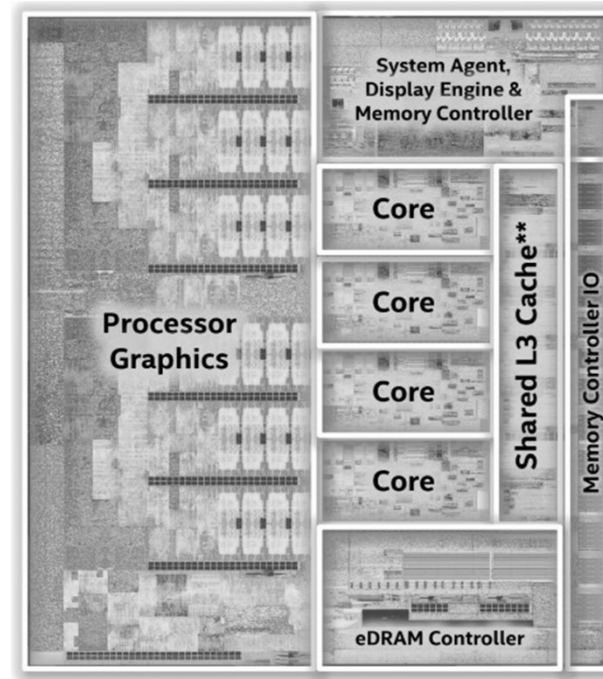
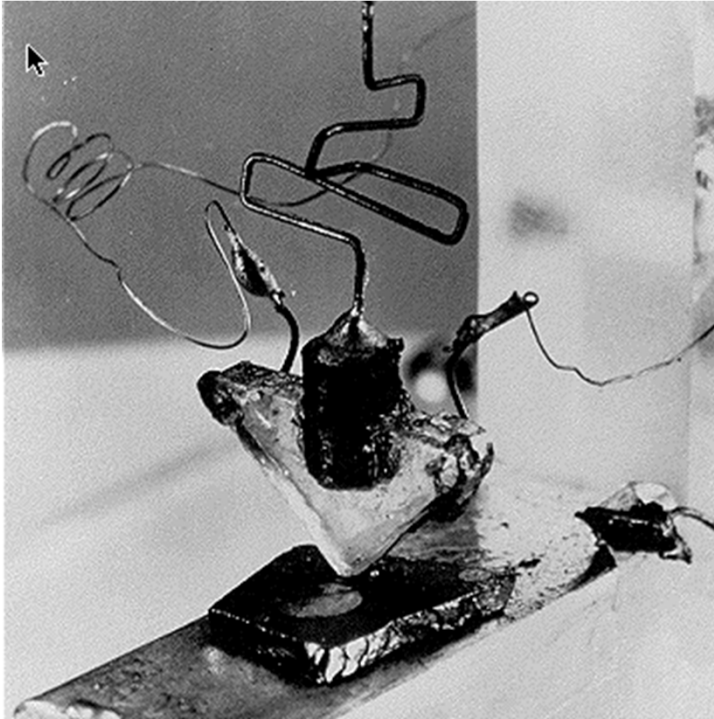


<https://www.computershopper.com/computex-2015/performance-preview-desktop-broadwell-at-computex-2015>

- The first transistor
  - One workbench at AT&T Bell Labs
  - 1947
  - Bardeen, Brattain, and Shockley
- Intel Broadwell
  - 7.2 billion transistors, 14nm
  - 456 square millimeters
  - Up to 22 processing cores
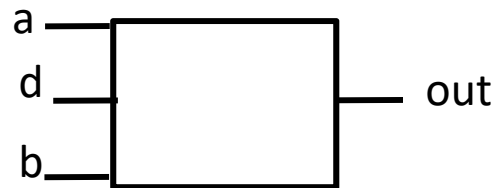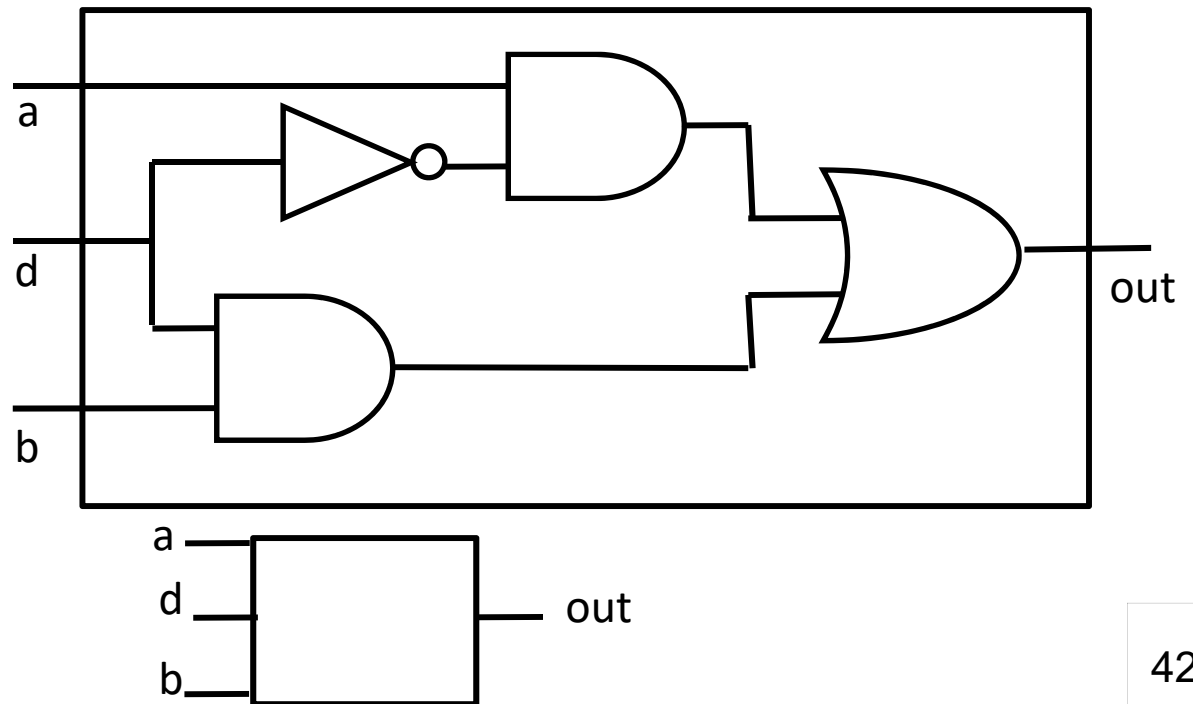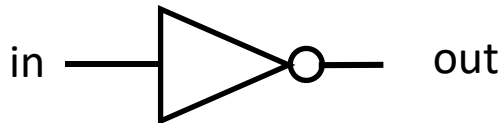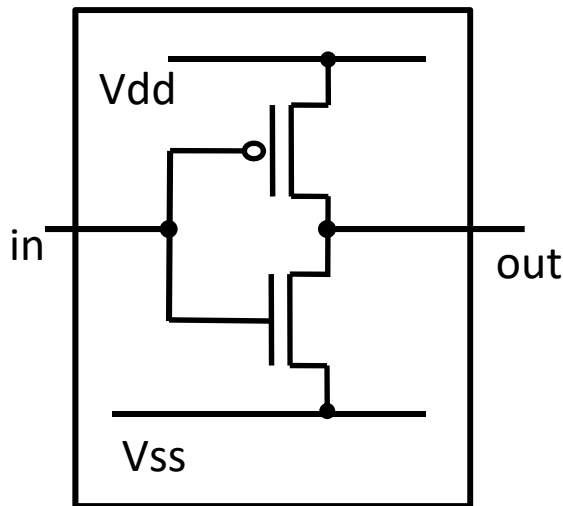
# Big Picture: Abstraction

- Hide complexity through simple abstractions
  - Simplicity
    - Box diagram represents inputs and outputs
  - Complexity
    - Hides underlying NMOS- and PMOS-transistors and atomic interactions



# Summary

- Most modern devices made of billions of transistors
  - You will build a processor in this course!
  - Modern transistors made from semiconductor materials
  - Transistors used to make logic gates and logic circuits
- We can now implement any logic circuit
  - Use P- & N-transistors to implement NAND/NOR gates
  - Use NAND or NOR gates to implement the logic circuit
  - *Efficiently*: use K-maps to find required minimal terms

