

Numbers and Arithmetic


Prof. Hakim Weatherspoon CS 3410

Computer Science Cornell University



[Weatherspoon, Bala, Bracy, and Sirer]

Big Picture: Building Processor

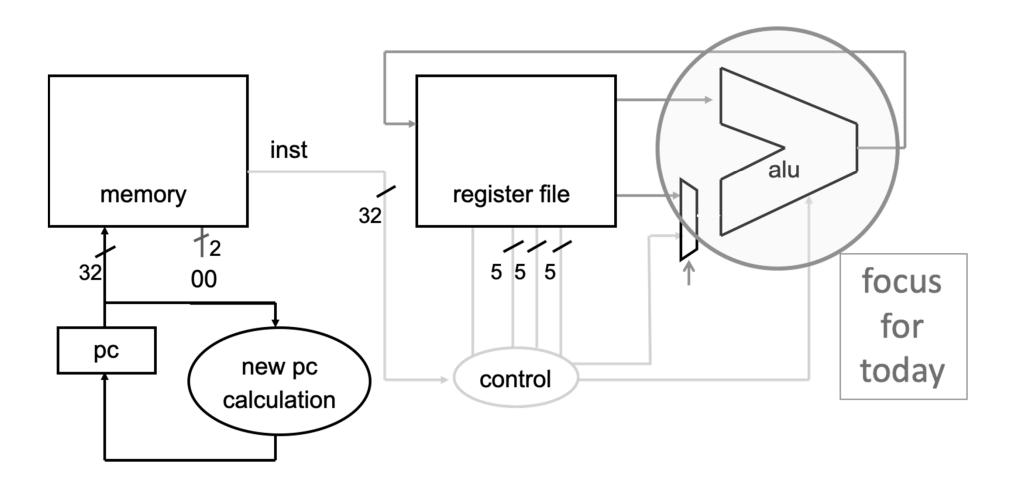

Simplified Single-cycle processor

Goals for Today

Binary Operations

- Number representations
- One-bit and four-bit adders
- Negative numbers and two's compliment
- Addition (two's compliment)
- Detecting and handling overflow
- Subtraction (two's compliment)

Recall: Binary

- Two symbols (base 2): true and false; 1 and 0
- Basis of Logic Circuits and all digital computers

So, how do we represent numbers in *Binary* (base 2)?

Recall: Binary

- Two symbols (base 2): true and false; 1 and 0
- Basis of Logic Circuits and all digital computers

So, how do we represent numbers in *Binary* (base 2)?

- We can represent numbers in Decimal (base 10).
 - E.g. 637
- Can just as easily use other bases

$$\frac{1}{2^9} \underbrace{0}_{2^8} \underbrace{0}_{2^7} \underbrace{1}_{2^6} \underbrace{1}_{2^5} \underbrace{1}_{2^4} \underbrace{1}_{2^3} \underbrace{1}_{2^2} \underbrace{0}_{2^1} \underbrace{1}_{2^6}$$

$$00\ \underline{1}_{8^3}\ \underline{1}_{8^2}\ \underline{7}_{8^1}\ \underline{5}_{8^0}$$

$$0x \underline{2}_{16^{2}16^{1}16^{0}} \underline{d}$$

Recall: Binary

- Two symbols (base 2): true and false; 1 and 0
- Basis of Logic Circuits and all digital computers

So, how do we represent numbers in *Binary* (base 2)?

We can represent numbers in Decimal (base 10).

- E.g.
$$6.3_{10^{2}}$$
 $6.10^{2} + 3.10^{1} + 7.10^{0} = 637$

Can just as easily use other bases

- Base 2 — Binary
$$1.2^9+1.2^6+1.2^5+1.2^4+1.2^3+1.2^2+1.2^0 = 637$$

- Base 8 — Octal
$$1.8^3 + 1.8^2 + 7.8^1 + 5.8^0 = 637$$

- Base 16 — Hexadecimal
$$2 \cdot 16^2 + 7 \cdot 16^1 + (d) 16^0 = 637$$

 $2 \cdot 16^2 + 7 \cdot 16^1 + (13) 16^0 = 637$

Number Representations: Activity #1 Counting

How do we count in different bases?

• Dec (base 10) Bin (base 2) Oct (base 8) Hex (base 16)

| 0 | 0 | 0 | 0 |
|-----|--------|----|----|
| 1 | 1 | 1 | 1 |
| 2 | 10 | 2 | 2 |
| 3 | 11 | 3 | 3 |
| 4 | 100 | 4 | 4 |
| 5 | 101 | 5 | 5 |
| 6 | 110 | 6 | 6 |
| 7 | 111 | 7 | 7 |
| 8 | 1000 | 10 | 8 |
| 9 | 1001 | 11 | 9 |
| 10 | 1010 | 12 | а |
| 11 | 1011 | 13 | b |
| 12 | 1100 | 14 | С |
| 13 | 1101 | 15 | d |
| 14 | 1110 | 16 | е |
| 15 | 1111 | 17 | f |
| 16 | 1 0000 | 20 | 10 |
| 17 | 1 0001 | 21 | 11 |
| 18 | 1 0010 | 22 | 12 |
| - | | | |
| 99 | | | |
| 100 | | | |
| 100 | | | |

```
0b 1111 1111 = ?
0b 1 0000 0000 = ?

0o 77 = ?
0o 100 = ?

0x ff = ?
0x 100 = ?
```

Number Representations: Activity #1 Counting

How do we count in different bases?

• Dec (base 10) Bin (base 2) Oct (base 8) Hex (base 16)

| • | | • | • |
|-----|---------|----------|---------------------------------------|
| 0 | 0 | 0 1 | 0 |
| 2 | 10 | 2 | 2 |
| 3 | 11 | 3 | 3 |
| 4 | 100 | 4 | 4 |
| 5 | 101 | 5 | 5 |
| 6 | 110 | 6 | |
| 7 | 111 | 7 | 6 7 |
| 8 | 1000 | 10 | , , , , , , , , , , , , , , , , , , , |
| 9 | 1001 | 11 | 9 |
| 10 | 1010 | | |
| 11 | 1011 | 12 13 | a b |
| 12 | 1100 | 14 | |
| 13 | 1101 | | C |
| 14 | 1110 | 15 | d |
| 15 | 1111 | 16 | е |
| 16 | 1 0000 | 17 20 | 10 |
| 17 | 1 0000 | | |
| 18 | 1 0001 | 21 | 11 |
| 10 | 1 00 10 | 22 | 12 |
| | | • | • |
| 99 | | | • |
| 100 | | | |

0b 1111 1111 = **255** 0b 1 0000 0000 = **256**

> 0o 77 = **63** 0o 100 = **64**

0x ff = 2550x 100 = 256

How to convert a number between different bases? Base conversion via repetitive division

Divide by base, write remainder, move left with quotient

```
637 ÷ 8 = 79 remainder 5
79 ÷ 8 = 9 remainder 7
9 ÷ 8 = 1 remainder 1
1 ÷ 8 = 0 remainder 1 msb (most significant bit)
```

•
$$637 = 0_{\text{msb}} 1175_{\text{lsb}}$$

Convert a base 10 number to a base 2 number Base conversion via repetitive division

Divide by base, write remainder, move left with quotient

| | | | | _ |
|---|--------------------|-----------|---|-----------------------------|
| • | $637 \div 2 = 318$ | remainder | 1 | lsb (least significant bit) |
| • | $318 \div 2 = 159$ | remainder | 0 | |
| • | $159 \div 2 = 79$ | remainder | 1 | |
| • | $79 \div 2 = 39$ | remainder | 1 | |
| • | $39 \div 2 = 19$ | remainder | 1 | |
| • | $19 \div 2 = 9$ | remainder | 1 | |
| • | $9 \div 2 = 4$ | remainder | 1 | |
| • | $4 \div 2 = 2$ | remainder | 0 | |
| • | $2 \div 2 = 1$ | remainder | 0 | |
| • | $1 \div 2 = 0$ | remainder | 1 | msb (most significant bi |

637 = 10 0111 1101 (can also be written as 0b10 0111 1101)

Slide 10

MP1

Meghna Pancholi, 12/5/2018

Clicker Question!

Convert the number 657₁₀ to base 16 What is the least significant digit of this number?

- a) D
- b) F
- c) 0
- d) 1
- e) 11

Clicker Question!

Convert the number 657₁₀ to base 16 What is the least significant digit of this number?

- a) D
- b) F
- c) 0
- d) 1
- e) 11

Convert a base 10 number to a base 16 number

Base conversion via repetitive division

Divide by base, write remainder, move left with quotient

```
    657 ÷ 16 = 41 remainder 1
    41 ÷ 16 = 2 remainder 9
    2 ÷ 16 = 0 remainder 2 msh
```

Thus, 657 = 0x291

Convert a base 10 number to a base 16 number

Base conversion via repetitive division

Divide by base, write remainder, move left with quotient

$$637 = 0x 2 7 (13) = ?$$

Thus, $637 = 0x27d$

Convert a base 2 number to base 8 (oct) or 16 (hex)

Binary to Hexadecimal

- Convert each nibble (group of four bits) from binary to hex
- A nibble (four bits) ranges in value from 0...15, which is one hex digit
 - Range: 0000...1111 (binary) => 0x0 ...0xF (hex) => 0...15 (decimal)
- E.g. 0b 10 0111 1101 \rightarrow 0x27d
 - Thus, 637 = 0x27d = 0b10 0111 1101

Binary to Octal

- Convert each group of three bits from binary to oct
- Three bits range in value from 0...7, which is one octal digit
 - Range: 0000...1111 (binary) => 0x0 ...0xF (hex) => 0...15 (decimal)
- E.g. 0b1 001 111 101 1 1 7 5 → 0o 1175
 - Thus, 637 = 0o1175 = 0b10 0111 1101

Number Representations Summary

We can represent any number in any base

Base 10 – Decimal

$$-\frac{6}{10^2} \frac{3}{10^1} \frac{7}{10^0}$$

$$6 \cdot 10^2 + 3 \cdot 10^1 + 7 \cdot 10^0 = 637$$

Base 2 — Binary

$$1 \cdot 2^9 + 1 \cdot 2^6 + 1 \cdot 2^5 + 1 \cdot 2^4 + 1 \cdot 2^3 + 1 \cdot 2^2 + 1 \cdot 2^0 = 637$$

Base 8 — Octal

$$1.8^3 + 1.8^2 + 7.8^1 + 5.8^0 = 637$$

Base 16 — Hexadecimal

$$-0x_{16^{2}16^{1}16^{0}}$$

$$2 \cdot 16^{2} + 7 \cdot 16^{1} + (d) \cdot 16^{0} = 637$$

 $2 \cdot 16^{2} + 7 \cdot 16^{1} + (3) \cdot 16^{0} = 637$

Achievement Unlocked!

There are 10 types of people in the world:

Those who understand binary

And those who do not

And those who know this joke was written

in base 2

Takeaway

Digital computers are implemented via logic circuits and thus represent *all* numbers in binary (base 2).

We (humans) often write numbers as decimal and hexadecimal for convenience, so need to be able to convert to binary and back (to understand what the computer is doing!).

Today's Lecture

Binary Operations

- Number representations
- One-bit and four-bit adders
- Negative numbers and two's compliment
- Addition (two's compliment)
- Detecting and handling overflow
- Subtraction (two's compliment)

Next Goal


Binary Arithmetic: Add and Subtract two binary numbers

Binary Addition

How do we do arithmetic in binary?

1 183 + <u>254</u> <u>-437</u>

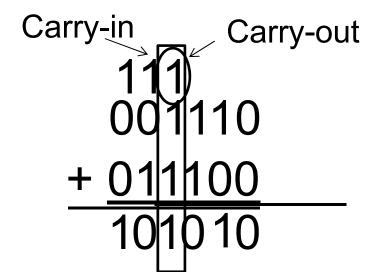- Addition works the same way regardless of base
 - Add the digits in each position
 - Propagate the carry



Unsigned binary addition is pretty easy

- Combine two bits at a time
- Along with a carry

Binary Addition

How do we do arithmetic in binary?

1 183 + <u>254</u> _437


- Addition works the same way regardless of base
 - Add the digits in each position
 - Propagate the carry

111 001110 + <u>011100</u> 101010 Unsigned binary addition is pretty easy

- Combine two bits at a time
- Along with a carry

Binary Addition

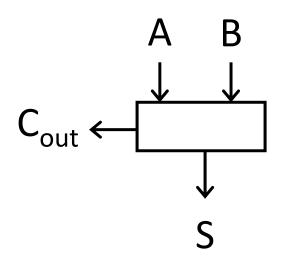- Binary addition requires
 - Add of two bits PLUS carry-in
 - Also, carry-out if necessary



| Α | В | C _{out} | S |
|---|---|------------------|---|
| 0 | 0 | | |
| 0 | 1 | | |
| 1 | 0 | | |
| 1 | 1 | | |


Half Adder

- Adds two 1-bit numbers
- Computes 1-bit result and 1bit carry
- No carry-in

Clicker Question

What is the equation for C_{out}?

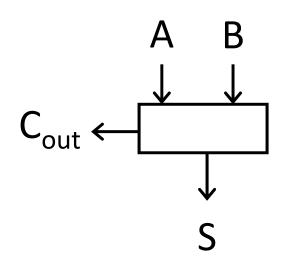- a) A + B
- b) AB
- c) A⊕B
- d) A + !B
- e) !A!B



| Α | В | C _{out} | S |
|---|---|------------------|---|
| 0 | 0 | | |
| 0 | 1 | | |
| 1 | 0 | | |
| 1 | 1 | | |


Half Adder

- Adds two 1-bit numbers
- Computes 1-bit result and 1bit carry
- No carry-in

Clicker Question

What is the equation for C_{out}?

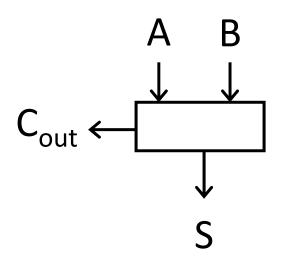- a) A + B
- b) AB
- c) A⊕B
- d) A + !B
- e) !A!B




| Α | В | C _{out} | S |
|---|---|------------------|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |


Half Adder

- Adds two 1-bit numbers
- Computes 1-bit result and 1bit carry
- No carry-in

•
$$S = \overline{A}B + A\overline{B}$$

•
$$C_{out} = AB$$

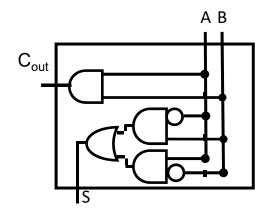

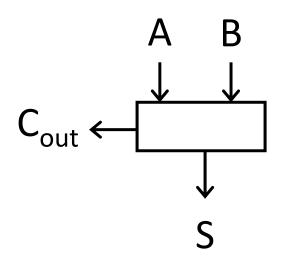


| Α | В | C _{out} | S |
|---|---|------------------|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |


Half Adder

- Adds two 1-bit numbers
- Computes 1-bit result and 1bit carry
- No carry-in

•
$$S = \overline{A}B + A\overline{B} = A \oplus B$$

•
$$C_{out} = AB$$

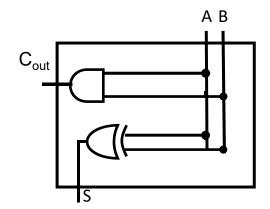

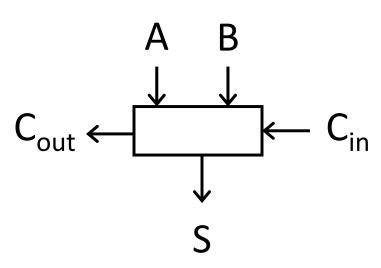


| Α | В | C _{in} | C _{out} | S |
|---|---|-----------------|------------------|---|
| 0 | 0 | 0 | | |
| 0 | 0 | 1 | | |
| 0 | 1 | 0 | | |
| 0 | 1 | 1 | | |
| 1 | 0 | 0 | | |
| 1 | 0 | 1 | | |
| 1 | 1 | 0 | | |
| 1 | 1 | 1 | | |

Full Adder

- Adds three 1-bit numbers
- Computes 1-bit result and 1bit carry
- Can be cascaded

Now You Try:

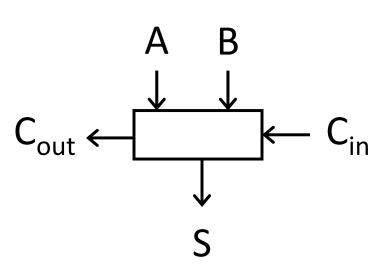- 1. Fill in Truth Table
- 2. Create Sum-of-Product Form
- 3. Minimization the equation
 - 1. Karnaugh Maps (coming soon!)
 - 2. Algebraic minimization
- 4. Draw the Logic Circuits



| Α | В | C _{in} | C _{out} | S |
|---|---|-----------------|------------------|---|
| 0 | 0 | 0 | | |
| 0 | 0 | 1 | | |
| 0 | 1 | 0 | | |
| 0 | 1 | 1 | | |
| 1 | 0 | 0 | | |
| 1 | 0 | 1 | | |
| 1 | 1 | 0 | | |
| 1 | 1 | 1 | | |


Full Adder

- Adds three 1-bit numbers
- Computes 1-bit result and 1bit carry
- Can be cascaded

Clicker Question

What is the equation for C_{out}?

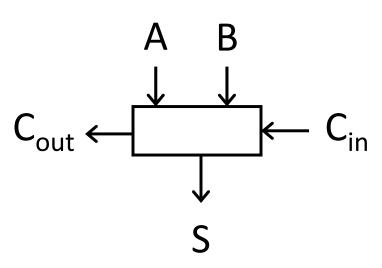- a) $A + B + C_{in}$
- b) $!A + !B + !C_{in}$
- c) $A \oplus B \oplus C_{in}$
- d) $AB + AC_{in} + BC_{in}$
- e) ABC_{in}



Full Adder


- Adds three 1-bit numbers
- Computes 1-bit result and 1bit carry
- Can be cascaded

| Α | В | C _{in} | C _{out} | S |
|---|---|-----------------|------------------|---|
| 0 | 0 | 0 | | |
| 0 | 0 | 1 | | |
| 0 | 1 | 0 | | |
| 0 | 1 | 1 | | |
| 1 | 0 | 0 | | |
| 1 | 0 | 1 | | |
| 1 | 1 | 0 | | |
| 1 | 1 | 1 | | |

Clicker Question

What is the equation for C_{out}?

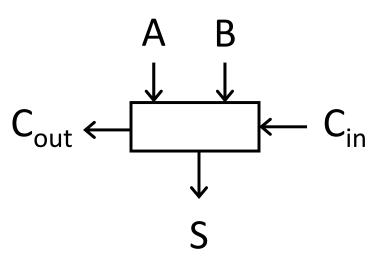- a) $A + B + C_{in}$
- b) !A + !B + ! C_{in}
- c) $A \oplus B \oplus C_i$
- d) $AB + AC_{in} + BC_{in}$
- e) ABC_{in}



| Α | В | C _{in} | C _{out} | S |
|---|---|-----------------|------------------|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

Full Adder


Adds three 1-bit numbers


Computes 1-bit result and 1-

bit carry

Can be cascaded

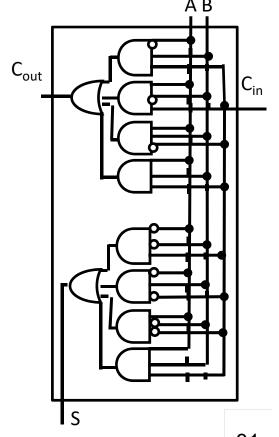 $S = \overline{AB}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$ $C_{out} = \overline{A}BC + A\overline{B}C + AB\overline{C} + ABC$



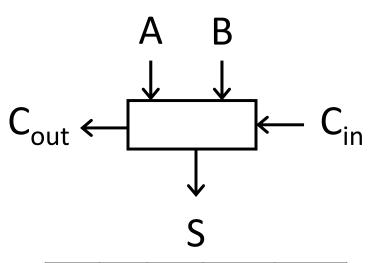

| Α | В | C _{in} | C _{out} | S |
|---|---|-----------------|------------------|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

Full Adder


Adds three 1-bit numbers

Computes 1-bit result and 1-


bit carry


$$S = \overline{AB}C + \overline{A}B\overline{C} + A\overline{BC} + ABC$$
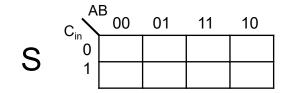
$$C_{out} = \overline{A}BC + A\overline{B}C + AB\overline{C} + ABC$$



| C_{in} | AE | 00 | 01 | 11 | 10 |
|--------------|-----|----|----|----|----|
| \mathbf{C} | o [| | | | |
| Cout | 1 [| | | | |

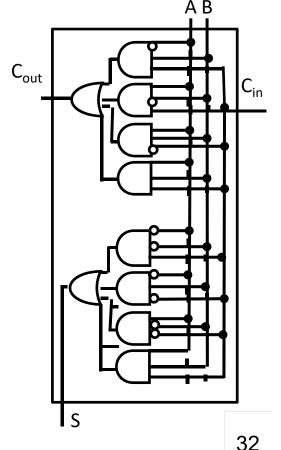

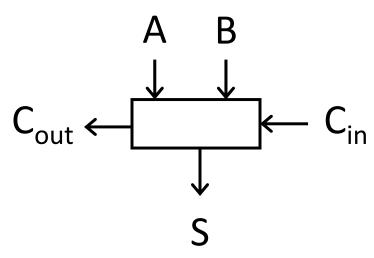

| Α | В | C _{in} | C _{out} | S |
|---|---|-----------------|------------------|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

Full Adder

Adds three 1-bit numbers


Computes 1-bit result and 1-


bit carry


$$S = \overline{AB}C + \overline{A}B\overline{C} + A\overline{BC} + ABC$$

$$C_{out} = \overline{A}BC + A\overline{B}C + AB\overline{C} + ABC$$

$$C_{out} = AB + AC + BC$$

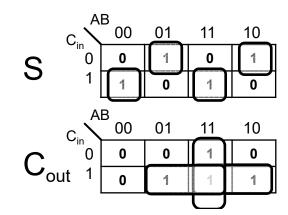

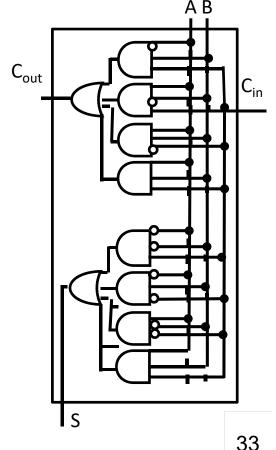

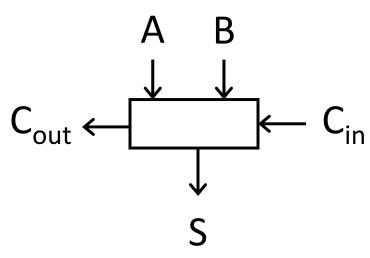

| Α | В | C _{in} | C _{out} | S |
|---|---|-----------------|------------------|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

Full Adder

Adds three 1-bit numbers

Computes 1-bit result and 1-


bit carry


$$S = \overline{AB}C + \overline{A}B\overline{C} + A\overline{BC} + ABC$$


$$S = \overline{A}(\overline{B}C + B\overline{C}) + A(\overline{BC} + BC)$$

$$S = \overline{A}(B \oplus C) + A(\overline{B \oplus C})$$

$$S = A \oplus (B \oplus C)$$

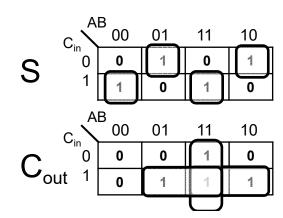

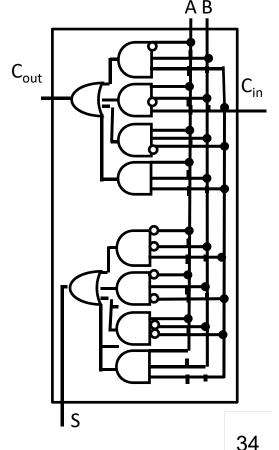

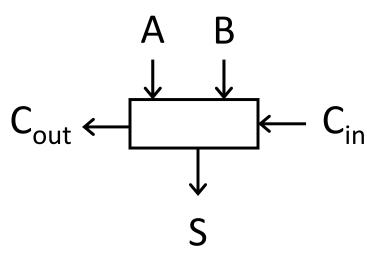

| Α | В | C _{in} | C _{out} | S |
|---|---|-----------------|------------------|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

Full Adder

Adds three 1-bit numbers

Computes 1-bit result and 1-

bit carry

$$S = \overline{AB}C + \overline{A}B\overline{C} + A\overline{BC} + ABC$$


$$S = \overline{A}(\overline{B}C + B\overline{C}) + A(\overline{BC} + BC)$$

$$S = \overline{A}(B \oplus C) + A(\overline{B \oplus C})$$


$$S = A \oplus (B \oplus C)$$

$$C_{out} = \overline{A}BC + A\overline{B}C + AB\overline{C} + ABC$$


$$C_{out} = AB + AC + BC$$

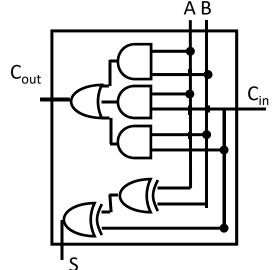

Lab1 1-bit Adder with Carry

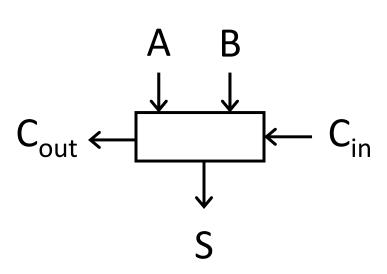

| Α | В | C _{in} | C _{out} | S |
|---|---|-----------------|------------------|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

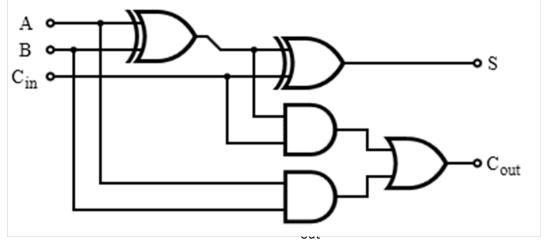

cascaded

$$S = \overline{AB}C + \overline{A}B\overline{C} + A\overline{BC} + ABC$$

$$S = \overline{A}(\overline{B}C + B\overline{C}) + A(\overline{BC} + BC)$$

$$S = \overline{A}(B \oplus C) + A(\overline{B \oplus C})$$

$$S = A \oplus (B \oplus C)$$

$$C_{out} = \overline{A}BC + A\overline{B}C + AB\overline{C} + ABC$$


$$C_{out} = \overline{A}BC + A\overline{B}C + AB(\overline{C} + C)$$

$$C_{out} = \overline{A}BC + A\overline{B}C + AB$$

$$C_{out} = (\overline{A}B + A\overline{B})C + AB$$

$$C_{out} = (A \oplus B)C + AB$$


4-bit Adder

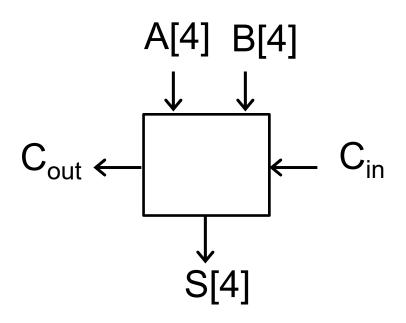

4-Bit Full Adder


- Adds two 4-bit numbers and carry in
- Computes 4-bit result and carry out
- Can be cascaded

4-bit Adder

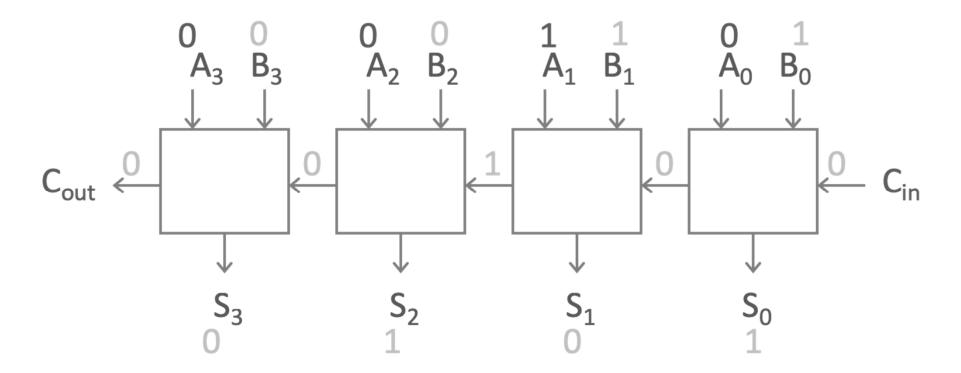

- Adds two 4-bit numbers, along with carry-in
- Computes 4-bit result and carry out
- Carry-out = overflow indicates result does not fit in 4 bits

4-bit Adder

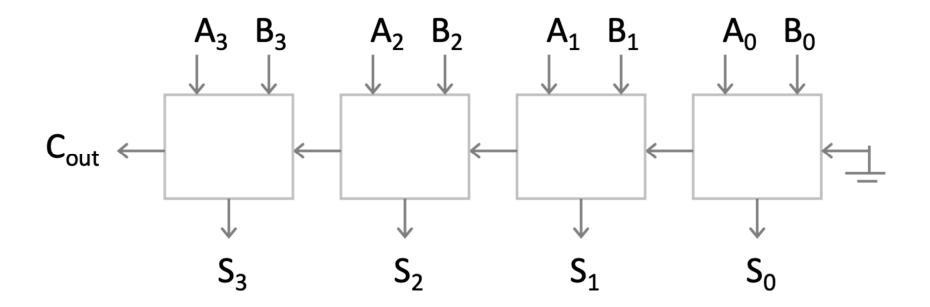

- Adds two 4-bit numbers, along with carry-in
- Computes 4-bit result and carry out
- Carry-out = overflow indicates result does not fit in 4 bits

Takeaway

Digital computers are implemented via logic circuits and thus represent *all* numbers in binary (base 2).

We (humans) often write numbers as decimal and hexadecimal for convenience, so need to be able to convert to binary and back (to understand what computer is doing!).

Adding two 1-bit numbers generalizes to adding two numbers of any size since 1-bit full adders can be cascaded.

Today's Lecture

Binary Operations

- Number representations
- One-bit and four-bit adders
- Negative numbers and two's compliment
- Addition (two's compliment)
- Detecting and handling overflow
- Subtraction (two's compliment)

Next Goal

How do we subtract two binary numbers? Equivalent to adding with a negative number

How do we represent negative numbers?

1st Attempt: Sign/Magnitude Representation

- First Attempt: Sign/Magnitude Representation
 - 1 bit for sign
 (0=positive, <u>0</u>111 = 7
 1=negative) <u>1</u>111 = -7
 - N-1 bits for magnitude

Problem?

- Two zero's: +0 $\underline{0000} = +0$ different than -0 $\underline{1000} = -0$
- Complicated circuits
- -2 + 1 = ???



IBM 7090, 1959:

"a secondgeneration transist
orized version of
the
earlier IBM
709 vacuum
tube mainframe
computers"





Second Attempt: One's complement

- Second Attempt: One's complement
 - Leading 0's for positive and 1's for negative
 - Negative numbers: complement the positive number

0111 = 71000 = -7

- Problem?
 - Two zero's still: +0 different than -0
 - -1 if offset from two's complement
 - Complicated circuits
 - Carry is difficult

$$0000 = +0$$

1111 = -0



PDP 1

Two's Complement Representation

What is used: Two's Complement Representation

Nonnegative numbers are represented as usual

• 0 = 0000, 1 = 0001, 3 = 0011, 7 = 0111

Leading 1's for negative numbers To negate any number:

- complement all the bits (i.e. flip all the bits)
- then add 1
- -1: $1 \Rightarrow 0001 \Rightarrow 1110 \Rightarrow 1111$
- $-3: 3 \Rightarrow 0011 \Rightarrow 1100 \Rightarrow 1101$
- $-7:7 \Rightarrow 0111 \Rightarrow 1000 \Rightarrow 1001$
- $-8: 8 \Rightarrow 1000 \Rightarrow 0111 \Rightarrow 1000$
- -0: $0 \Rightarrow 0000 \Rightarrow 1111 \Rightarrow 0000$ (this is good, -0 = +0)

Two's Complement

Non-negatives Negatives (two's complement) (as usual): flip then add 1 +0 = 0000 $\overline{0} = 1111$ -0 = 0000+1 = 0001 $\overline{1} = 1110$ -1 = 1111+2 = 0010 $\overline{2} = 1101$ -2 = 1110+3 = 0011 $\overline{3} = 1100 \quad -3 = 1101$ +4 = 0100 $\overline{4} = 1011$ -4 = 1100+5 = 0101 $\overline{5} = 1010$ -5 = 1011+6 = 01106 = 1001-6 = 1010+7 = 0111 $\overline{7} = 1000$ -7 = 1001+8 = 1000 $\bar{8} = 0111$ -8 = 1000

Two's Complement

Non-negatives Negatives (two's complement) (as usual): flip then add 1 $\overline{0} = 1111$ +0 = 0000-0 = 0000+1 = 0001 $\overline{1} = 1110$ -1 = 1111+2 = 0010 $\overline{2} = 1101 -2 = 1110$ +3 = 0011 $\overline{3} = 1100 \quad -3 = 1101$ +4 = 0100 $\overline{4} = 1011$ -4 = 1100+5 = 0101 $\overline{5} = 1010$ -5 = 1011+6 = 0110 $\overline{6} = 1001 -6 = 1010$ +7 = 0111 $\overline{7} = 1000$ -7 = 1001+8 = 1000 $\bar{8} = 0111$ -8 = 1000

Two's Complement vs. Unsigned

4 bit
Two's
Complement
-8 ... 7

```
-1 = 1111 = 15
-2 = 1110 = 14
-3 = 1101= 13
-4 = 1100 = 12
-5 = 1011= 11
-6 = 1010 = 10
-7 = 1001 = 9
-8 = 1000 = 8
+7 = 0111 = 7
+6 = 0110 = 6
+5 = 0101 = 5
+4 = 0100 = 4
+3 = 0011 = 3
+2 = 0010 = 2
+1 = 0001 = 1
 0 = 0000 = 0
```

4 bit Unsigned Binary 0 ... 15

Clicker Question!

What is the value of the 2s complement number 11010

- a) 26
- b) 6
- c) -6
- d) -10
- e) -26

Clicker Question!

What is the value of the 2s complement number 11010

- a) 26
- b) 6
- (c) -6
- d) -10
- e) -26

11010

$$-6 = 00110$$

Two's Complement Facts

```
Signed two's complement
 Negative numbers have leading 1's
 zero is unique: +0 = -0
 wraps from largest positive to largest negative
N bits can be used to represent
 unsigned: range 0...2<sup>N</sup>-1
   eg: 8 bits \Rightarrow 0...255
 signed (two's complement): -(2^{N-1})...(2^{N-1}-1)
   E.g.: 8 bits \Rightarrow (1000 000) ... (0111 1111)
   -128 ... 127
```

Sign Extension & Truncation

Extending to larger size

- 1111 = -1
- 1111 1111 = -1
- 0111 = 7
- 0000 0111 = 7

Truncate to smaller size

- 0000 1111 = 15
- BUT, 0000 1111 = 1111 = -1

- Addition with two's complement signed numbers
- Addition as usual. Ignore the sign. It just works!
- Examples
 - 1 + -1 =
 - -3 + -1 =
 - -7 + 3 =
 - 7 + (-3) =

| -1 = | 1111 | = 15 |
|------|------|------|
| -2 = | 1110 | = 14 |
| -3 = | 1101 | = 13 |
| -4 = | 1100 | = 12 |
| -5 = | 1011 | = 11 |
| -6 = | 1010 | = 10 |
| -7 = | 1001 | = 9 |
| -8 = | 1000 | = 8 |
| +7 = | 0111 | = 7 |
| +6 = | 0110 | = 6 |
| +5 = | 0101 | = 5 |
| +4 = | 0100 | = 4 |
| +3 = | 0011 | = 3 |
| +2 = | 0010 | = 2 |
| +1 = | 0001 | = 1 |
| 0 = | 0000 | = 0 |

- Addition with two's complement signed numbers
- Addition as usual. Ignore the sign. It just works!
- Examples

```
1 + -1 = 0001 + 1111 =
-3 + -1 = 1101 + 1111 =
-7 + 3 = 1001 + 0011 =
7 + (-3) = 0111 + 1101 =
```

```
-1 =
      1111
             = 15
-2 =
       1110
             = 14
             = 13
-3 =
      1101
-4 =
      1100
             = 12
-5 = 1011
             = 11
-6 =
      1010
             = 10
      1001
-7 =
             = 9
-8 =
      1000
             = 8
+7 =
      0111
             = 7
+6 =
      0110
             = 6
+5 =
      0101
             = 5
+4 =
      0100
             = 4
+3 = 0011
             =3
+2 =
      0010
             = 2
+1 =
      0001
             = 1
      0000
             = 0
0 =
```

- Addition with two's complement signed numbers
- Addition as usual. Ignore the sign. It just works!
- Examples

```
1 + -1 = 0001 + 1111 = 0000 (0)
-3 + -1 = 1101 + 1111 = 1100 (-4)
-7 + 3 = 1001 + 0011 = 1100 (-4)
7 + (-3) = 0111 + 1101 = 0100 (4)
```

```
-1 =
       1111
              = 15
-2 =
       1110
              = 14
-3 =
              = 13
       1101
-4 =
       1100
              = 12
 -5 = 1011
              = 11
 -6 =
       1010
              = 10
       1001
 -7 =
              = 9
 -8 =
       1000
              = 8
 +7 =
       0111
              = 7
 +6 =
       0110
              = 6
 +5 =
       0101
              = 5
 +4 =
       0100
              = 4
 +3 =
       0011
              =3
 +2 =
       0010
              = 2
 +1 =
       0001
              = 1
       0000
 0 =
              = 0
```

- Addition with two's complement signed numbers
- Addition as usual. Ignore the sign. It just works!
- Examples

•
$$1 + -1 = 0001 + 1111 = 0000 (0)$$
• $-3 + -1 = 1101 + 1111 = 1100 (-4)$
• $-7 + 3 = 1001 + 0011 = 1100 (-4)$
• $-7 + (-3) = 0111 + 1101 = 0100 (4)$
• $-5 = 1011$

Clicker Question

Which of the following has problems?

a)
$$7 + 1$$

b)
$$-7 + -3$$

c)
$$-7 + -1$$

- d) Only (a) and (b) have problems
- e) They all have problems

```
= 14
-3 = 1101
                = 13
        1100
                = 12
-5 =
        1011
                = 11
-6 =
        1010
                = 10
-7 =
        1001
                = 9
 -8 =
        1000
                = 8
        0111
 +7 =
                = 7
 +6 =
        0110
                = 6
 +5 =
        0101
                = 5
        0100
                = 4
 +3 =
        0011
                =3
+2 =
                = 2
        0010
 +1 =
                = 1
        0001
        0000
 0 =
                = 0
```

= 15

- Addition with two's complement signed numbers
- Addition as usual. Ignore the sign. It just works!
- Examples

•
$$1 + -1 = 0001 + 1111 = 0000 (0)$$
• $-3 + -1 = 1101 + 1111 = 1100 (-4)$
• $-7 + 3 = 1001 + 0011 = 1100 (-4)$
• $-7 + (-3) = 0111 + 1101 = 0100 (4)$
• $-5 = 1011$

Clicker Question

Which of the following has problems?

a)
$$7 + 1 = 1000$$

b)
$$-7 + -3 = 10110$$

c)
$$-7 + -1 = 1000$$

- d) Only (a) and (b) have problems
- e) They all have problems

```
= 14
-3 = 1101
                = 13
        1100
                = 12
        1011
                 = 11
 -6 =
        1010
                = 10
 -7 =
        1001
                 = 9
 -8 =
        1000
                 = 8
        0111
 +7 =
                 = 7
 +6 =
        0110
                 = 6
        0101
                 = 5
        0100
                 = 4
 +3 =
                 = 3
        0011
 +2 =
        0010
                 = 2
        0001
                = 1
        0000
                 = 0
```

= 15

- Addition with two's complement signed numbers
- Addition as usual. Ignore the sign. It just works!
- Examples

•
$$1 + -1 = 0001 + 1111 = 0000 (0)$$
• $-3 + -1 = 1101 + 1111 = 1100 (-4)$
• $-7 + 3 = 1001 + 0011 = 1100 (-4)$
• $-7 + (-3) = 0111 + 1101 = 0100 (4)$
• $-4 = 1100 = 12$
• $-5 = 1011 = 11$

Clicker Question

Which of the following has problems?

- a) 7 + 1 = 1000 overflow
- b) -7 + -3 = 10110 overflow
- c) -7 + -1 = 1000 fine
- d) Only (a) and (b) have problems
- e) They all have problems

```
= 13
                = 12
                = 11
-6 =
        1010
                = 10
        1001
-7 =
                = 9
-8 =
        1000
                = 8
+7 =
        0111
                = 7
+6 =
        0110
                = 6
+5 =
        0101
                = 5
+4 =
        0100
                = 4
+3 =
                = 3
        0011
+2 =
        0010
                = 2
+1 =
        0001
                = 1
        0000
                = 0
```

Next Goal

In general, how do we detect and handle overflow?

Overflow

When can overflow occur?

- adding a negative and a positive?
 - Overflow cannot occur (Why?)
 - Always subtract larger magnitude from smaller
- adding two positives?
 - Overflow can occur (Why?)
 - Precision: Add two positives, and get a negative number!
- adding two negatives?
 - Overflow can occur (Why?)
 - Precision: add two negatives, get a positive number!

Rule of thumb:

 Overflow happens iff carry into msb != carry out of msb

Overflow

When can overflow occur?


- adding a negative and a positive?
 - Overflow cannot occur (Why?)
 - Always subtract larger magnitude from smaller
- adding two positives?
 - Overflow can occur (Why?)
 - Precision: Add two positives, and get a negative number!
- adding two negatives?
 - Overflow can occur (Why?)
 - Precision: add two negatives, get a positive number!

Rule of thumb:

 Overflow happens iff carry into msb != carry out of msb

Overflow

When can overflow occur?

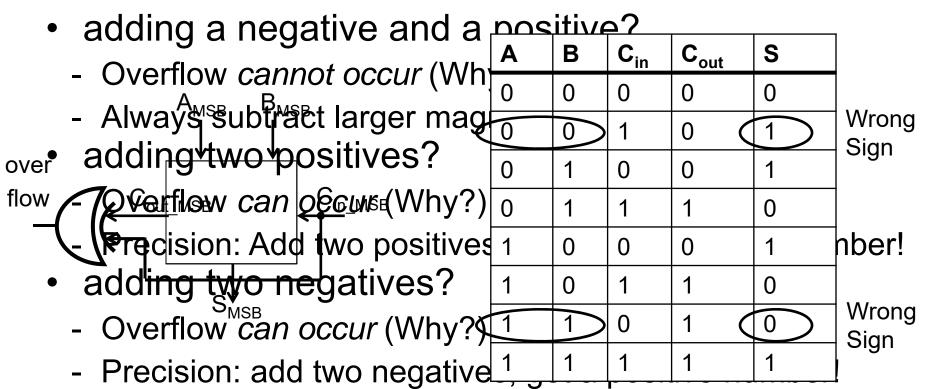

Rule of thumb:

 Overflow happens iff carry into msb != carry out of msb



YouTube

Shared publicly - Dec 1, 2014

We never thought a video would be watched in numbers greater than a 32-bit integer (=2,147,483,647 views), but that was before we met PSY. "Gangnam Style" has been viewed so many times we had to upgrade to a 64-bit integer (9,223,372,036,854,775,808)!

Hover over the counter in PSY's video to see a little math magic and stay tuned for bigger and bigger numbers on YouTube.



Today's Lecture

Binary Operations

- Number representations
- One-bit and four-bit adders
- Negative numbers and two's compliment
- Addition (two's compliment)
- Detecting and handling overflow
- Subtraction (two's compliment)

Binary Subtraction

Why create a new circuit?


Just use addition using two's complement math

How?

Binary Subtraction


- Two's Complement Subtraction
 - Subtraction is simply addition,
 where one of the operands has been negated
 - Negation is done by inverting all bits and adding one
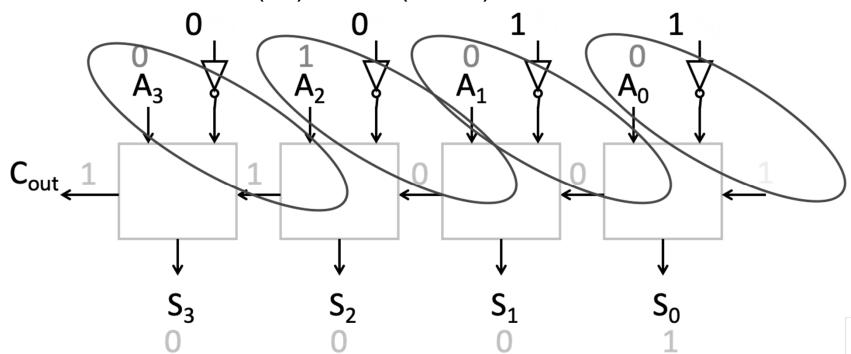
$$A - B = A + (-B) = A + (\overline{B} + 1)$$



Binary Subtraction

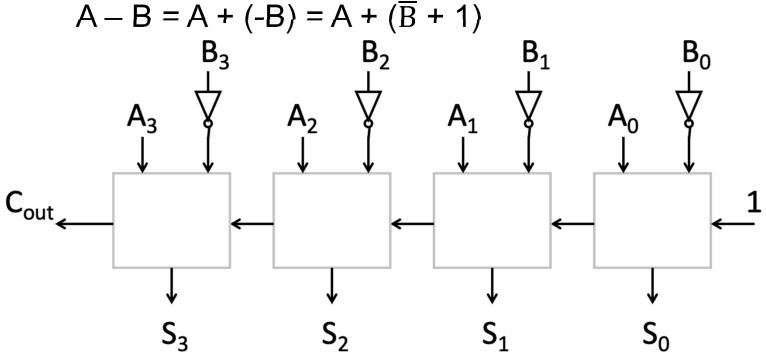
- Two's Complement Subtraction
 - Subtraction is simply addition,
 where one of the operands has been negated
 - Negation is done by inverting all bits and adding one




Q: How do we detect and handle overflows?

Q: What if (-B) overflows?

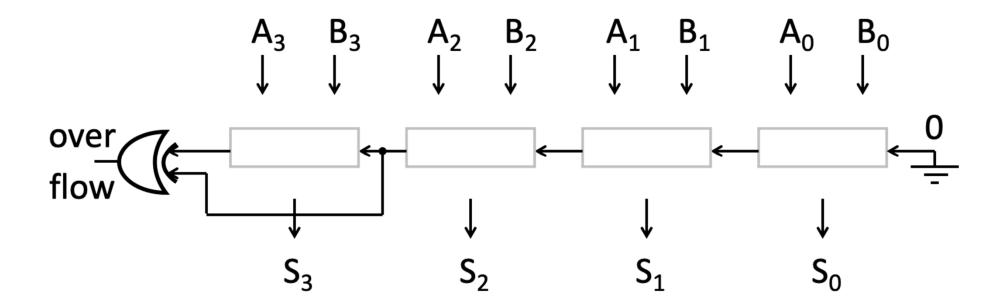
Two's Complement Adder with overflow detection



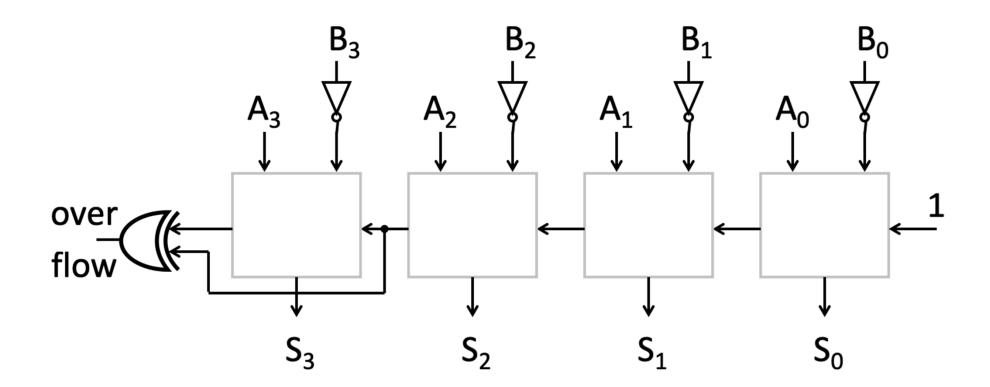Two's Complement Adder with overflow detection




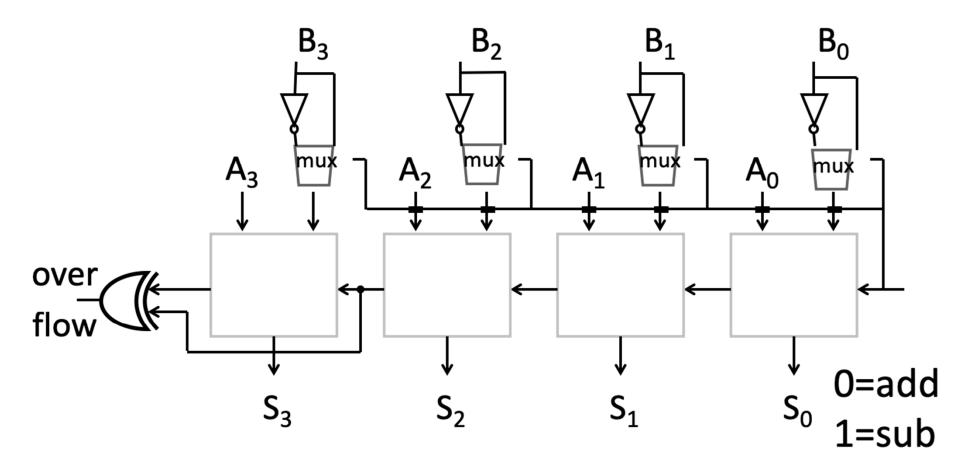Two's Complement Adder with overflow detection




Note: 4-bit adder is drawn for illustrative purposes and may not represent the optimal design. 70

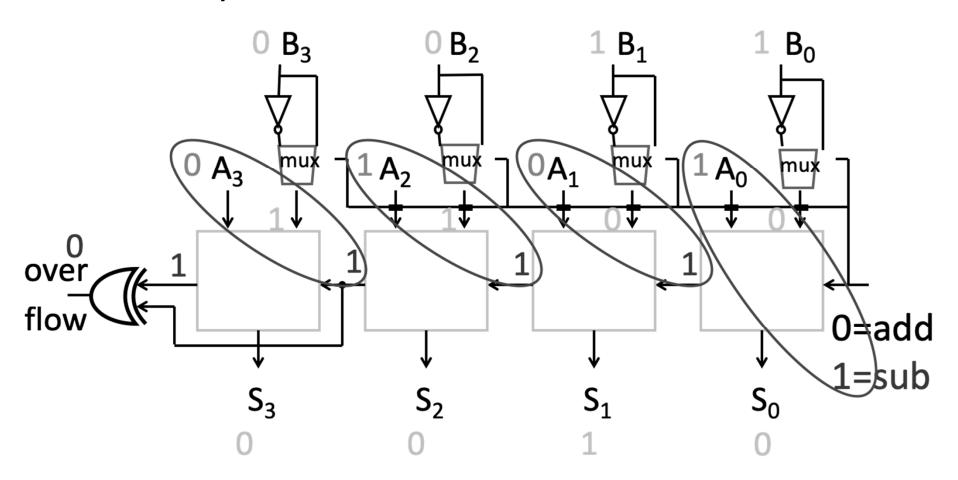Two's Complement Adder with overflow detection




Note: 4-bit adder is drawn for illustrative purposes and may not represent the optimal design. 71

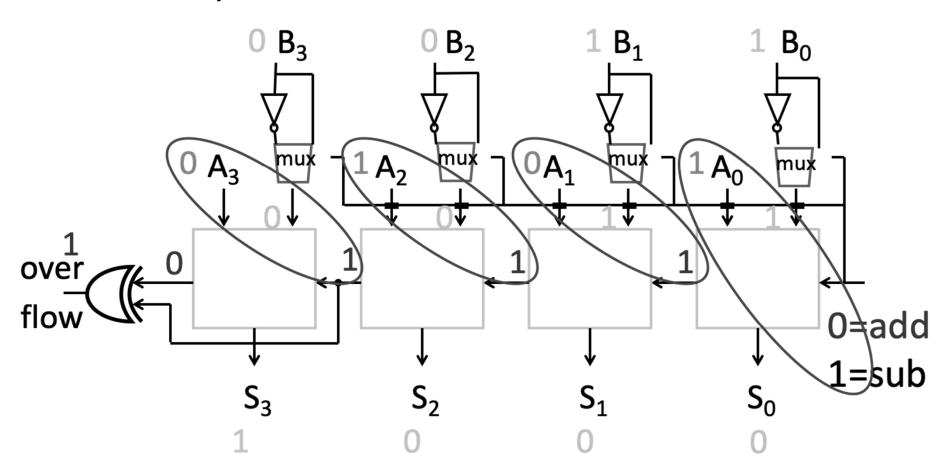Two's Complement Adder with overflow detection



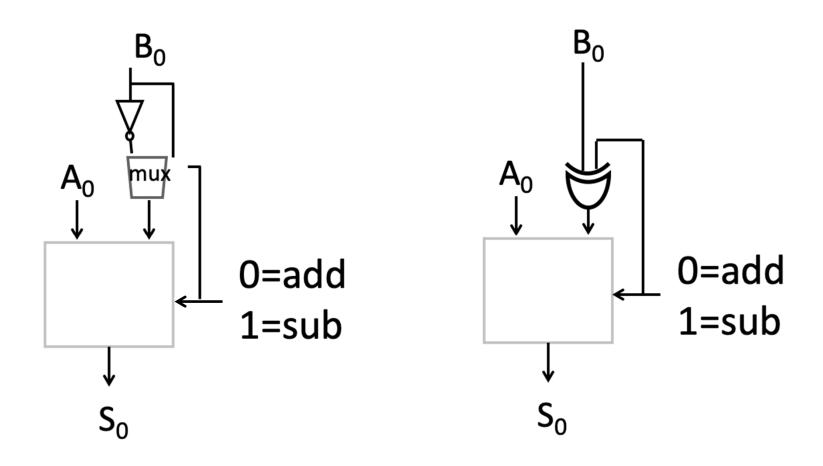Two's Complement Adder with overflow detection



Before: 2 inverters, 2 AND gates, 1 OR gate After: 1 XOR gate

Takeaways

Digital computers are implemented via logic circuits and thus represent *all* numbers in binary (base 2).

We write numbers as decimal or hex for convenience and need to be able to convert to binary and back (to understand what the computer is doing!).

Adding two 1-bit numbers generalizes to adding two numbers of any size since 1-bit full adders can be cascaded.

Using Two's complement number representation simplifies adder Logic circuit design (0 is unique, easy to negate). Subtraction is adding, where one operand is negated (two's complement; to negate: flip the bits and add 1).

Overflow if sign of operands A and B != sign of result S. Can detect overflow by testing C_{in} != C_{out} of the most significant bit (msb), which only occurs when previous statement is true.

Summary

We can now implement combinational logic circuits

- Design each block
 - Binary encoded numbers for compactness
- Decompose large circuit into manageable blocks
 - 1-bit Half Adders, 1-bit Full Adders,
 - *n*-bit Adders via cascaded 1-bit Full Adders, ...
- Can implement circuits using NAND or NOR gates
- Can implement gates using use PMOS and NMOStransistors
- And can add and subtract numbers (in two's compliment)!
- Next time, state and finite state machines...